

Reducing Output Ripple and Noise with the TPS84259

Jason Arrigo
DC Solutions

ABSTRACT

Analog circuits that need a negative output voltage, such as high-speed data converters, power amplifiers, and sensors are sensitive to noise. This application report examines different techniques to minimize the output ripple and noise with the TPS84259 negative output voltage power module. Other modules in the TPS84K family can also implement these noise-reducing techniques, such as adding additional output capacitance, pi-filtering, or a low noise low drop-out regulator.

Contents

1	Introduction	2
2	TPS84259 with Standard Filtering	2
3	TPS84259 with Additional Ceramic Output Capacitance	3
4	TPS84259 Filtering for Noise Sensitive Applications	4
5	Summary	6

List of Figures

1	Diagram of the TPS84259 with Standard Filtering	2
2	Output Ripple Waveform with Standard Filtering	2
3	Diagram of the TPS84259 with Additional Ceramic Capacitance	3
4	Output Ripple Waveform with Additional Ceramic Capacitance	3
5	PI-Filter Added to the TPS84259	4
6	Output Ripple Waveform with PI-Filter	4
7	PI-Filter Attenuation Versus Frequency	5
8	Diagram of the TPS84259 with Ultra-Low Noise LDO	5
9	Low-Noise on TPS84259 Output	5
10	Power-Supply Rejections Ratio Versus I_{OUT}	6

List of Tables

1	Output Filter Solutions.....	6
---	------------------------------	---

1 Introduction

Many industrial applications require both positive and negative voltages to power their analog circuitry. Many of these analog circuits such as data converters, audio amplifiers, sensors, and RF applications require low noise and ripple. The TPS84259 is a negative output voltage power module which can provide the negative output voltage for these circuits. Although the TPS84259 produces very little ripple over many operating conditions, some applications require better ripple performance than the TPS84259 provides. For those applications, additional filtering can reduce the noise and ripple to acceptable levels.

2 TPS84259 with Standard Filtering

Standard applications not requiring extremely low noise and ripple may be able to get by with the minimum required ceramic output capacitance. Figure 1 shows the TPS84259 with only $2 \times 47\text{-}\mu\text{F}$ ceramic capacitors to filter the output. Figure 2 shows the output voltage ripple waveform of the TPS84259 operating from 24-V input, -12-V output at 1 A with only $2 \times 47\text{-}\mu\text{F}$, X5R, ceramic output capacitors. The output ripple is approximately 21 mV under these operating conditions.

The output filtering for this minimum solution size only requires two ceramic capacitors, each in a 1206 package. These two capacitors take up 10.3 mm^2 of board space.

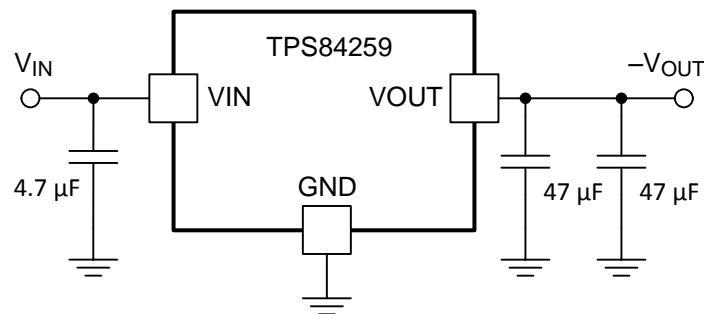


Figure 1. Diagram of the TPS84259 with Standard Filtering

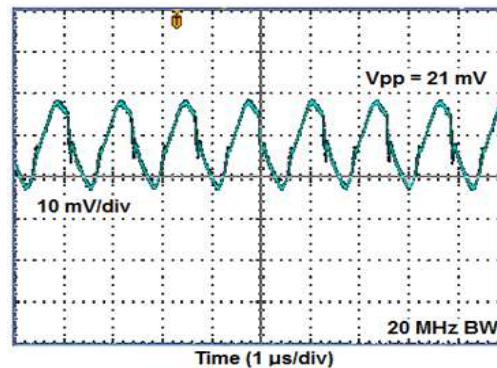


Figure 2. Output Ripple Waveform with Standard Filtering

3 TPS84259 with Additional Ceramic Output Capacitance

Applications that require slightly lower noise and ripple than what is achieved with the minimum required output capacitance benefit by adding additional ceramic output capacitance. Figure 3 shows the TPS84259 with 2 times the minimum-required ceramic output capacitance. The output ripple waveform for this circuit is shown in Figure 4. By doubling the amount of ceramic output capacitors, the output ripple voltage was reduced to approximately 12 mV.

By adding the extra output capacitors, the output filter solution size is increased. These four 1206 package capacitors take up 20.6 mm² of board space.

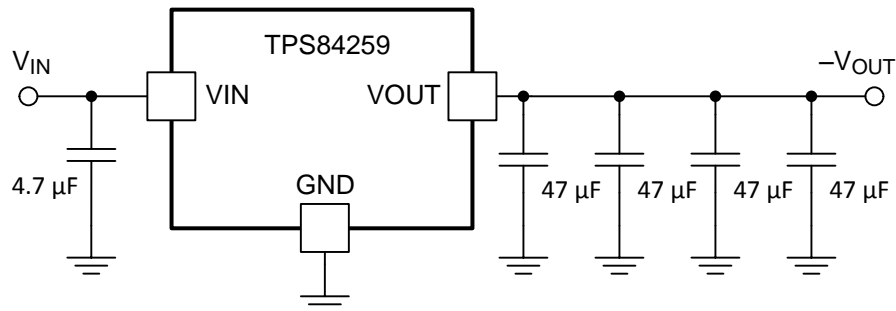


Figure 3. Diagram of the TPS84259 with Additional Ceramic Capacitance

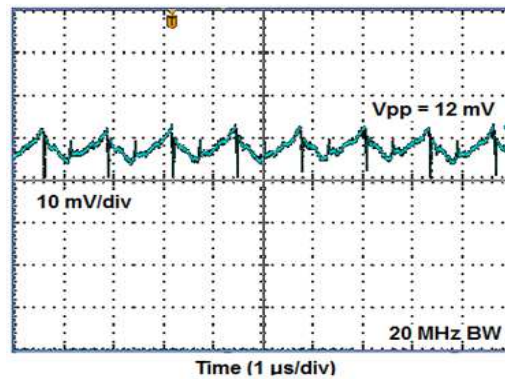


Figure 4. Output Ripple Waveform with Additional Ceramic Capacitance

4 TPS84259 Filtering for Noise Sensitive Applications

This section discusses filtering options for noise-sensitive applications.

4.1 PI Filter

Applications requiring extremely low noise and ripple (less than 5 mV) can add additional filtering along with ceramic output capacitance. In these applications a pi-filter can be added to the output. [Figure 5](#) shows the TPS84259 with 2 × 47- μF , X5R, ceramic output capacitors along with a pi-filter. The additional pi-filter is made up of a surface-mount ferrite bead and a 22- μF , X5R, 1206 package ceramic capacitor. The ferrite bead is 73-type material rated for up to 5 A (Fair-Rite part number 2773021447). This output filter is able to reduce the output ripple waveform to approximately 3 mV peak-to-peak, as shown in [Figure 6](#).

[Figure 7](#) shows the attenuation of the pi filter over frequency. The pi filter is most effective over the switching frequency range of the TPS84259.

The output filter size, including the two minimum required output capacitors, the SMD ferrite bead, and the 22- μF , X5R, ceramic capacitor, takes up 44.7 mm² of board space.

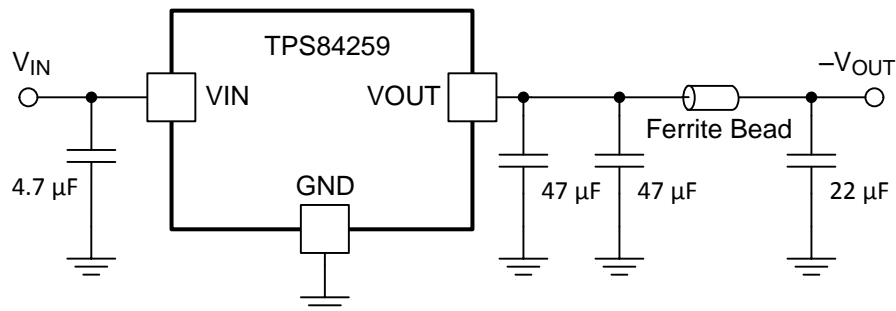


Figure 5. PI-Filter Added to the TPS84259

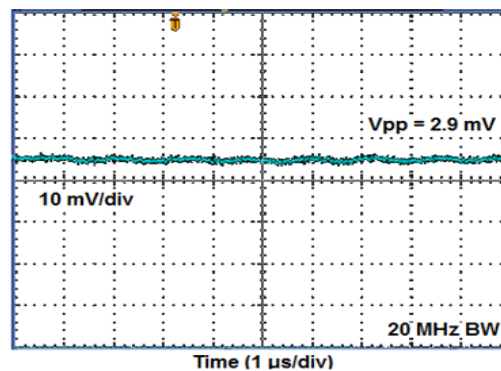


Figure 6. Output Ripple Waveform with PI-Filter

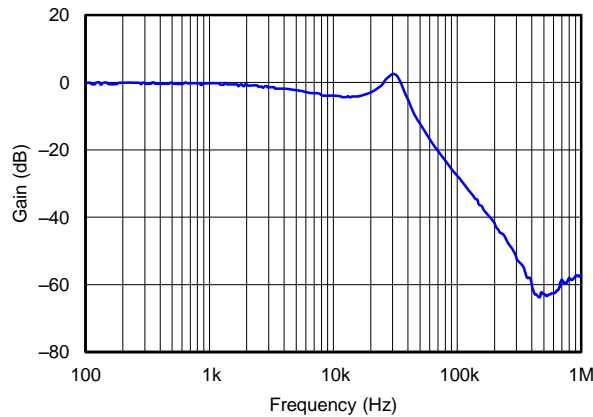


Figure 7. PI-Filter Attenuation Versus Frequency

4.2 Linear Regulator

Another option for achieving extremely low noise and ripple is adding an ultra-low-noise LDO to the output as shown in Figure 8. The output voltage of the TPS84259 must be adjusted up to allow for the voltage drop-out of the LDO. The LDO used in this application is the TPS7A3301. The TPS7A3301 is a negative-input-voltage, negative-output-voltage LDO capable of handling up to 1 A of current. Figure 9 shows the low noise measured on the output. The amount of output ripple measured was approximately 3 mV.

Figure 10 shows the PSRR of the TPS7A3301 over frequency for different output currents. Other graphs are found in the TPS7A3301 datasheet (SBVS169). This output filter solution size which includes the required output capacitors along with the LDO and its required components is 46.8 mm².

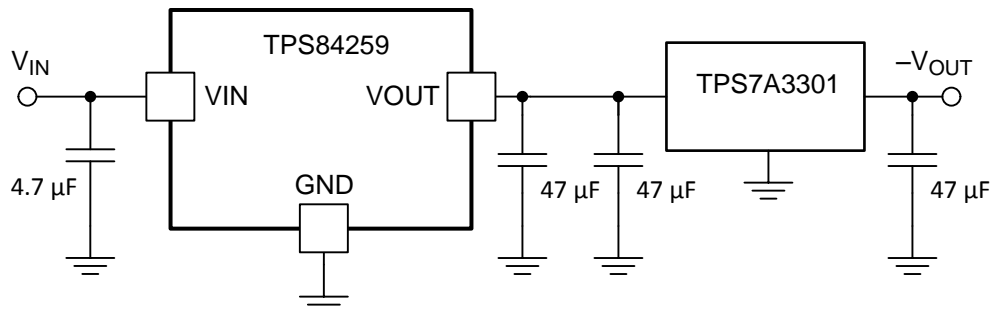


Figure 8. Diagram of the TPS84259 with Ultra-Low Noise LDO

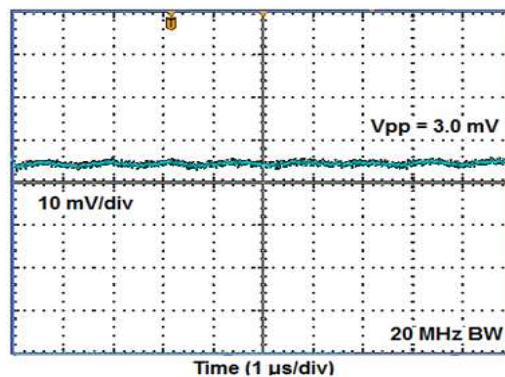


Figure 9. Low-Noise on TPS84259 Output

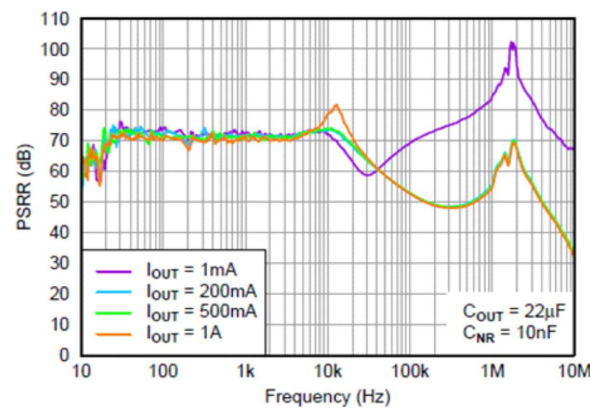


Figure 10. Power-Supply Rejections Ratio Versus I_{OUT}

5 Summary

In summary, the amount of output filtering required depends on the application. For many standard applications the minimum required output capacitance suffices. However, for low-noise applications additional output filtering may be required. In these cases adding extra capacitance, a pi-filter, or a linear regulator reduces the output ripple and noise to acceptable levels. [Table 1](#) summarizes the four output filter solutions discussed above. Included in the table are the resulting output ripple voltage and the board size required for the filter components.

Table 1. Output Filter Solutions

Output Filter	V _{pp} (TYP)	Board Side
2 × 47-µF ceramic capacitors	21 mV	10.3 mm ²
4 × 47-µF ceramic capacitors	12 mV	20.6 mm ²
2 × 47-µF ceramic caps + pi filter	2.9 mV	44.7 mm ²
2 × 47-µF ceramic caps + LDO	3.0 mV	46.8 mm ²

Each solution is fairly simple and takes up very little board space. Each application's noise requirement determines how much, if any, additional filtering is required.

The TPS84259, combined with the appropriate output filter, is the perfect device for providing a negative output voltage for low-noise applications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com