

LMX1501A

AN-885 Introduction to Single Chip Microwave PLL's



Literature Number: SNOA295

Introduction to Single Chip Microwave PLLs

National Semiconductor
 Application Note 885
 Cynthia L. Barker
 Wireless Communications
 March 1993



ABSTRACT

Synthesizer and Phase Locked Loop (PLL) figures of merit including phase noise, spurious output and lock time, at microwave frequencies, are examined. Measurement methods for these parameters and supporting software are discussed in detail. The requirements for the loop filter, the charge pump, the dual modulus prescaler and their effects on PLL performance are analyzed.


INTRODUCTION

Phase Locked Loops are used for many radio applications including frequency synthesizers, carrier recovery and clock recovery circuits, tunable filters, frequency multipliers, re-

ceiver demodulators and modulators. This application note will concentrate on the use of a PLL as a frequency synthesizer, as shown in *Figure 1*.

There are two main reasons for using a PLL as a frequency synthesizer. One is to translate the frequency accuracy of a high quality signal source to a tunable signal source. The second is to translate the noise characteristics of a high quality signal source to a lower quality signal source. The block diagram of a basic PLL is shown in *Figure 1*. The high quality signal source, in this case, is a crystal reference.

 A single chip PLL consists of the reference divider, the main divider (including a dual modulus prescaler), the phase detector and a charge pump.



TL/W/11815-1

FIGURE 1. Block Diagram of a Basic Phase Locked Loop

SYNTHESIZER AND PLL FIGURES OF MERIT

Phase noise is a measure of the spectral purity of the tone produced by the PLL. It is dependent on the noise characteristics of the crystal oscillator reference and the VCO as well as some noise contribution of the dividers. Phase noise is defined as the ratio of the single sideband power (within a 1 Hz bandwidth at some offset frequency) to the total carrier power. Phase noise is often measured in units of dBc/Hz.


Spurious output is a measure of the level of the reference spurs (sometimes referred to as reference sidebands) on the output tone. The reference spurs appear on the output tone at the center frequency \pm the reference frequency and at integer multiples of the reference frequency. For example, a PLL operating at 836 MHz with a reference frequency of 25 kHz will have reference spurs at 836.025 MHz, 835.075 MHz, 836.050 MHz, 835.050 MHz, etc.

Lock time or switching speed is a measure of the settling time of the PLL once a change in frequency has been initiated. The frequency step and the frequency accuracy to define "locked" must both be defined for this measurement to be useful.

PHASE NOISE MEASUREMENT METHODS

The phase noise characteristics of the PLL can be measured on a spectrum analyzer or using a phase noise test set. The spectrum analyzer test technique is described here. Phase noise is measured in units of dBc/Hz. This is done at several offsets from the output signal such as 1 kHz, 10 kHz and 100 kHz. The spectrum analyzer is tuned to the desired center frequency and the span is adjusted so the appropriate offset frequency can be viewed. The differ-

ence between the level of the carrier and the noise level minus 10 [log (resolution bandwidth)] is equal to the phase noise in dBc/Hz. The resolution bandwidth is read directly from the spectrum analyzer. The phase noise result in dBc/Hz is a negative number. Since phase noise is measured in dBc/Hz the measurement is always normalized to a 1 Hz bandwidth. The video averaging feature of the analyzer is used to better determine the noise level. An example of such a measurement, for the LMX1501A PLL using a reference frequency of 25 kHz, is shown in *Figure 2*. Refer to the LMX1501A data sheet for application circuits.

 

TL/W/11815-2

FIGURE 2. An 826 MHz Synthesizer Phase Noise Measurement @ 100 kHz = -116 dBc/Hz. Using the LMX1501A PLL.

Example Phase Noise Calculation
phase noise

$$\begin{aligned}
 (@100 \text{ kHz}) &= -76 \text{ dBc} - 10 \cdot \log(\text{res.BW}) \\
 &= -76 \text{ dBc} - 10 \cdot \log(10 \text{ kHz}) \\
 &= (-76 - 10 \cdot 4) \text{ dBc/Hz} \\
 &= -116 \text{ dBc/Hz}
 \end{aligned}$$

REFERENCE SIDEBAND MEASUREMENT METHODS

The reference sidebands can be seen on a spectrum analyzer and are measured in dBc. The analyzer is set to the desired center frequency and the span is set to allow the reference sidebands to be viewed. For example, to see the reference spurs for a 1.7 MHz reference frequency the span would be set to 10 MHz. The spurious output is the difference between the level of the PLL tone (at the center frequency) and the level of the reference spur (at the center frequency \pm the reference frequency). In *Figure 3*, the reference sidebands for a 1.7 MHz reference frequency are about 78 dB down from the PLL tone, or -78 dBc . Refer to the LMX2320 data sheet for application circuits.

 


FIGURE 3. An 1881 MHz Synthesizer with a Reference Frequency of 1.7 MHz and Sidebands @ 1.7 MHz = -78 dBc . Using the LMX2320 PLL.

SWITCHING SPEED MEASUREMENT METHODS

Switching speed is measured on an oscilloscope by probing the VCO tuning voltage. The transient response will be seen

 


FIGURE 4. Test Setup and Lock Time for 10 MHz Step = 1.77 ms using a LMX1501A with a Reference Frequency of 25 kHz.

directly. This method shows the damping characteristics of the loop but does not provide the accuracy of the frequency match.

Figure 4 illustrates an evaluation method using a mixer to determine the accuracy of the frequency match. The signal generator is phase locked to the crystal reference input to the PLL. This is accomplished by using a signal generator for the crystal reference and having the 10 MHz reference used as an external reference for the other signal generator. The output of the VCO is mixed with a signal (from a signal generator) at the desired frequency (using the mixer as a phase detector). When the frequencies are matched a DC voltage appears at the output of the mixer. When the frequencies are mismatched a beat note appears at the output of the mixer. Either of these signals is viewed on a scope. The peak to peak amplitude of the beat note represents a phase offset of $\pm 180^\circ$. The slope of the beat note represents a change in phase divided by time, which is equivalent to frequency. This frequency represents the frequency mismatch. As the slope of the line approaches zero the frequencies converge, and the loop locks. This method gives a frequency accuracy within 100 Hz.

An example of the above two types of switching speed measurements is shown in *Figure 4*. Channel 1 shows the VCO tuning voltage and channel 2 shows the output of the mixer IF port.

A third method uses a spectrum analyzer to view the transient response by setting the frequency span to 0 Hz. The display is effectively now frequency versus time. The video bandwidth should be set on maximum. The frequency offset will be equal to the resolution bandwidth setting at 10 dB down from the top on the vertical axis. This is due to the filter characteristics of the analyzer. To be fully accurate the external trigger of the analyzer should be triggered off the loading of the new frequency. This method is not recommended for measuring lock times under 10 milliseconds because on some spectrum analyzers the display response time of the analyzer is longer than a few milliseconds and erroneous data can result. A modulation domain analyzer can also be used to measure switching speed. It displays frequency versus time directly but it is not available in all labs.

SUPPORTING SOFTWARE

A software program of some kind is needed in order to program the PLL chip to test it. National Semiconductors LMX series of PLL chips are programmed via a three line MICROWIRE™ serial interface (clock, data, load enable). National Semiconductor Corporation provides a DOS program to allow the user to program the chip from the parallel port of a DOS personal computer. The user enters the frequency of operation, the reference frequency and the crystal frequency then presses one key to load in the appropriate divider values. The frequency can be tuned in steps of the reference frequency and a switching mode is available to test the lock time. The user enters the number of steps and the PLL will switch between the two frequencies. The user interface for the program is function key driven. Detailed operating instructions are provided with the software. For more information on the PLL software program contact:

(in Asia Pacific region)

Wireless Communications Product Applications
National Semiconductor Hong Kong Ltd.
Ocean Center 15/F, Straight Block
5 Canton Road
Tsimshatsui, Kowloon, Hong Kong
852-737-1800

(in Europe)

Wireless Communications Field Applications
National Semiconductor European Headquarters
Industriestrasse 10
D-8080 Furstenteldbruck
Germany
49-8141-103-557

(in Japan)


Innovative Product Application Engineering
Communication Business Center
National Semiconductor Japan Ltd.
Sansei-doh Shinjuku Bldg. 5F
4-15-3 Nishi Shinjuku
Shinjuku-ku, Tokyo, Japan
81-3-3299-7001

(in North or South America)

Wireless Communications Applications
National Semiconductor Corp.
1090 Kifer Rd.
Santa Clara, CA
(408) 721-4748

LOOP FILTER

The design of the loop filter involves a trade off between reference sidebands and switching speed. The loop filter must be designed for the correct balance between reference spurs and lock time that the system requires. Generally, the narrower the loop bandwidth the lower the reference spurs but the longer the lock time. The circuit in Figure 5 shows a type 2 third order passive loop filter configuration and its transfer function.

 


TL/W/11815-6

$$G_{LF}(s) = \frac{R \cdot C2 \cdot s + 1}{s(C2 + C1(R \cdot C2 \cdot s + 1))}$$


FIGURE 5. Passive Loop Filter Circuit and Loop Filter Transfer Function.

A type 2 loop has two integrators within the loop, a VCO and an integrator/filter. The order of the loop is determined by number of poles of the transfer function. Using the phase detector and VCO constants (K_ϕ and K_V) and the loop filter transfer function (G_{LF}) the open loop Bode plot can be calculated. K_ϕ and K_V are available from the PLL IC and VCO manufacturers. The control circuit, the open loop transfer function and the open loop Bode plot are shown in Figure 6. The loop bandwidth is shown on the Bode plot as (ω_p) the point of unity gain.

 

TL/W/11815-8

 (G = Forward transfer function, H = Feed back)
Open Loop Transfer Equation
$$GH(s) = \frac{K_\phi G_{LF}(s) K_V}{Ns}$$



TL/W/11815-9


FIGURE 6. Control Circuit, Open Loop Equation and Bode Plot

CHARGE PUMP AND PHASE DETECTOR


A current charge pump and a phase frequency detector are implemented in National Semiconductor's LMX series of PLL chips. To increase the VCO frequency the charge pump outputs a pump up (source) current. To decrease the VCO frequency the charge pump outputs a pump down (sink) current. This current pulse charges the voltage of the capacitor C1. The charge pump is capable of supplying a controlled charge to the loop filter over a wide range of voltages, as shown in Figure 7.

The phase detector and charge pump are difficult to characterize separately. The figures of merit for the combination include linearity, sensitivity and deadband range. The linearity of the charge produced by the charge pump with respect to the detected phase error is critical to providing low spurious and low phase noise. The sensitivity (K_{ϕ}) is measured in mA/radian and depends on the charge pump current capability. Current mode charge pumps commonly have a dead zone where the gain changes dramatically for a very small phase error. The divider outputs f_r and f_p are a series of pulses whose relative timing reflect the phase or frequency error, as shown in Figure 8. At some point the pulses are too close together for the phase frequency detector to dis-

 tinguish them. This is the deadband or dead zone, as shown in Figure 9. The LMX series of PLLs use a proprietary feedback method to minimize deadband.




 TL/W/11815-7
FIGURE 7. Charge Pump Current vs Voltage for the LMX Series of PLL Chips



TL/W/11815-11
FIGURE 8. Phase/Frequency Error Pulses

Phase Detector/Charge Pump Linearity

 

TL/W/11815-10

FIGURE 9. Charge Pump Current vs. Phase Error, showing Deadband.

DUAL MODULUS PRESCALER

Dual modulus prescalers allow operation of the divider chain at high frequencies while most of the divider operates at a lower frequency. However, this capability sets limits on the range of the divider. The divider is made up of an A counter and a B counter. The A counter is the swallow counter and the B counter is the programmable divider. The condition for a legal divide ratio is that $B \geq A$.

The necessary divide number (N) is calculated by dividing the desired frequency by the reference frequency.

$$f_{out} = N f_{ref} = \frac{N}{R} f_{crystal}$$

$$R = \text{reference divide ratio} = \frac{\text{crystal frequency}}{f_{ref}}$$

The output frequency must be an integer multiple of the reference frequency. Once the divide ratio is calculated a check can be made to determine whether it is above the minimum continuous divide ratio. The minimum continuous divide ratio is equal to $P(P-1)$ where P is the prescaler divider. For example the minimum divide ratio for a 64/65 prescaler is $64(64-1)$ or 4032. If the divide ratio required (N) is below the minimum continuous divide ratio it may be a legal number but it must be verified that $B \geq A$. The values for A and B can be calculated from the following equations:

$$B = N \text{ div } P$$

$$A = N \text{ mod } P$$

A divide ratio that is above the minimum continuous divide ratio or satisfies the condition $B \geq A$ is a legal divide number. The PLL will not operate if it is programmed with an illegal divide number. For example, in choosing a prescaler for a DECT (Digital European Cordless Telephony) system the required divide ratios for the transmit side would be 1089 to 1098. The frequencies of operation for DECT are

1881.792MHz to 1897.344 MHz with a channel spacing of 1.728 MHz. The reference frequency used is 1.728 MHz.

$$\frac{1881.792}{1.728} = 1089 \quad \text{and} \quad \frac{1897.344}{1.728} = 1098$$

The minimum continuous divide ratio for a 64/65 prescaler is $64(64-1)$ or 4032. The minimum continuous divide ratio for a 128/129 prescaler is $128(128-1)$ or 16,256. For DECT the divide ratios required do not exceed the minimum continuous divide ratio for a 64/65 or 128/129 prescaler. Therefore, it must be verified that the condition of $B \geq A$ holds true. This is determined as follows:

TABLE I. Example Dual Modulus Prescaler Calculation

N	64/65		128/129	
	B	A	B	A
1089	17	1	8	65
1090	17	2	8	66
-	-	-	-	-
-	-	-	-	-
-	-	-	-	-
1097	17	9	8	73
1098	17	10	8	74

For the 64/65 prescaler, Table 1 shows $B \geq A$ therefore it can be used. The 128/129 prescaler cannot be used since $A > B$. The above calculation demonstrates that a 64/65 prescaler can be used in the DECT system for the transmit PLL.

CONCLUSION

The performance of a PLL as a frequency synthesizer is measured in terms of phase noise, spurious output and lock time. The techniques for measuring these parameters have been discussed. The loop filter, charge pump/phase detector and dual modulus prescaler and their impact on PLL performance have been analyzed. Example performance metrics were demonstrated for National Semiconductor's LMX series of PLL chips. These ICs provide the capability to produce a low power, low noise, low spurious and fast switching frequency synthesizer. With a properly designed loop filter excellent performance can be achieved. The LMX series of PLL chips provide the building block around which a high performance frequency synthesizer can be designed.

References

- W.F. Egan: *Frequency Synthesizers By Phase Lock*, John Wiley and Sons, 1981
- F.M. Gardner: *Phaselock Techniques*, Wiley, 1989
- F.M. Gardner: "Charge-Pump Phase-Lock Loops", IEEE Transactions on Communications, Com-28, No. 11, November 1980
- U.L. Rohde: *Digital PLL Frequency Synthesizers: Theory and Design*, Prentice Hall, 1983

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform, when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.



National Semiconductor Corporation
 2900 Semiconductor Drive
 P.O. Box 58090
 Santa Clara, CA 95052-8090
 Tel: 1(800) 272-9959
 TWX: (910) 339-8240

National Semiconductor GmbH
 Livny-Gargan-Str. 10
 D-82256 Fürstenfeldbruck
 Germany
 Tel: (81-41) 35-0
 Telex: 527849
 Fax: (81-41) 35-1

National Semiconductor Japan Ltd.
 Sumitomo Chemical
 Engineering Center
 Bldg. 7F
 1-7-1, Nakase, Mihama-Ku
 Chiba-City,
 Ciba Prefecture 261
 Tel: (043) 299-2300
 Fax: (043) 299-2500

National Semiconductor Hong Kong Ltd.
 13th Floor, Straight Block,
 Ocean Centre, 5 Canton Rd.
 Tsimshatsui, Kowloon
 Hong Kong
 Tel: (852) 2737-1600
 Fax: (852) 2736-9960

National Semicondutores Do Brazil Ltda.
 Rue Deputado Lacorda Franco
 120-3A
 Sao Paulo-SP
 Brazil 05418-000
 Tel: (55-11) 212-5066
 Telex: 391-1131931 NSBR BR
 Fax: (55-11) 212-1181

National Semiconductor (Australia) Pty, Ltd.
 Building 16
 Business Park Drive
 Monash Business Park
 Nottingham, Melbourne
 Victoria 3168 Australia
 Tel: (3) 558-9999
 Fax: (3) 558-9998

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated