

# Power Supply Design Seminar

Introduction to the trans-inductor voltage regulator (TLVR)

---

Authors

Matthew Schurmann and Mohamed Ahmed





# Agenda/overview


- Background and motivation
- Transinductor voltage regulator (TLVR) topology introduction
- Practical considerations
- Conclusion
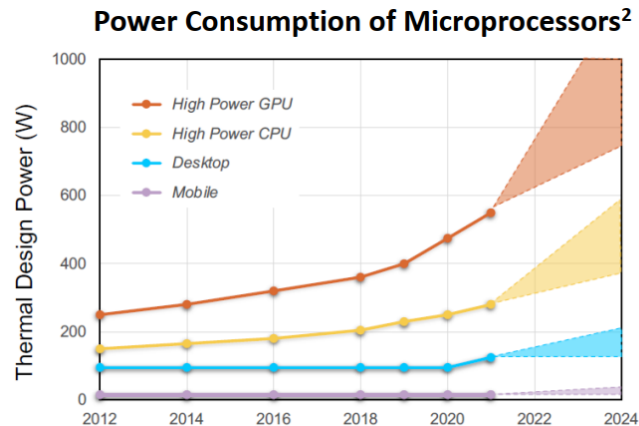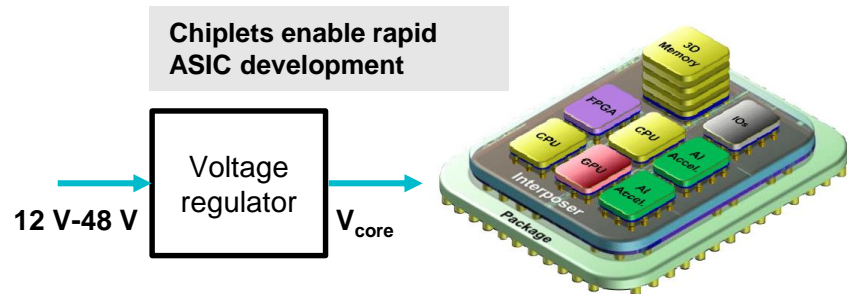
# Voltage regulator design challenges


- **Silicon technology continues to shrink** (but this is slowing)  
3-nm digital → lower
- Application-specific integrated circuit (ASIC) **operating voltages remain** 0.7 V to 1.0 V (up to 1.8 V)
- High-core-count designs and chiplet revolution driving **rapid increase in operating currents**  
>1,000-A designs
- Extreme load transient requirements  
1,000 A/ $\mu$ s,  $\pm 3\%$



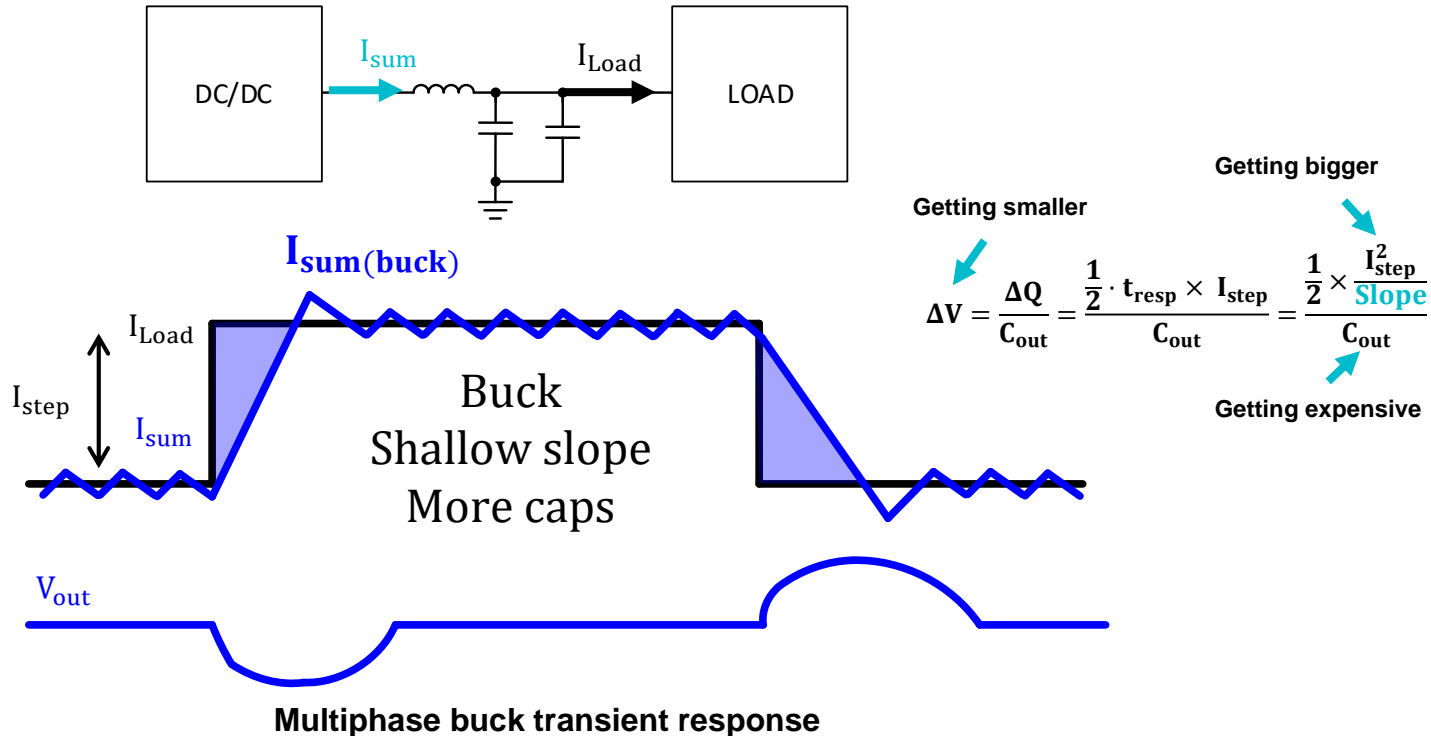
# Motivation for TLVR: Improving transient response


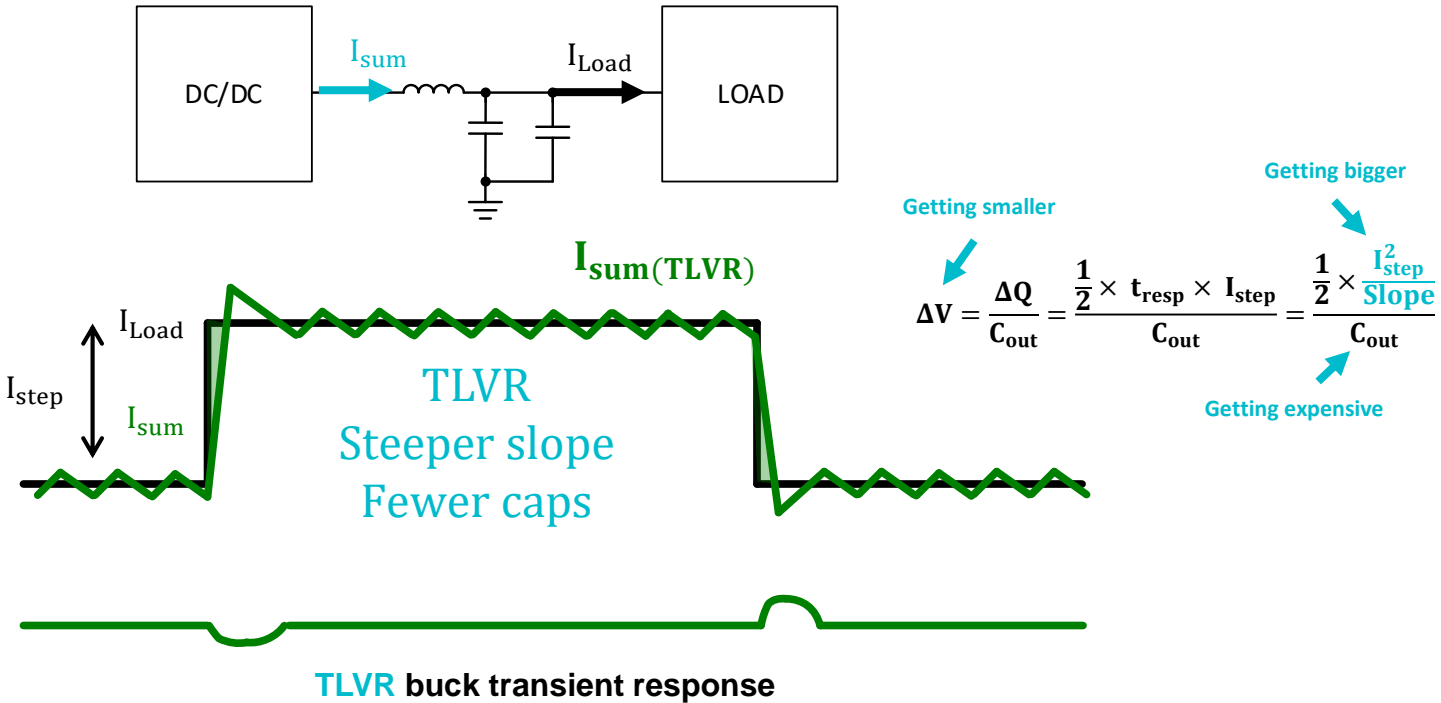
# Motivation for TLVR: Improving transient response





# Buck converter vs. TLVR topology

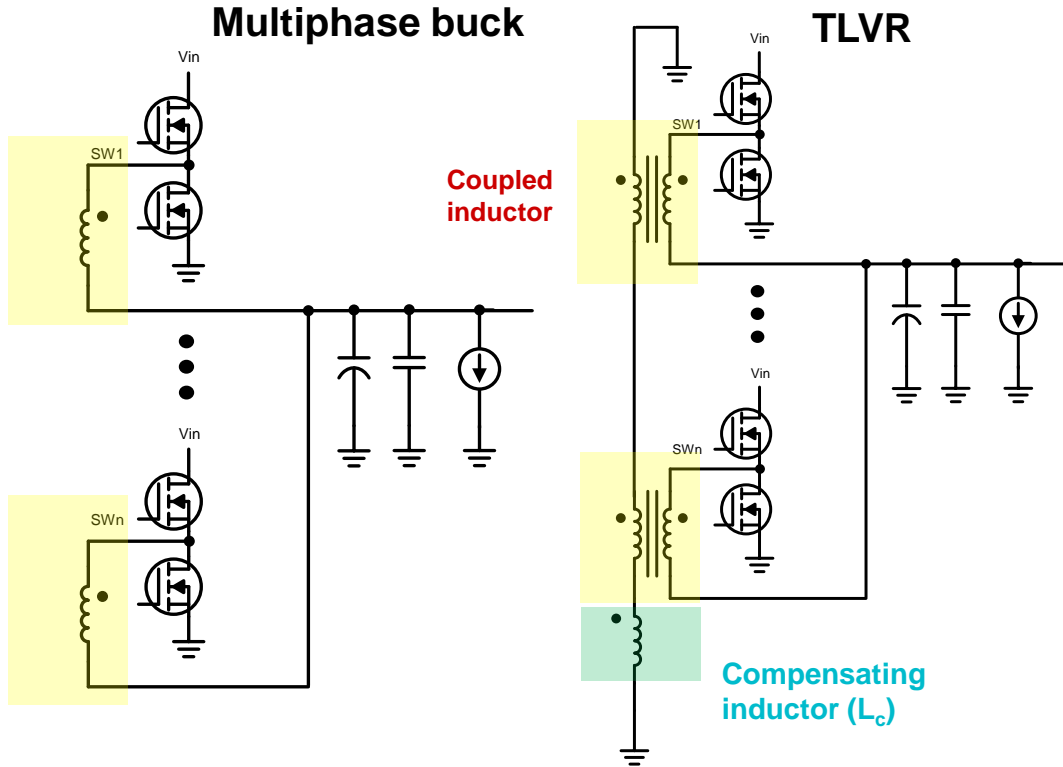

- **Buck-derived** topology optimized for fast transient response
- TLVR is a new twist on the coupled-inductor buck converter
- **When it makes sense:**
  - High phase count (>six phases)
  - High di/dt load transient
  - Moderate voltage ripple


# Traditional coupled inductor
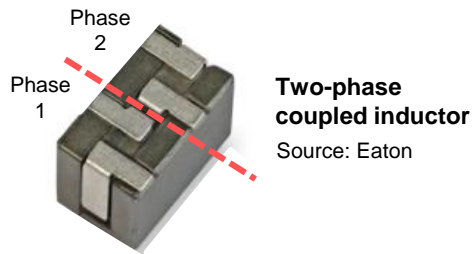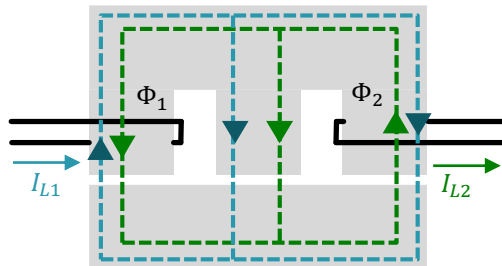
## Traditional coupled inductor (two phase)



- Multiple windings share a single core
- Typical coupling coefficient:  $\approx 0.5$  to  $0.7$
- Higher power density
- Customized design for phase count/layouts

## Difficult to extend to higher phases

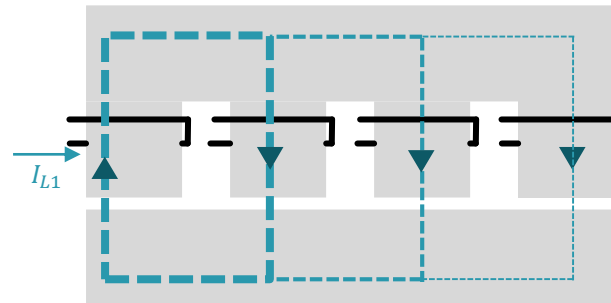


- **Challenge:** Symmetry is required for equal coupling among phases
- **Challenge:** Complex geometry required to maintain symmetry at higher phase counts

Coupling allows high steady state inductance (low ripple) and low transient inductance (fast transient)



# Indirect-coupled inductor

## Indirect-coupled inductor (two phase)

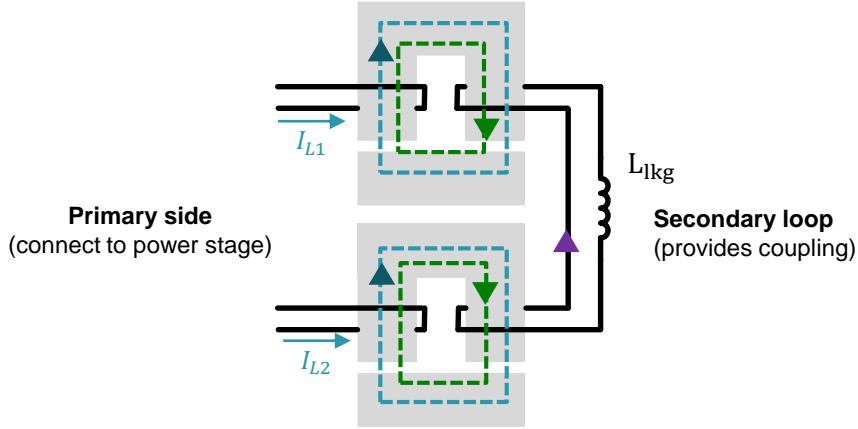

- Phases are coupled symmetrically without a sharing core
- **Simple core geometry, scalable solution**
- **Challenging to control coupling**
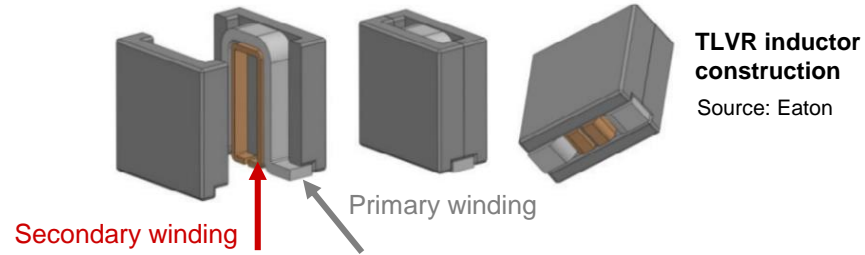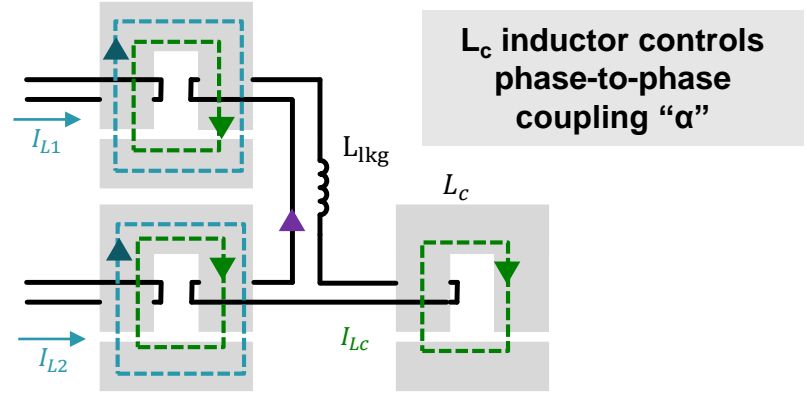
## TLVR: Indirect-coupling and compensating inductor ( $L_c$ )






# TLVR topology overview

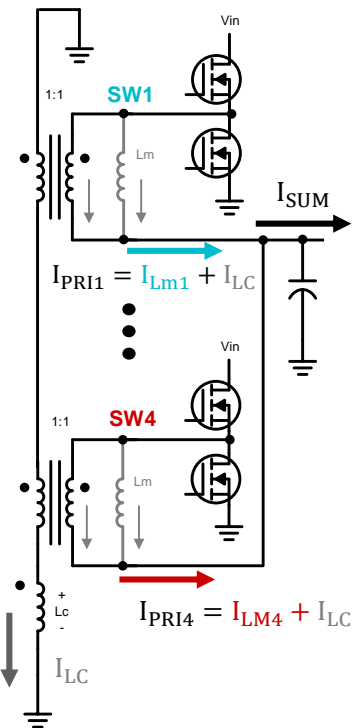
# TLVR operating principle: Steady state

TLVR steady-state operation (four-phase example, no overlap)





## Phase current description ( $I_{PRI4}$ )

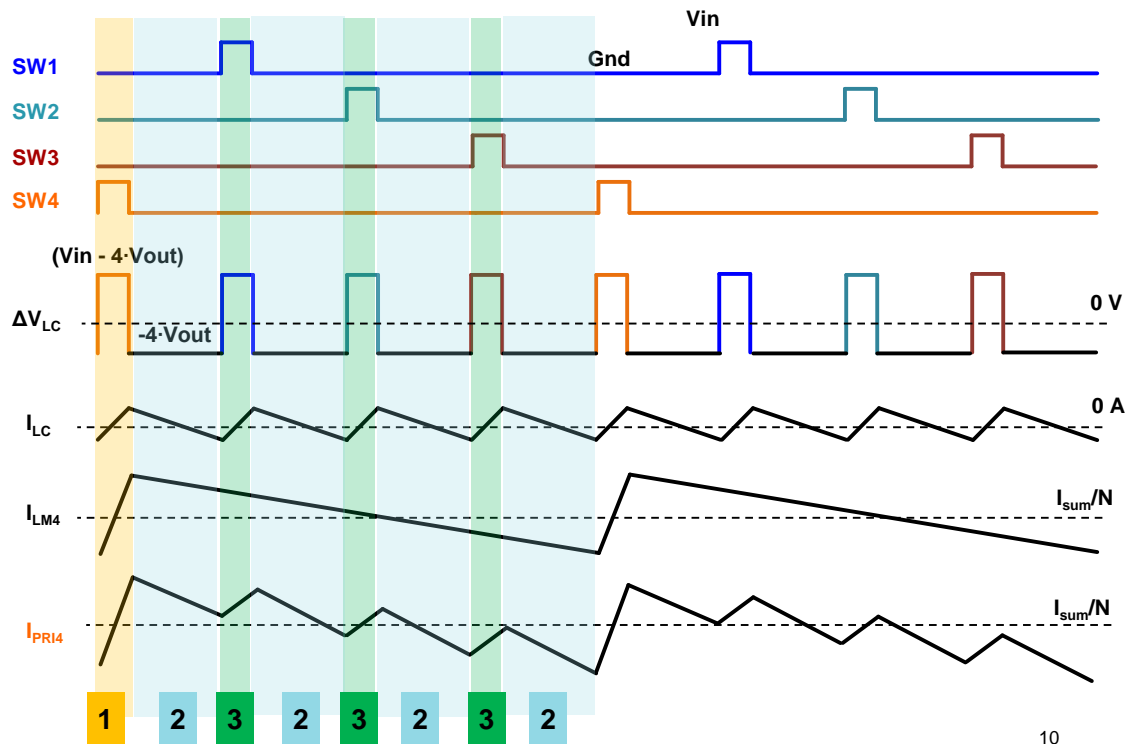1. This phase (SW4) is on; all others are off  
 $I_{LM4}$  increases  
 $I_{LC}$  increases
2. All phases are off  
 $I_{LM4}$  decreases  
 $I_{LC}$  decreases
3. This phase (SW4) is off, but others are on  
 $I_{LM}$  decreases  
 $I_{LC}$  increases


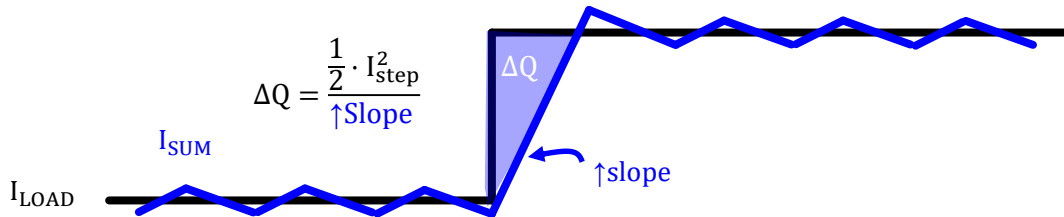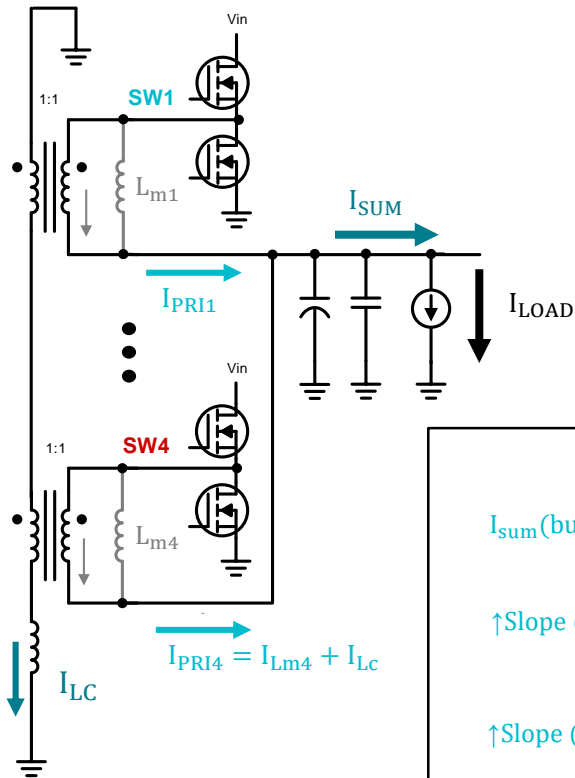
# TLVR operating principle: Transient step-up



Controller **turns on multiple phases** in response.

$N_{ON}$  phases are on,  $N_{OFF}$  phases are off

## Multiphase buck

$$I_{sum}(buck) = I_{L1} + I_{L2} + \dots$$

$$\uparrow Slope (buck) = \frac{\Delta V_{L1}}{L} + \frac{\Delta V_{L2}}{L} + \dots$$

$$\uparrow Slope (buck) \approx N_{on} \left( \frac{V_{in} - V_{out}}{L} \right) - N_{off} \left( \frac{V_{out}}{L} \right)$$

## TLVR



$$I_{sum}(TLVR) = I_{pri1} + I_{pri2} + \dots$$

$$I_{sum}(TLVR) = (I_{Lm1} + I_{Lc}) + (I_{Lm2} + I_{Lc}) + \dots$$

$$\uparrow Slope (TLVR) = \left( \frac{\Delta V_{L1}}{L_m} + \frac{\Delta V_{Lc}}{L_c} \right) + \left( \frac{\Delta V_{L2}}{L_m} + \frac{\Delta V_{Lc}}{L_c} \right) + \dots$$

$$\uparrow Slope (TLVR) \approx \uparrow Slope(buck) + N_{total} \left[ \frac{N_{on} \cdot V_{in} - N_{total} \times V_{out}}{L_c} \right]$$
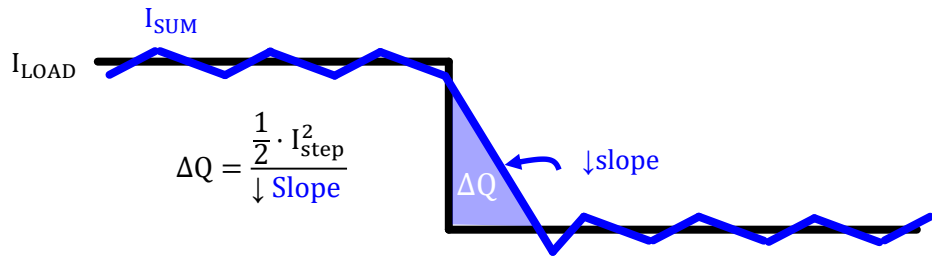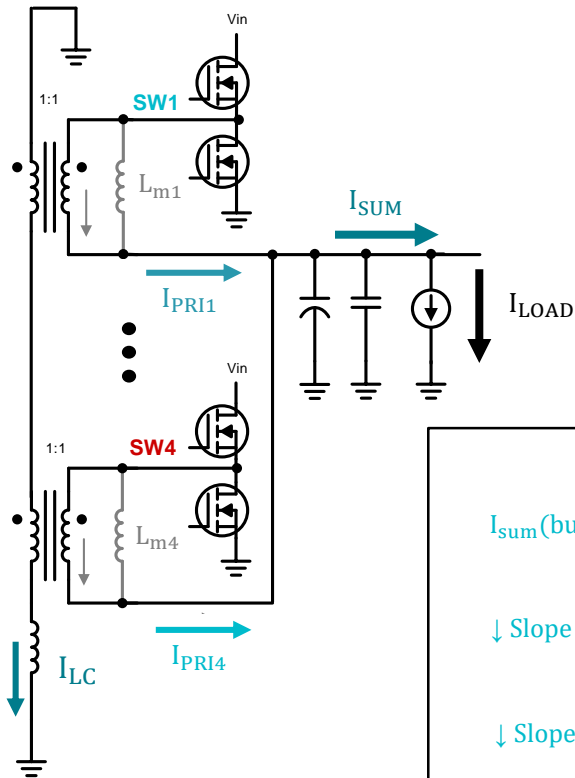
# TLVR operating principle: Transient step-down



Controller **turns off all phases** in response

$N_{TOTAL}$  phases are off

## Multiphase buck

$$I_{sum}(buck) = I_{L1} + I_{L2} + \dots$$

$$\downarrow \text{Slope (buck)} = \frac{\Delta V_{L1}}{L} + \frac{\Delta V_{L2}}{L} + \dots$$

$$\downarrow \text{Slope(buck)} \approx -N_{total} \left( \frac{V_{out}}{L} \right)$$

## TLVR

$$I_{sum}(TLVR) = I_{pri1} + I_{pri2} + \dots$$


$$I_{sum}(TLVR) = (I_{Lm1} + I_{Lc}) + (I_{Lm2} + I_{Lc}) + \dots$$

$$\downarrow \text{Slope (TLVR)} = \left( \frac{\Delta V_{L1}}{L_m} + \frac{\Delta V_{Lc}}{L_c} \right) + \left( \frac{\Delta V_{L2}}{L_m} + \frac{\Delta V_{Lc}}{L_c} \right) + \dots$$


$$\downarrow \text{Slope (TLVR)} \approx \downarrow \text{Slope(buck)} - N_{total} \left[ \frac{N_{total} \times V_{OUT}}{L_c} \right]$$

# Side-by-side comparison: Load step-up

## Multiphase buck

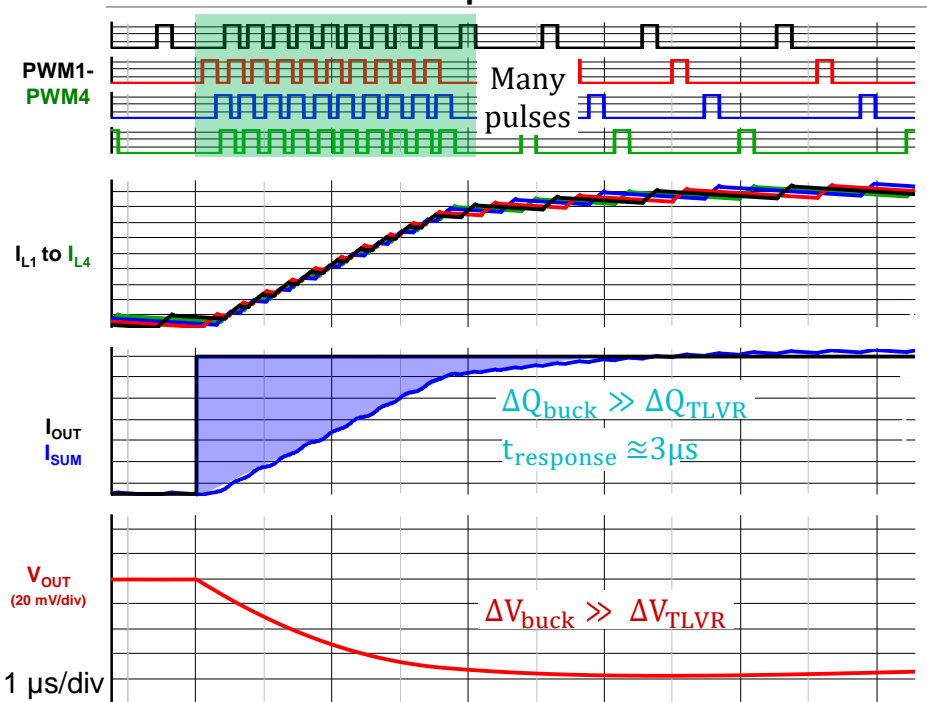


## TLVR

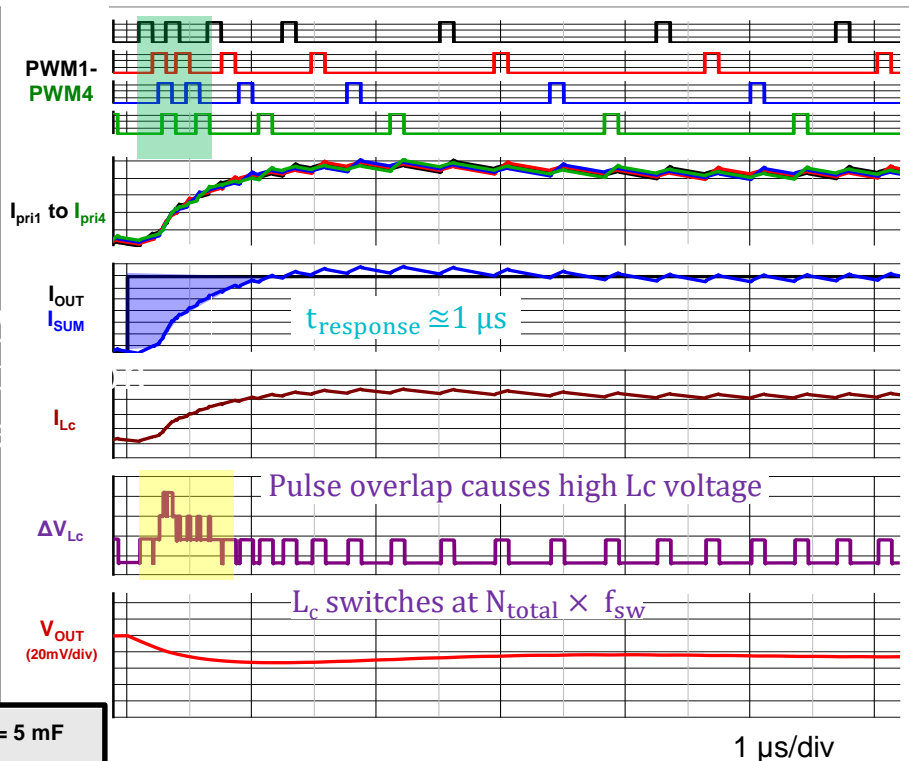


- $V_{IN} = 12 \text{ V}$
- $V_{OUT} = 0.8 \text{ V}$
- $F_{sw} = 600 \text{ kHz}$ , four phases
- $I_{OUT} = 25 \text{ A}$ -325 A, instantaneous
- Buck:  $L_{buck} = 150 \text{ nH}$
- TLVR:  $L_m = 150 \text{ nH}$ ,  $L_c = 180 \text{ nH}$
- $C_{OUT} = 5 \text{ mF}$
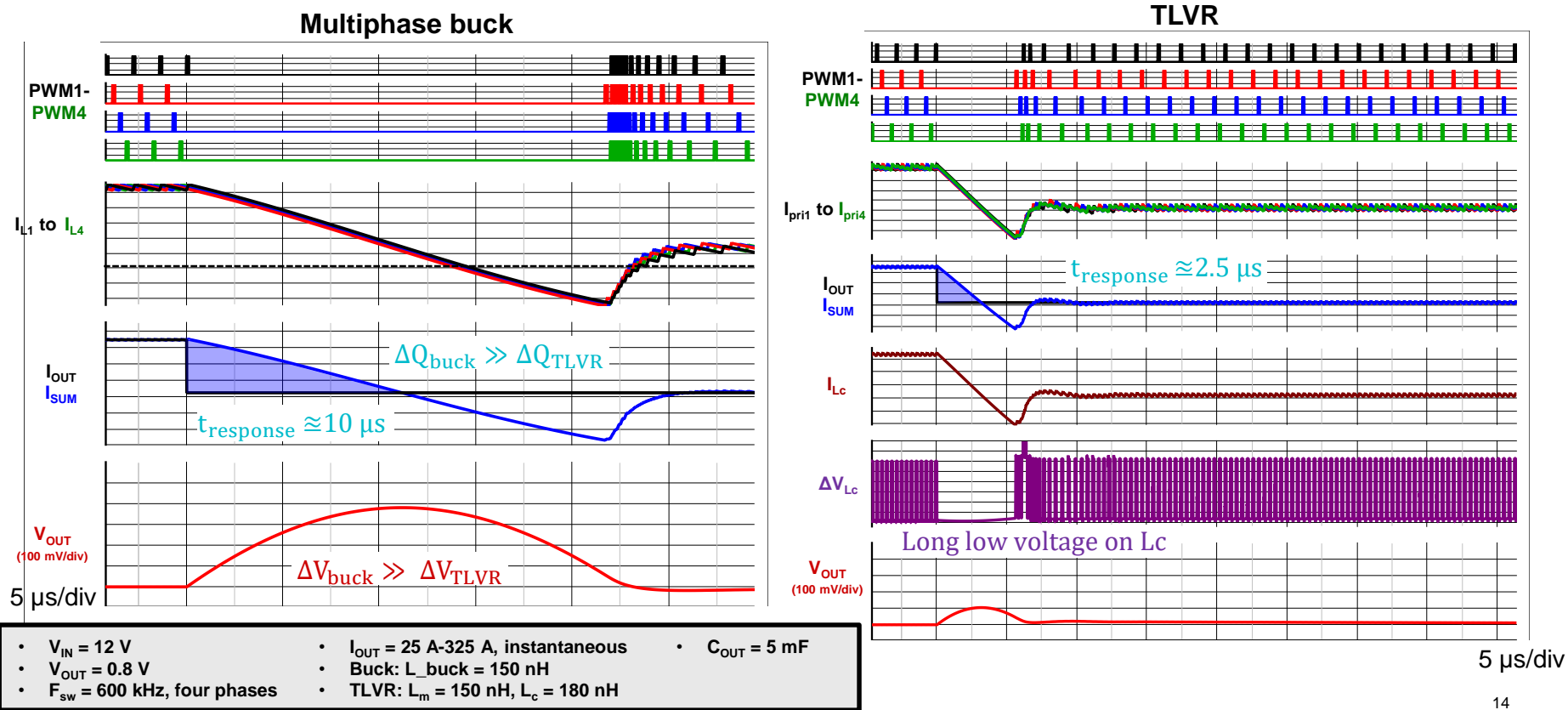
# Side-by-side comparison: Load step-down



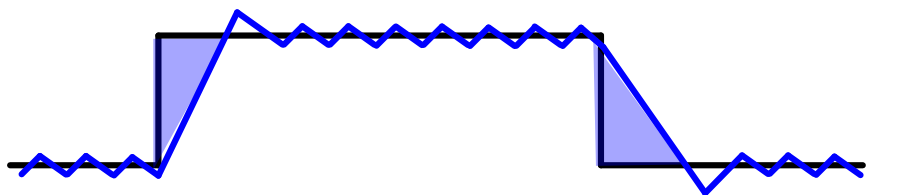
# DC load line further reduces output capacitance


DC load-line (DCLL) behavior is **identical** between buck and TLVR designs



$R_{LL} = 0 \text{ m}\Omega$

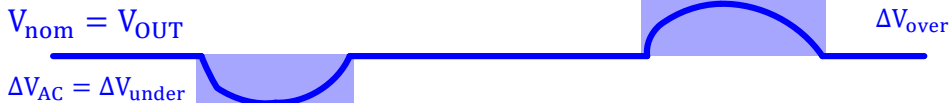

$R_{LL} \neq 0 \text{ m}\Omega$

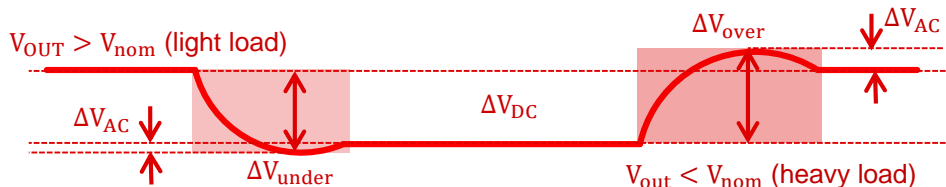

$V_{OUT} > V_{nom}$  (light load)

$V_{out} < V_{nom}$  (heavy load)

$$R_{DCLL} = \frac{\Delta V_{DC}}{\Delta I_{step}}$$

Capacitor savings

$$C_{out(\min, \text{step up})} = \frac{\Delta Q_{\text{under}}}{\Delta V_{\text{under}}} = \frac{\Delta Q_{\text{under}}}{\Delta V_{ac} + R_{LL} \times I_{\text{step}}}$$


$$C_{out(\min, \text{step down})} = \frac{\Delta Q_{\text{over}}}{\Delta V_{\text{over}}} = \frac{\Delta Q_{\text{over}}}{\Delta V_{ac} + R_{LL} \times I_{\text{step}}}$$

Reduced output power


$$P_{out} = I_{out} \times (V_{out} - R_{LL} \times I_{out})$$

# $L_c$ as an AC inductor – $I_{Lc}$ during a transient

Low-frequency transient (<1 kHz)

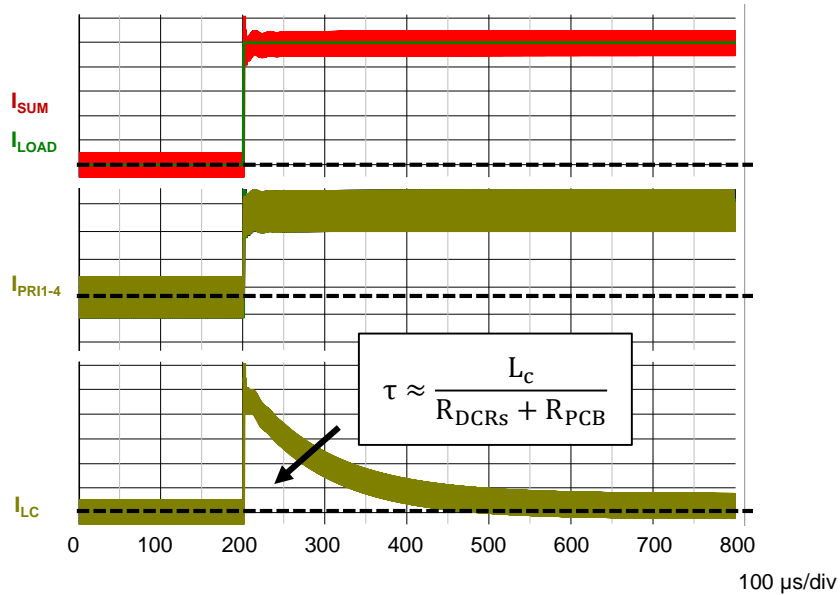


High-frequency transient (65 kHz)

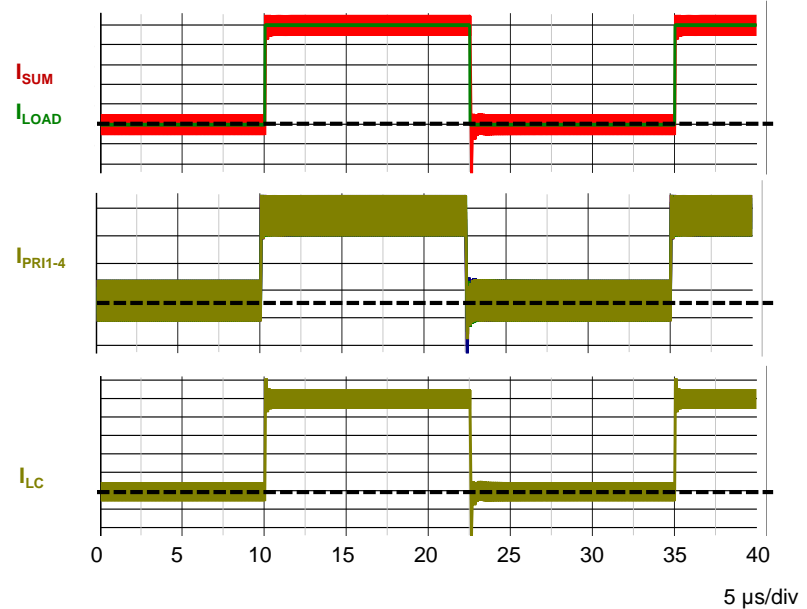



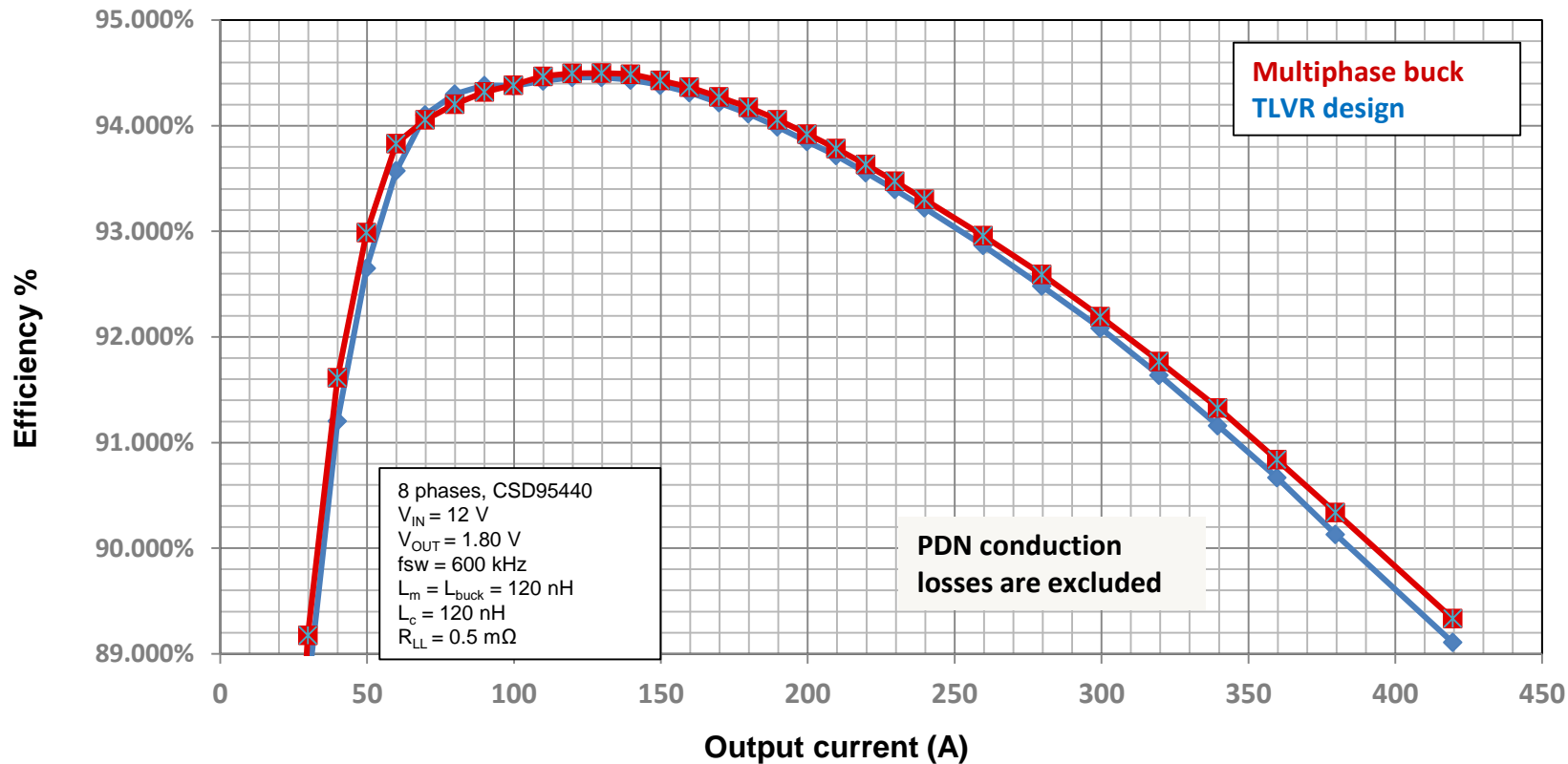
# VR vs. TLVR efficiency comparison ( $L_{BUCK} = L_M = L_C$ )



# Dynamic phase shedding

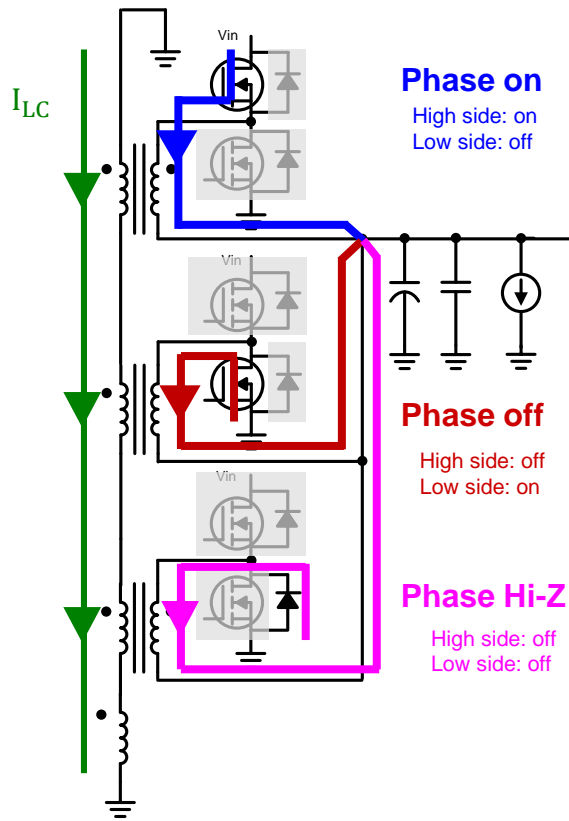


$$\Delta V_{LC} = N_{on} \times (V_{IN} - V_{OUT}) + N_{off} \times (-V_{OUT}) + N_{HiZ} \times (V_{diode})$$

0 when DPS is off

$$P_{cond,HiZ} \approx I_{rms(L_c)} \times V_{diode}$$

$$P_{cond,HiZ} \ll P_{switching}$$


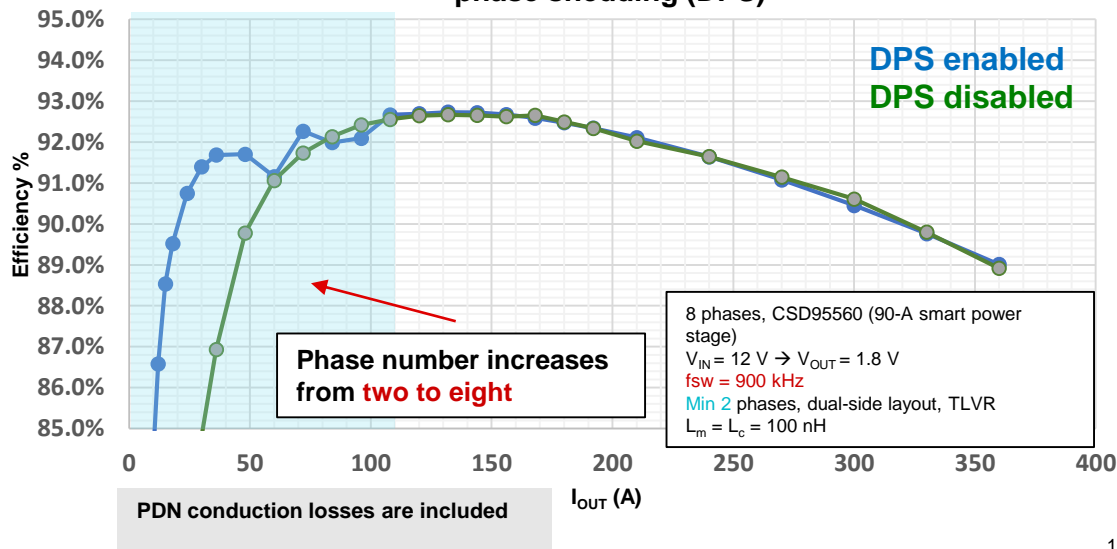
Efficiency comparison (including power delivery network [PDN]) vs. dynamic phase shedding (DPS)



# Example side-by-side design

Parameter	TLVR	Multiphase buck
Controller/SPS	TPS53689, CSD95440	
$V_{IN}$	12 V	
$V_{OUT}$	1.8 V	
Number of phases	8 phases	
Switching frequency	900 kHz	
Load step	60 A-430 A, 1,000 A/ $\mu$ s, 1 kHz-1 MHz	
Load line	0.5 m $\Omega$	
$L_m/L_{buck}$	150 nH	70 nH
$L_C$	100 nH	–
$C_{bulk}$ (polymer)	0 $\times$ 470 $\mu$ F	5 $\times$ 470 $\mu$ F
Multilayer ceramic capacitors	80 $\times$ 22 $\mu$ F 0402	80 $\times$ 22 $\mu$ F 0402
	56 $\times$ 47 $\mu$ F 0603	45 $\times$ 47 $\mu$ F 0805
	0 $\times$ 100 $\mu$ F 0805	15 $\times$ 100 $\mu$ F 0805
	8 $\times$ 0.1 $\mu$ F 0402	8 $\times$ 0.1 $\mu$ F 0402
Total $C_{out}$	<b>4.4 mF</b>	<b>7.7 mF</b>

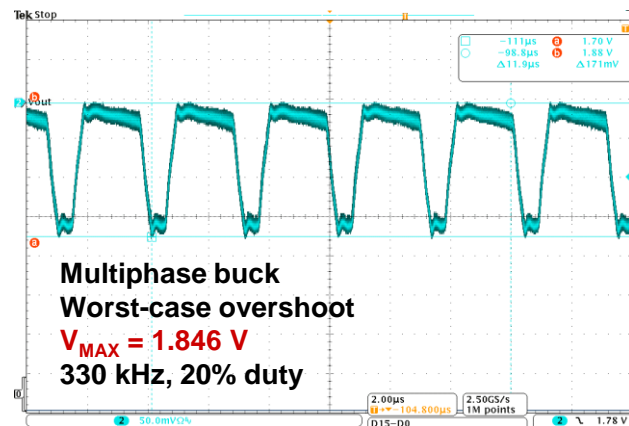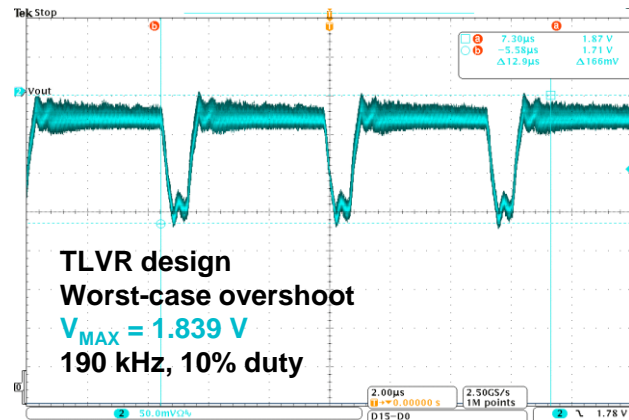More transient margin with 45% reduction  
in output capacitance required



# Practical considerations

# $L_c$ inductor selection

- Typically select  $L_c$  between  $L_m$  and  $1.25 \times L_m$

- Minimal root-mean-square current (RMS) required

$$I_{\text{rms}(L_c)} \approx \frac{\Delta I_{Lc}}{\sqrt{12}}$$

- High saturation current required

$$I_{\text{sat}} \gg t_{\text{resp}} \times \left[ \frac{N_{\text{on(step)}} \times V_{\text{IN}} - N_{\text{total}} \times V_{\text{OUT}}}{L_c} \right]$$

- Voltage across  $L_c$  can be  $\gg V_{\text{IN}}$


$$V_{Lc(\text{max})} = N_{\text{on(step)}} \times V_{\text{IN}} - N_{\text{total}} \times V_{\text{OUT}}$$

## Example $L_c$ selection

Parameter	Value
$V_{\text{IN}}$	12 V
$V_{\text{OUT}}$	0.8 V
$F_{\text{sw}}$	600 kHz
$N_{\text{total}}$	8 phases
$L_m$	150 nH
$L_c$	180 nH
Load transient	50-500 A, 1,000 A/ $\mu$ s
$\Delta I_{Lc}$	5.0 A
$F_{Lc}$	4.8 MHz
$I_{\text{RMS}(Lc)}$	2.8 A
Margin for $I_{\text{SAT}}$	25%
$I_{\text{SAT}(\text{min})}$	75 A
$\Delta V_{Lc(\text{max})}$	30 V ( $N_{\text{OVERLAP}} = 3$ )

# Output-ripple cancellation

Output-voltage ripple (simple model)

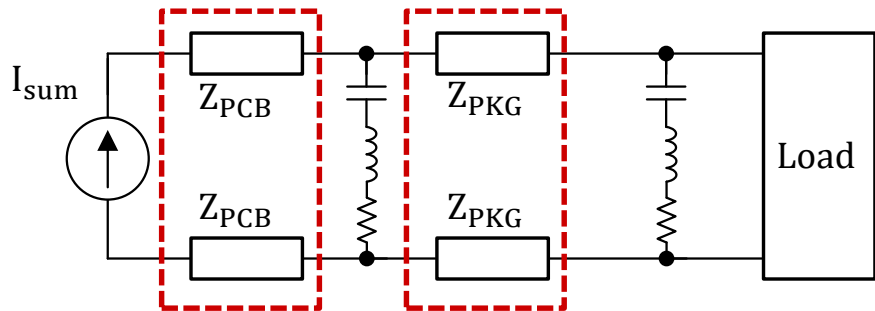


Same  $L_c$  current gets added at every phase-shift offset

$$I_{\text{sum}} = (I_{Lm1} + I_{Lc}) + (I_{Lm2} + I_{Lc}) + \dots$$


$0 \times \frac{360^\circ}{N}$  phase shift     $1 \times \frac{360^\circ}{N}$  phase shift

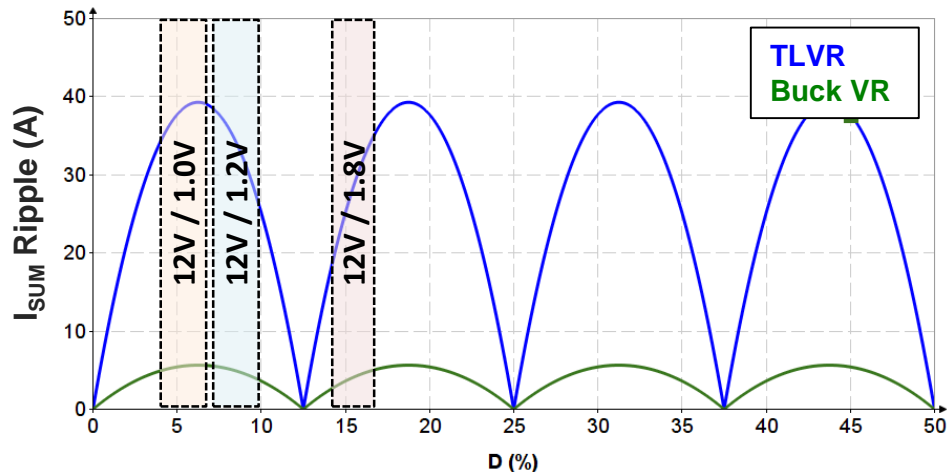Example:  
TLVR vs. multiphase buck  $I_{\text{OUT}}$  ripple vs. duty cycle




$V_{\text{IN}} = 12 \text{ V}$ ,  $F_s = 700 \text{ kHz}$ ,  $L_m = 150 \text{ nH}$ ,  
 $L_c = 120 \text{ nH}$ ,  $L_{\text{VR}} = L_{\text{eq}} = 125 \text{ nH}$ , eight phases
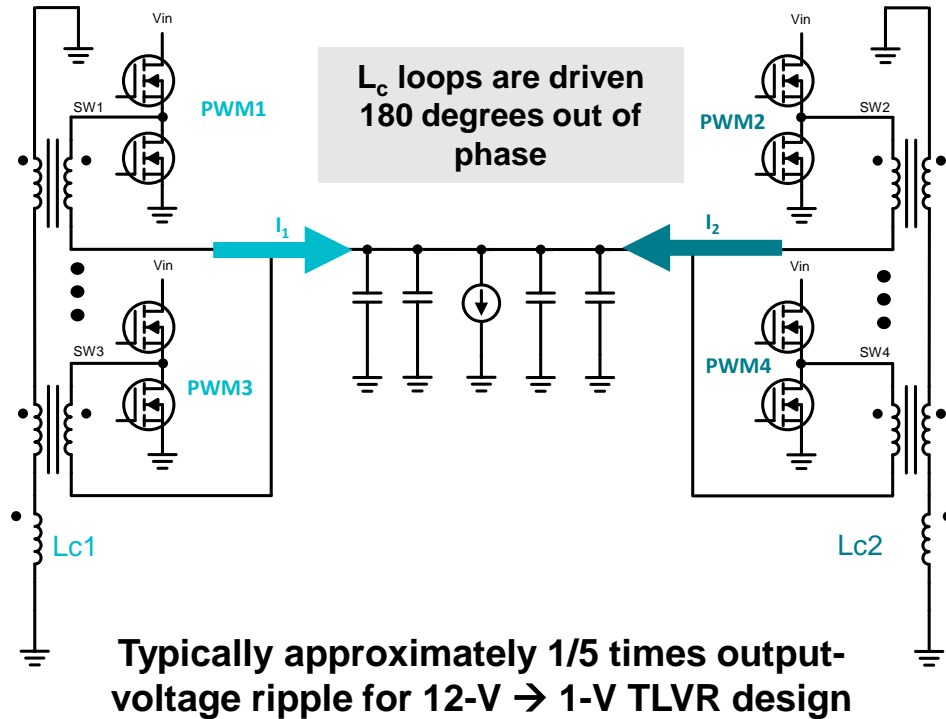
# Reduced ripple voltage: Interleaved TLVR




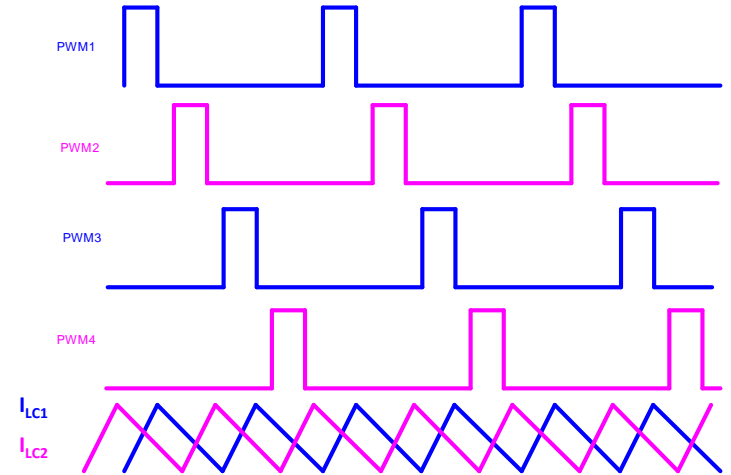- For high-phase-count (>12 phase) designs, creating two (or more)  $L_c$  loops achieves interleaving
- May also be advantageous for layout and electromagnetic interference (EMI) concerns (reduced  $L_c$  frequency, reduced maximum  $L_c$  voltage)



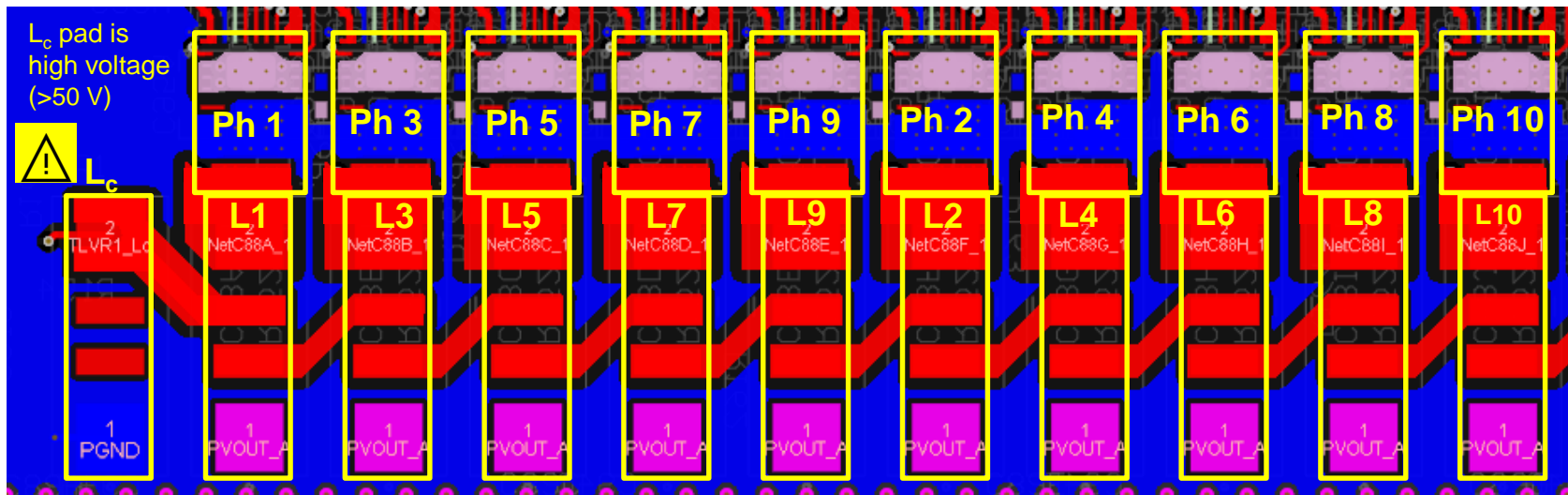
# Typical power-stage layout

- Interleaving phase fire order reduces crosstalk and reduces input capacitor stress
- $L_c$  current still carries high current in a transient
- Recommend  $\approx 50$  mils




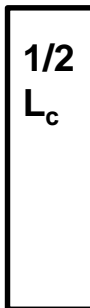Option for reduced EMI 1/2  $L_c$  on each end




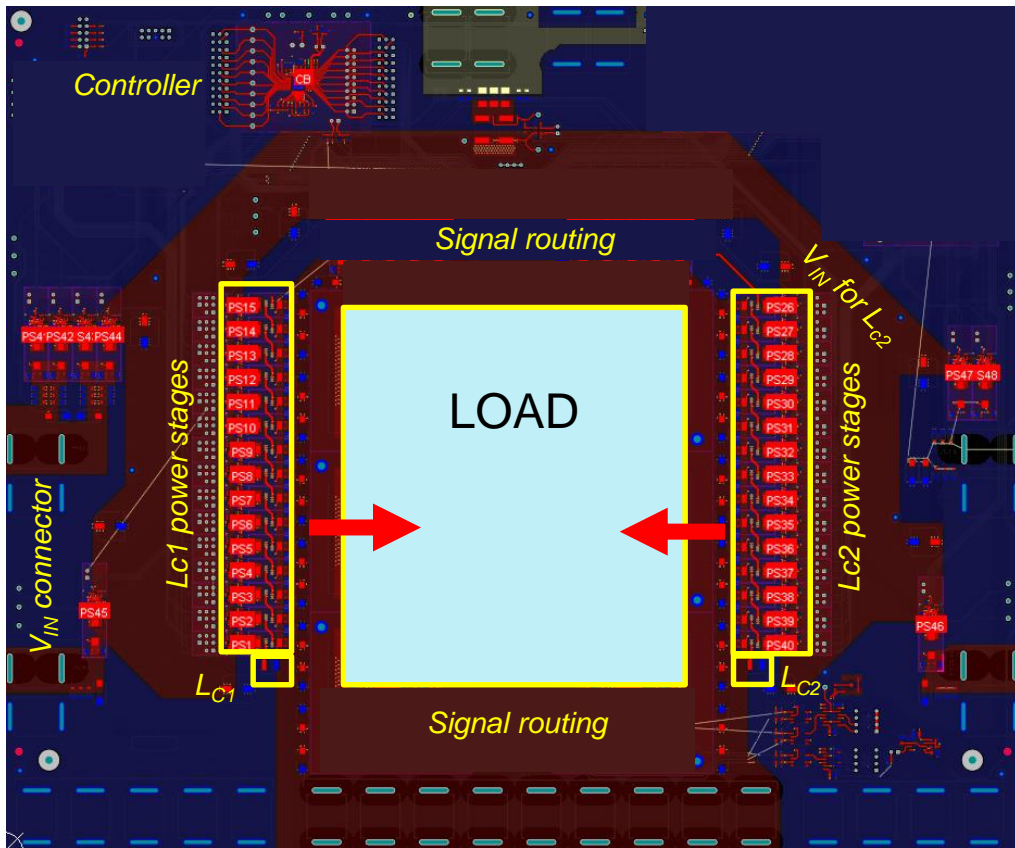
# Printed circuit board layout: Multiside power delivery



## Example:


- 32-phase design
- Two  $L_c$  interleaved design

## Recommendations:

- Symmetrical power train and  $L_c$  layout
- Decoupling and current-resistance (IR) drop on input traces
- PWM pin trace capacitance
  - Controller PWM drive strength
- Current-sense trace capacitance
  - Low-pass filter effect for current monitor (Imon) signals

# TLVR-optimized controllers and power stages

## TLVR-optimized power stages

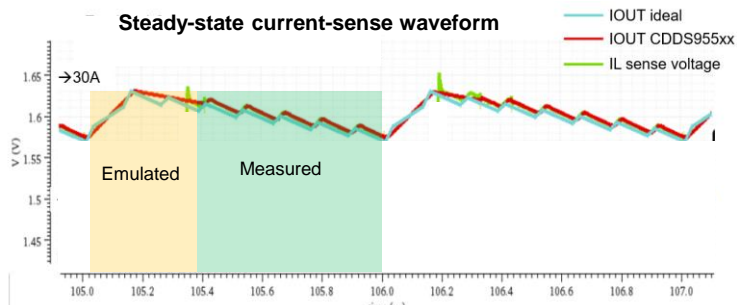


### High bandwidth, real current information reporting

Part number	Current rating	Package/features
CSD95440	80-A peak, 40 A <sub>RMS</sub>	5 mm × 6 mm (voltage I <sub>mon</sub> )
CSD95510	90-A peak, 50 A <sub>RMS</sub>	4 mm × 6 mm (voltage I <sub>mon</sub> )
CSD95560	90-A peak, 50 A <sub>RMS</sub>	4 mm × 6 mm (current I <sub>mon</sub> )
CSD95520	60-A peak, 30 A <sub>RMS</sub>	4 mm × 5 mm (voltage I <sub>mon</sub> )
CSD95570	60-A peak, 30 A <sub>RMS</sub>	4 mm × 5 mm (current I <sub>mon</sub> )

## TLVR-optimized controllers
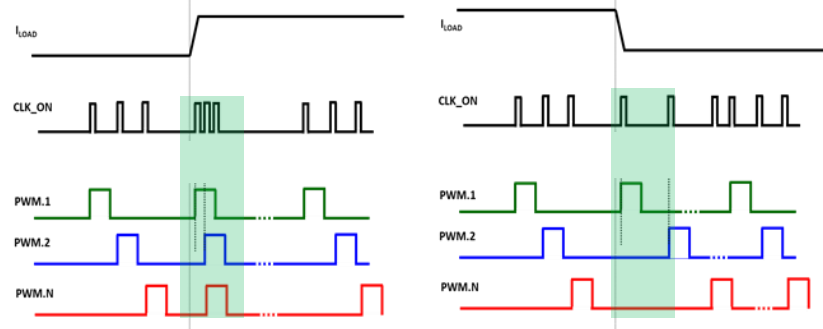
### PWM-based L<sub>c</sub> current emulation (patent pending)



### Load transient detection based on PWM timing

Part number	Phases	Package/features
TPS53685	8	5 mm × 5 mm AMD interface
TPS536C5	12	6 mm × 6 mm AMD interface
TPS53689T	8	5 mm × 5 mm Intel interface
TPS536C9T	12	6 mm × 6 mm Intel interface

# Conclusion

# Summary

- Introduced the TLVR topology
  - Buck-derived topology similar to coupled inductors for high-phase-count designs
  - Better modularity and reuse for TLVR, since inductors do not share a core
  - Significant output capacitor savings given coupled-inductor behavior
- Practical considerations for TLVR designs
  - TLVR designs typically have higher ripple current and voltage vs. buck
  - Interleaving for high-phase-count designs
  - Printed circuit board layout for TLVR designs is similar to buck, with  $L_c$  loop added
- TLVR-optimized components
  - High-bandwidth and system-level optimizations needed to optimize for TLVR designs

# References

- "Fast multi-phase trans-inductor voltage regulator." Technical Disclosure Commons. May 2019. [https://www.tdcommons.org/cgi/viewcontent.cgi?article=3261&context=dpubs\\_series](https://www.tdcommons.org/cgi/viewcontent.cgi?article=3261&context=dpubs_series)
- Radhakrishnan, K., and J. Douglas. "Microprocessor Power Delivery Challenges." APEC 2022, March 2022.
- Parisi, C. "Multiphase Buck Design From Start-to-Finish (Part 1)." <https://www.ti.com/lit/an/slva882b/slva882b.pdf>
- Dong, Y. "Investigation of Multiphase Coupled-Inductor Buck Converters in Point-of-Load Applications." Ph.D. thesis, Virginia Tech, 2009. [https://vtechworks.lib.vt.edu/bitstream/handle/10919/28469/ETD\\_final\\_Rev2.pdf](https://vtechworks.lib.vt.edu/bitstream/handle/10919/28469/ETD_final_Rev2.pdf)
- Qiu, Y. "Coupled inductors for power supplies: advantages and compromises." June 2007. EETimes. <https://www.eetimes.com/coupled-inductors-for-power-supplies-advantages-and-compromises>
- Lu, Z., and W. Chen. "Multi-Phase Inductor Coupling Scheme with Balancing Winding in VRM Applications." APEC 2007, March 2007.
- Zhu, F. "Transient Analysis of Multi-Phase Voltage Regulator with Nonlinear Indirect-coupled Inductor." CPES PMC Review, June 2021.
- Jiang, S., X. Li, M. Yazdani, and C. Chung. "Driving 48V Technology Innovations Forward – Hybrid Converters and Trans-Inductor Voltage Regulator (TLVR)." APEC 2020.
- Erickson, R., and D. Maksimovic. "Fundamentals of Power Electronics." Springer AG, Third Edition. 2020.



© Copyright 2024 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated