

# Power Supply Design Seminar

Creating a primary-side regulation flyback converter using a conventional boost controller

---

Author

Jiri Panacek



# Agenda

- Flyback converters
  - Basics
  - Secondary-side regulation (SSR) vs. primary-side regulation (PSR)
- PSR
  - Detailed look at auxiliary winding waveforms
  - Three different flavors of PSR
  - The problem statement
- Design example using the LM5156-Q1 boost controller
  - Outlining input data and feasibility check
  - Resolving feedback
  - Further optimizations (artificial load, current sensing, snubbers)
- Conclusion and additional materials



# Flyback converter

## Turnon

- Switch conducts; primary current ( $I_{PRI}$ ) stores the energy in the coupled inductor
- Secondary-side rectifier is reverse-polarized (secondary voltage [ $V_{SEC}$ ] < 0)
- Coupled inductor stores the energy
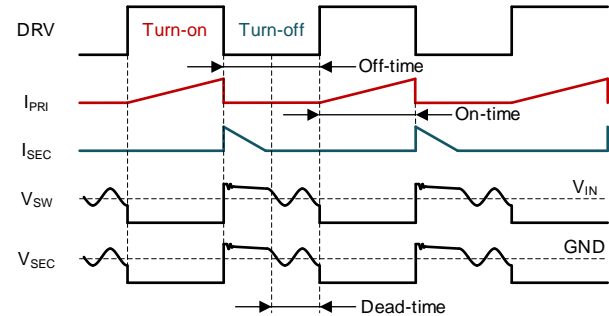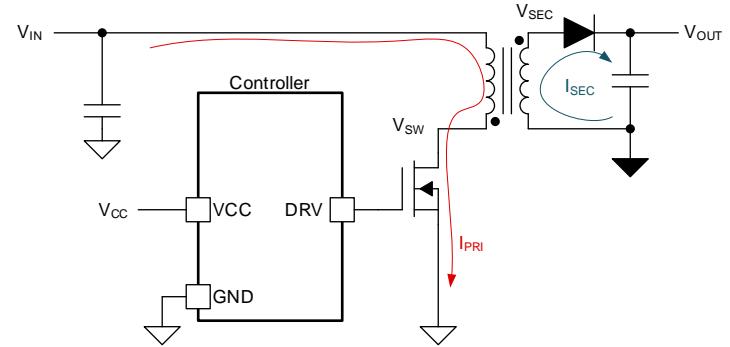
## Turnoff

- Switch opens; magnetized coupled inductor changes the polarity ( $V_{SEC} > 0$ )
- Secondary current ( $I_{SEC}$ ) flows through the secondary winding and energizes the load




# Flyback converter feedback

## PSR sensing

- Sensing across the auxiliary winding (A)
- Sensing the reflected voltage on the switch node (B)

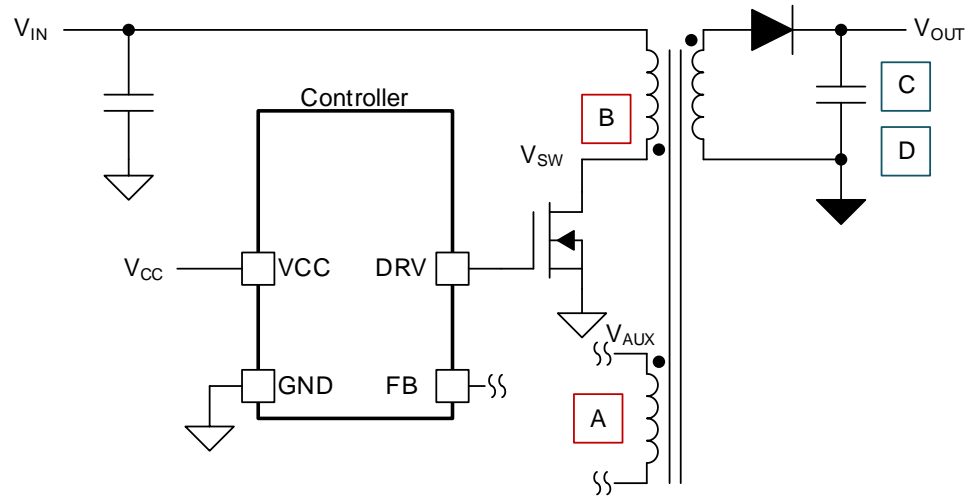
## SSR sensing

- Using a resistor divider (C)
- Using an optocoupler (D)



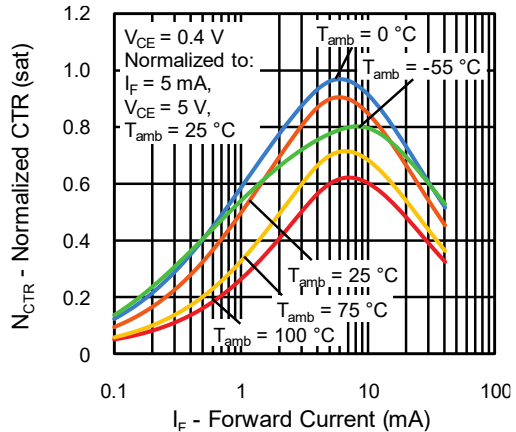
# Closing the loop: SSR

- 431-type shunt regulator senses the output and adjusts the current through the optocoupler



Source: Vishay, Application Note 45

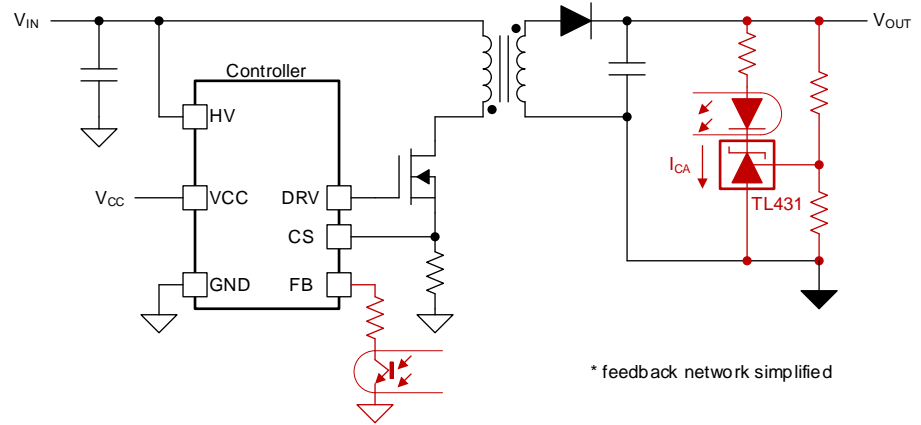


\* feedback network simplified

- Current-transfer ratio (CTR) of the optocoupler changes with:
  - Time
  - Temperature
  - Current
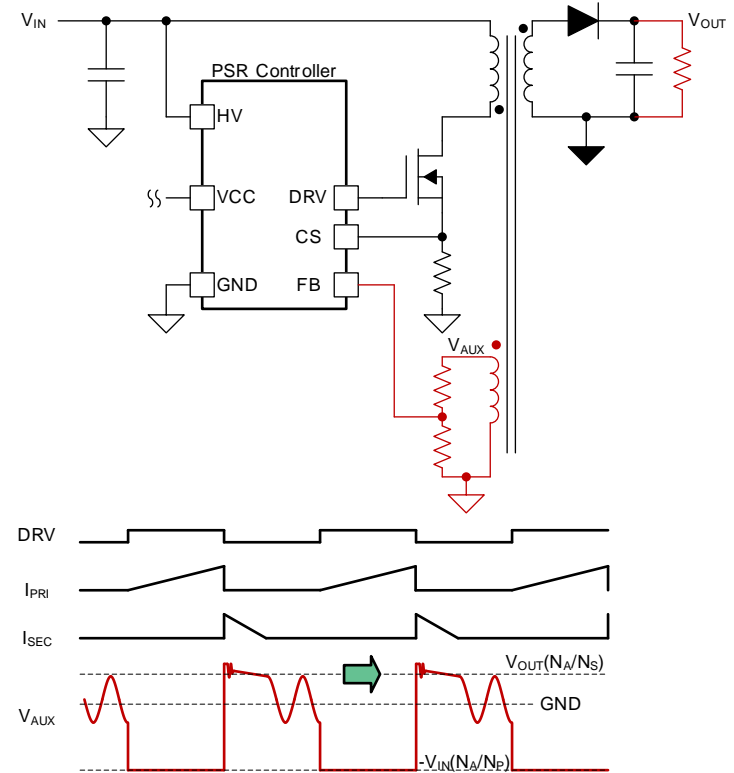
# Closing the loop: PSR



- Auxiliary winding is referenced to the primary side
- Voltage tracks the isolated output
- The controller senses the voltage across the auxiliary winding
- Continuous switching of PSR flybacks is crucial, as it ensures that the auxiliary winding voltage accurately represents the output



# SSR vs. PSR

Parameter	SSR with an optocoupler	PSR
Light-load behavior	<b>Good light-load regulation</b>	Requires minimal load
Feedback	Complex feedback network using 431-type regulator and optocoupler	<b>Sampled reflected output voltage</b>
Initial output-voltage accuracy	<b>Excellent</b>	Average
Load regulation	<b>Very good load regulation (&lt;1%)</b>	Average load regulation (>1%)
Reliability	Optocoupler aging factor affects reliability	<b>Excellent</b>
Transient response	Limited by optocoupler bandwidth	Mostly limited by the switching frequency
Cost	Average	<b>Improved because of the optocoupler removal</b>
Self-biasing	Requires auxiliary winding	<b>Leverages auxiliary winding for both bias and feedback</b>
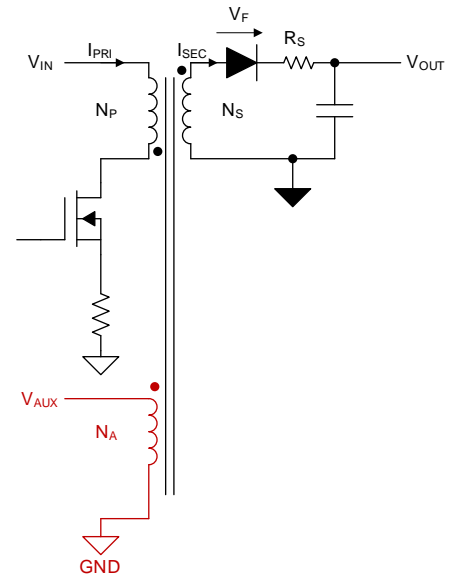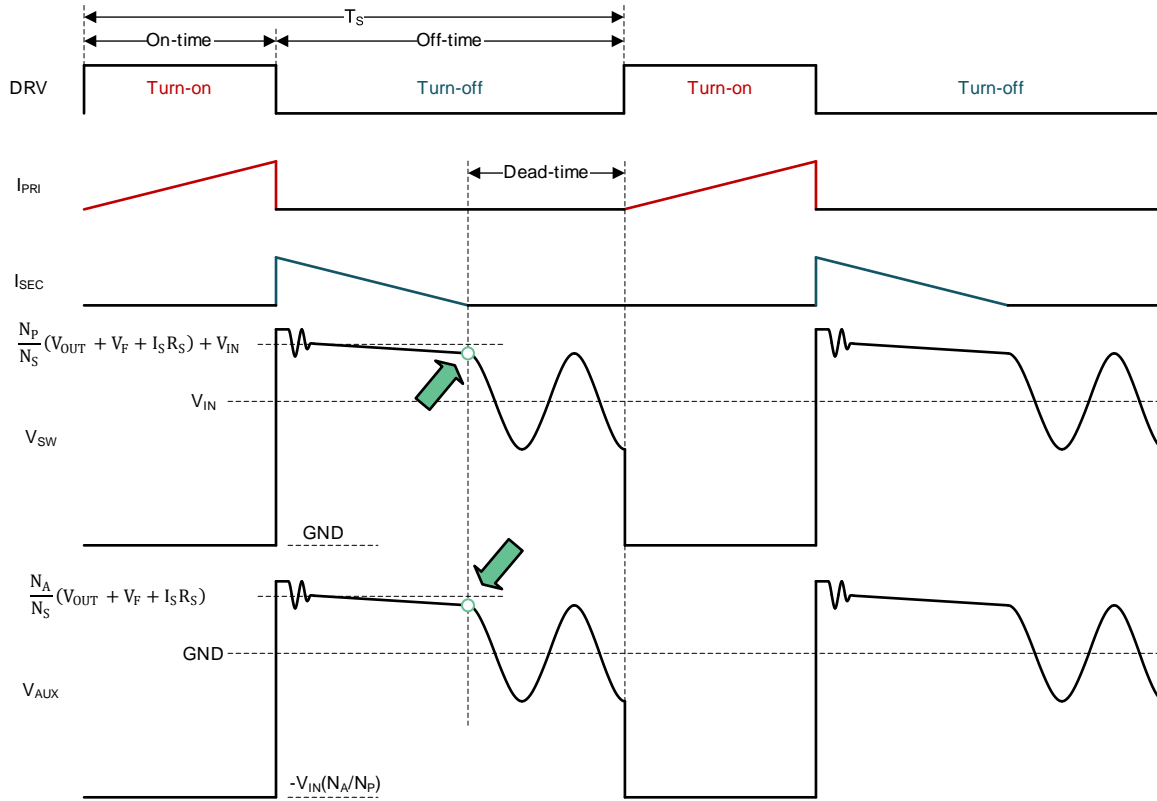
# Detailed look at the auxiliary winding waveforms




- Ideal sampling point is when  $I_{SEC}$  drops to zero



# Auxiliary winding waveforms during load transient




- Current increase at  $t_1$  causes output voltage ( $V_{OUT}$ ) drop
- Controller finds current demand increase (A) within one switching cycle ( $T_S$ )
- Controller **increases** on-time ( $t_{ON}$ )
- Switching frequency ( $f_{SW}$ ) **decreases**
- $V_{OUT}$  returns to desired level after several cycles
- At  $t_2$  the process repeats with inverse logic (B)

## Quasi-resonant PSR controller example

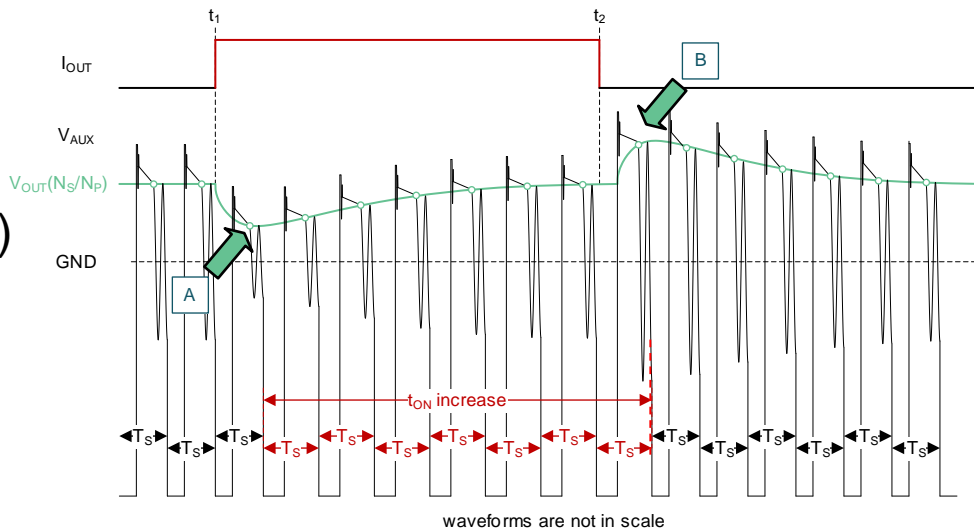

◦ Discriminator and sampler circuit sampling points (UCC28700-Q1)


# Three flavors of PSR

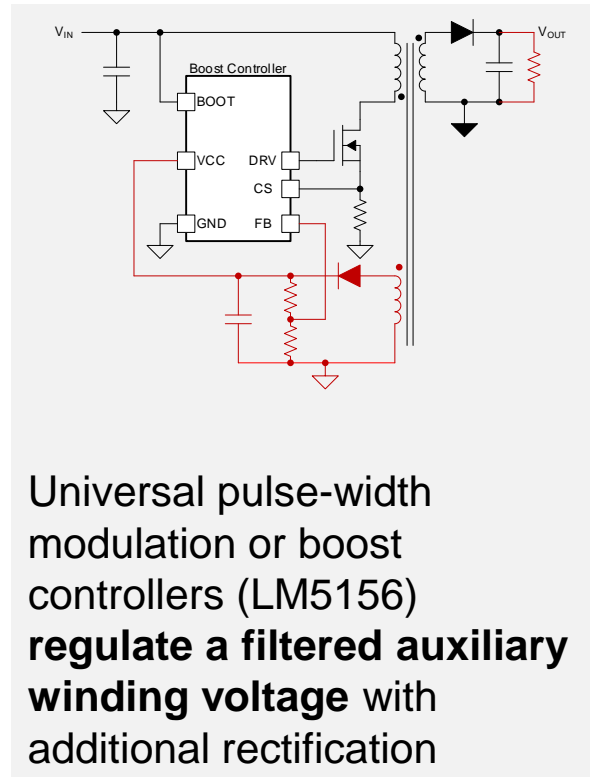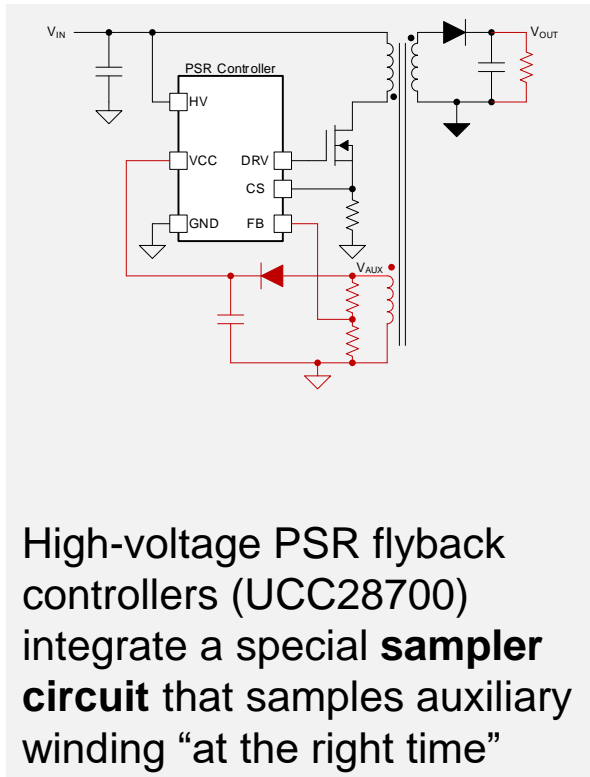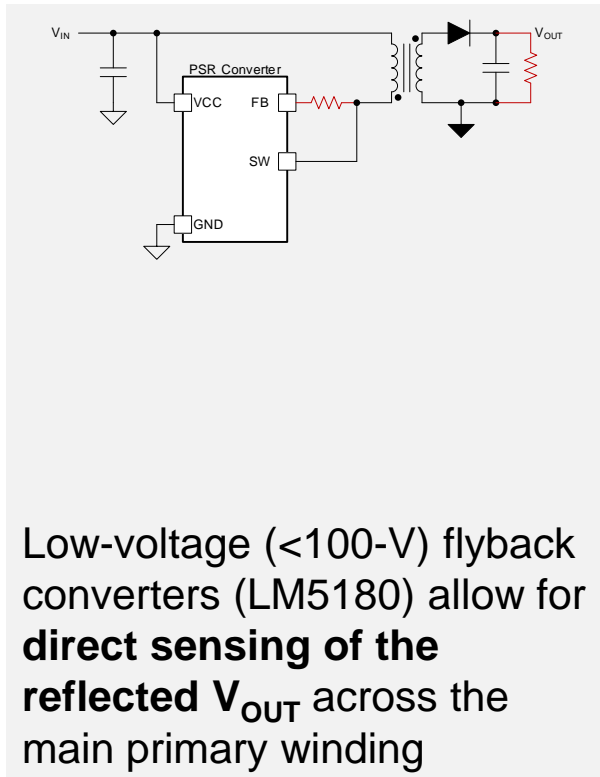
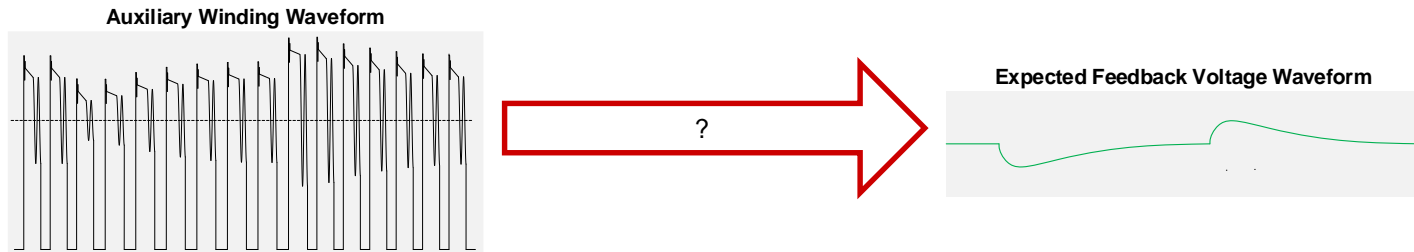
# Problem statement

- $V_{AUX}$  waveform is composite and carries a lot of information
- $V_{AUX}$  provides accurate  $V_{OUT}$  information only once per period when  $I_{SE}$  drops to zero
- PSR regulators feedback use **sample and hold**
- Standard boost controllers expect **continuous** feedback voltage

How do you convert the auxiliary winding waveform?



# Step-by-step design example


Isolated gate-driver bias supply with the LM5156-Q1 boost flyback controller



17 x 44 x 14mm (W x L x H)



# Suggested PSR flyback design flow

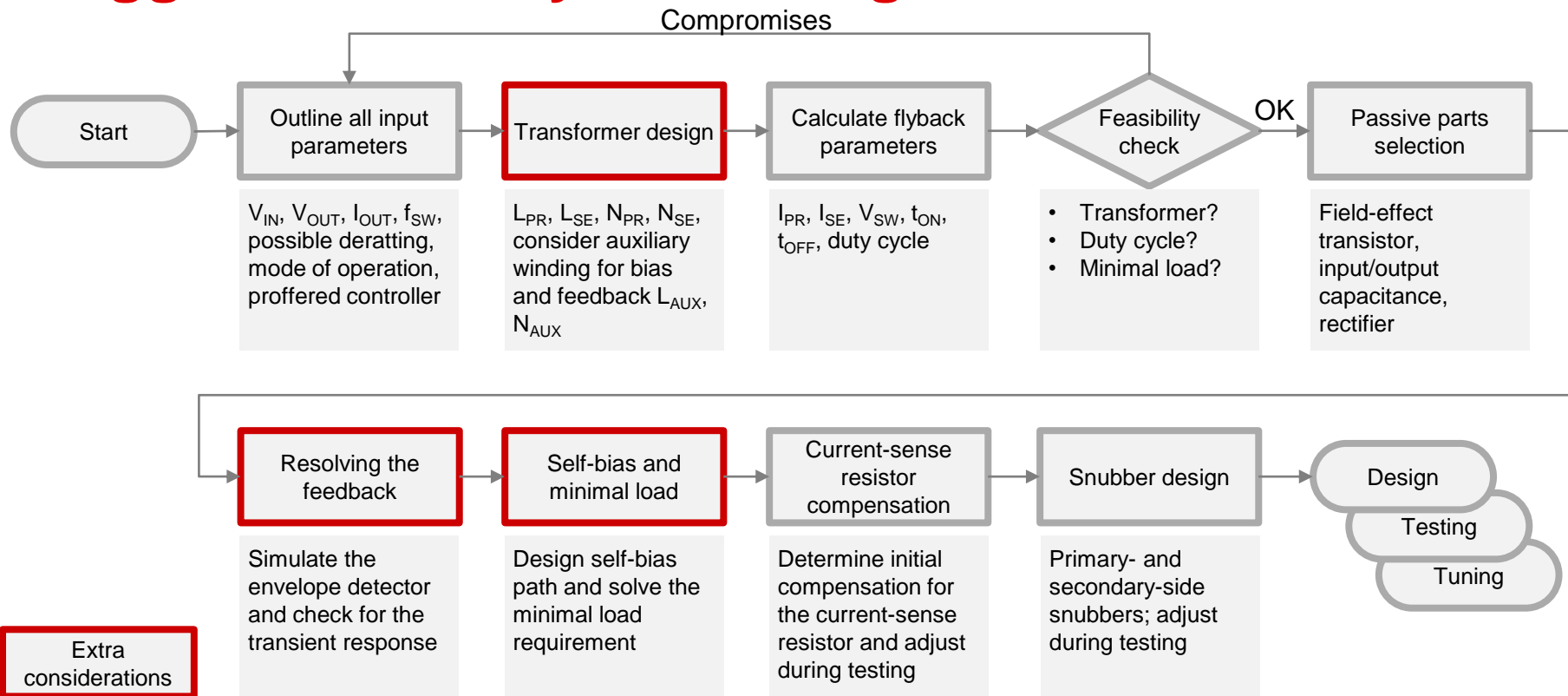

# Define converter parameters

- Isolated gate-driver bias supply powered from the 12-V vehicle battery


Parameter	Specification
Input voltage ( $V_{IN}$ )	6 V <sub>DC</sub> -42 V <sub>DC</sub> (52-V transient)
Output voltage ( $V_{OUT}$ )	+15 V, -9 V ( $V_{OUT} = 24$ V)
Output current ( $I_{OUT}$ )	180 mA
Switching frequency ( $f_{SW}$ )	400 kHz
Mode of operation	Discontinuous conduction mode (DCM)
Primary-to-secondary isolation	Basic, 2.5 kV
Controller	LM5156-Q1

# Identify corner cases

- No frequency fallback or boundary conduction mode (BCM) is possible. A conventional controller either:
  - Operates with constant  $f_{SW}$
  - Enters pulse-skipping mode when  $V_{OUT}$  exceeds the regulated level
- Transformer turns ratio and inductance have to allow for DCM at  $f_{SW}$
- Worst-case scenarios – extreme duty cycles:
  - $V_{IN(MIN)}$  and  $I_{OUT(MAX)}$  result in a maximal duty cycle
  - $V_{IN(MAX)}$  and  $I_{OUT(MIN)}$  result in a minimal duty cycle
- The Power Stage Designer™ software iterative process suggests transformer  $L_{PRI} = 4 \mu\text{H}$ ,  $L_{SEC} = 16 \mu\text{H}$ , turns ratio  $N_P:N_S = 1:2$

# Feasibility check for worst-case scenarios

Power Stage Designer software finds the minimal load for  $V_{IN} = 42\text{ V}$

Parameter	Minimum duty condition	Maximum duty condition	LM5156-Q1 device data sheet specification
On-time	0.13 $\mu\text{s}$	1.57 $\mu\text{s}$	Minimum 130 ns (Figure 8-12)
Off-time	0.43 $\mu\text{s}$	0.76 $\mu\text{s}$	
Duty cycle	5.10%	62.86%	Maximum 92.8% (Figure 8-16)
Zero time	1.94 $\mu\text{s}$	0.16 $\mu\text{s}$	
Maximum primary current ( $I_{PR}$ )	1.33 A	2.36 A	
Maximum secondary current ( $I_{SE}$ )	0.66 A	1.18 A	
Required minimum load ( $I_{L(MIN)}$ )	<b>60 mA</b> 	Alternatively, the controller enters pulse-skipping mode	




# First design review

- Magnetics supplier confirms that the transformer design is reasonable
- The LM5156-Q1 can support required duty cycles even at  $f_{SW} = 400$  kHz
- The converter requires a  $\approx 60$ -mA artificial load at  $V_{IN} = 42$  V for constant  $f_{SW}$ , which negatively impacts efficiency at light loads ( $\approx 5$  mA at  $V_{IN} = 12$  V)
- Allowing the controller to enter pulse-skipping mode is a good compromise between:
  - Reducing the artificial load, thus increasing efficiency
  - Reducing the transient response in pulse-skipping mode

Designer decision: Does this solution still satisfy expectations?
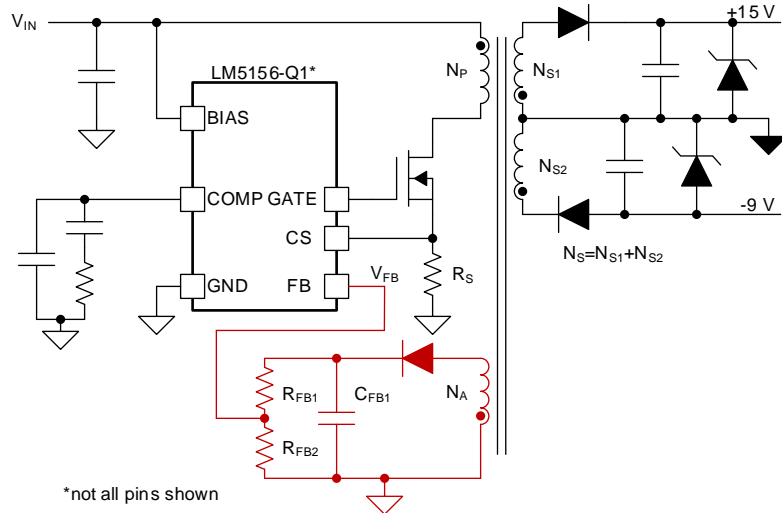
# Resolving the feedback

- Use diode as a half-wave rectifier (peak detector)
- Detector (filter) must be able to track the output transient



- Set the auxiliary winding turns ratio such that the rectified voltage allows for self-biasing (such as 15 V)


$$V_{VCC} \approx V_{OUT} \times \frac{N_A}{N_S}$$

- Calculate the resistor divider to match the feedback voltage ( $V_{FB}$ )

$$V_{FB} = V_{OUT} \times \frac{N_A}{N_S} \left( \frac{R_{FB2}}{R_{FB1} + R_{FB2}} \right)$$
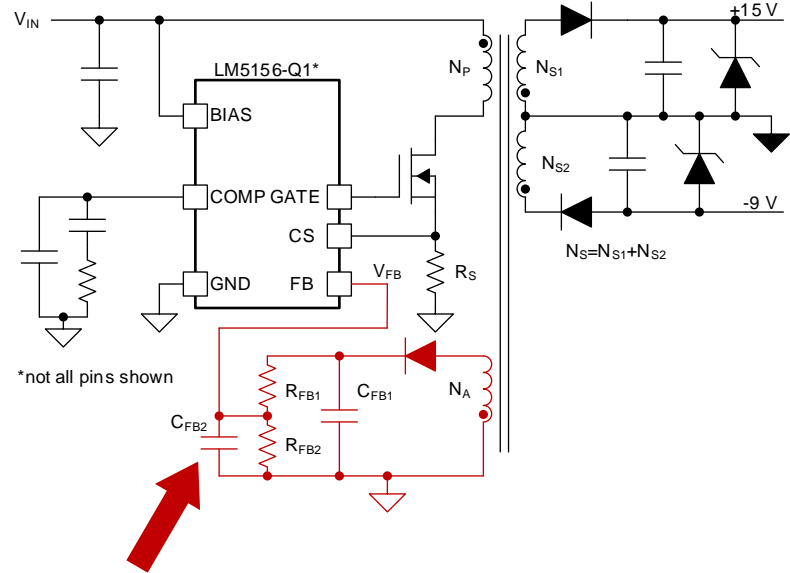
# Resolving the feedback



- A passive, second-order filter is recommended to filter out the  $V_{AUX}$  envelope
- Capacitors  $C_{FB1}$  and  $C_{FB2}$  define the filter time constant ( $\tau$ )
- Use a simulation tool to find out optimal  $C_{FB1}$  and  $C_{FB2}$  values



# Resolving feedback: Simulation in PSpice



## Three steps

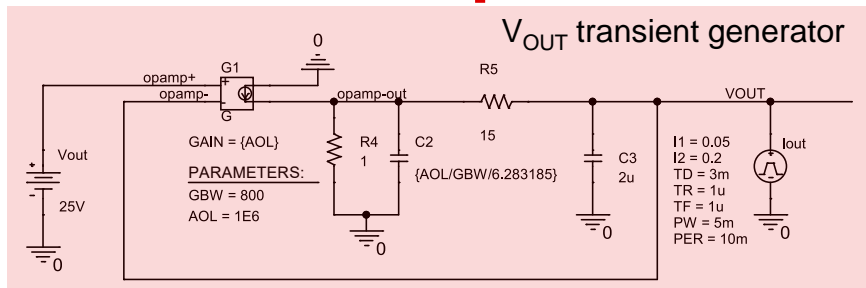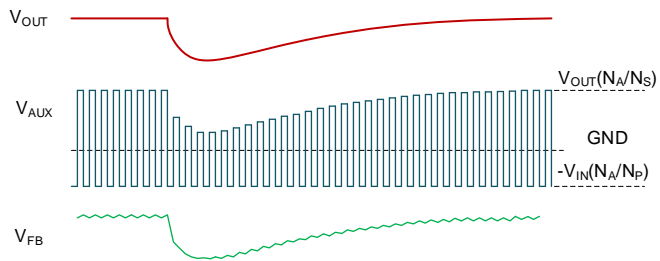1. **Generate** desired  $V_{OUT}$  transient response
2. **Approximate** the  $V_{AUX}$
3. **Adjust** the rectifier-filter transient response using  $C_{FB1}$  and  $C_{FB2}$



PARAMETERS:

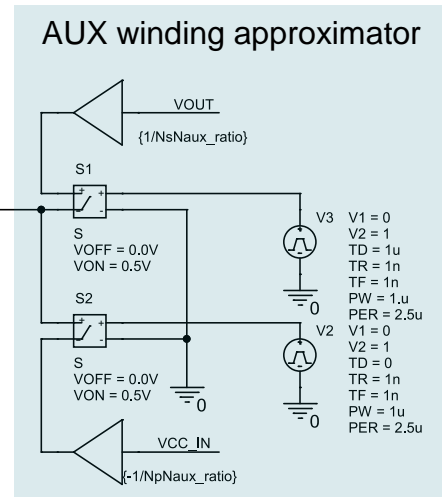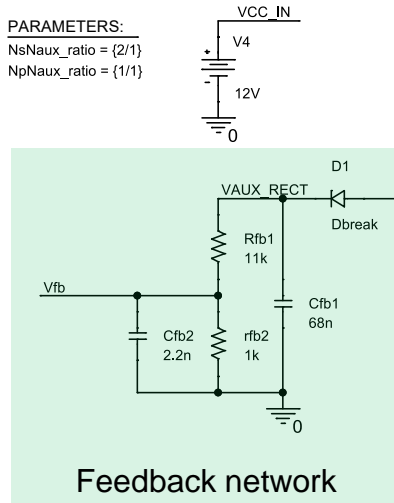
- $N_s N_{aux\_ratio} = \{2/1\}$
- $N_p N_{aux\_ratio} = \{1/1\}$




# Simulated filter (peak detector) response

Check that  $V_{FB}$  is able to track  $V_{OUT}$


$\tau$  is too long

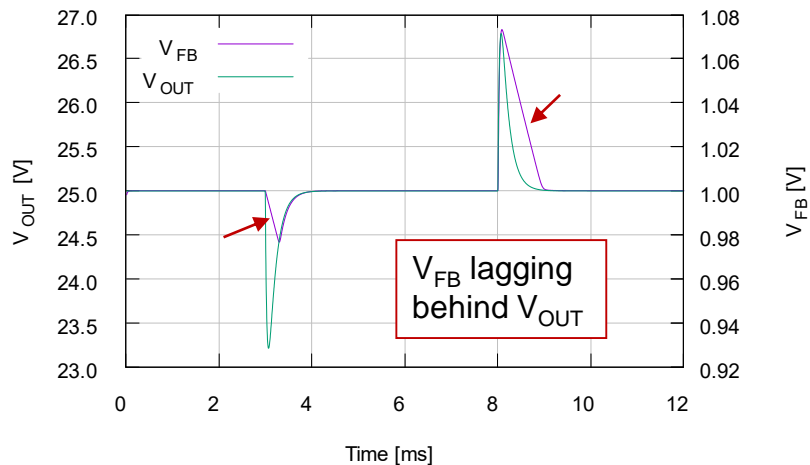


$\tau$  is optimal

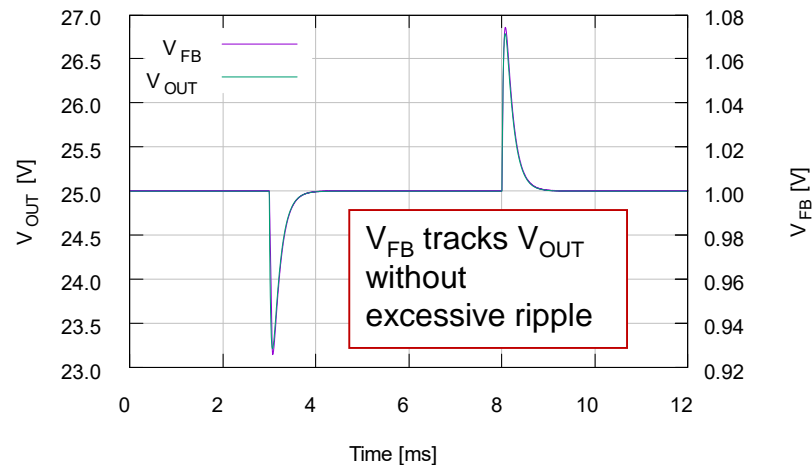
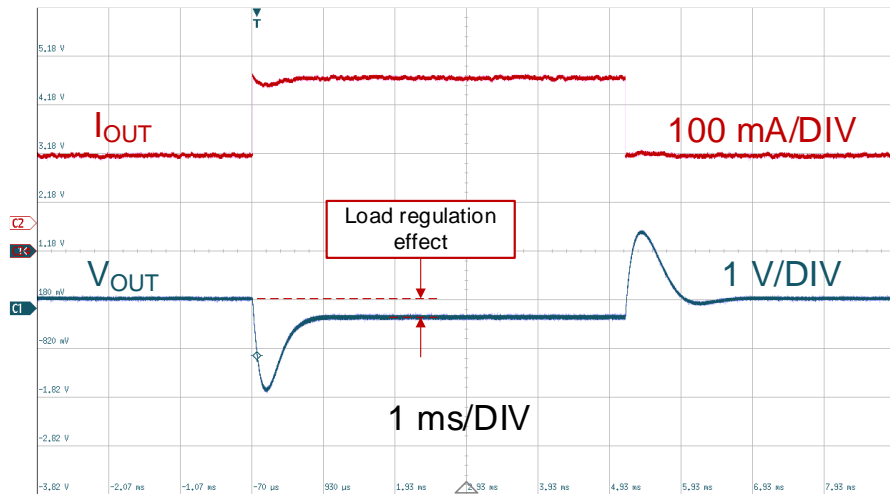
# $V_{OUT}$ transient response and $V_{AUX}$ feedback



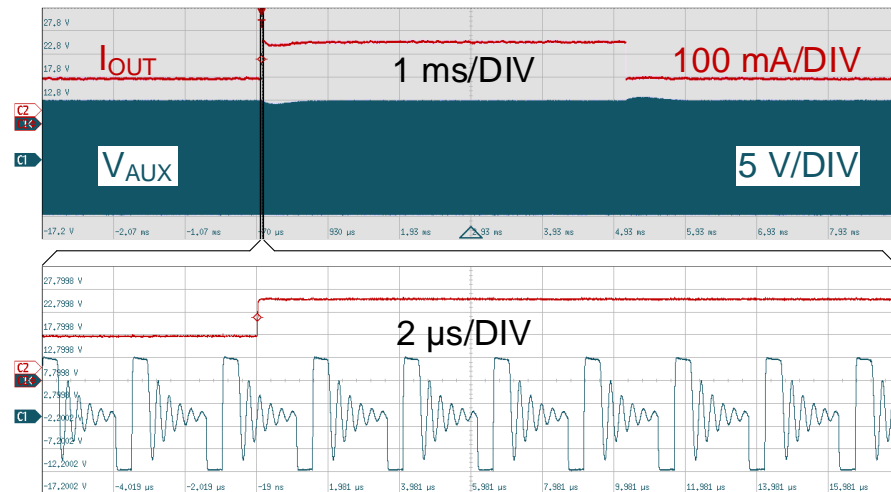
$V_{OUT}$  transient response for  $I_{OUT}$  from 45 mA to 135 mA



$V_{AUX}$  transient response for  $I_{OUT}$  from 45 mA to 135 mA


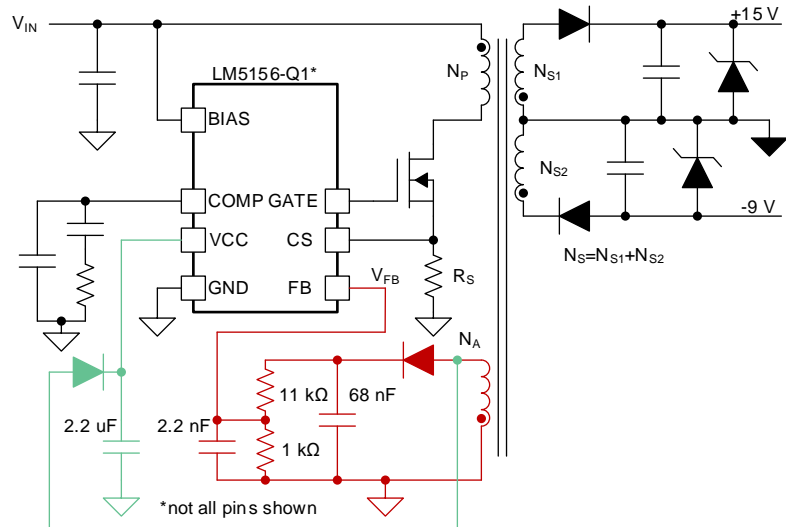
# Biasing scheme to improve light-load efficiency

- The feedback and self-power have different requirements
- **Self-power (bias)** from the auxiliary winding requires large bulk capacitance to keep the voltage rail stable
- **The feedback path** requires a fast transient response to quickly track the  $V_{OUT}$
- Two separate paths offer the best performance without compromises


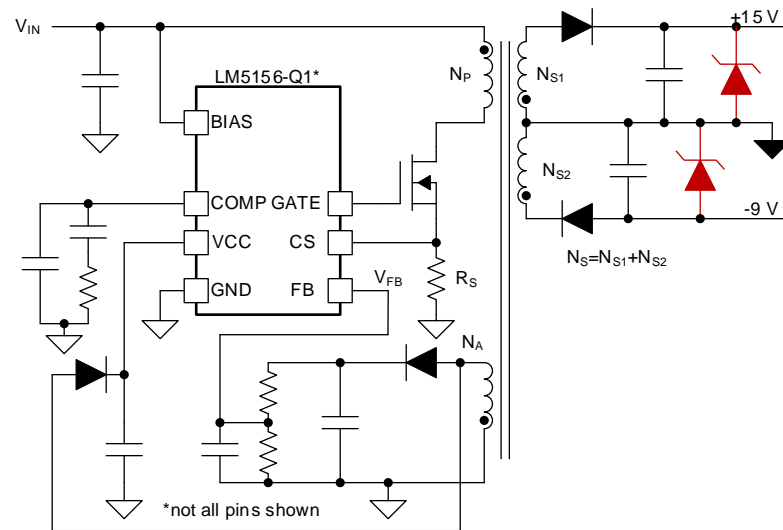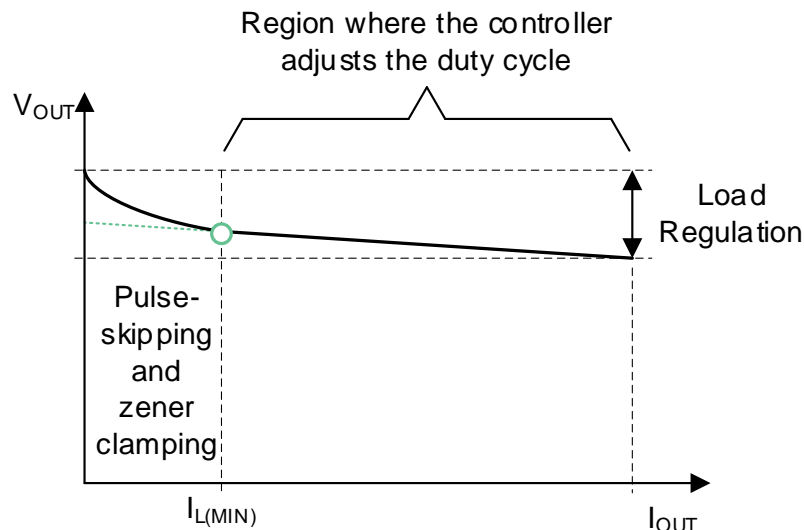
# Solving the minimal load

- There are two options:
  - Resistors as a dummy load
  - Zener diodes




- The controller can't further reduce  $t_{ON}$
- $V_{OUT}$  increases, Zener diodes sink current
- Pulse-skipping occurs


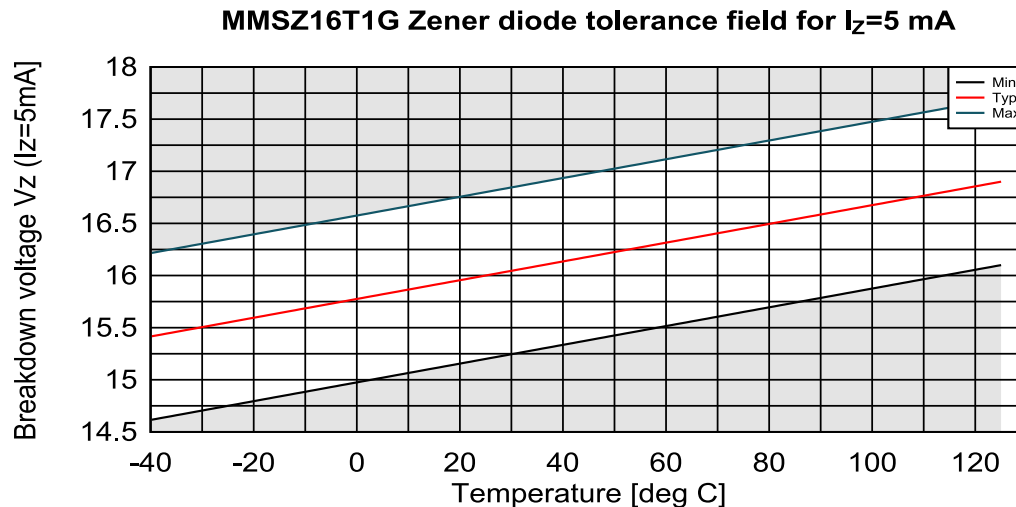
# Zener diodes and their accuracy


- Zener diodes are inexpensive but not very accurate
- Diodes with approximately:
  - $V_Z < 4.7$  V have a negative temperature coefficient
  - $V_Z > 4.7$  V have a positive temperature coefficient
- Out-of-the-box accuracy varies



Parameter	MMSZ10T1G ( $V_Z = 10$ V)	MMSZ16T1G ( $V_Z = 16$ V)
Lowest Zener voltage	8.9 V	14.6 V
Highest Zener voltage	11.4 V	17.7

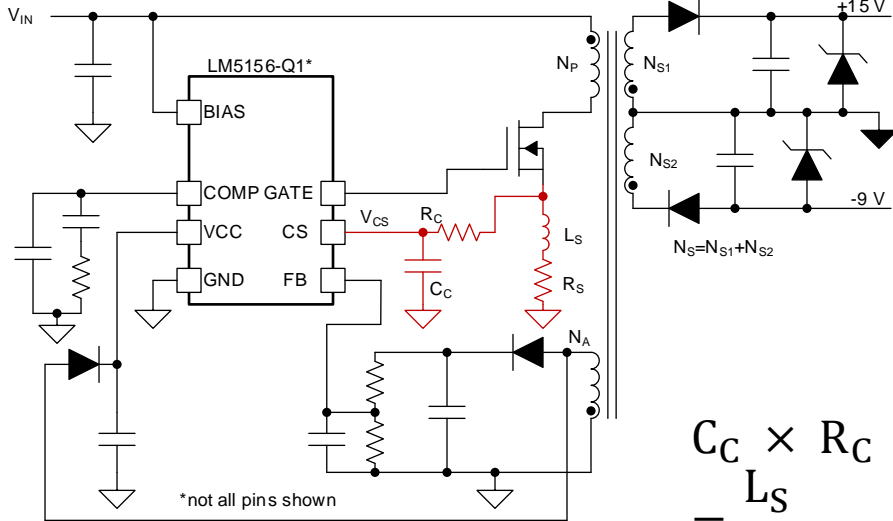
# Compensating the current-sense resistor

- Ringing on the current-sense resistor may cause false overcurrent events
- Compensation network is necessary




(The example uses a 0.33Ω 0603 shunt resistor)

$$C_C \times R_C = \frac{L_S}{R_S}$$

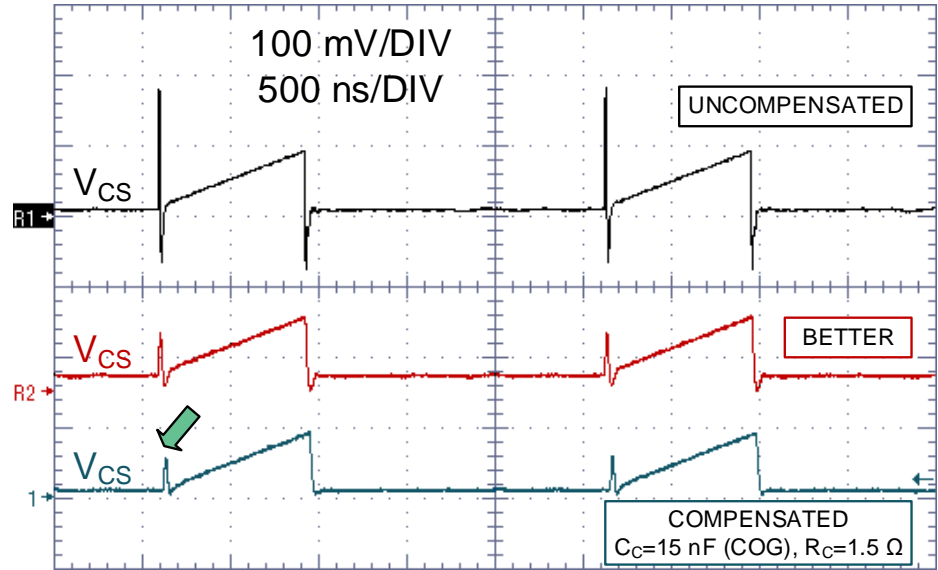

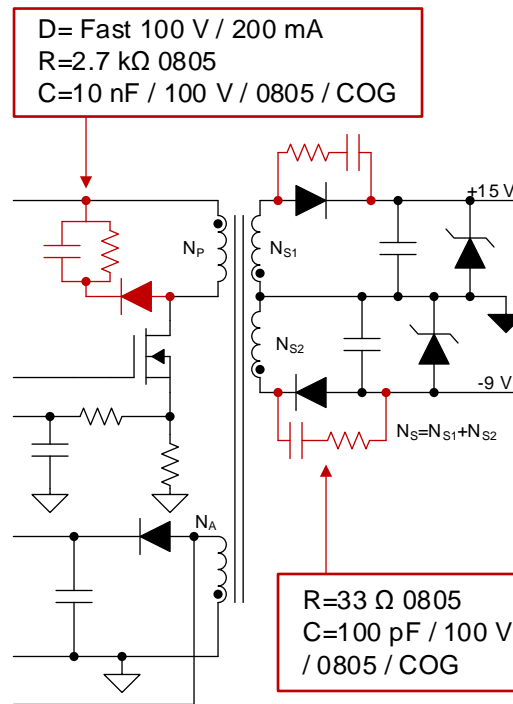
# Snubber circuits

- Snubber circuits reduce ringing that:
  - Causes electromagnetic interference (EMI)
  - Stress the power transistor during the turnoff transient
- The ringing also negatively affects the auxiliary waveform and affects feedback
- Ringing is proportional with  $I_{OUT}$



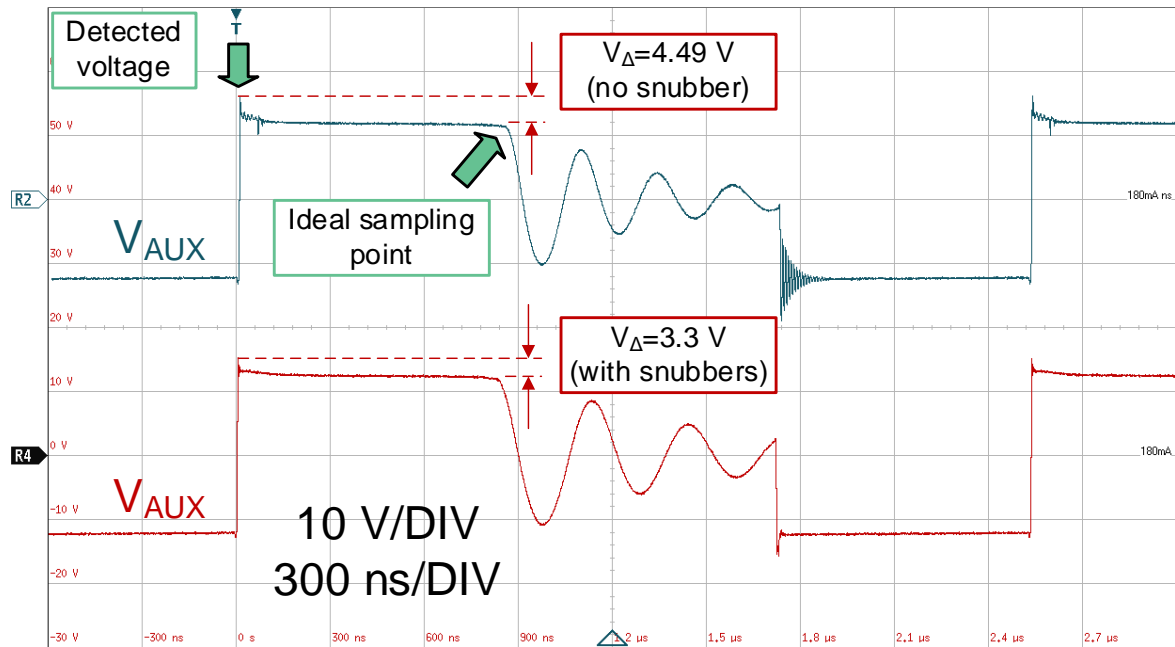
# $V_{AUX}$ waveforms with and without snubber circuits



$V_{AUX}$  waveforms for  $I_{OUT} = 180 \text{ mA}$
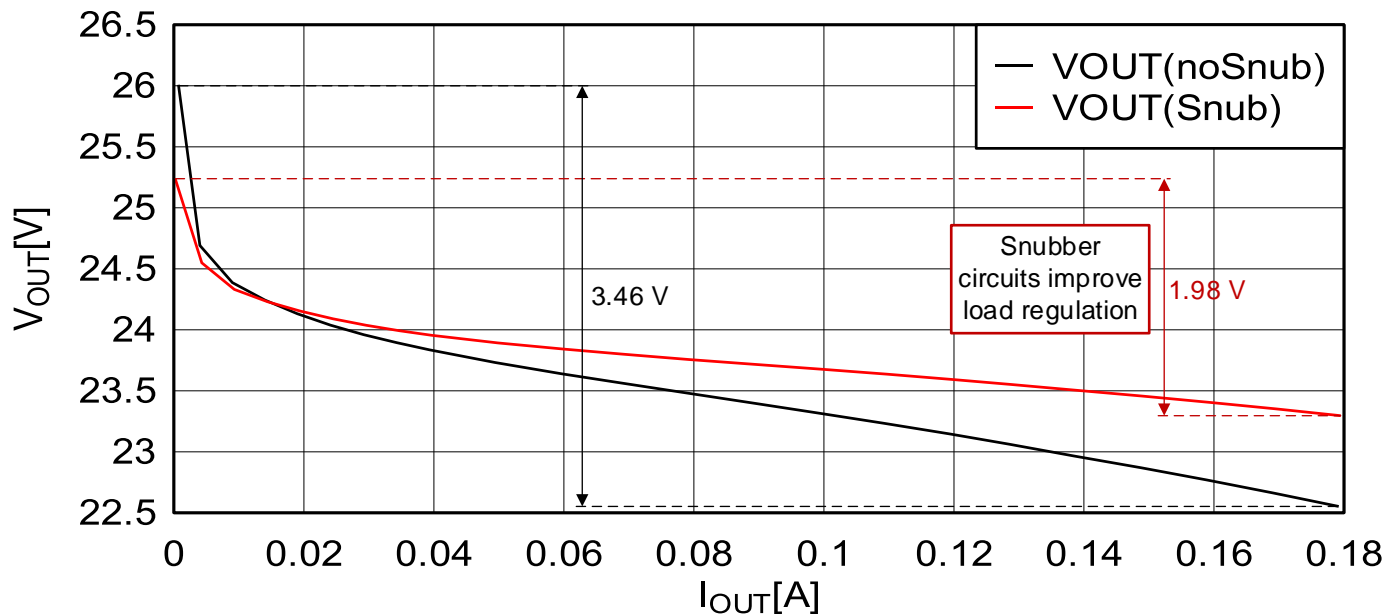
# Snubber circuit effect on load regulation



# Conclusion

- PSR flybacks are popular for low-cost isolated DC/DC converters
- A PSR flyback with a conventional boost controller requires these considerations for feedback:
  - Identify the minimum and maximum duty cycle for the given operating conditions
  - Design the  $V_{AUX}$  envelope detector (filter) such that it tracks the  $V_{OUT}$
  - Minimize ringing using snubbers
  - Split the self-bias and feedback paths to enable a fast transient response
  - Add a compensation network to the current-sensing resistor
  - Design the compensation with the envelope detector in mind, accounting for a higher phase margin
  - Verify the transient response for the minimal, maximal and nominal input voltage

# Resources and more reading

## [UCC28700-Q1 Datasheet, chapter 7.4.1](#)

- How the discriminator and sampler circuit works

## [LM5180-Q1 Datasheet, chapter 7.3.2](#)

- How the frequency fallback, BCM and PSR work

## [Power Stage Designer software](#)

- Essential tool for initial component selection

## [Under the Hood of Flyback SMPS Designs](#) (SLUP261)

- In-detail description of flyback converters

## [TI Drive](#) (access code rn4N8w;r )

- Design resources for this presentation

## [PSPICE-FOR-TI](#)

- PSpice® for TI design and simulation tool

access code rn4N8w;r





© Copyright 2024 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)



## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated