

High-Voltage Power Supply Using the Highly Integrated TPS61040

PMP Portable Power

ABSTRACT

The TPS61040 is a highly integrated, low-power, boost converter capable of delivering output voltages up to 28 V. Additionally, using a coupled inductor enables the TPS61040 to be used in applications where higher voltages are required – up to 75 V can be achieved.

1 Features


- 1.8 V to 6 V Input Voltage Range
- Adjustable Output Voltage Range up to 28 V
- 400 mA (TPS61040) and 250 mA (TPS61041) Internal Switch Current
- Up to 1 MHz Switching Frequency
- 28 μ A Typical No Load Quiescent Current
- 1 μ A Typical Shutdown Current
- Internal Softstart
- Available in a Tiny 5-Pin SOT23 Package

2 TPS61040 Reference Design

The reference design uses the TPS61040 boost converter to generate an 18-V output from a single-cell, Li-Ion battery (3 V to 4.2 V). The output voltage in the design can be adjusted up to 28 V by modifying the resistor values used in resistor divider R1 and R2.

3 TPS61040 Schematic and Bill of Materials


3.1 TPS61040 Schematic

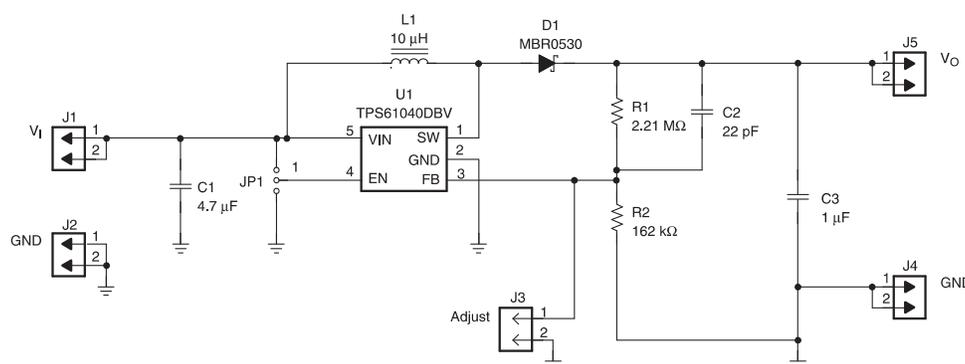

3.2 Bill of Materials

QTY	Reference	Description	Size	MFG	Part Number
1	C1	Capacitor, ceramic, 4.7 μ F, 6.3 V, X5R, 15%	0805	Murata	GRM21B60J475KA11
1	C2	Capacitor, ceramic, 22 pF, 50 V, C0G, 5%	0603	Murata	GRM1885C1H220JZ01
1	C3	Capacitor, ceramic, 1 μ F, 25 V, X7R, 10%	1206	Murata	GRM31MR7E105KC01
1	D1	Diode, Schottky 0.5 A 30 V	SOD-123	On Semi	MBR0530T1
5	J1–J5	Header, 2-pin, 100-mil spacing (36-pin strip)	0.1 \times 2"	Sullins	PTC36SAAN
1	JP1	Header, 3-pin, 100-mil spacing (36-pin strip)	0.1 \times 3"	Sullins	PTC36SAAN
1	L1	Inductor, SMT, 10 μ H, 0.76 A, 0.23 Ω	0.15 \times 0.162	Sumida	CR32-100
1	R1	Resistor, chip, 2.21 M Ω , 1/16 W, 1%	0603	Standard	Standard
1	R2	Resistor, chip, 162 k Ω , 1/16 W, 1%	0603	Standard	Standard
1	U1	IC, high efficiency boost converter	SOT23-5 (DBV)	TI	TPS61040DBV
1		PCB, 1.5" \times 1" \times 0.062"		Any	SLVP209
1		Shunts, 100-mil, black	0,1 mm	3M	929950-00

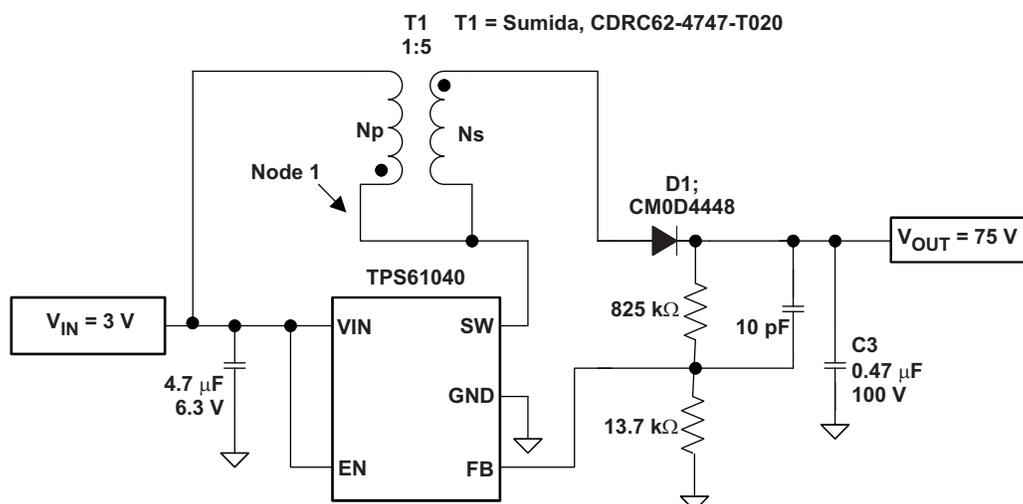4 Modified TPS61040EVM for Higher Voltages



By substituting the inductor with a 1-to-5 transformer, the TPS61040 can deliver output voltages over 75 V. In this configuration, the output voltage can be achieved at any voltage as long as V_{sw} is kept below 28 V. This design generates a 75-V output that can supply up to 6 mA, depending on the input voltage.

When the internal power switch of the TPS61040 is closed, current flows from the input, through the primary winding of T1, through the internal switch, to ground. During this time, the voltage at node 1 (V_{sw}) is 0 V. The primary voltage (V_p) and the secondary voltage (V_s) are given by the following equations:

$$V_p = V_{in} = 3 \text{ V} \quad (1)$$

$$V_s = \frac{N_s}{N_p} \times V_p = \frac{5}{1} \times 3 \text{ V} = 15 \text{ V} \quad (2)$$

During this time, D1 is reverse biased, so that the output current is supplied by the output capacitor, C3. When the internal power switch of the TPS61040 is open, current flows from the input, through the primary and secondary of T1, through D1, to the output. During this time, the voltage at node 1 (V_{sw}), the primary voltage (V_p), and the secondary voltage (V_s) can be calculated by the following equations:

$$V_p = \frac{N_p}{N_p + N_s} \times (V_{out} - V_{in}) = \frac{1}{6} \times (75 - 3) = 12 \text{ V} \quad (3)$$

$$V_s = \frac{N_s}{N_p + N_s} \times (V_{\text{out}} - V_{\text{in}}) = \frac{5}{6} \times (75 - 3) = 60 \text{ V} \quad (4)$$

$$V_{\text{sw}} = V_{\text{in}} + V_p = 3 \text{ V} + 12 \text{ V} = 15 \text{ V} \quad (5)$$

The output is regulated to 75 V through the feedback divider that goes back to the FB pin of the TPS61040.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
Low Power Wireless	www.ti.com/lpw	Telephony	www.ti.com/telephony
		Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments
Post Office Box 655303 Dallas, Texas 75265