

# Meet Airline Restrictions with Power-path Control for Dual Batteries




Thomas Regan

With the Federal Aviation Administration restricting the size of batteries allowed on airplanes, it can be challenging to design applications with batteries down to 100 Wh. Some companies design applications using two small batteries instead of one to meet the regulations, but having two batteries often requires the implementation of redundant or duplicate power supplies, which increases power-path design complexity.

In this article, I will present a simple yet effective configuration to share the load current between multiple power supplies or batteries using two TI LM74700-Q1 ideal diode controllers. This configuration enables you to use multiple batteries or power supplies in your systems and is appropriate for applications such as oxygen concentrators, laptops and portable oscilloscopes.

For systems that include multiple batteries, the load-sharing configuration shown in [Figure 1](#) can dramatically increase battery life because each battery supplies only half of the total load current at a time.

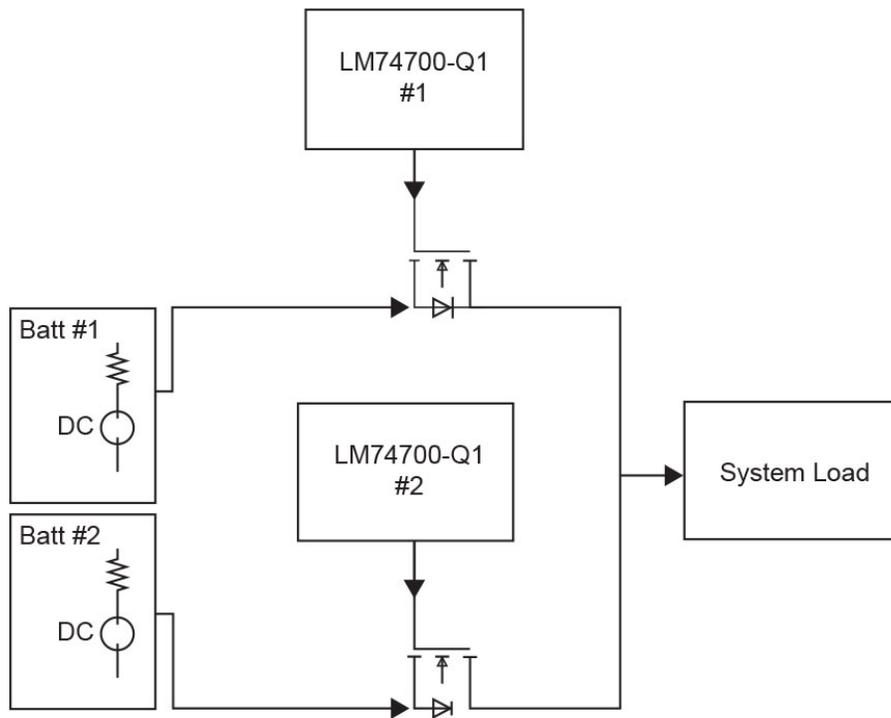

**Figure 1. A system block diagram with multiple batteries**

Supplying only half of the total load current reduces the  $I^2R$  across the batteries' internal impedance by a factor of 2, as shown in Equations 1 and 2:


$$I_{load}^2 R > \left(\frac{I_{load}}{2}\right)^2 R + \left(\frac{I_{load}}{2}\right)^2 R$$

$$I_{load}^2 > \frac{I_{load}^2}{2}$$

### Design verification

When implementing multiple batteries in a system, you cannot assume that two batteries that seem the same are exact copies of each other. They may have different internal impedances or discharge at different rates, which may cause backfeeding or a battery that sources no current. Using the LM74700-Q1 enables each battery to source current proportional to its voltage.

To illustrate this capability, [Figure 2](#) shows the current draw from two 9-V batteries sourcing a constant current load. One battery was new and the other had been partially drained.

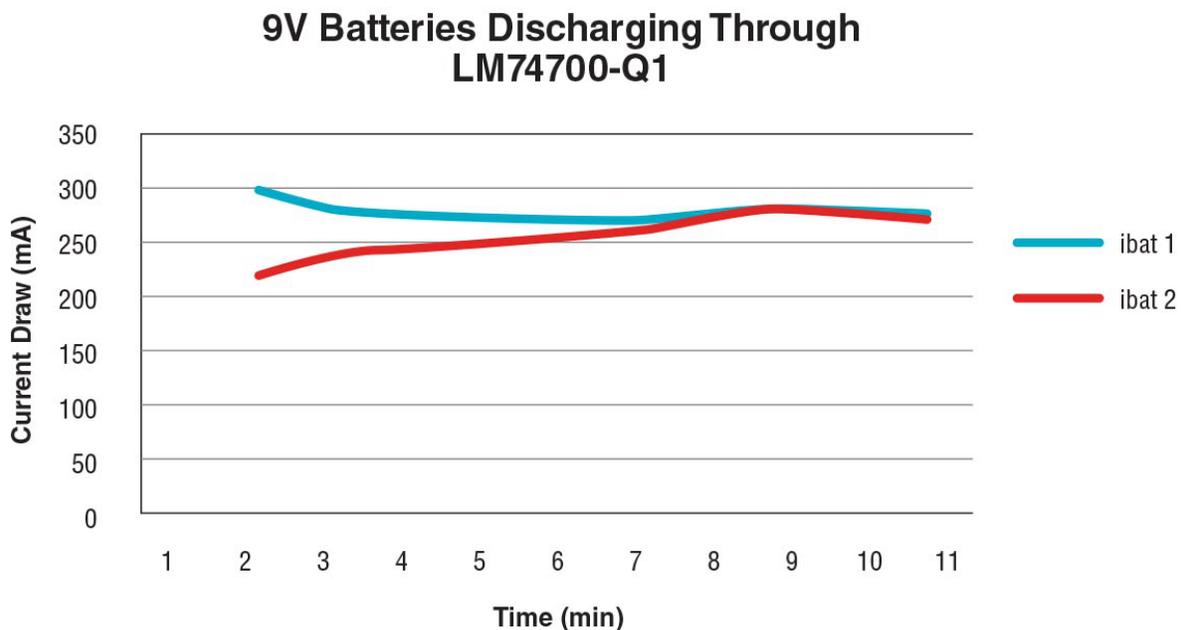

**Figure 2. Current draw from two 9-V batteries**

As you can see in [Figure 2](#), the higher-voltage battery sources slightly more current than the lower charged battery. Then, as the higher-voltage battery discharges, its voltage lowers such that it converges with the second battery. Both batteries then begin to supply approximately the same amount of current to the load.

### Design considerations

The LM74700-Q1 has an integrated charge pump, which enables the LM74700-Q1 to control N-channel field-effect transistors (FETs) that see as much as 65 V<sub>DC</sub> across them. The charge pump is able to fully saturate the FETs with a gate voltage up to 15 V above the source.

Implementing an ideal diode controller that uses N-channel FETs as opposed to P-channel FETs is a good fit for battery-powered systems (or any efficiency-driven system). An N-channel FET will typically have a lower  $R_{DS(on)}$ , a smaller package and a lower gate-charge threshold than a typical P-channel FET with similar voltage ratings. Having a lower  $R_{DS(on)}$  FET will further reduce  $I^2R$  losses in a system's power path, and a lower gate-charge threshold will enable the FETs to turn on and off more quickly.


To minimize losses and optimize the transient response, proper FET selection is important. Using a LM74700-Q1 ideal diode controller greatly reduces DC conduction losses compared to losses when using a Schottky diode or even P-channel FET implementations. There are a few key parameters to consider when selecting the right N-channel FET for your design, however. If you need the FETs to toggle on and off quickly, then inspect the gate charge ( $Q_g$ ) parameter specified on most TI N-channel FET data sheets. The relationship between the  $Q_g$  and gate-drive current ( $I_g$ ) to the time it takes to toggle a FET on and off can be seen in Equations 3 and 4:

$$t_{on} = \frac{Q_g}{I_{gate\ source}} + t_{hysteresis}$$

$$t_{off} = \frac{Q_g}{I_{gate\ sink}} + t_{hysteresis}$$

The gate-drive current for the LM74700 is 11 mA and the gate-sink current is 2,370 mA. Having such a high  $I_g$  can lead to a faster response time for a system, whether it is a turnon and turnoff command or a reaction to a higher voltage detected on the output. A fast transition ensures that your batteries are protected from any overvoltage events on the output and minimal holdup capacitance is required when transitioning between battery power and a DC power source.

In order to have a balanced current draw on multiple power supplies used in a system, an equivalent resistance in the discharge path is important, as shown in [Figure 3](#). Having a difference in voltage or resistance between batteries will affect the ability to equally source current.

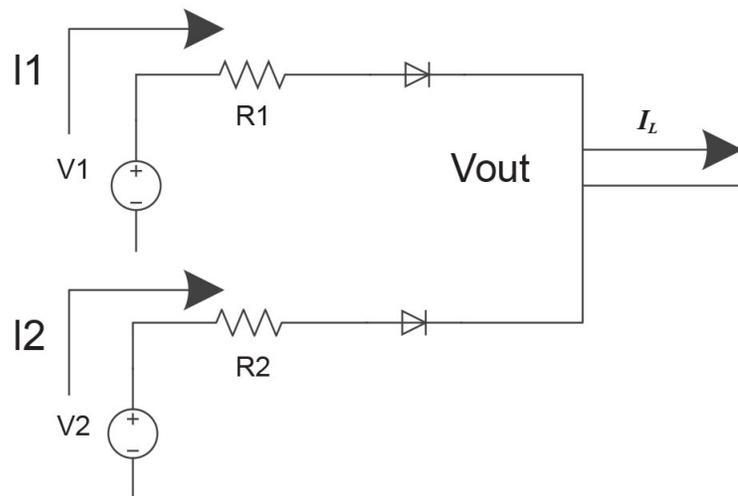

**Figure 3. Schematic of an equivalent resistance in the discharge path**

As you can see in Equations 5 and 6, even if the same source voltages exist in a system, a difference in series resistance can vary the amount of current they will provide. Consider this possibility when implementing systems with multiple chemistries or ages, as they may have different internal impedances.

$$I_L = I_1 + I_2$$

$$I_L = \frac{V_1 - V_{out}}{R_1} + \frac{V_2 - V_{out}}{R_2}$$

### Conclusion

Using LM74700-Q1 ideal diode controllers to manage the discharge path for systems with multiple batteries or power supplies can provide a simple and effective methodology. An ideal diode controller helps create an efficient and quick reaction path, especially compared to systems using diodes or P-channel FETs in a similar control scheme.

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated