
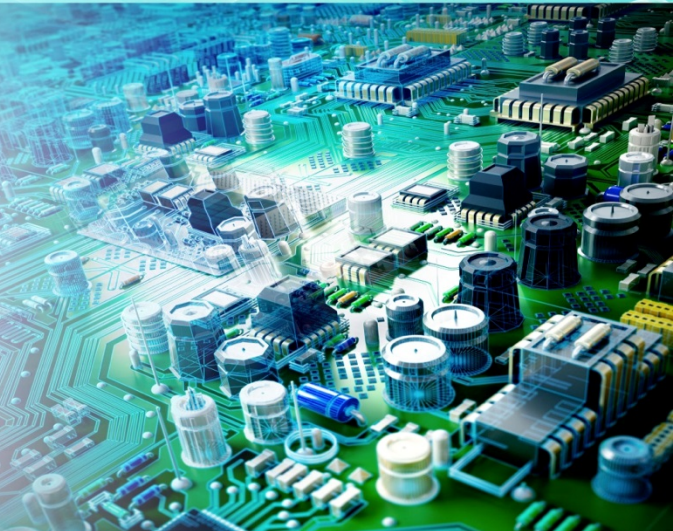


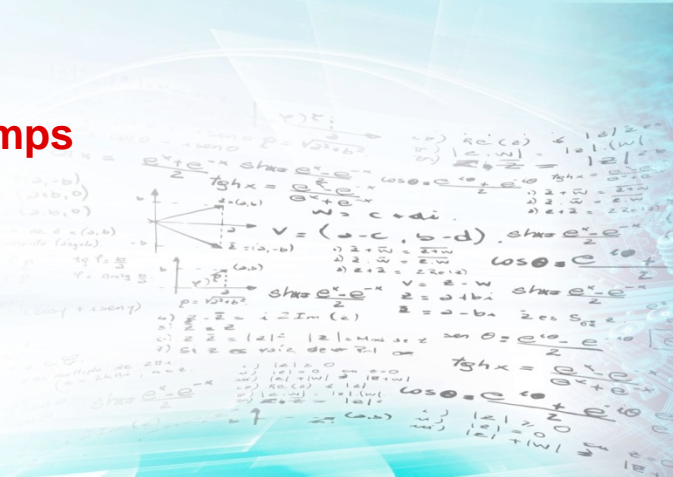

Fully Differential Amplifiers - 2

TIPL 2022

TI Precision Labs: Op Amps



Prepared and Presented by Samir Cherian

Diff-In to Diff-Out: Common-mode Analysis

Assume $V_{ID-} = -V_{ID+} = 0.2V_{PP}$,

$V_{ID\pm_CM} = 0V$, & $V_{OCM} = 2.5V$


At the FDA Output

$$V_{OUT+_CM} = V_{OUT-_CM} = V_{OCM} = 2.5V$$

At the FDA Input, use KCL

$$\frac{(V_{ID\mp_CM} - V_{IN_CM})}{R_G} = \frac{(V_{IN_CM} - V_{OUT\pm_CM})}{R_F}$$

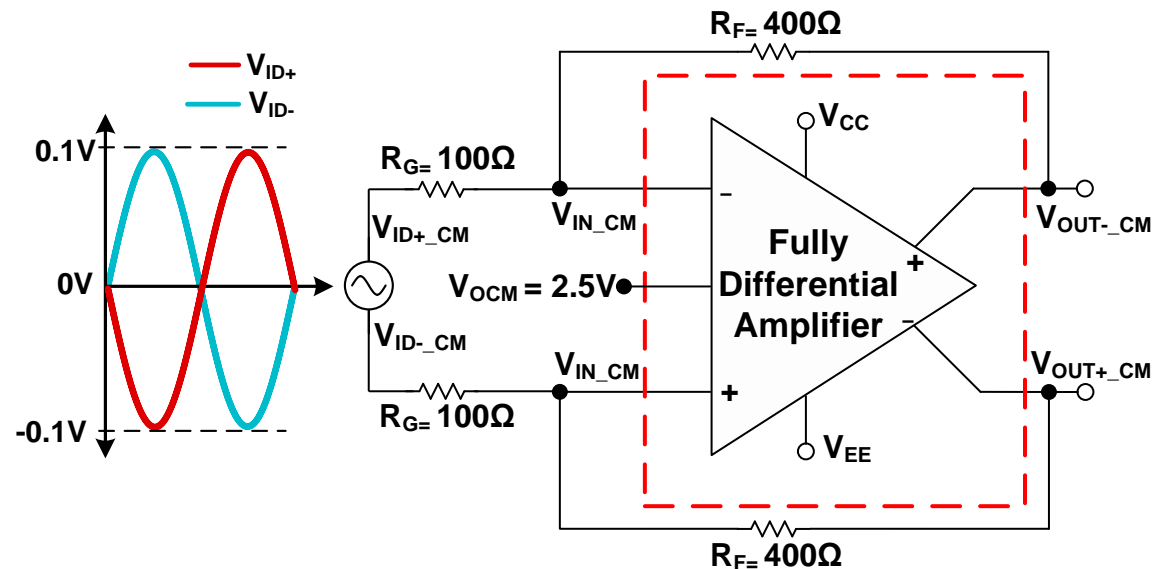
$$V_{IN_CM} = 2.5V \cdot \frac{100\Omega}{(400\Omega + 100\Omega)} = 0.5V$$



Diff-In to Diff-Out: Differential Analysis

Assume $V_{ID-} = -V_{ID+} = 0.2V_{PP}$,

$V_{ID\pm_CM} = 0V$, & $V_{OCM} = 2.5V$

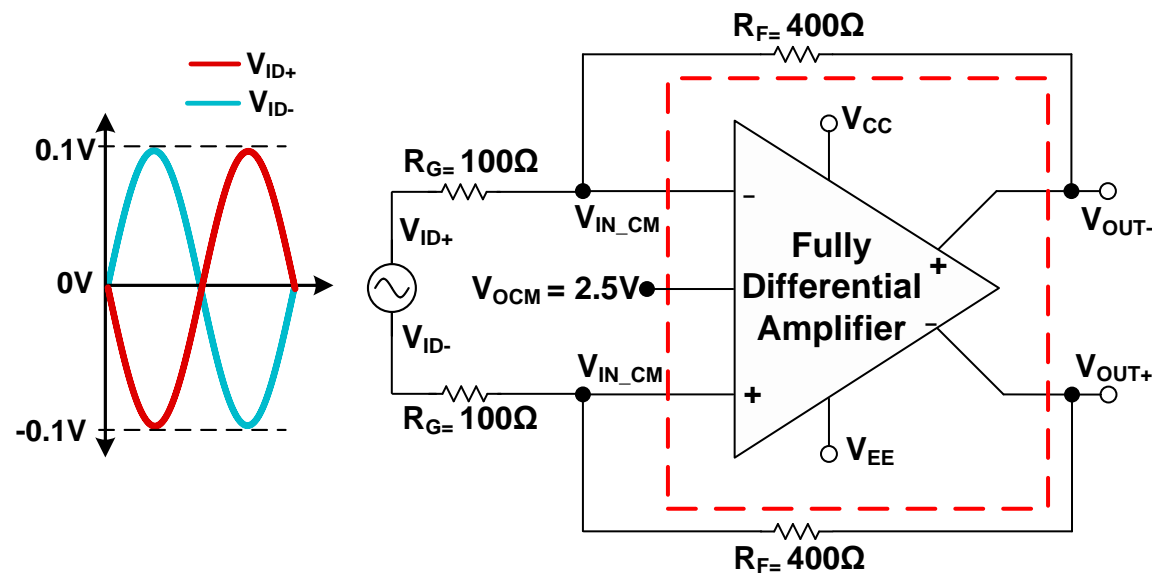

Taking each half of the FDA separately and applying KCL,

$$V_{IN_CM} = \frac{V_{OUT-} + V_{ID+} \left(\frac{R_F}{R_G} \right)}{\left(1 + \frac{R_F}{R_G} \right)}, \text{ and } \textcircled{1}$$

$$V_{IN_CM} = \frac{V_{OUT+} + V_{ID-} \left(\frac{R_F}{R_G} \right)}{\left(1 + \frac{R_F}{R_G} \right)} \textcircled{2}$$

Equating (1) & (2)

$$(V_{OUT-} - V_{OUT+}) = - \left(\frac{R_F}{R_G} \right) \cdot (V_{ID+} - V_{ID-}) \textcircled{3}$$

$$\frac{\Delta V_{OUT}}{\Delta V_{ID}} = - \left(\frac{R_F}{R_G} \right)$$

Diff-In to Diff-Out: Differential + CM Analysis



At the FDA Output

Differential V_{OUT} ,

$$V_{OUT-} = -V_{OUT+} = 4 \times 0.2V_{PP} = 0.8V_{PP}$$

(Differential + CM) V_{OUT} ,

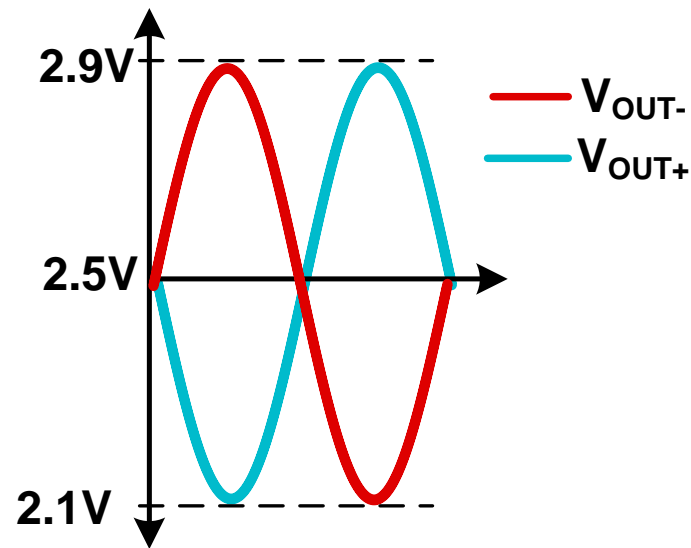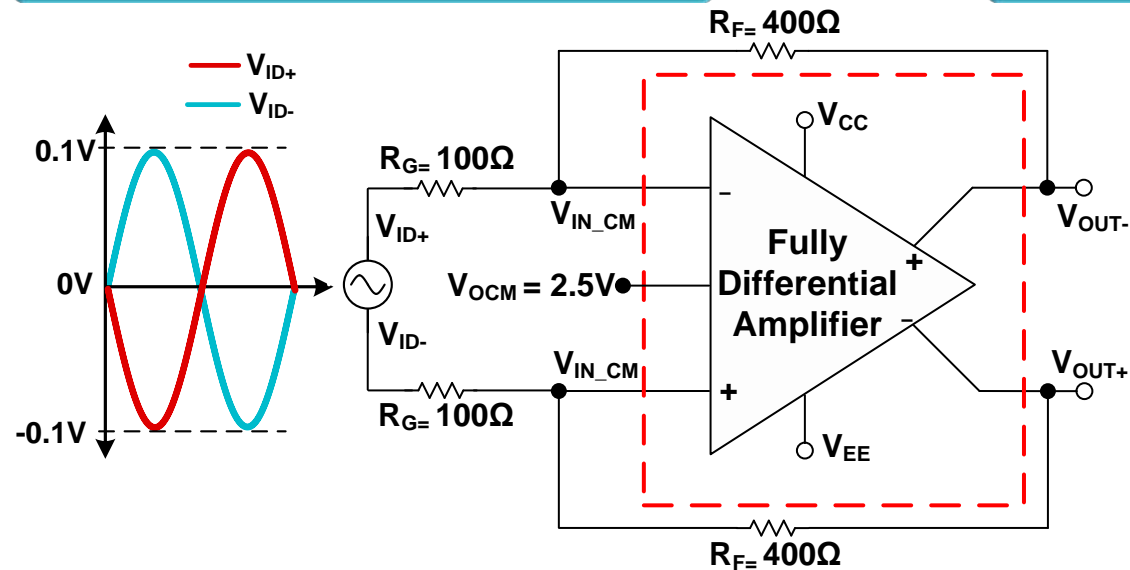
$$V_{OUT-} = 2.5V \pm 0.8V, \text{ and, } V_{OUT+} = 2.5V \mp 0.8V$$





Single-ended-In to Diff-Out: Common-Mode Analysis

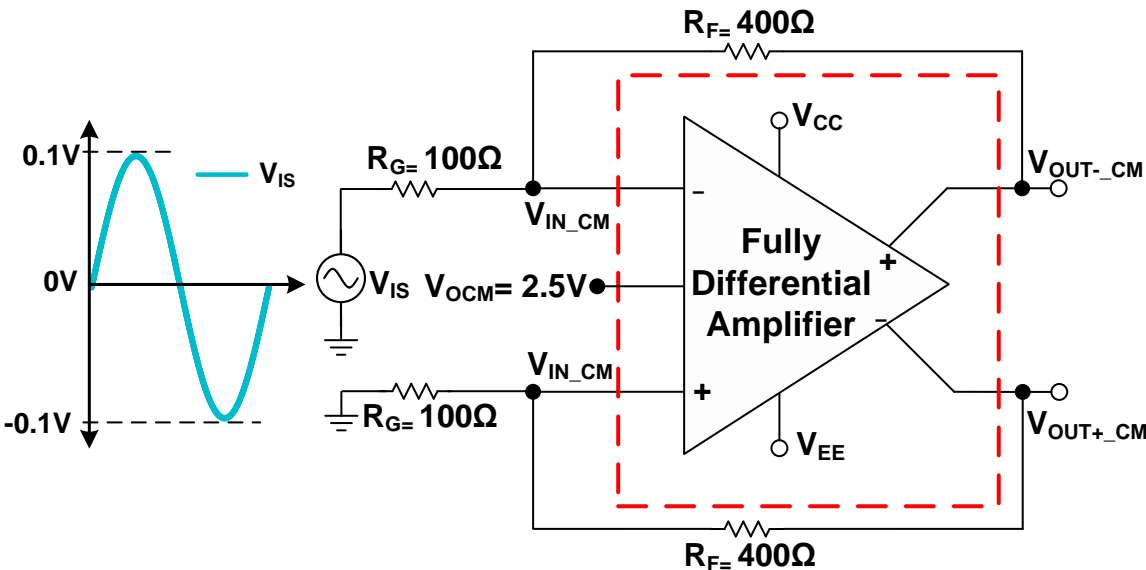Assume $V_{IS} = 0.2V_{PP}$, $V_{IS_CM} = 0V$,
& $V_{OCM} = 2.5V$



At the FDA Output

$$V_{OUT+_{CM}} = V_{OUT-_{CM}} = V_{OCM} = 2.5V$$


**At the FDA Input, use KCL on
non-driven input**

$$\frac{(V_{OUT+_{CM}} - V_{IN_CM})}{R_F} = \frac{(V_{IS_CM} - V_{IN_CM})}{R_G}$$

$$V_{IN_CM} = 2.5V \cdot \frac{100\Omega}{(400\Omega + 100\Omega)} = 0.5V$$

Single-ended-In to Diff-Out: Differential Analysis

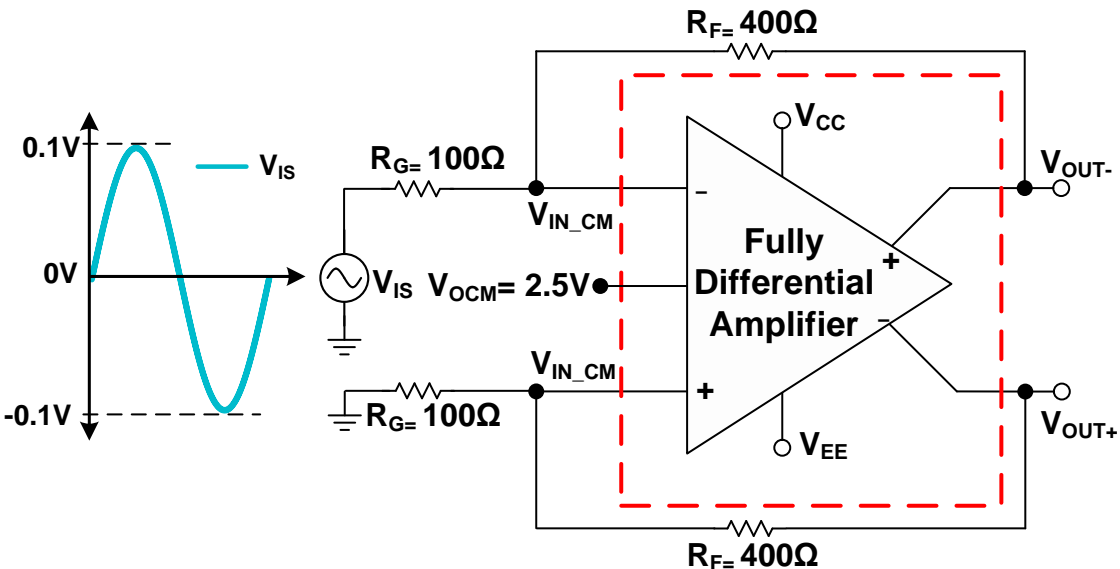Assume $V_{IS} = 0.2V_{PP}$, $V_{IS_CM} = 0V$,
& $V_{OCM} = 2.5V$



First find the Input Common-mode,

$$V_{IN_CM} = \frac{V_{OUT+}}{\left(1 + \frac{R_F}{R_G}\right)} \quad \text{1}$$

Use KCL on the driven half,

$$\frac{V_{IS} - V_{IN_CM}}{R_G} = \frac{V_{IN_CM} - V_{OUT-}}{R_F}$$




$$V_{IS} \left(\frac{R_F}{R_G}\right) = V_{IN_CM} \left(1 + \frac{R_F}{R_G}\right) - V_{OUT-} \quad \text{2}$$

From (1) & (2)

$$V_{IS} \left(\frac{R_F}{R_G}\right) = \frac{V_{OUT+}}{\left(1 + \frac{R_F}{R_G}\right)} \left(1 + \frac{R_F}{R_G}\right) - V_{OUT-}$$


$$\frac{V_{OUT-} - V_{OUT+}}{V_{IS}} = \frac{\Delta V_{OUT}}{V_{IS}} = -\left(\frac{R_F}{R_G}\right)$$

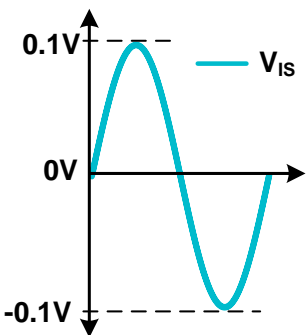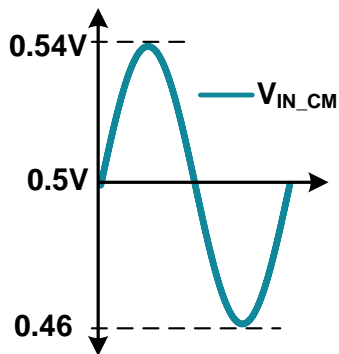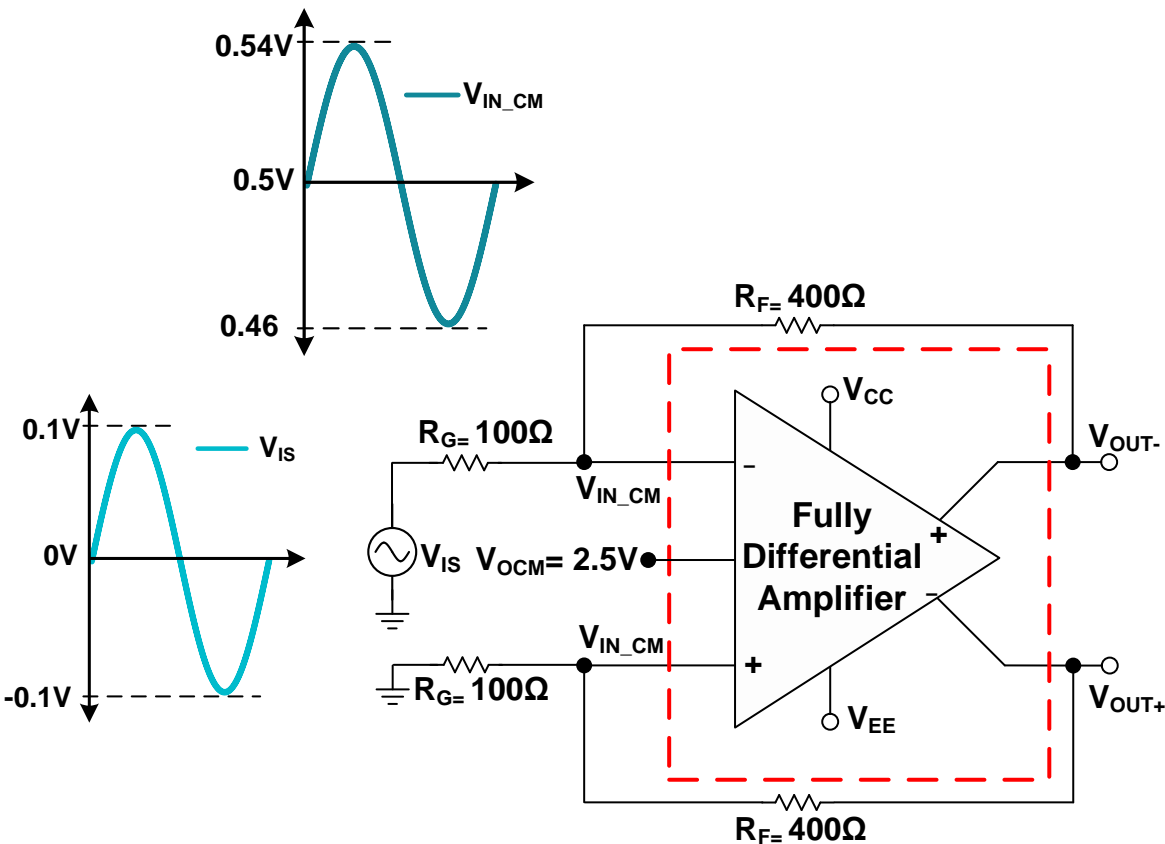Single-ended-In to Diff-Out: Differential + CM analysis




$$V_{IN_CM}(DC) = \frac{V_{OCM}}{1 + \frac{R_F}{R_G}} = \frac{2.5V}{5} = 0.5V$$
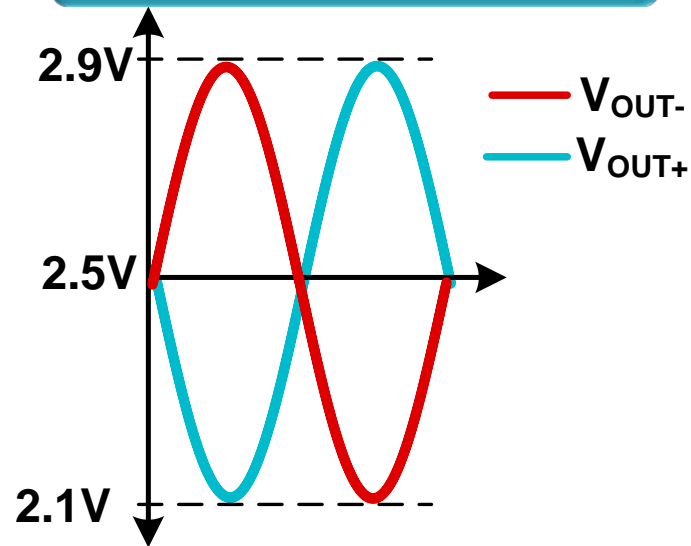
$$V_{IN_CM}(AC) = \frac{V_{OUT\pm}}{1 + \frac{R_F}{R_G}} = \frac{400mV_{PP}}{5} = 80mV_{PP}$$



Bipolar Input Signals with Single-sided Supply Voltage

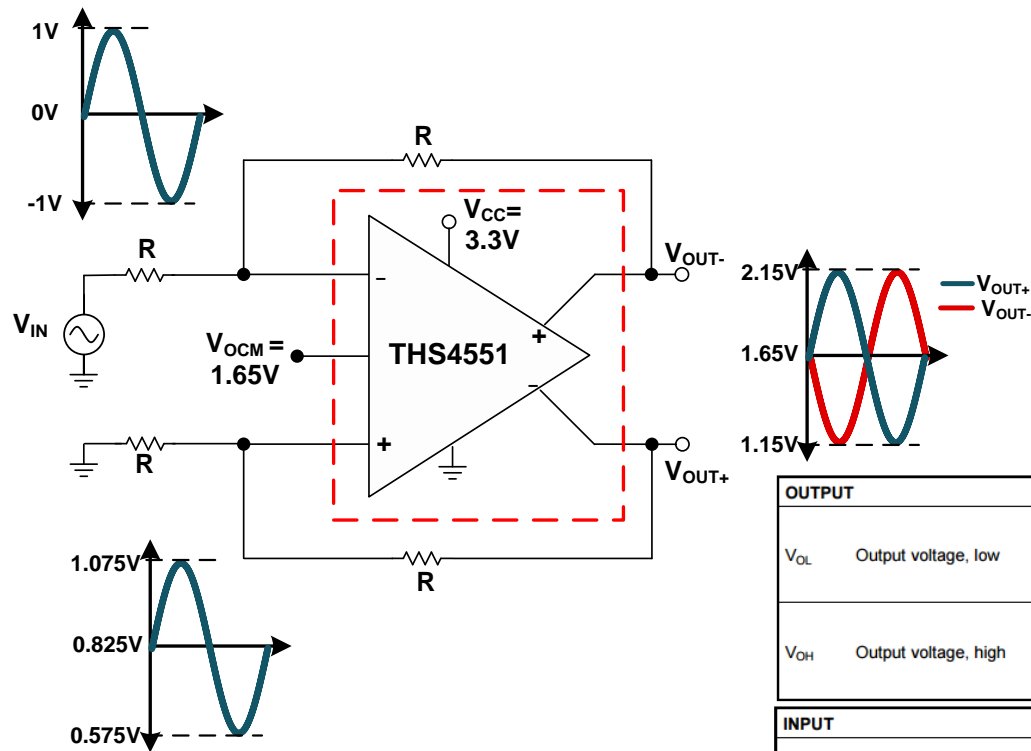- $A_V = 1V/V$, $V_{OCM} = 1.65V$, $V_S = 3.3V$
- Input = $2V_{PP}$ around GND



OUTPUT					
V_{OL}	Output voltage, low	$T_A = 25^\circ\text{C}$	$(V_{S-}) + 0.2$	$(V_{S-}) + 0.21$	V
		$T_A = -40^\circ\text{C to } +125^\circ\text{C}$	$(V_{S-}) + 0.2$	$(V_{S-}) + 0.22$	
V_{OH}	Output voltage, high	$T_A = 25^\circ\text{C}$	$(V_{S+}) - 0.21$	$(V_{S+}) - 0.2$	V
		$T_A = -40^\circ\text{C to } +125^\circ\text{C}$	$(V_{S+}) - 0.22$	$(V_{S+}) - 0.2$	

INPUT					
Common-mode input, low	> 87-dB CMRR at input range limits	$T_A = 25^\circ\text{C}$	$(V_{S-}) - 0.2$	$(V_{S-}) - 0.1$	V
		$T_A = -40^\circ\text{C to } +125^\circ\text{C}$	$(V_{S-}) - 0.1$	V_{S-}	
Common-mode input, high	> 87-dB CMRR at input range limits	$T_A = 25^\circ\text{C}$	$(V_{S+}) - 1.2$	$(V_{S+}) - 1.1$	V
		$T_A = -40^\circ\text{C to } +125^\circ\text{C}$	$(V_{S+}) - 1.3$	$(V_{S+}) - 1.2$	



©Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com


Fully Differential Amplifiers - 2

Exercises

TI Precision Labs: Op Amps

Questions

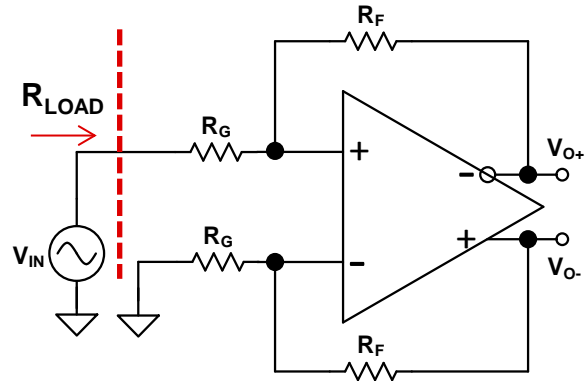
1. How would you AC couple a single-ended input source to an FDA?
2. What is the load seen by the single-ended input source? (HINT: It is not R_G). Assume that both the $V_{OCM} = 0V$ and the input signal common-mode is $0V$.



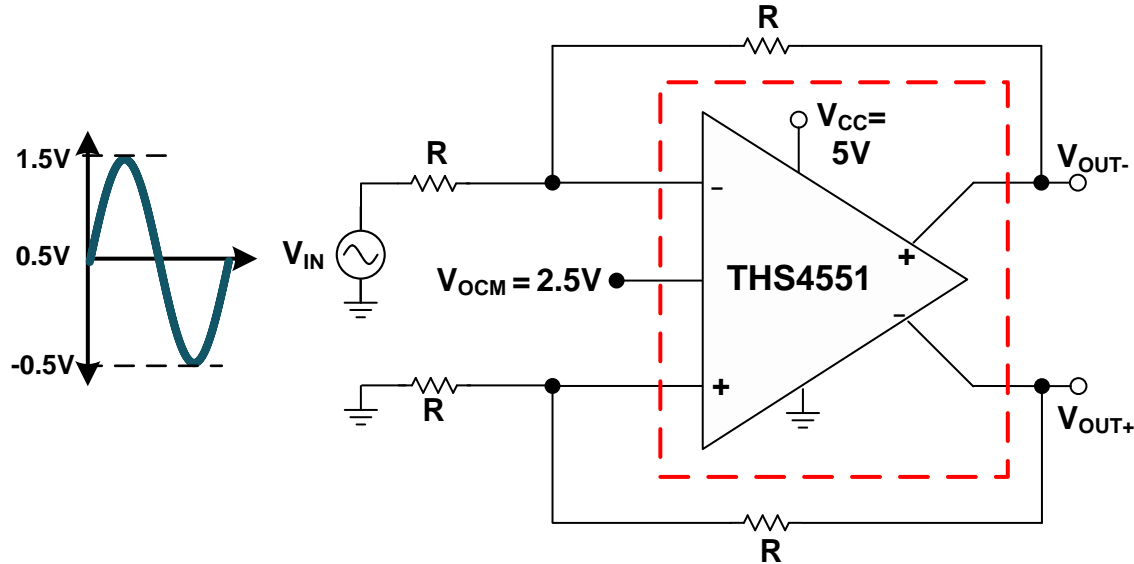
3. For the circuit shown below what is the,

- Output signal (differential and common-mode), and
- Input signal (differential and common-mode)

(HINT: The signal input common-mode is 0.5V while the non-driven input is at GND.)



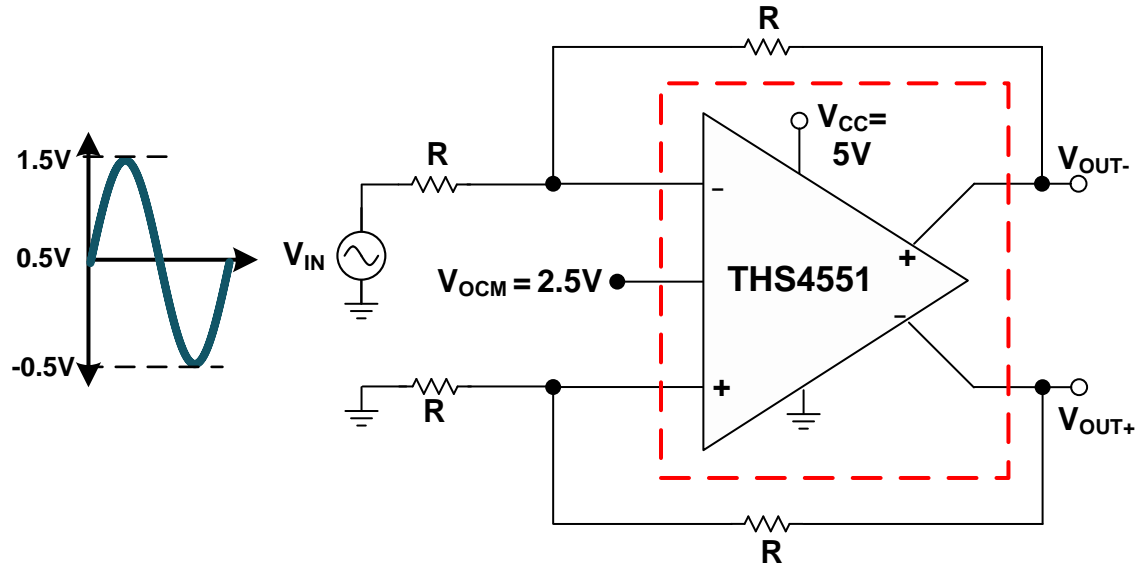
4. In the previous question how would you solve the problem of each output having a different common-mode (2.75V and 2.25V)



Answers

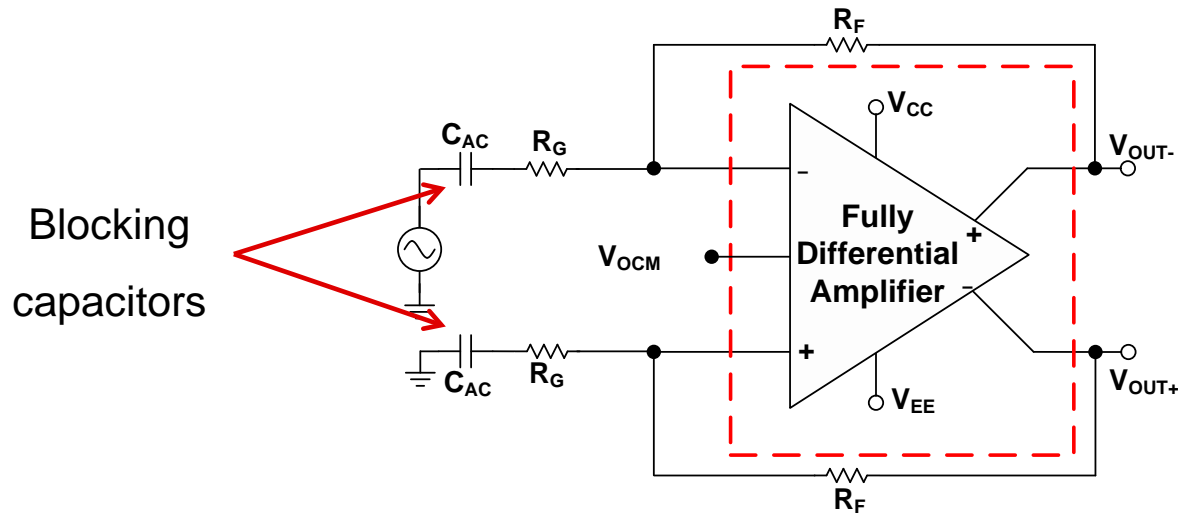1. How would you AC couple a single-ended input source to an FDA?

Answer: This circuit configuration is useful when the DC and low-frequency signal content can be ignored. If the single-ended input common-mode is not GND, then using this circuit configuration precludes the need for a 2nd opamp on the un-driven FDA side, to match the common-mode of the input signal.



2. What is the load seen by the single-ended input source? (HINT: It is not R_G). Assume that both the $V_{OCM} = 0V$ and the input signal common-mode is $0V$.

Answer: The load is not R_G because the amplifiers input common-mode is not fixed but is a function of the signal input and the feedback network.

$$V_{CM} = V_{O-} \left(\frac{R_G}{R_G + R_F} \right) \rightarrow (1) \text{ Using KCL on the bottom half of FDA}$$


$$\frac{V_{O-}}{V_{IN}} = \frac{1}{2} (\text{SignalGain}) = \frac{1}{2} \left(\frac{R_F}{R_G} \right) \rightarrow \text{By definition}$$

$$\Rightarrow V_{O-} = \frac{1}{2} \left(\frac{R_F}{R_G} \right) V_{IN} \rightarrow (2)$$

$$I_{LOAD} = \frac{V_{IN} - V_{CM}}{R_G} = \frac{V_{IN} - \frac{1}{2} \left(\frac{R_F}{R_G} \right) V_{IN} \left(\frac{R_G}{R_G + R_F} \right)}{R_G}$$

$$R_{LOAD} = \frac{V_{IN}}{I_{LOAD}} = \frac{R_G}{\left(1 - \frac{1}{2} \left(\frac{R_F}{R_G + R_F} \right) \right)}$$

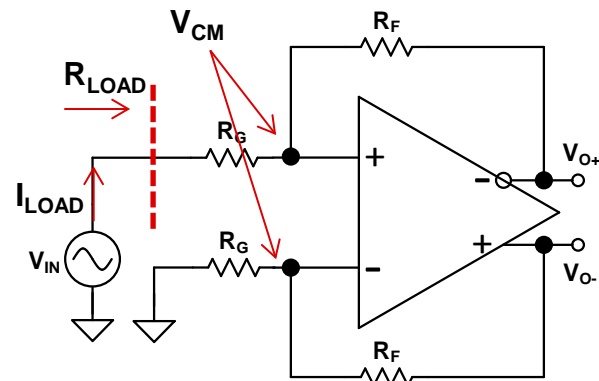Divide R_G by this factor to find the load seen by the signal source




3. For the circuit shown below what is the,
- Output signal (differential and common-mode), and
 - Input signal (differential and common-mode)

Answer: First lets start with the common-mode analysis

- The input common-mode is 0.5V and 0V respectively.
- The difference in common-mode is amplified by the signal gain and manifests itself as a differential signal centered on the output common-mode of 2.5V.
- The common-mode for V_{OUT-} is therefore equal to 2.25V and $V_{OUT+} = 2.75V$
- Also the input common-mode, $V_{CM} = \frac{1}{2} V_{OUT+} = 1.375V$
- The mathematical derivation for this is shown on the next slide.

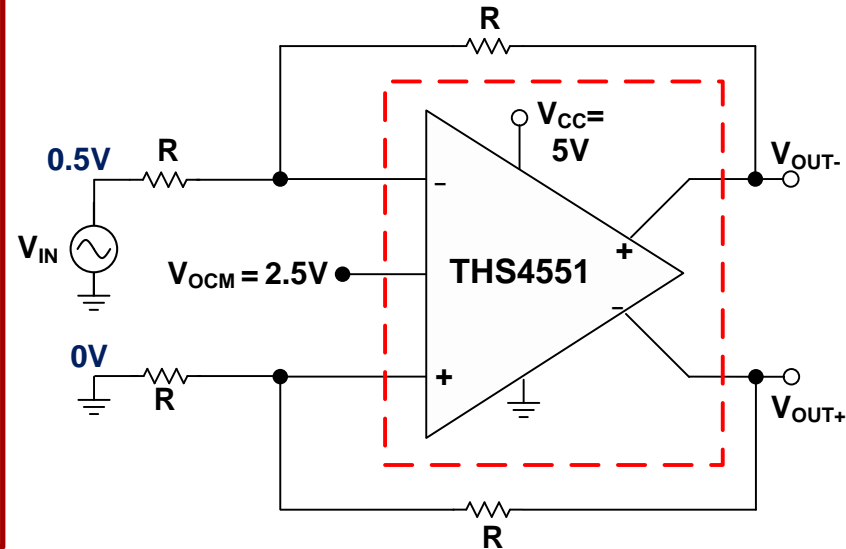**Intuitive derivation of
input and output
common-mode**



$$V_{CM} = \frac{1}{2}(V_{OUT+}) \rightarrow \text{Simple resistive divider on un-driven side} \quad \textcircled{1}$$

$$V_{OCM} = 2.5V = \left(\frac{V_{OUT+} + V_{OUT-}}{2} \right) \rightarrow \text{By definition} \Rightarrow V_{OUT-} = (2V_{OCM} - V_{OUT+}) \quad \textcircled{2}$$

$$\frac{0.5 - V_{CM}}{R} = \frac{V_{CM} - V_{OUT-}}{R} \rightarrow \text{Using KCL on the driven side}$$

$$\Rightarrow \frac{0.5V - \frac{1}{2}(V_{OUT+})}{R} = \frac{\frac{1}{2}(V_{OUT+}) - (2V_{OCM} - V_{OUT+})}{R}$$

$$\Rightarrow \left(\frac{1}{2} \right) V_{OUT+} + \left(\frac{1}{2} \right) V_{OUT+} + V_{OUT+} = 0.5V + 5V$$


$$\Rightarrow 2V_{OUT+} = 5.5V \Rightarrow V_{OUT+} = 2.75V$$

From $\textcircled{2}$ and $\textcircled{1}$ respectively -

$$V_{OUT-} = (2V_{OCM} - V_{OUT+}) = (5V - 2.75V) = 2.25V$$

$$V_{CM} = \frac{1}{2}(V_{OUT+}) = \frac{1}{2}(2.75) = 1.375V$$

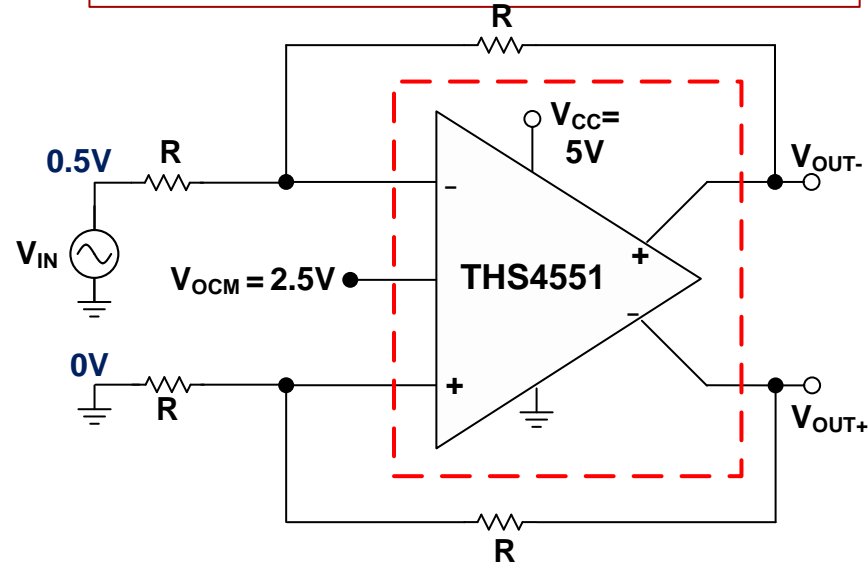
**Mathematical derivation of input
and output common-mode**



Answer: Now on to differential analysis

- Input sine-wave is $2V_{PP}$. FDA gain is $1V/V$. So each output will swing $1V_{PP}$ on each outputs common-mode of $2.75V$ and $2.25V$.
- The input common-mode will swing $0.5V_{PP}$ on the common-mode of $1.375V$.
- The results are shown below. Mathematical derivation is left as an exercise. Use similar concepts as shown for the common-mode.

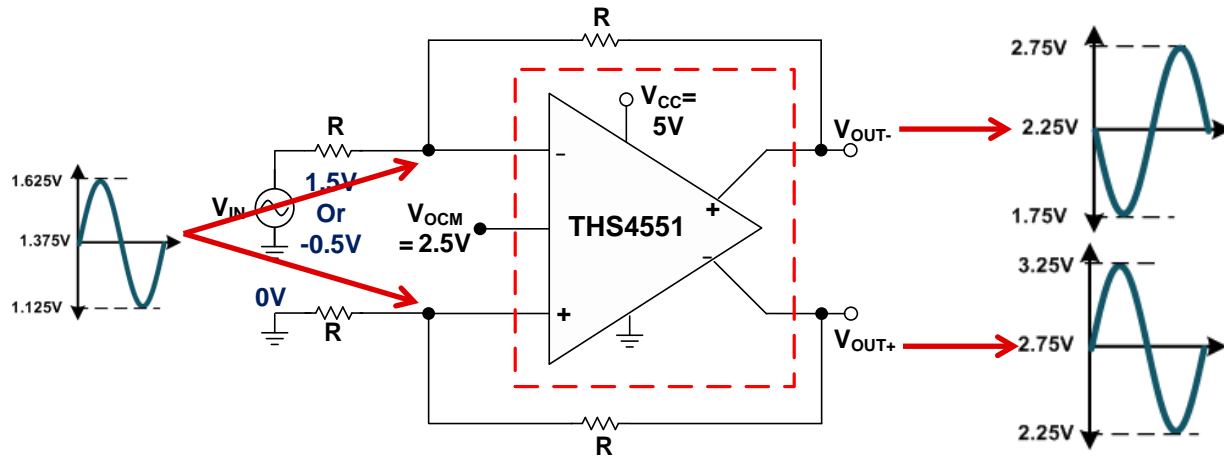**Intuitive derivation of input
and output differential-mode**



4. In the previous question how would you solve the problem of each output having a different common-mode (2.75V and 2.25V)

Answer: Use a 2nd single-ended opamp to drive 0.5V into the un-driven side. It is important to use a wideband amplifier that has a bandwidth on par with the FDA used. (Try the OPA836)

