



TI Webinar Series

# Using Isolated Gate Drivers for MOSFET, IGBT and SiC applications

Nagarajan Sridhar

Strategic Marketing Manager – New Products and Roadmap

High Power Driver Solutions, HVPS, SVA


Texas Instruments

# This webinar is intended to provide

- ✓ An understanding of an isolated driver
- ✓ A guideline on how to and when to identify an isolated driver and the type of driver depending on the power switch and application

X This webinar is not intended to discuss details on isolation technology – That will be discussed in a webinar on October 20<sup>th</sup>, 2017.

# Motivation in power management

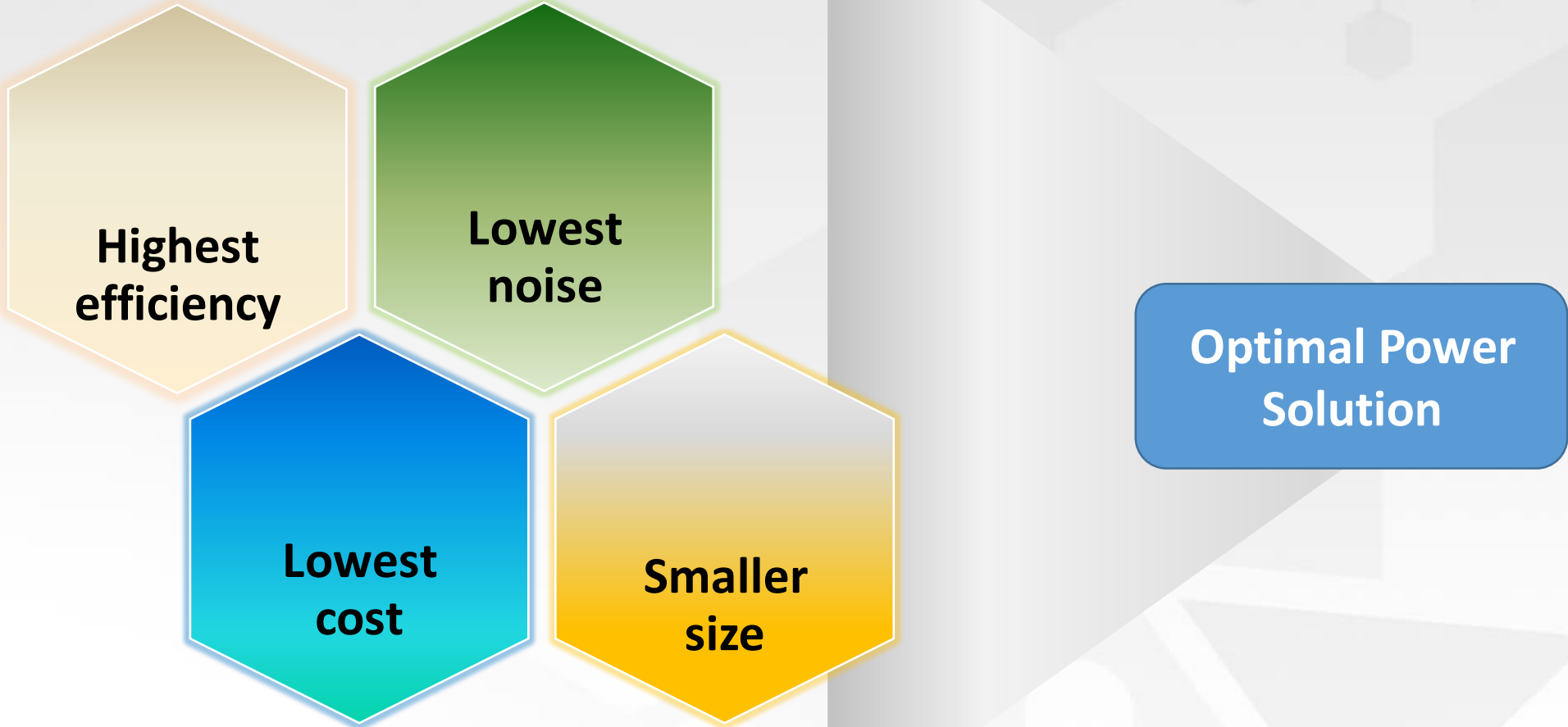

# Agenda

- Isolation:
  - Definition, why isolate, how to isolate and applications
- Concept of power electronics and definition of a gate driver
- Types of gate driver
- Motivation for an isolated gate driver
  - Walking through an example application
- Types of isolation techniques, terminology and standards
- Isolated gate driver requirements
- MOSFET vs IGBT isolated gate driver and applications
- Wide band gap semiconductors
  - Value of SiC and gate driver requirements
- More information on TI isolated gate driver family and isolation

# What is Isolation

A means of transporting data & power between a high voltage and a low voltage circuit while preventing:


- Hazardous DC or
- Uncontrolled transient current from flowing in between the two circuits.

# Why isolate?

- To protect from and safely withstand high voltage surges that would damage equipment or harm humans
- To protect expensive controllers – intelligent systems
- To tolerate large ground potential differences and disruptive ground loops in circuits that have high energy or are separated by large distance
- To communicate reliably with high side components in high-voltage high performance solutions

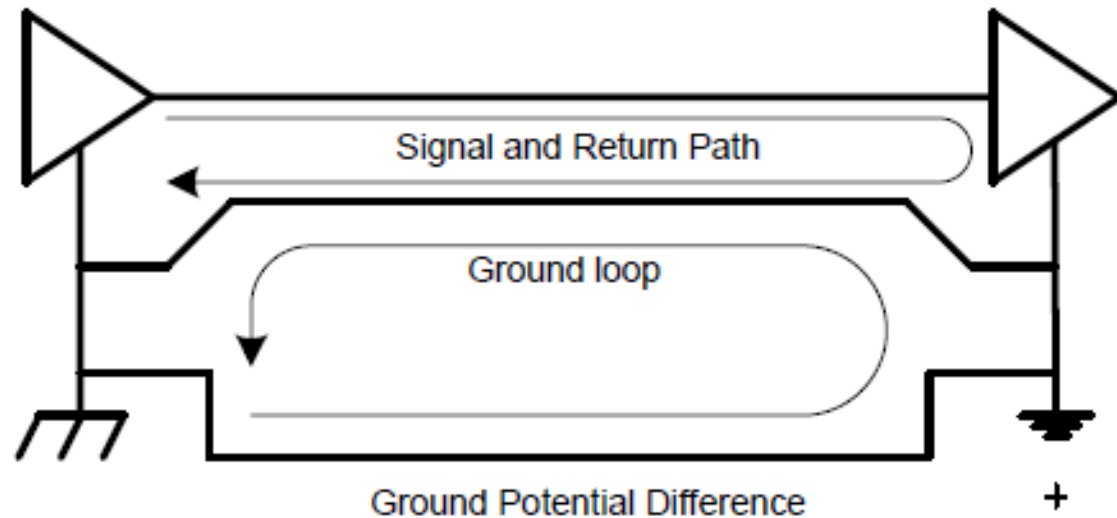
# When to use isolation?

- ❖ More than one conductive path between two circuits creates a ground-loop
- ❖ Multiple ground paths can lead to unintended compensation currents


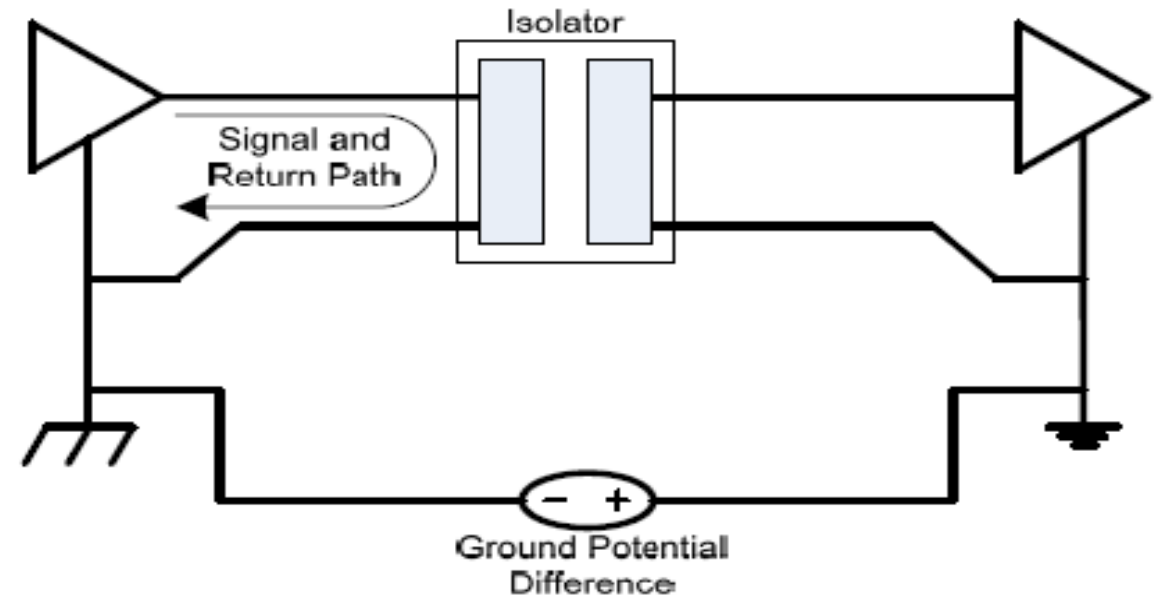
# How to isolate?

- ❖ Ground loops can be broken by
  - Disconnecting the grounds
  - Common-mode chokes
  - Frequency selective grounding
  - Differential amplifiers
  - Galvanic isolators



***Only galvanic isolation provides protection for very large potential differences***



# Applications

*For switched-mode power electronic applications involved in high-power and high-voltage conversion*



**Factory automation**



**Enterprise power & telecom**



**Automotive**



**Motor drive and control**




**Smart grid**



**Other industrials**

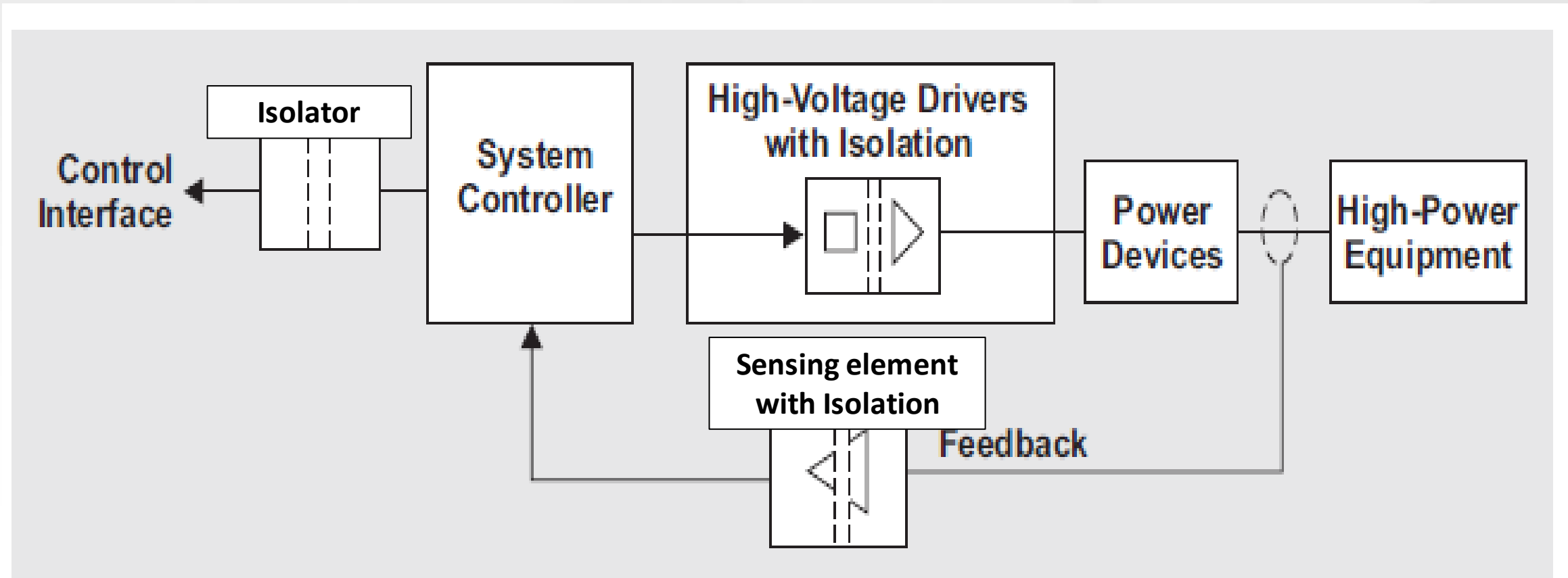
# A conceptual power drive system block diagram

*Electronic devices and integrated circuits (ICs) used for isolation are called isolators*


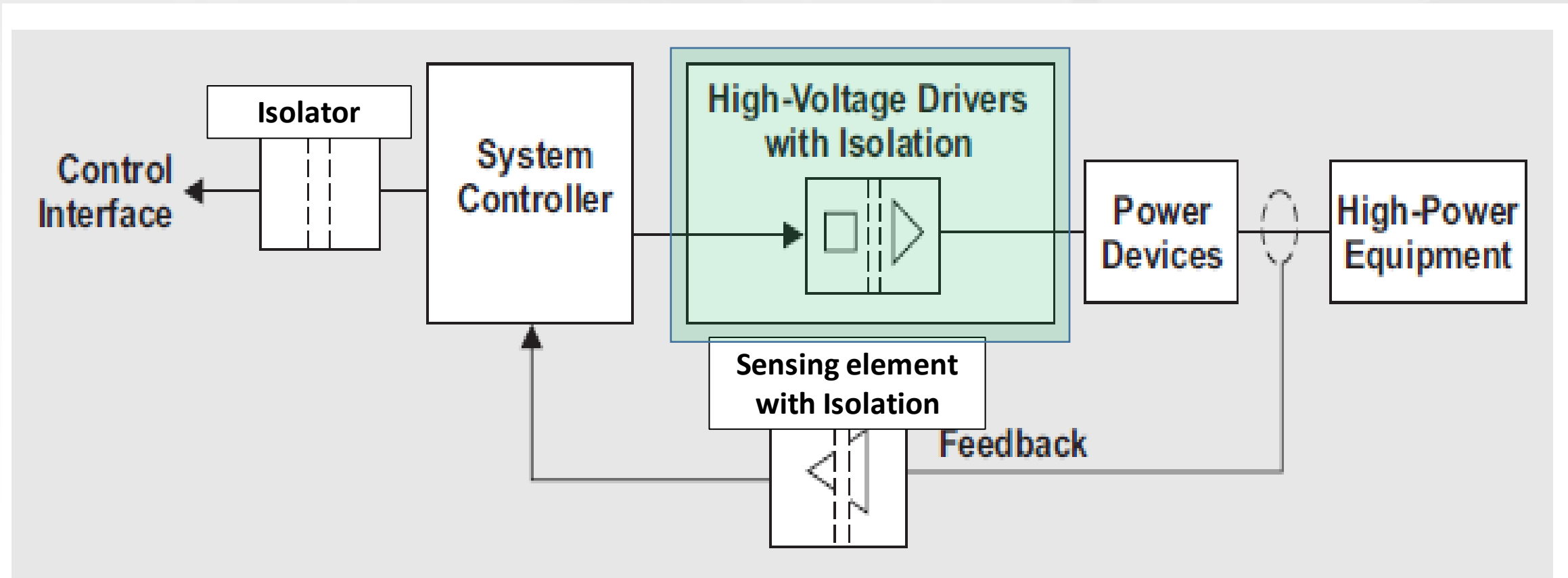
# A conceptual power drive system block diagram


*Electronic devices and integrated circuits (ICs) used for isolation are called isolators*



Let us take a step back and understand

- The concept of power electronics
- What is a gate driver
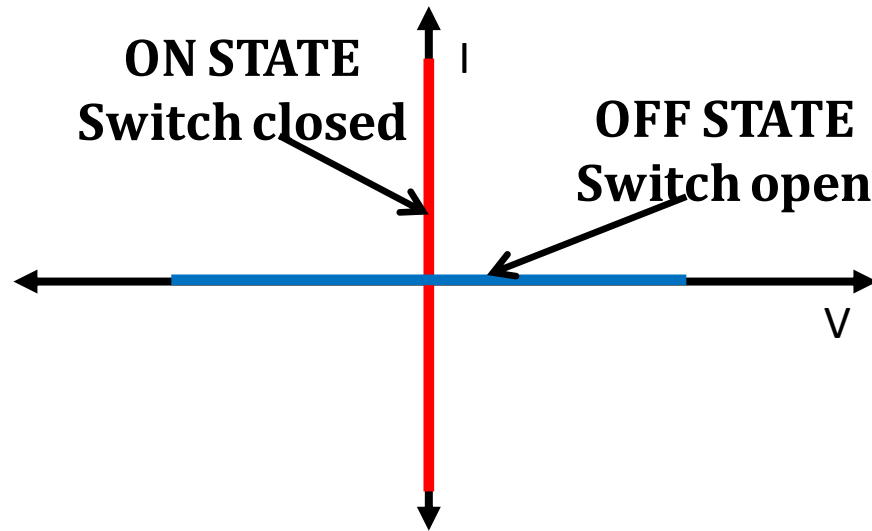
# 'Power Switch' - Fundamental Component in Power Electronics




**Ideal switch:**  
Blocking loss,  $P_{OFF} = V_{OFF} \times I_{OFF} = 0$   
Conduction loss,  $P_{ON} = V_{ON} \times I_{ON} = 0$   
4 quadrant operation

**Power Switches control flow of current in power electronic circuits by operating in 2 states (ON/OFF)**



|        |  |      |  |           |                      |
|--------|--|------|--|-----------|----------------------|
| MOSFET |  | IGBT |  | ON<br>I ↓ | OFF<br>↓<br>+ V<br>- |
|--------|--|------|--|-----------|----------------------|

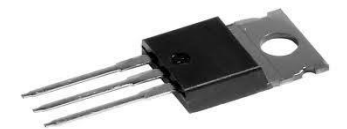


- GATE (G) terminal controls ON/OFF status of switch
- Modern Power Electronics dominated by Switch Mode Power conversion

# How does GATE terminal of a Power Switch Work ?
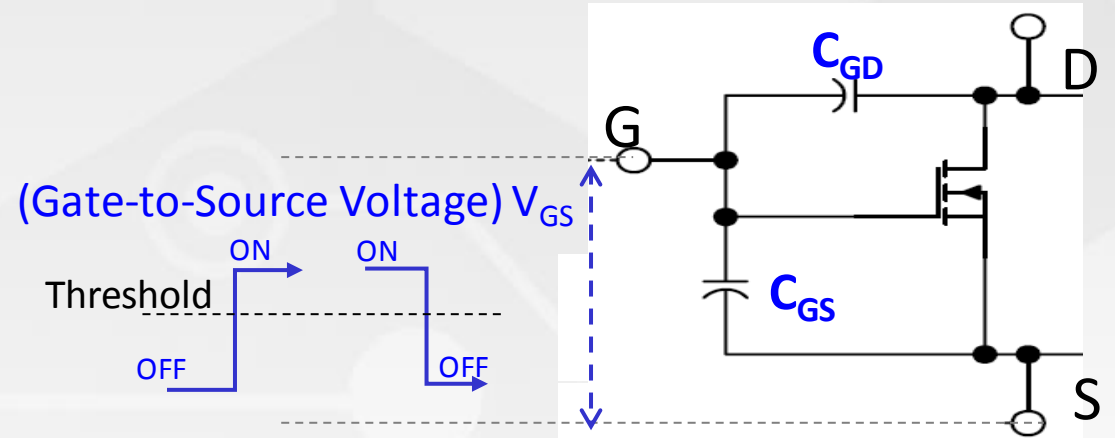
## Let's take example of a power MOSFET

- GATE terminal controls ON/OFF state of MOSFET
- $V_{GS}$  = Voltage Between Gate & Source
- To turn ON: Apply a positive voltage,
- $V_{GS} >$  Threshold level
- To turn OFF:  $V_{GS} <$  Threshold level
- GATE is a capacitive input, high-impedance terminal
- 2 parasitic capacitors inside MOSFET internal structure ( $C_{GS}$ ,  $C_{GD}$ )



Now, about Gate Drivers....


# What is a Gate Driver

*It is a power amplifier that accepts a low-power input from a controller IC and produces the appropriate high-current gate drive for a power MOSFET*

Gate Driver device applies voltage signal ( $V_{GS}$ ) between Gate (G) & Source (S) of power MOSFET, while providing a high-current pulse


- ➔ To charge/discharge  $C_{GS}$ ,  $C_{GD}$  QUICKLY
- ➔ To switch ON/OFF power MOSFET QUICKLY

## Gate Driver

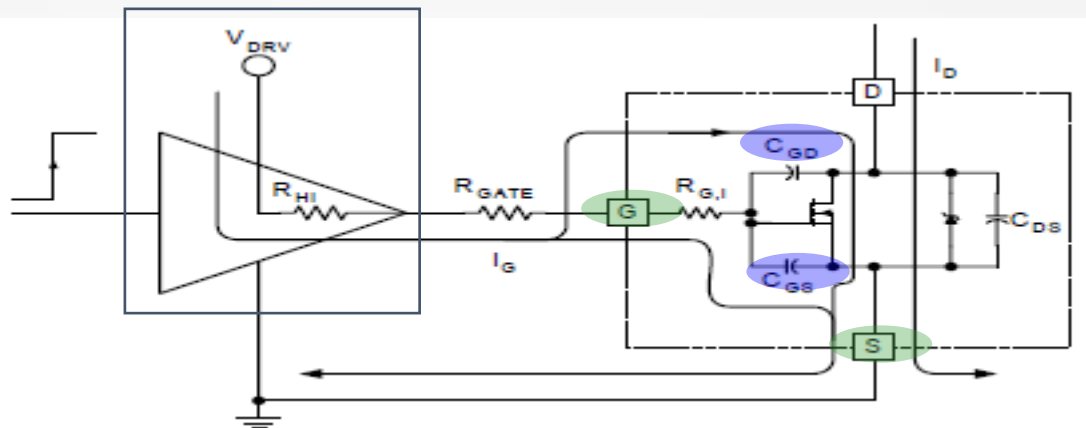

Switch Turn-On

## Gate Driver

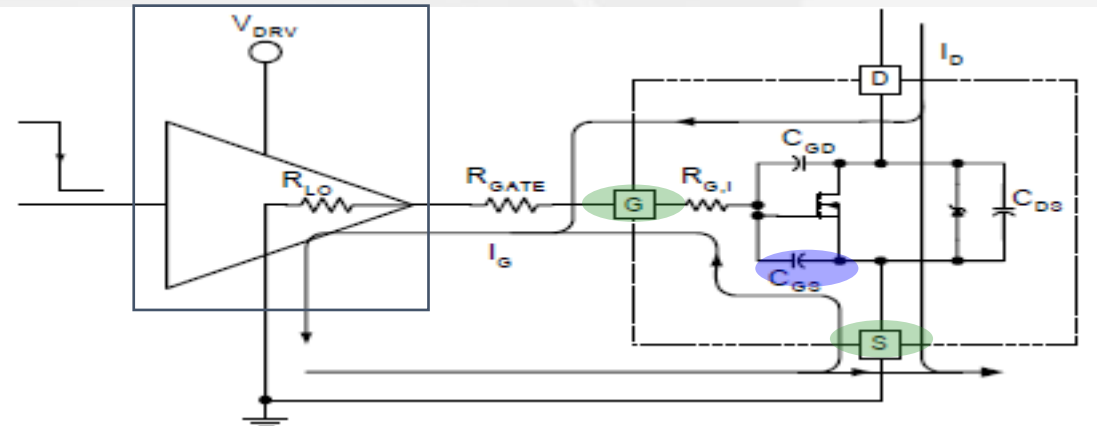


Switch Turn-Off




# Why are Gate Drivers Necessary in Power Electronics?

## Turn-ON

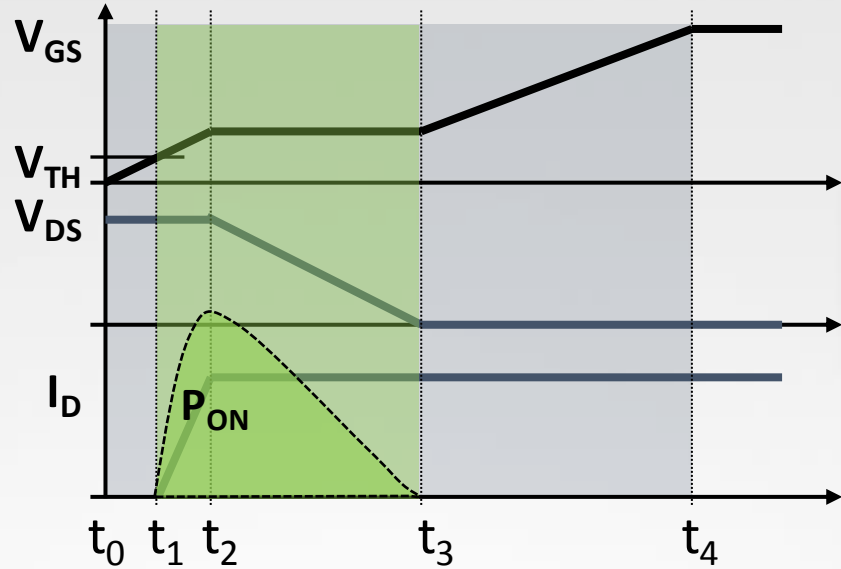

## Turn-OFF



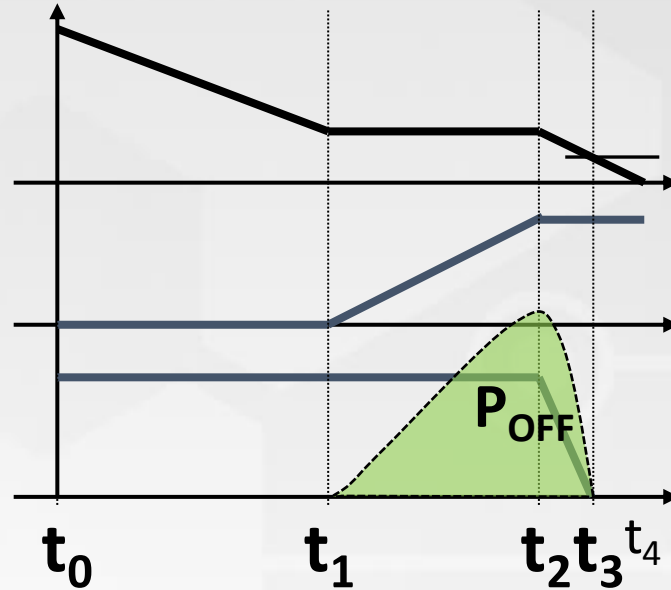


Switching On Loss

$$\int_{t_1}^{t_3} V_{DS}(t) \cdot I_D(t) dt + E_{OSS}$$

$$t_{1\sim3} \propto \frac{1}{I_{Drv}}$$

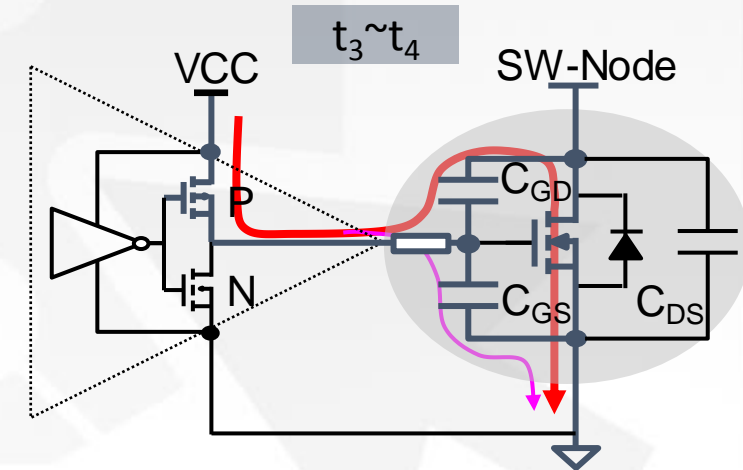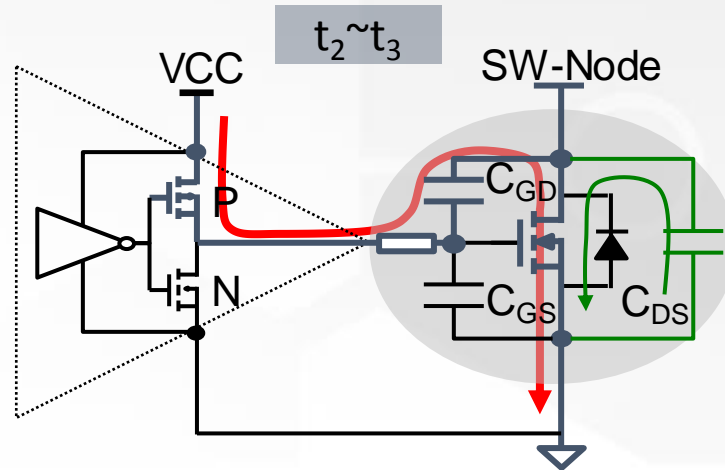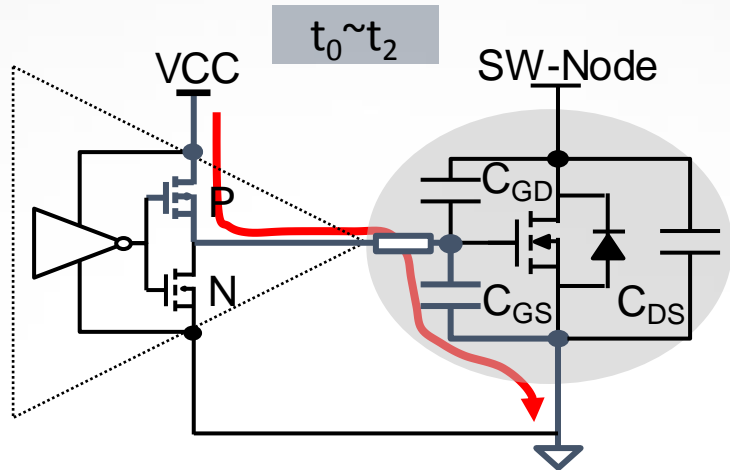**Stronger Driver → lower switching loss**




Fast charge/discharge of  $C_{GS}$ ,  $C_{GD}$  reduces power loss in time intervals

# Types of Gate Drivers – Based on Switch Position/Arrangement


## 1. Low Side Drivers

Used to Drive GND referenced switches



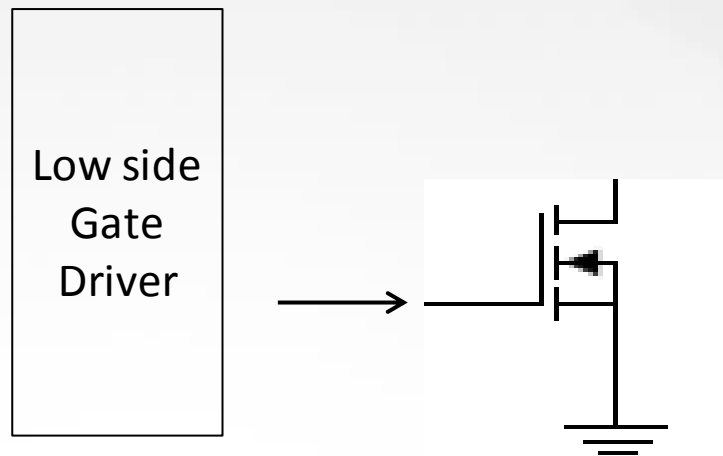

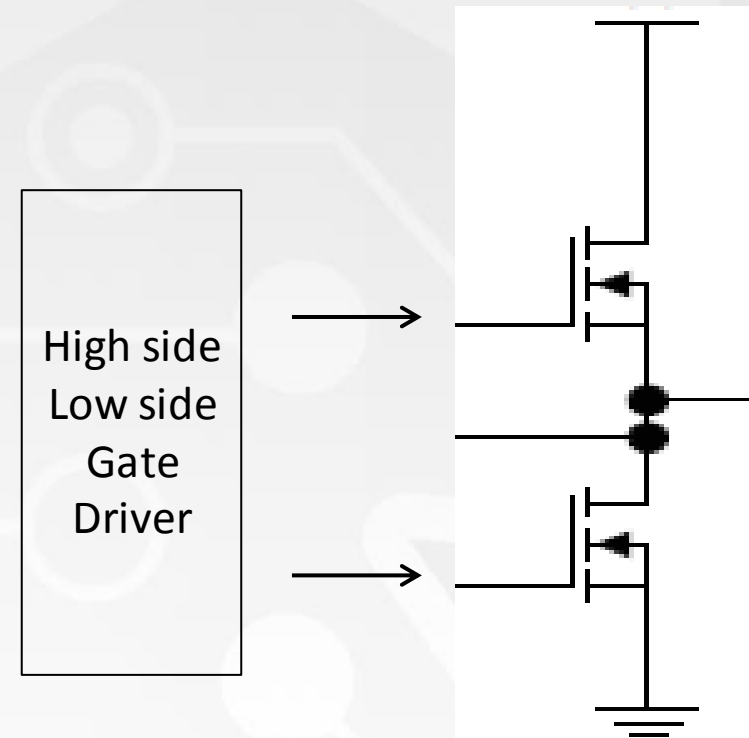
## 2. High side-Low Side Drivers

Used to Drive 2 switches connected in Bridge Arrangement



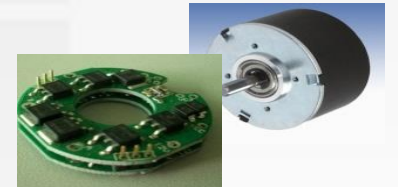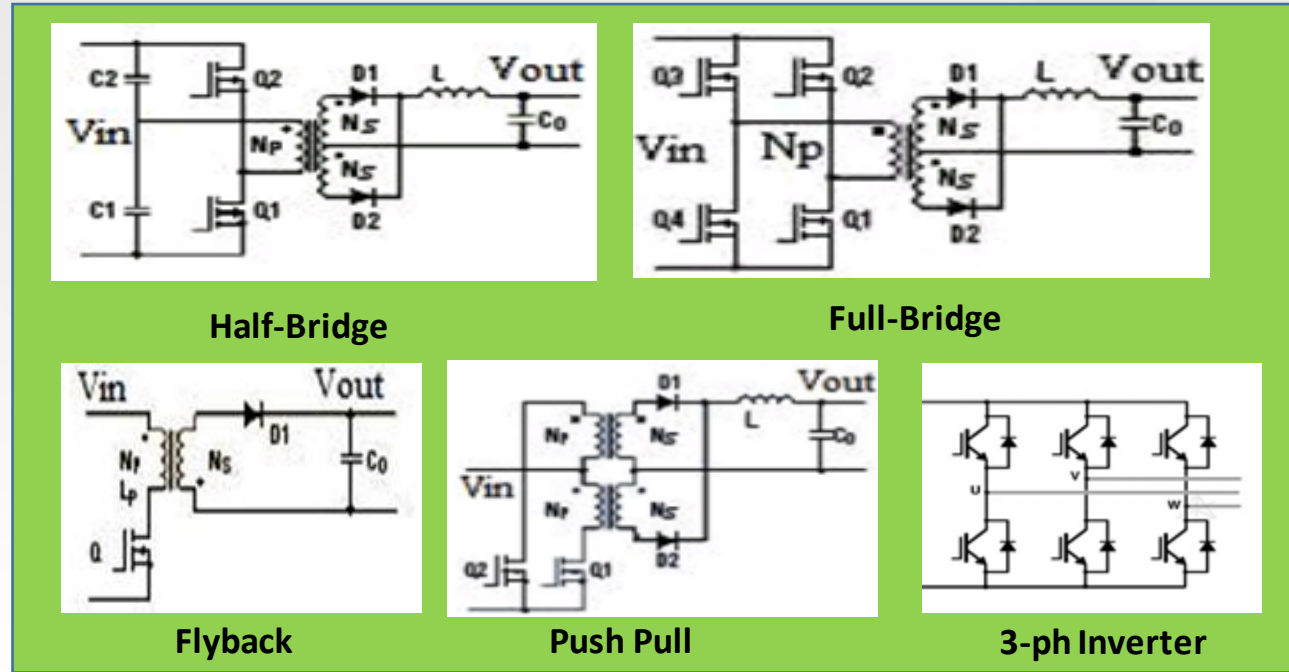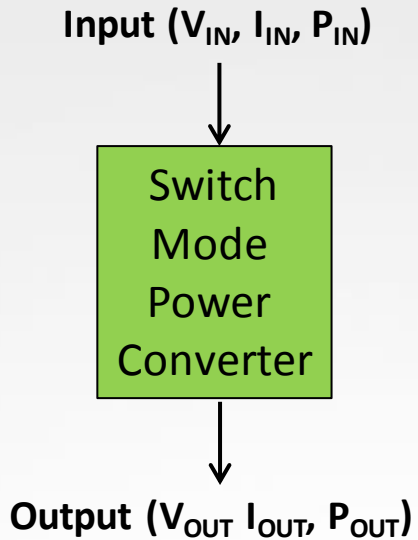
# Topologies in switched mode power electronics



**Lets look at a power supply application**

# Power Supply application

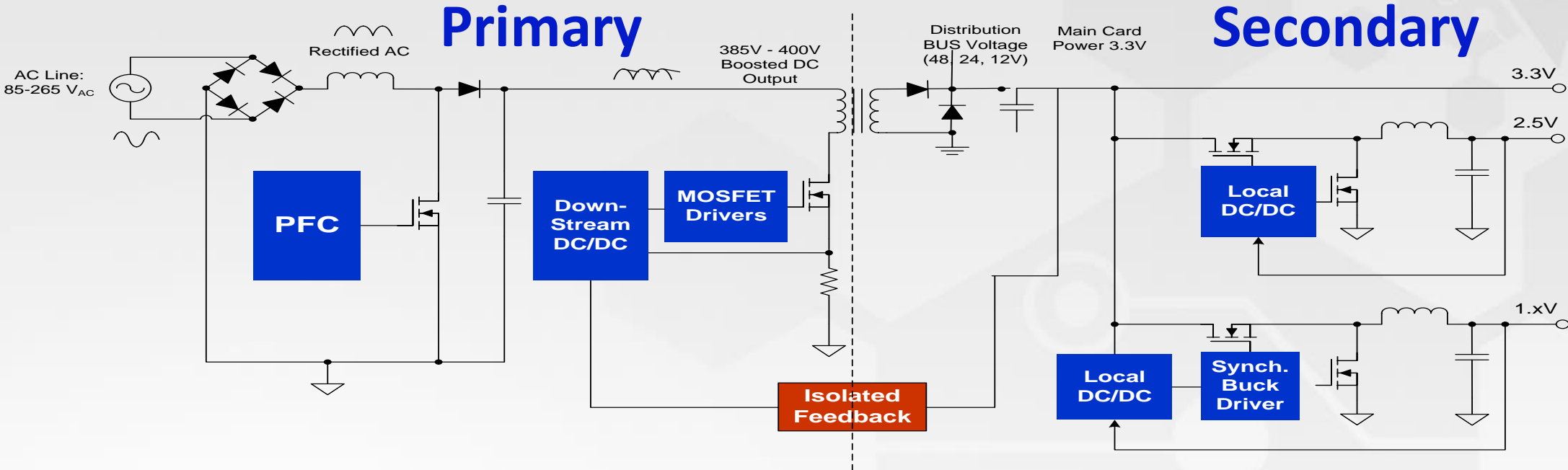

**There is high voltage involved on the primary side of DCDC**

**PFC Boost**

Reduces Harmonic Content, lowers peak current and makes load look Resistive


**PWM**

PWM is main loop to regulate Vo, provides proper duty cycle


**Local POL Regulators**

PWM is main loop to regulate Vo, provides proper duty cycle

# Server / Telecom Power Supply example

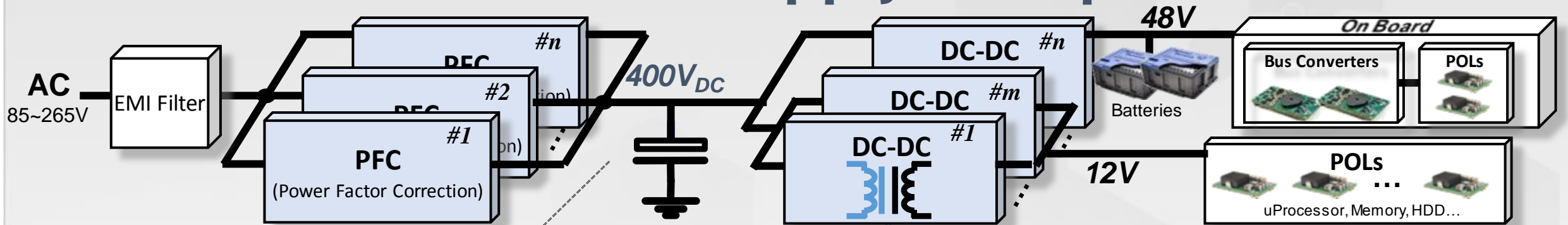


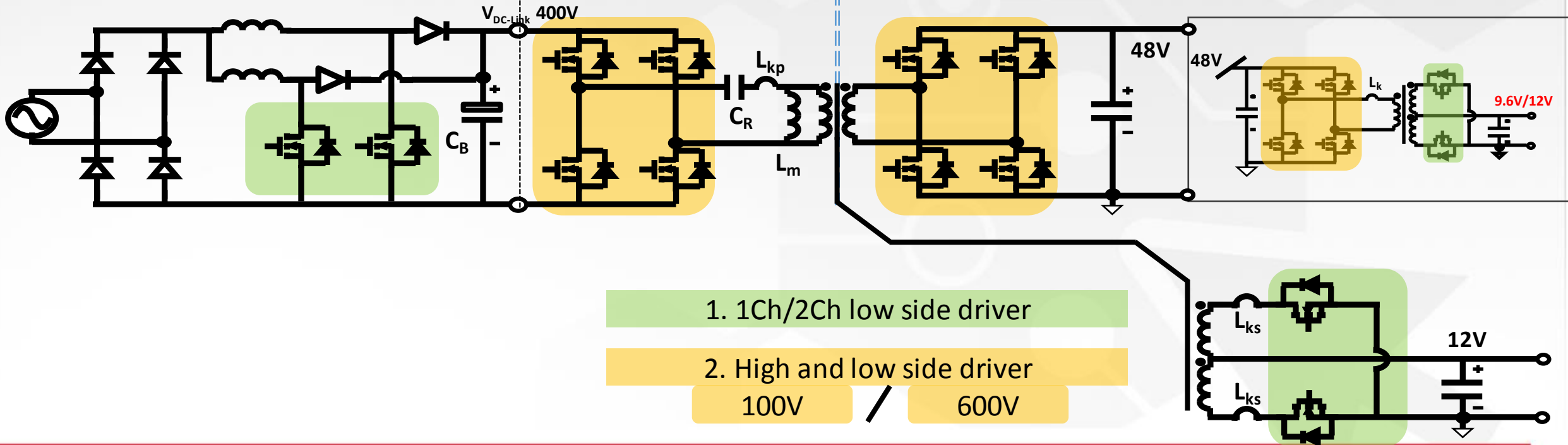All pictures are Used under Fair use, 2015



**Based on the positioning/placement of the controller, isolation is required between the controller and the driver**

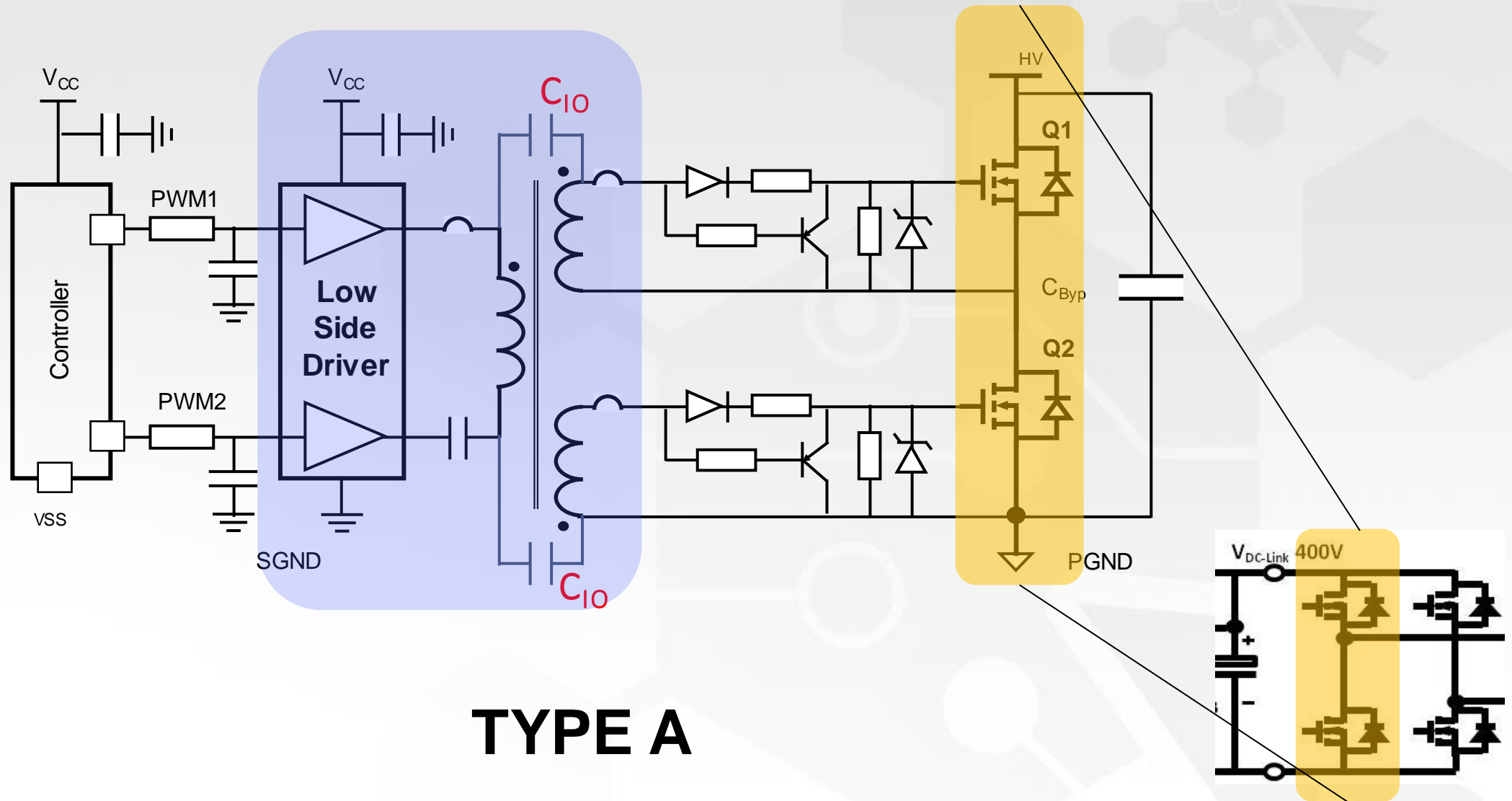
# Traditional method of isolation: Transformer



**TYPE A**



# Consider an Isolator + Driver

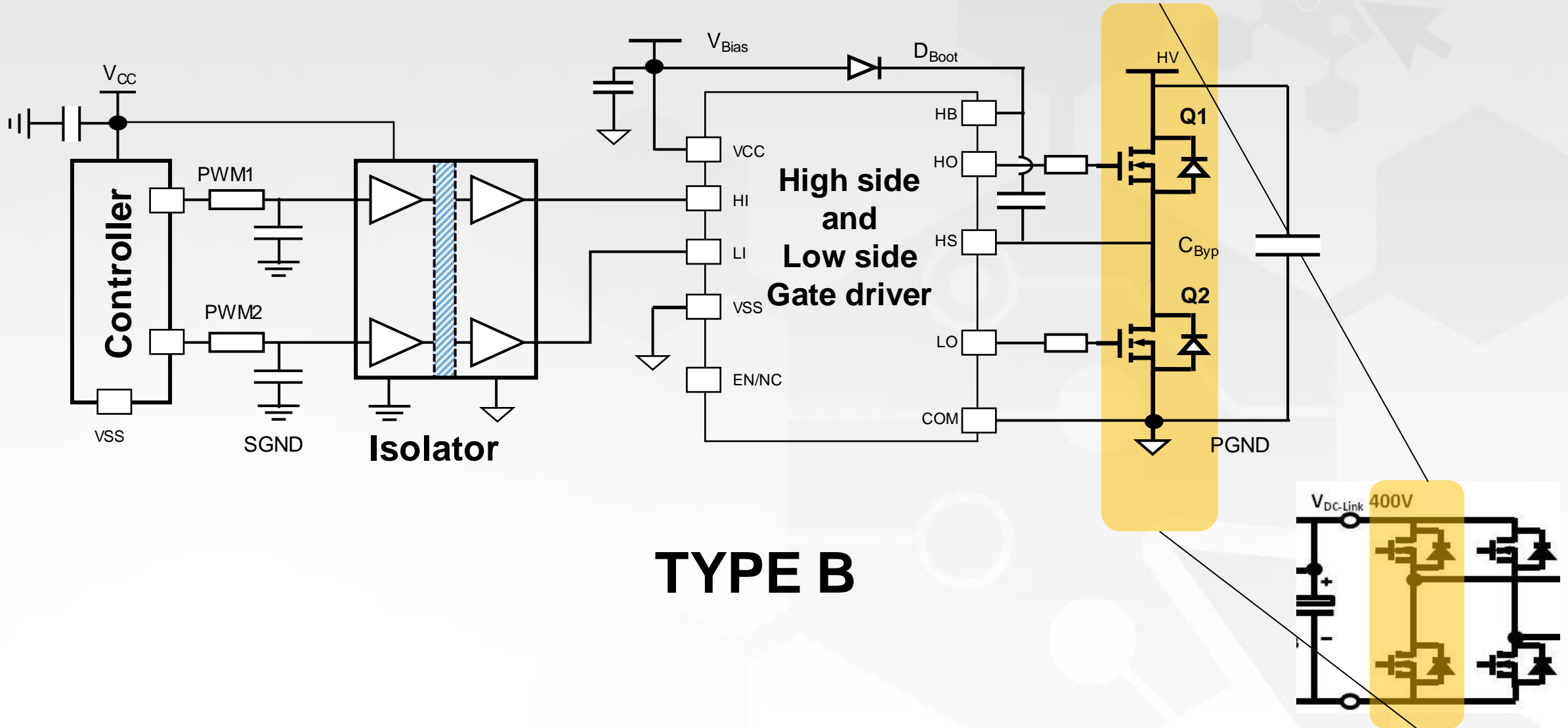



**TYPE B**

# Comparison between Gate Drive Transformer & High & Low Side Driver with isolator

|                   | Type A                    | Type B                 |
|-------------------|---------------------------|------------------------|
| $T_{\text{Prop}}$ | $\approx 20\text{ns}$     | $\approx 100\text{ns}$ |
| Bias Power        | <b>NO</b>                 | <b>Yes</b>             |
| $C_{\text{IO}}$   | $\geq 10\text{pF}$        | $\leq 1\text{pF}$      |
| Parasitics        | Large ( $L_{\text{LK}}$ ) | <b>Very small</b>      |
| Overshoot         | Large                     | Small                  |
| Size              | Bulky                     | Small                  |

# Trending towards integration: Isolated gate driver

## TYPE B

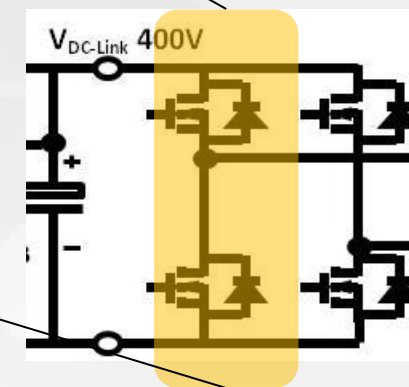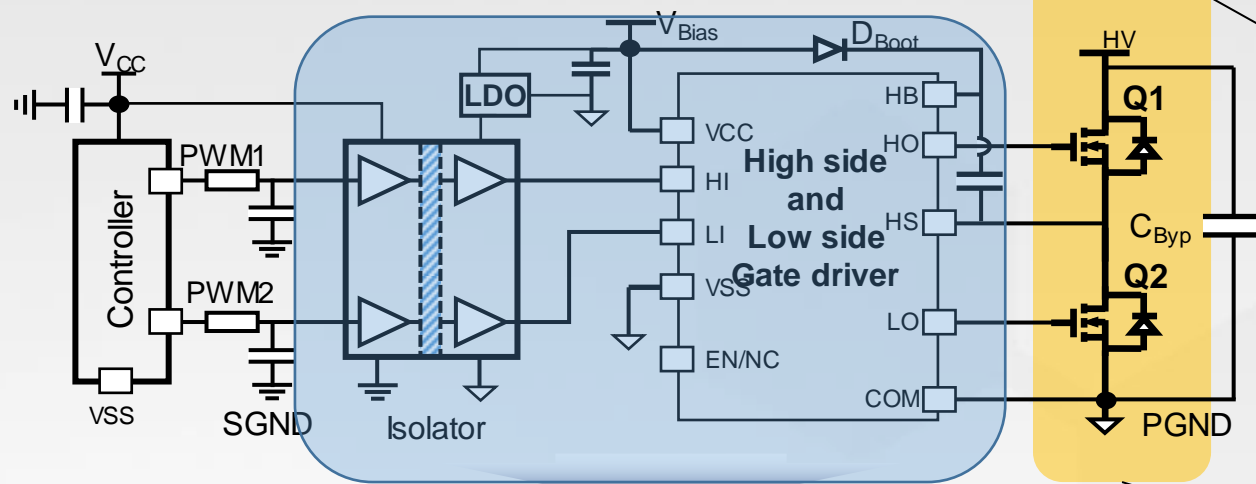

## TYPE C: ISO Driver

- ✓  $CMTI > 100V/ns$
- ✓ 5kVrms reinforced isolation
- ✓  $T_{Prop}: 25ns$  Typ.
- ✓  $Match./T_{PWD} < 5ns$

✓ 110mm<sup>2</sup>

# Trending towards integration: Isolated gate driver

## TYPE A

|        |           | W (mm) | L (mm) | H (mm)     | Area (mm <sup>2</sup> ) | Vol (mm <sup>3</sup> ) |
|--------|-----------|--------|--------|------------|-------------------------|------------------------|
| Type A | UCC27324  | 5      | 6.2    | 1.75       | 31                      | 54.25                  |
|        | GA3550-BL | 17.4   | 24.13  | 10         | 420                     | 4200                   |
|        |           |        |        | <b>SUM</b> | <b>451</b>              | <b>4254</b>            |

## TYPE B

|        |          |      |      |            |            |            |
|--------|----------|------|------|------------|------------|------------|
| Type B | ISO7520C | 10.5 | 10.6 | 2.65       | 111.3      | 295        |
|        | UCC27714 | 8.75 | 6.2  | 1.75       | 54.25      | 95         |
|        | MURS360  | 8.1  | 6.1  | 2.4        | 49.41      | 119        |
|        |          |      |      | <b>SUM</b> | <b>215</b> | <b>509</b> |

PCB Area  
Reduction – 76%

## TYPE C: ISO Driver (UCC21520)



- ✓ CMTI > 100V/ns
- ✓ 5kVrms reinforced isolation
- ✓  $T_{Prop}$ : 25ns Typ.
- ✓ Match./ $T_{PWD}$  < 5ns
- ✓ 110mm<sup>2</sup>

# Why is driver + isolation integration trend important?

- Adding isolation is becoming mandatory as part of regulatory compliance
- System solutions becoming smaller in size
  - Datacenters – space limited – but more storage
  - Telecom bay stations and RRUs – Higher data transactions
- Higher efficiency
  - Switching to higher voltages
  - More intelligence to systems → More protection of controls
- Higher performance density
- Isolation robustness
- Availability of high voltage devices
  - Wide band gap devices – SiC, GaN

# Construction of an isolated gate driver




## Multichip module

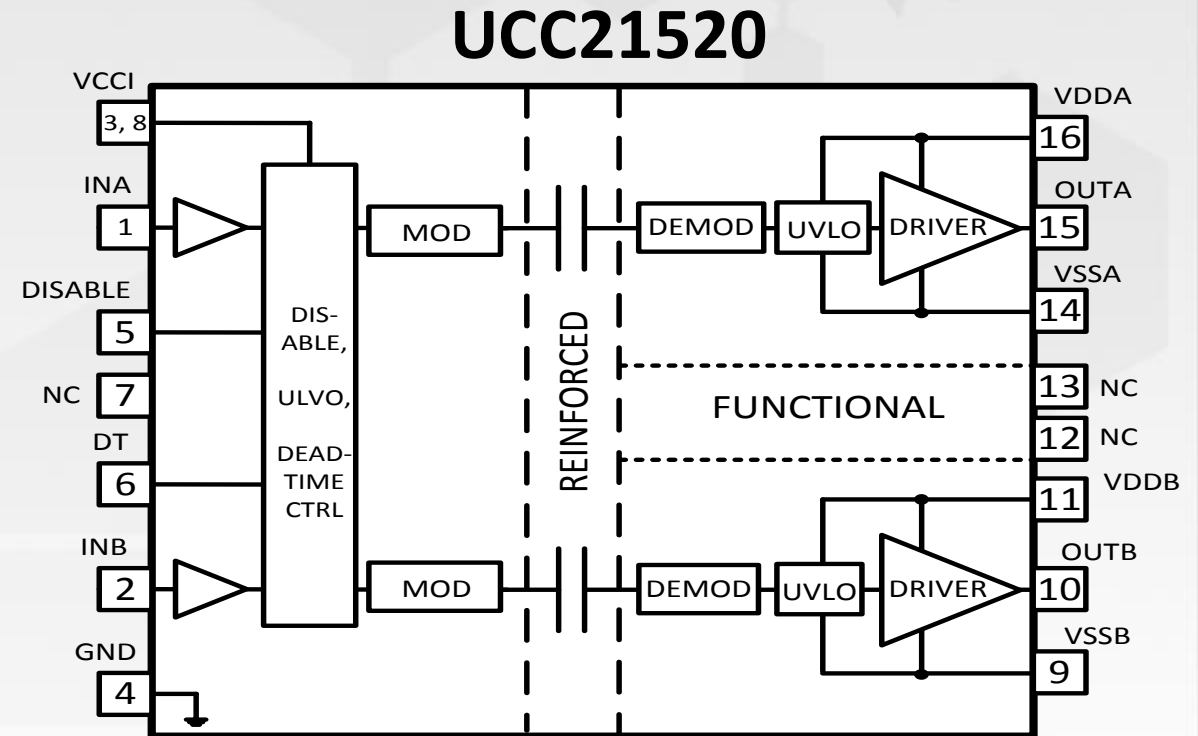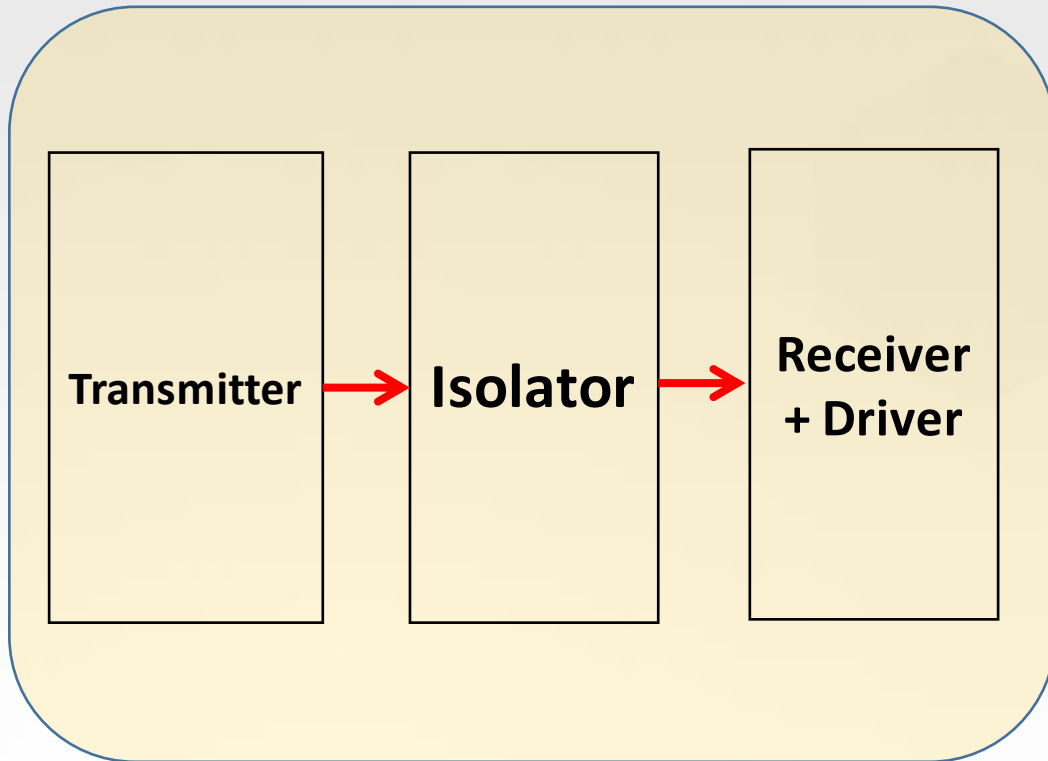

[Visit the UCC21520 webpage](#)




# Types of isolation methods

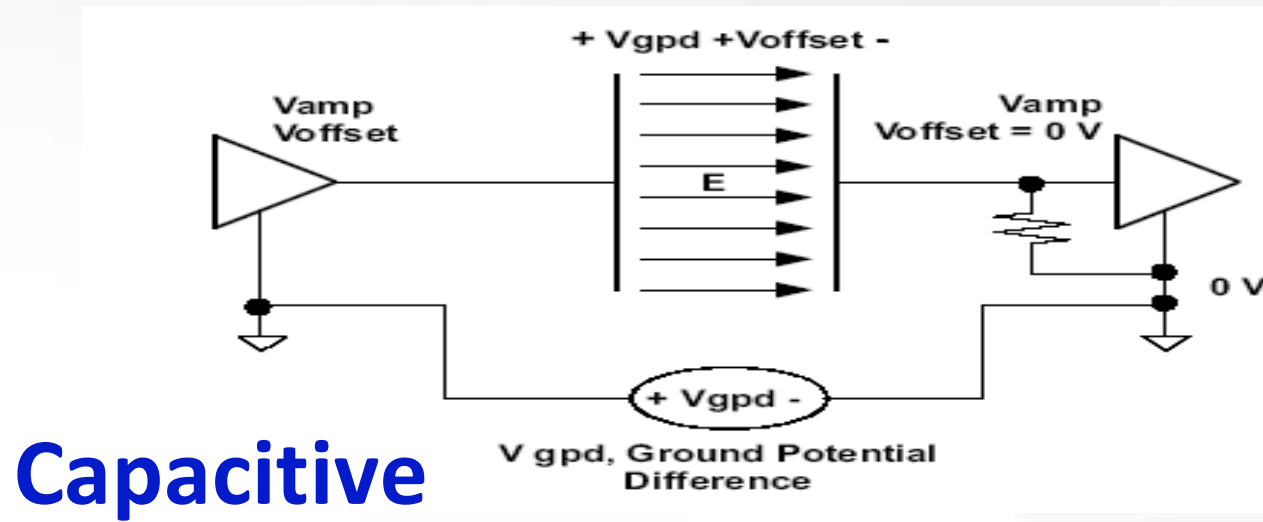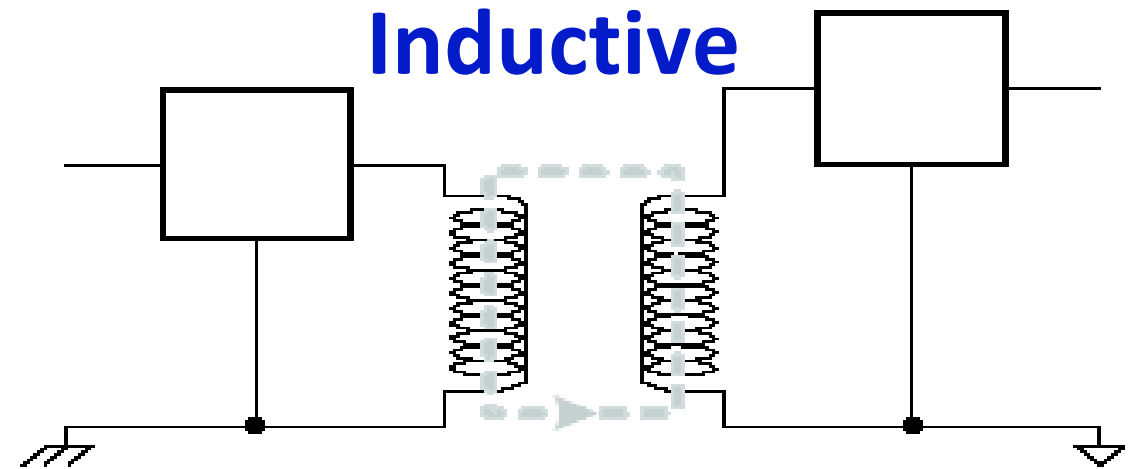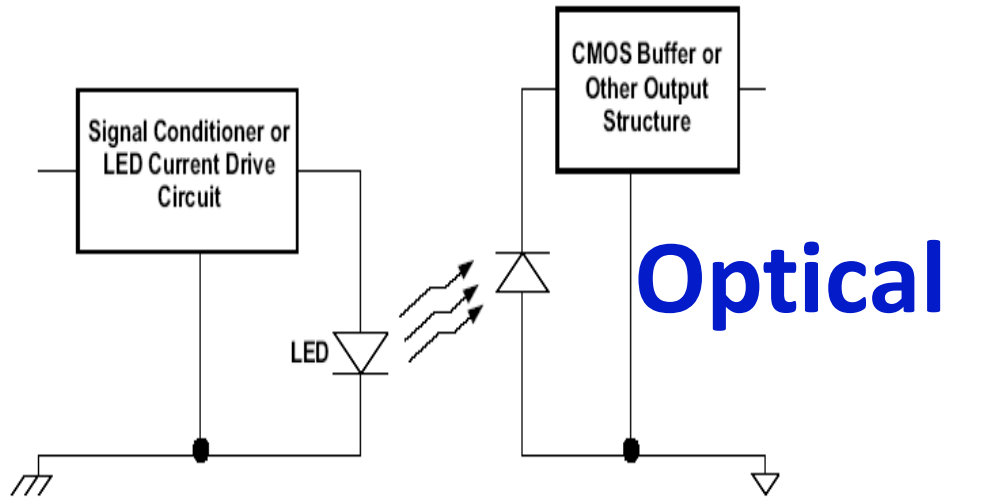
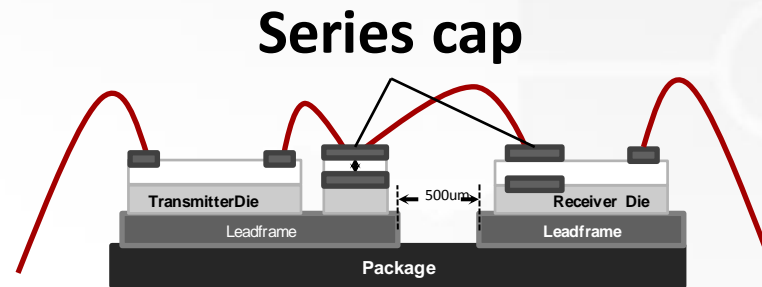
# TI uses Capacitive Isolation Technology

- ✓ **SiO<sub>2</sub> is the most stable dielectric over temperature and moisture**
- ✓ Highest lifetime in the industry, >1.5 kV<sub>RMS</sub> for 40 years
  - ✓ Superior transient protection for harsh environments, >12.8kV
- ✓ **Leverage advantages of TI's process technology**
  - ✓ Manufacturing repeatability leading to tight part-to-part skew
  - ✓ Integration path with many other circuits
  - ✓ No wear out mechanisms, low defect levels, high MTBF





# Value of Capacitive isolation



## Higher power density, enabling smaller solutions

High drive currents reduces switching losses with a rise time of 6ns and fall time of 7ns for a 1.8nF load for high frequency switch mode power applications (UCC21520)



## Isolation robustness

Best-in-class surge protection of 12.8kV and noise immunity greater than 100V/ns with integrated dead-time control is ideal for safety-critical applications.



## Low power consumption

Reduced standby power as low as 1milliamps (mA) helps increase energy efficiency and increase the life of the device.

# Levels of Isolation

- **Functional Isolation**
  - Functional Isolation is necessary for the proper operation of a product. There is no need for protection against electric shock
- **Basic Isolation**
  - Basic Isolation is single level of isolation providing basic protection against electric shock
- **Reinforced Isolation**
  - A single insulation system that provide electrical shock protection equal to double insulation
- **Supplementary Isolation**
- **Double Isolation**

# Standards that apply to Isolated drivers

## • Component level Standards:

- IEC 60747-5-5 (VDE 0884-5-5) .
- VDE 0884-10 / VDE 0884-11
- IEC 60747-17
- UL 1577
- ---

**TI Isolated gate drivers  
must pass**

## • System Level / End Equipment Standards


- IEC 61800-5-1, safety requirements for adjustable speed drives
- IEC 60601-1, Medical equipment standard
- IEC 61010-1, safety standard for measurement, control and Lab equipment
- IEC 60950-1, Telecom equipment standard
- ISO 6469-3, Electric Vehicle Safety Standard
- ....

**Customer boards and  
systems must pass – TI  
Isolated gate drivers  
should enable**

# Common Isolation Terminologies

- Isolation Rating Voltage (Vrms) : Viso
- Working/Operating/Repetitive Voltage (Vrms)
- Impulse or Surge Voltage (Vpk): Viosm
- Channel to channel voltage

- Creepage Distance
- Clearance

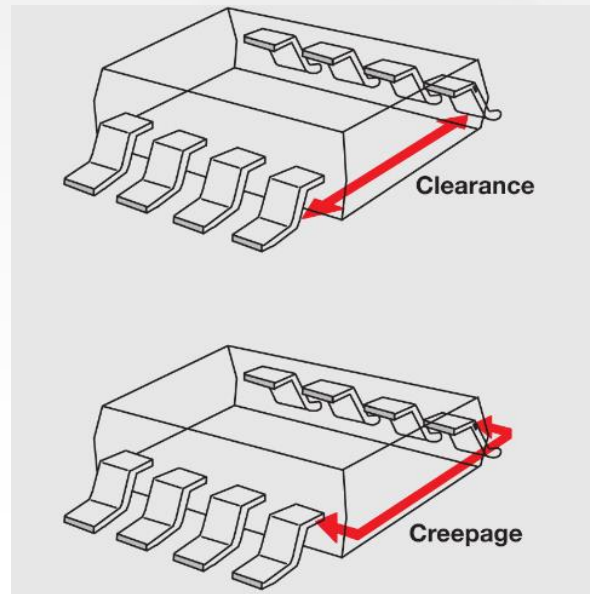

- Tracking
- Comparative Tracking Index (CTI)

| CTI              | Material Group |
|------------------|----------------|
| 600 <= CTI       | I              |
| 400 <= CTI < 600 | II             |

- Pollution Degree 1
- Pollution Degree 2
- Pollution Degree 3

Details on these terminologies to be discussed in the Oct 20<sup>th</sup> webinar offered on isolation

# Key requirements for an isolated driver




In addition to understanding the levels of isolation.... It is important to find out about the driver functionalities:

- Propagation delay
- Common Mode Transient Immunity (CMTI)
- Rise time/fall time
- Maximum driver side supply voltage
- UVLO
- Channel to channel delay
- Protection schemes
- Dead time control and overlap
- Enable/disable features

# Type of isolated gate drivers

| Type                | Single                       | Dual                      |
|---------------------|------------------------------|---------------------------|
| Power switch        | MOSFET, IGBT                 | MOSFET                    |
| Pinouts             | 8, 16, 24, 32                | 16 (for SOIC), 13,14      |
| Type of isolation   | Basic and Reinforced         | Basic and Reinforced      |
| Package type        | SOIC (narrow and wide)       | SOIC (narrow & wide), LGA |
| Protection features | Yes (for 16, 24 and 32 pins) | No                        |


## Examples

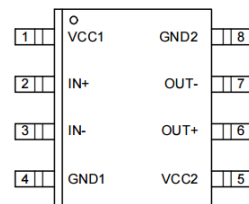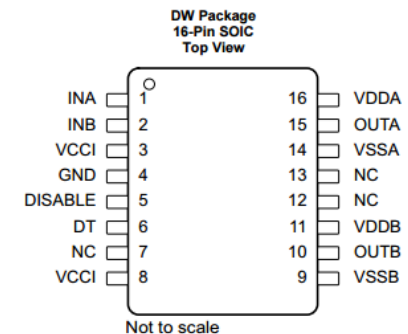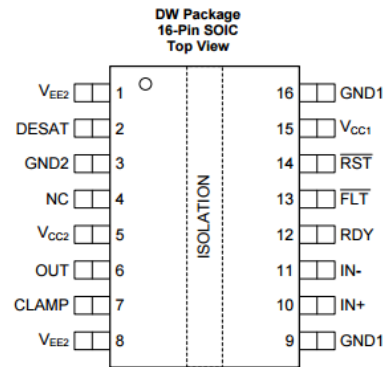

# Comparison between MOSFET and IGBT iso drivers

| Power Switch           | MOSFET   | IGBT   |
|------------------------|--|--|
| Switching frequencies  | High (>20 kHz)   | Low to Medium (5-20kHz)  |
| # Channels             | Single and Dual  | Single   |
| Protection             | No   | Yes – Desaturation, Miller Clamping  |
| Max Vdd (power supply) | 20V  | 30V  |
| Vdd range              | 0-20V  | -10 to 20V   |
| Operating Vdd          | 10-12V   | 12-15V   |
| UVLO                   | 8V   | 12V  |
| CMTI                   | 50-100V/ns   | <50V/ns  |
| Propagation delay      | Smaller the better (<50ns)   | High (not critical)  |
| Rail Voltage           | Up to 650V   | >650V  |
| Typical Applications   | Power supplies – Server, datacom, telecom, factory automation, onboard and offboard chargers, solar u-inverters and string inverters (<3kW), 400-12V DCDC - Auto | Moto drives (AC machines), UPS, Solar central and string power inverters (>3kW), Traction inverters for auto |

# Motor drive application

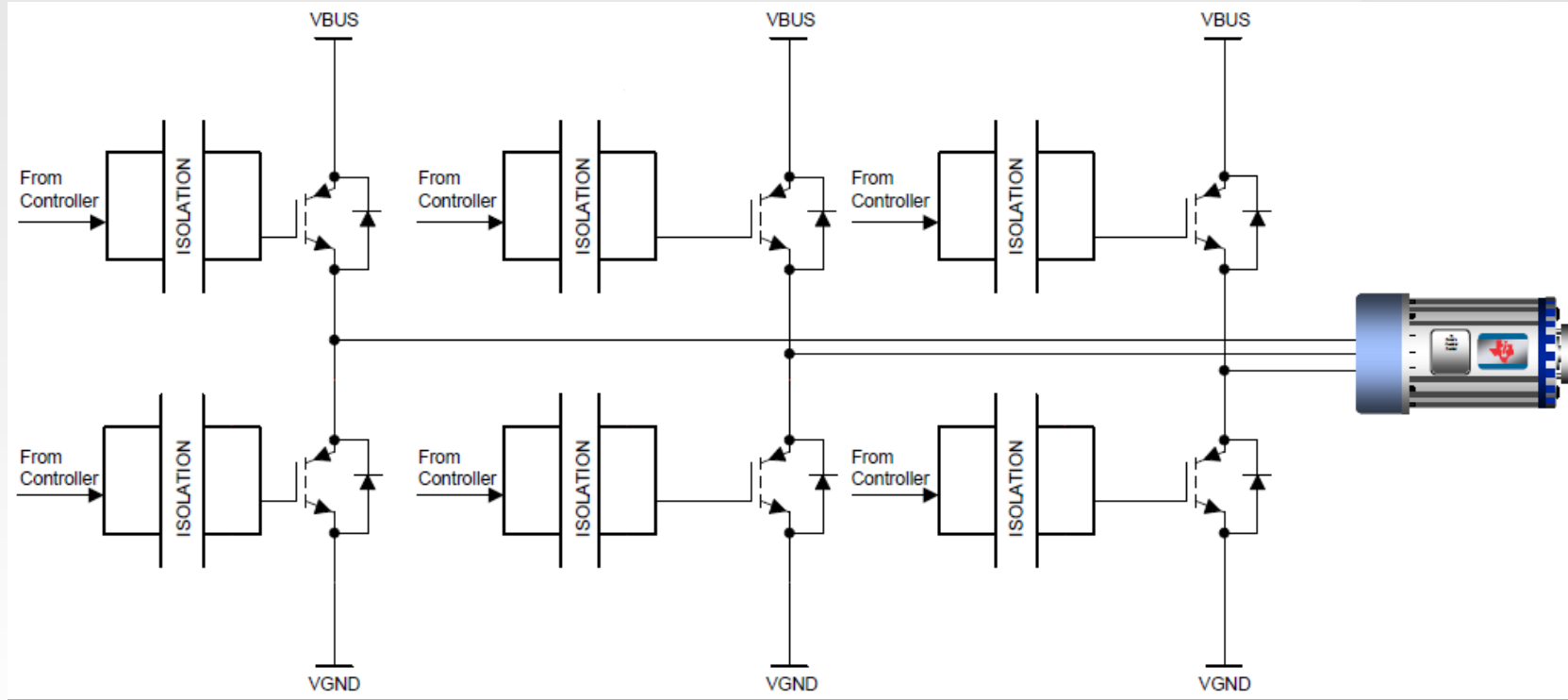


## Gate driver options:

- 6 single channel iso drivers with no protection ( 8pin) and usually reinforced
- 6 single channel iso drivers with protection (DESAT, Miller clamp or split output) (16 pin)
- 3 single channel iso drivers for high side only (8 or 16 pin) along with 3 non isolated drivers



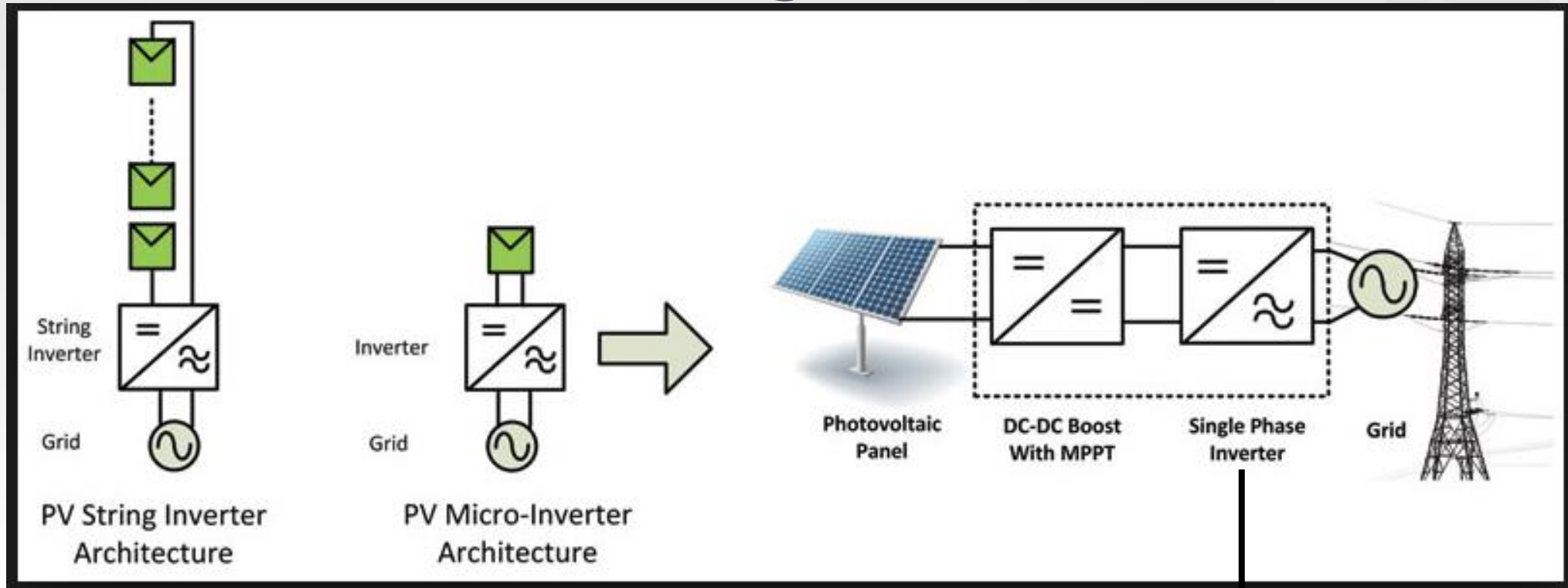
# Solar micro (300W)/string (<3kW) inverter




Usually MOSFET single inverters needing isolated (basic or reinforced) drivers

# State-of-the-art Power Semiconductors (Wide Band Gap)


**Si-MOSFET**

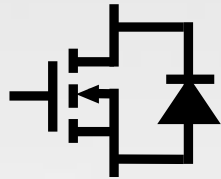

**IGBT**

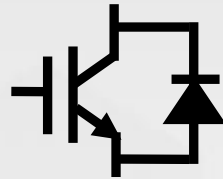

**SiC-MOSFET**

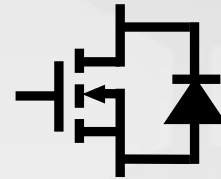

**GaN**




Nom-ON

Nom-OFF

|                                    |         |           |          |        |          |
|------------------------------------|---------|-----------|----------|--------|----------|
| <b>Voltage Ratings</b>             | 20~650V | ≥650V     | ≥650V    | ≤650V  |          |
| <b>Optimal <math>V_{GS}</math></b> | 0~15V   | -10~15V   | -5~20V   | -5~10V | -4~6V    |
| <b>Max.Limit</b>                   | (±20V)  | (-10~20V) | (-5~25V) | (±18V) | (-10~7V) |


**Si-MOSFET**

10V

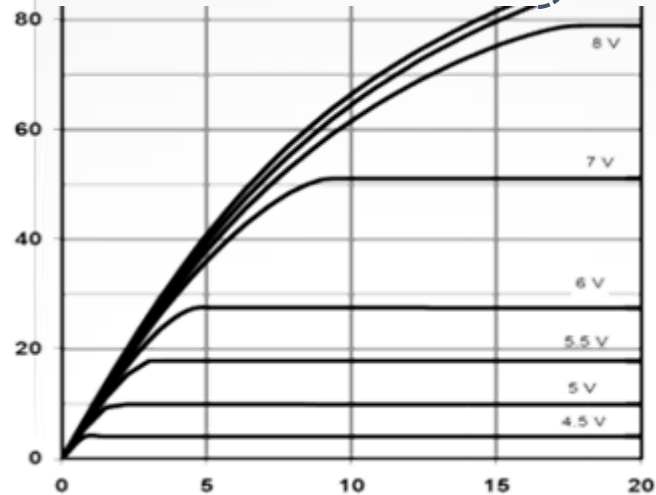


**IGBT**

12V

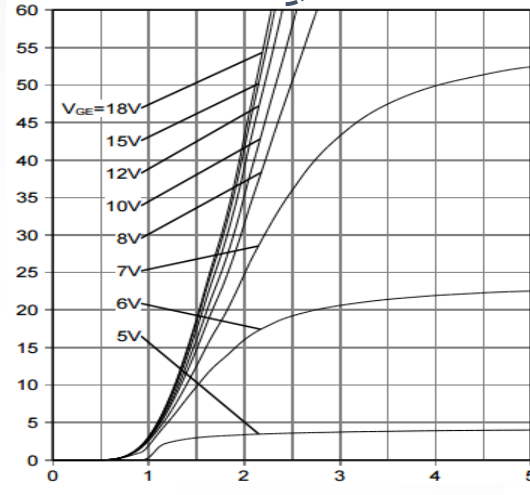


**SiC-MOSFET**

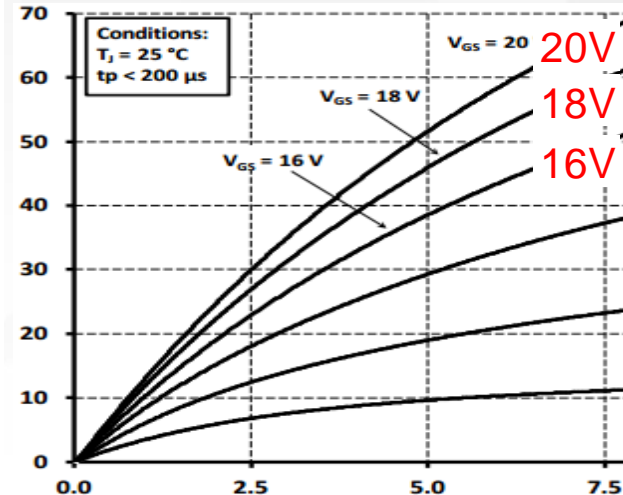

**GaN**

5V

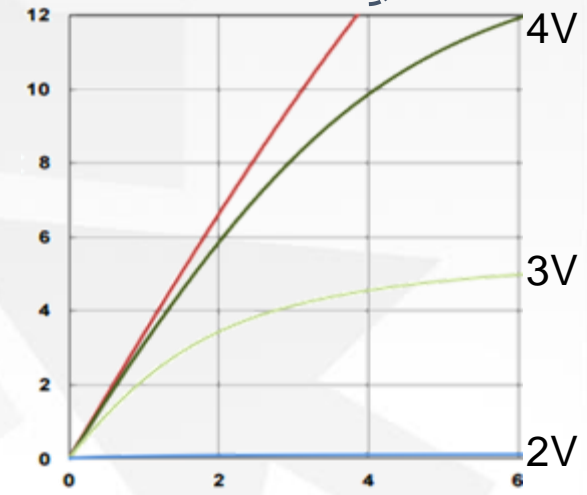

- I-V curves are from datasheets of Infineon, CREE, EPC

# Value of Silicon carbide in high voltage & high power applications

- ✓ High power density – 10x more than Silicon
  - ✓ High current density
- ✓ High breakdown voltage
- ✓ Drive higher current in a reduced footprint
- ✓ High thermal conductivity
- ✓ High mobility – ability to switch at high frequencies

# Comparison of SiC to MOSFET and IGBT iso drivers

| Power Switch           | MOSFET   | IGBT   | SiC  |
|------------------------|--|--|--|
| Switching frequencies  | High (>20 kHz)   | Low to Medium (5-20kHz)  | High (>50 kHz)   |
| # Channels             | Single and Dual  | Single   | Single and Dual  |
| Protection             | No   | Yes – Desaturation, Miller Clamping  | Yes – Current sense, Miller Clamping   |
| Max Vdd (power supply) | 20V  | 30V  | 30V  |
| Vdd range              | 0-20V  | -10 to 20V   | -5 to 25V  |
| Operating Vdd          | 10-12V   | 12-15V   | 15-18V   |
| UVLO                   | 8V   | 12V  | 12-15V   |
| CMTI                   | 50-100V/ns   | <50V/ns  | >100V/ns   |
| Propagation delay      | Smaller the better (<50ns)   | High (not critical)  | Smaller the better (<50ns)   |
| Rail Voltage           | Up to 650V   | >650V  | >650V  |
| Typical Applications   | Power supplies – Server, datacom, telecom, factory automation, onboard and offboard chargers, solar u-inverters and string inverters (<3kW), 400-12V DCDC - Auto | Moto drives (AC machines), UPS, Solar central and string power inverters (>3kW), Traction inverters for auto | PFC – Power supplies, Solar inverters, DCDC for EV/HEV and traction inverters for EV, Motor drives, Railways |

**Note: Blue font highlights similarities**

# TI isolated gate driver family

All families support MOSFETs, SiC MOSFETs, IGBTs

| Driver Type                               | ISO*****  |  | UCC*****                                 |
|---|---|--|--|
| # Channels                                | 1   |  | 2, 1                                     |
| DESAT, Soft Turn-off, Miller clamp        | Yes   |  | No (yes for Miller Clamp)                |
| SiC support                               | Yes   |  | Yes                                      |
| Withstand Isolation voltage ( $V_{ISO}$ ) | 5.7kVrms / 8kVpk  |  | 5.7KVrms/8kVpk                           |
| ISO working voltage ( $V_{IOWM}$ )        | 1.5kVrms / 2.121kVpk  | 1kVrms / 1.42kVpk  | 1.5kVrms / 2.121kVpk<br>850Vrms/1.2kVpk  |
| CMTI (Min)                                | 100kV/ $\mu$ s  |  | 100kV/ $\mu$ s                           |
| Supply type                               | Unipolar, Bipolar   |  | Unipolar, Bipolar                        |
| Peak drive current                        | 2.5A/5A   |  | 4A/6A<br>8A/12A - with Parallel Channels |
| Rising and Falling time                   | 20ns/20ns @1.0nF  |  | 6ns/7ns @1.8nF                           |
| VCC, Input                                | 2.25V to 5.5V   |  | 3V to 18V                                |
| VDD, Output                               | 15V to 30V  |  | 9.2V to 25V                              |
| VDD, quiescent current                    | 3.6mA   |  | 1mA                                      |
| Propagation delay (Typ)                   | 76ns  |  | 19ns                                     |
| Protection                                | UVLO, Power ready indication, Fault Feedback                    |  | UVLO, Disable,<br>Programmable Dead Time |
| Packages                                  | SOIC-16 (>8mm Creepage)   |  | SOIC -16 ( <b>Wide Body</b> )            |
| Devices                                   | <a href="#">ISO5851</a><br><a href="#">ISO5852S</a> (split O/P) | <a href="#">ISO5451</a><br><a href="#">ISO5452</a> (split O/P) | ISO53xx<br><br><a href="#">UCC21520</a>  |

# Discover more about isolation

## High-voltage reinforced isolation: Definitions and test methodologies

Anant S Kamath  
Systems Engineer, Isolation, Interface Group  
Texas Instruments

Kannan Soundarapandian  
Product Line Manager, Isolation, Interface  
Texas Instruments

| Parameter            | Definition   | Relevance  |
|----------------------|--|--|
| Basic Isolation      | Isolation that can provide protection against high voltage as long as the barrier is intact.                                     | Basic isolation needs to be coupled with another insulation barrier, if human access is possible.  |
| Reinforced Isolation | Isolation that is equivalent to two basic isolation barriers in series.  | Reinforced isolation by itself is sufficient as a safety barrier against high voltage.   |
| $V_{EDTM}$           | The sinusoidal voltage isolator can tolerate for 60sec (defined in pk)   | Tolerance to temporary overvoltage on supplies due to load changes, arcing etc.  |
| $V_{ISO}$            | The sinusoidal voltage isolator can tolerate for 60sec (defined in rms)  |  |
| $V_{EDFM}$           | Maximum periodic voltage that the isolator has to handle on a continuous basis throughout its operating life (defined in pk)     | The voltage that the isolator has to handle as part of normal operation (for eg. an isolated gate driver sees a pk voltage equal to the DC bus voltage). |
| $V_{EDWM}$           | Maximum continuous working voltage that the isolator has to on a continuous basis throughout its operating life (defined in rms) |  |
| $V_{SURGE}$          | Maximum peak voltage of the 1.2us/50us standard surge waveform that the isolator can handle.                                     | Represents direct and indirect lightning strikes. Min 10kV required for reinforced isolation.  |
| Creepage             | Minimum distance from pins on side 1 to side 2 along the surface of the package  | Limits working voltage or continuous voltage due to degradation along package surface (called tracking)  |
| Clearance            | Minimum distance from pins on side 1 to side 2 through the air   | Limits peak voltages and surge voltages in system environment due to air breakdown   |
| CMTI                 | The maximum rate of change of ground potential difference (GND1-GND2) that the isolator can withstand without bit errors         | Indicates robustness of isolator to ground noise. Very important in gate-drive applications  |

- Reliability and isolation resources:
  - [High-voltage reinforced isolation: Definitions and test methodologies](#)
  - [High-voltage isolation quality and reliability for AMC130x](#)
- [Understanding isolation terminology and relevance](#)
- Discover our [isolation glossary](#)
- Watch part [one](#) and [two](#) of our introduction to digital isolation video series
- Join the [TI E2E™ Community Isolation forum](#)

# Helpful information for readers: UCC21520

## TI E2E™ community



As a member of my.TI you can join the TI E2E™ Community where you can ask questions, share ideas and collaborate with fellow engineers and TI experts

Contents are provided "AS IS" by the respective TI and Community contributors and do not constitute TI specifications. See [Terms of use](#).

### Engage in the Community

• Amplifiers • Data Converters • Logic

• Bro...  
• Clo

### TI E2E Community >

Support forums

Blogs

Groups

Videos

Blogs > Power House

+ New

### Why is the cloud isolated?

[Tweet](#) [G+](#) [Like 0](#)

The demand for information transaction and retrieval is ubiquitous. Whether in line at the grocery store or waiting for a train, we use our smartphones to check our social media accounts, text messages or emails. But have you ever paused to think about from where this information comes? The answer is the cloud, that workhorse of real-time connectivity across the globe. Because information and storage retrieval such as your music playlists and video streams happens behind the scenes, you can see why the cloud is isolated.

The cloud is physically located in a data center. Fiber or coax cables or wireless telecom base stations transmit information to and from data centers.

Now let's peel back the layers of the cloud and see what is inside it. It is the power delivery unit, commonly referred to as the power supply. Why is the power supply so important? All of the information is stored in servers, known as cloud servers. These servers need power to store and retrieve information back and forth to consumers. Power delivery units are in the range of a few hundred to thousands of watts. They operate off the grid, which is the AC line voltage in the range of hundreds to thousands of volts and hence they are referred to as the high-voltage unit.

Unsubscribe to this blog



Nagarajan Sridhar

Jul 18, 2016

Like



- View the [UCC21520 datasheet](#).
- Download the application note, "[UCC21520: A Universal Isolated Gate Driver with Fast Dynamic Response](#)."
- Watch videos about the [value of an isolated driver](#) and [dynamic performance of an isolated driver](#).
- Learn more about TI's [gate driver portfolio](#) and find technical resources.
- Read the Power House blog post, "[Why is the cloud isolated?](#)"
- Join the [TI E2E™ Community Power Management forum](#)



# Thank you