

Challenges with 3-wire RTD systems

TI Precision Labs – ADCs


Created by Bryan Lizon

Presented by Josh Brown

**Low-side R_REF shown; high-side R_REF is possible


1x IDAC versus 2x IDACs for 3-wire RTDs

3-wire RTD using 1x IDAC**

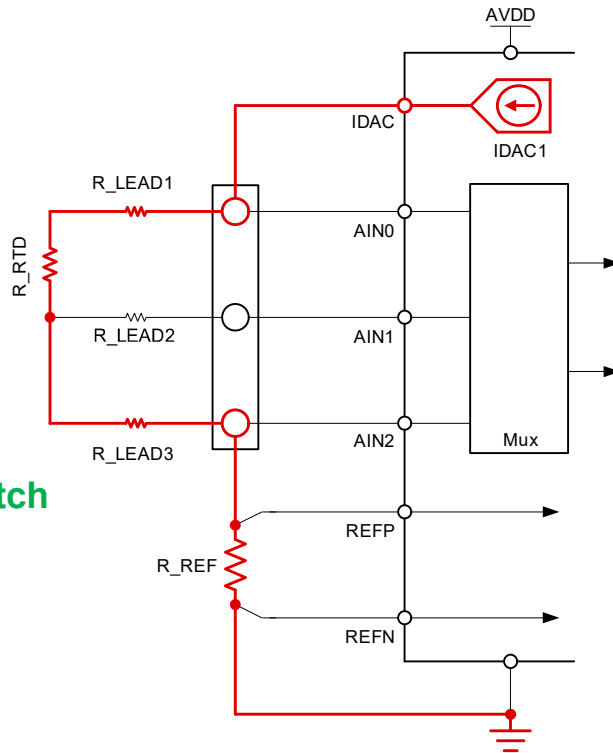

- ✓ No IDAC mismatch errors
- ✗ Requires 2x measurements


3-wire RTD using 2x IDACs**

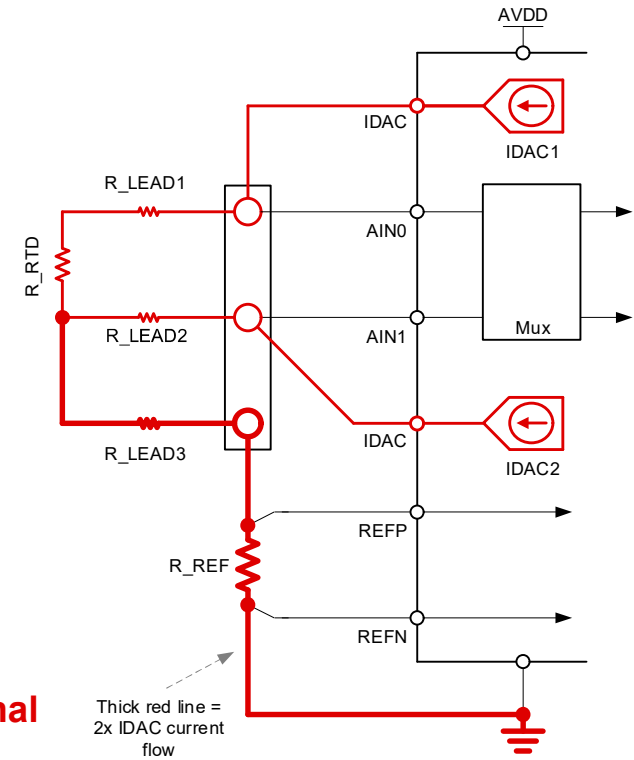


- ✓ Automatic lead resistance cancellation
- ✗ IDAC mismatch causes additional error

Two measurements using 3-wire RTD and 1x IDAC

Circuit for measurement #1

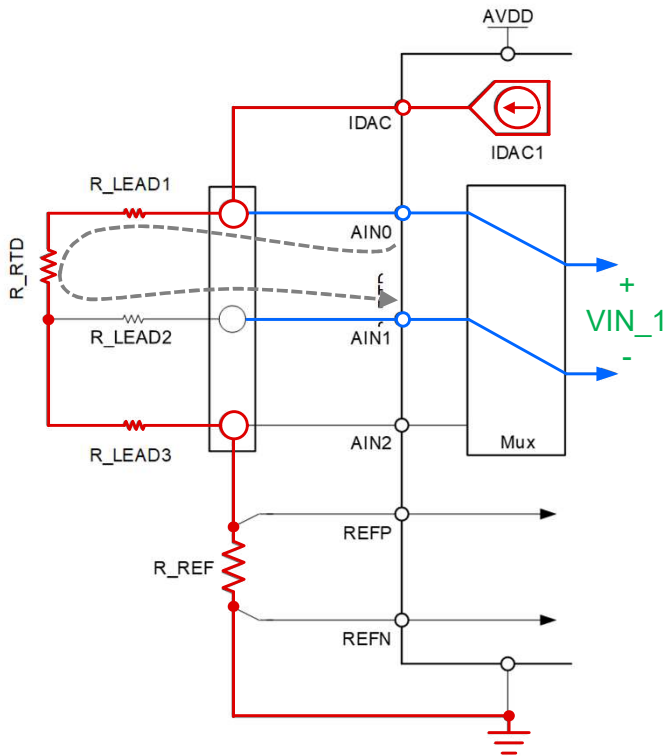

Circuit for measurement #2

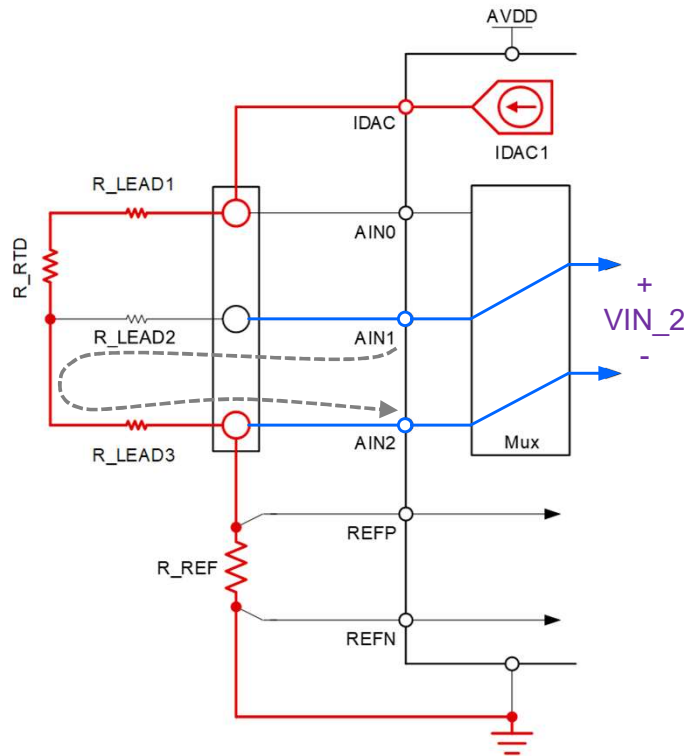

$$VIN_1 = AIN0 - AIN1$$


$$VIN_1 = V_{LEAD1} + V_{RTD}$$

$$VIN_2 = AIN1 - AIN2$$


$$VIN_2 = V_{LEAD3}$$

ADC output code for a 3-wire RTD using 1x IDACs

Circuit for measurement #1

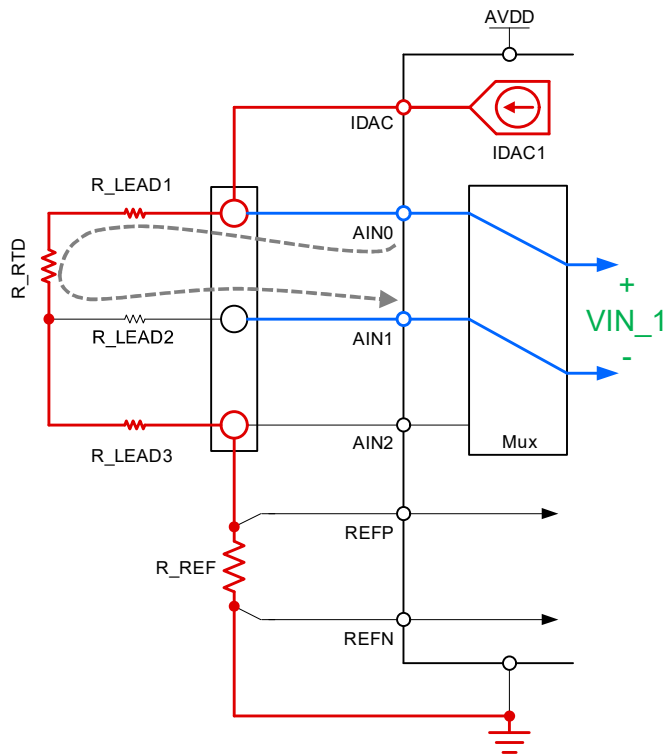

Circuit for measurement #2

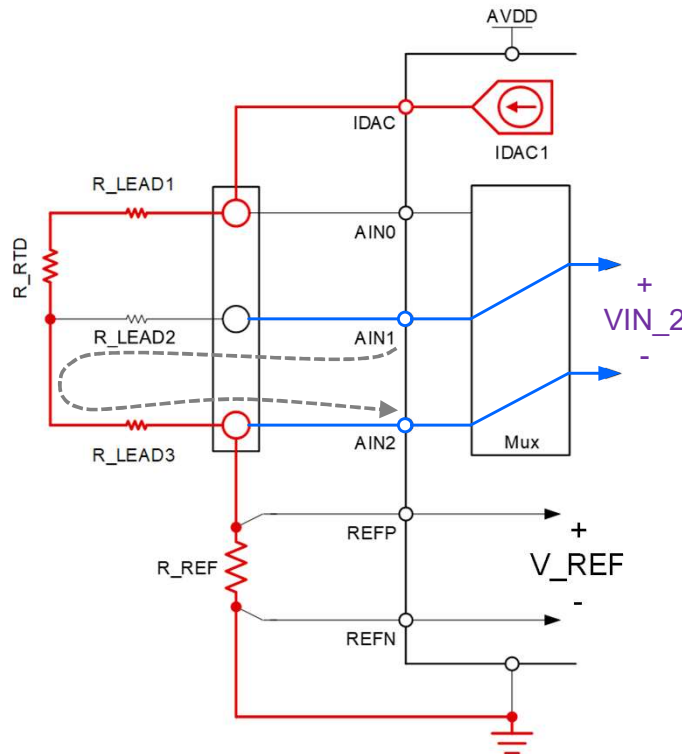

$$VIN_1 = V_{LEAD1} + V_{RTD}$$

$$VIN_2 = V_{LEAD3}$$


$$V_{REF} = IDAC1 * R_{REF}$$

$$\begin{aligned}
 \text{ADC code} &= \frac{VIN_1}{V_{REF}} - \frac{VIN_2}{V_{REF}} \\
 &= \frac{IDAC1 * R_{RTD}}{IDAC1 * R_{REF}} + \frac{IDAC1 * R_{LEAD1}}{IDAC1 * R_{REF}} - \frac{IDAC1 * R_{LEAD3}}{IDAC1 * R_{REF}}
 \end{aligned}$$

$$\text{ADC code} = \frac{R_{RTD}^{**}}{R_{REF}}$$

**If $R_{LEAD1} = R_{LEAD3}$

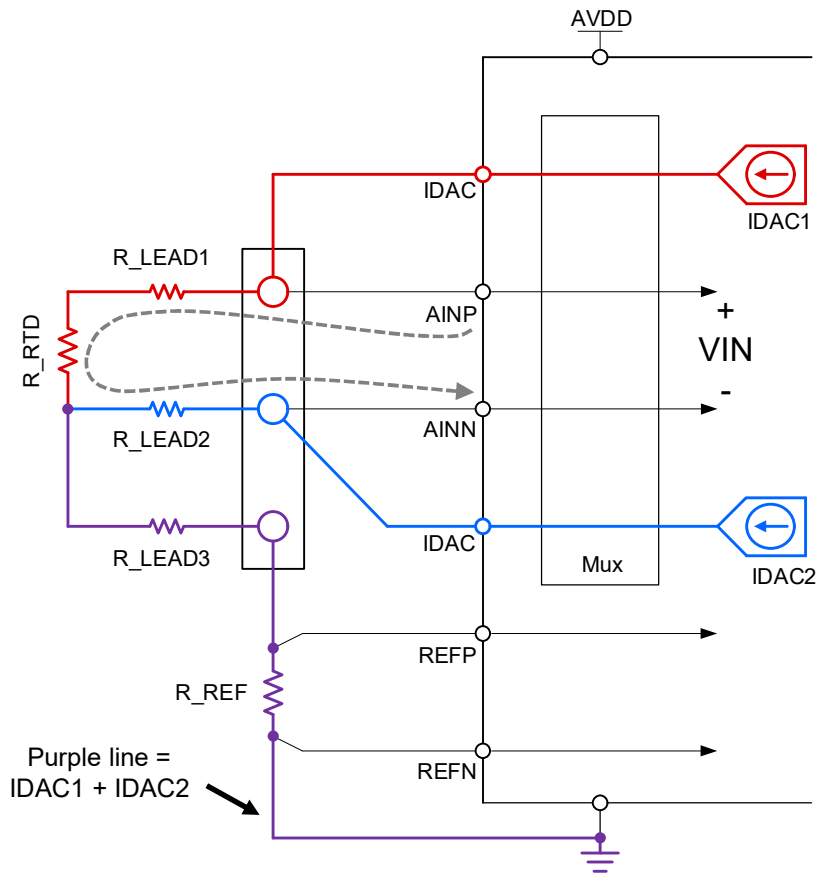Measuring VIN (3-wire RTD, 2x IDACs, LS R_REF)




$$V_{IN} = A_{INP} - A_{INN}$$

$$V_{IN} = V_{LEAD1} + V_{RTD} - V_{LEAD2}$$

- $V_{LEAD1} = IDAC1 * R_{LEAD1}$
- $V_{RTD} = IDAC1 * R_{RTD}$
- $V_{LEAD2} = IDAC2 * R_{LEAD2}$

$$V_{IN} = IDAC1 * (R_{RTD} + R_{LEAD1}) - IDAC2 * R_{LEAD2}$$

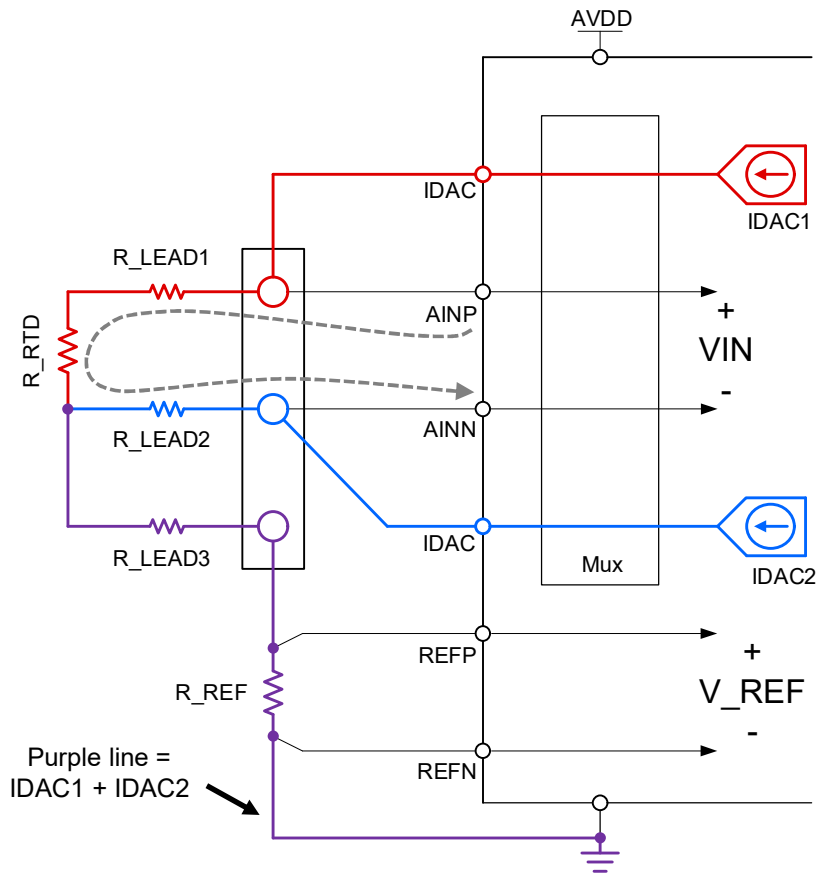ADC output code (3-wire RTD, 2x IDACs, LS R_REF)



$$V_{IN} = IDAC1 * (R_{RTD} + R_{LEAD1}) - IDAC2 * R_{LEAD2}$$

$$V_{REF} = (IDAC1 + IDAC2) * R_{REF}$$

$$\begin{aligned}
 \text{ADC code} &= \frac{V_{IN}}{V_{REF}} \\
 &= \frac{IDAC1 * (R_{RTD} + R_{LEAD1}) - IDAC2 * R_{LEAD2}}{(IDAC1 + IDAC2) * R_{REF}} \\
 &= \frac{R_{RTD} + R_{LEAD1} - R_{LEAD2}}{2 * R_{REF}} \\
 &= \frac{R_{RTD}}{2 * R_{REF}}
 \end{aligned}$$

Assume IDAC1 = IDAC2


Assume R_LEAD1 = R_LEAD2

Understanding IDAC specifications

ADS124S08 IDAC parameters

	Parameter	Condition	MIN	TYP	MAX	Unit
Compliance voltage ensures both IDACs can maintain constant current	Compliance voltage	10 μ A to 750 μ A, 0.1% deviation	AVSS		AVDD - 0.4	V
		1 mA to 2 mA, 0.1% deviation	AVSS		AVDD - 0.6	
Ratiometric measurements allow relaxed absolute IDAC specifications	Accuracy (each IDAC)	T _A = 25°C, 10 μ A to 100 μ A	-5%	0.7%	5%	
		T _A = 25°C, 250 μ A to 2 mA	-3%	0.5%	3%	
	Temperature drift (each IDAC)	10 μ A to 750 μ A		20	120	ppm/°C
		1 mA to 2 mA		10	80	
Matching specifications are most critical for 3-wire RTD systems using 2x IDACs	Current mismatch between IDACs	T _A = 25°C, 10 μ A to 100 μ A		0.15%	0.8%	
		T _A = 25°C, 250 μ A to 750 μ A		0.10%	0.6%	
		T _A = 25°C, 1 mA to 2 mA		0.07%	0.4%	
	Temperature drift matching between IDACs	10 μ A to 100 μ A		3	25	ppm/°C
		250 μ A to 2 mA		2	15	

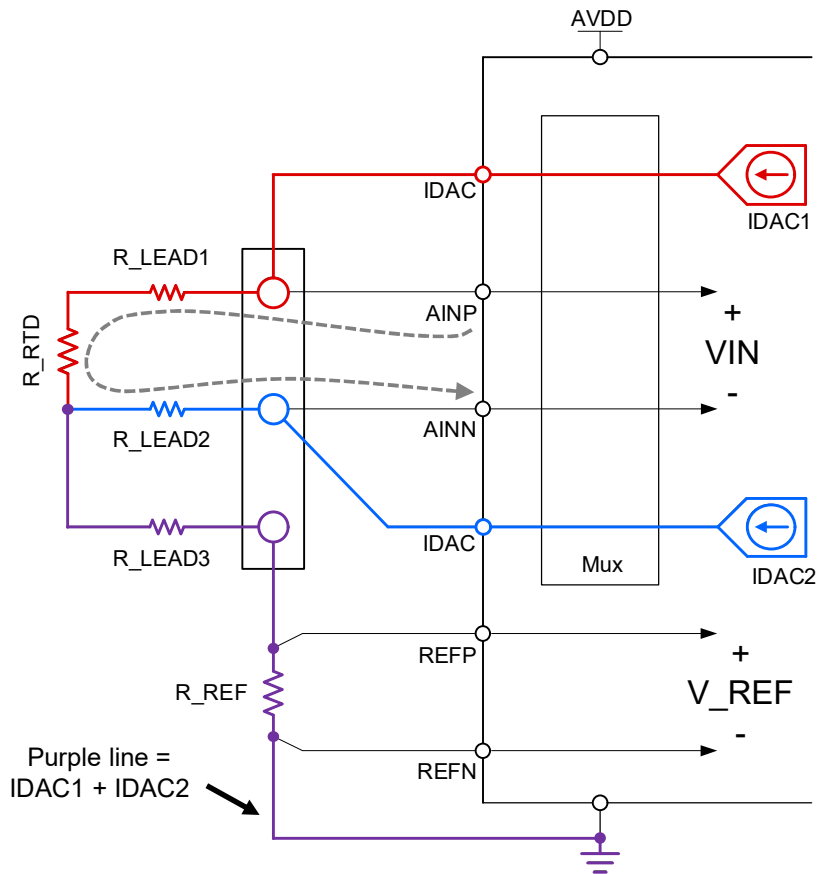How IDAC mismatch errors affect 3-wire RTDs



ADS124S08 IDAC parameters


Parameter	Condition	MIN	TYP	MAX	Unit
Current mismatch between IDACs	T _A = 25°C, 10 μA to 100 μA		0.15%	0.8%	
	T _A = 25°C, 250 μA to 750 μA		0.10%	0.6%	
	T _A = 25°C, 1 mA to 2 mA		0.07%	0.4%	

$$\text{ADC code} = \frac{V_{IN}}{V_{REF}}$$

$$= \frac{\text{IDAC1} * (R_{RTD} + R_{LEAD}) - \text{IDAC2} * R_{LEAD}}{(\text{IDAC1} + \text{IDAC2}) * R_{REF}}$$

IDAC mismatch error (E_{IM})
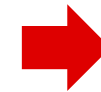
$$E_{IM} = 1 - \frac{\text{IDAC1}}{\text{IDAC2}}$$



- IDAC1 = 500 μA
- IDAC2 = 503 μA
- Mismatch error = 0.006 (0.6%)

$$\text{IDAC1} = \text{IDAC2} * (1 - E_{IM})$$

How IDAC mismatch affects 3-wire RTDs (LS R_REF)

$$\text{ADC code} = \frac{\text{IDAC1} * (\text{R_RTD} + \text{R_LEAD}) - \text{IDAC2} * \text{R_LEAD}}{(\text{IDAC1} + \text{IDAC2}) * \text{R_REF}}$$

$$\text{ADC code} = \frac{\cancel{\text{IDAC2}} * (1 - E_{\text{IM}}) * (\text{R_RTD} + \text{R_LEAD}) - \cancel{\text{IDAC2}} * \text{R_LEAD}}{[\cancel{\text{IDAC2}} * (1 - E_{\text{IM}}) + \cancel{\text{IDAC2}}] * \text{R_REF}}$$

IDAC mismatch error (E_{IM})

$$E_{\text{IM}} = 1 - \frac{\text{IDAC1}}{\text{IDAC2}}$$



$$\text{ADC code} = \frac{(\text{R_RTD} + \text{R_LEAD} - \text{R_LEAD} * E_{\text{IM}} - \text{R_RTD} * E_{\text{IM}}) - \text{R_LEAD}}{[(1 - E_{\text{IM}}) + 1] * \text{R_REF}}$$

$$\text{IDAC1} = \text{IDAC2} * (1 - E_{\text{IM}})$$

$$\text{ADC code} = \frac{\text{R_RTD} * (1 - E_{\text{IM}}) - \text{R_LEAD} * E_{\text{IM}}}{(2 - E_{\text{IM}}) * \text{R_REF}}$$

$$\text{ADC code} = \frac{\text{R_RTD} * (1 - E_{\text{IM}})}{\text{R_REF} * (2 - E_{\text{IM}})} - \frac{\text{R_LEAD} * E_{\text{IM}}}{\text{R_REF} * (2 - E_{\text{IM}})}$$

How much ADC error does IDAC mismatch contribute?

Calculating ADC error due to E_{IM} (LS R_{REF})

General form of the error equation

$$\text{ADC error} = \left(\frac{\text{ADC code}_{\text{Mismatch}} - \text{ADC code}_{\text{Ideal}}}{\text{ADC code}_{\text{Ideal}}} \right) * 100\%$$

Apply system-specific expressions

$$\text{ADC error} = \left(\frac{\left[\frac{R_{RTD} * (1 - E_{IM})}{R_{REF} * (2 - E_{IM})} - \frac{R_{LEAD} * E_{IM}}{R_{REF} * (2 - E_{IM})} \right] - \left[\frac{R_{RTD}}{2 * R_{REF}} \right]}{\frac{R_{RTD}}{2 * R_{REF}}} \right) * 100\%$$

Divide out R_{REF}

$$\text{ADC error} = \left(\frac{\left[\frac{R_{RTD} * (1 - E_{IM})}{2 - E_{IM}} - \frac{R_{LEAD} * E_{IM}}{2 - E_{IM}} \right] - \left[\frac{R_{RTD}}{2} \right]}{\frac{R_{RTD}}{2}} \right) * 100\%$$

Multiply top and bottom by $\frac{2}{R_{RTD}}$ and simplify

$$\text{ADC error} = \left(\frac{2 * (1 - E_{IM})}{2 - E_{IM}} - \frac{2 * R_{LEAD} * E_{IM}}{R_{RTD} * (2 - E_{IM})} - 1 \right) * 100\%$$


Set the constant $1 = \frac{2 - E_{IM}}{2 - E_{IM}}$

$$\text{ADC error} = \left(\frac{2 - 2 * E_{IM}}{2 - E_{IM}} - \frac{2 * R_{LEAD} * E_{IM}}{R_{RTD} * (2 - E_{IM})} - \frac{2 - E_{IM}}{2 - E_{IM}} \right) * 100\%$$

Simplify and factor out the common variable $\frac{-E_{IM}}{2 - E_{IM}}$

$$\text{ADC error} = \frac{-E_{IM}}{2 - E_{IM}} * \left(1 + \frac{2 * R_{LEAD}}{R_{RTD}} \right) * 100\%$$

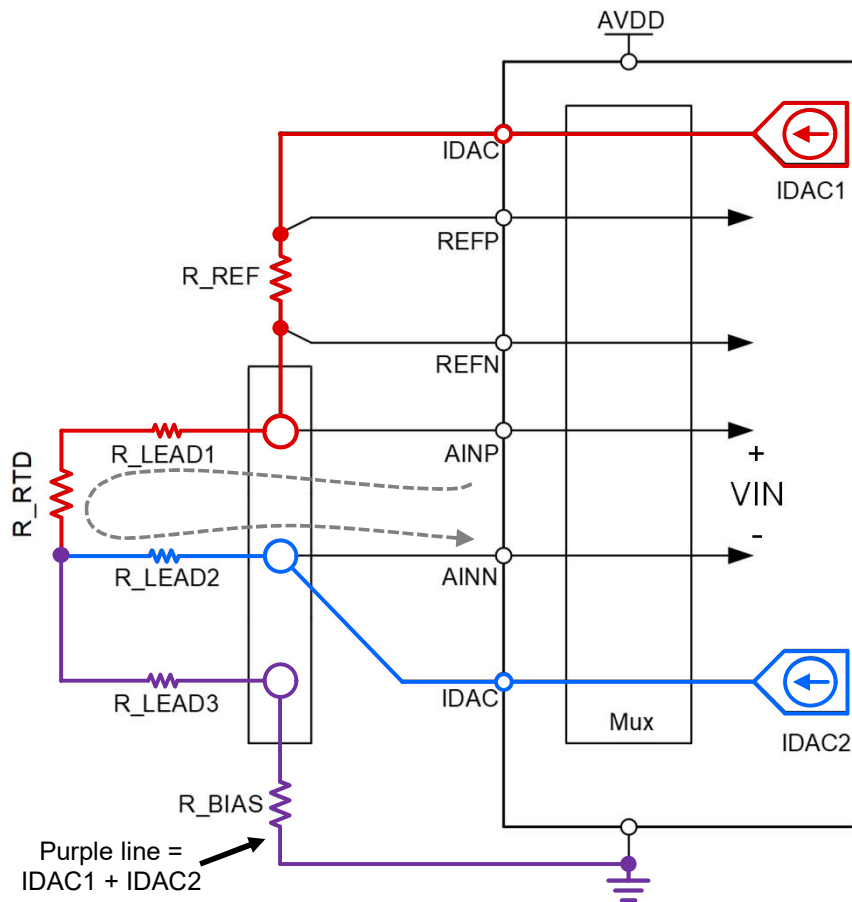Measuring VIN (3-wire RTD, 2x IDACs, HS R_REF)



$$V_{IN} = A_{INP} - A_{INN}$$


$$V_{IN} = V_{LEAD1} + V_{RTD} - V_{LEAD2}$$

- $V_{LEAD1} = IDAC1 * R_{LEAD1}$
- $V_{RTD} = IDAC1 * R_{RTD}$
- $V_{LEAD2} = IDAC2 * R_{LEAD2}$

$$V_{IN} = IDAC1 * (R_{RTD} + R_{LEAD1}) - IDAC2 * R_{LEAD2}$$

(same VIN equation as low-side R_REF configuration)

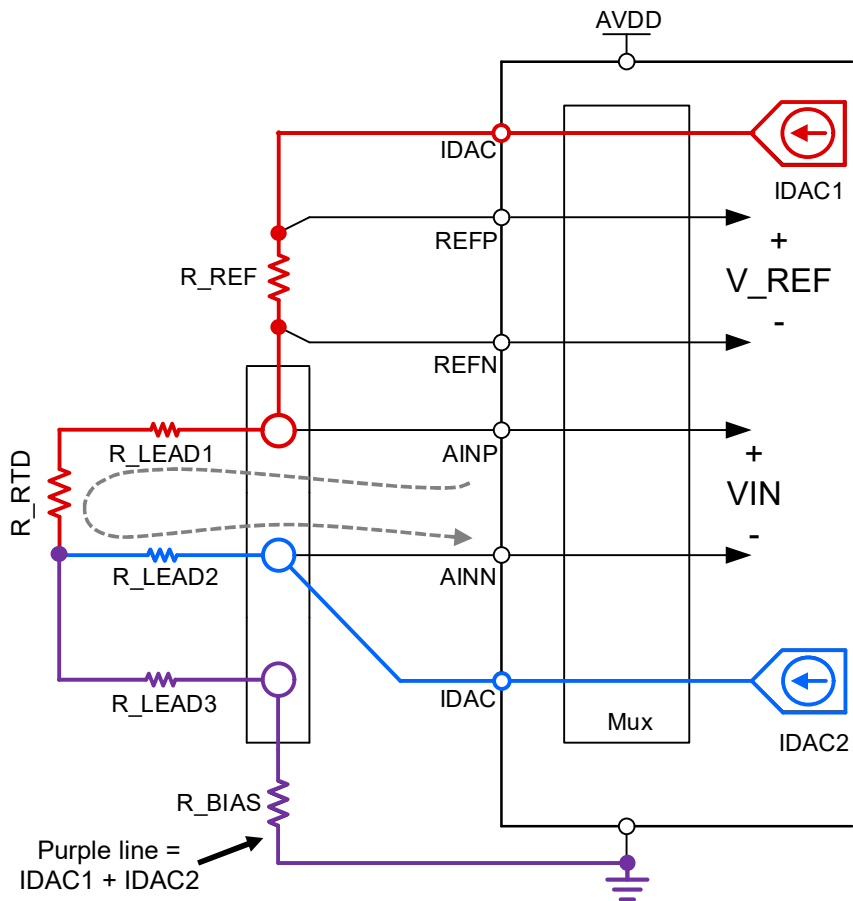ADC output code (3-wire RTD, 2x IDACs, HS R_REF)



$$V_{IN} = IDAC1 * (R_{RTD} + R_{LEAD1}) - IDAC2 * R_{LEAD2}$$

$$V_{REF} = IDAC1 * R_{REF}$$

$$ADC\ code = \frac{V_{IN}}{V_{REF}}$$

$$= \frac{IDAC1 * (R_{RTD} + R_{LEAD1}) - IDAC2 * R_{LEAD2}}{(IDAC1) * R_{REF}}$$

$$= \frac{R_{RTD} + R_{LEAD1} - R_{LEAD2}}{R_{REF}}$$

$$= \frac{R_{RTD}}{R_{REF}}$$

Assume
IDAC1 = IDAC2

Assume
R_LEAD1 = R_LEAD2

What if IDAC1 ≠ IDAC2?

How IDAC mismatch affects 3-wire RTDs (HS R_REF)

$$\text{ADC code} = \frac{\text{IDAC1} * (\text{R_RTD} + \text{R_LEAD}) - \text{IDAC2} * \text{R_LEAD}}{\text{IDAC1} * \text{R_REF}}$$

$$\text{ADC code} = \frac{\cancel{\text{IDAC2}} * (1 - E_{\text{IM}}) * (\text{R_RTD} + \text{R_LEAD}) - (\cancel{\text{IDAC2}} * \text{R_LEAD})}{[\cancel{\text{IDAC2}} * (1 - E_{\text{IM}})] * \text{R_REF}}$$

IDAC mismatch error (E_{IM})

$$E_{\text{IM}} = 1 - \frac{\text{IDAC1}}{\text{IDAC2}}$$



$$\text{ADC code} = \frac{\text{R_RTD} - \text{R_RTD} * E_{\text{IM}} - \text{R_LEAD} * E_{\text{IM}} + \cancel{\text{R_LEAD}} - \cancel{\text{R_LEAD}}}{(1 - E_{\text{IM}}) * \text{R_REF}}$$

$$\text{IDAC1} = \text{IDAC2} * (1 - E_{\text{IM}})$$

$$\text{ADC code} = \frac{\text{R_RTD} * (1 - E_{\text{IM}})}{\text{R_REF} * (1 - E_{\text{IM}})} - \frac{\text{R_LEAD} * E_{\text{IM}}}{(1 - E_{\text{IM}}) * \text{R_REF}}$$

$$\text{ADC code} = \frac{\text{R_RTD}}{\text{R_REF}} - \frac{\text{R_LEAD} * E_{\text{IM}}}{\text{R_REF} * (1 - E_{\text{IM}})}$$

How much ADC error does IDAC mismatch contribute?

Calculating ADC error due to E_{IM} (HS R_{REF})

General form of the error equation

$$\text{ADC error} = \left(\frac{\text{ADC code}_{\text{Mismatch}} - \text{ADC code}_{\text{Ideal}}}{\text{ADC code}_{\text{Ideal}}} \right) * 100\%$$

Apply system-specific expressions

$$\text{ADC error} = \left(\frac{\left[\frac{\cancel{R_{RTD}}}{\cancel{R_{REF}}} - \frac{R_{LEAD} * E_{IM}}{\cancel{R_{REF}} * (1 - E_{IM})} \right] - \left[\frac{\cancel{R_{RTD}}}{\cancel{R_{REF}}} \right]}{\frac{R_{RTD}}{\cancel{R_{REF}}}} \right) * 100\%$$

Divide out R_{REF}

$$\text{ADC error} = \left(\frac{\left[R_{RTD} + \frac{R_{LEAD} * E_{IM}}{1 - E_{IM}} \right] - R_{RTD}}{R_{RTD}} \right) * 100\%$$

Divide each term by R_{RTD}

$$\text{ADC error} = \left(\left[\frac{\cancel{R_{RTD}}}{\cancel{R_{RTD}}} + \frac{R_{LEAD} * E_{IM}}{R_{RTD} * (1 - E_{IM})} \right] - \frac{\cancel{R_{RTD}}}{\cancel{R_{RTD}}} \right) * 100\%$$

Simplify




$$\text{ADC error} = \frac{E_{IM}}{1 - E_{IM}} * \left(\frac{R_{LEAD}}{R_{RTD}} \right) * 100\%$$

Comparing errors due to E_{IM} (LS R_{REF} & HS R_{REF})

Condition	ADC Error		Comment
	Low-side R_{REF}	High-side R_{REF}	
General form	$= \frac{-E_{IM}}{2 - E_{IM}} * \left(1 + \frac{2 * R_{LEAD}}{R_{RTD}} \right) * 100\%$	$= \frac{E_{IM}}{1 - E_{IM}} * \left(\frac{R_{LEAD}}{R_{RTD}} \right) * 100\%$	
E_{IM} is small (<2%)	$\approx \frac{-E_{IM}}{2} * \left(1 + \frac{2 * R_{LEAD}}{R_{RTD}} \right) * 100\%$	$\approx E_{IM} * \left(\frac{R_{LEAD}}{R_{RTD}} \right) * 100\%$	Typical E_{IM} values are very small e.g. ADS124S08 = 0.15%
$R_{RTD} \approx R_{LEAD}$	$\approx -\frac{3}{2} * E_{IM} * 100\%$	$\approx E_{IM} * 100\%$	When R_{RTD} is small, the LS R_{REF} error due to E_{IM} is 1.5x larger compared to the HS R_{REF}
$R_{RTD} \gg R_{LEAD}$	$\approx -\frac{1}{2} * E_{IM} * 100\%$	$\approx 0\%$	When R_{RTD} is large, a HS R_{REF} has virtually no error due to E_{IM}



Plotting errors due to E_{IM} (LS R_{REF} & HS R_{REF})

Low-side R_{REF}	High-side R_{REF}
$= \frac{-E_{IM}}{2 - E_{IM}} * \left(1 + \frac{2 * R_{LEAD}}{R_{RTD}}\right) * 100\% \approx -\frac{1}{2} * E_{IM} * 100\%$	$= \frac{E_{IM}}{1 - E_{IM}} * \left(\frac{R_{LEAD}}{R_{RTD}}\right) * 100\% \approx 0\%$

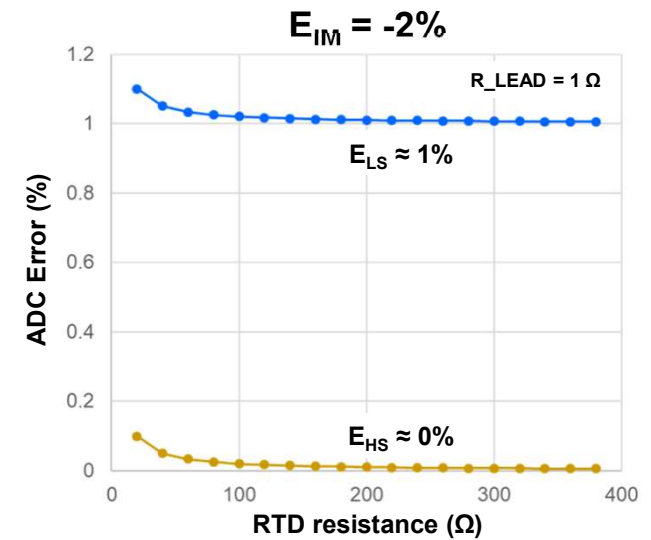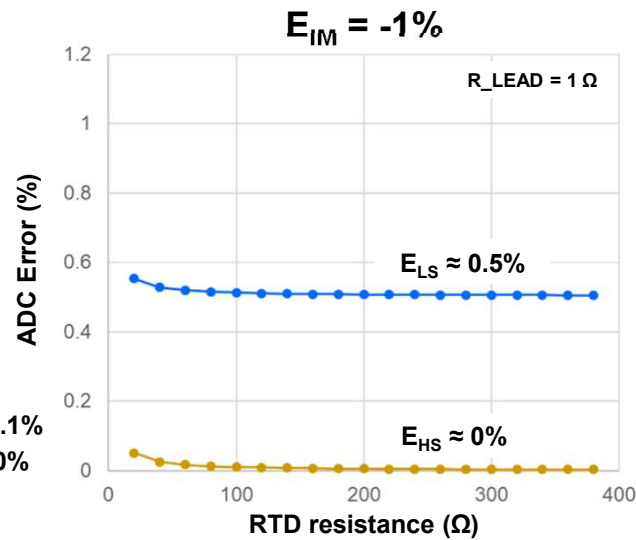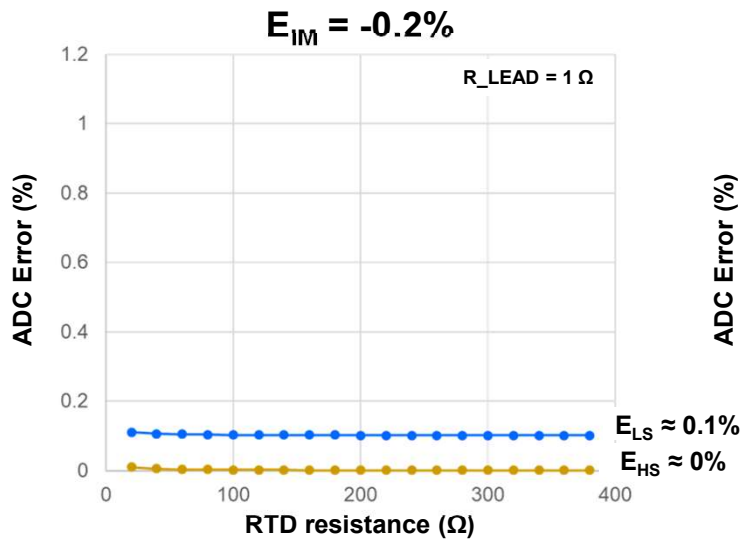

****Choose high-side R_{REF} if possible****

How IDAC chop works (LS R_REF)

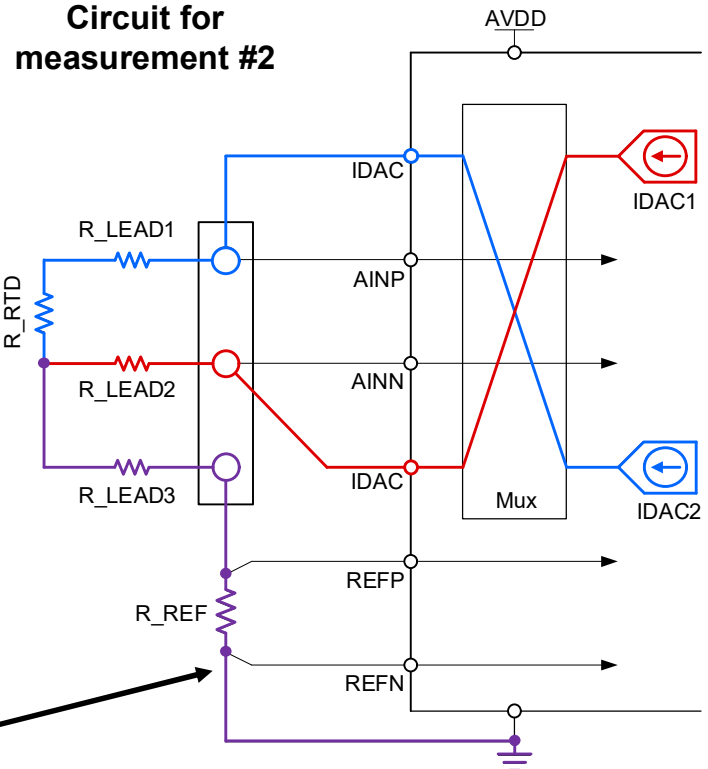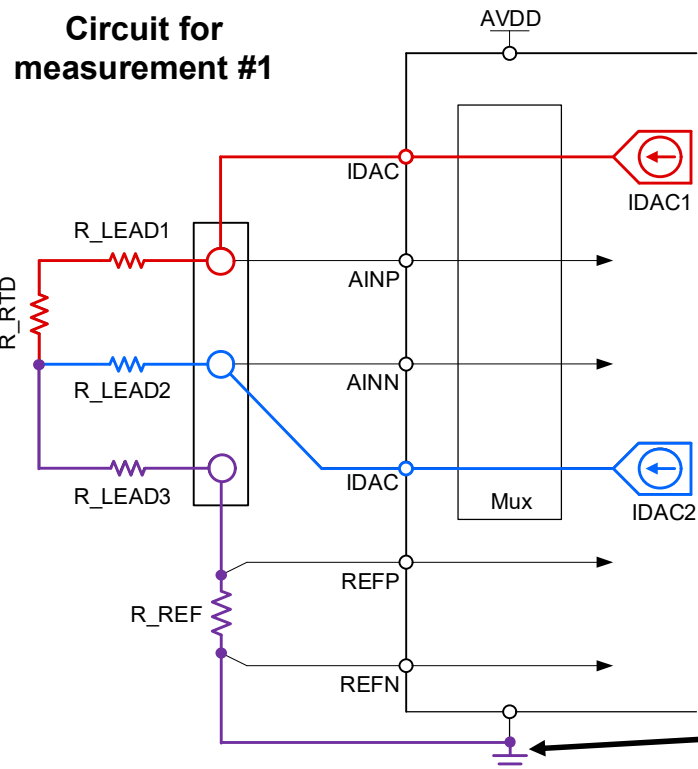

Purple line = IDAC1 + IDAC2

$$\text{ADC Code \#1} = \frac{\text{IDAC1} * (\text{R_RTD} + \text{R_LEAD1}) - \text{IDAC2} * \text{R_LEAD2}}{\text{R_REF} * (\text{IDAC1} + \text{IDAC2})}$$

$$\text{ADC Code \#2} = \frac{\text{IDAC2} * (\text{R_RTD} + \text{R_LEAD1}) - \text{IDAC1} * \text{R_LEAD2}}{\text{R_REF} * (\text{IDAC1} + \text{IDAC2})}$$

Calculating the IDAC chop result

General form of the error equation

$$ADC\ code = \frac{Measurement\ #1 + Measurement\ #2}{2}$$

Apply system-specific expressions

$$ADC\ code = \frac{\left(\frac{IDAC1 * (R_RTD + R_LEAD1) - IDAC2 * R_LEAD2}{R_REF * (IDAC1 + IDAC2)} + \frac{IDAC2 * (R_RTD + R_LEAD1) - IDAC1 * R_LEAD2}{R_REF * (IDAC1 + IDAC2)} \right)}{2}$$

Combine all IDAC1 and IDAC2 terms

$$ADC\ code = \frac{IDAC1 * (R_RTD + R_LEAD1 - R_LEAD2) + IDAC2 * (R_RTD + R_LEAD1 - R_LEAD2)}{2 * R_REF * (IDAC1 + IDAC2)}$$

Factor out the (R_RTD + R_LEAD1 - R_LEAD2) term

$$ADC\ code = \frac{(R_RTD + R_LEAD1 - R_LEAD2) * (IDAC1 + IDAC2)}{2 * R_REF * (IDAC1 + IDAC2)}$$

Simplify assuming R_LEAD1 = R_LEAD2

$$ADC\ code = \frac{R_RTD * (IDAC1 + IDAC2)}{2 * R_REF * (IDAC1 + IDAC2)}$$

Reduces to ideal ADC output code equation

$$ADC\ code = \frac{R_RTD}{2 * R_REF}$$

**Thanks for your time!
Please try the quiz.**

Quiz: Challenges with 3-wire RTD systems

1. (T/F) Measuring 3-wire RTDs using one IDAC generally has lower error compared to using two IDACs because the two IDAC method introduces IDAC mismatch errors.
 - a) True
 - b) False
2. When measuring 3-wire RTDs using two IDACs, which configuration has the lowest error?
 - a) Low-side reference configuration
 - b) High-side reference configuration
3. (T/F) Measuring 3-wire RTDs using two IDACs is faster compared to using one IDAC because the two IDAC method only requires one measurement.
 - a) True
 - b) False

Quiz: Challenges with 3-wire RTD systems

4. What is IDAC chop used for?
 - a) It is used to effectively cut the IDAC into multiple equal sized pieces
 - b) It is a method used on single IDAC measurements where the IDAC is pulse-width modulated
 - c) It is used to remove IDAC mismatch in 3-wire, two IDAC systems by taking one measurement, then swapping the position of the IDACs, taking another measurement, and finally averaging the results

5. What is the disadvantage of IDAC chop?
 - a) Two measurements are required, which increases measurement time
 - b) It always requires an external multiplexer
 - c) It can lead to uncontrolled oscillations

Thanks for your time!



© Copyright 2023 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com