

# Op Amp Technology Overview

Developed by Art Kay, Thomas Kuehl, and Tim Green


Presented by Ian Williams

Precision Analog – Op Amps

# Bipolar vs. CMOS / JFET


- Transistor technologies
  - Bipolar, CMOS and JFET
- Vos and Ib and Drift
  - Laser Trim, Package Trim, and Zero Drift
- Noise
  - JFET, MOSFET, and Bipolar (1/f noise)
- Input Structures
  - Rail-to-Rail, Charge Pump
  - Chopper (Zero-Drift)
    - Chopper Noise Sources
  - Input crossover distortion
  - Input back-to-back diodes
- Output Structures – The “Claw Curve”
  - Rail-to-Rail vs. Non Rail-to-Rail
  - Open Loop Output Impedance, Zo
- Bandwidth
- Summary
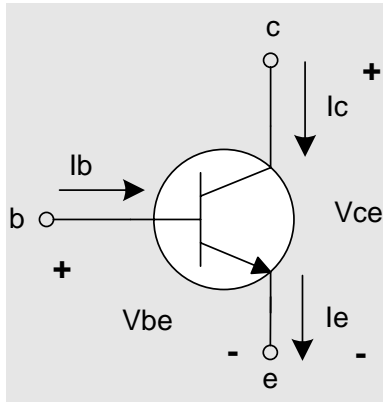
# Bipolar, CMOS, JFET (Op Amp input device structures)




NPN **Bipolar**

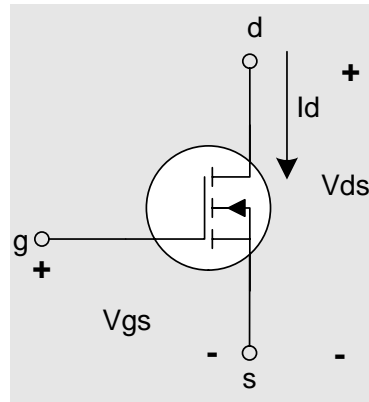- 1) **Current Controlled Device**
- 2) **“Current Controlled Current Source”**
- 3)  **$I_c = I_b \cdot h_{fe}$**
- 4)  **$I_b = 0A$  turns bipolar off**
- 5) **Base is op amp +/- input**
- 6) **Highest Op Amp input current**



N-Channel **CMOS**

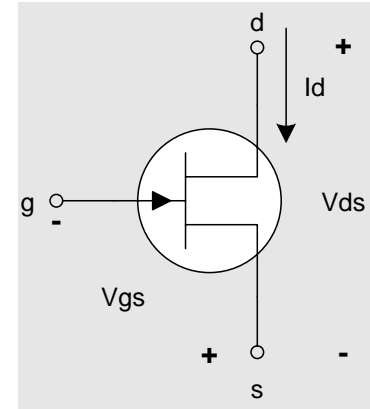
- 1) **Voltage Controlled Device**
- 2) **“Voltage Controlled Resistor”**
- 3)  **$V_{gs} > 2V$  controls  $R_{ds\_on}$**
- 4)  **$V_{gs}=0V$  turns MOSFET off**
- 5) **Gate is op amp +/- input**
- 6) **Very Low Op Amp input current**



N-Channel **JFET**

- 1) **Voltage Controlled Device**
- 2) **“Voltage Controlled Resistor”**
- 3)  **$0V < V_{gs} < -2V$  controls  $R_{ds\_on}$**
- 4)  **$V_{gs} < -2V$  turns JFET off**
- 5) **Gate is op amp +/- input**
- 6) **Very Low Op Amp input current**

# Vos & Ib: Model and Hand Calculations

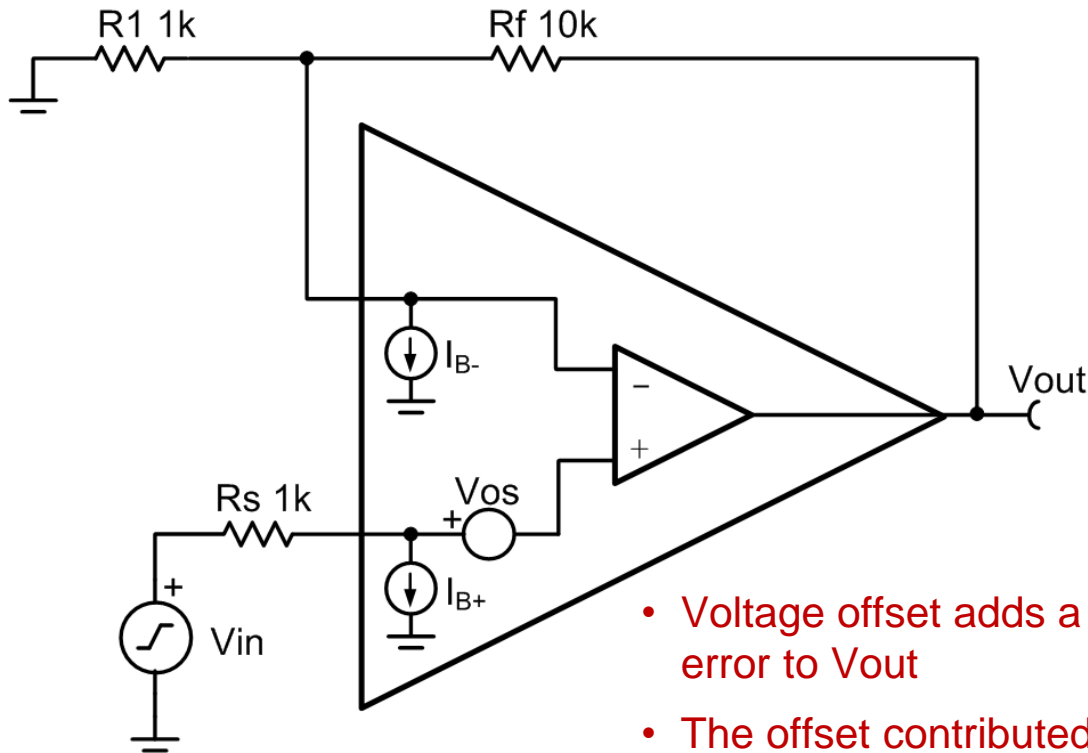

- Voltage offset adds a dc error to  $V_{out}$
- The offset contributed is unique to each device

$$R_{eq} = \frac{R_f \cdot R_1}{R_f + R_1}$$

$$G_n = \frac{R_f}{R_1} + 1$$

$$V_{o\_vos} = V_{os} \cdot G_n$$


$$V_{o_{Ib+}} = I_b \cdot R_s \cdot G_n$$

$$V_{o_{Ib-}} = I_b \cdot R_{eq} \cdot G_n$$


$$V_{o\_os\_Ib} = V_{o\_vos} + V_{o_{Ib+}} + V_{o_{Ib-}}$$

# What's inside the Amplifier – Bipolar vs. CMOS

Bipolar input op amp

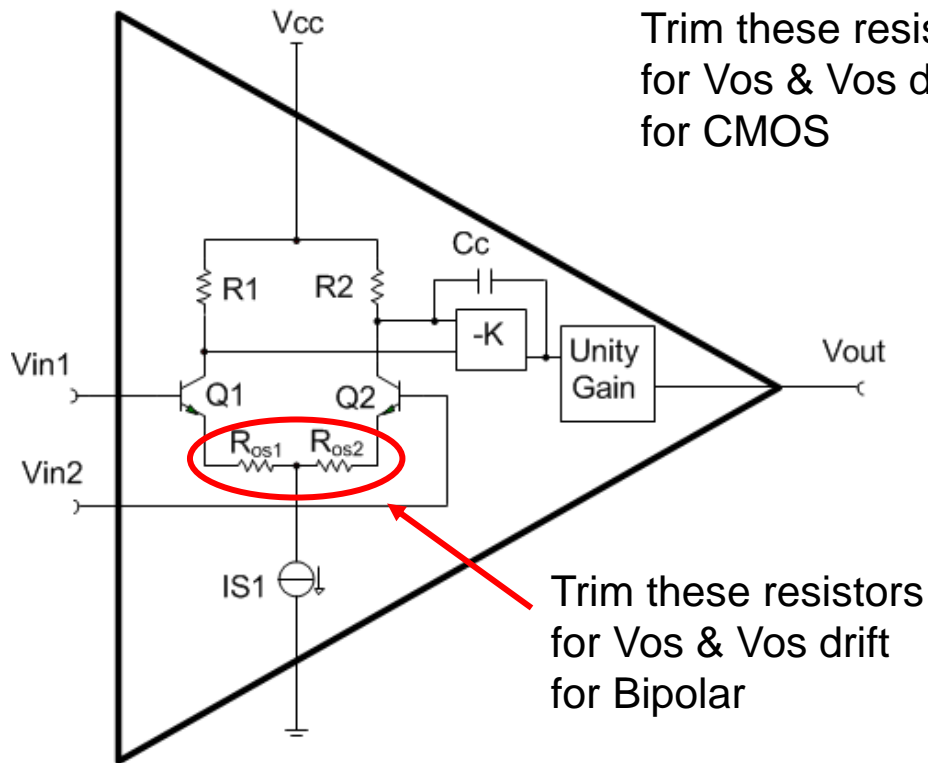

CMOS input op amp

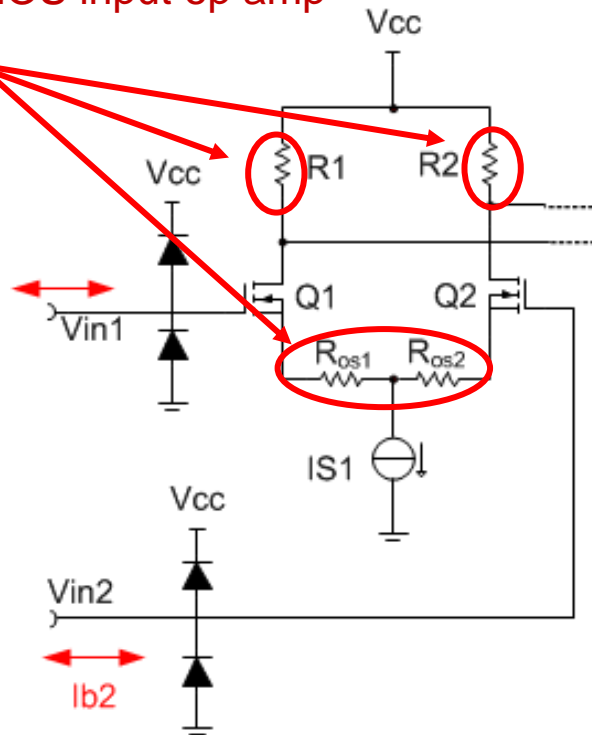


# Bipolar and CMOS

Model	Tech- nology	Rail- to- rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA211	Bipolar	RRO	4.5 - 36 V	3.6 mA	60 $\mu$ V	0.35 $\mu$ V/ $^{\circ}$ C	60 nA	1.1 nV/ $\sqrt{\text{Hz}}$	45 MHz	27 V/us
OPA350	CMOS	RRIO	2.7 - 5.5 V	5.2 mA	150 $\mu$ V	4 $\mu$ V/ $^{\circ}$ C	0.5 pA	16 nV/ $\sqrt{\text{Hz}}$	38 MHz	22 V/us

- OPA2x11 - Ultra low Noise, low power, precision op amp
  - Ideal for driving high-precision 16-bit ADCs or buffering the output of high-resolution digital-to-analog converters DACs
- OPAX350 High-Speed, Single-Supply, Rail-to-Rail I/O
  - High-performance ADC driver, very high  $C_{\text{Load}}$  drive capability


# Inherent Drift of Bipolar vs. CMOS

*Bipolar Drift of Input Stage*

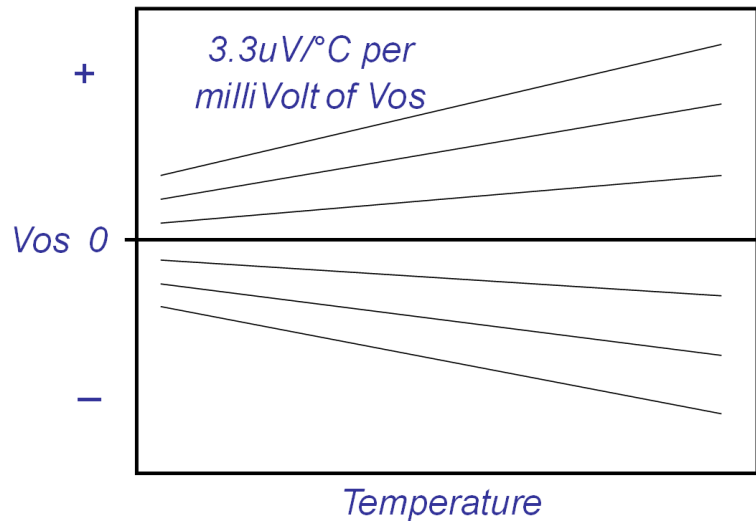


- Drift is proportional to offset
- When Vos trimmed to zero, drift is near zero.
- Simple one step trim: just trim offset

*CMOS & JFET Drift of Input Stage*

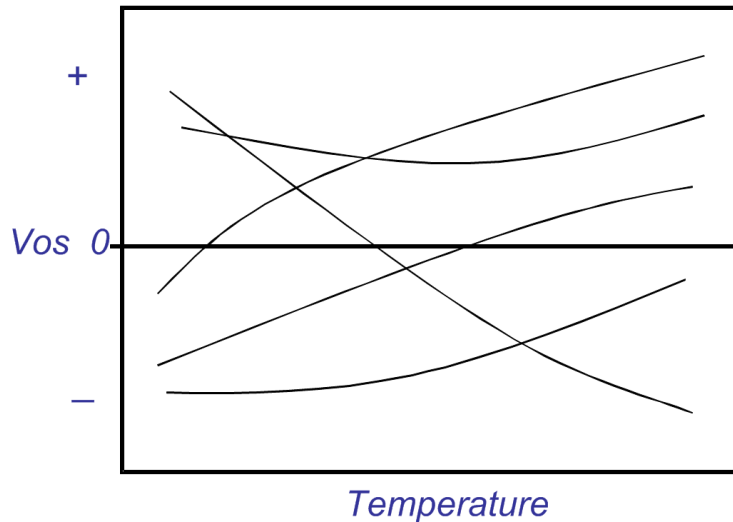


- Frequently more curvature than bipolar
- When Vos trimmed to zero, drift remains.
- More complex two part trim: drift first, then offset
- Offset and drift trims interact, difficult to optimize both

# Laser Trim – What does it look like?

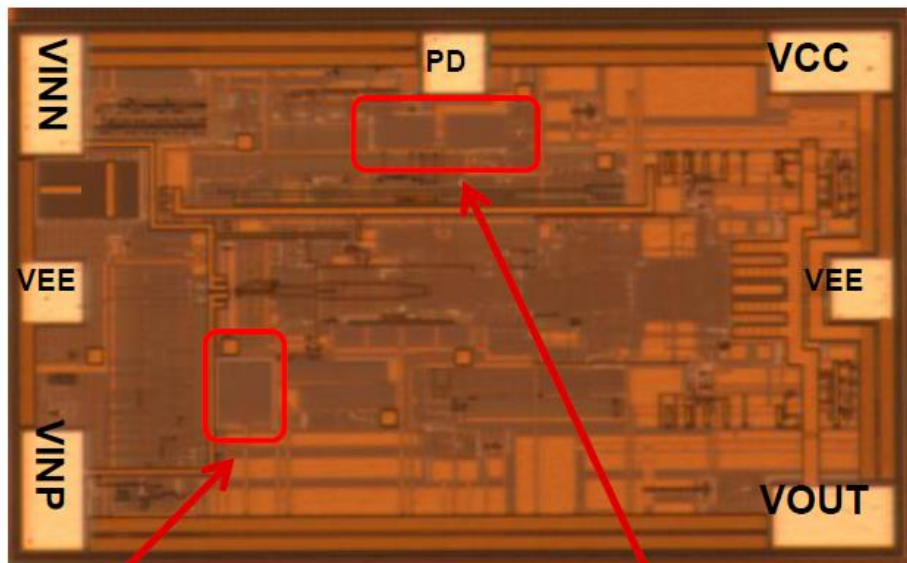

**IQ Trim**

**Vos Trim**

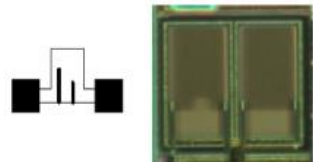

- Bipolar, CMOS, JFET can be used
  - Only way to trim bipolar
- Trimmed in wafer form before package
- Laser makes narrow cuts in resistor
- Increases resistance continuously
- Circuit can be active, but laser may disturb circuit function—requires cutting in bursts (long test time)
- Generally each trim has a pair of resistors for bidirectional trim





# Bipolar vs. CMOS

Op amps that utilize thin-film resistor laser trimming for improved offset and drift

Model	Technology	Rail-to-rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA1612	Bipolar	Out	4.5 – 36 V	3.6 mA	100 $\mu$ V	1 $\mu$ V/ $^{\circ}$ C	60 nA	1.1 nV/ $\sqrt$ Hz	40 MHz	27 V/ $\mu$ s
OPA320S	LV CMOS	RRIO	1.8 – 5.5 V	1.5 mA	40 $\mu$ V	1.5 $\mu$ V/ $^{\circ}$ C	0.2 pA	8.5 nV/ $\sqrt$ Hz	20 MHz	10 V/ $\mu$ s

- OPA1612 - SoundPlus™ High-Performance, Bipolar-Input Audio Op Amp
  - Achieves very low noise density with an ultralow distortion of 0.000015% at 1 kHz.
  - Rail-to-rail output swing to within 600 mV with a 2-k $\Omega$  load
- OPA320S - 20-MHz, Low-Noise, RRI/O, Low operating current, with shutdown
  - A combination of very low noise, high gain-bandwidth, and fast slew make it ideal for signal conditioning and sensor amplification requiring high gain

# Package level electronic trim, e-trim™

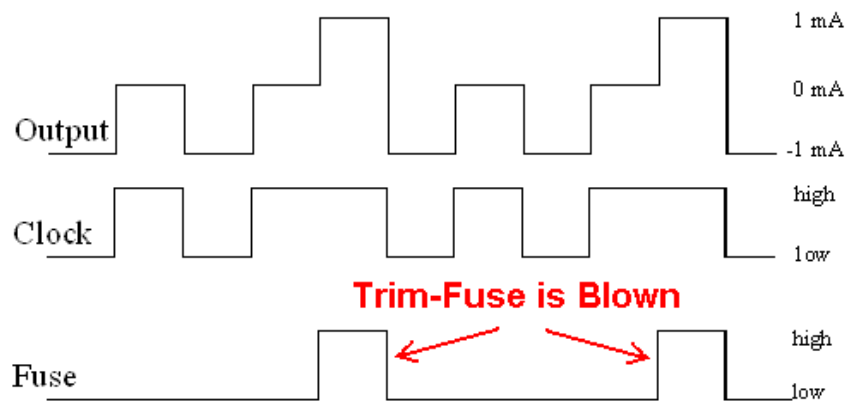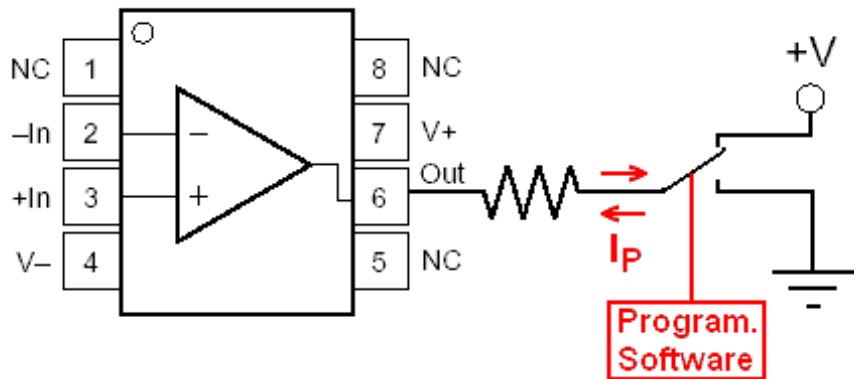


- CMOS op amps only due to digital circuitry requirements
- Standard pinout
  - Trim data is entered through output current load
- Blow and set internal fuses
- Disable trim mechanism after the trim is completed
  - No customer access to trim function
- Programmed fuses are read at each power-on

Model	Tech- nology	Rail- to- rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA376	LV CMOS	RRIO	2.2 – 5.5 V	760 $\mu$ A	5 $\mu$ V	0.26 $\mu$ V/°C	0.2 pA	7.5 nV/ $\sqrt$ Hz	5.5 MHz	2 V/ $\mu$ s
OPA192	HV CMOS	RRIO	8 – 36 V	1 mA	5 $\mu$ V	0.1 $\mu$ V/°C	5 pA	5.5 nV/ $\sqrt$ Hz	10 MHz	20 V/ $\mu$ s

- OPA376 – Precision, Low-noise, Low offset, Low quiescent current
  - Well-suited for driving SAR ADCs as well as 24-bit and higher resolution converters
- OPA192 - Precision, 36 V, Low offset, Fast slewing
  - differential input-voltage range to the supply rail
  - high output current ( $\pm$ 65 mA)

# What's inside the Amplifier – Bipolar vs. CMOS

Bipolar input op amp

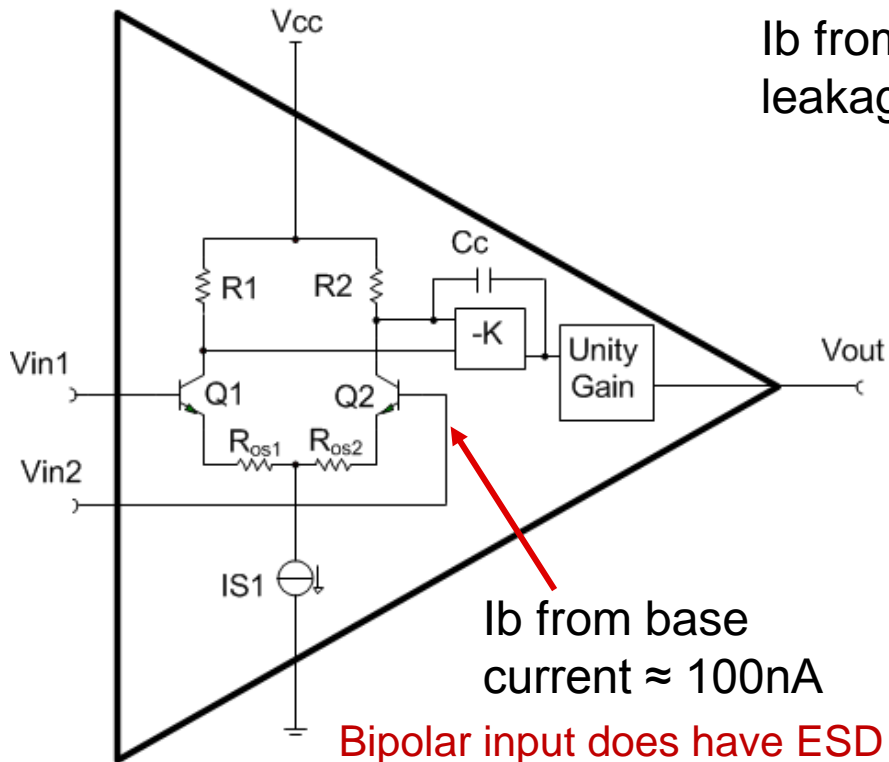


$I_b$  from base current  $\approx 100\text{nA}$

Bipolar input does have ESD cells, but  $I_b \gg I_{leak}$


CMOS input op amp

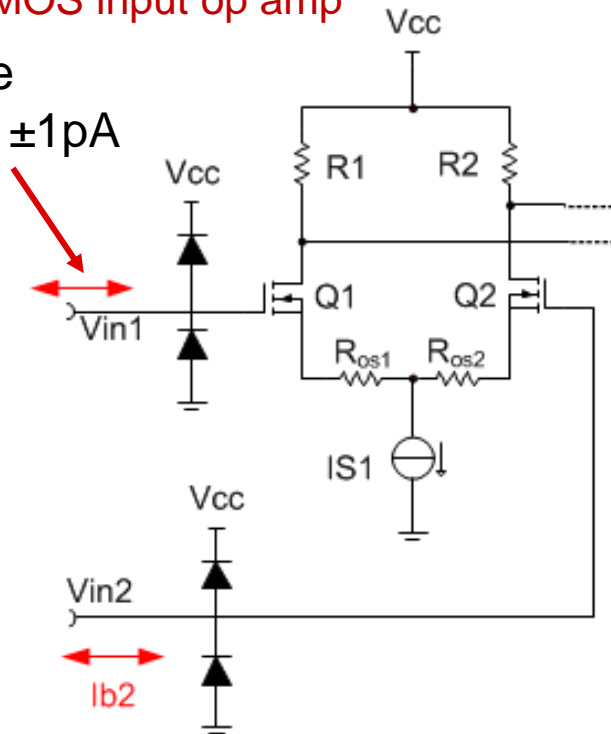$I_b$  from diode leakage  $I_b \approx \pm 1\text{pA}$



$I_{b2}$

# Bipolar - Bias Current Cancellation

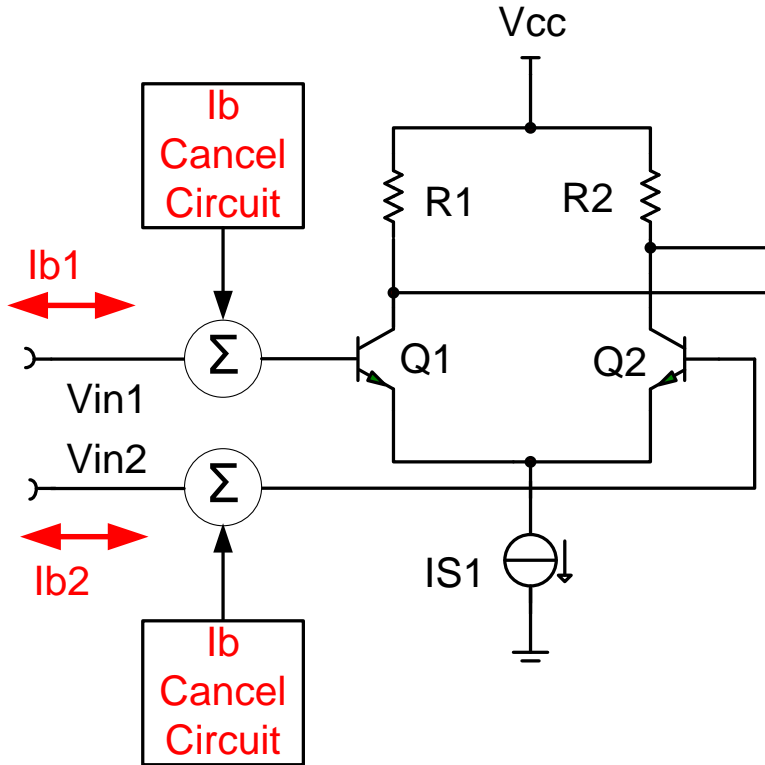

Bipolar IB	Typical
Uncancelled	100nA
Cancelled	1nA


# Bipolar - Bias Current Cancellation

## Cancellation vs non-cancellation

Model	Technology	Rail-to-rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA209	Bipolar with Ib cancel	RRO	4.5 - 36 V	2.2 mA	35 $\mu$ V	0.05 $\mu$ V/ $^{\circ}$ C	1 nA typ 4.5 nA max	2.2 nV/ $\sqrt{\text{Hz}}$	18 MHz	6.4 V/ $\mu$ s
OPA211	Bipolar w/o Ib cancel	RRO	4.5 - 36 V	3.6 mA	60 $\mu$ V	0.35 $\mu$ V/ $^{\circ}$ C	60 nA typ 175 nA max	1.1 nV/ $\sqrt{\text{Hz}}$	45 MHz	27 V/ $\mu$ s


- OPA209 – 36 V, low power, noise, offset, drift and input bias current
  - Suitable for fast, high-precision applications. Has fast settling time to 16-bit accuracy
- OPA2x11 - Ultra low Noise, low power, precision op amp
  - Ideal for driving high-precision 16-bit ADCs, or buffering the output of high-resolution DACs
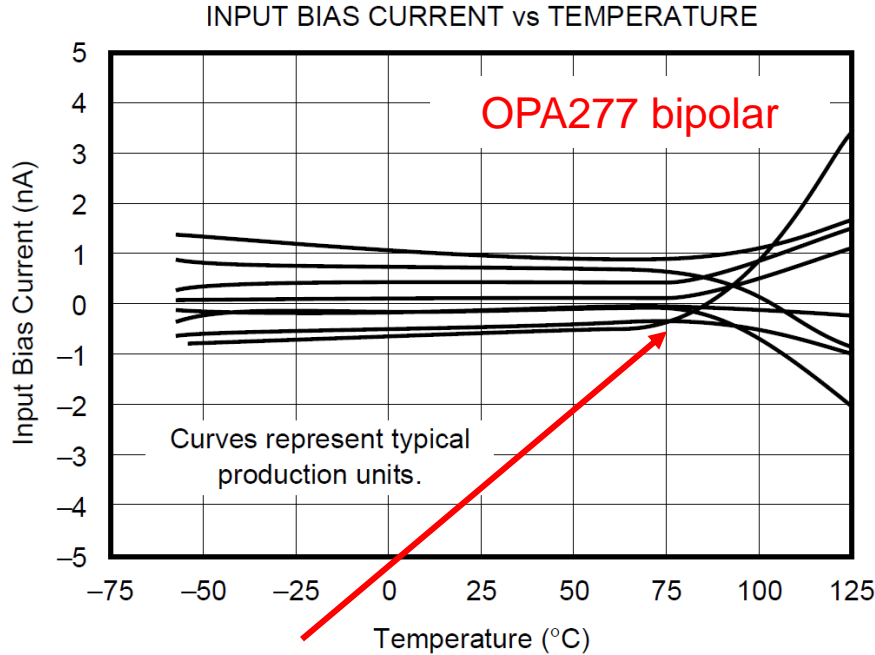
# Bipolar vs. CMOS bias current drift (I<sub>b</sub> vs Temp)


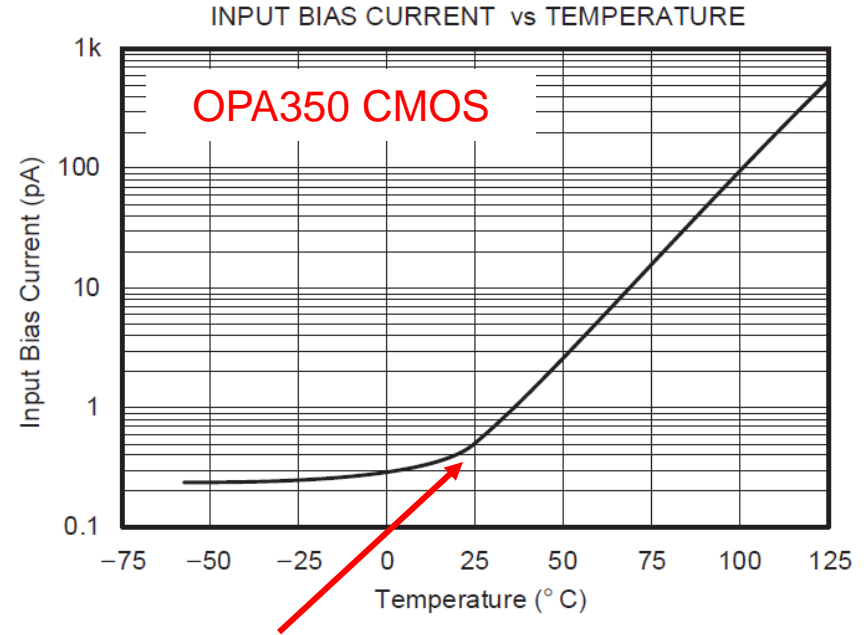
## Bipolar amplifier:


In this case you see a dramatic increase in bias current at 75 °C.



## CMOS amplifier:

In this case you see a dramatic increase in bias current at 25 °C. Note the logarithmic graph, which doubles every 10 °C.

# JFET, Bipolar, and CMOS Noise

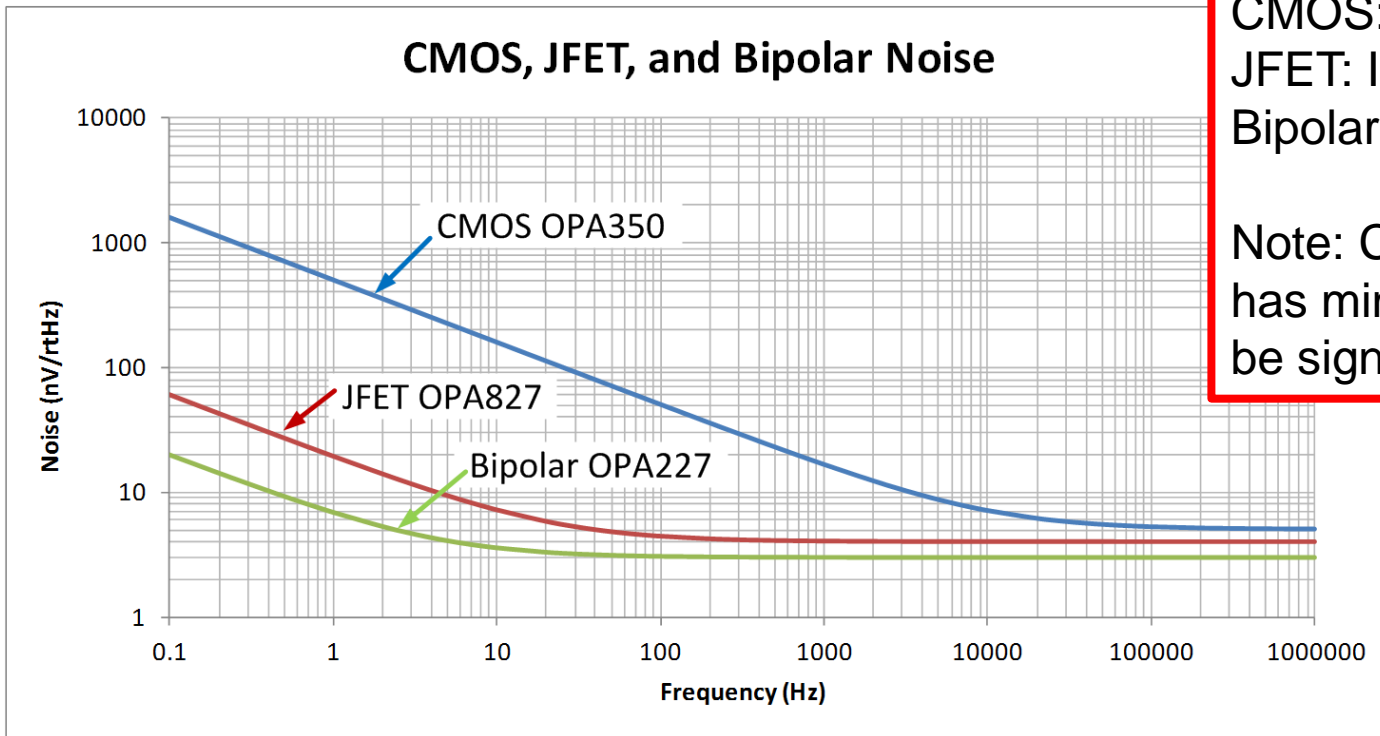

CMOS:  $I_{n_{350}} = 4\text{fA}/\text{rtHz}$   
JFET:  $I_{n_{827}} = 2.2\text{fA}/\text{rtHz}$   
Bipolar:  $I_{n_{277}} = 200\text{fA}/\text{rtHz}$

Note: CMOS current noise has minimal  $1/f$ , but it may be significant in bipolar





# JFET, Bipolar, and CMOS Noise

Model	Tech-nology	Rail-to-rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA827	JFET + Bipolar	No	8 – 36 V	4.8 mA	75 $\mu$ V	0.1 $\mu$ V/ $^{\circ}$ C	3 pA	4 nV/ $\sqrt$ Hz	22 MHz	28 V/ $\mu$ s
OPA227	Bipolar	No	10 – 36 V	3.7 mA	10 $\mu$ V	0.3 $\mu$ V/ $^{\circ}$ C	2.5 nA	3 nV/ $\sqrt$ Hz	8 MHz	2.3 V/ $\mu$ s
OPA350	CMOS	RRIO	2.7 – 5.5 V	5.2 mA	150 $\mu$ V	4 $\mu$ V/ $^{\circ}$ C	0.5 pA	16 nV/ $\sqrt$ Hz	38 MHz	22 V/ $\mu$ s

- OPA827 - Low-Noise, High-Precision, JFET-Input
  - Precision 16-bit to 18-bit mixed signal systems, transimpedance amplifiers
- OPA227 - High Precision, Low Noise
  - Ideal for applications requiring both AC and precision DC performance
- OPAx350 High-Speed, Single-Supply, Rail-to-Rail I/O
  - High-performance ADC driver, very high  $C_{Load}$  drive capability

# OPA703 Complementary CMOS – Rail-to-Rail


PARAMETER	CONDITION	MIN	TYP	MAX	UNITS
<b>INPUT VOLTAGE RANGE</b>					
Common-Mode Voltage Range	$V_{CM}$	$(V-) - 0.3$		$(V+) + 0.3$	V
Common-Mode Rejection Ratio	$CMRR$	$V_S = \pm 5V, (V-) - 0.3V < V_{CM} < (V+) + 0.3V$	70	90	dB
<b>over Temperature</b>		$V_S = \pm 5V, (V-) < V_{CM} < (V+)$	<b>68</b>		<b>dB</b>
		$V_S = \pm 5V, (V-) - 0.3V < V_{CM} < (V+) - 2V$	80	96	dB
<b>over Temperature</b>		$V_S = \pm 5V, (V-) < V_{CM} < (V+) - 2V$	<b>74</b>		<b>dB</b>

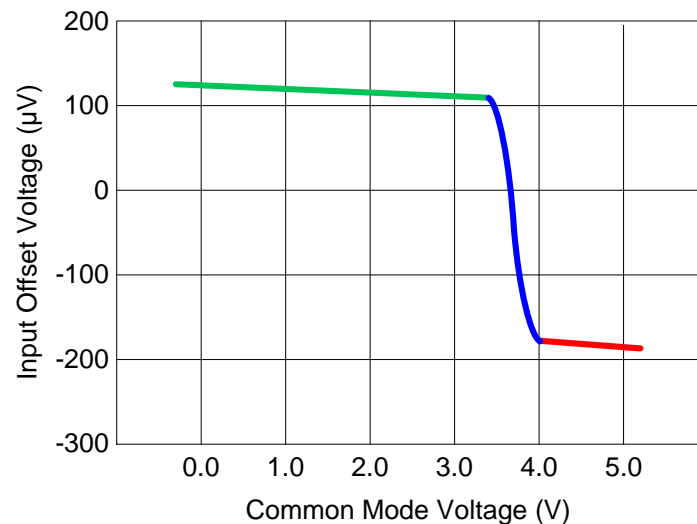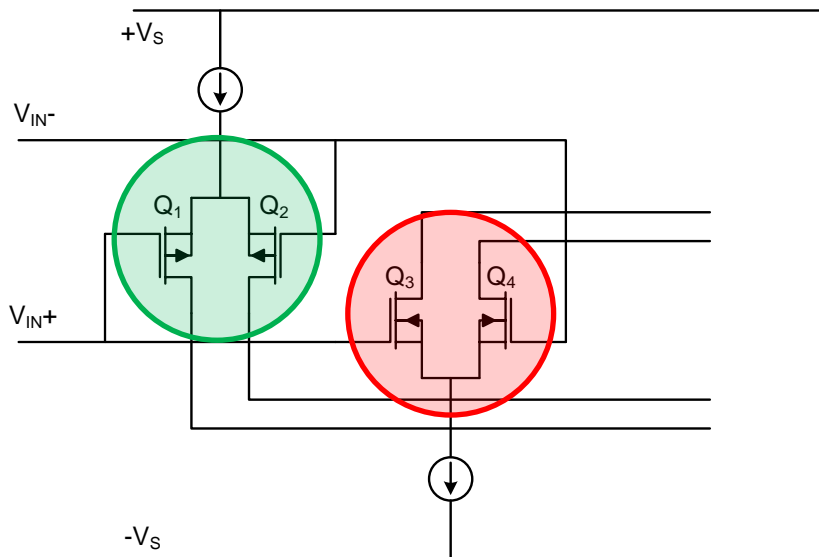


# Complementary CMOS – Rail-to-Rail

Abrupt offset change at input P-ch/ N-ch switchover point

Model	Tech- nology	Rail- to- rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA703	12 V CMOS	RRIO	4 - 12 V	160 $\mu$ A	35 $\mu$ V	4 $\mu$ V/ $^{\circ}$ C	1 pA	45 nV/ $\sqrt{\text{Hz}}$	1 MHz	0.6 V/ $\mu$ s
OPA314	LV CMOS	RRIO	1.8 – 5.5 V	150 $\mu$ A	60 $\mu$ V	1 $\mu$ V/ $^{\circ}$ C	0.4 pA	14 nV/ $\sqrt{\text{Hz}}$	2.7 MHz	1.5 V/ $\mu$ s




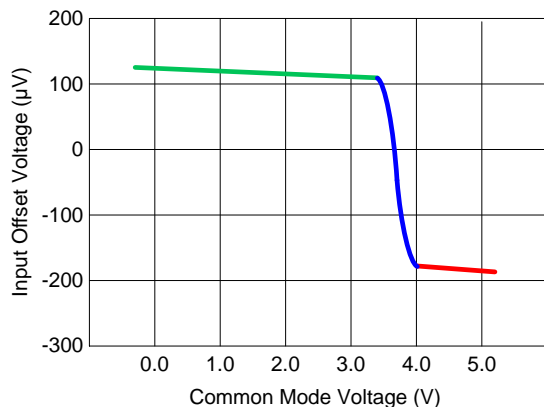


OPA703 0 to +5 V input,  $V_S \pm 5$  V

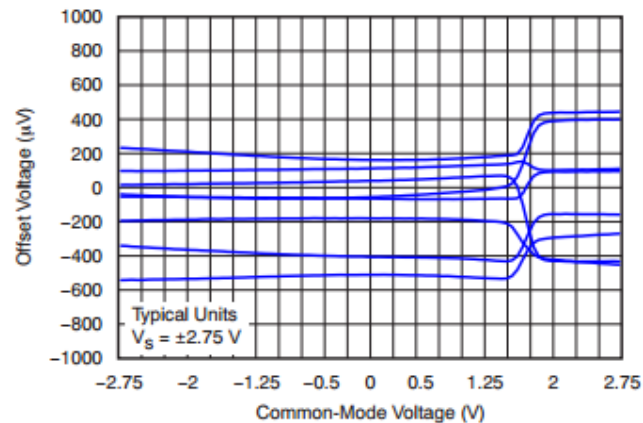

OPA314  $\pm 2.75$  V input,  $V_S \pm 2.75$  V


# Input Crossover Distortion

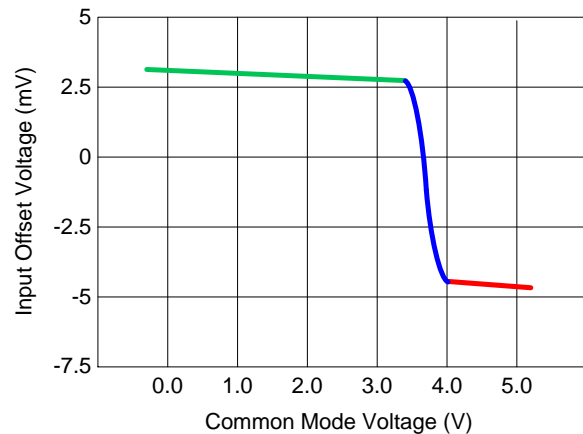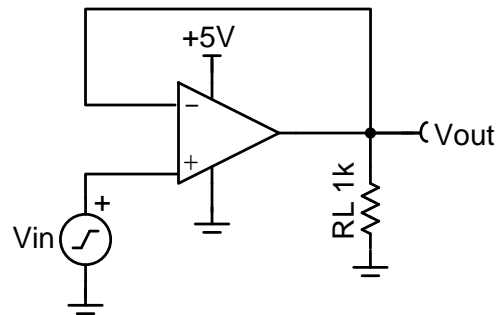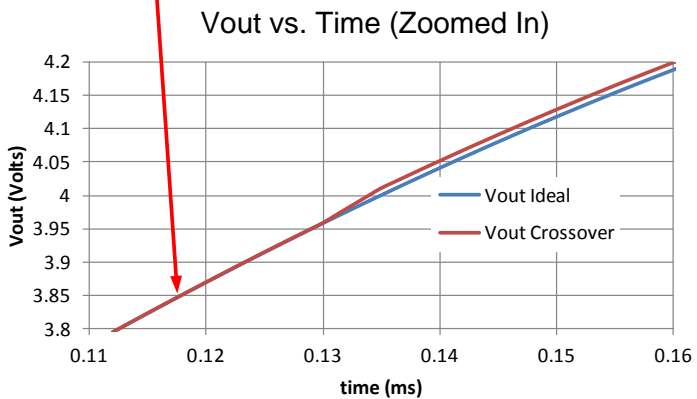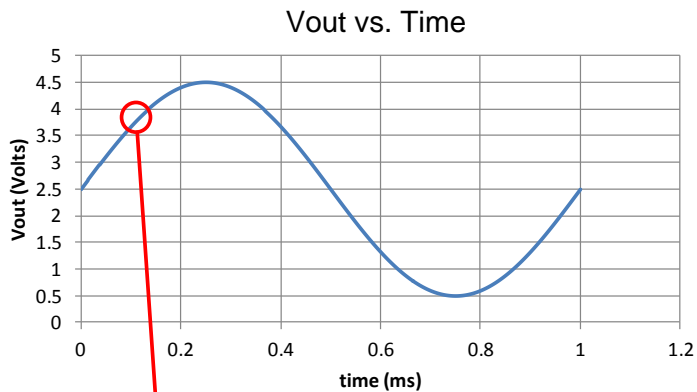
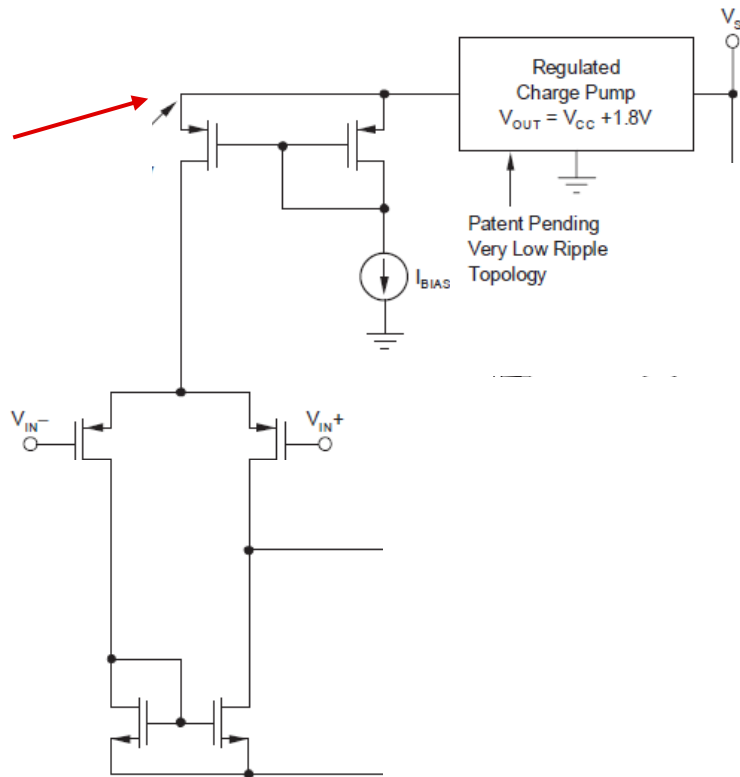
# OPA365 MOSFET Charge Pump – Rail-to-Rail

$$V_{OUT} = +V_S + 1.8V$$

- Uses charge pump to raise V+ rail and overcome V<sub>sat</sub> + V<sub>gs</sub> of input PMOS FETs
- Charge pump switches at 10 MHz which is within op amp 50 MHz GBW
- Pump design is patented and has very low ripple
- Charge pump noise is small relative to broadband noise



# MOSFET Charge Pump – Rail-to-Rail




Eliminates input stage crossover distortion

Model	Tech- nology	Rail- to- rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA365	LV CMOS	RRIO	2.2 – 5.5 V	4.6 mA	100 $\mu$ V	1 $\mu$ V/ $^{\circ}$ C	0.2 pA	12 nV/ $\sqrt{\text{Hz}}$	50 MHz	25 V/ $\mu$ s
OPA322	LV CMOS	RRIO	1.8 – 5.5 V	1.5 mA	500 $\mu$ V	1.5 $\mu$ V/ $^{\circ}$ C	0.2 pA	8.5 nV/ $\sqrt{\text{Hz}}$	20 MHz	10 V/ $\mu$ s


- OPA365 – Wide bandwidth, Low-Distortion, High CMRR
  - High performance optimized for low voltage, single-supply applications
- OPA322 – Wide bandwidth, Low-Noise, Low current
  - Optimized for low noise and wide bandwidth while requiring low quiescent current
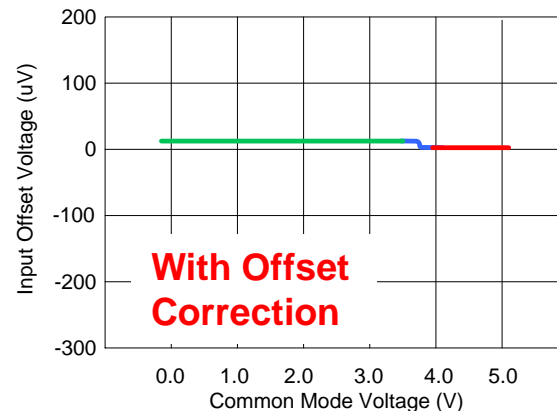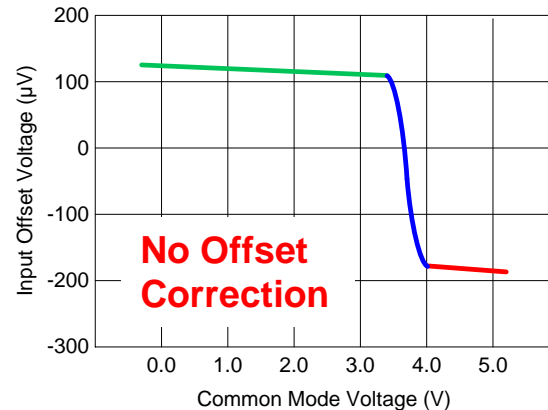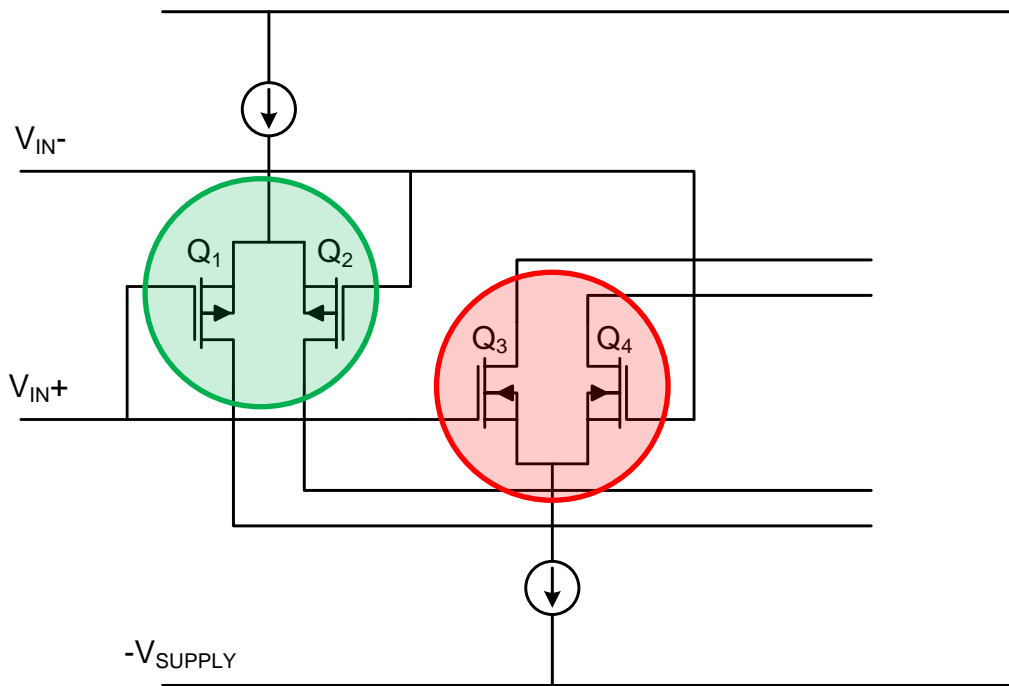
# Chopper and Zero Drift MOSFET – Rail-to-Rail


“Chopper” and “Zero-Drift” CMOS Op Amps use complementary input P-ch/ N-ch concept with Digital Calibration for Offset Correction


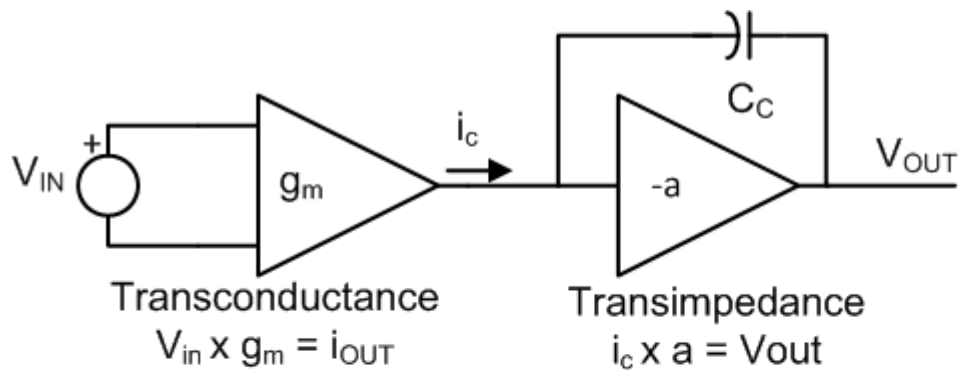
# Comparing Common Architectures vs. Chopper




CMOS Vos/drift	Typ Vos (uV)	Typ Drift (uV/C)
Uncorrected	1000	5
Zero Drift (chopper)	10	0.05
Package Trim	10	0.5

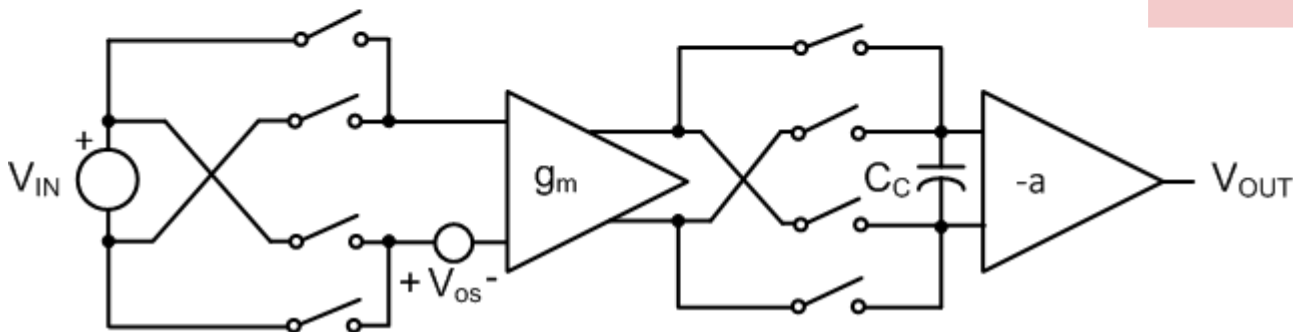






# Chopper Amplifying $V_{IN}$

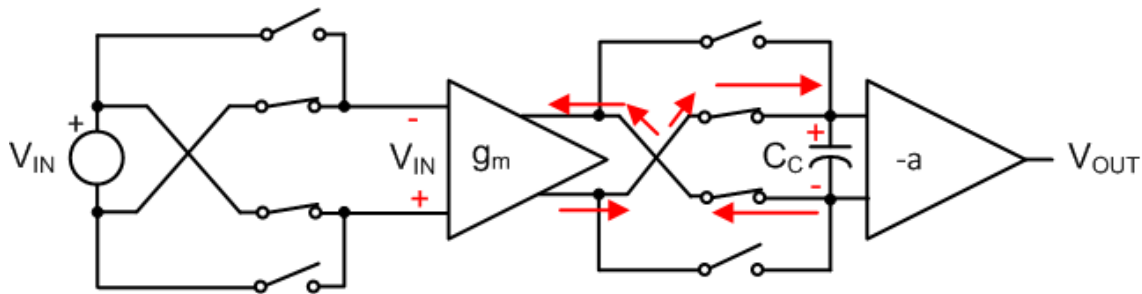

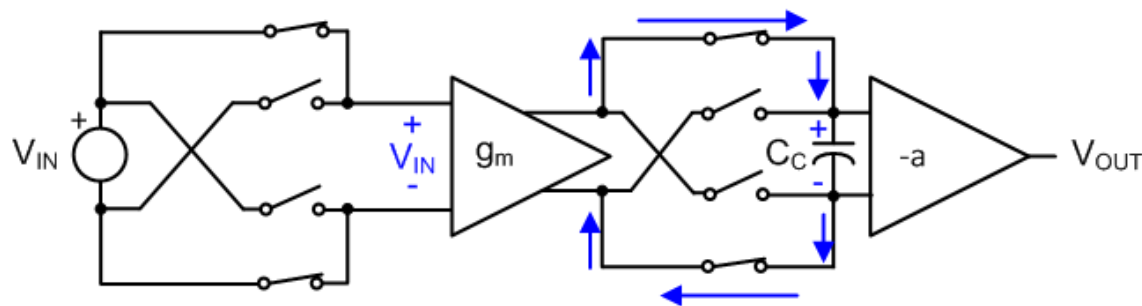- $V_{IN}$  inverted at the input and output every other calibration cycle
- Overall signal path doesn't see an inversion



# Chopper Amplifying Vos

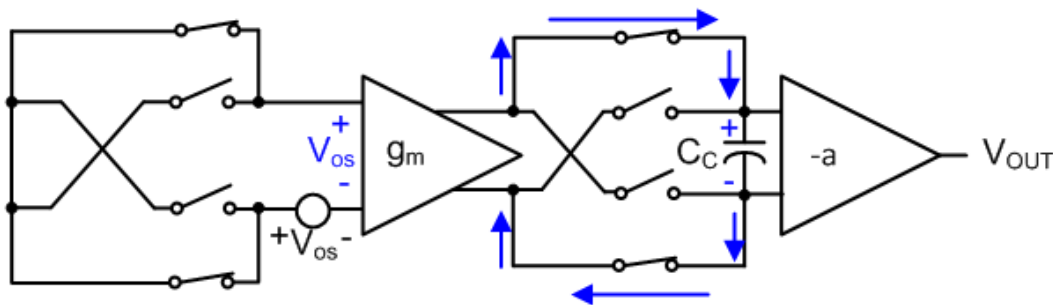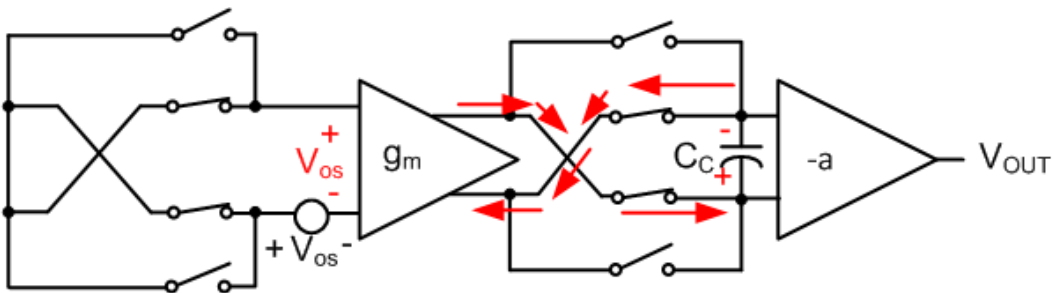


- Vos only inverted at output every other calibration cycle
- Offset translates to triangle wave
- Offset average is zero
- Sync Filter eliminates triangle wave


$f = 125\text{kHz}$  on OPA333

Average = 0

Slope =  $(V_{os} \cdot g_m) / C_c$


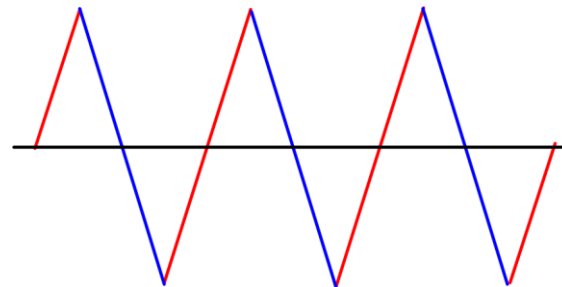


# Chopper: A more complete diagram

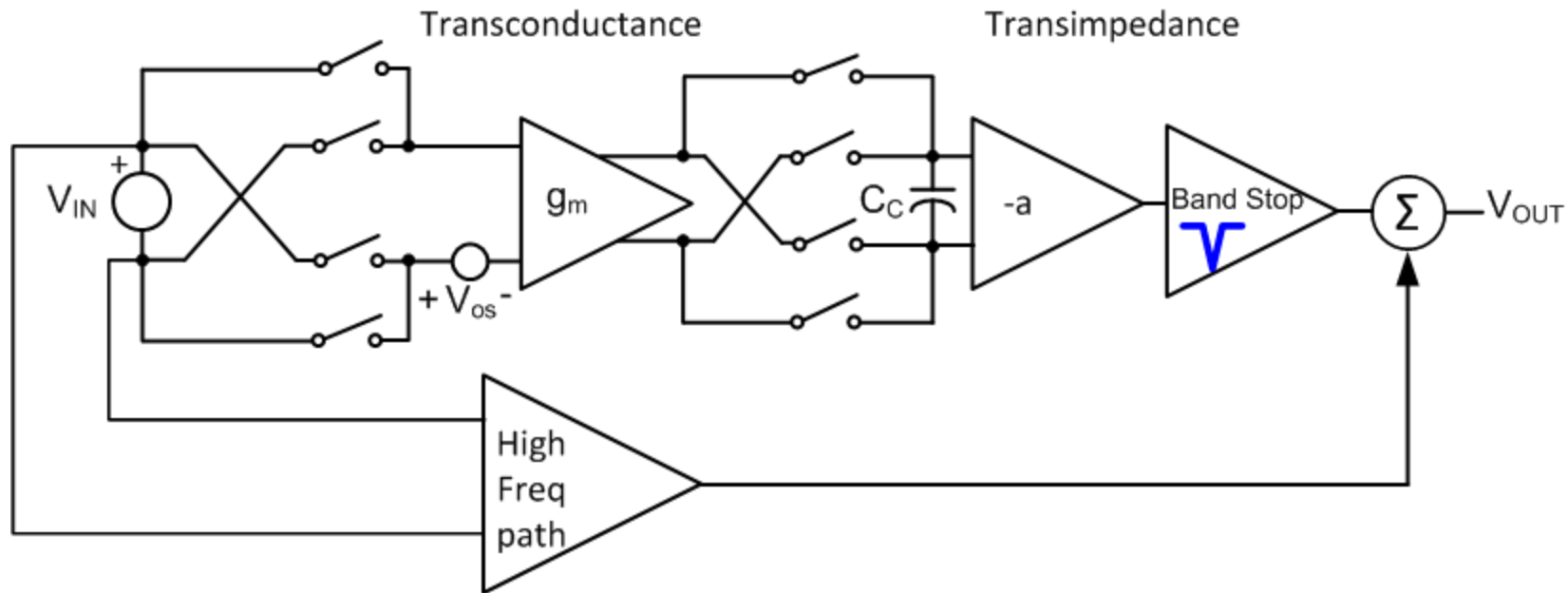


# Chopper Noise Sources and $I_b$
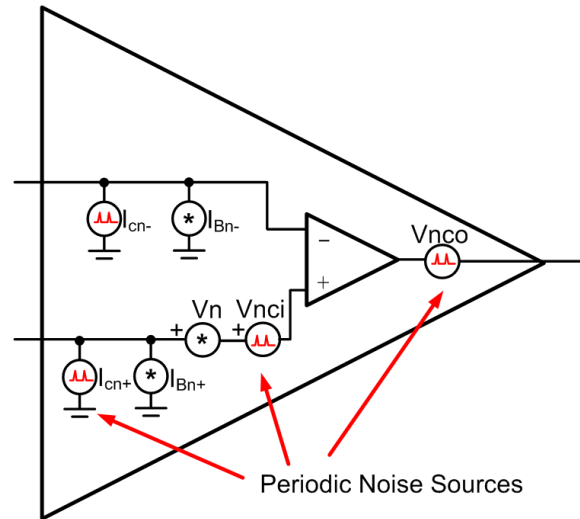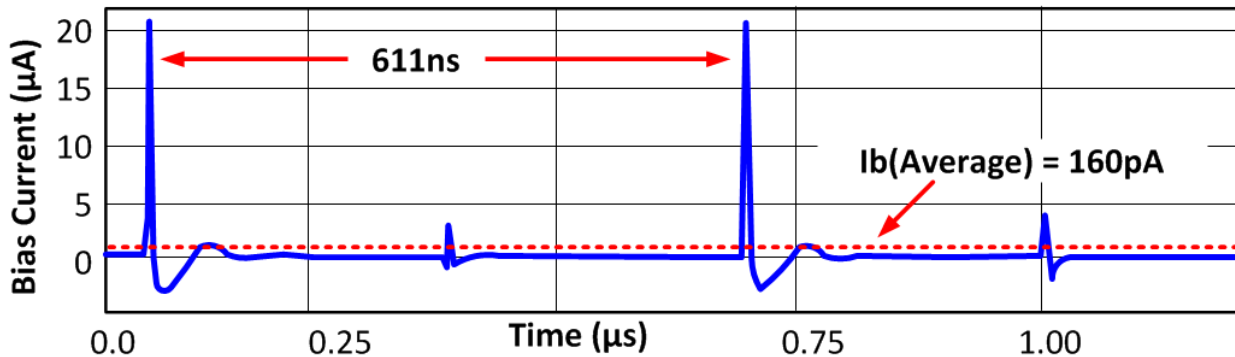
### OPA188 IB – Chopper Calibration Feedthrough



### OPA188 Noise Density vs. Frequency

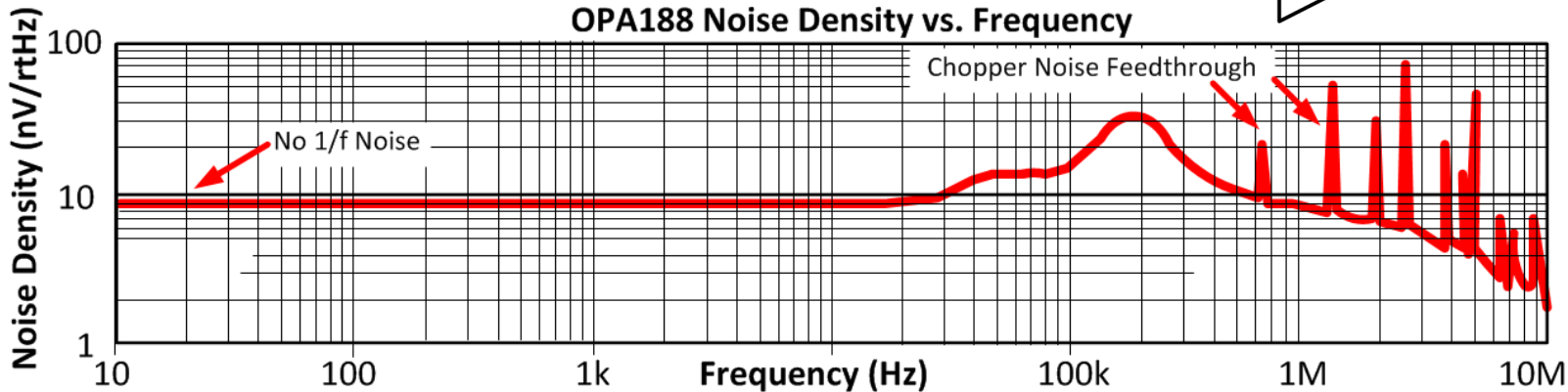

# Chopper Op Amps

Chopper techniques provide low offset voltage and near zero-drift over time and temperature

Model	Technology	Rail-to-rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA333	LV CMOS	RRIO	1.8 – 5.5 V	17 uA	2 uV	0.02 uV/°C	70 pA	55 nV/ $\sqrt{\text{Hz}}$	350 kHz	0.16 V/us
OPA188	HV CMOS	RRO	4- 36 V	425 uA	6 uV	0.03 uV/°C	160 pA	8.8 nV/ $\sqrt{\text{Hz}}$	2 MHz	0.8 V/us

- OPA333 - 1.8 V, Precision, microPower
  - Provides excellent CMRR without the crossover associated with traditional complementary input stages
- OPA2188 – 36 V, Precision, Low-Noise, Rail-to-Rail Output
  - Offers very low offset and drift with high CMRR, PSRR, and AOL performance

# Input Stage Back-to-Back Diodes


**CMOS:** May not be needed, Check Data Sheet.

**JFET:** May not be needed, Check Data Sheet.



**Bipolar:** Generally Required.

These diodes prevent overstress damage on input base to emitter junctions.

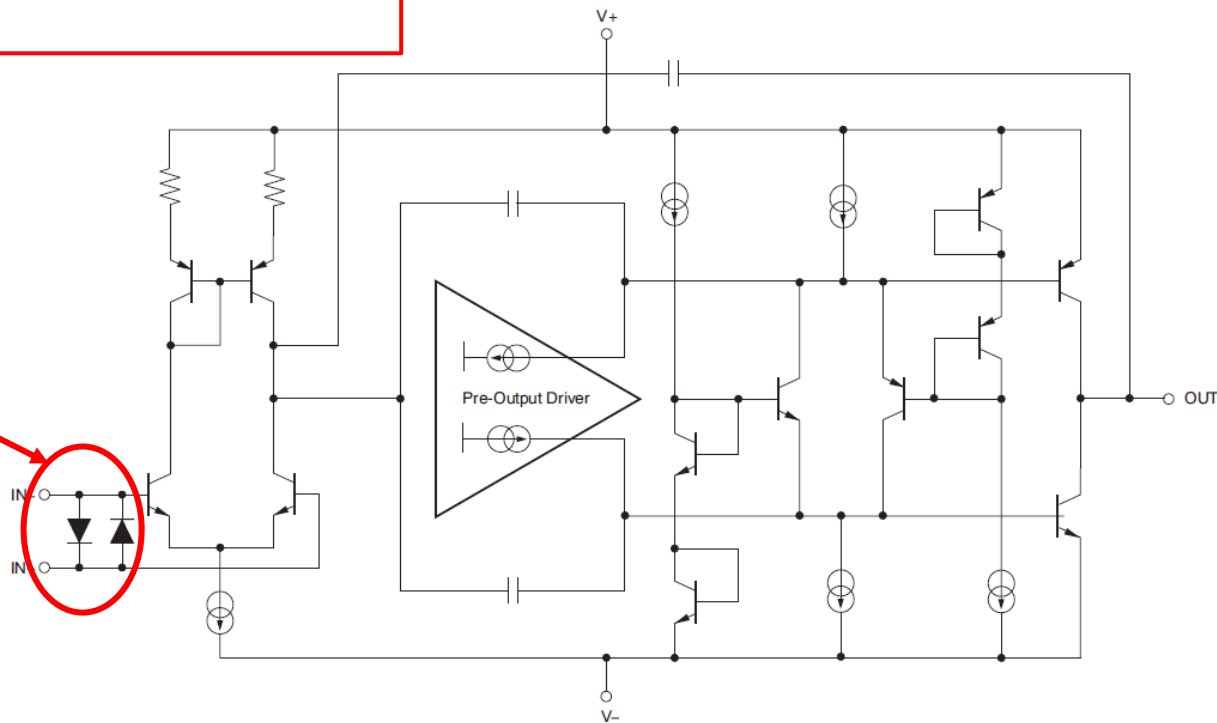- Diodes can cause problems in multiplexed applications
- See TIPD151 for details



# Input Stage Back-to-Back Diodes

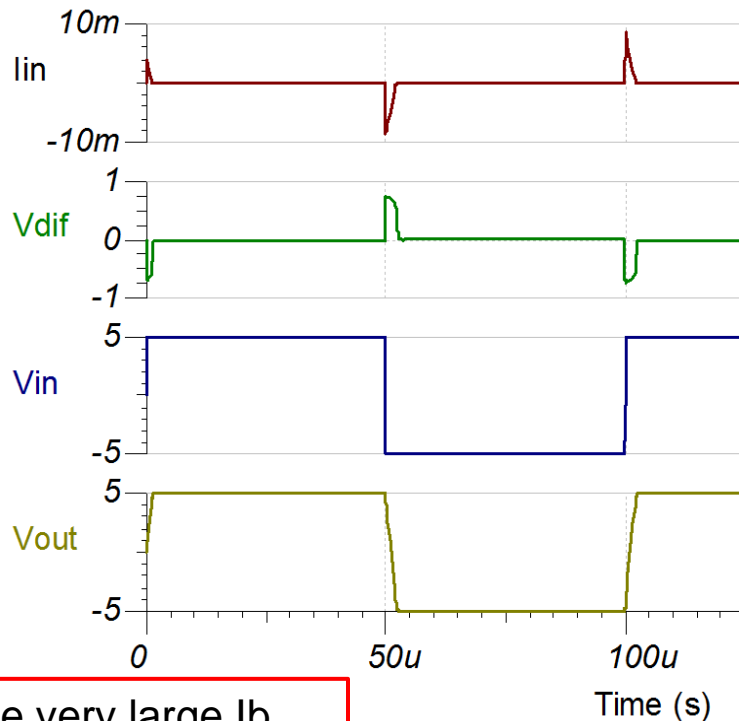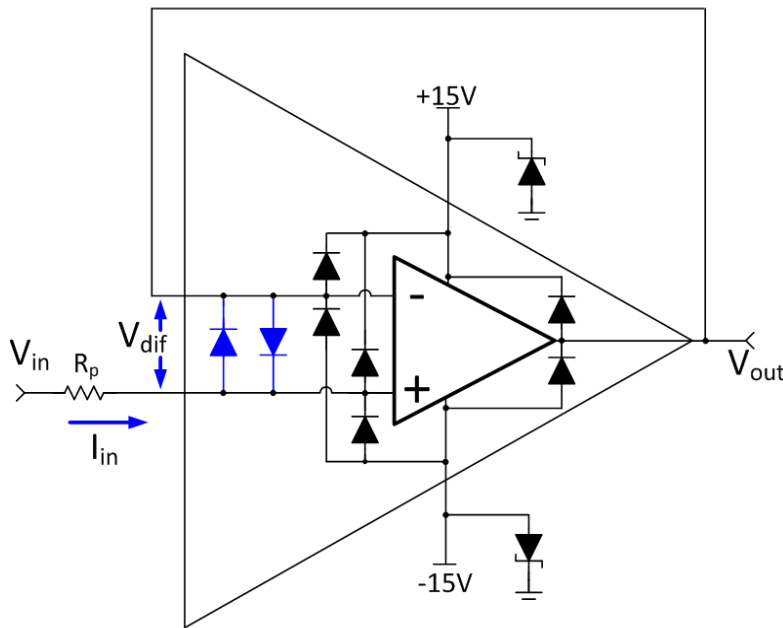

The diodes can turn on during slewing and cause very large  $I_b$ .  
Can be a significant problem in Mux applications (TIPD151).

# Input Stage Back-to-Back Diodes


Op amps with differential input over-voltage protection

Model	Technology	Rail-to-rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA171	HV CMOS	RRO	2.7 - 36 V	475 $\mu$ A	250 $\mu$ V	0.3 $\mu$ V/ $^{\circ}$ C	8 pA	14 nV/ $\sqrt{\text{Hz}}$	3 MHz	1.5 V/ $\mu$ s
OPA1622	Bipolar	No	4 - 36 V	2.6 mA	100 $\mu$ V	0.5 $\mu$ V/ $^{\circ}$ C	1.2 $\mu$ A	2.8 nV/ $\sqrt{\text{Hz}}$	8 MHz	10 V/ $\mu$ s


- OPAx171 - 36-V, Single-Supply, SOT553, General-Purpose Op Amps
  - single-supply, low-noise, low offset and drift, and low quiescent current
- OPA1622 - SoundPlus™ High-Fidelity, Bipolar-Input, Audio Op Amp
  - very low noise density, with an ultralow THD+N of -119.2 dB at 1 kHz
  - drives a 32- $\Omega$  load at 100 mW output power


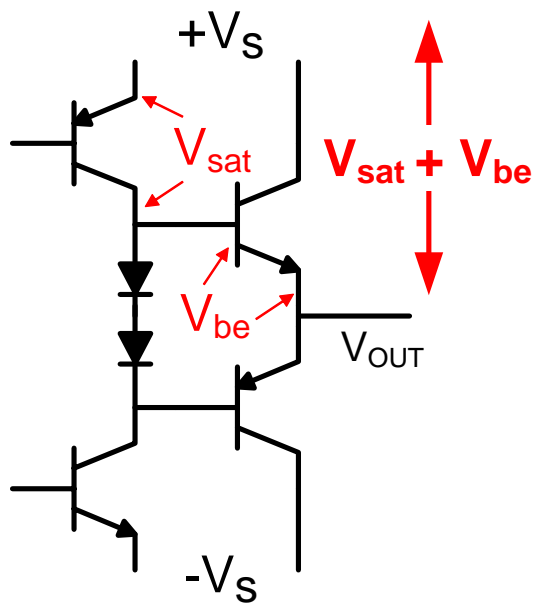
# Classic Bipolar vs. Rail-to-Rail Output Stage



**Classic Bipolar**

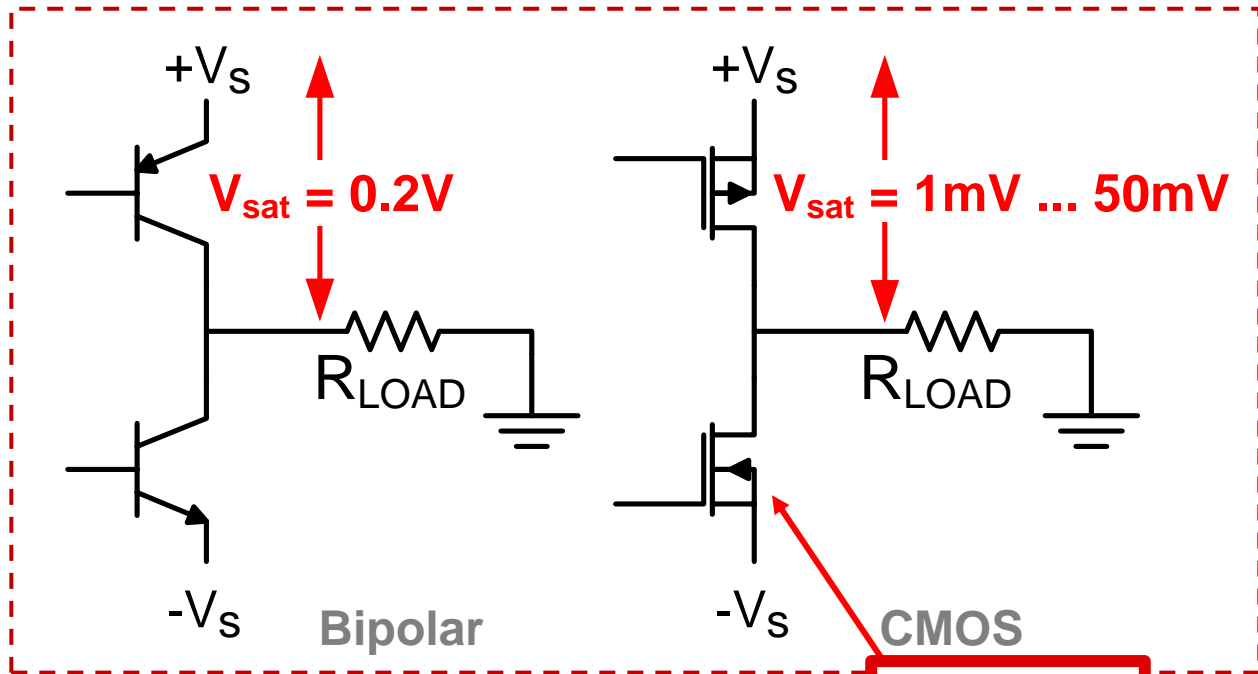

**Rail-to-Rail**


Note: W/L sets  $R_{on}$

# Classic Bipolar vs. Rail-to-Rail Output Stage


Model	Tech- nology	Output design	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Output Swing
OPA827	JFET + Bipolar	PNP/ NPN Emitter Followers	8 – 36 V	4.8 mA	75 uV	0.1 uV/°C	3 pA	(V-) + 3 V, (V+) – 3 V RL = 1 kΩ, Aol > 120 dB
OPA209	Bipolar	PNP/NPN Collectors	10 – 30 V	3.7 mA	10 uV	0.3 uV/°C	2.5 nA	(V-) + 0.6 V, (V+) – 0.6 V RL = 2 kΩ, Aol > 94 dB
OPA340	LV CMOS	P-Drain N-Drain	2.5 – 5.5 V	750 uA	150 uV	4 uV/°C	0.2 pA	(V-) + 1mV, (V+) – 1m V RL = 100 kΩ, Aol > 106 dB

- OPA340
  - Rail-to-rail CMOS op amp optimized for low-voltage, single-supply operation
  - Voltage Output Swing typically 1 mV from rails for  $R_L = 100 \text{ k}\Omega$ ,  $A_{ol} \geq 106 \text{ dB}$
  - Closest swing to rail of any PA op amp
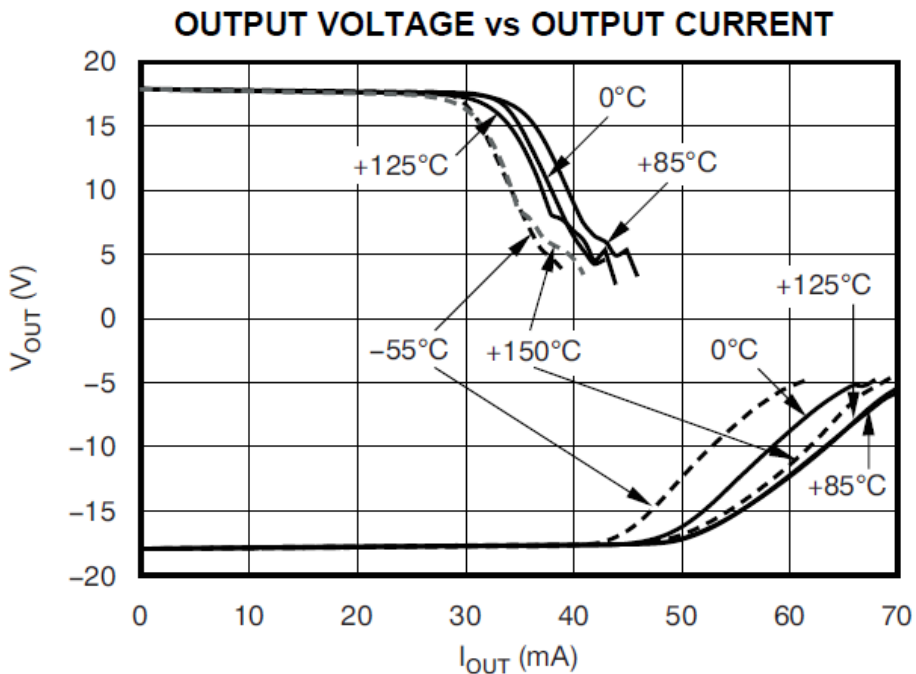
# Bipolar vs. CMOS Output Swing vs. I<sub>out</sub>




**Bipolar**

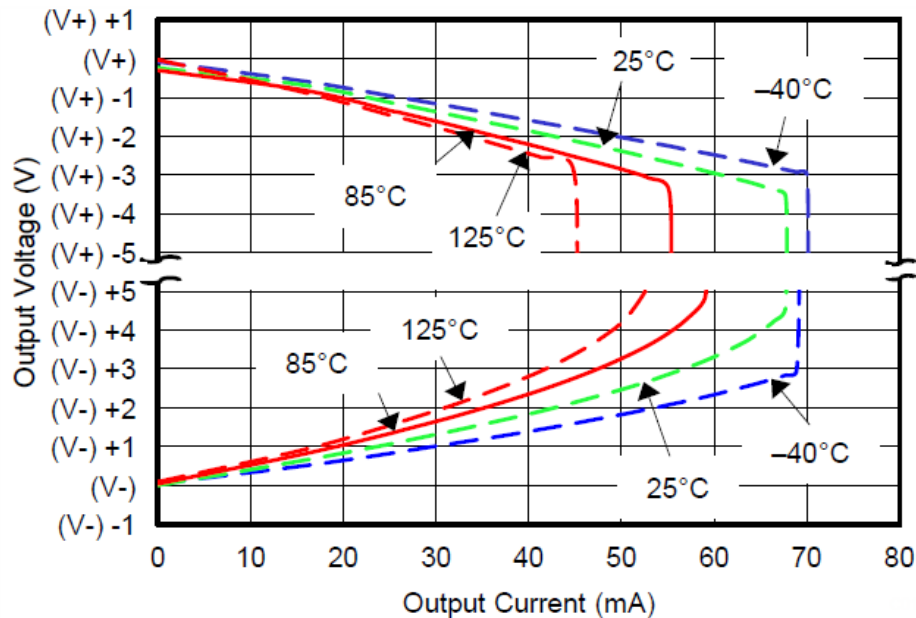


**CMOS**

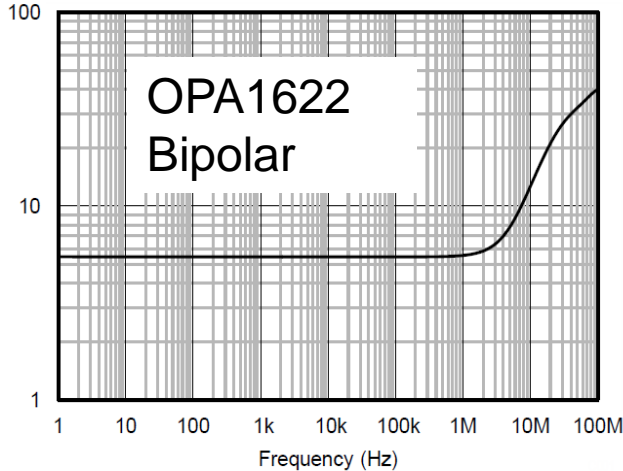
# Open Loop Output Impedance: $Z_o$ – Bipolar vs. CMOS



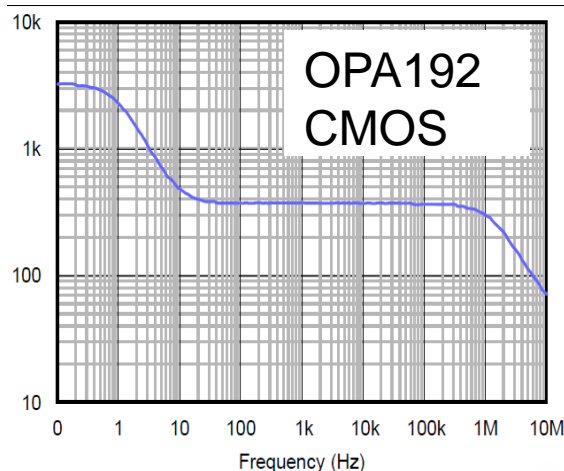Bipolar is generally the flattest and lowest  $Z_o$



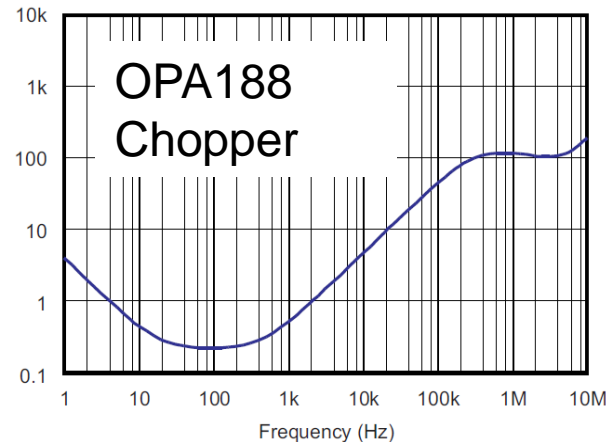CMOS  $Z_o$  is often higher and not as flat as Bipolar.



Zero Drift amplifiers and microPower amplifiers often have a complex  $Z_o$ .

## Note:

$Z_o$  is an important factor when an op amp drives capacitive loads.

Accurate SPICE op amp macromodels can be used to predict behavior and stabilize op amp circuits.

# Bipolar vs. CMOS Bandwidth vs. Iq

BIPOLAR

$$g_m = \frac{q \cdot I_c}{k \cdot T}$$

$$r_{gm} = \frac{1}{g_m}$$

$$BW = \frac{g_m}{2 \cdot \pi C_c} = \frac{1}{2 \cdot \pi C_c \cdot r_{gm}}$$

$$BW = \frac{q \cdot I_c}{2 \cdot \pi C_c \cdot k \cdot T}$$

- CMOS BW increases by increasing W/L or Id
- CMOS BW increases by square root of Id
- Bipolar increases linearly with Ic




MOSFET

$$g_m = \sqrt{2 \cdot I_D \cdot \mu \cdot C_{ox} \cdot \frac{W}{L}}$$

$$r_{gm} = \frac{1}{g_m}$$

$$BW = \frac{g_m}{2 \cdot \pi C_c} = \frac{1}{2 \cdot \pi C_c \cdot r_{gm}}$$

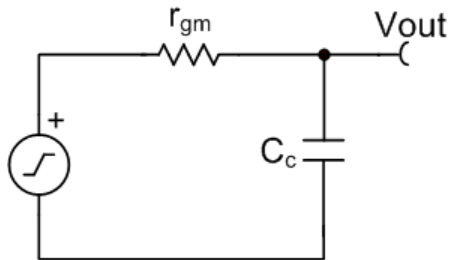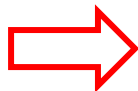
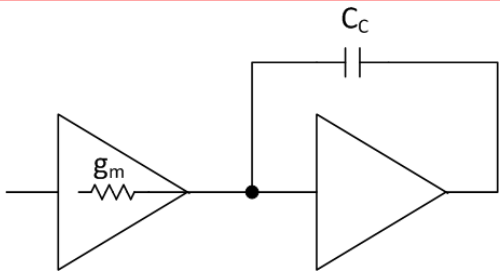
$$BW = \frac{\sqrt{2 \cdot I_D \cdot \mu \cdot C_{ox} \cdot \frac{W}{L}}}{2 \cdot \pi C_c}$$




$$BW = \frac{g_m}{2 \cdot \pi C_c} = \frac{1}{2 \cdot \pi C_c \cdot r_{gm}}$$

# Junction Isolation vs. Dielectrically Isolated

**Junction Isolation**

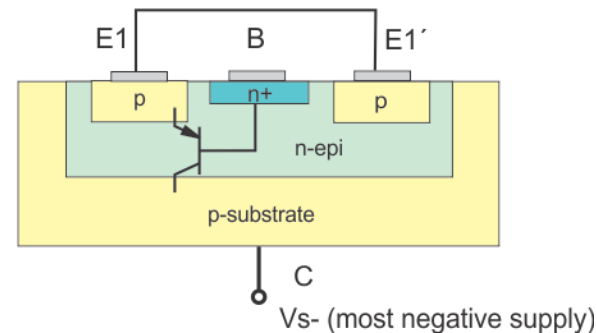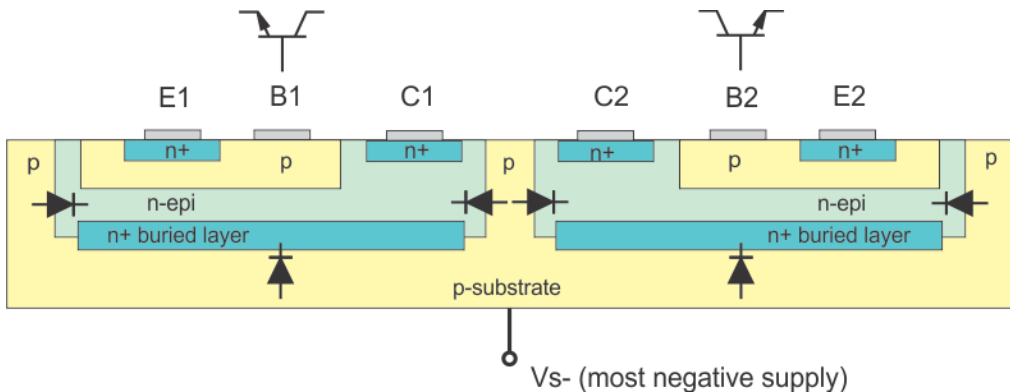

**Dielectrically Isolated**

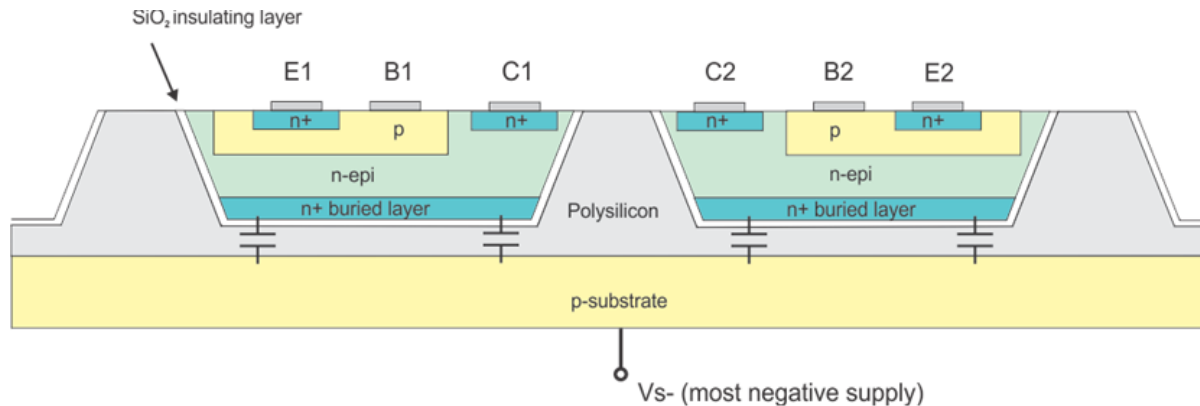

# Junction Isolation vs. Dielectrically Isolated

High performance, JFET input, bipolar op amps

Model	Technology	Rail-to-rail	Supply V+ to V-	Op Current typ	Offset typ	Offset drift typ	Bias Current typ	Voltage noise 1 kHz	GBW	Slew rate
OPA827	Junction isolation	No	8V - 36 V	4.8 mA	75 $\mu$ V	0.1 $\mu$ V/ $^{\circ}$ C	8 pA	4 nV/ $\sqrt{\text{Hz}}$	22 MHz	28 V/ $\mu$ s
OPA627	Dielectric isolation	No	9V - 36 V	7 mA	40 $\mu$ V	0.4 $\mu$ V/ $^{\circ}$ C	1 pA	5.2 nV/ $\sqrt{\text{Hz}}$	16MHz	55 V/ $\mu$ s

- OPA827 - Low-Noise, High-Precision, JFET-Input op amp
  - Precision 16-bit to 18-bit mixed signal systems, transimpedance amplifiers
- OPA627 – “Hallmark” High-Precision JFET-Input op amp
  - lower noise, lower offset voltage, and higher speed than most JFET input op amps
  - Voltage noise performance comparable with the best bipolar-input op amps

# Summary CMOS vs. Bipolar vs. JFET

Parameter	CMOS	Bipolar	JFET
Vos	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Generally Larger than bipolar. Complex trim. Inherent <math>\approx 5\text{mV}</math>, Trimmed <math>\approx 500\mu\text{V}</math></li> <li><input checked="" type="checkbox"/> Can use zero drift, and package trim.</li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Generally smaller than JFET and CMOS. Laser Trim Only. Inherent <math>\approx 200\mu\text{V}</math>, Trimmed <math>\approx 20\mu\text{V}</math></li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Generally Larger than bipolar. Complex trim. Laser Trim Only. Inherent <math>\approx 1\text{mV}</math>, Trimmed <math>\approx 100\mu\text{V}</math></li> </ul>
Vos Drift	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Generally Larger than bipolar. Complex trim.</li> <li><input checked="" type="checkbox"/> Very good if using chopper.</li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Inherently linear and easier to trim. Laser Trim Only.</li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Generally Larger than bipolar. Complex trim. Laser Trim Only.</li> </ul>
Ib	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Low compared with bipolar <math>I_b \approx 1\text{pA}</math> @ 25C</li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Much larger than CMOS and JFET. Can use bias current calculation. Inherent <math>\approx 100\text{nA}</math>, Canceled <math>\approx 1\text{nA}</math></li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Low compared with bipolar <math>I_b \approx 1\text{pA}</math> @ 25C</li> </ul>
Ib Drift	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Doubles every 10C, diode leakage <math>I_{B\_room} \approx 1\text{pA}</math>, <math>T = 25\text{C}</math> <math>I_{B\_hot} \approx 1000\text{pA}</math>, <math>T = 125\text{C}</math></li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Small compared to room temp <math>I_{B\_room} \approx 1\text{nA}</math>, <math>T = 25\text{C}</math> <math>I_{B\_hot} \approx 3\text{nA}</math>, <math>T = 125\text{C}</math></li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Doubles every 10C, diode leakage <math>I_{B\_room} \approx 1\text{pA}</math>, <math>T = 25\text{C}</math> <math>I_{B\_hot} \approx 1000\text{pA}</math>, <math>T = 125\text{C}</math></li> </ul>
Ibos	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Large offset current that is comparable to <math>I_b</math>. Don't use resistor to cancel effects. <math>I_b \approx \pm 1\text{pA}</math>, <math>I_{bos} = \pm 1\text{pA}</math></li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> When bias current cancellation is not used <math>I_{bos}</math> is low relative to <math>I_b</math>. Resistor can help cancel effects. <math>I_b = 100\text{nA}</math>, <math>I_{bos} = \pm 1\text{nA}</math></li> <li><input checked="" type="checkbox"/> When bias current cancellation is used <math>I_{bos}</math> is comparable to <math>I_b</math>. Don't use resistor to cancel effects. <math>I_b = \pm 1\text{nA}</math>, <math>I_{bos} = \pm 1\text{nA}</math></li> </ul>	<ul style="list-style-type: none"> <li><input checked="" type="checkbox"/> Large offset current that is comparable to <math>I_b</math>. Don't use resistor to cancel effects. <math>I_b \approx \pm 1\text{pA}</math>, <math>I_{bos} = \pm 1\text{pA}</math></li> </ul>



# Summary CMOS vs. Bipolar vs. JFET

Parameter	CMOS	Bipolar	JFET
Broadband Noise	<input checked="" type="checkbox"/> Generally Larger than bipolar. Noise decreases to the square root of $I_d$ .	<input checked="" type="checkbox"/> Generally smaller than JFET and CMOS. Noise decreases directly with $I_d$ .	<input checked="" type="checkbox"/> Slightly higher than Bipolar
1/f Noise	<input checked="" type="checkbox"/> Generally worse than bipolar. Noise Corner > 1kHz	<input checked="" type="checkbox"/> Generally better than CMOS. Noise Corner < 10Hz	<input checked="" type="checkbox"/> Generally better than CMOS, but not as good as bipolar. Noise Corner < 100Hz
Back-to-Back Diodes	<input checked="" type="checkbox"/> May or may not be required. Check Data Sheet!	<input checked="" type="checkbox"/> Generally required	<input checked="" type="checkbox"/> Not required. Check Data Sheet
Integrated Digital?	<input checked="" type="checkbox"/> Yes. i.e. Chopper, package trim	<input checked="" type="checkbox"/> No	<input checked="" type="checkbox"/> No
Rail to Rail Input	<input checked="" type="checkbox"/> Yes	<input checked="" type="checkbox"/> No.	<input checked="" type="checkbox"/> Not common. Difficult
Rail to Rail Output	Very close to the rail. 10mV	Close to the rail. 200mV	Same as bipolar
Output vs. Load	<input checked="" type="checkbox"/> Falls off quickly with load. Ron of output transistor.	<input checked="" type="checkbox"/> Relatively flat until you reach current limit. $V_{sat}$ not related to Ron as with CMOS.	Same as bipolar

# Thank you