

High **VOLT** Interactive

Where power supply design meets collaboration

Hysteresis loss in high voltage MOSFETs:
Findings and effects for high frequency AC-DC converters

Bernard Keogh

What will I get out of this session?

Purpose:

- Highlight Coss hysteresis loss
 - Occurs for all SJ MOSFETs, from ALL manufacturers, but to greater/lesser extent
- Illustrate how it can be measured
- Show how it impacts MOSFET choice for ZVS topologies

- Part numbers mentioned:
 - UCC24612 SR driver
 - UCC27712 600-V half-bridge driver
- Reference designs mentioned:
 - TI high-efficiency active-clamp Flyback EVM (under development)
- Relevant End Equipments:
 - High-density adapters
 - High-efficiency PSUs

Introduction

- Industry trend → high efficiency & small size adapters & PSUs
 - Standard 65-W adapter → 8 W/in³
 - Zolt 70-W → 14 W/in³
 - Finsix Dart → 17 W/in³
- Higher power density
 - Higher frequency → smaller magnetics
 - Small size → less surface area to dissipate heat → need higher efficiency with less dissipation
- Need soft-switching or zero-voltage-switching (ZVS) topologies to enable high Fsw
- ZVS – eliminate switching loss
 - Allows higher Fsw → smaller magnetics (still limited by HF core loss, AC resistance)
 - Allows larger switching devices with lower conduction loss – no capacitive losses, right?



$f_{sw}=65\text{kHz}$




RM8 ~7300 mm³

$f_{sw}=200\text{k}\sim 400\text{kHz}$




EE16 ~3500 mm³

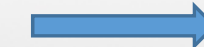


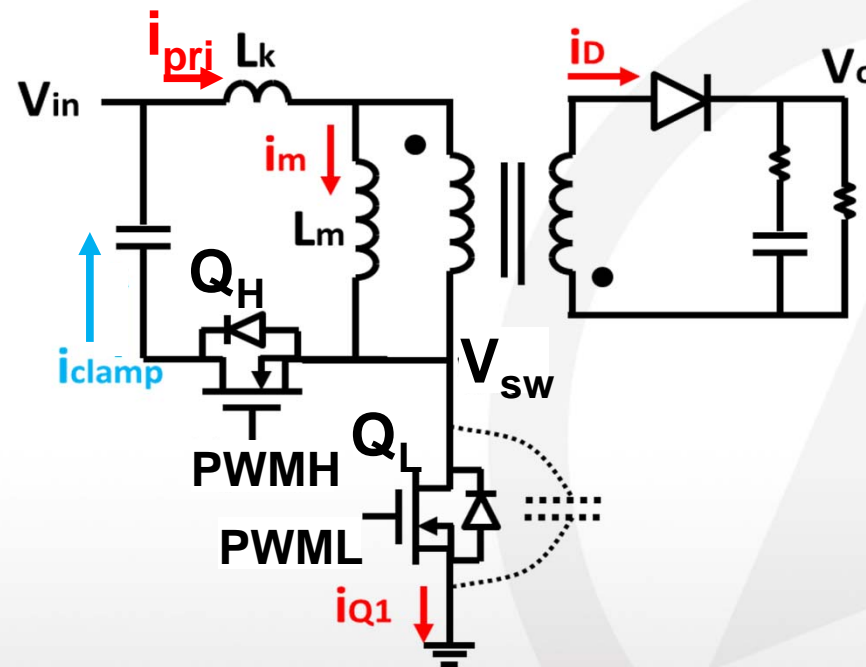Example ZVS topology – Active-Clamp Flyback

- QR Flyback only achieves partial ZVS
- Add active-clamp switch to achieve full ZVS
- Also recycle transformer leakage inductance energy



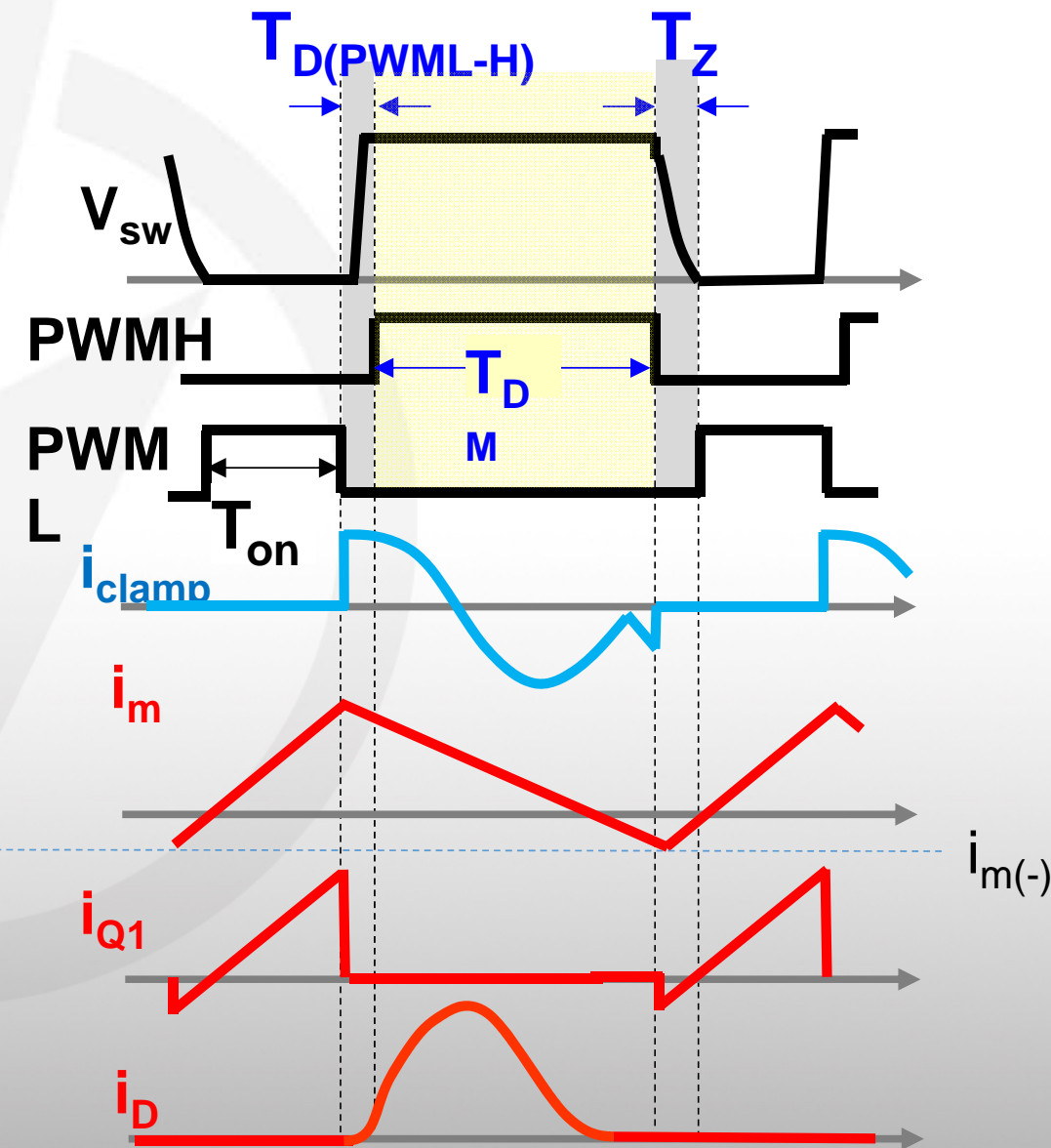ZVS criteria: $\frac{1}{2} L_m i_{m(-)}^2 \geq \frac{1}{2} C_{sw} V_{sw}^2$



Zero-voltage-switching (ZVS) trade-offs

- ZVS – eliminate switching loss
 - Allows higher F_{sw} → smaller magnetics
 - Push F_{sw} higher – how high can or should you go?
 - Magnetics still limited by HF core loss, AC resistance loss
 - Allows larger switching devices with lower conduction loss
 - No capacitive losses, right?
 - Can push the capacitance way up, right?
- Not quite!

Superjunction high-voltage MOSFET

- Brief history:
 - Superjunction concept patents date from 1978-1990s
 - First commercialized 1998/9 by Infineon (CoolMOS) , 2000 by ST (MDMesh)
 - Breaks the theoretical Si limit of $R_{ds(on)}$ at high voltage
 - Uses vertical pillars of P/N to for more uniform field distribution
 - Allows much higher N-doping level (10x to 100x) vs std. MOSFET
 - Gives higher breakdown (uniform field) at very low $R_{ds(on)}$ (N-doping)
- Many Superjunction vendors:
 - Infineon/IR, ST, Toshiba, AOS, Fairchild/On, Vishay, Fuji, Rohm, NXP, EPC, Fujitsu, & others
- Non-linear C_{oss} vs VDS
 - More pronounced with newer gen lower $R_{ds(on)}$, smaller feature size

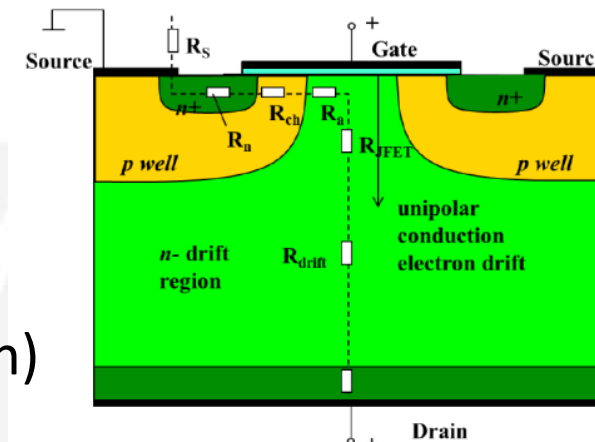


Fig. 1. Planar power MOSFET structure and the schematic representation of the resistance components of different regions in the on-state.

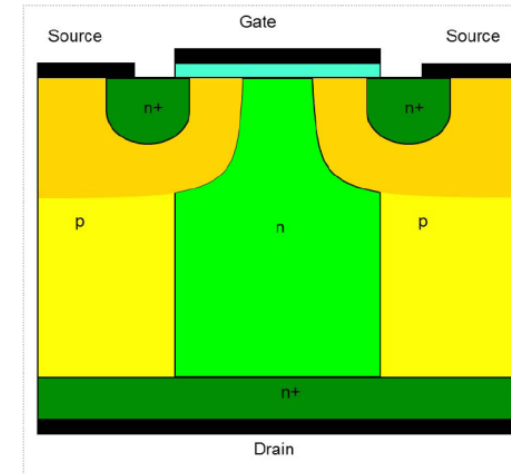


Fig. 8. CoolMOS structure using a planar gate [8].

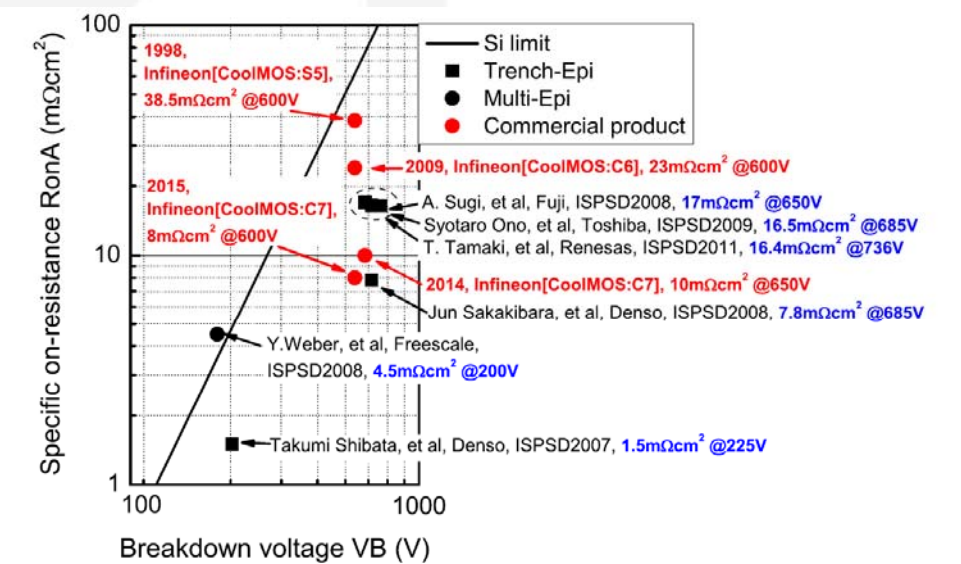


Fig. 11. Specific on-state resistance for different superjunction devices using trench epi and multi-epi processes against the limit of silicon. The graph includes the first generation CoolMOS S5 and last generation C7.

All images reproduced with permission from "Superjunction Power Devices, History, Development and Future Prospects", Florin Udrea, Gerald Deboy, Tatsuhiko Fujihira, IEEE Transaction on Electron Devices, Vol. 64, No. 3, March 2017, © IEEE

Eoss loss – background

- What is Eoss?
 - Energy-related loss due to charge stored in Coss
 - Depends on the bus voltage & device
- Eoss completely dissipated in hard-switching topologies
- Eoss partly recovered in quasi-resonant topologies
- ZVS topologies ideally avoid all Eoss loss
 - Can switch at very high frequency
 - Lower Eoss \Rightarrow less circulating energy to achieve ZVS
- Big variation in Eoss loss for different devices
 - New generations continually achieve lower Eoss
 - Curves show latest gen C7/P7/G7 close to WBG
- However MOSFET Coss charge and discharge has hysteresis

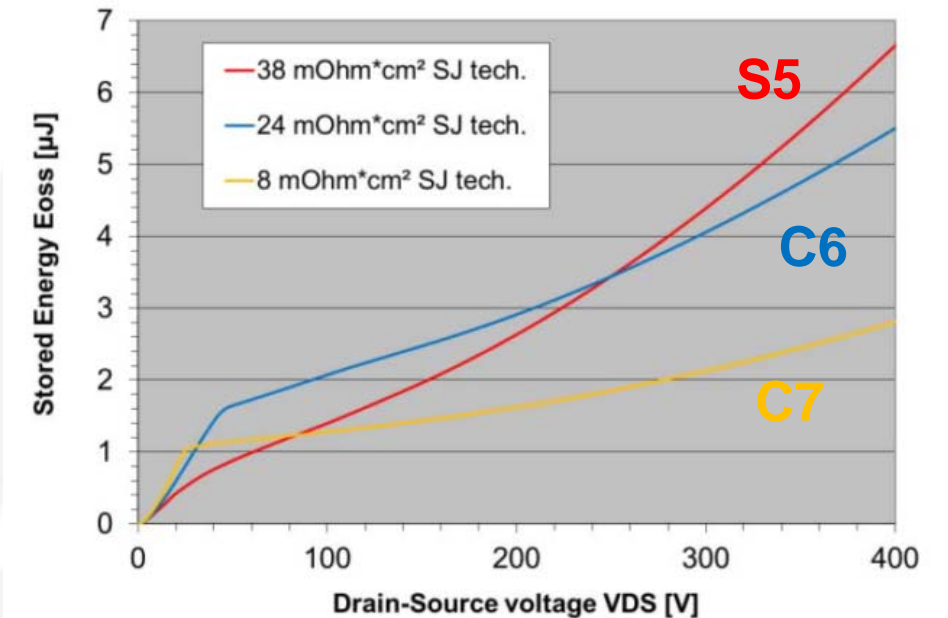


Fig. 13. Energy stored in the output capacitance of three subsequent generations of superjunction devices.

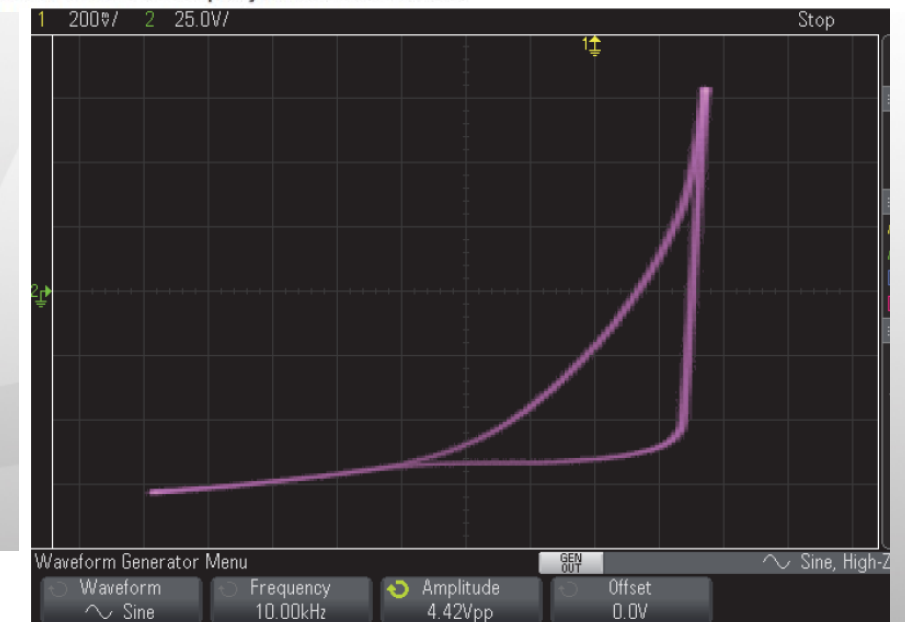


Fig. 1. Oscilloscope capture for Device A being n

Fig. 13 reproduced with permission from "Superjunction Power Devices, History, Development and Future Prospects", Florin Udrea, Gerald Deboy, Tatsuhiko Fujihira, IEEE Transaction on Electron Devices, Vol. 64, No. 3, March 2017, © IEEE; Fig. 1 reproduced with permission from "Coss Hysteresis in Advanced Superjunction MOSFETs", J. B. Fedison, M. J. Harrison, Enphase Energy Inc., APEC 2016, © IEEE

Coss hysteresis loss – the discovery

- Phenomenon first reported APEC 2014 by Enphase*
- Measured Coss to help choose best devices for HF ZVS
- Observed asymmetric charge/discharge waveforms
- Significant temperature rise for expected lossless charge & discharge of Coss
- Waveforms & losses did not match models & simulation
- Big variation in Coss loss for different devices A-E
- Proposed new ZVS Figure of Merit

Table 2. Characteristics of the superjunction MOSFETs measured.

Device	V _{DSS} at 25°C (V)	R _{DSON} max at 25°C (Ω)	C _{iss} at V _{DS} =0 (nF)	E _{stored} *† (μJ)	E _{dissipated} *‡ (μJ)	Area Specific On-Resistance typ at 25°C (mΩ cm ²)
Device A	650	0.148	2.0	1.47	4.050	19
Device B	600	0.160	2.1	2.75	0.5664	27
Device C	600	0.178	2.0	2.46	0.242	26
Device D	600	0.158	3.3	4.06	0.140	30
Device E	600	0.160	1.9	2.67	0.079	33

*V_{GS}=0, V_{DS}=200V. †Calculated from small-signal C_{oss} versus V_{DS}. ‡Measured energy dissipation of C_{oss} per ZVS cycle.

All images reproduced with permission from "Coss Related Energy Loss in Power MOSFETs Used in Zero-Voltage-Switched Applications", J. B. Fedison, M. Fornage, M. J. Harrison, D. R. Zimmanck, Enphase Energy Inc., APEC 2014, © IEEE

* Authors now with ST

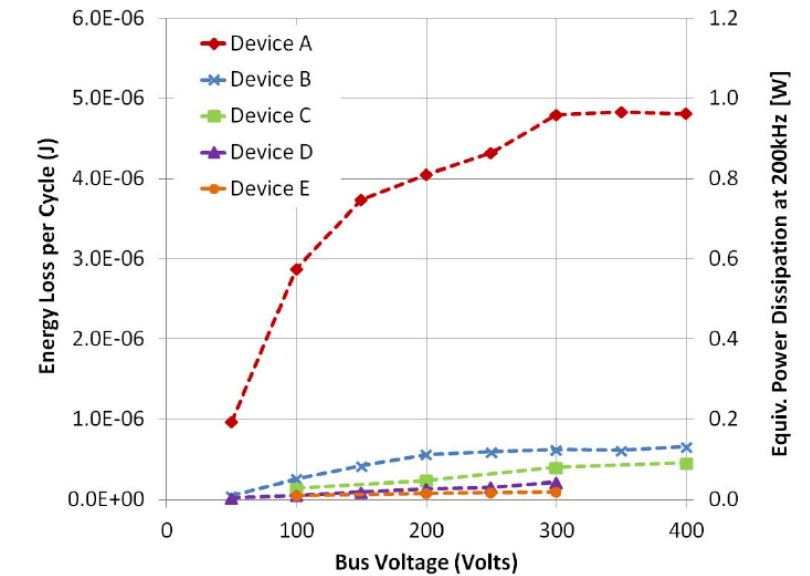


Figure 4. Measured C_{oss} related energy loss (per device) versus bus voltage of state-of-the-art MOSFETs from multiple vendors.

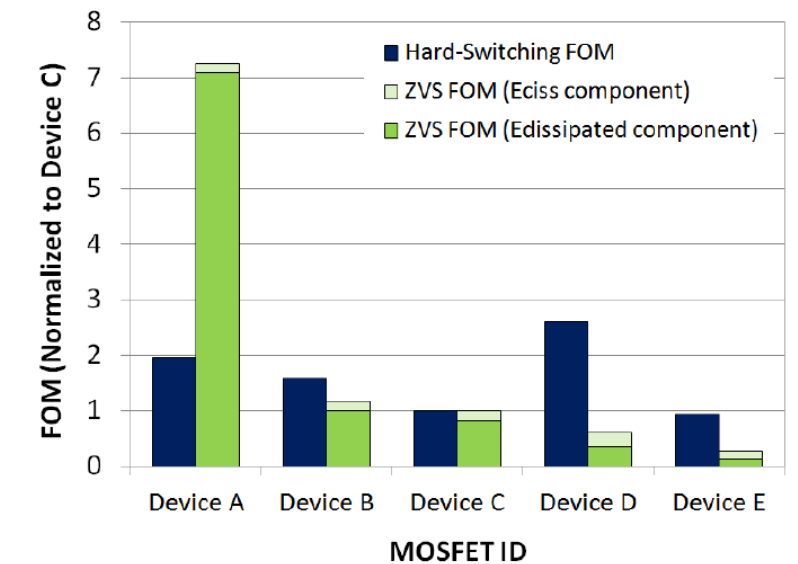


Figure 9. Comparison of normalized hard-switched and ZVS figures of merit with V_{GS}=10V and V_{DS}=300V for the MOSFETs tested where ZVS FOM [E_{Ciss} component] = R_{DSON} × E_{Ciss} and ZVS FOM [E_{dissipated} component] = R_{DSON} × E_{dissipated}. The FOMs have been normalized to device C which has FOM_{ZVS} = 100 nJ Ω and FOM_{HS} = 1.51 nC Ω.

Coss hysteresis loss – other published results

- What causes hysteresis in Coss charge/discharge? Why are some devices better?
- Jaume Roig & Filip Bauwens proposed cause due to “stranded charges”, much worse in MEMI (multi-implant multiepitaxy) technology vs. TFEG (trench-filling epitaxial growth)
 - “Origin of Anomalous Coss Hysteresis in Resonant Converters With Superjunction FETs”, Jaume Roig, Filip Bauwens, OnSemiconductor Power Technology Centre, IEEE Transactions on Electron Devices, Vol. 62, No. 9, September 2015
- Possibly explains why different devices show grossly varying hysteresis loss?
- How can hysteresis loss be measured? Fedison et al (Enphase) used Sawyer-Tower method (detailed in the paper) for same FETS A-E:
 - “Coss Hysteresis in Advanced Superjunction MOSFETs”, J. B. Fedison, M. J. Harrison, Enphase Energy Inc., APEC 2016


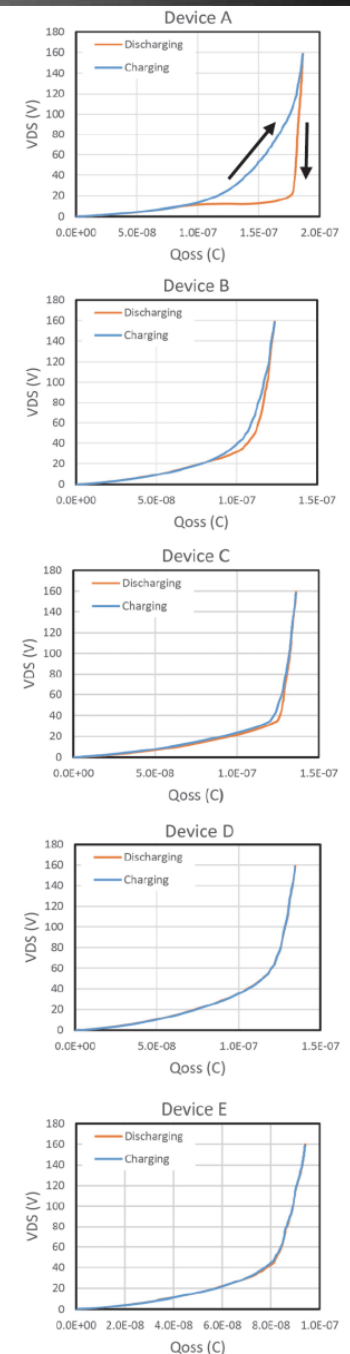


Image reproduced with permission from “Coss Hysteresis in Advanced Superjunction MOSFETs”, J. B. Fedison, M. J. Harrison, Enphase Energy Inc., APEC 2016, © IEEE

Fig 3. V_{DS} versus Q_{oss} curves measured with the Sawyer-Tower circuit for devices A – E. Sweep frequency = 10kHz and peak-to-peak voltage = 160V.

TI investigation of Coss loss – test circuit




- Connect 2 identical DUTs back-to-back in series
 - Back-to-back body diodes \Rightarrow no diode conduction
 - G-S short \Rightarrow FET off \Rightarrow no channel conduction
- Connect to driving high-freq high-voltage square-wave
 - Driving square-wave generated by half-bridge circuit
- Observe Vds of low-side DUT & inductor current
- Measure low-side DUT temperature rise to assess level of Coss hysteresis loss.
- Measure low-side DUT temperature rise ΔT
- Calibrate result
 - Same environmental setup (same thermal conditions)
 - Current I through body diode V_f to get same ΔT
 - $P_{diss} = I * V_f$
 - $E_{oss(hyst)} = P_{diss} / F_{sw}$

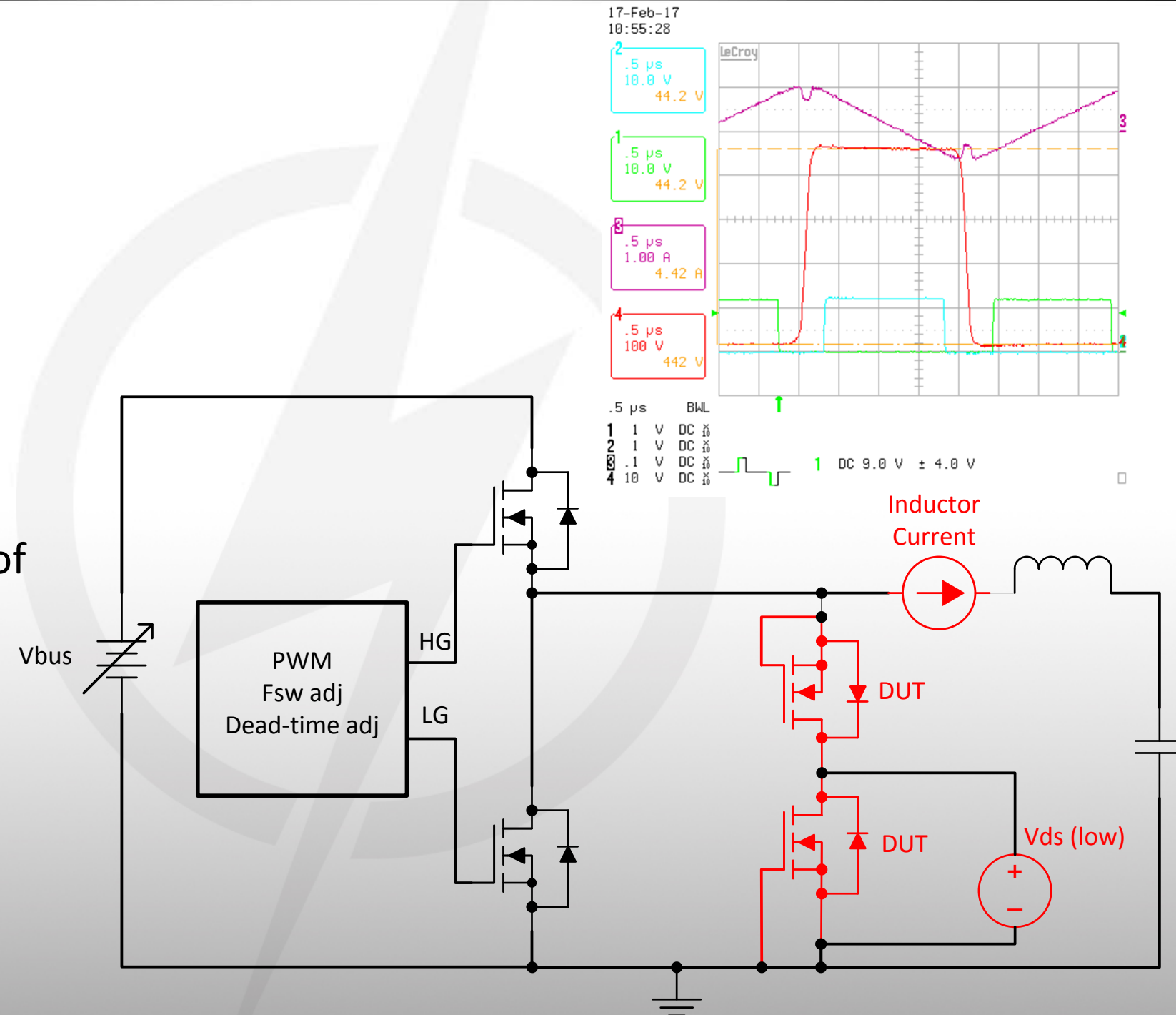

TI investigation of Coss loss – test setup

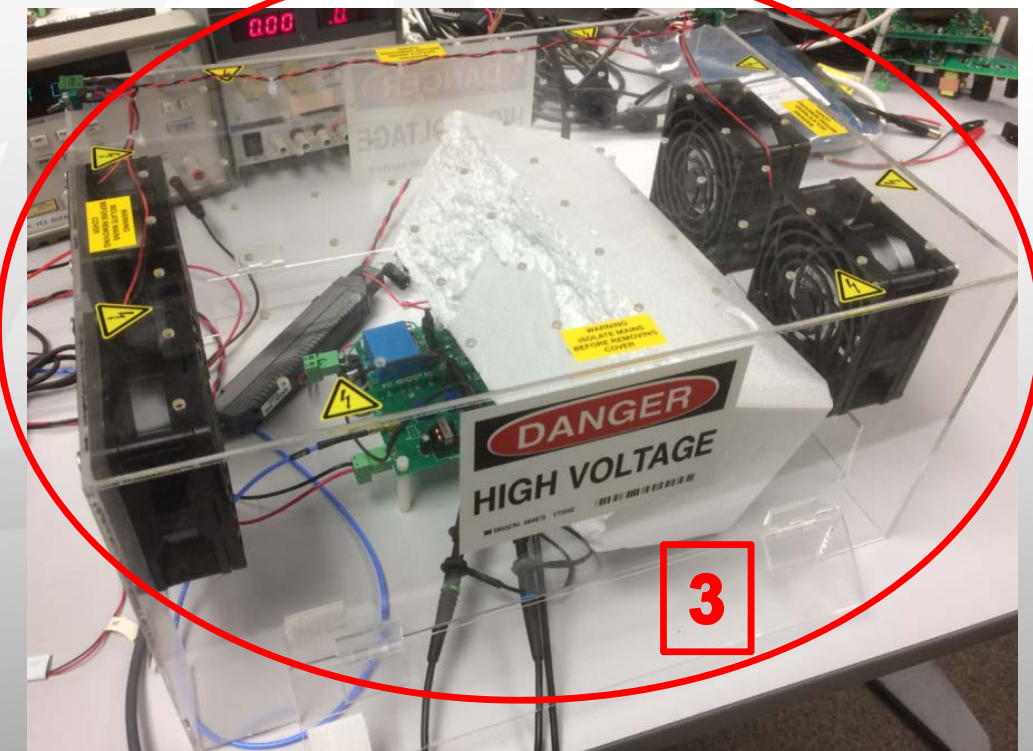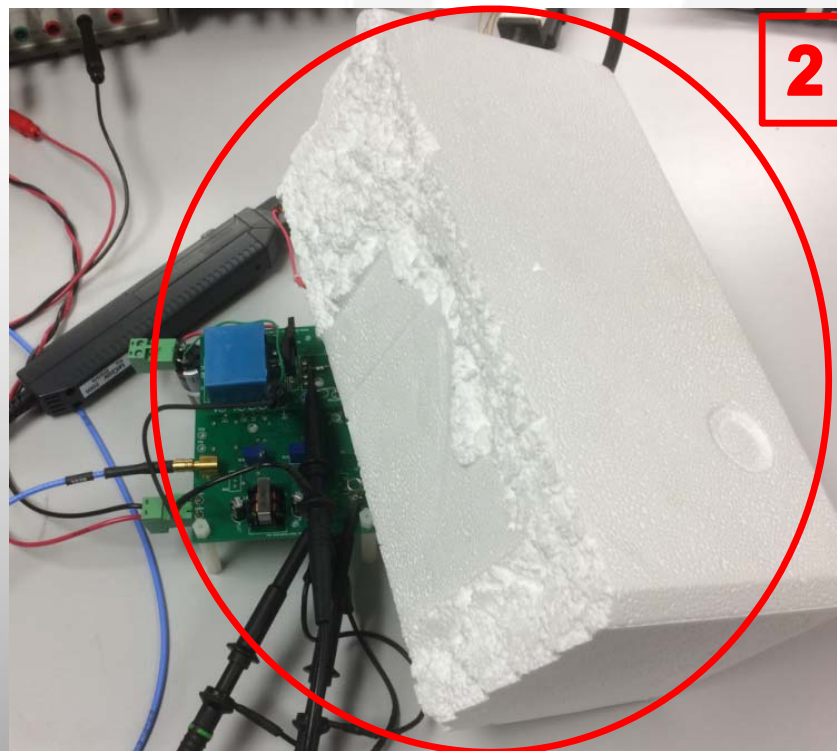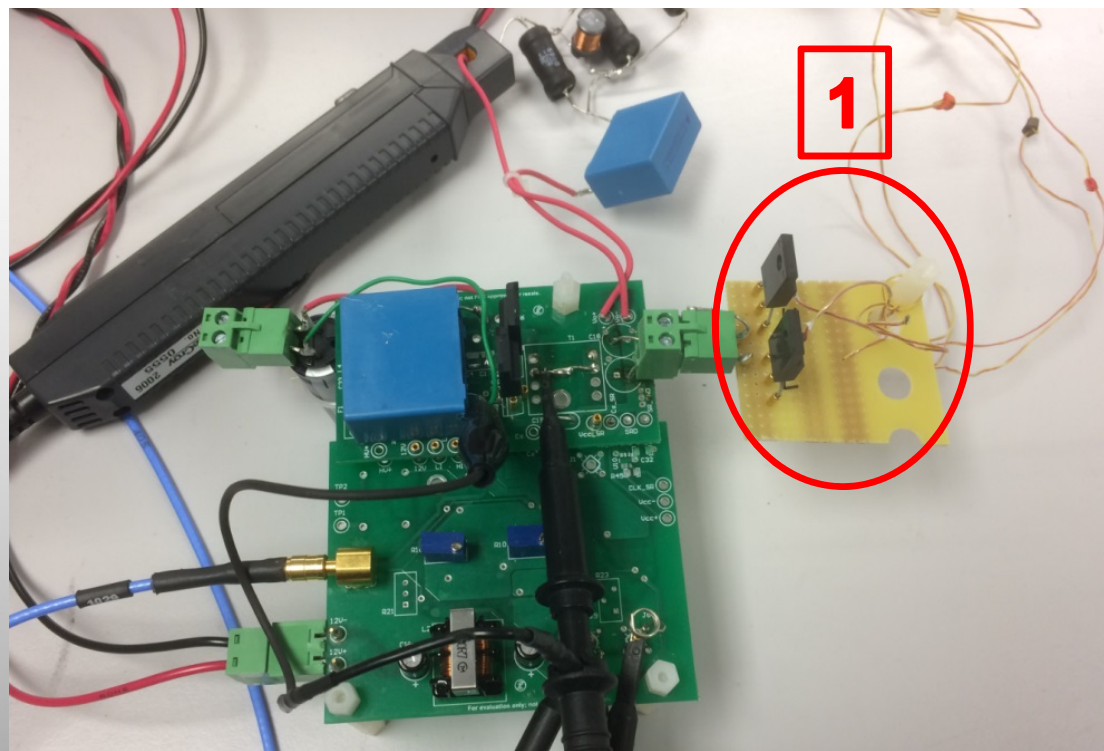1. DUTs socketed with thermocouples glued to plastic body (not metal tab)
2. Styrofoam box to isolate DUTs from external HB FETs & inductor
3. Plastic safety enclosure over entire setup to block ambient air-conditioning airflow

Four K-type thermocouples measured – #1 Low DUT, #2 High DUT, #3 Ambient inside styrofoam, #4 DUT PCB



Devices tested – Infineon CoolMOS 600-V, 650-V & 700-V rated

- Note that Coss hysteresis loss is observed for ALL SJ MOSFETs – regardless of manufacturer
 - Actual loss varies, depending on internal design specifics
- Results summarised here – all Infineon
 - ***Not intended to single out Infineon, just take one manufacturer's broad portfolio as an example***
 - ***To show comparative performance across families for a single manufacturer***
 - CoolMOS 700-V:
 - P7 – IPA70R360P7, IPA70R600P7, IPS70R900P7, IPS70R1K4P7
 - CoolMOS 650-V:
 - C7 – IPP65R225C7, IPA65R190C7, IPP65R125C7, IPP65R045C7
 - G7 – IPT65R195G7
 - CoolMOS 600-V:
 - C3 – SPP20N60C3
 - C6 – IPP60R190C6, IPP60R380C6, IPP60R600C6, IPP60R950C6
 - C7 – IPP60R180C7
 - G7 – IPT60R150G7

Key test results – C6 series

DUT	Vds	Series	Rdson	Eoss @ 450 V (uJ)	Eoss hyst (uJ)	Eoss Hyst %
SPP20N60C3XKSA1	600	C3	190	8.7	0.833	9.6%
IPP60R190C6	600	C6	190	5.9	0.636	10.8%
IPP60R380C6	600	C6	380	3.2	0.298	9.3%
IPP60R600C6	600	C6	600	2.1	0.288	13.7%
IPP60R950C6	600	C6	950	1.5	0.138	9.2%

- Good Eoss reduction (-33%) vs old C3/CP generations
- 600-V C6 family shows low hysteresis loss <10%
- Good choice for ZVS compared to older gen devices
- E.g. – 0.636 uJ @ 500 kHz = 0.32 W – not negligible! Significant temp rise
- E.g. – 50 W @ 93% eff → extra 0.32 W loss → ~0.55% eff drop

Key test results – C7 series

DUT	Vds	Series	Rdson	Eoss @ 450 V (uJ)	Eoss hyst (uJ)	Eoss Hyst %
IPP65R225C7	650	C7	225	2.6	1.478	56.8%
IPA65R190C7	650	C7	190	3.1	1.390	44.8%
IPP65R125C7	650	C7	125	4.7	1.766	37.6%
IPP65R045C7	650	C7	45	13	4.656	35.8%
IPP60R180C7	600	C7	180	3	0.264	8.8%

- Significant Eoss reduction vs older C6 generation
- 600-V C7 shows low hysteresis loss <9%, but also lower Eoss to begin with
 - 600-V C6 vs C7 – 0.636 uJ vs 0.264 uJ – 60% reduction
- 650-V C7 shows significantly higher hysteresis loss
 - Compare 180/190 mR 600/650-V devices – 8.8% vs 45%!

Key test results – P7 series

DUT	Vds	Series	Rdson	Eoss @ 450 V (uJ)	Eoss hyst (uJ)	Eoss Hyst %
IPA70R360P7	700	P7	360	2	0.603	30.1%
IPA70R600P7	700	P7	600	1.23	0.374	30.4%
IPS70R900P7	700	P7	900	0.97	0.235	24.2%
IPS70R1K4P7	700	P7	1400	0.64	0.196	30.6%

- Comparable Eoss values vs C7 650-V generation
- Achieves same Eoss at higher VDS 700 V
- 700-V P7 shows reduced higher hysteresis loss vs 650-V C7
 - Compare 225-mR 650-V C7 (57%) vs 360-mR 700-V P7 (30%)


Key test results – G7 series

DUT	Vds	Series	Rdson	Eoss @ 450 V (uJ)	Eoss hyst (uJ)	Eoss Hyst %
IPT60R150G7	600	G7	150	3.15	0.170	5.4%
IPT65R195G7	650	G7	195	2.6	0.889	34.2%

- Initially marketed as “P7 Gold”, later converted to G7
- Best-in-class Eoss (lower than C6/C7/P7)
- Comparable Eoss – 600-V G7 vs 600-V C7, but at lower Rds(on) (-17%)
- Comparable Eoss – 650-V G7 vs 650-V C7, but at lower Rds(on) (-14%)
- Again – observe a penalty at higher voltage – 650-V vs 600-V 34% vs 5%

Results summary

Eoss Loss vs. Hysteresis Loss Portion

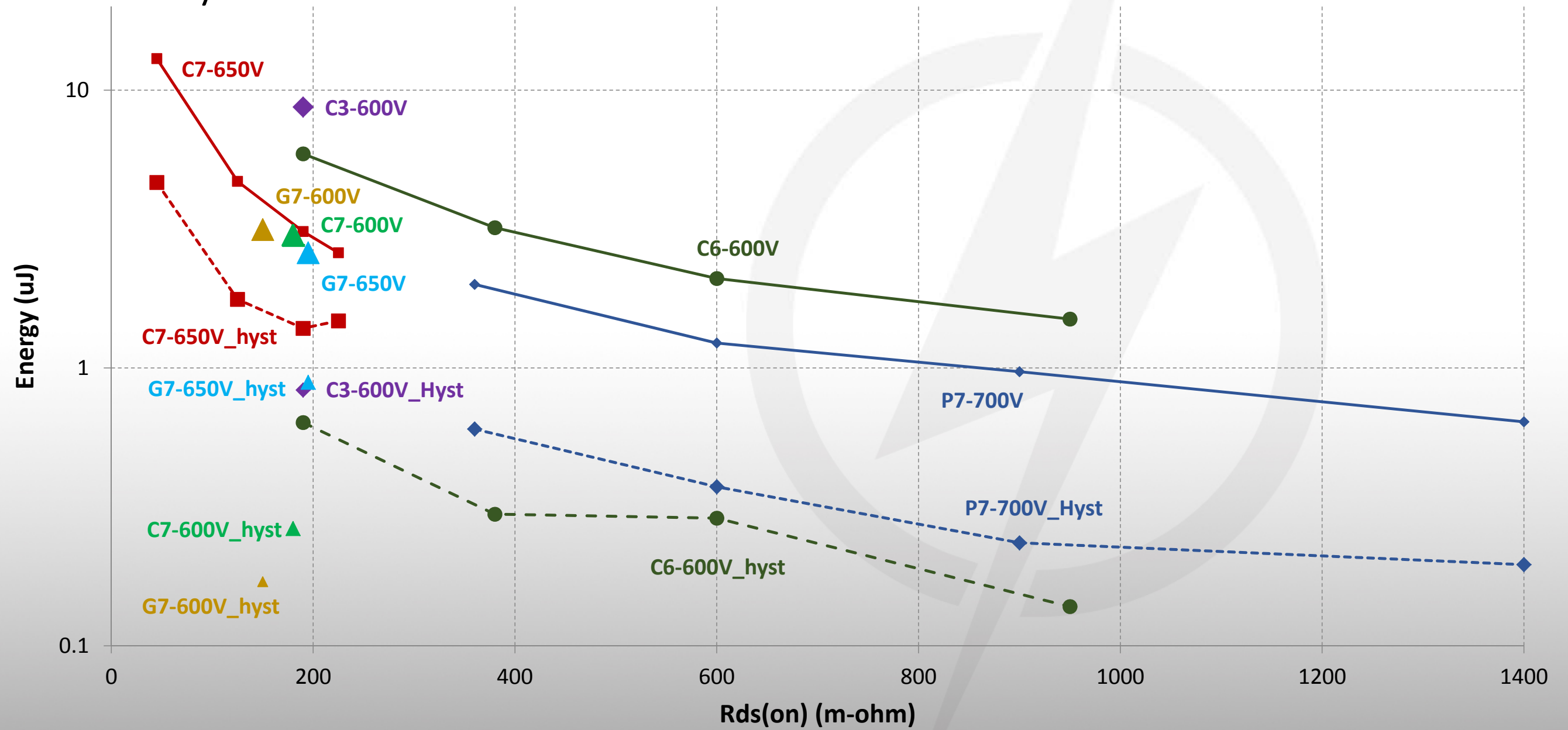

Conclusions & key take-aways

- Coss hysteresis is REAL and can be very apparent in ZVS topologies
- MOSFET datasheets do not include Coss hysteresis loss data; it cannot be predicted from other data
- Industry must encourage MOSFET vendors to test for and publish this data – and to reduce the loss!
- Different MOSFET generations are better suited to various hard-switched, QR & ZVS topologies
- Newer generation devices are improving – lower $R_{ds(on)}$, lower E_{oss} & lower hysteresis loss
- Specific observation – Coss Hysteresis Loss vs VDS Rating:
 - *Similar $R_{ds(on)}$, similar E_{oss} curves – observe higher loss for 650-V vs 600-V rated device*
 - *Depends on internal design and process, cannot be related to VDS rating alone*
- Advantage of Active-Clamp Flyback (ACF) ZVS topology –
 - *“Clean” waveforms allow use of 600-V MOSFETs with lowest E_{oss} and lowest hysteresis loss*
 - *EVM (under development) using 600-V FETs, UCC27712 HB driver, UCC24612 SR driver*



© Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com