

ADC Noise Hands-on Experiment

TIPL 4204-L
TI Precision Labs – SAR ADCs


by Art Kay and Dale Li

Required/Recommended Equipment

- Calculation
 - Simple calculation using OPA320
 - ADS8860 Data Sheet to find RMS noise voltage
 - Combine ADS8860, REF6050, and OPA320 noise for total noise
- Simulation
 - Simulation using OPA320 and REF6050 Models
- Measurement
 - PLABS-SAR-EVM-PDK
 - <http://www.ti.com/tool/plabs-sar-evm-pdk>
 - <http://www.ti.com/tool/ANALOG-ENGINEER-CALC>
 - Download EVM software and purchase EVM

System we are Analyzing and Measuring

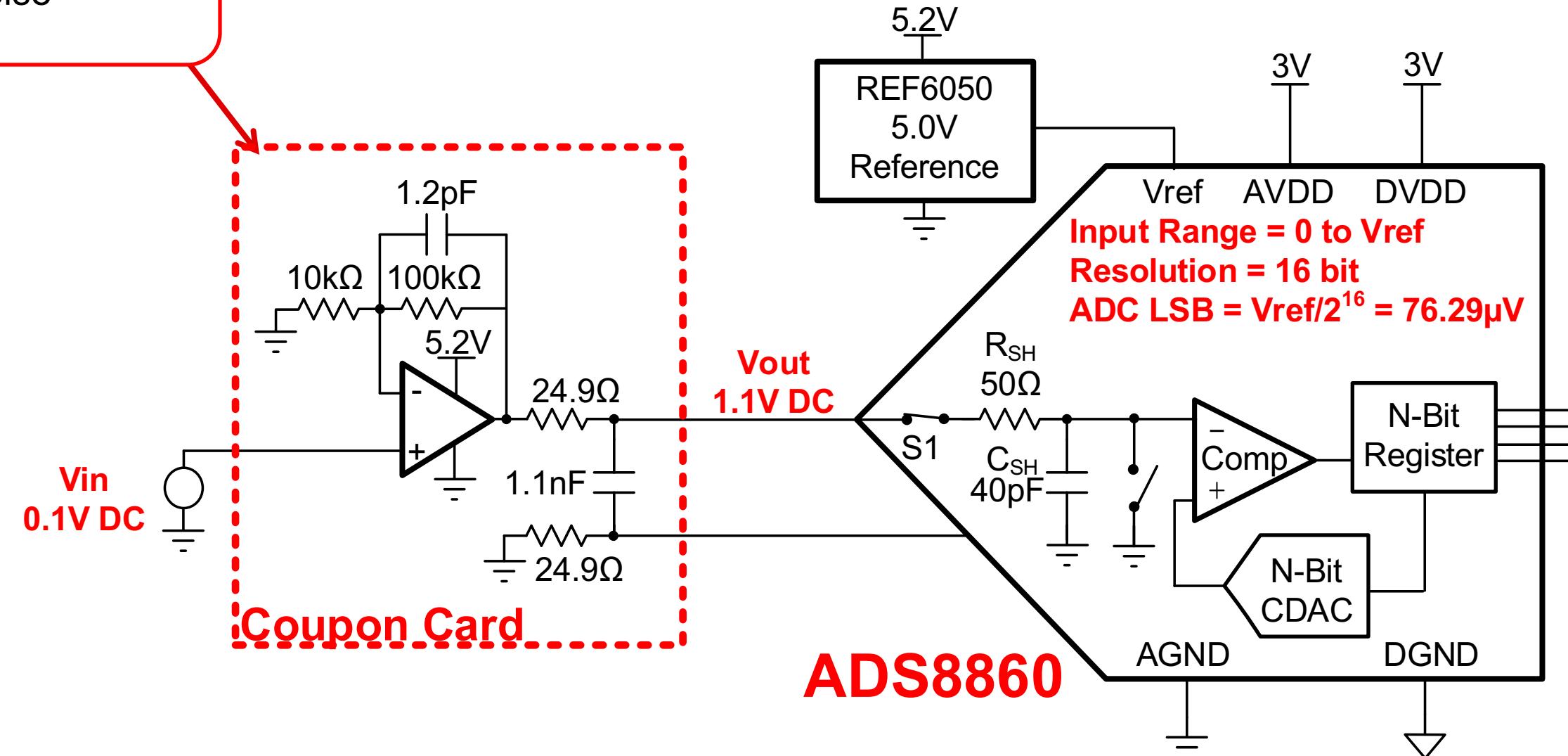
We will use two different "Coupon Cards". Each will have different noise characteristics..




Noise Hand Calculation

- Both circuits have the same: gain, bandwidth, and output filter
- The difference is feedback network resistance is scaled by a factor of 100
- The objective is to see how thermal noise from feedback impacts overall noise

Noise 1

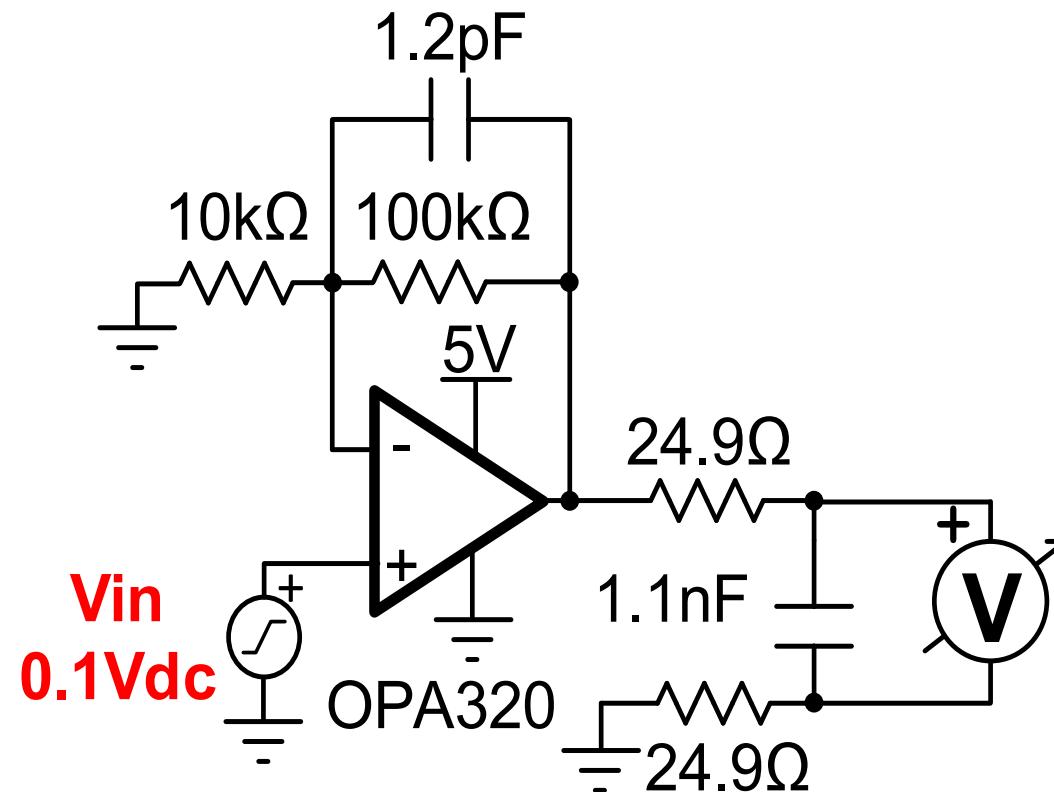

Noise 2

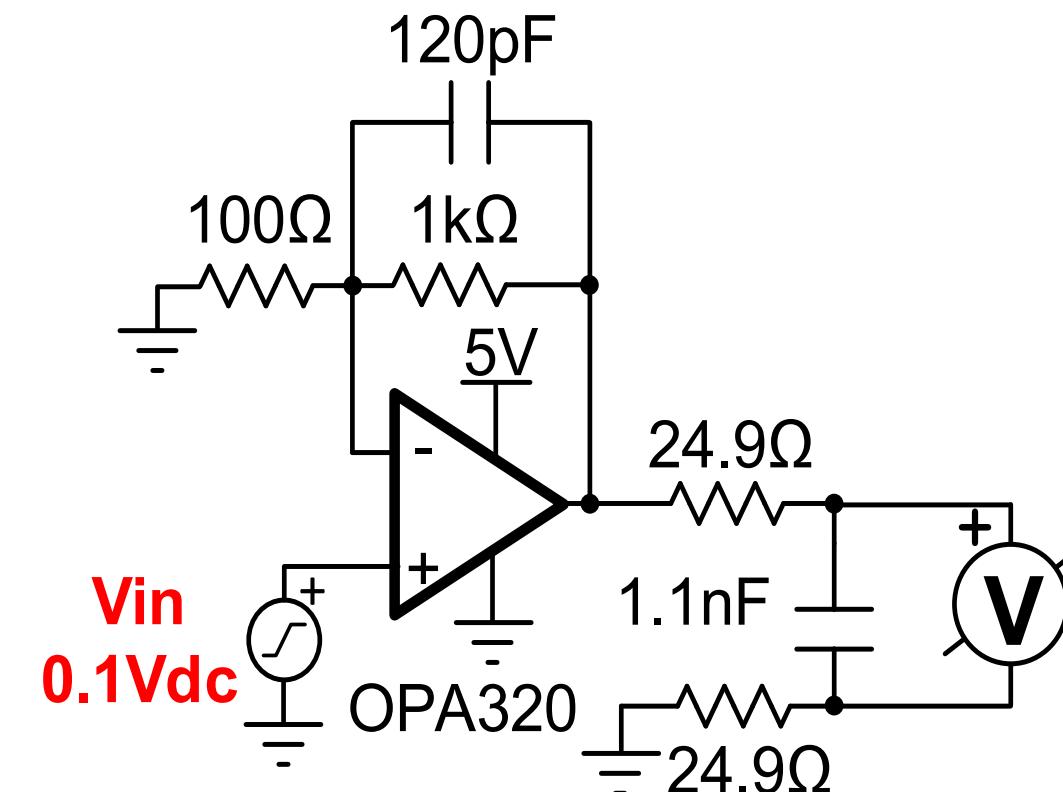

Noise Calculation for Noise 1

$$f_{c_feedback} = \frac{1}{2 \cdot \pi \cdot R_f \cdot C_f} = \frac{1}{2 \cdot \pi \cdot (100k\Omega) \cdot (1.2pF)} = 1.33MHz$$

$$f_{c_ChargeBucket} = \frac{1}{2 \cdot \pi \cdot R_{filt} \cdot C_{filt}} = \frac{1}{2 \cdot \pi \cdot (24.9\Omega) \cdot (1.1nF)} = 5.81MHz$$

$$f_{c_Amp} = \frac{GBW}{Gain} = \frac{20}{11} = 1.82MHz$$

$$f_{c_system_estimate} = 1.33MHz$$

$$BW_n = K_n \cdot f_{c_system_estimate} = (1.22) \cdot (1.33MHz) = 1.62MHz$$

$$R_{eq} = \frac{R_f \cdot R_g}{R_f + R_g} = \frac{(100k\Omega) \cdot (10k\Omega)}{100k\Omega + 10k\Omega} = 9.09k\Omega$$

$$e_{nReq} = \sqrt{4 \cdot k \cdot R_{eq} \cdot T_k} = \sqrt{4 \cdot (1.38 \cdot 10^{-23} J/K) \cdot (9.09k\Omega) \cdot (298.15K)} = 12.23 nV/\sqrt{Hz}$$

$$e_{nTotal} = \sqrt{(e_{nReq})^2 + (e_{nAmp})^2} = \sqrt{(12.23 nV/\sqrt{Hz})^2 + (7 nV/\sqrt{Hz})^2} = 14.09 nV/\sqrt{Hz}$$

$$E_{nTotal_RTI} = e_{nTotal} \cdot \sqrt{BW_n} = (14.09 nV/\sqrt{Hz}) \cdot \sqrt{(1.62MHz)} = 17.88 \mu V \text{ rms}$$

$$E_{nTotal_RTO} = \text{Gain} \cdot E_{nTotal_RTI} = (11) \cdot (17.88 \mu V) = 196.7 \mu V \text{ rms}$$

The system bandwidth is limited by three factors: feedback filter, charge bucket filter, and amplifier gain bandwidth. The overall bandwidth assumes that the feedback and amplifier poles are close, so the system is approximately second order.

Noise from the feedback network.

Combined noise from op amp and feedback network. Integrated and referred to the output.

Noise Calculation for Noise 2

$$f_{c_feedback} = \frac{1}{2 \cdot \pi \cdot R_f \cdot C_f} = \frac{1}{2 \cdot \pi \cdot (1k\Omega) \cdot (120pF)} = 1.33MHz$$

$$f_{c_ChargeBucket} = \frac{1}{2 \cdot \pi \cdot R_{filt} \cdot C_{filt}} = \frac{1}{2 \cdot \pi \cdot (24.9\Omega) \cdot (1.1nF)} = 5.81MHz$$

$$f_{c_Amp} = \frac{GBW}{Gain} = \frac{20}{11} = 1.82MHz$$

$$f_{c_system_estimate} = 1.33MHz$$

$$BW_n = K_n \cdot f_{c_system_estimate} = (1.22) \cdot (1.33MHz) = 1.62MHz$$

$$R_{eq} = \frac{R_f \cdot R_g}{R_f + R_g} = \frac{(1k\Omega) \cdot (100\Omega)}{1k\Omega + 100\Omega} = 90.9\Omega$$

$$e_{n_{Req}} = \sqrt{4 \cdot k \cdot R_{eq} \cdot T_k} = \sqrt{4 \cdot (1.38 \cdot 10^{-23} J/K) \cdot (90.9\Omega) \cdot (298.15K)} = 1.22 nV/\sqrt{Hz}$$

$$e_{n_{Total}} = \sqrt{(e_{n_{Req}})^2 + (e_{n_{Amp}})^2} = \sqrt{(1.22 nV/\sqrt{Hz})^2 + (7 nV/\sqrt{Hz})^2} = 7.11 nV/\sqrt{Hz}$$

$$E_{n_{Total_RTI}} = e_{n_{Total}} \cdot \sqrt{BW_n} = (7.11 nV/\sqrt{Hz}) \cdot \sqrt{(1.62MHz)} = 9.02 \mu V \text{ rms}$$




$$E_{n_{Total_RTO}} = \text{Gain} \cdot E_{n_{Total_RTI}} = (11) \cdot (17.88 \mu V) = 99.2 \mu V \text{ rms}$$

The system bandwidth is limited by three factors: feedback filter, charge bucket filter, and amplifier gain bandwidth. The overall bandwidth assumes that the feedback and amplifier poles are close, so the system is approximately second order.

Noise from the feedback network.


Combined noise from op amp and feedback network. Integrated and referred to the output.

Simulation of Noise1

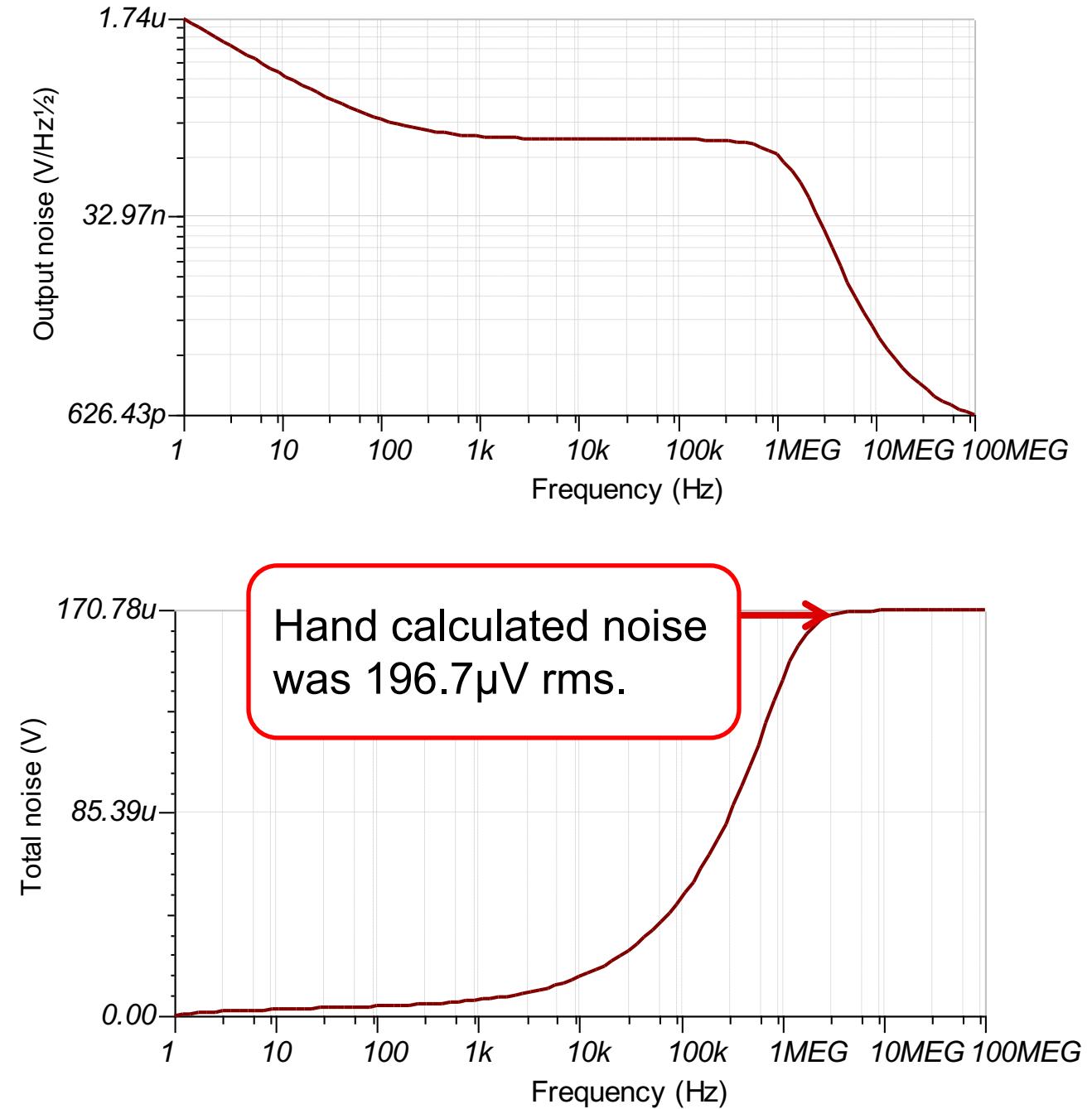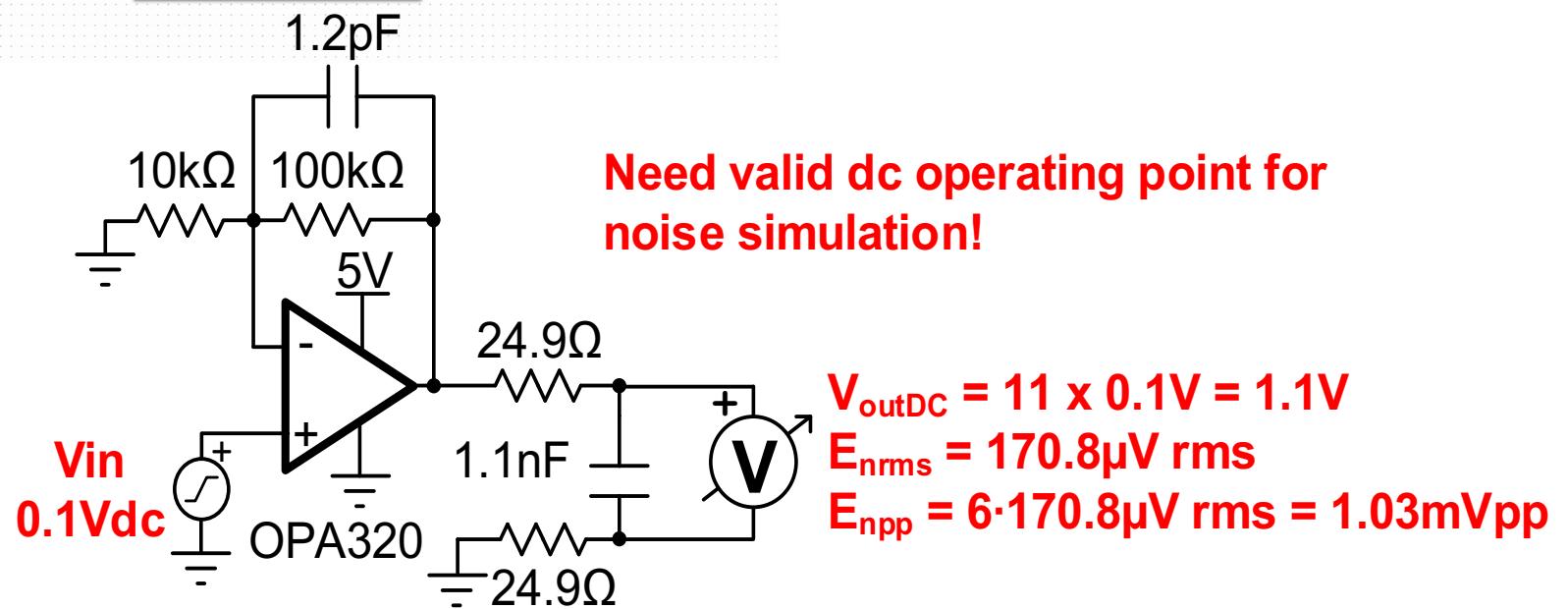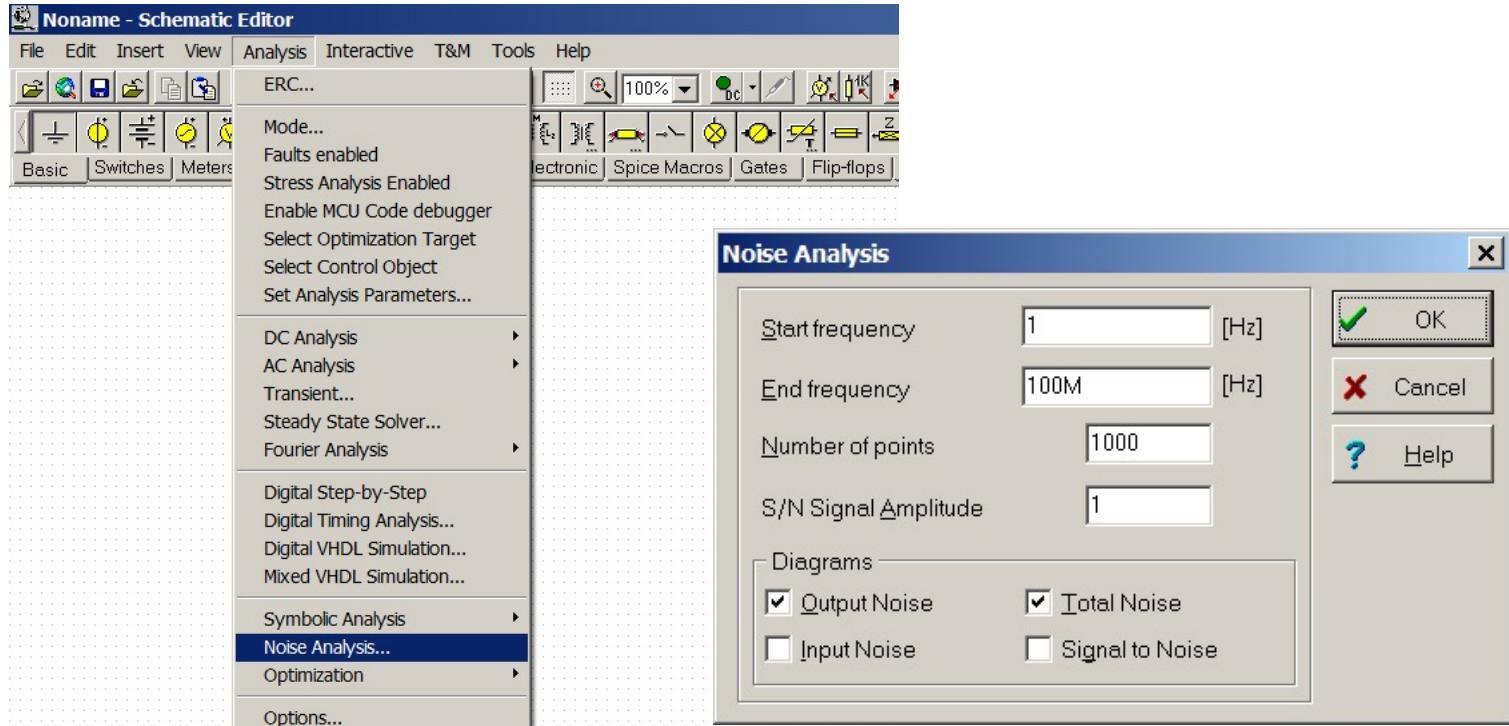


Noise 1 vs Noise 2

Noise 1

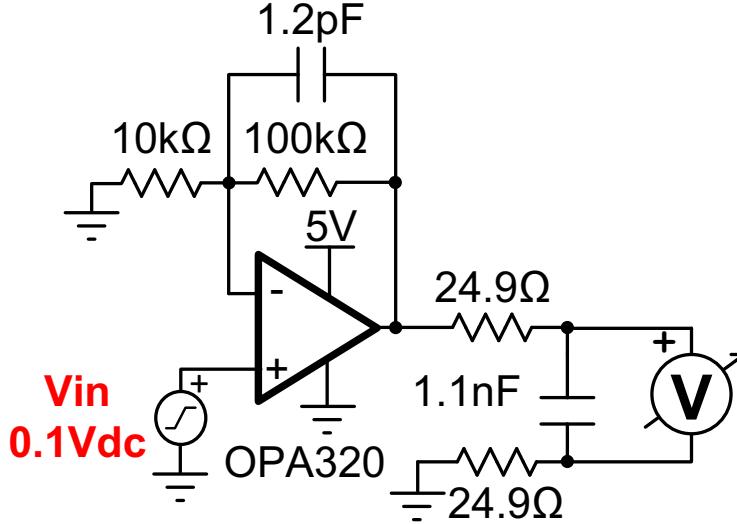

Noise 2

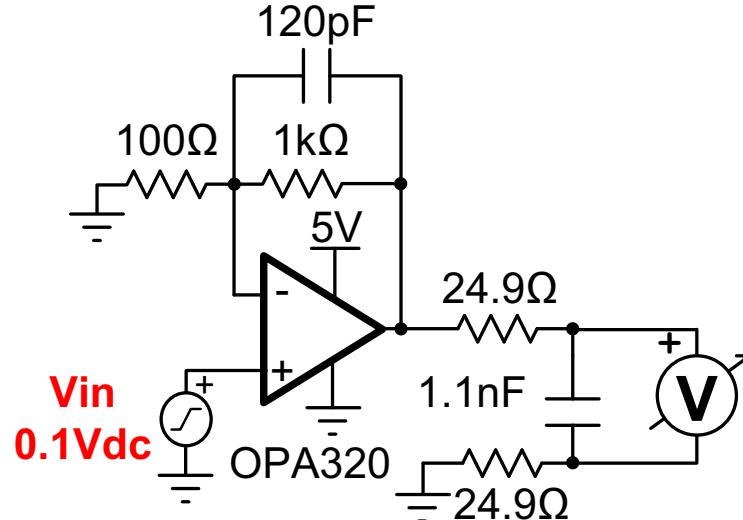


Click to access
TINA simulation.

OPA320_Noise1.TSC



OPA320_Noise2.TSC

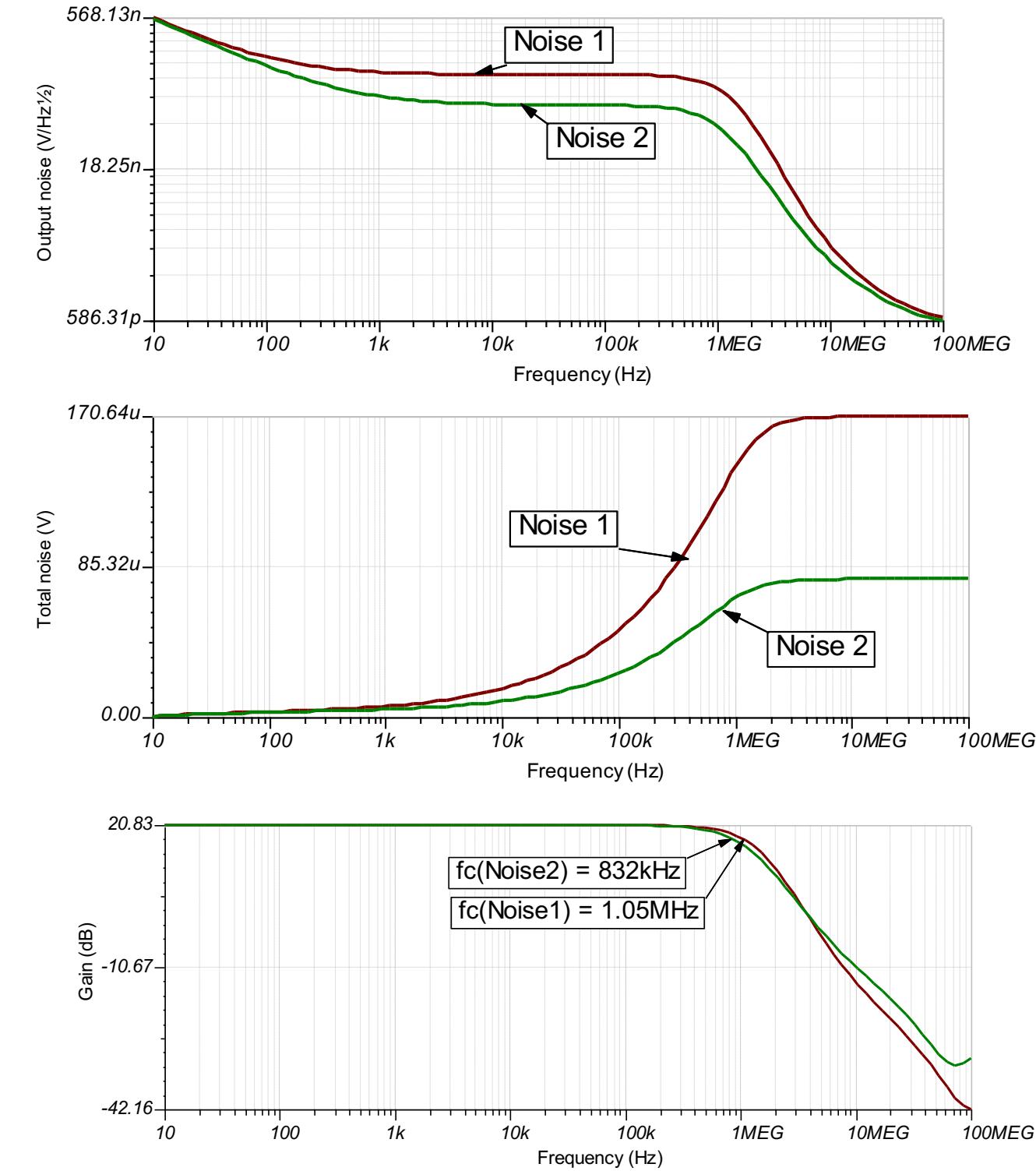

Find the REF6050 Noise

1. Analysis> Noise Analysis

2. Enter the bandwidth and select the diagrams

3. The integrated noise is the “total noise”. Look at the final value $V_{nRef} \approx 6.31\mu V$ rms

U1 REF6050

REF6050

VIN

EN

SS

FILT

OUT_F

OUT_S

GND_S

GND_F

VREF

C4 22u

VG 5.5

R5 120k

C2 1u

Noise Analysis

Start frequency 1 [Hz]

End frequency 1MEG [Hz]

Number of points 1000

S/N Signal Amplitude 1

Diagrams

Output Noise Total Noise

Input Noise Signal to Noise

Noname - Total noise8

Total noise (V)

6.31u

3.15u

0.00

1.00


1.00k

1.00MEG

Frequency (Hz)

Total noise6 Output noise7 Total noise7 Output noise8 Total noise8

Total System Noise for OPA320_Noise1

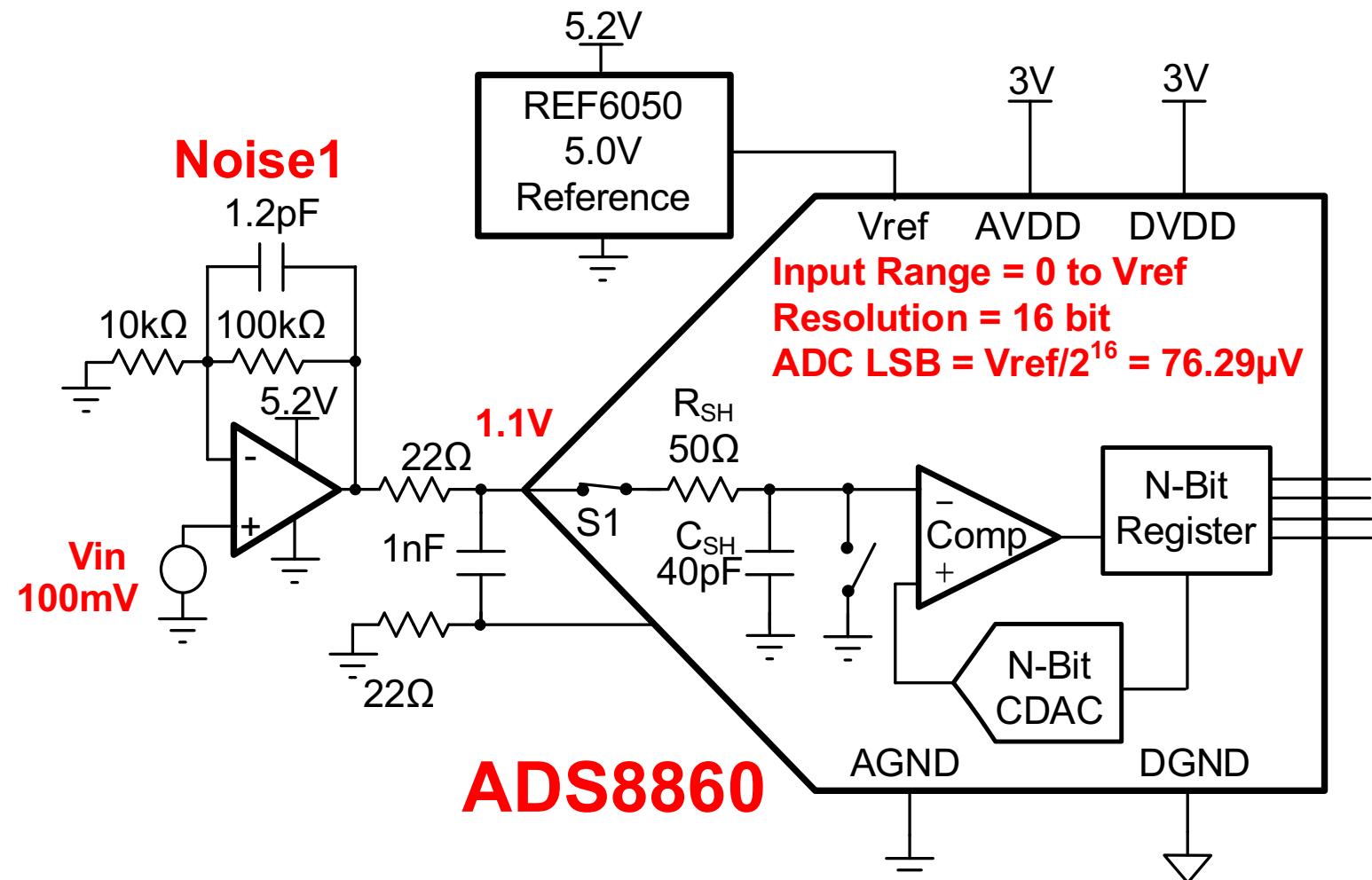


$$\begin{aligned} V_{FSR_rms} &= V_{FSRpk} \cdot 0.707 \\ V_{FSR_rms} &= 0.5 \cdot FSR \cdot 0.707 \\ &= 0.5 \cdot 5\text{V} \cdot 0.707 = 1.767\text{V} \end{aligned}$$

$$V_{nADC} = \frac{V_{FSR_rms}}{10^{\left(\frac{SNR_{ADC}}{20}\right)}} = \frac{1.767\text{V}}{10^{\left(\frac{93\text{dB}}{20}\right)}} = 39.6\mu\text{V rms}$$


$$\begin{aligned} V_{nT} &= \sqrt{(V_{nADC})^2 + (V_{nAmp})^2 + (V_{nRef})^2} \\ &= \sqrt{(39.6\mu\text{V})^2 + (170.8\mu\text{V})^2 + (6.3\mu\text{V})^2} = 175.4\mu\text{V rms} \end{aligned}$$

$$SNR_{total} = 20 \cdot \log\left(\frac{V_{FSR_{rms}}}{V_{nT}}\right) = 20 \cdot \log\left(\frac{1.767\text{V}}{175.4\mu\text{V}}\right) = 80.1\text{ dB}$$

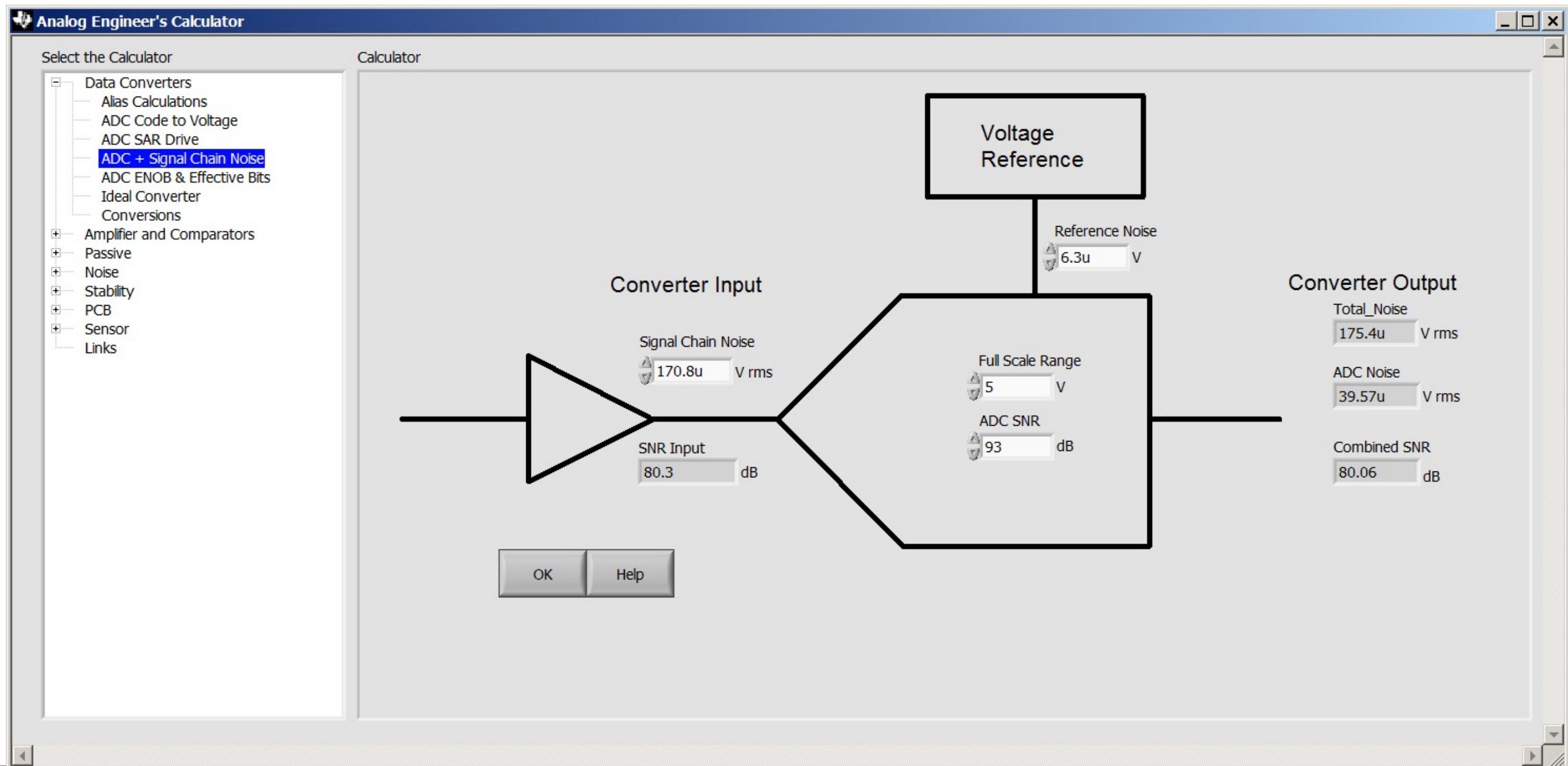
Solve Using the Analog Engineer's Calculator




Connect the hardware

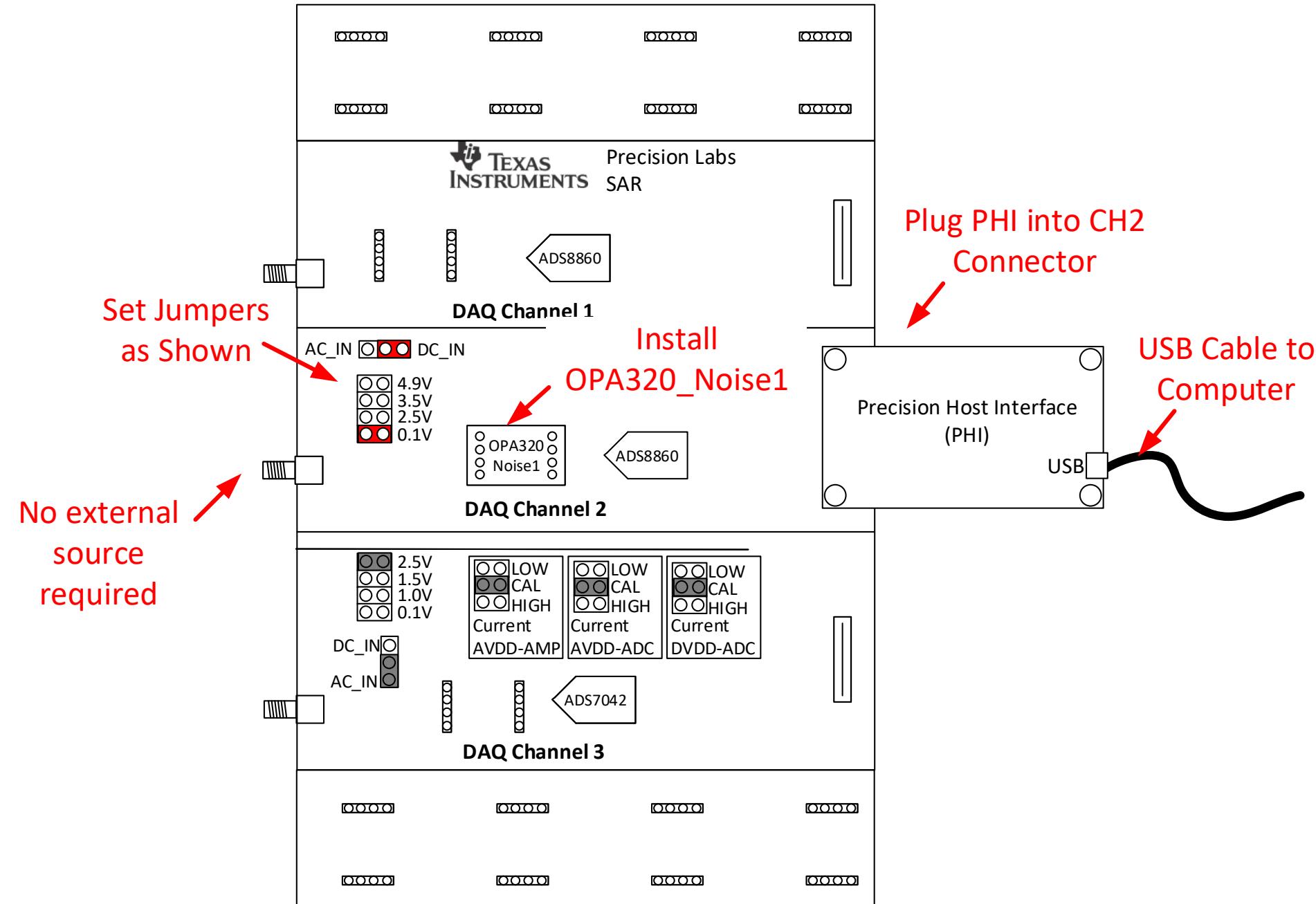

Start & Setup the PLABS-SAR EVM Software

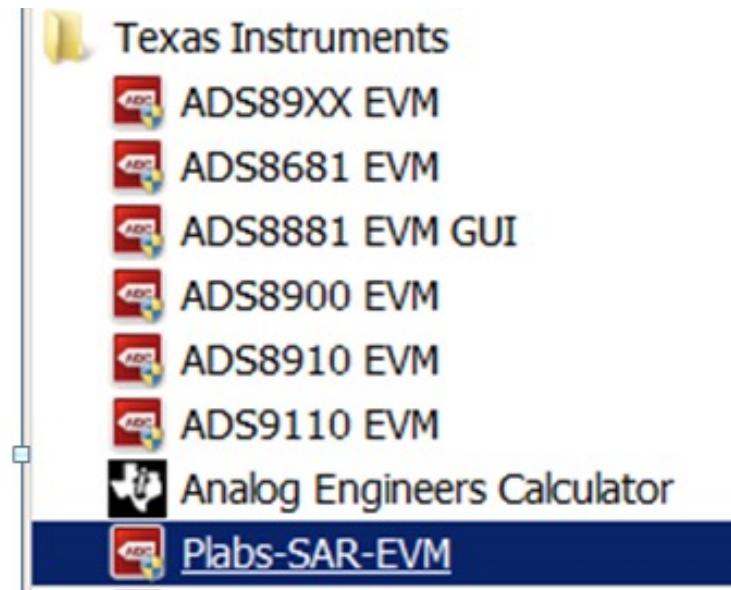

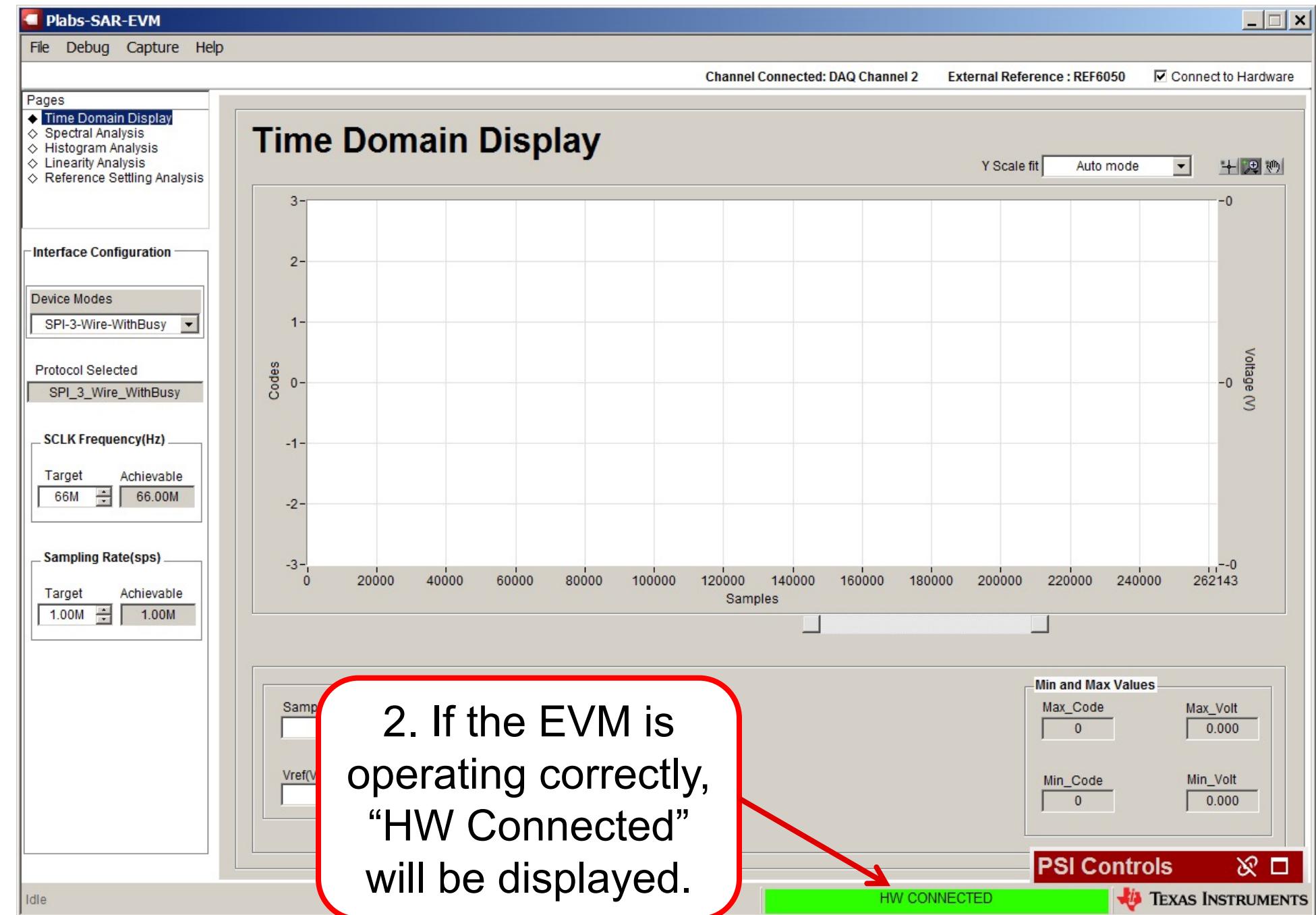
1. Select “Plabs-SAR-EVM” from “start>All Programs”




2. If the EVM is operating correctly, “HW Connected” will be displayed.

Measure the Noise and DC Level

4. Change page to “Histogram Analysis”

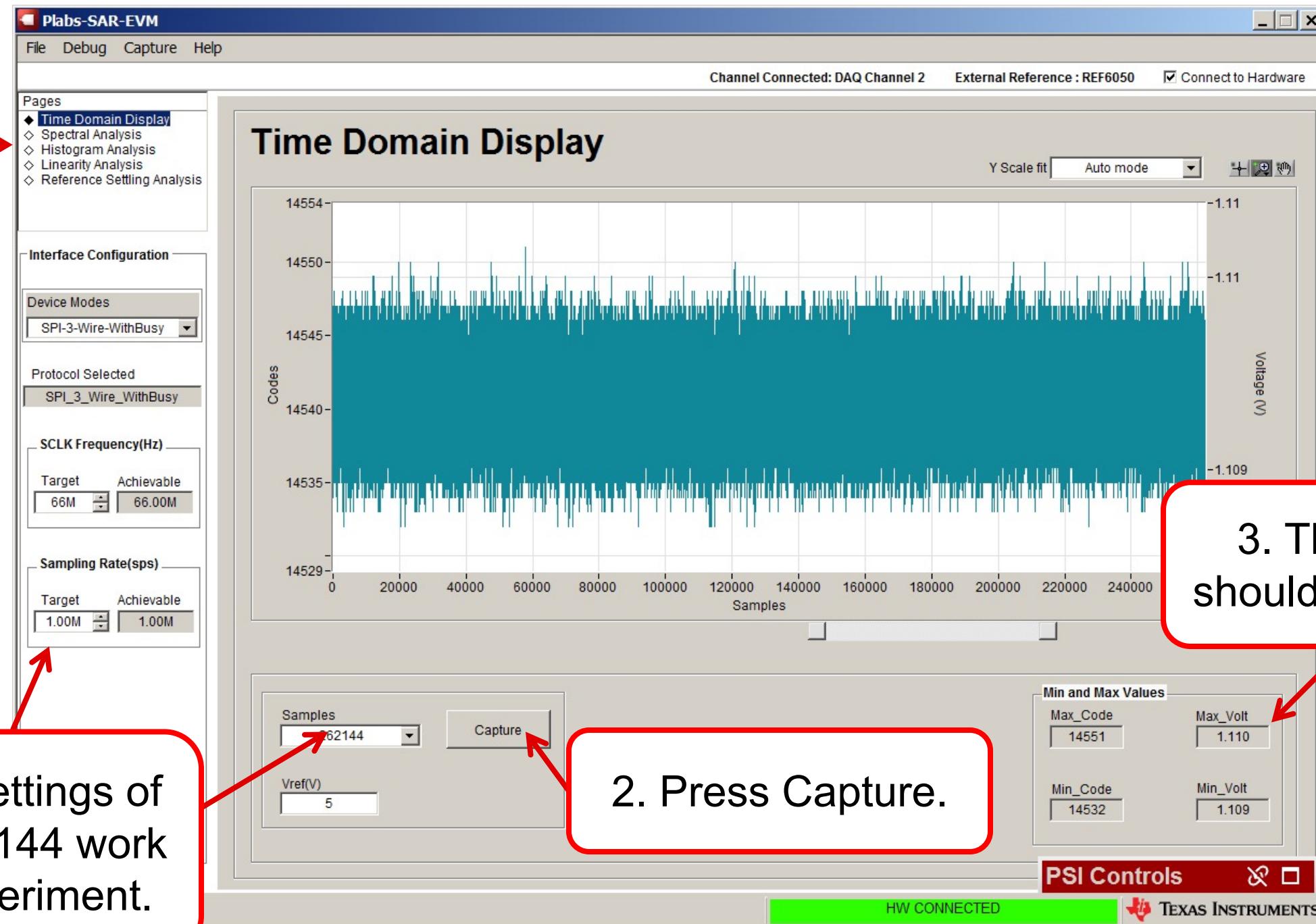

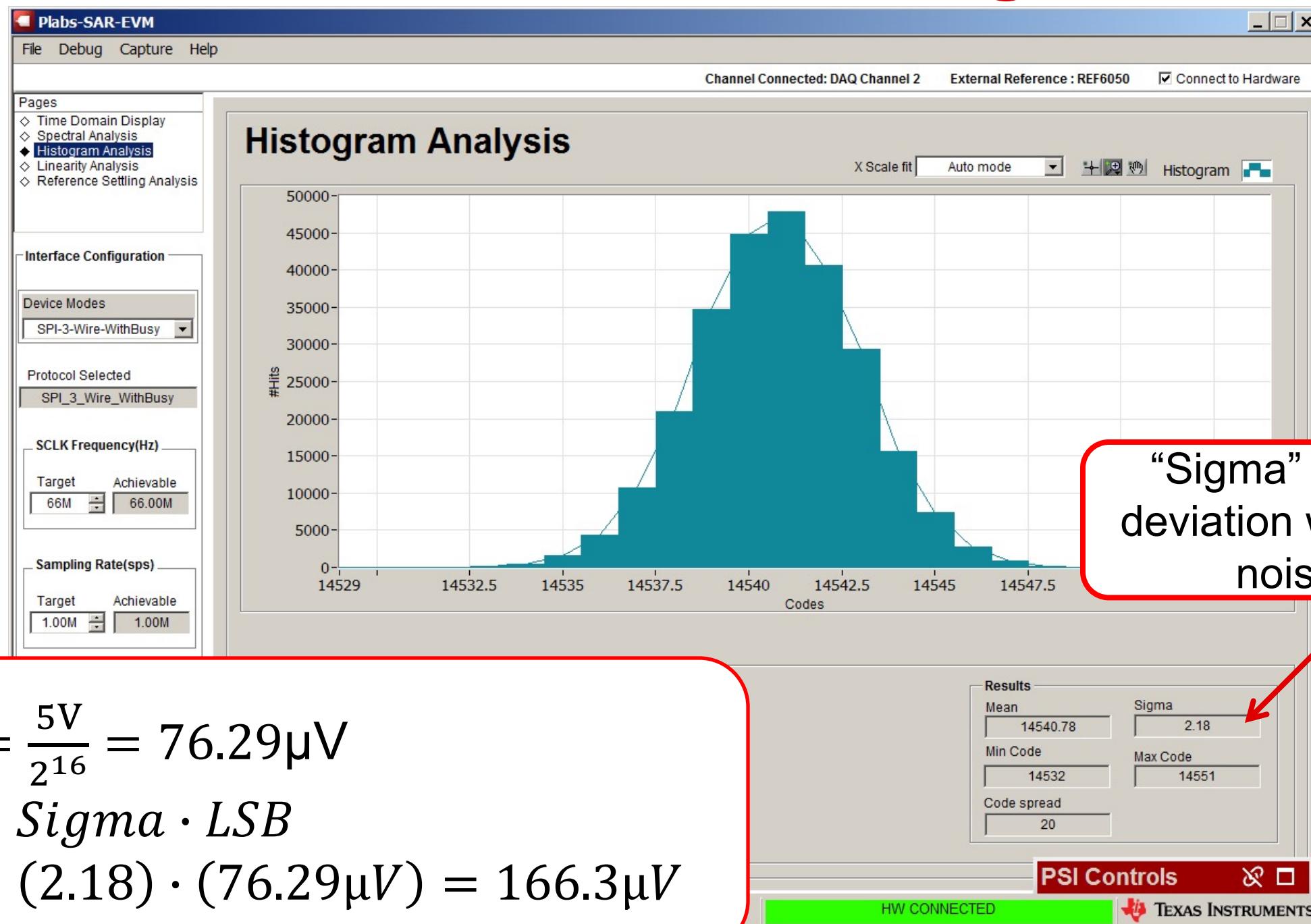Look at the Statistics Under “Histogram Analysis”




Measured vs Expected Results

Your results should show the same trend as the expected result but the specific values will differ.

		$V_{in} = 0.1V \text{ DC}, f_{samp} = 1\text{MHz}, V_{ref} = 5V, LSB = 76.29\mu\text{V}$							
Device	Hand Calc	Simulated				Example Measurements		Your Measurements	
	Amp Noise (uV)	Amp Noise (uV)	ADC Noise (uV)	Ref Noise (uV)	Total Noise (uV)	Sigma	Noise (uV)	Sigma	Noise (uV)
Noise1	196.7	170.8	39.6	11.2	175.4	2.18	166.3		
Noise2	99.1	78.8	39.6	11.2	88.4	1.16	88.5		

Export Data to Excel

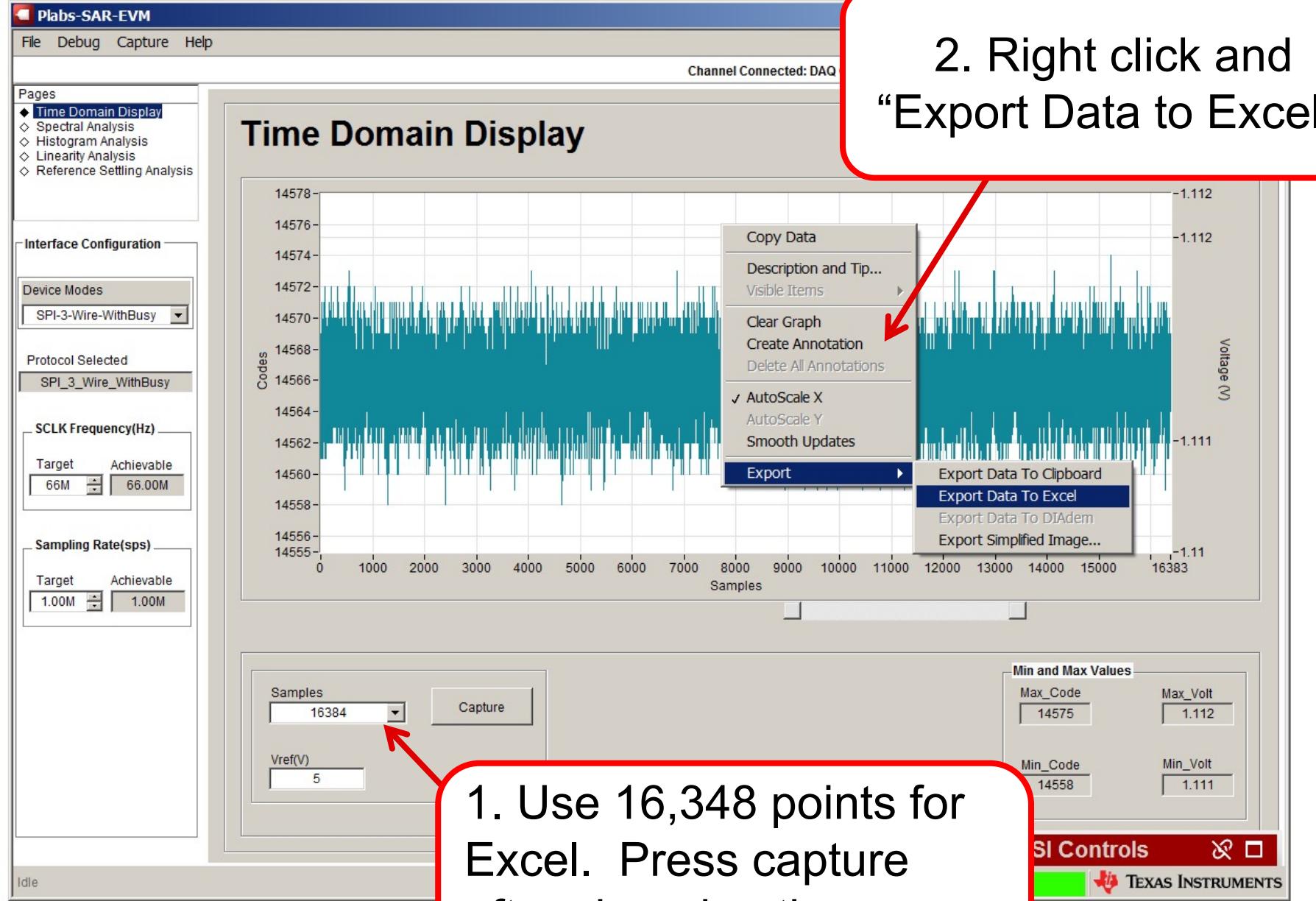

A	B
1	Samples - Analog Channel 0
2	Codes - Analog Channel 0
3	14559
4	14566
5	14566
6	14567
7	14567
8	14568
9	14563
10	14564
11	14564
12	14564
13	14568
14	14562
15	14566
16	14567
17	14567
18	14566
19	14567
20	14569
21	14564
22	14562
23	14567

3. An Excel spreadsheet will open up.

Selecting a Column in Excel

2. Press “Shift-Ctrl-Down Arrow” to select the entire row.




3. Press “Ctrl-C” to copy.

1. Select cell “B2” in the spreadsheet.

	A	B	C
1	Samples - Analog Channel 0	Codes - Analog Channel 0	
2	0	14559	
3	1	14566	
4	2	14566	
5	3	14567	
6	4	14567	
7	5	14568	
8	6	14568	
9	7	14563	
10	8	14564	
11	9	14564	
12	10	14564	
13	11	14568	
14	12	14562	
15	13	14566	
16	14	14567	
17	15	14567	
18	16	14566	
19	17	14567	
20	18	14569	
21	19	14564	
22	20	14562	
23	21	14567	

Paste Your Results Under “Raw Codes”

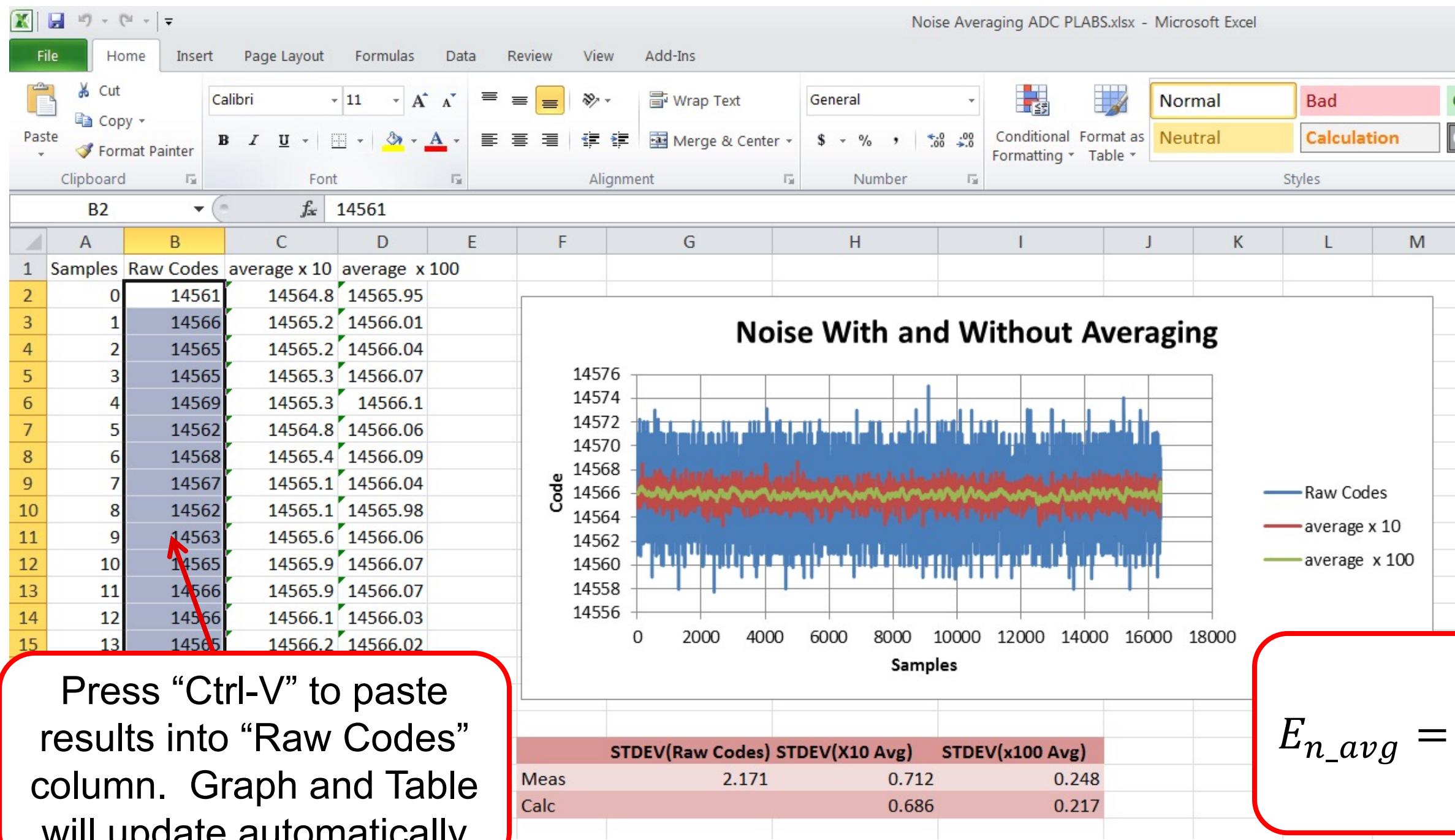

Click to access
Excel
Spreadsheet.



Microsoft Excel
Worksheet

$$E_{n_avg} = \frac{E_{n_raw}}{\sqrt{N}}$$

Press “Ctrl-V” to paste results into “Raw Codes” column. Graph and Table will update automatically

Thanks for your time!