


Developing the SAR Reference Input Model

TIPL 4505


TI Precision Labs – ADCs

Created by Luis Chioye



Presented by Cynthia Sosa

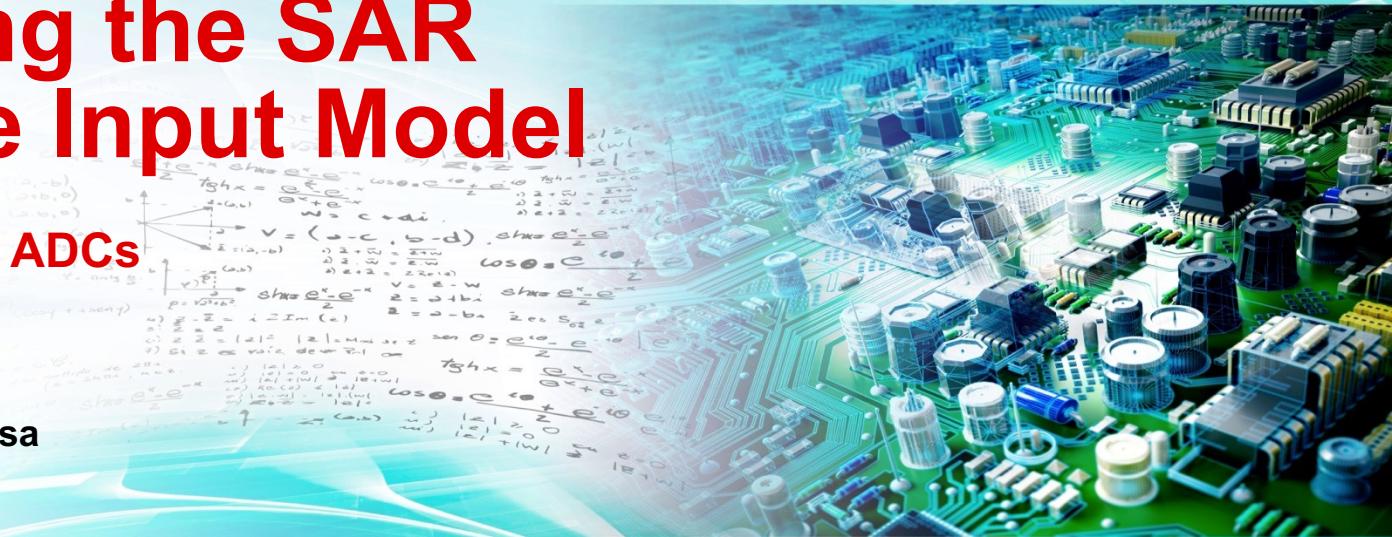

We need to configure the switch timing

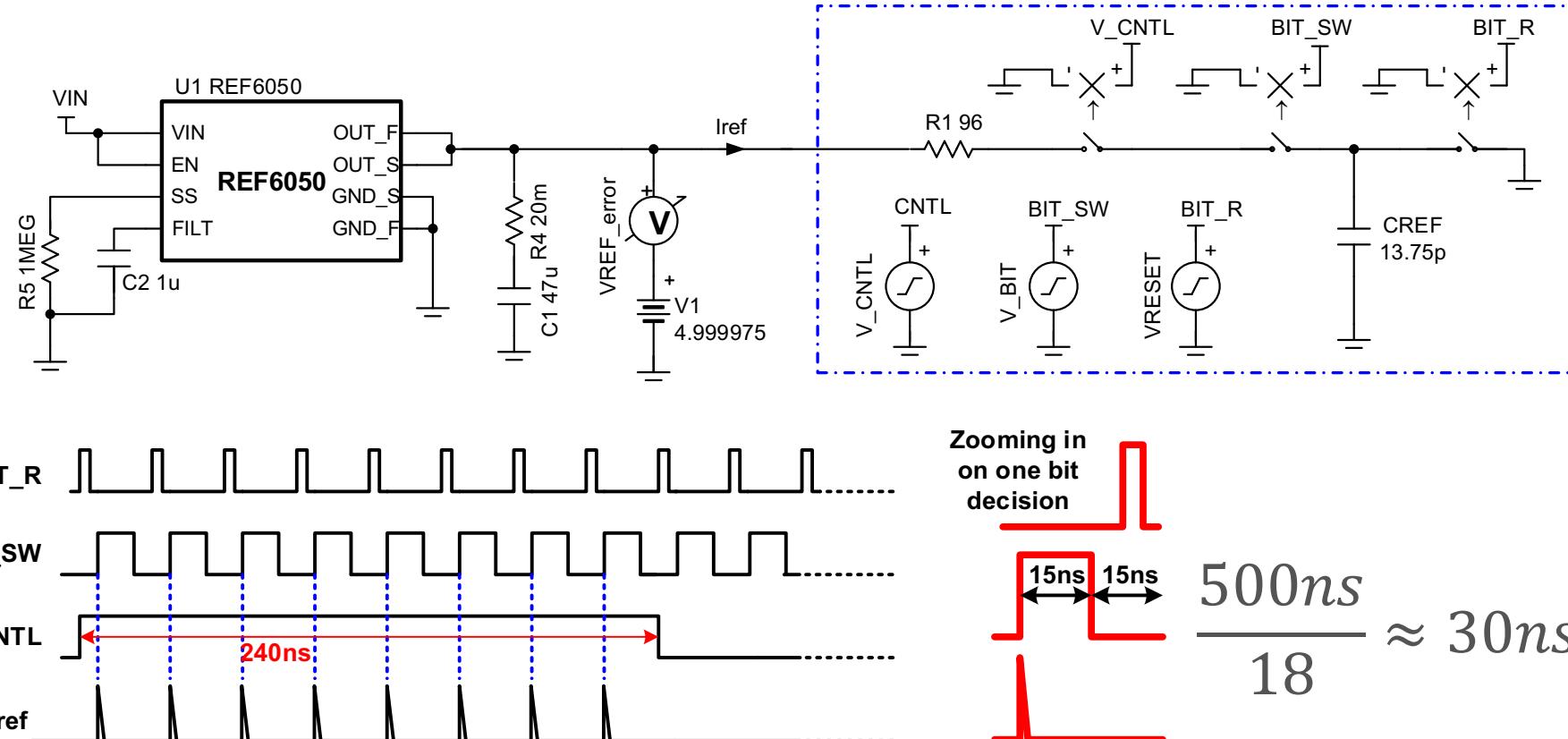

Configure the voltage controlled switch

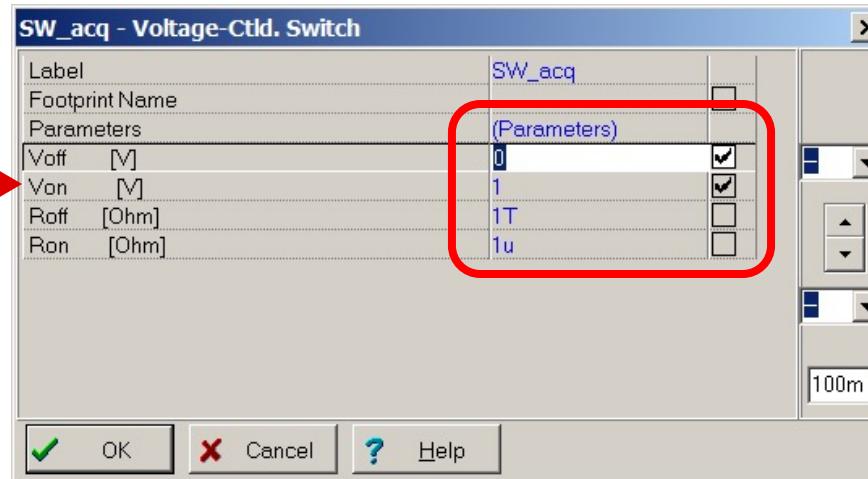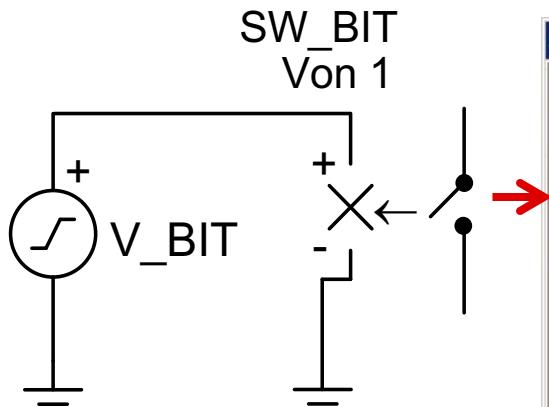

Set all parameters as shown.


Default Roff=1GΩ and Ron=0Ω will impact accuracy.




TEXAS INSTRUMENTS

Configure the signal source to control the switch

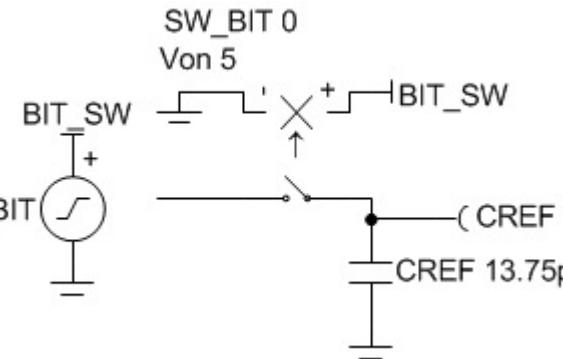
1. Click on source to select and edit switch control signal




3. Select
“Piecewise linear”

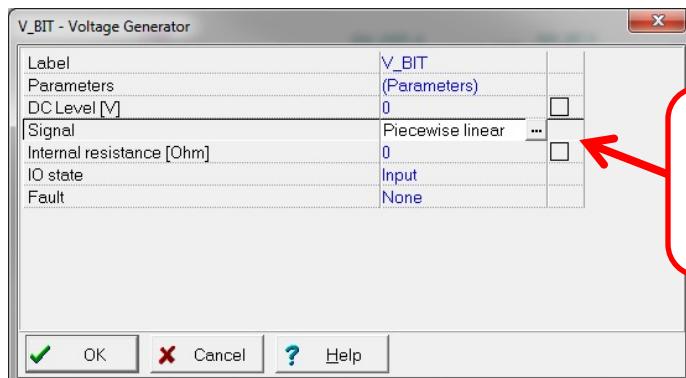

2. Under signal, click here to edit.

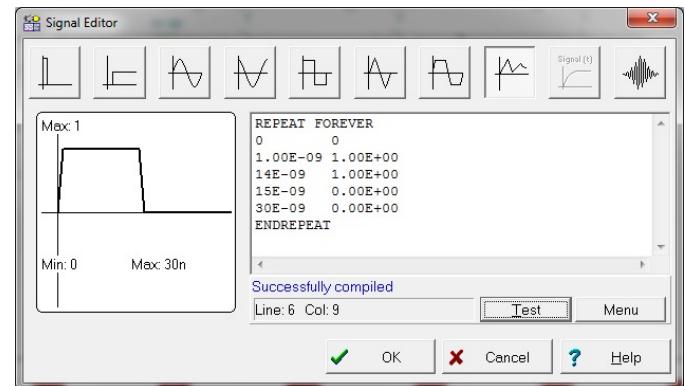


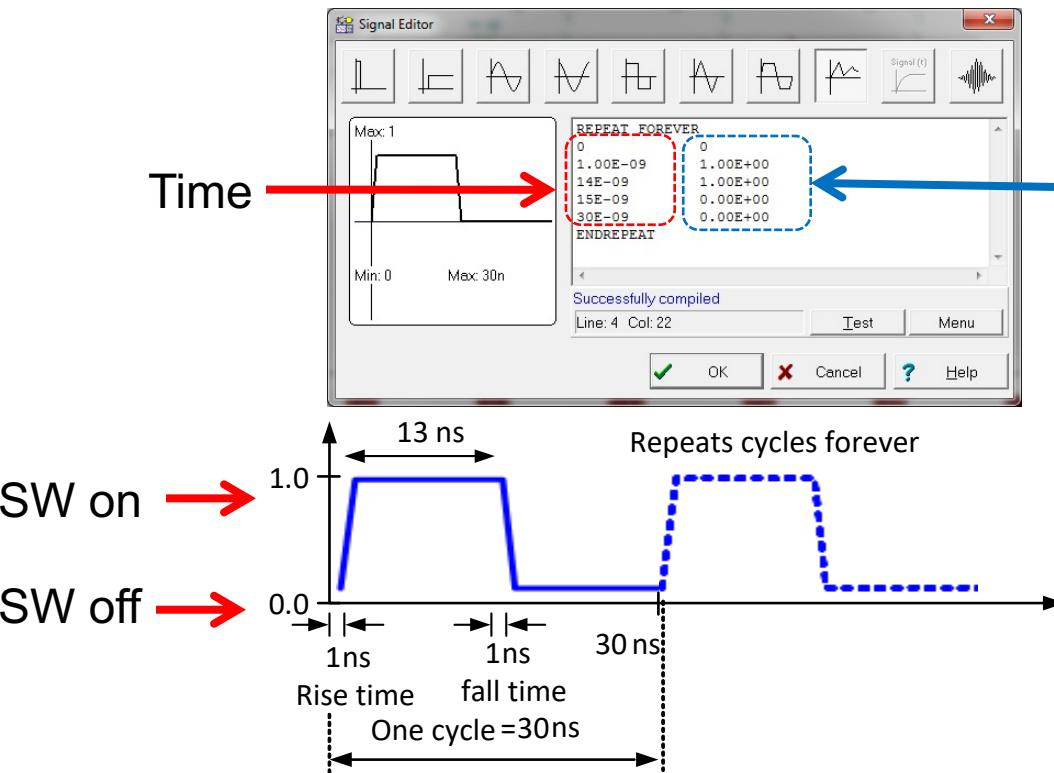Configure the signal source to control the switch




Voltage levels
On: $V \geq 1V$
Off: $V \leq 0$


Example simulation: simulator settings

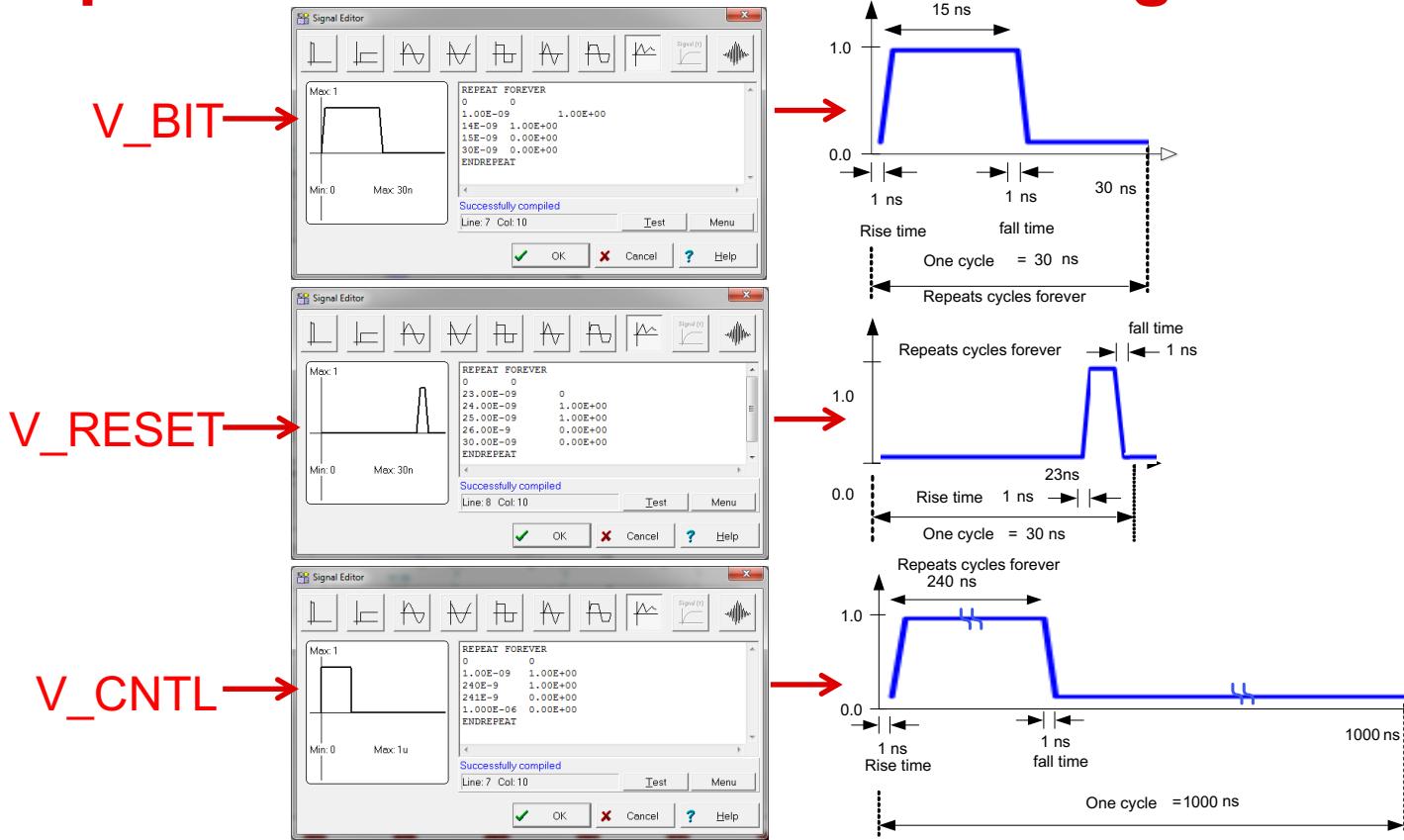

Optimizing Simulation Results

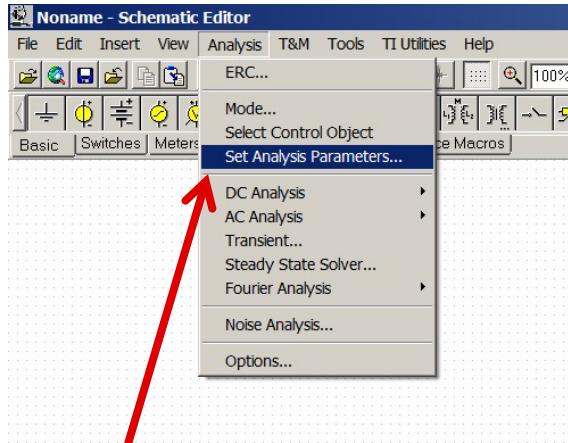

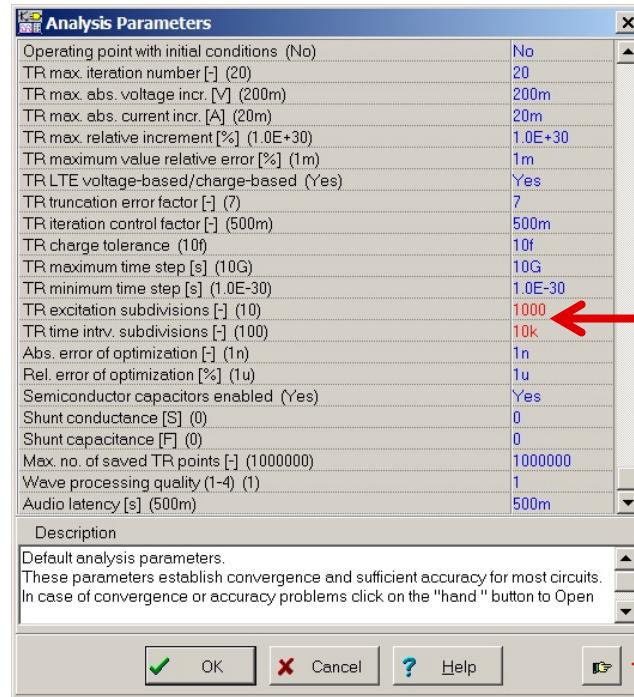"Set Analysis Parameters"
adjusts how the simulator math
engine operates.




TR excitation subdivisions = 1000
TR time intrv. subdivisions = 10k
This increases the number of
points vs time so that transient
behaviors aren't obscured.

Press this button to
expand the list.




Texas Instruments


Optimizing Simulation Results

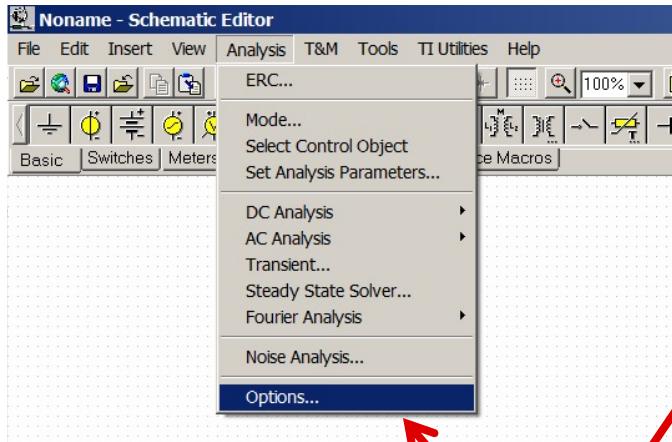

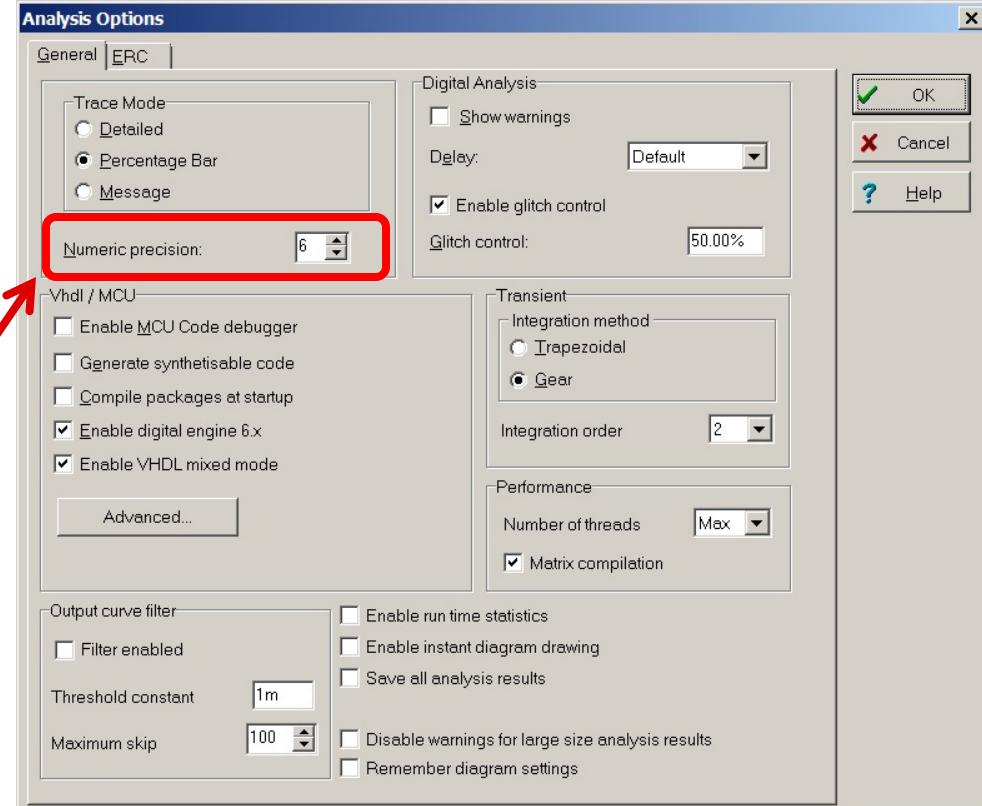Set the “numeric precision” to 6 digits.
This will allow us to see dc operating
points to six digits. The importance of
this is highlighted on the next slide.





Steady state Simulation Results

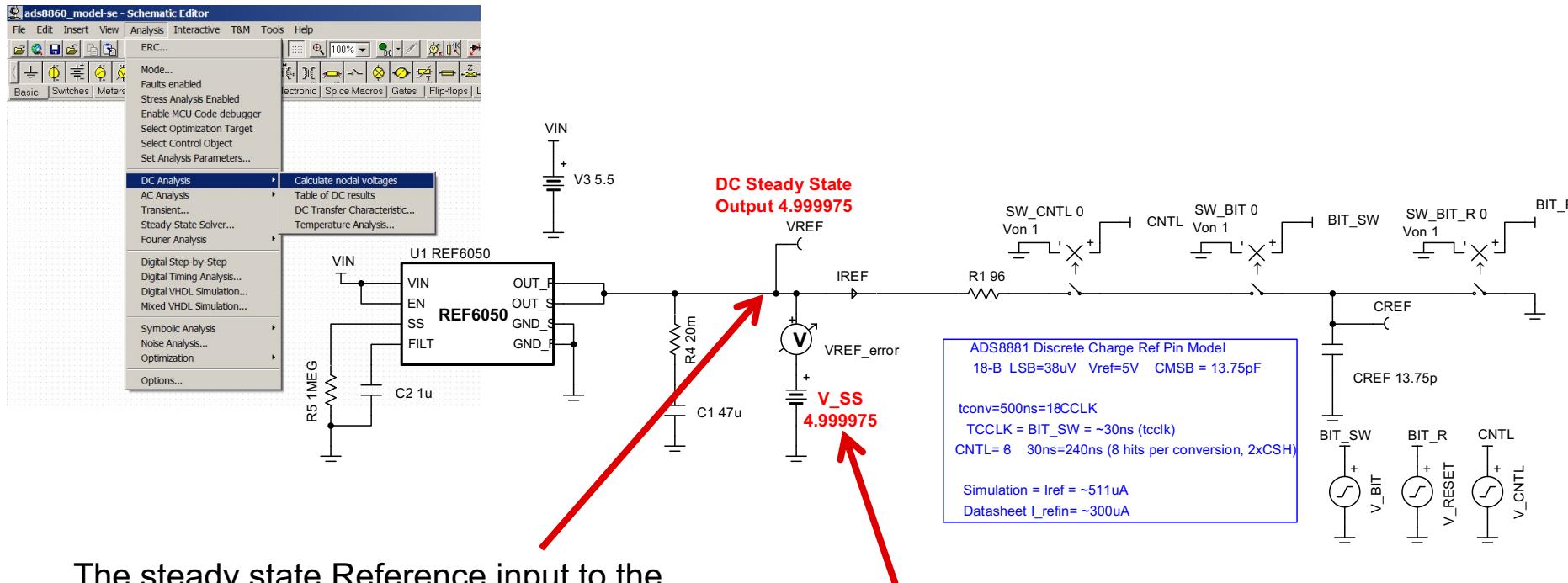



The steady state Reference input to the includes external reference initial accuracy error.

Set the **V_SS** source to match the steady state Reference input.

Example simulation: transient results

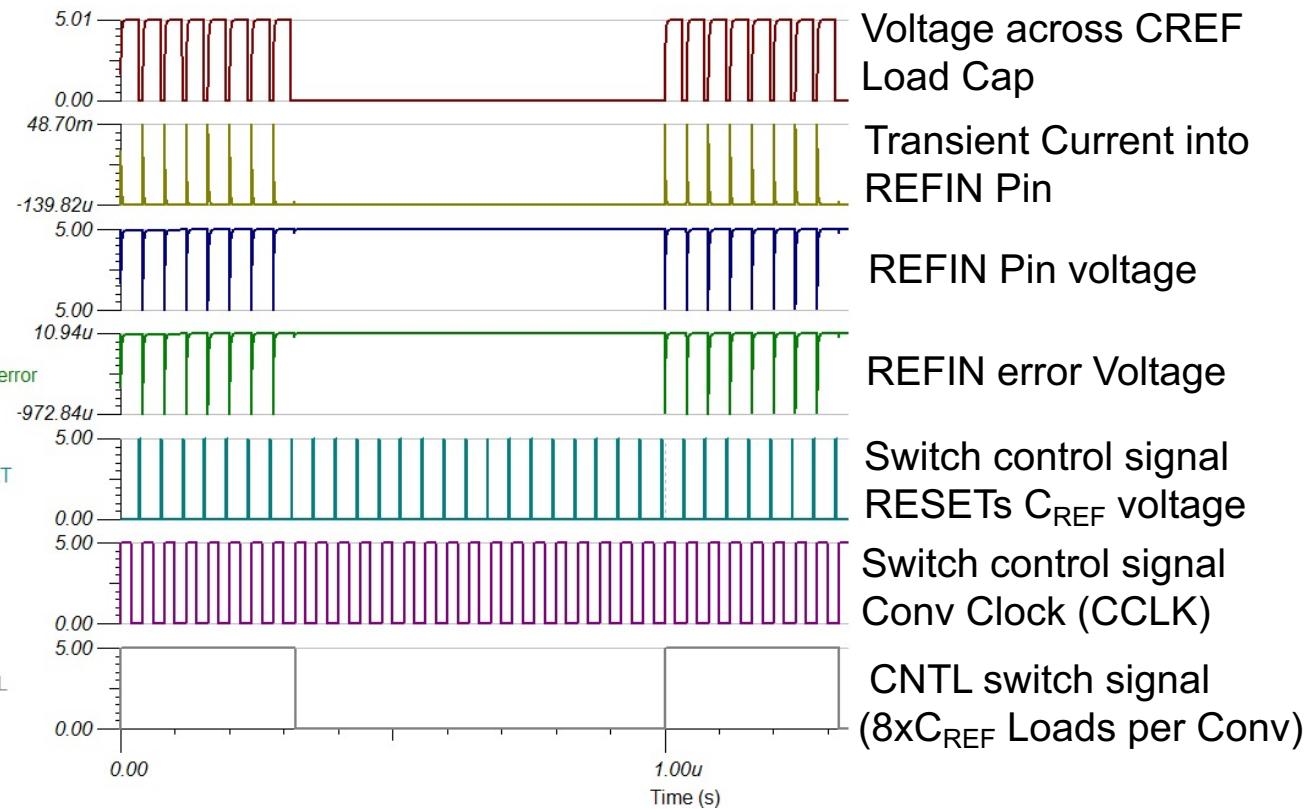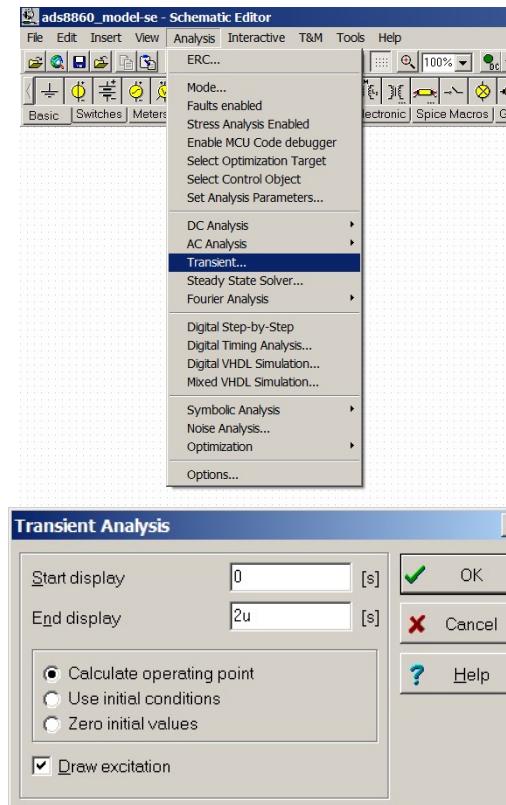



Key Result: Error Signal

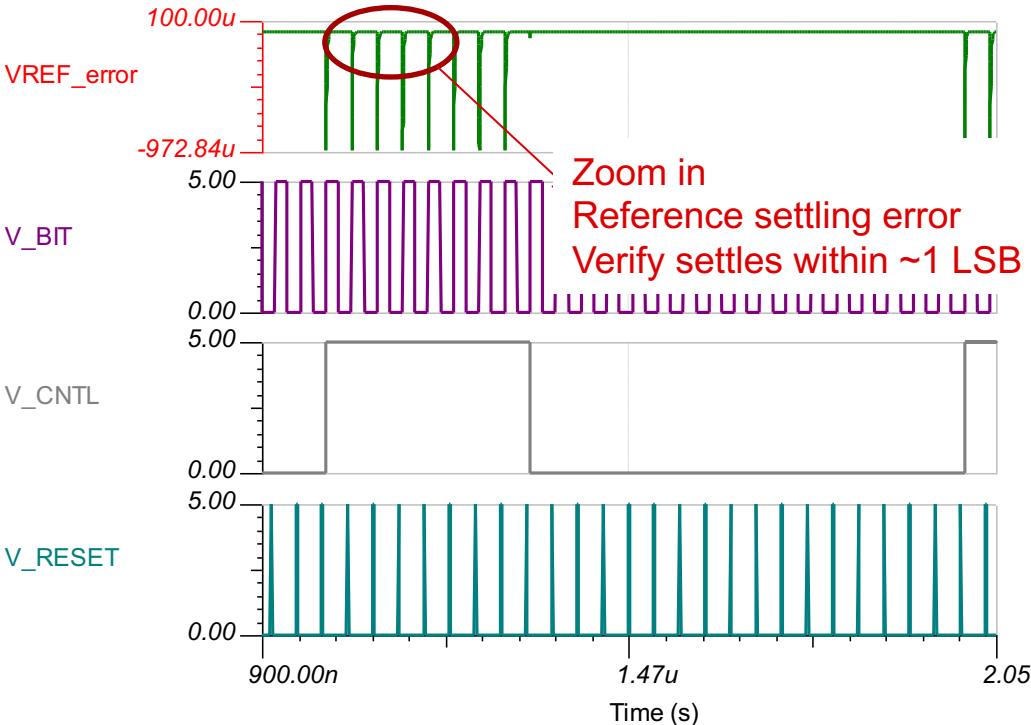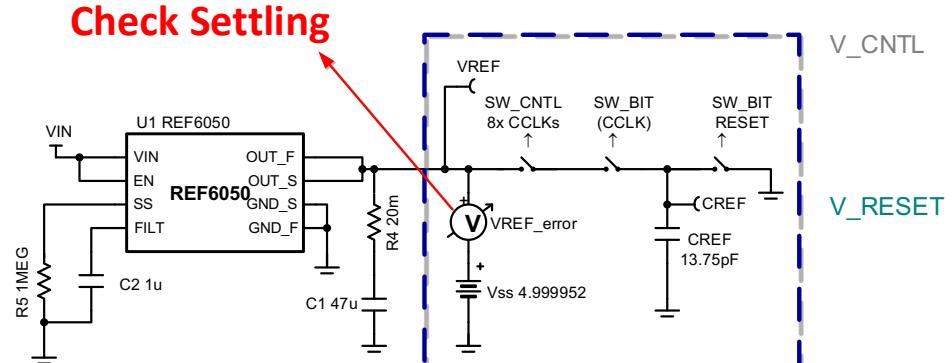

Key Result: Error Signal

$$LSB = \frac{\pm VREF}{2^N} = \frac{2 \cdot VREF}{2^{18}} = 38.14\mu V$$



Check Settling

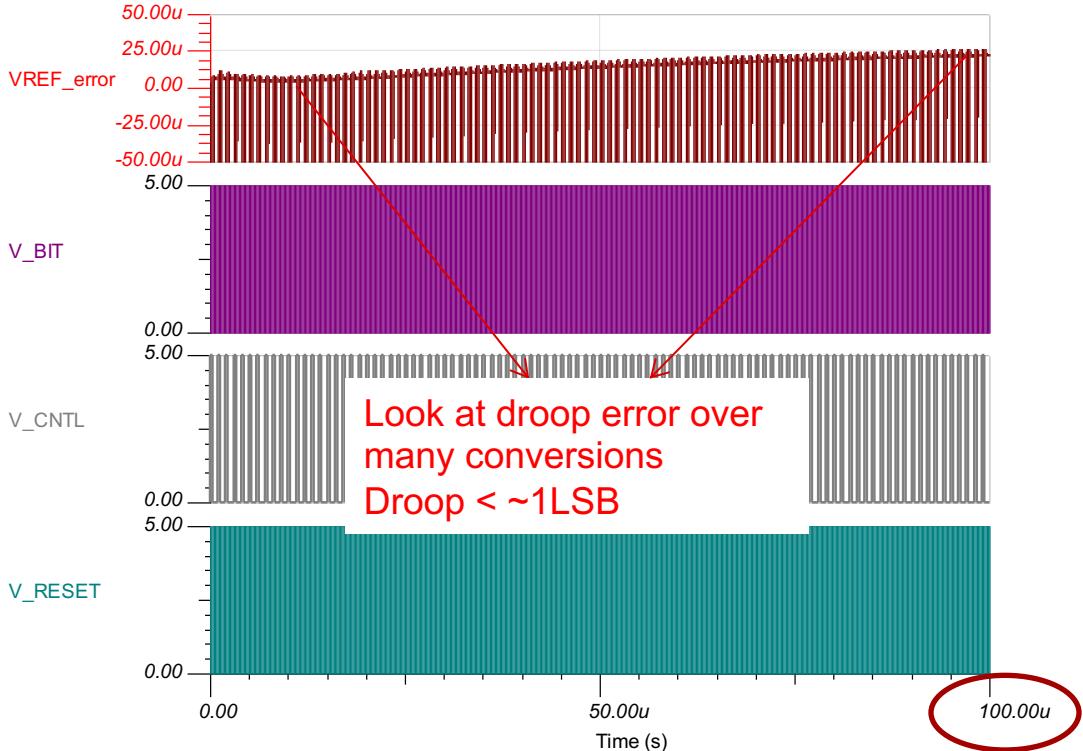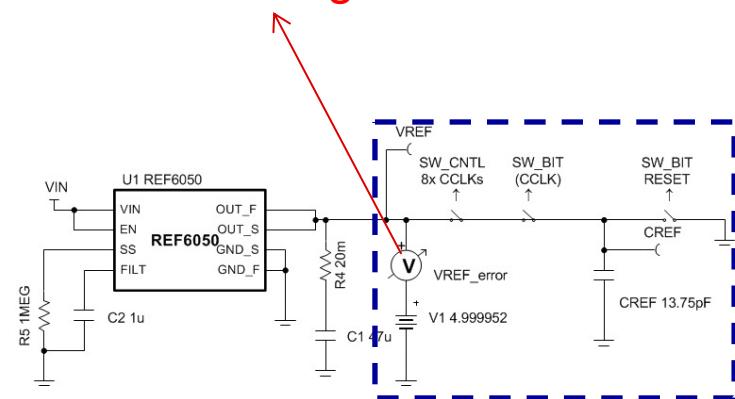

Key Result: Error Signal

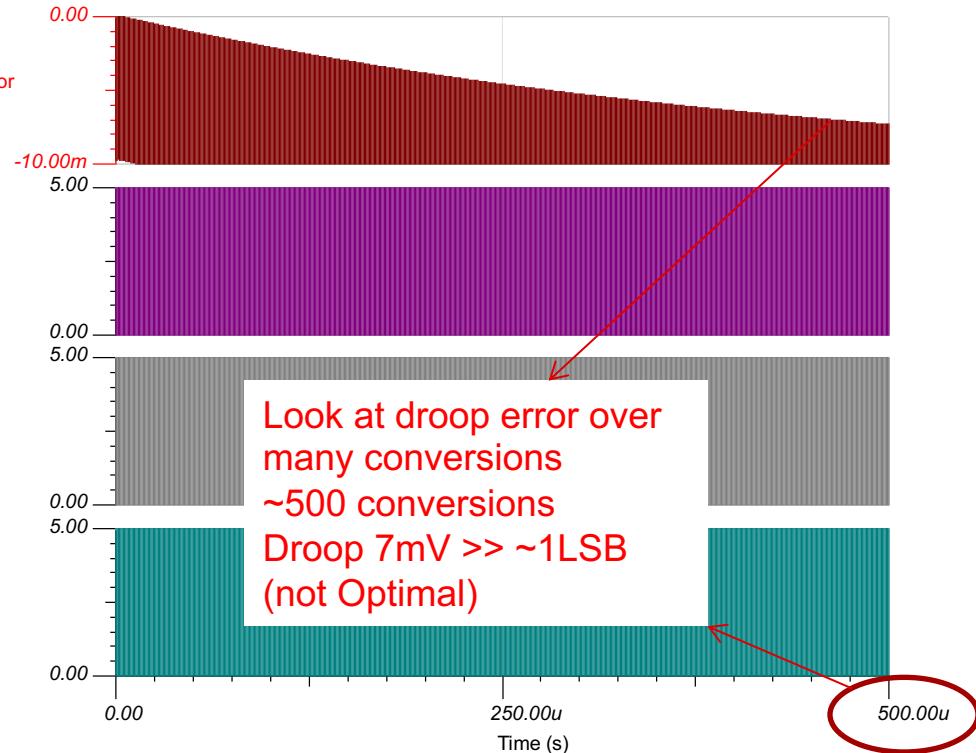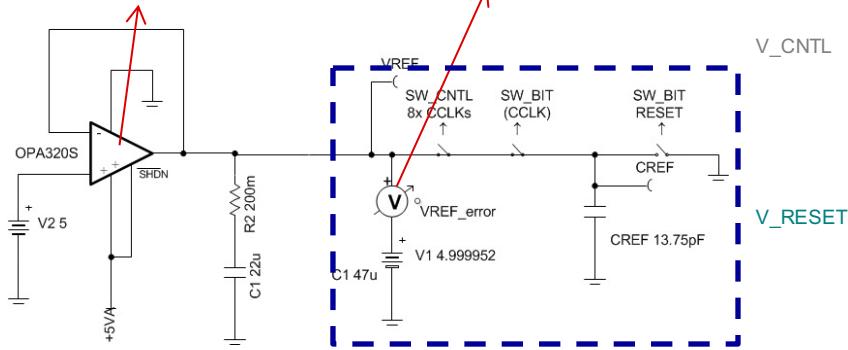Example with excessive droop

OPA320 Stable
driving load,
but unable to recover
at 1-MSPS.




Key Result: Average Current

Average Current per
Datasheet spec is $300\mu A$

Average Current per
simulation spec is $530\mu A$
Useful to compare sim vs datasheet

Simulation Current
Meter


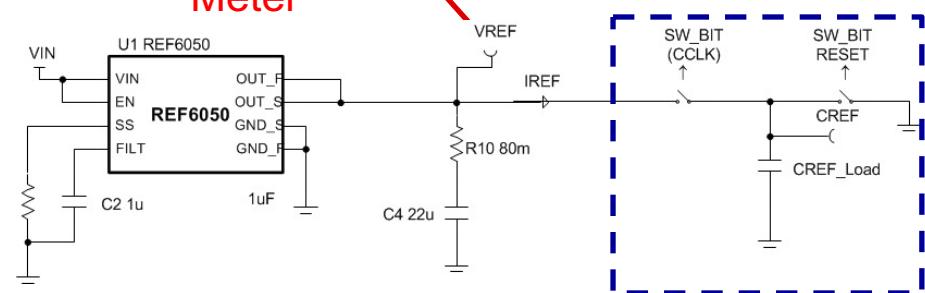


Key Result: Average Current

Average Current per
Datasheet spec is $300\mu\text{A}$

Average Current per
simulation spec is $530\mu\text{A}$



Useful to compare sim vs datasheet

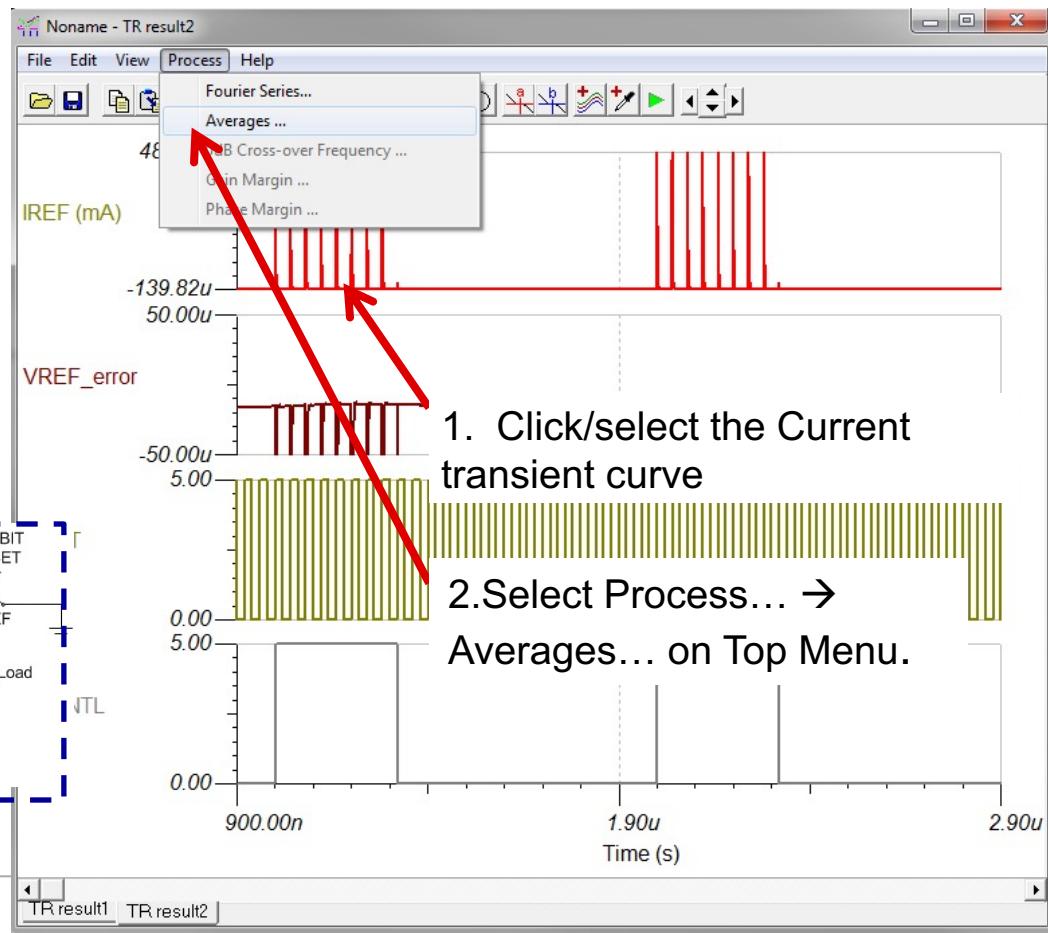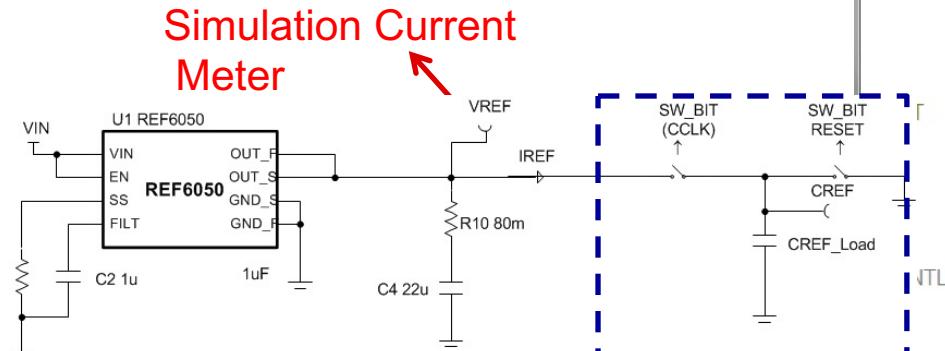

Key Result: Average Current

Average Current per
Datasheet spec is $300\mu A$

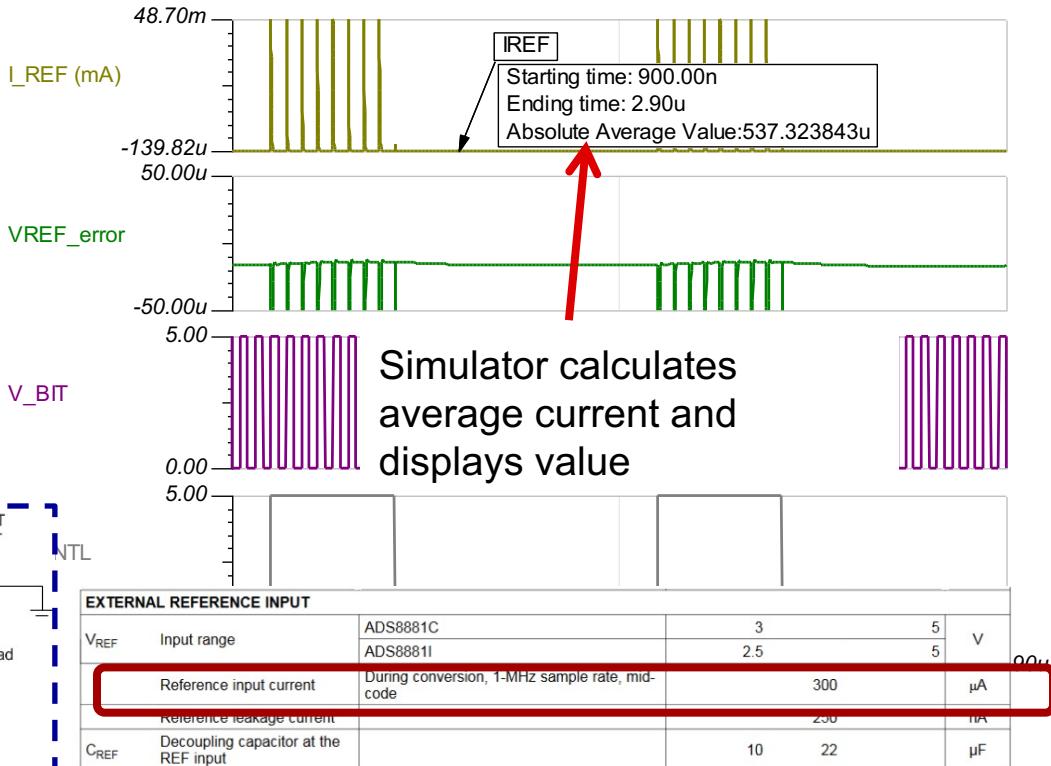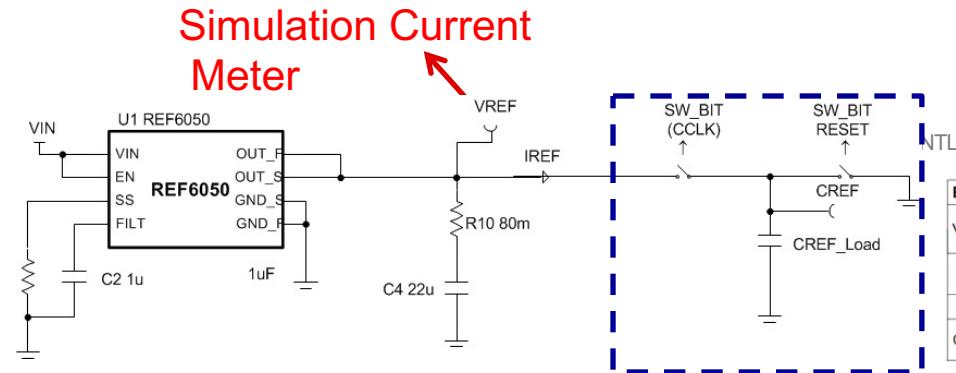Average Current per
simulation spec is $530\mu A$
Useful to compare sim vs datasheet



Agenda

Reference Performance Specifications:

- Initial Accuracy, Drift, Long Term Drift, Noise and Output Drive

Overview of SAR REF Drive Topologies:

- Reference standalone VS Buffered Reference

- SAR ADCs with Internal Reference Buffer

SAR REF Input Overview: The Capacitive DAC (CDAC)

Build TINA REF Input Model for a SAR:

- Discrete Charge Model

- TI Device Specific Model**

SAR REF Drive Circuit Design:

- Reference Bypass Capacitor


- Reference Buffer Stability and Compensation





REFIN TI Device Specific Model

- Device specific: model closer to device topology
- Uses variable weighted switching capacitor load
- Behavior may be more accurate and/or closer to real silicon, at the cost of slower simulations/circuit complexity

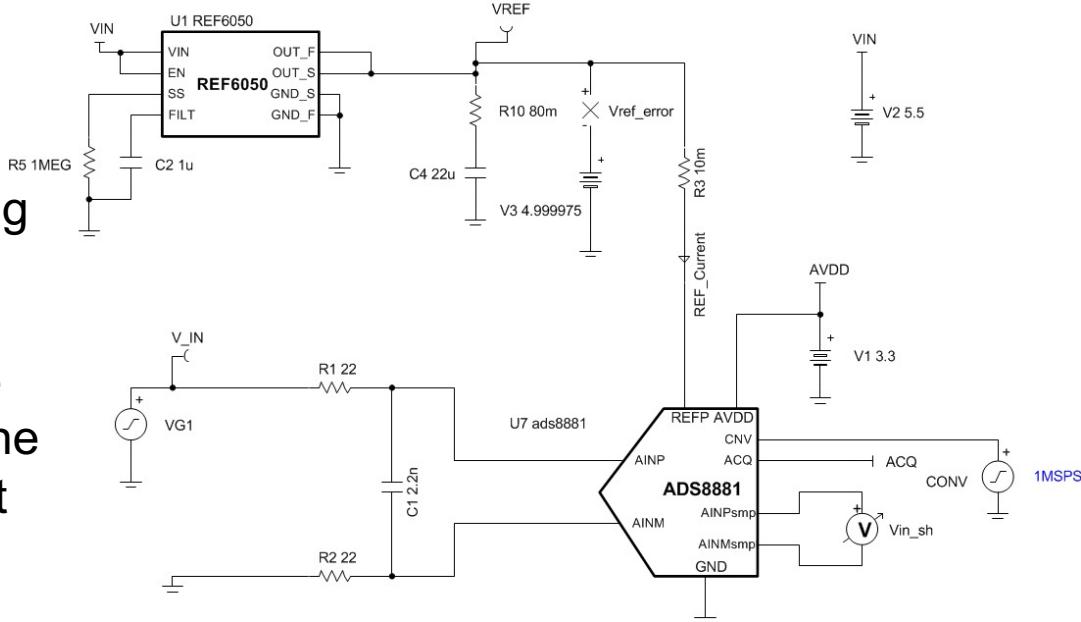REF6050 Reference Design: Settling Analysis



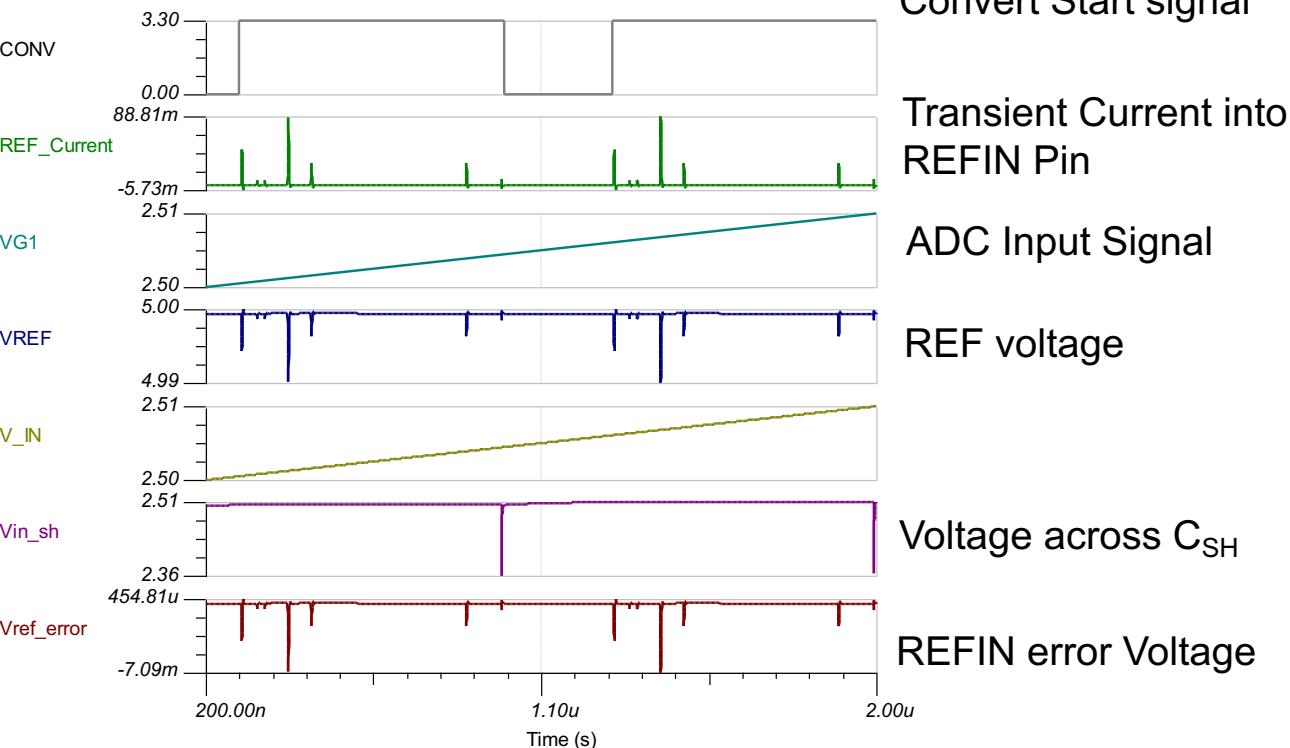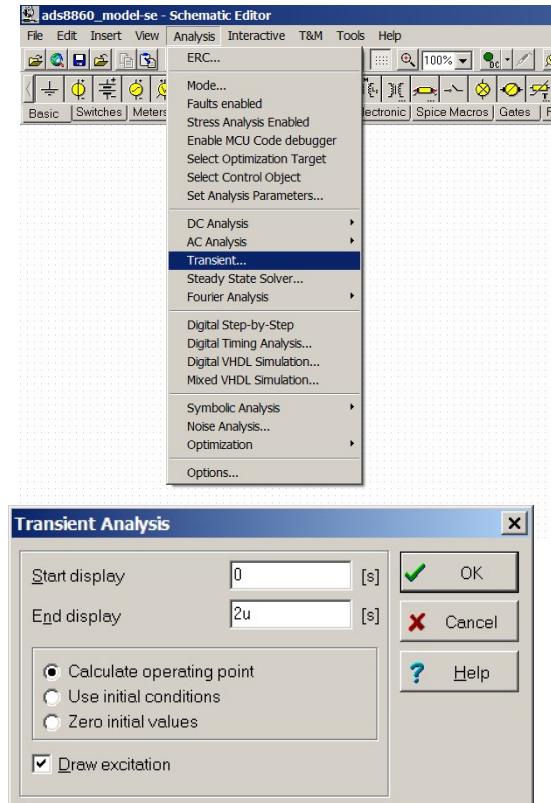REFIN TI Device Specific Model: transient results



Convert Start signal

Transient Current into
REFIN Pin

ADC Input Signal

REF voltage

Voltage across C_{SH}

REFIN error Voltage



Texas Instruments

Device Specific VS Discrete Charge Model

Discrete Charge REFIN model	Device Specific Model
Conservative approach to load: switching MSB load several times per conversion.	Binary Weighted or variable switching capacitive load, modeling specific device topology.
Offers faster simulation results, conservative approach	More accurate results, sometimes at the cost of circuit complexity and slower simulation.
Robust convergence/ fast simulations allows easy Reference drive circuit optimization	Tends to be more accurate, but slower. May have convergence issues on complex circuits. Can be used to verify final circuit.
Created from datasheet parameters	Provided by factory, not available on old devices



Thanks for your time!



TEXAS INSTRUMENTS



©Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com