




# Using fully differential amplifiers to optimize high speed signal chain interfaces

# Agenda


- **What is a fully differential amplifier (FDA)?**
- **Solving interface challenges using an FDA**
  - Overcoming challenges of balun
  - Level shifting using the FDA
  - Optimizing stability of FDA for low gain
  - Buffering a clock source using FDA
  - DAC buffering to drive single-ended load
- **Summary**
- **Q/A (15min)**
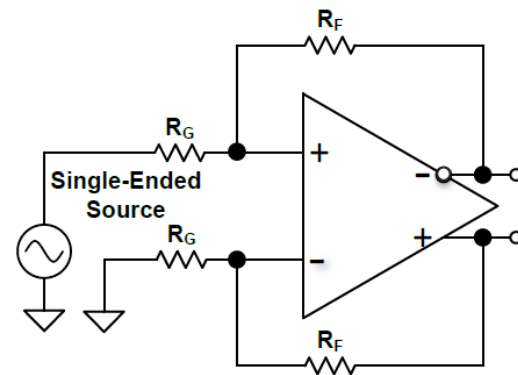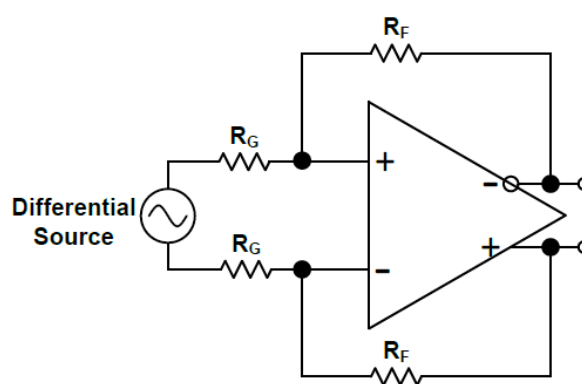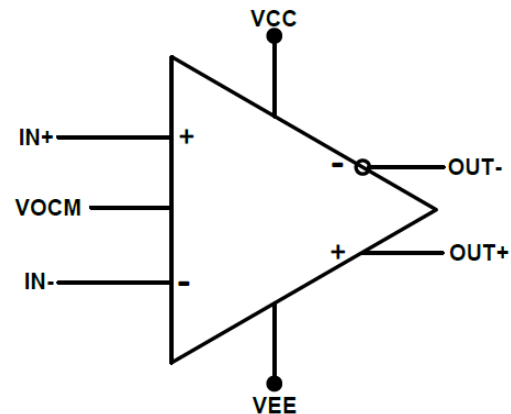
# What is a fully differential amplifier (FDA)?

- Processes the difference voltage between its two inputs converting differential input to differential output
- Converts single-ended input to differential output
- FDA's output common mode voltage can be controlled independently of the differential voltage via the V<sub>OCM</sub> pin



# Inside a typical FDA

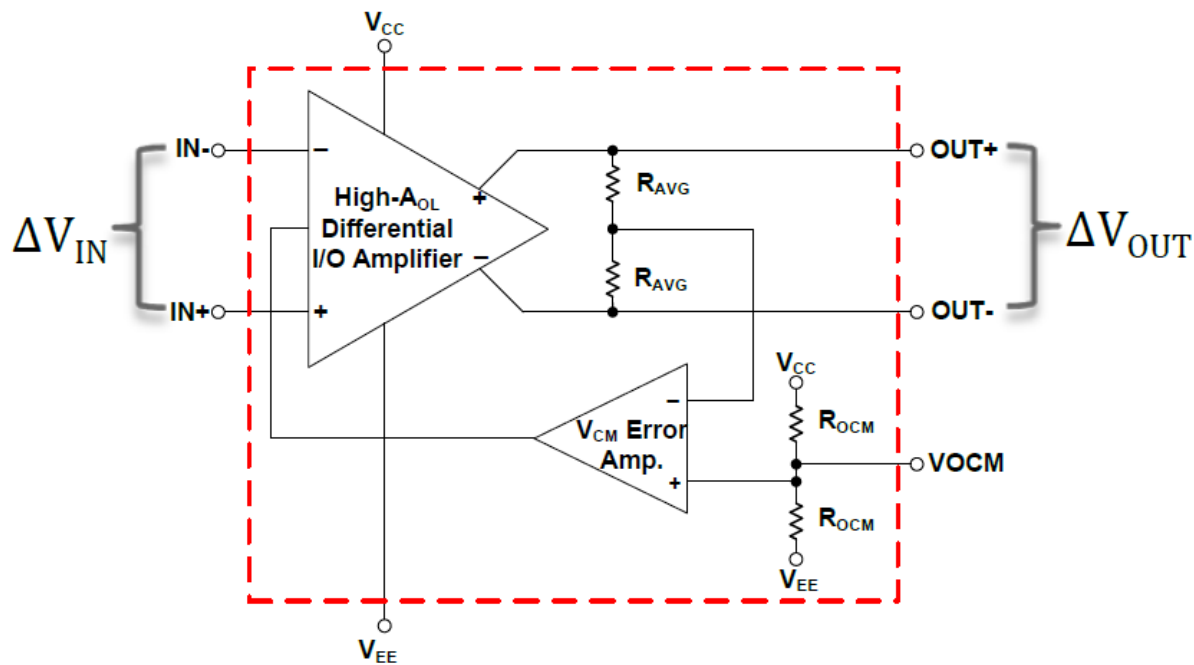

- **Integrated fully-differential high AOL amplifier**


**Integrated wide-bandwidth, common-mode feedback, error amplifier**

**Integrated resistors to detect the average output common-mode voltage**

**Integrated mid-supply, common mode set resistors**

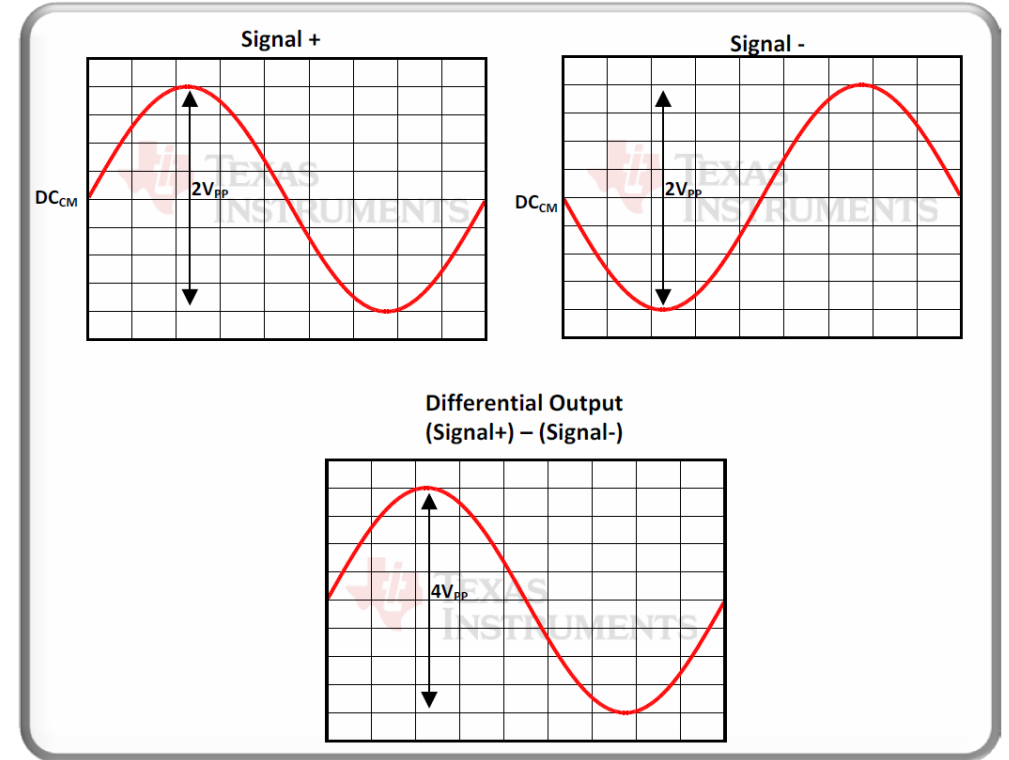
# Differential signaling benefits

- Higher output voltage swing for a given power rail
- Increased immunity to noise as any signal common to both inputs is cancelled
- Lower even-order harmonics with differential signaling


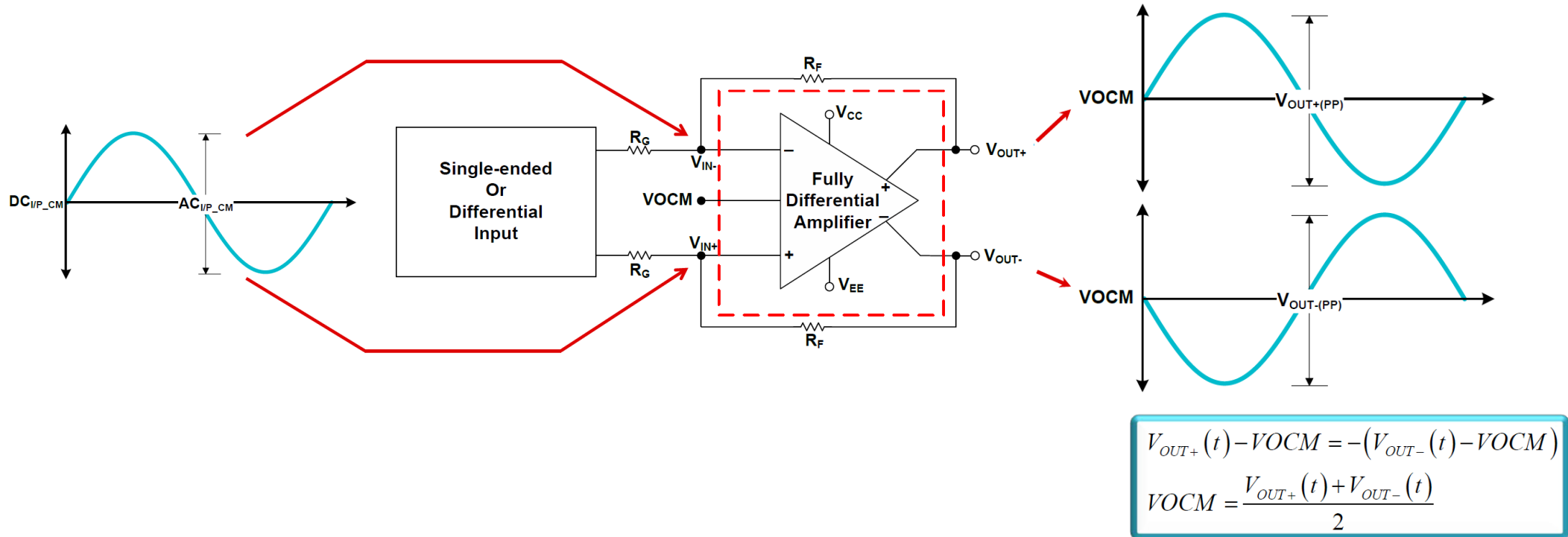
# Three rules governing FDA operation

- 1** The voltage at the input nodes to the amplifier track each other exactly (virtual short across inputs)
- 2** The two outputs are 180° out of phase
- 3** The two outputs have the same DC offset voltage equal to  $V_{OCM}$



# FDA common mode voltages

1

At the FDA Input, use KCL

$$\frac{(V_{ID\pm\_CM} - V_{IN\_CM})}{R_G} = \frac{(V_{IN\_CM} - V_{OUT\pm\_CM})}{R_F}$$
$$V_{IN\_CM} = 2.5V \cdot \frac{100\Omega}{(400\Omega + 100\Omega)} = 0.5V$$

2


At the FDA Output

$$V_{OUT+\_CM} = V_{OUT-\_CM} = V_{OCM} = 2.5V$$

$$V_{ID-} = -V_{ID+} = 0.2 V_{PP}$$

$$V_{ID\pm\_CM} = 0 V$$

$$V_{OCM} = 2.5 V$$


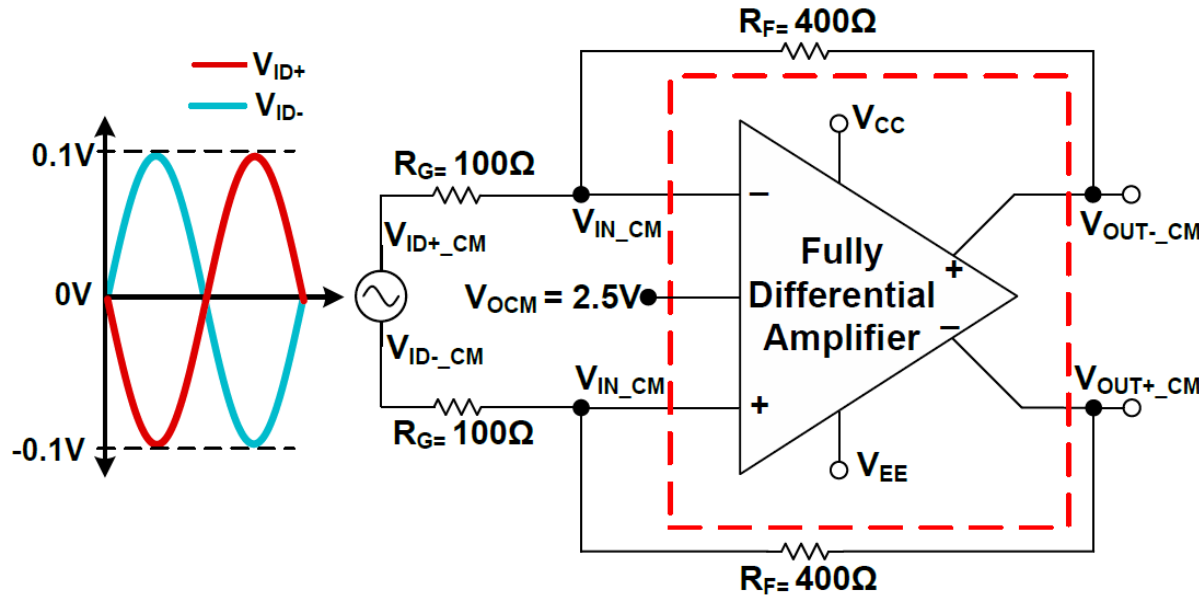


# FDA differential voltages

$$V_{ID-} = -V_{ID+} = 0.2 V_{PP}$$

$$V_{ID\pm\_CM} = 0 V$$

$$V_{OCM} = 2.5 V$$

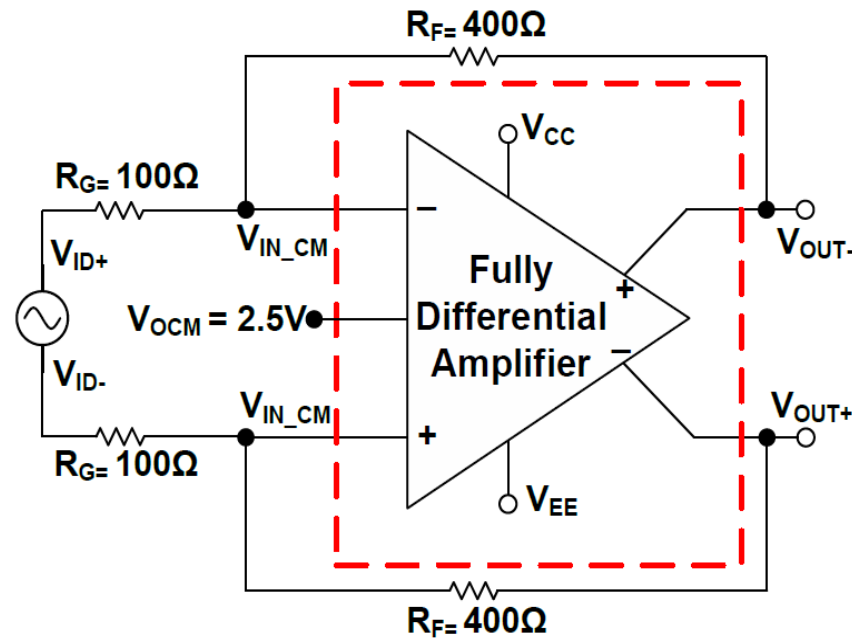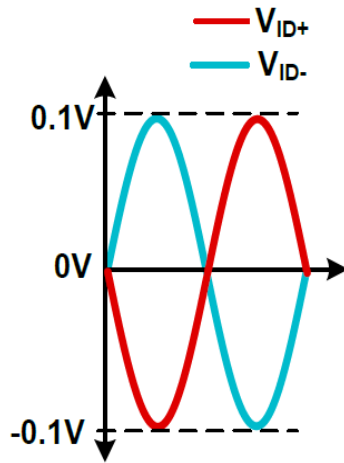

Taking each half of the FDA separately and applying KCL,

$$V_{IN\_CM} = \frac{V_{OUT-} + V_{ID+} \left( \frac{R_F}{R_G} \right)}{\left( 1 + \frac{R_F}{R_G} \right)}, \text{ and} \quad 3$$

$$V_{IN\_CM} = \frac{V_{OUT+} + V_{ID-} \left( \frac{R_F}{R_G} \right)}{\left( 1 + \frac{R_F}{R_G} \right)} \quad 4$$


Equating (1) & (2)

$$(V_{OUT-} - V_{OUT+}) = - \left( \frac{R_F}{R_G} \right) \cdot (V_{ID+} - V_{ID-}) \quad 5$$

$$\frac{\Delta V_{OUT}}{\Delta V_{ID}} = - \left( \frac{R_F}{R_G} \right) = G_V \quad 6$$




# FDA output signal

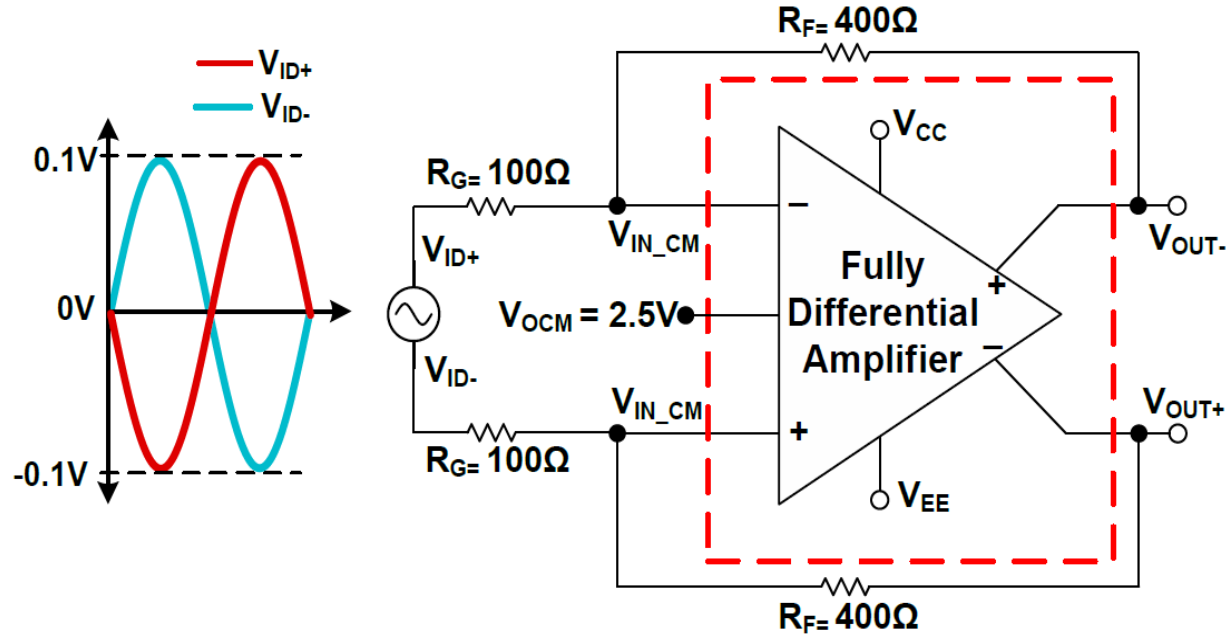

Differential  $V_{OUT}$ ,

$$V_{OUT-} = -V_{OUT+} = 4 \times 0.2V_{PP} = 0.8V_{PP}$$

7

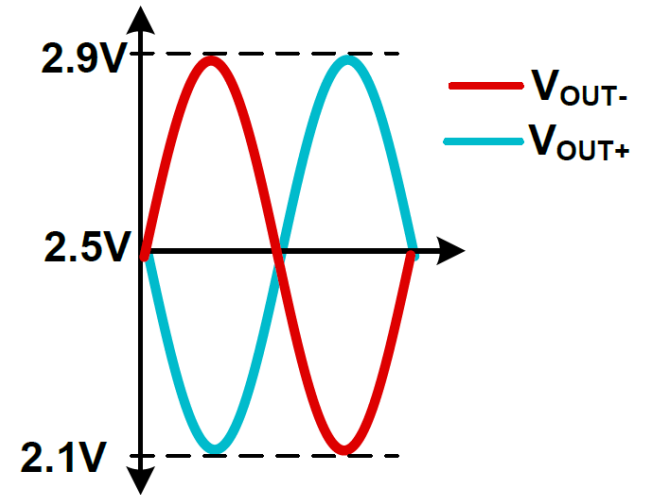


(Differential + CM)  $V_{OUT}$ ,

$$V_{OUT-} = 2.5V \pm 0.8V, \text{ and, } V_{OUT+} = 2.5V \mp 0.8V$$

8
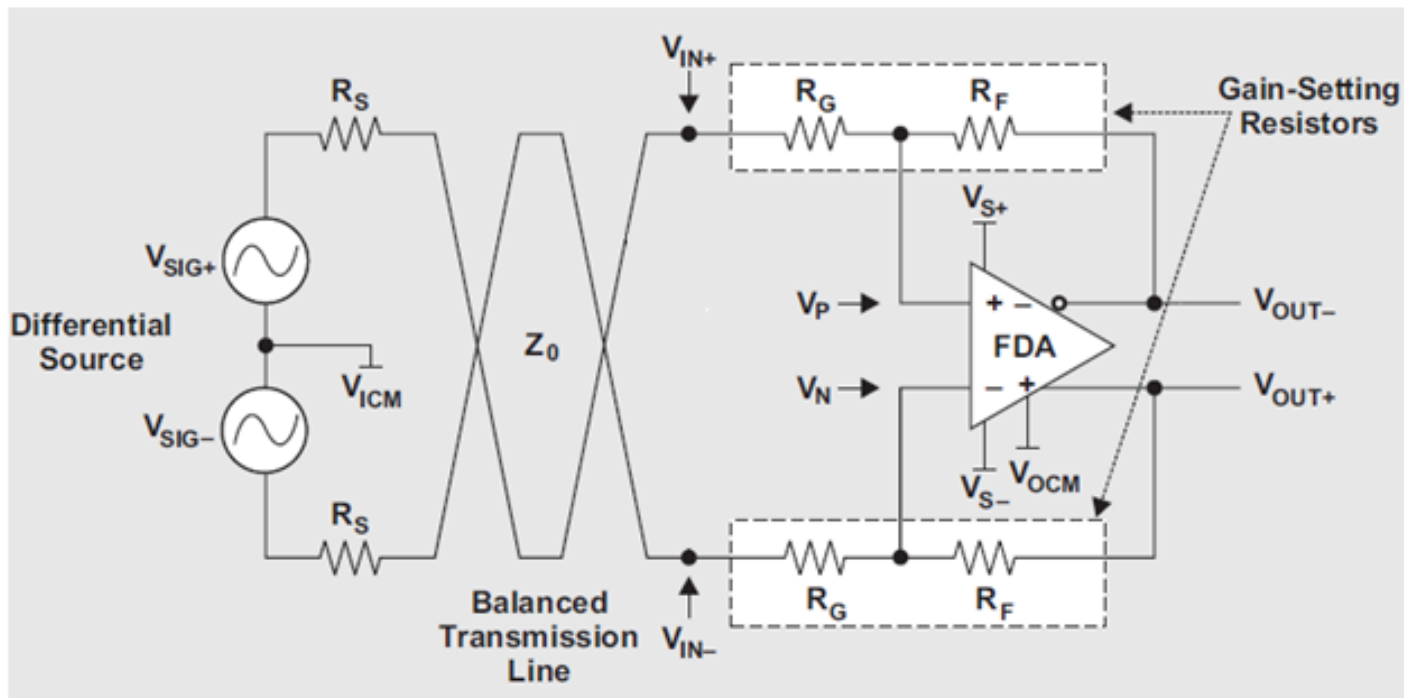
# Impedance matching differential input of FDA





- Signal gain of amplifier,  $G_V$ , is conventionally defined from  $V_{IN}$  signal at  $R_G$  resistor to  $V_{OUT}$  signal of FDA
- $G_V$  is independent of source and load

**Example 1: Impedance match amplifier to  $R_S = 50$  ohms with  $G_V = 1$  V/V**

**$R_G = 50$  ohms,  $R_F = 50$  ohms ( $R_F$  is too low!!)**
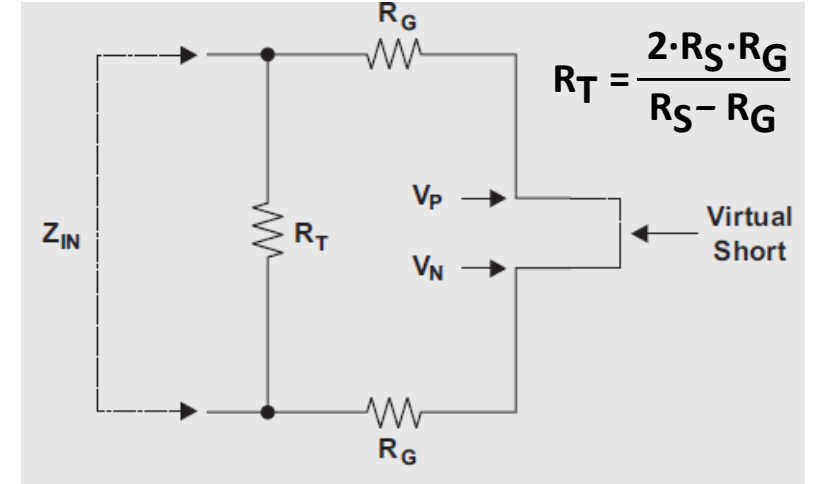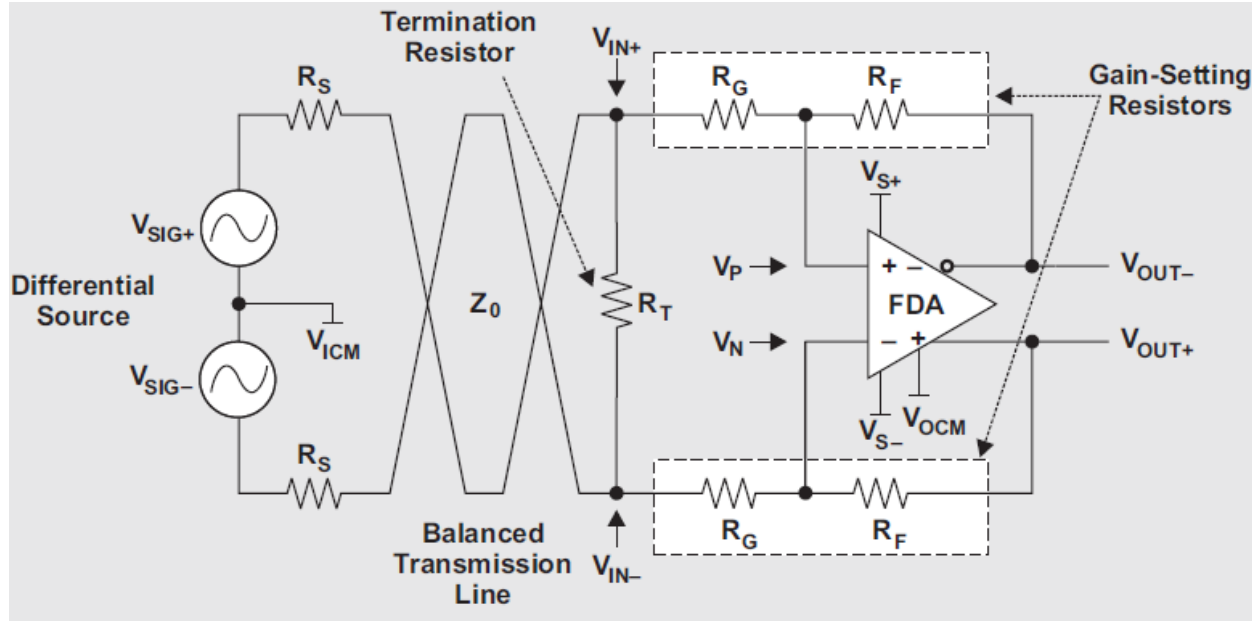
# Impedance matching differential input of FDA

- $R_T$  is used when  $R_G$  must be set greater than the input impedance,  $R_S$ , in order to achieve the desired gain target




1

**Example2:** Impedance match amp to  $R_S = 50$  ohms with  $G_V = 1V/V$

- $R_G = 200$  ohms,  $R_F = 200$  ohms,  $R_T = 133$  ohms
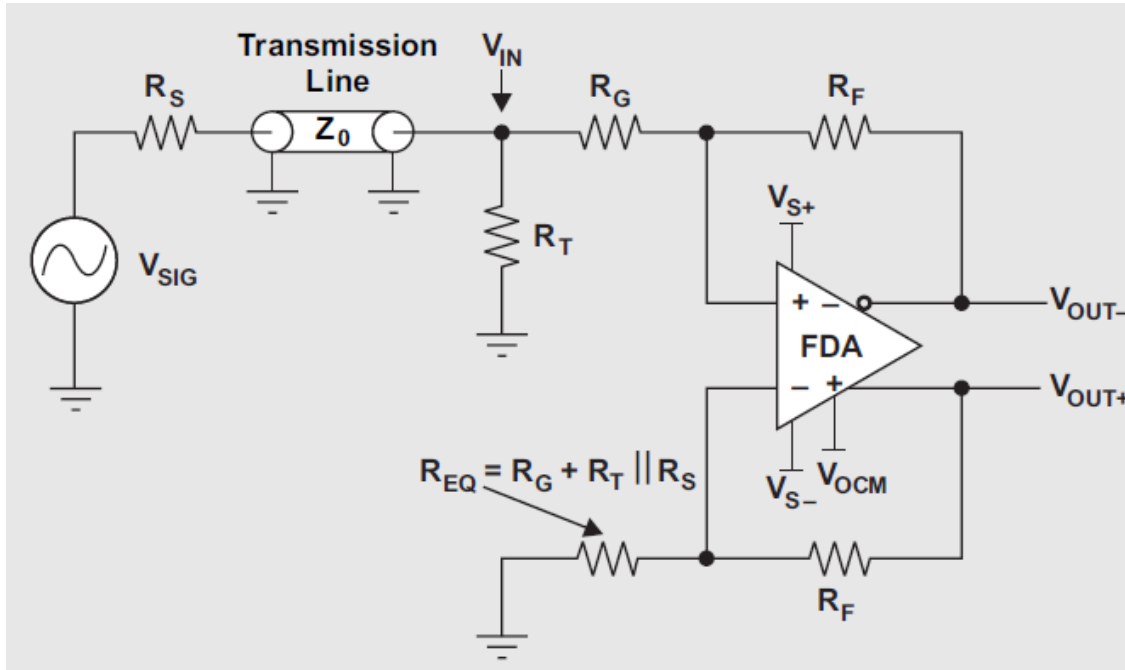
# Impedance matching single-ended input of FDA



- With only one side driven, input pins of amplifier are no longer a fixed DC voltage - there is a AC component
- Common mode compliance on the input nodes to amplifier becomes more of a concern as inputs move with AC signal


LMH5401-SP

7.5 Electrical Characteristics:  $V_S = 5\text{ V}$

PARAMETER	TEST CONDITIONS	SUBGROUP <sup>(3)</sup>	MIN	TYP	MAX	UNIT
$V_{ICH}$	Input common-mode high voltage	[1, 2, 3]	$(V_{S+}) - 1.41$	$(V_{S+}) - 1.2$		V
$V_{ICL}$	Input common-mode low voltage	[1, 2, 3]		$V_{S-}$	$(V_{S-}) + 0.41$	V



# FDA: Generalized transfer function

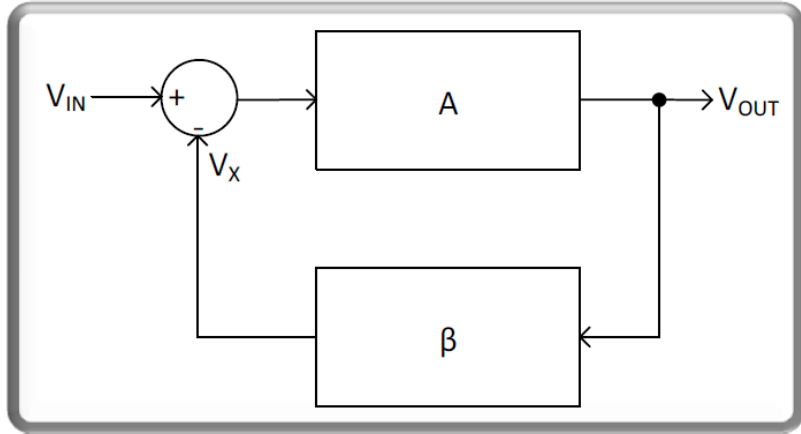

$A \Rightarrow$  Forward open-loop gain of system

$\beta \Rightarrow$  Reverse transfer function of feedback path

$V_X \Rightarrow$  Fraction of system output fed back to input

$$V_{OUT} = A(V_{IN} - V_X) \quad \text{1}$$

$$V_X = \beta \cdot V_{OUT} \quad \text{2}$$

$$V_{OUT} = A(V_{IN} - \beta \cdot V_{OUT}) \quad \text{3}$$

$$V_{OUT}(1 + A \cdot \beta) = V_{IN} \quad \text{4}$$

$$\text{Gain} = \frac{V_{OUT}}{V_{IN}} = \frac{A}{(1 + A \cdot \beta)} \quad \text{5}$$


# FDA: Generalized transfer function

$$\text{Signal Gain} = -\frac{R_F}{R_G} \quad \text{6}$$

6

$$\beta = R_G / (R_F + R_G) \quad \text{7}$$

7

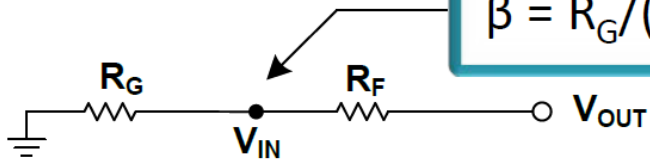


$$\text{Noise Gain} = \frac{1}{\text{Feedback Factor}}$$

$$\text{Noise Gain} = \frac{1}{\beta} = 1 + \frac{R_F}{R_G} \quad \text{8}$$

8

Signal Gain  $\neq$  Noise Gain

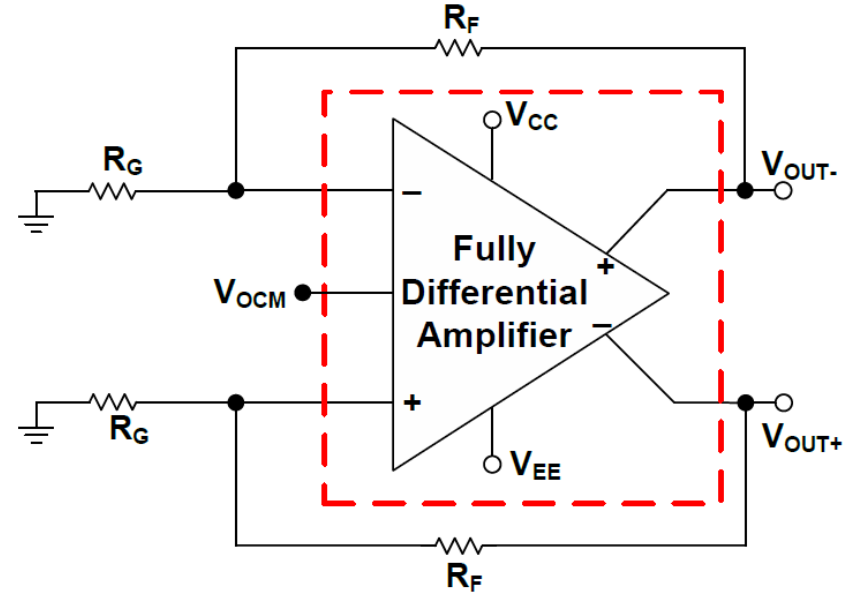

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}, \text{ As } A_{OL} \rightarrow \infty, \quad A_{CL} = \frac{1}{\beta} \quad \text{9}$$

9

$A_{OL}\beta \rightarrow$  Loop Gain.


Frequency @ which  $|A_{OL}\beta| = 1$ , is the ( $A_{CL}$ ) -3dB BW

# FDA solving signal chain challenges


- **Solving interface challenges using an FDA**
  - Overcoming challenges of balun
  - DC level shifting
  - Optimizing stability of FDA for low gain
  - Clock buffer using FDA
  - DAC output buffering

# FDA replacing balun to drive high speed ADC

## Conventional Balun Approach

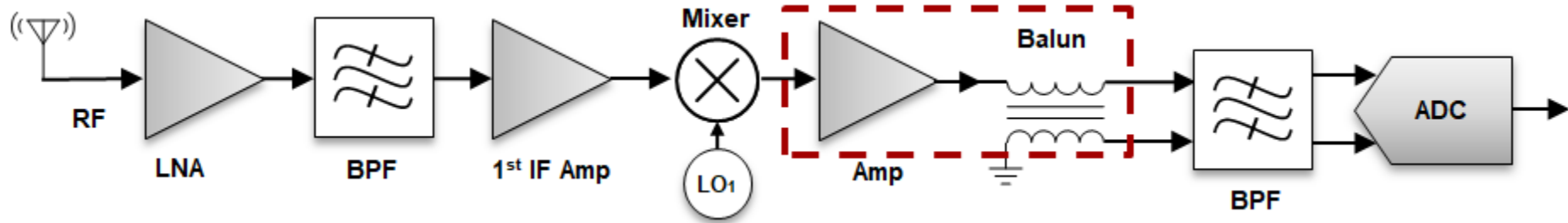

## FDA Approach

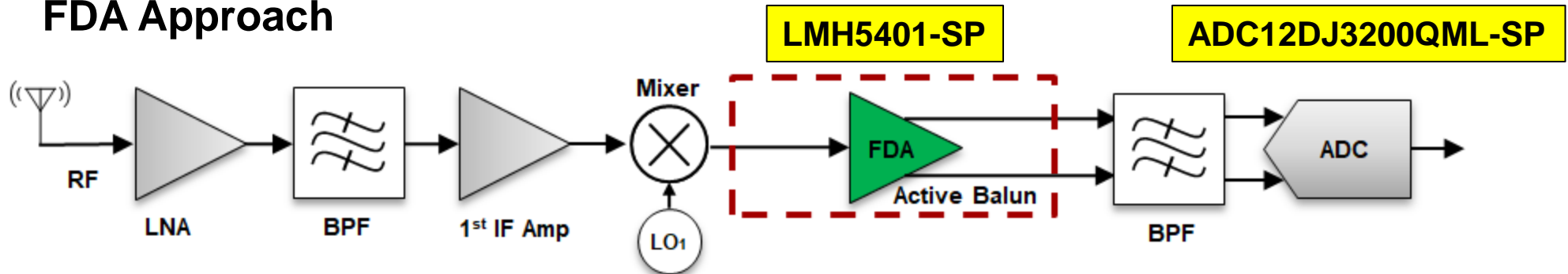



# FDA compared to balun

Parameter	Balun	FDA
Size	<b>Larger</b> size (66 mm <sup>2</sup> )	<b>Smaller</b> size (LMH5401-SP: 33mm <sup>2</sup> )
DC coupled	<b>Not suitable</b> for DC coupled application	<b>Suitable</b> for DC coupled applications
Frequency response	<b>Not suitable</b> for wide bandwidth: <b>Large</b> insertion loss and <b>varies</b> with frequency	<b>Suitable</b> for wide bandwidth: <b>Minimal</b> insertion loss and almost <b>constant</b> across frequency
Power gain	<b>No</b> power gain - Impedance matching and voltage/current gain are <b>dependent</b>	<b>Supports</b> power gain - Impedance matching and gain are <b>independent</b>
Buffering	<b>No</b> buffering - Requirement on <b>previous stage to drive</b> filter and ADC input load  - <b>No reverse isolation</b>	<b>Buffered</b> - <b>Previous stage is isolated</b> from filter and ADC input load  - <b>Reverse isolation:</b> Avoids ADC switching components going back to previous stages (ex: antenna)
Distortion	<b>Worse</b> distortion due to phase unbalance	<b>Better</b> distortion with wideband amplifiers
Noise	<b>Less noise</b> (dependent on insertion loss)	<b>Adds noise</b>
Temperature range	<b>Limited</b> temp range (ex: -20 to 85C) <b>Large gain variation</b> across temperature	<b>Wide</b> temp range (ex: -55°C to +125°C for LMH5401-SP) <b>Small gain variation</b> across temperature
Reliability	<b>Less reliable</b> due to mechanical construction (ex: vibration during flight)	<b>Reliable</b> due to monolithic implementation

# FDA excel calculator tool

<https://e2e.ti.com/support/amplifiers/f/14/t/771636>


	A	B	C	D	E	F	G
1	<b>LMH5401-SP SE-DIFF CALCULATOR</b>						
2	Given $G_v$ , $R_s$ , and $R_f$ , solve for $R_f^*$ , $R_t$ , $R_{g1}$ , and $R_{g2}$ such that input impedance is matched in single-ended input to differential output configuration.						
3							
4							
5							
6							
7	<b>INPUT Parameter</b>	<b>Value</b>	<b>Units</b>				
8	Enter Target Voltage Gain, $G_v$ (at AMPOUT)	7.100	V/V				
9	Enter Source Impedance, $R_s$	50	ohms				
10	Enter Target Feedback Resistance, $R_f$	225	ohms				
11							
12							
13	<b>CALCULATED Solution</b>	<b>Value</b>	<b>Units</b>				
14	Voltage Gain, $G_v$ (V/V)	7.114	V/V				
15	Voltage Gain, $G_v$ (dB)	17.043	dB				
16	Realizable $R_f^*$	200.0	ohms				
17	Realizable $R_t$	1150.0	ohms				
18	Realizable $R_{g1}$	12.7	ohms				
19	Realizable $R_{g2}$	60.4	ohms				
20	Zin (looking into $R_t$ )	49.8	ohms				
21	Noise Gain, $G_n$	4.725	V/V				

Example Circuit showing naming Convention

**LMH5401-SP Default EVM Config: 7.1V/V**

- Calculator solves for voltage gain at AMPOUT node, node internal to device inside series 10 ohms on each output. Aligns with datasheet specifications.
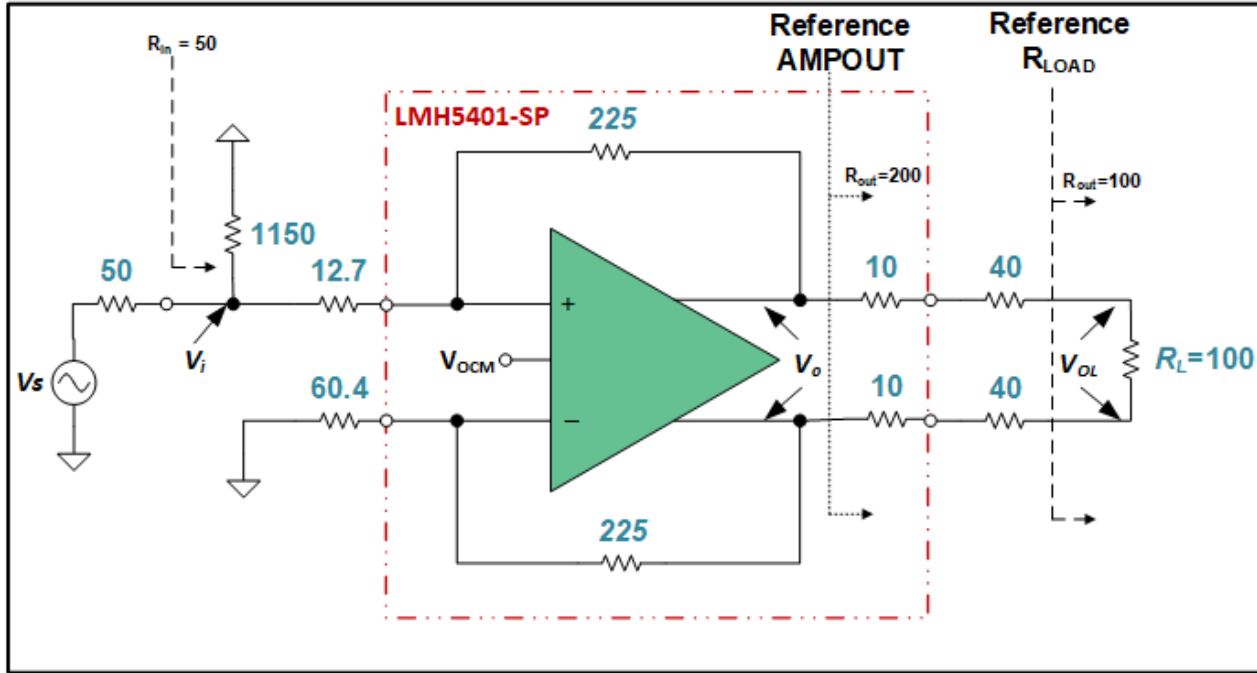
# Power gain, voltage gain and reference plane



## Reference AMPOUT

$$G_V = V_o/V_i = 7.1 \text{ V/V} = 17\text{dB} \quad \text{1}$$


$$G_P = \frac{P_o}{P_i} = G_V + 10 \log\left(\frac{R_{in}}{R_{out}}\right) = 11\text{dB} \quad \text{2}$$

## Reference R\_LOAD

$$G_V = \frac{V_{OL}}{V_i} = \frac{V_o}{2 * V_i} = 3.55 \text{ V/V} = 11\text{dB} \quad \text{3}$$

$$G_P = \frac{P_{OL}}{P_i} = G_V + 10 \log\left(\frac{R_{in}}{R_{LOAD}}\right) = 8\text{dB} \quad \text{4}$$
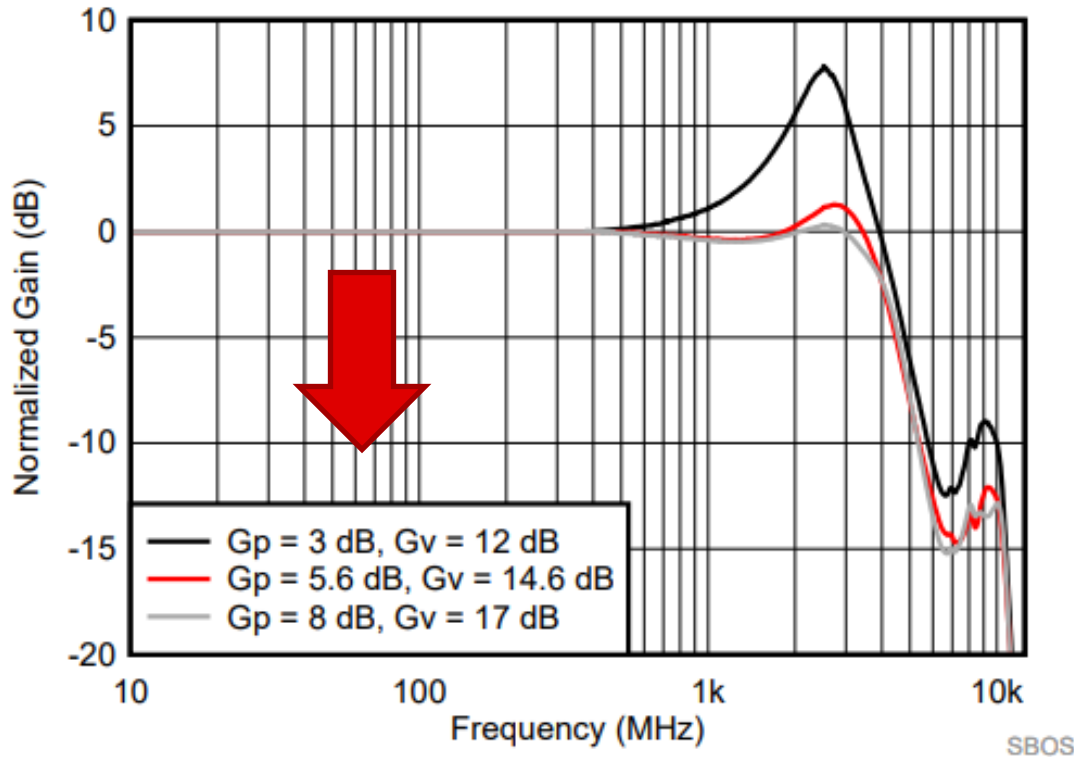
# Power gain, voltage gain and reference plane




SE-DE Small Signal Frequency Response vs Gain


- Frequency response normalized to 0dB
- Both power gain,  $G_p$ , and voltage gain,  $G_v$  shown in legend
- Power gain assumes matched input and output impedance.


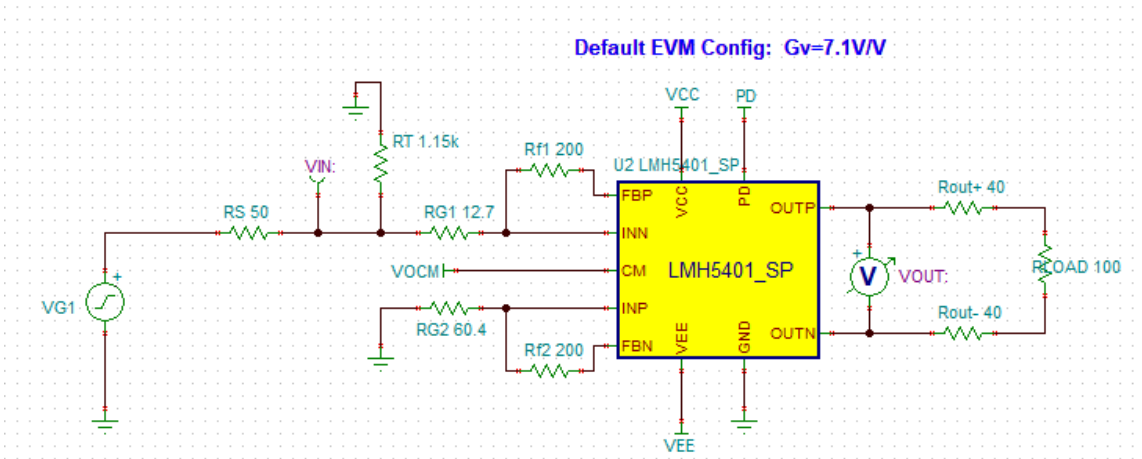
# TINA simulation single-ended in to differential out




19	Realizable $R_{gz}$	60.4	ohms
20	Zin (looking into $R_t$ )	49.8	ohms
21	Noise Gain, $G_N$	4.725	V/V

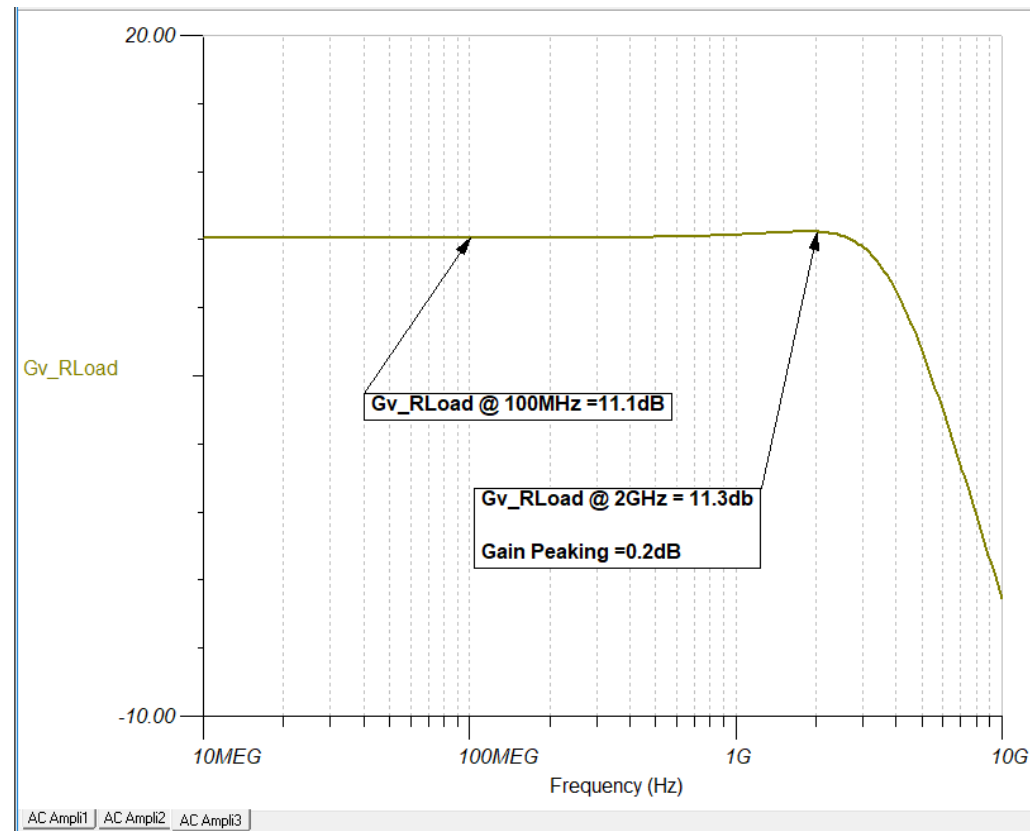

# Low gain single-ended to differential input

	A	B	C	D
1	<b>LMH5401-SP SE-DIFF CALCULATOR</b>			
2	Given $G_v$ , $R_s$ , and $R_f$ , solve for $R_t$ , $R_{g1}$ , and $R_{g2}$ such that input impedance is matched in single-ended input to differential output configuration.			
3				
4				
5				
6				
7	<b>INPUT Parameter</b>	<b>Value</b>	<b>Units</b>	
8	Enter Target Voltage Gain, $G_v$ (at AMPOUT)	2.810	V/V	
9	Enter Source Impedance, $R_s$	50	ohms	
10	Enter Target Feedback Resistance, $R_f$	225	ohms	
11				
12				
13	<b>CALCULATED Solution</b>	<b>Value</b>	<b>Units</b>	
14	Voltage Gain, $G_v$ (V/V)	2.793	V/V	
15	Voltage Gain, $G_v$ (dB)	8.922	dB	
16	Realizable $R_f^*$	200.0	ohms	
17	Realizable $R_t$	84.5	ohms	
18	Realizable $R_{g1}$	69.8	ohms	
19	Realizable $R_{g2}$	100.0	ohms	
20	$Z_{in}$ (looking into $R_t$ )	50.0	ohms	
21	Noise Gain, $G_N$	3.250	V/V	

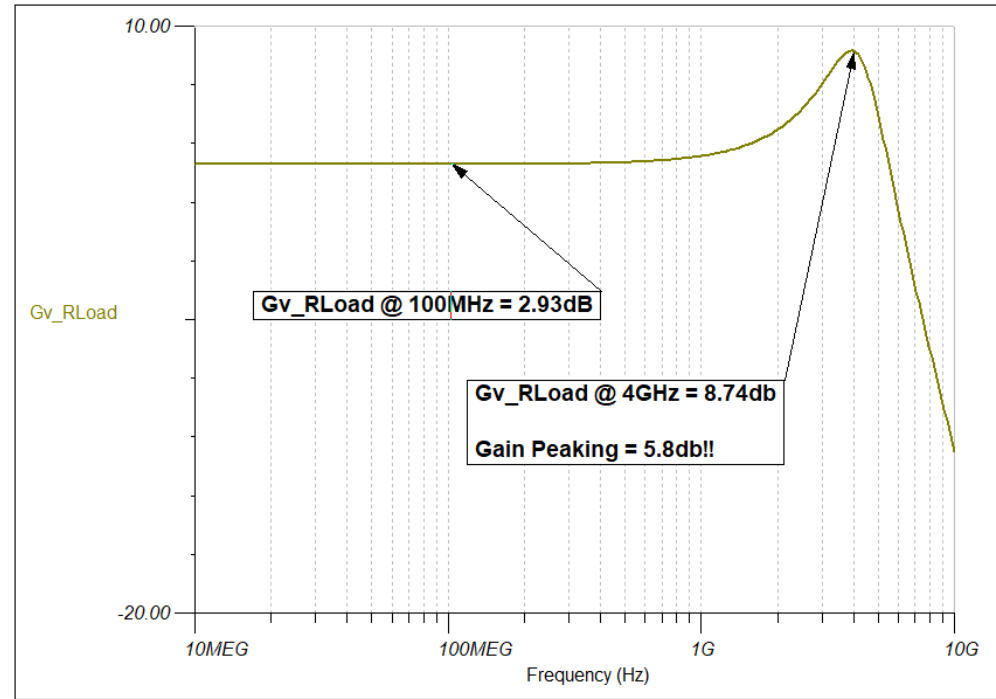- Design for 0dB power gain from source to load. ( $G_{v\_load} = 3$  dB,  $G_{v\_AMPOUT} = 2.8$  V/V = 9dB)



# FDA Stability

## Barkhausen Stability Criterion

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta}, \quad \text{1}$$



When  $|A_{OL}\beta| = 1$ , and phase shift around the loop is  $180^\circ$ ,

$$A_{CL} = \frac{A_{OL}}{1-1} = \infty \quad \text{2}$$

the denominator is unbounded and the system is unstable.


$$\text{Loop Gain} = A_{OL}\beta = \frac{A_{OL}}{\left(\frac{1}{\beta}\right)} = \left( (A_{OL}) - \left(\frac{1}{\beta}\right) \right)_{dB} \quad \text{3}$$

$$\text{Loop Gain crossover occurs when } |A_{OL}\beta| = 1, \Rightarrow |A_{OL}| = \left|\frac{1}{\beta}\right| \quad \text{4}$$

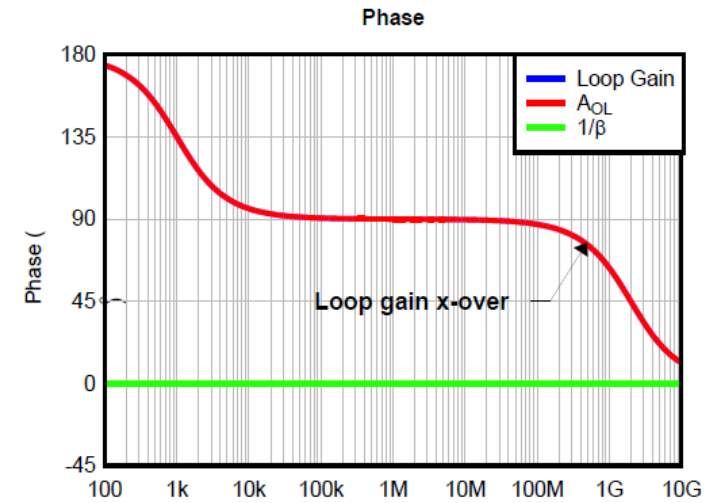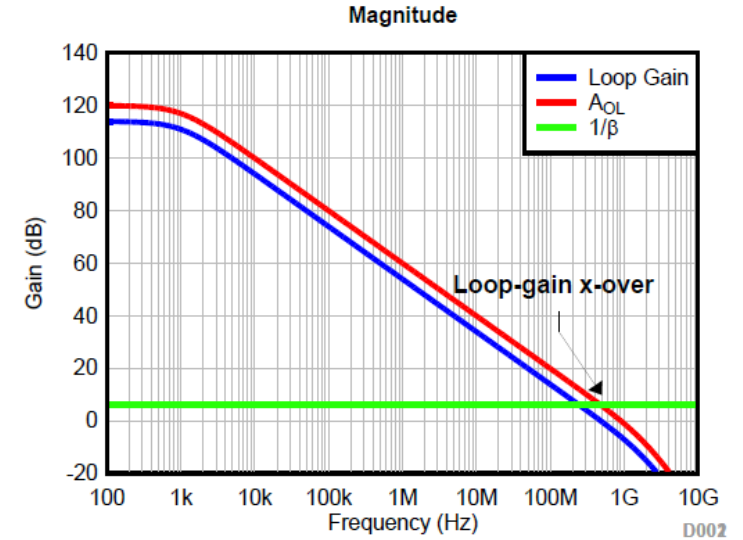


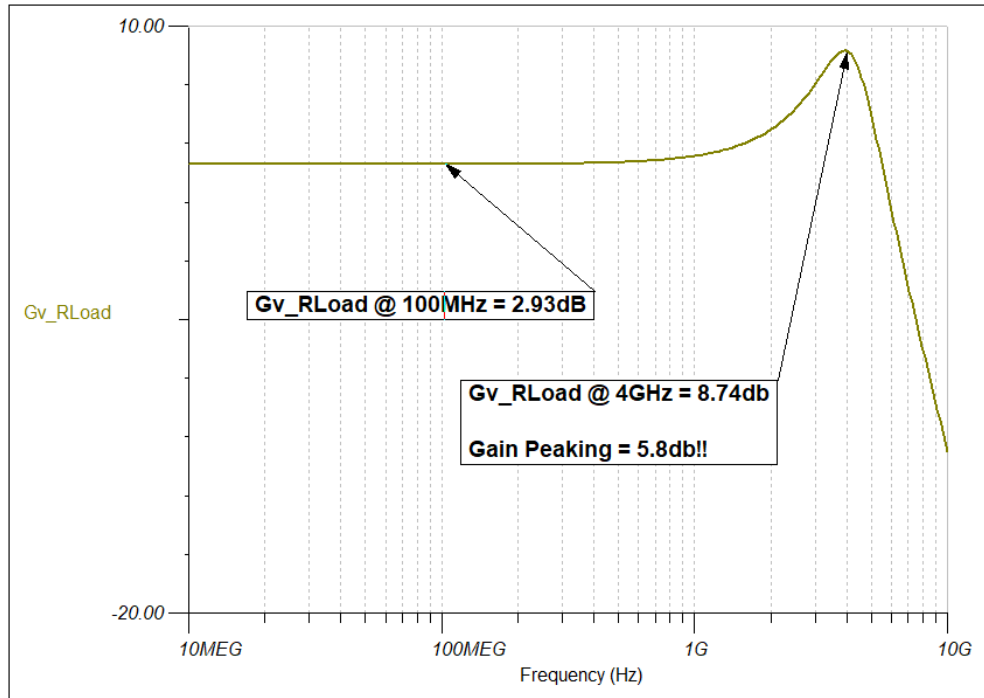
# Low gain single-ended to differential input





- Design Targets:
  - $G_p = 0\text{dB}$
  - $Gv\_load = 3\text{ dB}$
  - $Gv\_AMPOUT = 9.0\text{ dB}$
  - $Gv\_AMPOUT = 2.8\text{ V/V}$
- Simulated Results:
  - $G_p = -0.07\text{dB}$
  - $Gv\_load = 2.93\text{ dB}$
  - $Gv\_AMPOUT = 8.3\text{dB}$
  - $Gv\_AMPOUT = 2.6\text{ V/V}$
  - **AC Peaking = 5.8 dB**

# Noise gain compensation for low signal gains

72	Noise Gain, $G_N$	3.250	V/V	
73				
74				
75	Target Noise Gain, $G_N$	4.725	V/V	<=
76	Rcomp_calculated	305.085	ohms	301
77	Rcomp_actual (closest 1% value)	309	ohms	309
78				

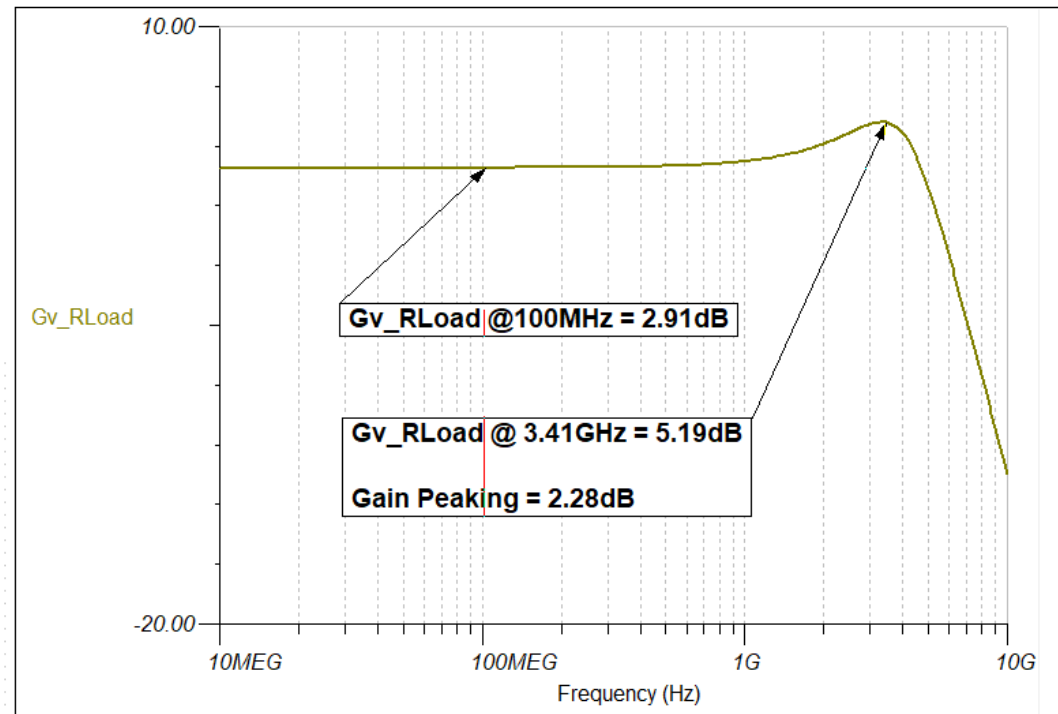
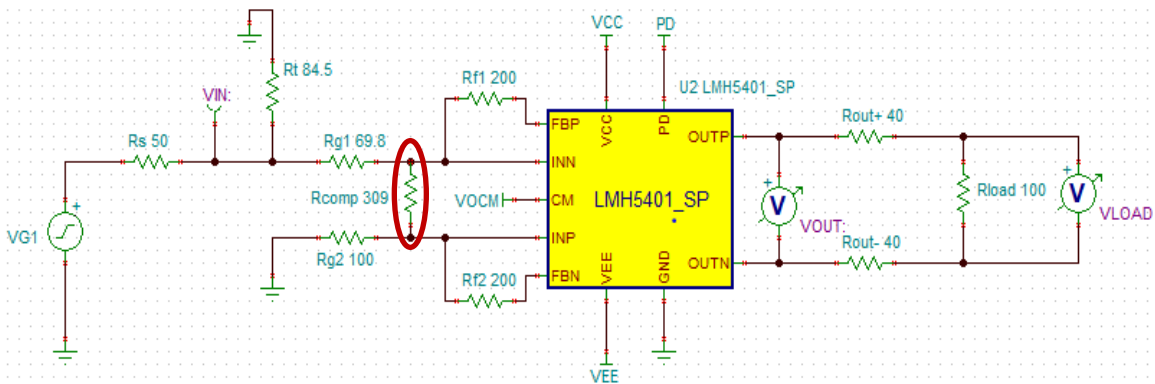
$$G_N = 1 + \frac{R_f}{R_{g2} \parallel \frac{R_{comp}}{2}}$$




# Noise gain compensation for low signal gains

72	Noise Gain, $G_N$	3.250	V/V	
73				
74				
75	Target Noise Gain, $G_N$	4.725	V/V	<=
76	Rcomp_calculated	305.085	ohms	301
77	Rcomp_actual (closest 1% value)	309	ohms	309
78				
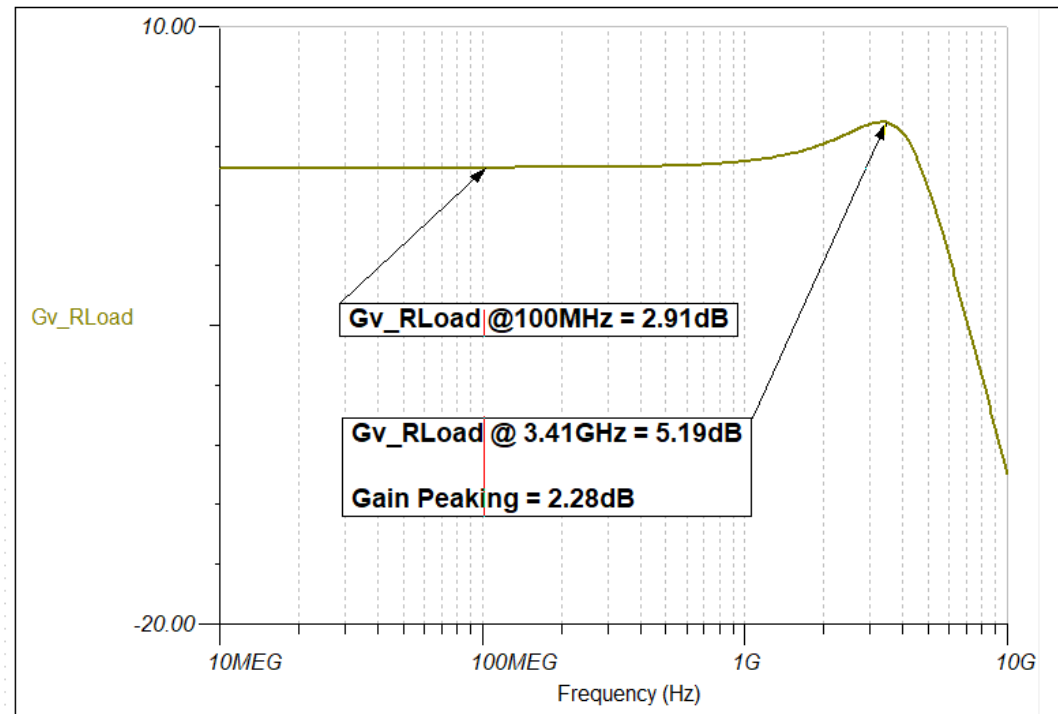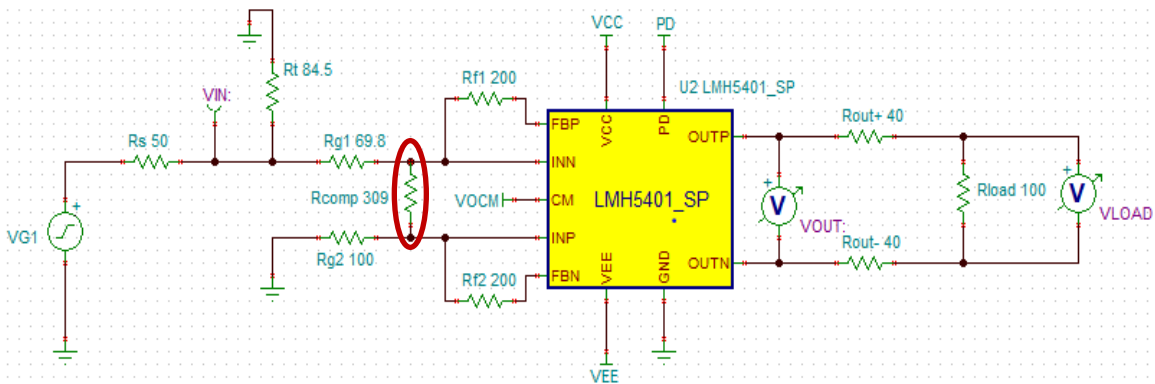
$$G_N = 1 + \frac{R_f}{R_{g2} \parallel \frac{R_{comp}}{2}}$$




# Noise shaping for improved stability

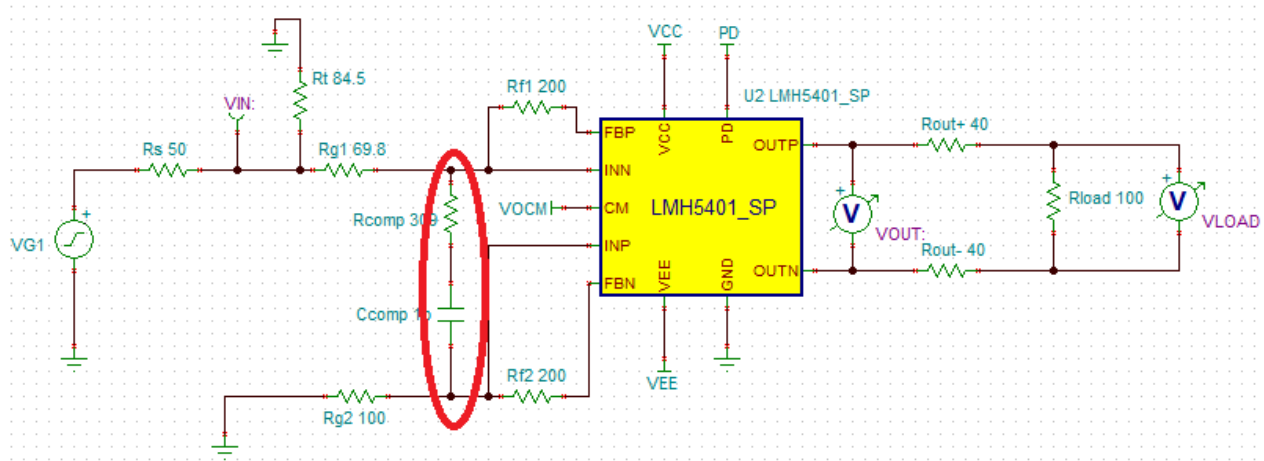

- Shunt C can be added in series with resistor to shape noise
- At low frequencies capacitor is open, noise gain is unaffected (remains low) where stability is not a problem
- At higher frequencies, capacitor shorts presenting shunt path to circuit and increasing noise gain, thus, decreasing AC gain peaking.
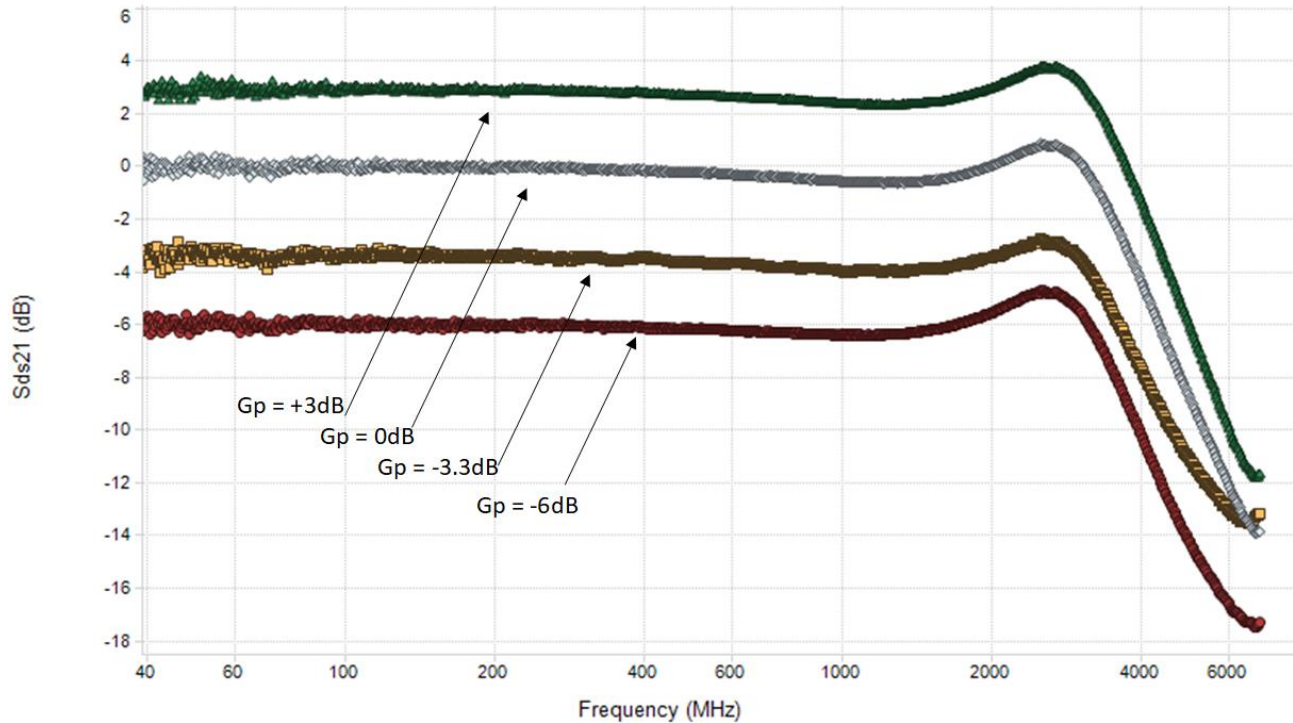
# Low gain single-ended to differential freq. response




- **Sds21 is:**
  - **S-parameter measurement using vector network analyzer instrument**
  - **Power gain**
- **Optimal noise gain compensation resistor determined for each signal gain curve**

$G_p$ (dB)	$G_{VAMP\text{OUT}}$ (dB)	AC Peaking (dB)	3DB_BW (MHz)	$G_N$ (V/V)
3.0	12.0	0.84	3742	4.77
0.0	9.0	0.84	3706	4.76
-3.3	5.7	0.65	3670	5.07
-6.0	3.0	1.40	3670	4.74

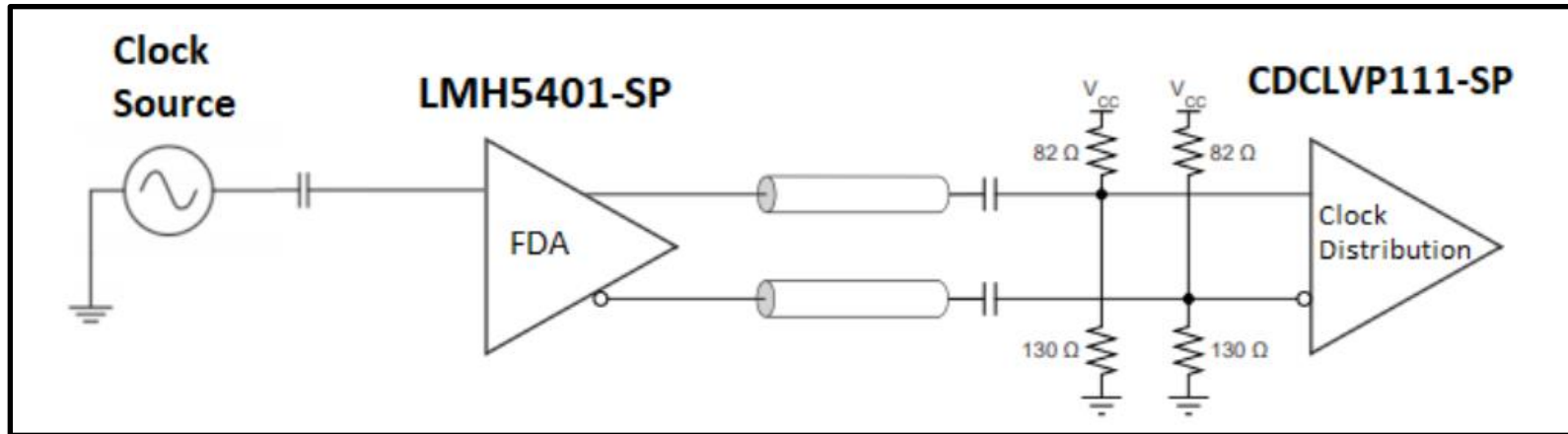
# FDA used as a clock buffer

- FDA replaces balun where single ended clock source drives differential input of clock distributor
- Gain of FDA overcomes the challenge of balun insertion loss and transmission line losses where clock source and clock distribution device are not in close proximity
- Additive jitter of FDA minimal



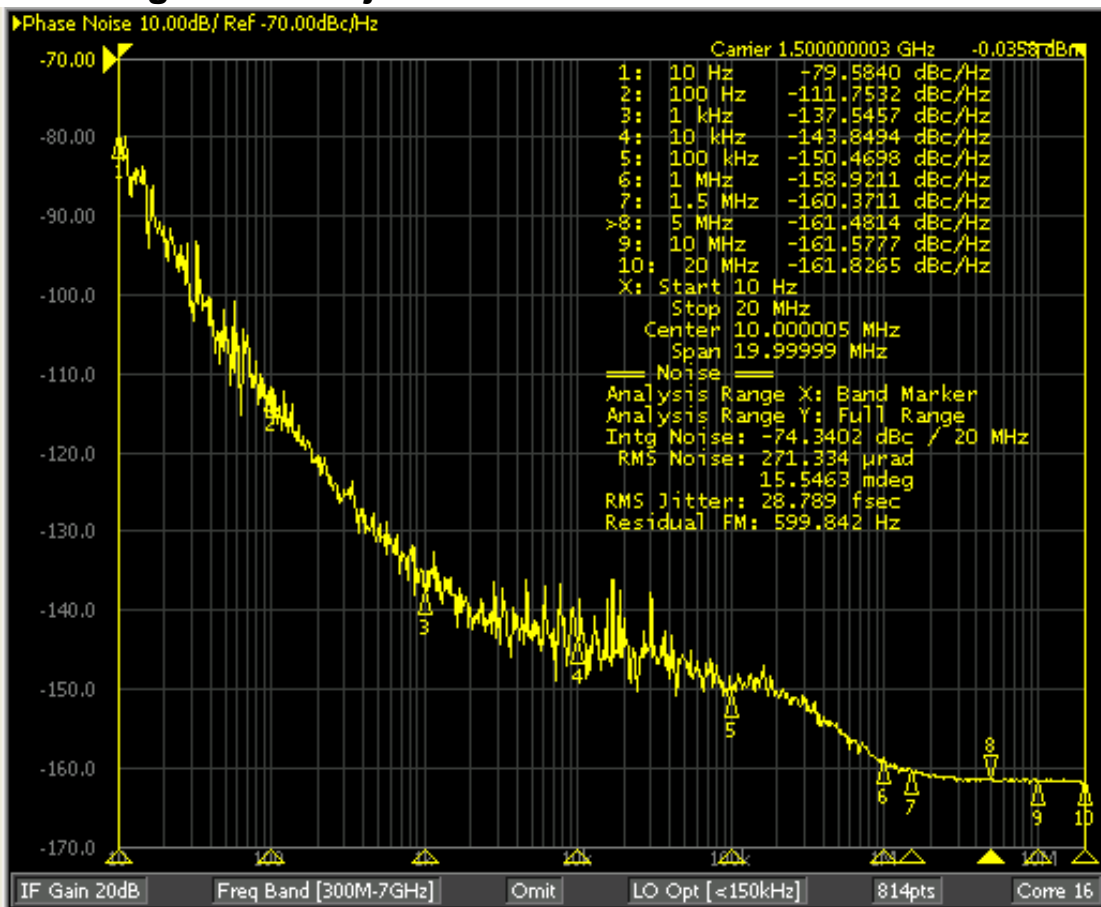
# FDA used as a clock buffer

- R&S SMA100B Signal Generator Phase Noise
- Integrated RMS jitter = 28.789 fsec at 1.5GHz




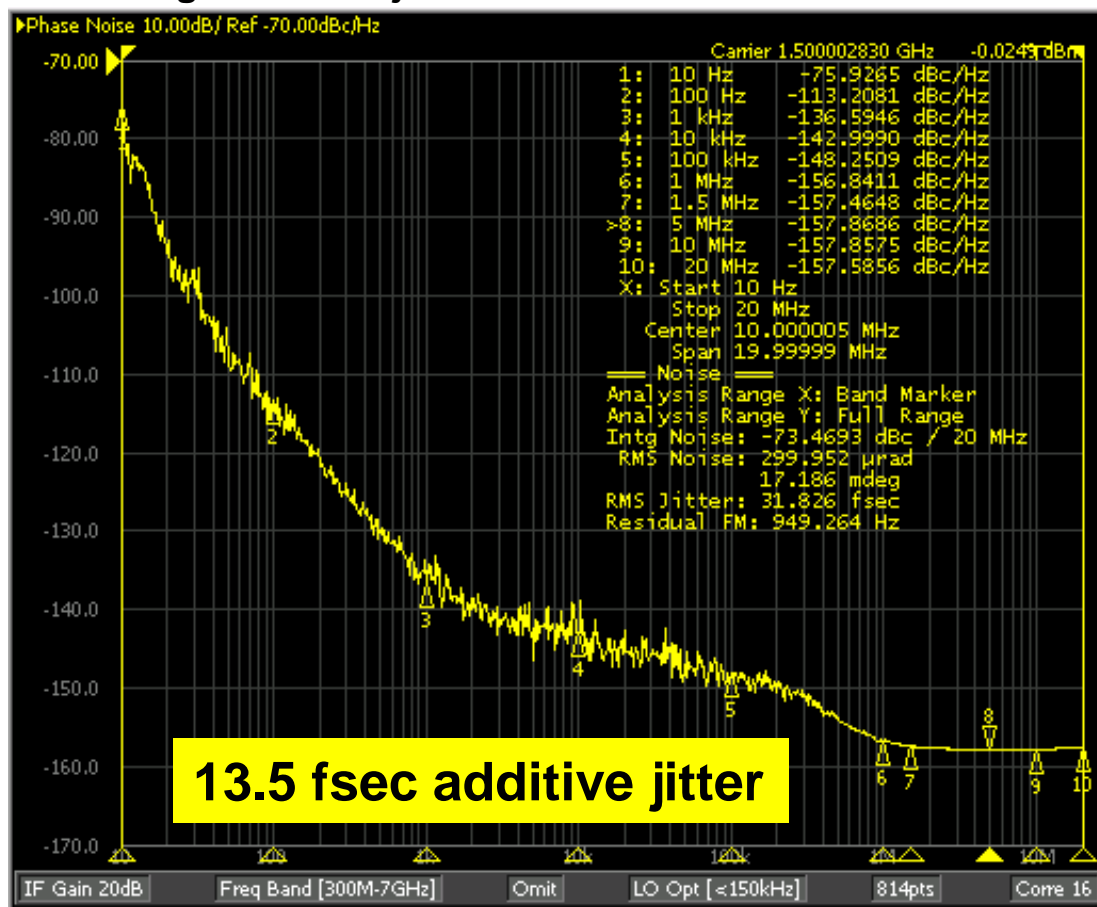- SMA100B + LMH5401-SP Phase Noise
- Integrated RMS jitter = 31.826 fsec at 1.5GHz


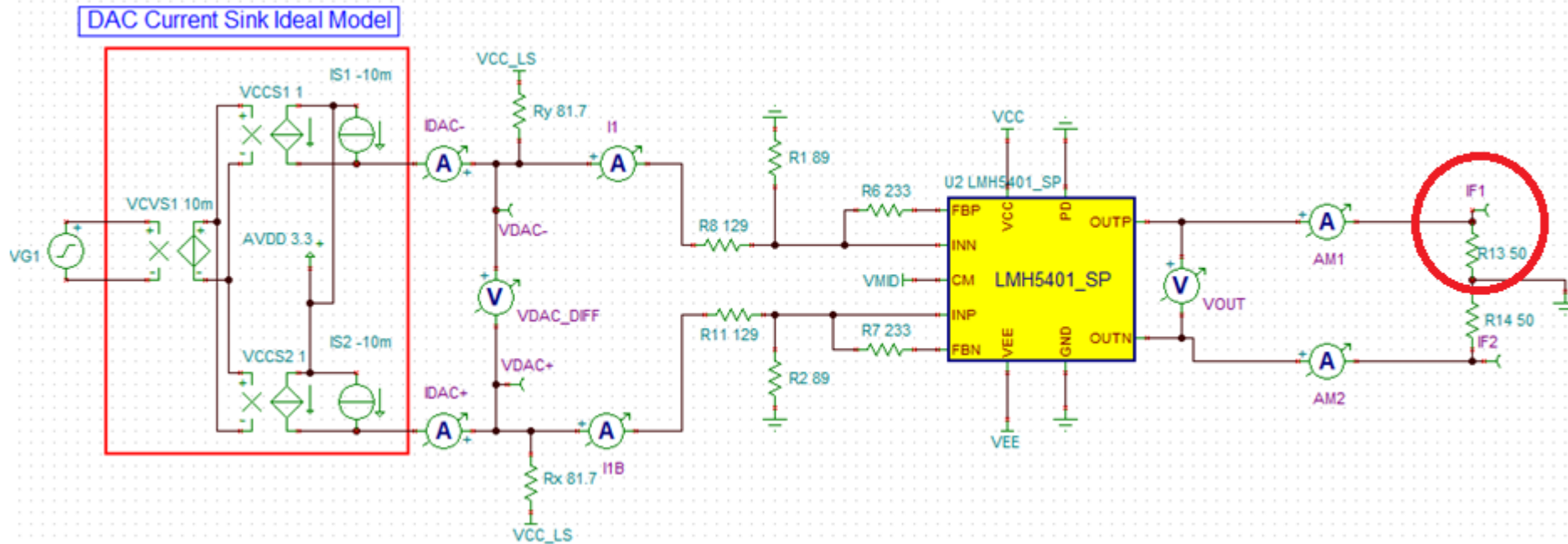
# FDA used as a DAC buffer



- Spice model available to evaluate current sink DAC model (DAC5675A) driving LMH5401-SP




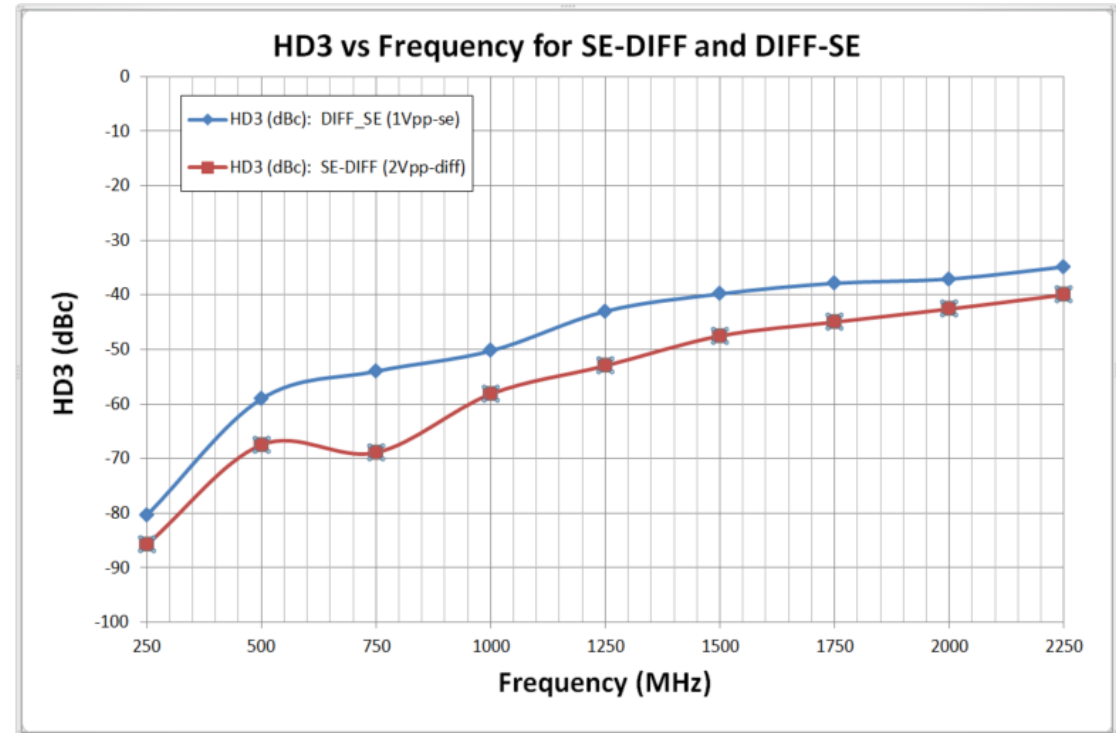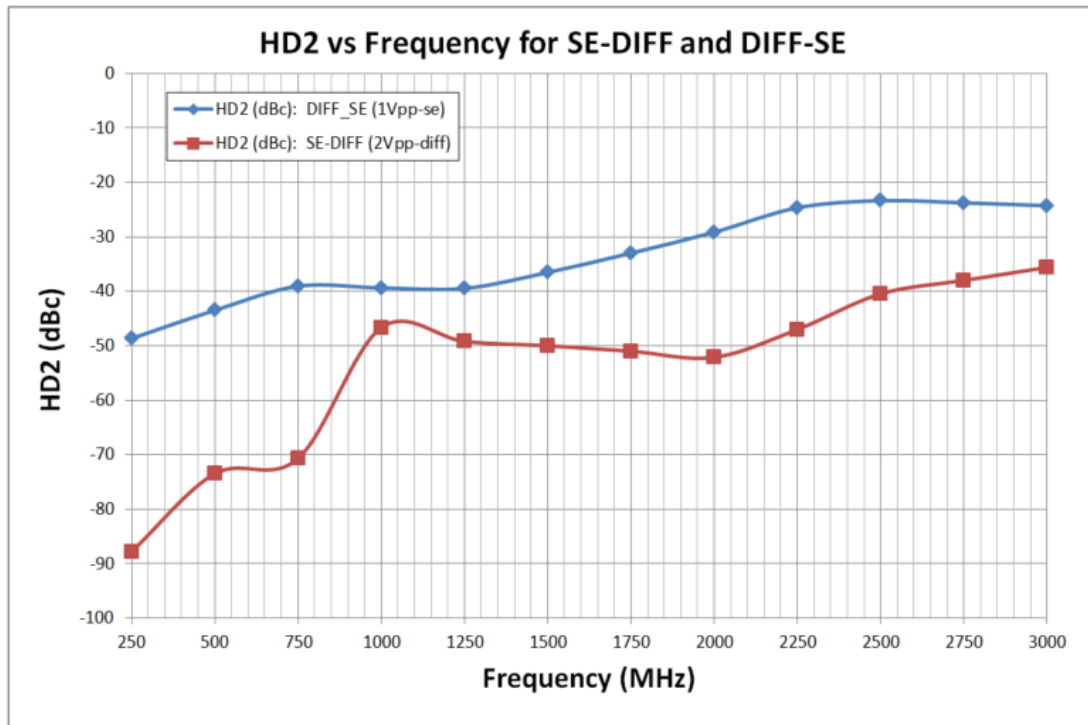
# FDA differential input to single-ended output

- Using one output of FDA is feasible if HD2 and HD3 requirements are relaxed




# FDA used to level shift common mode

- [insert content]

# TI devices referenced in this presentation

## LMH5401-SP: 6.5GHz fully diff amp

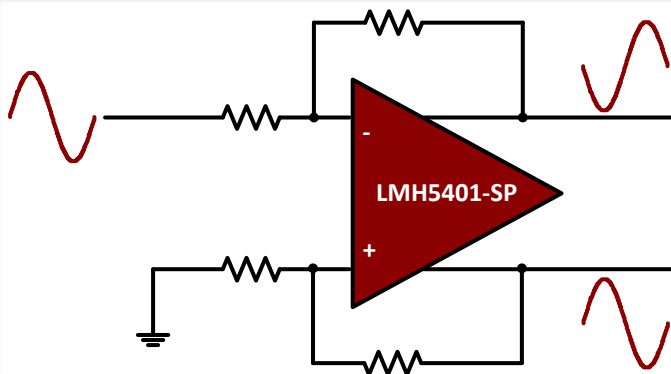


### Key features

- TID: 100 krad SEL: 85 MeV-cm<sup>2</sup>/mg
- Gain-bandwidth: 6.5 GHz
- Balun upgrade for high speed ADC/DAC interface
- Suitable for signal gain, level shifting, clock buffer
- 14-pin leadless Ceramic (5.5mm x 6mm)

In production

## ADC12DJ3200QML-SP: 3.2GSPS dual ADC

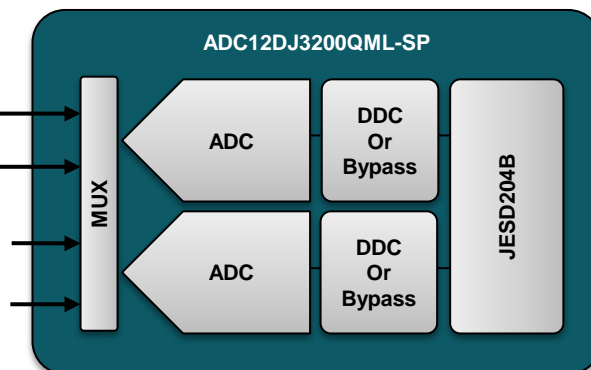


### Key features

- TID: 300 krad SEL: 120 MeV-cm<sup>2</sup>/mg
- 12-bit, >7-GHz input bandwidth
- Dual 3.2-GSPS or single 6.4-GSPS
- Up to 12.8-Gbps JESD204B serdes
- Optional DDC in dual mode
- Ceramic LGA package (15mm x 15mm)

In production

## CDCLVP111-SP: 1:10 Clock Distributor

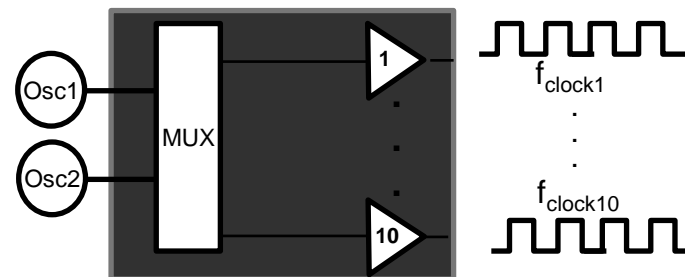


### Key features

- TID: 75 krad SEL: 120 MeV-cm<sup>2</sup>/mg
- DC to 3 GHz output
- Selectable Input Clock
- Additive RMS jitter: 125 fsec typical @ 200MHz (10 kHz to 20 MHz)
- 36 pins CCFP (9mm x 9mm)

In production

# TI devices referenced in this presentation

## DAC5675A-SP: 14-bit, 400MSPS DAC

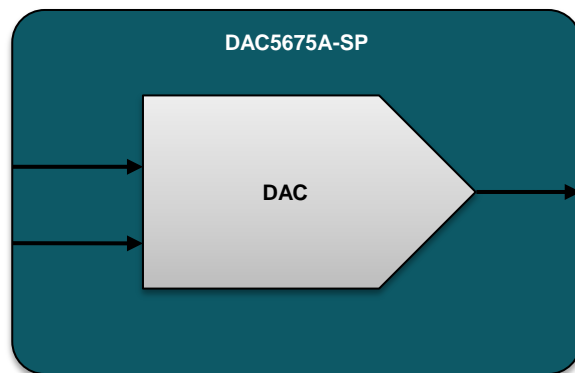

### Key features

- **SEL: 109 MeV-cm<sup>2</sup>/mg**
- **14-bit, 400 MSPS single DAC**
- **Ceramic QFP package (19mm x 10mm)**

**In production**

# Summary

- Fully differential amplifiers are extremely flexible in their use case configurations
- A single FDA part number, such as the LMH5401-SP, that offers wideband operation and is space qualified with TID and SEE reports published, alleviates the challenge of procuring several unique devices for different signal chain needs.
- TI support is available to help you meet your design requirements. Please ask.
  - <https://e2e.ti.com/support>

# Resources

- [TI Space Products Guide – Updated September, 2018](#)
- [New TI Aerospace & Defense Portal](#)
- [Radiation Handbook: Comprehensive radiation guide built using decades of knowledge from across TI's expert teams](#)
- **LMH5401-SP Tools**
  - [LMH5401-SP Spice Model](#)
  - [LMH5401-SP: Single-ended to Differential Circuit Design Calculator](#)
- **Content References**
  - [TI Precision Labs Training – FDAs](#)
  - [Analysis of fully differential amplifiers](#), Application note
  - [Fully differential amplifiers](#), Application note
  - [Input impedance matching with fully differential amplifiers](#), Application note
  - [Output impedance matching with fully differential amplifiers](#), Application note
  - [Using fully differential op amps as attenuators, Part 1](#), Application note
  - [Using fully differential op amps as attenuators, Part 2](#), Application note
  - [Using fully differential op amps as attenuators, Part 3](#), Application note
  - [Stabilizing Differential Amplifiers as Attenuators](#), TI Design
  - [How to use a fully differential amplifier as a level shifter](#), TI Blog

# Online technical training from Texas Instruments

## **Coming up: Implementing high current applications using POL devices – March 20<sup>th</sup>, 2018**

Learn about how to parallel Point of Load (POL) LDOs and DC-DC converters to help meet high current requirements. [Register](#)

## **Coming up: Understanding cosmic radiation effects on electronics – March 27<sup>th</sup>, 2018**



During this webinar we will cover different radiation effects, how it impacts electronic circuits and compare space rated and commercial off the shelf (COTS) devices. [Register](#)

## **Aerospace & Defense Training Series – Available Now**

The Aerospace and Defense Training Series is your one-stop portal for product specific and system applications training material. Learn about the latest solutions to help you simplify designs, improve performance and meet stringent project requirements. [Browse videos now!](#)
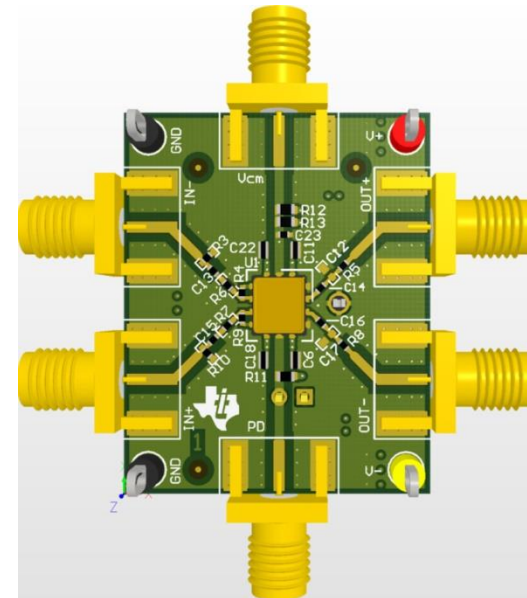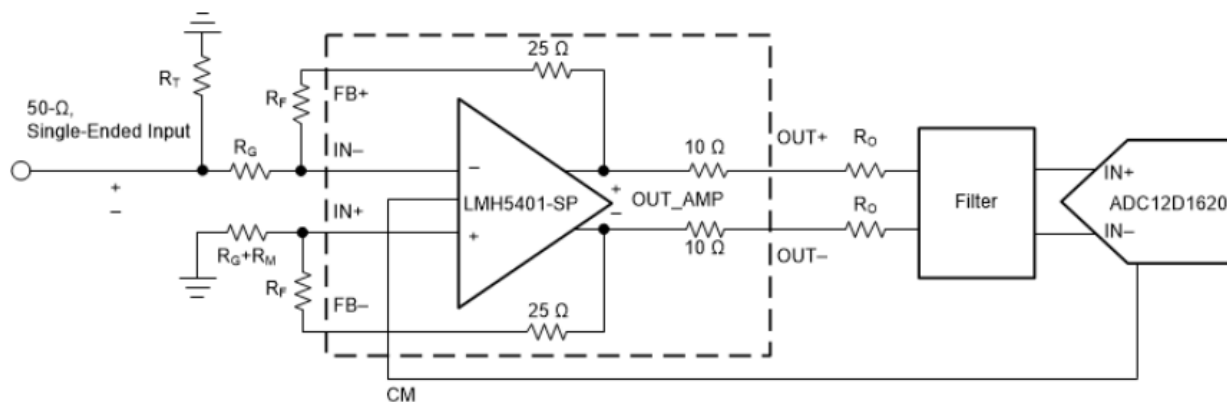
# Additional information

- [ti.com/product/LMH5401-SP](https://ti.com/product/LMH5401-SP)
- [ti.com/product/THS4511-SP](https://ti.com/product/THS4511-SP)
- [ti.com/product/THS4513-SP](https://ti.com/product/THS4513-SP)







© Copyright **2019** Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)