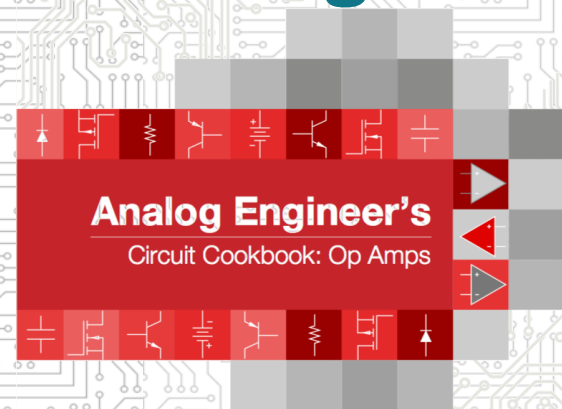


# How to Design Low-side, bidirectional current sensing circuit


General Purpose Amplifiers

[www.ti.com/general-amps](http://www.ti.com/general-amps)

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)




# Circuit Description

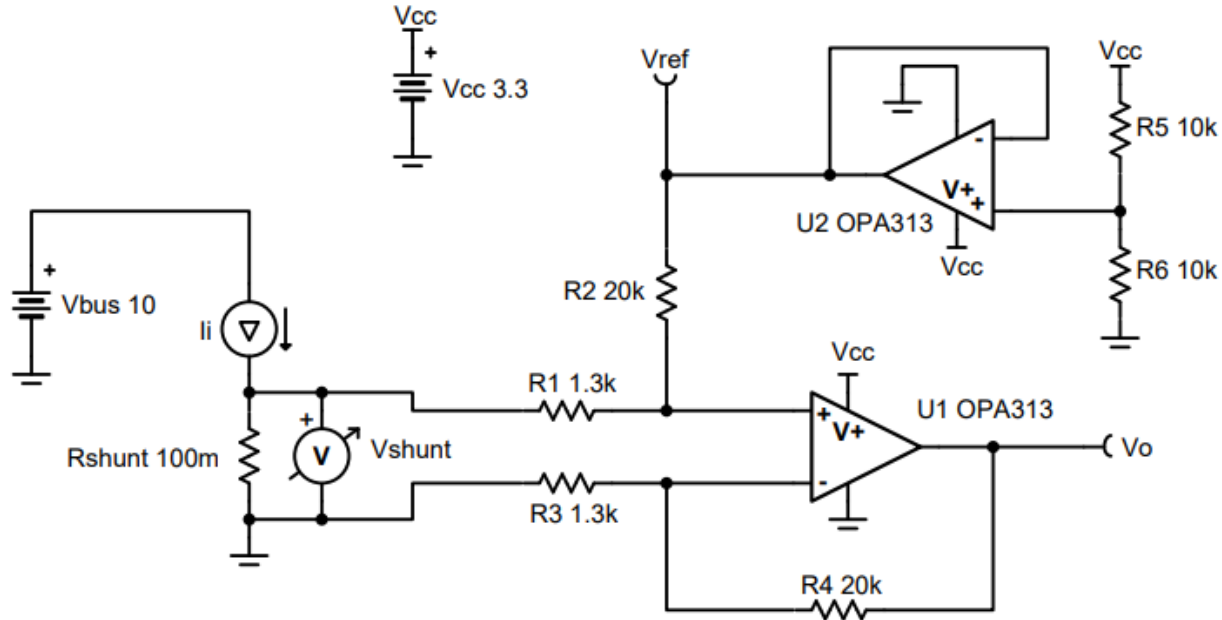

$$V_o = \left( I_i \times R_{shunt} \times \frac{R_4}{R_3} \right) + V_{ref}$$

# Design Goal

Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

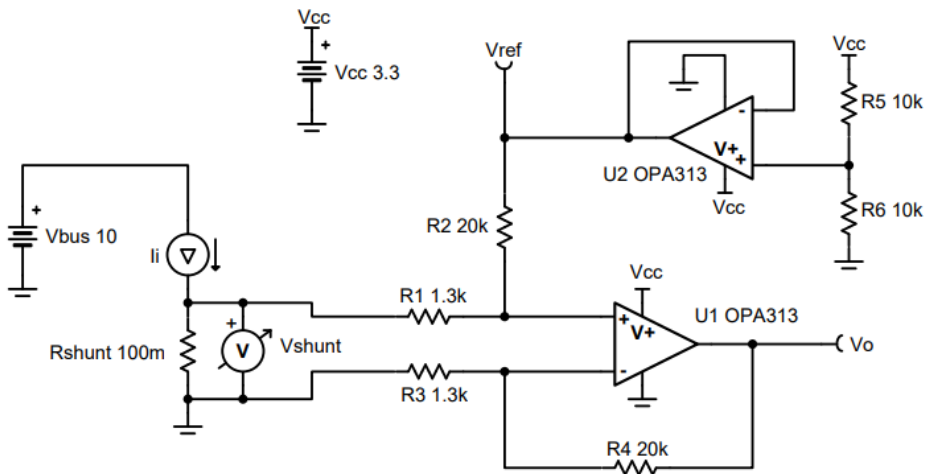

Current to Voltage

Reference Voltage


$$V_o = (I_i \times R_{shunt} \times \frac{R_4}{R_3}) + V_{ref}$$

↑  
Diff Amp  
Gain

$$V_{ref} = V_{cc} \times \frac{R_6}{R_5 + R_6}$$

# Design Steps


Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

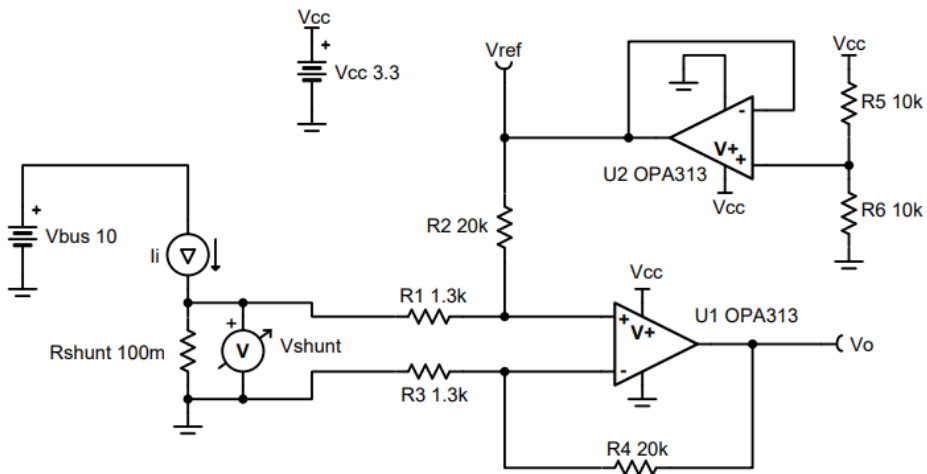

$$R_{shunt} = \frac{V_{shunt\_max}}{I_{iMax}} = \frac{100mV}{1A} = 100\ m\Omega$$

# Design Steps

Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

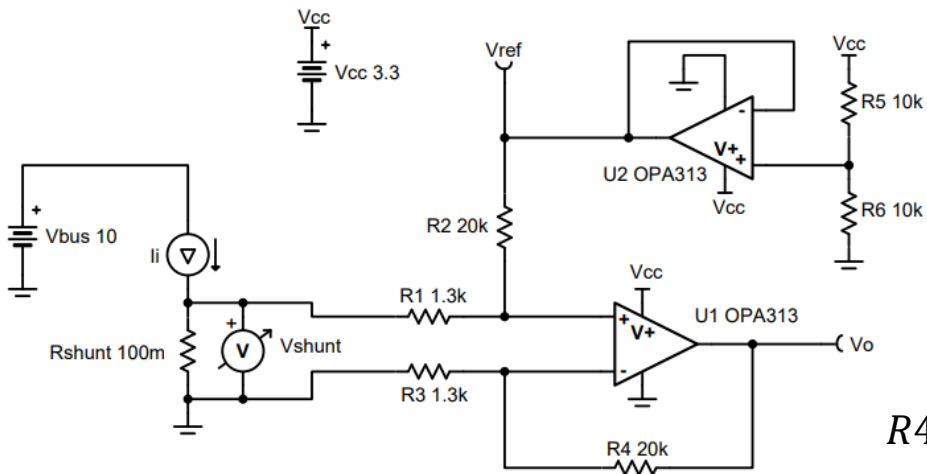

$$Gain = \frac{VoMax - VoMin}{Rshunt \times (IiMax - IiMin)} = 15.5 \text{ V/V}$$

$$Gain = \frac{R4}{R3}$$


$$R3 = R1 = 1.3 \text{ k}\Omega$$

$$R4 = R2 = Gain \times R3 = 15.5 \frac{\text{V}}{\text{V}} \times 1.3 \text{ k}\Omega = 20.15 \text{ k}\Omega$$

$$Gain_{actual} = 15.38 \frac{\text{V}}{\text{V}}$$

# Design Steps

Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

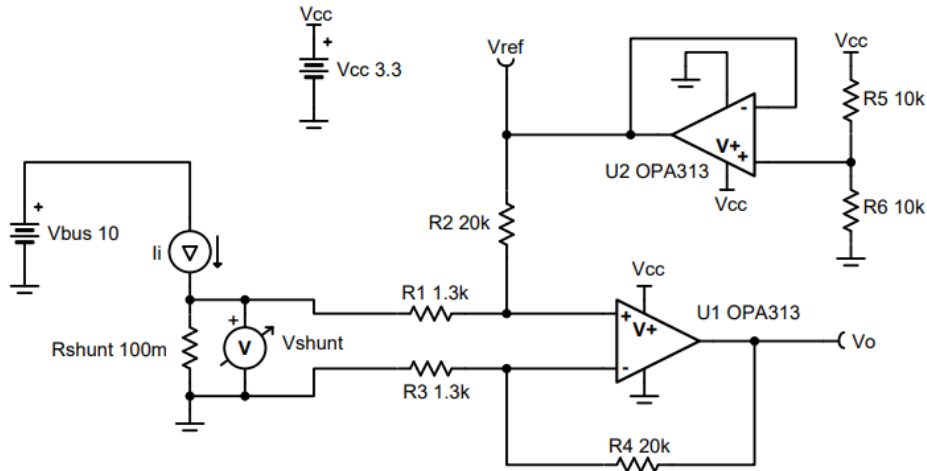



$$V_{ref} = V_{cc} \times \frac{R_6}{R_5 + R_6}$$

$$R_5 = R_6 = 10\text{ k}\Omega$$

$$V_{ref} = 3.3\text{ V} \times \frac{10\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega} = 1.65\text{ V}$$



# DC Results

Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

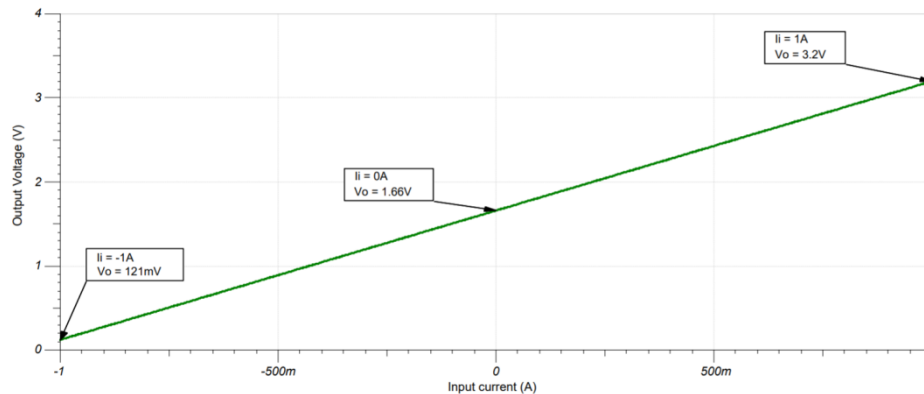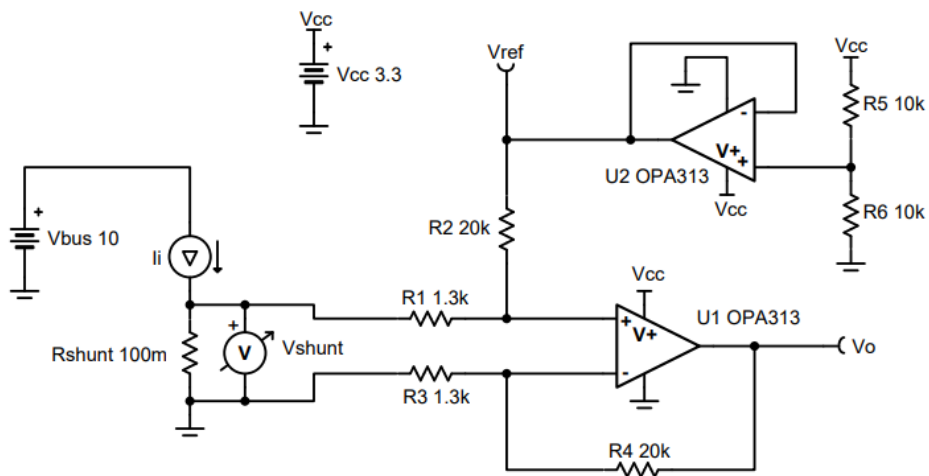

# AC Results


Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

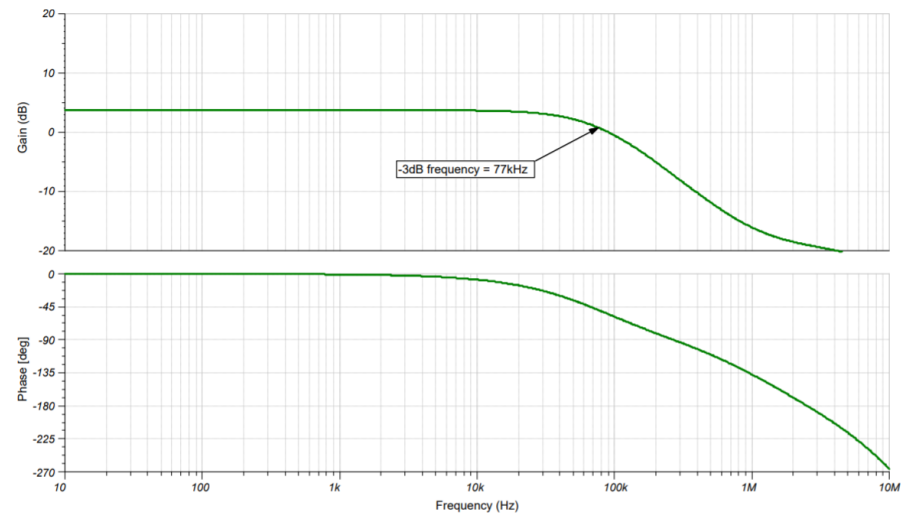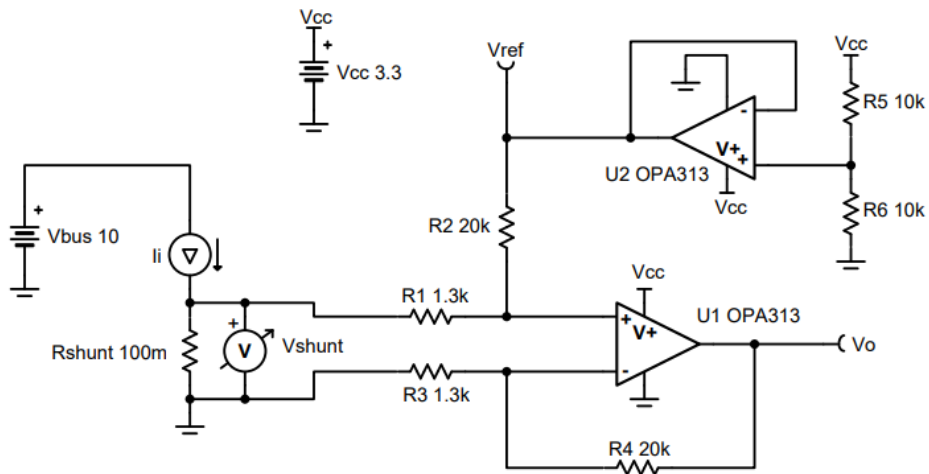



# Design Notes

Input		Output		Supply		
$I_{iMin}$	$I_{iMax}$	$V_{oMin}$	$V_{oMax}$	$V_{dd}$	$V_{ee}$	$V_{ref}$
-1 A	1 A	110mV	3.19V	3.3V	0V	1.65V

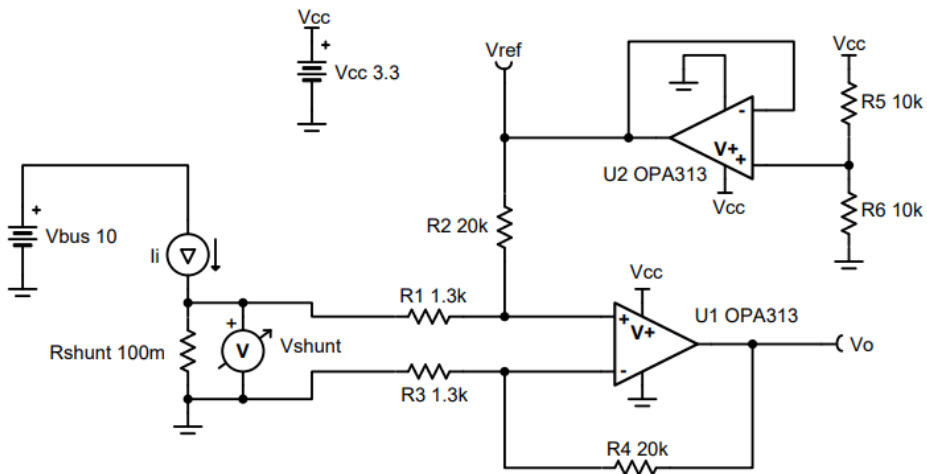

## Design Notes:

1. For low-side sensing, use op amps whose  $V_{cm}$  includes ground
2. Operate within the linear output voltage swing (See  $A_{OL}$  specification) to minimize non-linearity errors.
3. Buffer the voltage divider to provide a low impedance node to the reference voltage,  $V_{ref}$ .

# Design Resources

## EE Cookbook: Op Amp

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)

Step-by-step circuit design of common op amp building block circuits.

## TI Designs

[www.TI.com/tidesigns](http://www.TI.com/tidesigns)

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

## Analog Engineer's Pocket Reference

[www.TI.com/analogrefguide](http://www.TI.com/analogrefguide)

PDF, iTunes app and hardcopy available  
PCB, analog, mixed signal design formulae  
Conversions, tables, equations

## TI Precision Labs

[www.TI.com/precisionlabs](http://www.TI.com/precisionlabs)

Quiz questions, problems, solutions  
Labs and evaluation module (EVM) available

## TINA-TI™ simulation software

[www.TI.com/tool/tina-ti](http://www.TI.com/tool/tina-ti)

Complete SPICE simulator DC, AC, transient, noise analysis  
Schematic entry and post-processor for waveform math

## DIYAMP-EVM

[www.TI.com/DIYAMP-EVM](http://www.TI.com/DIYAMP-EVM)

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

## The Signal

[www.TI.com/signalbook](http://www.TI.com/signalbook)

PDF, iTunes app and hardcopy available  
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

## Analog Wire Blog

[www.TI.com/analogwire](http://www.TI.com/analogwire)

Technical blogs written by analog experts  
Tips, tricks, and design techniques

## TI E2E™ Community

[www.TI.com/e2e](http://www.TI.com/e2e)

Support forums for all TI products

## Op Amp Parametric Quick Search

[www.TI.com/amplifiers](http://www.TI.com/amplifiers)

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

## Op Amp Parametric Cross-Reference

[www.TI.com/opampcrossreference](http://www.TI.com/opampcrossreference)

Find similar TI op amps using competitive part numbers

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)



© Copyright 2019 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)