

Analog Input 2-wire 4-20mA Transmitters


TI Precision Labs – Current Loop Transmitters

Presented by Katlynne Jones

Prepared by Katlynne Jones

2-wire transmitter

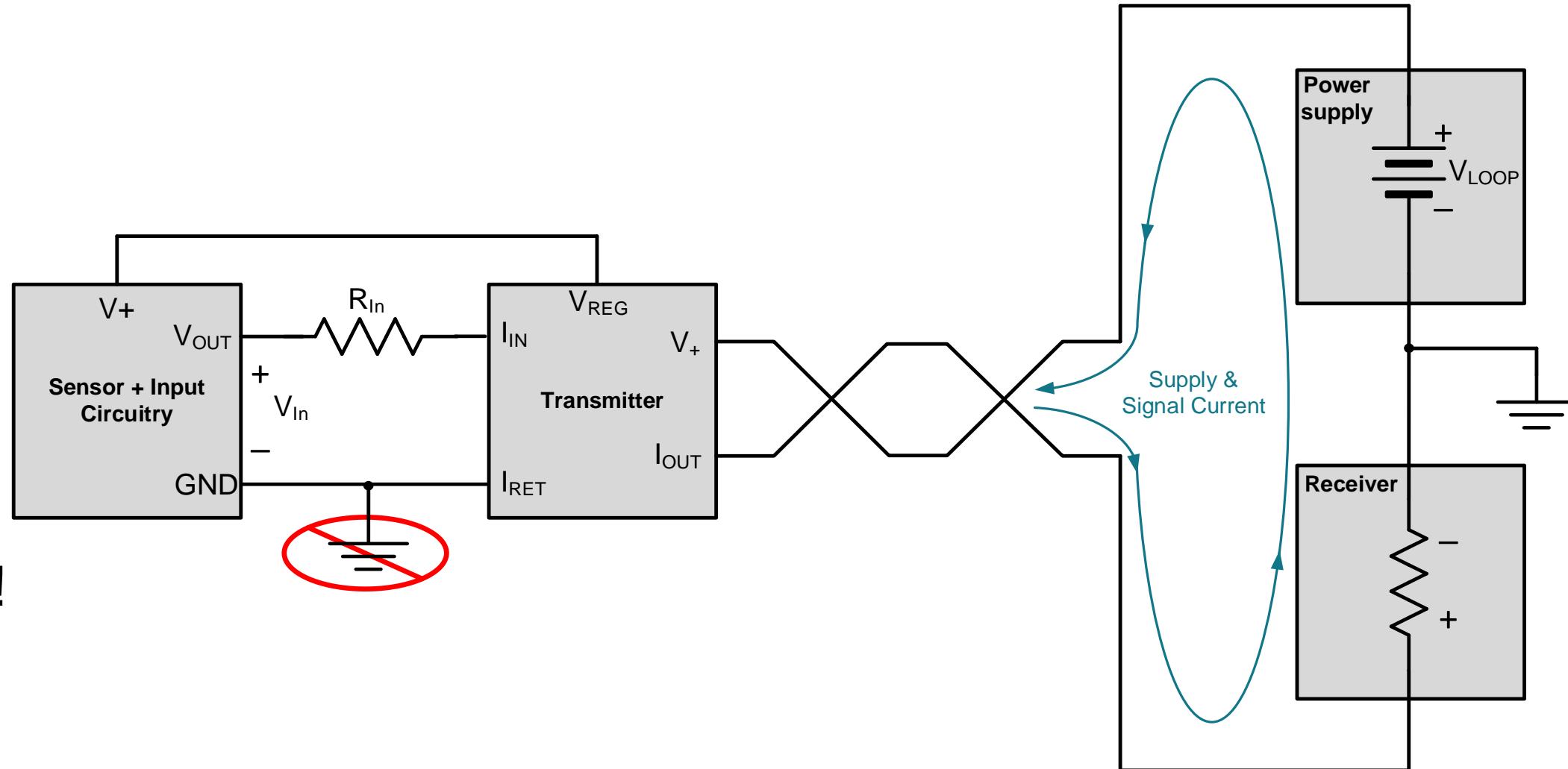- 2-wire transmitter block diagram
 - 2 wires create a loop that transmits the signal current and transmitter power
 - I_{RET} cannot be grounded to V_{LOOP} !
 - Transmitter, sensor, and input circuitry must consume $<4\text{mA}$



Derivation of transfer function

$$V_+ = V_-$$

$$I_{IN} = \left(\frac{V_{DAC}}{R_{IN}} + \frac{V_{REG}}{R_{OS}} \right)$$


$$V_+ = I_{IN} * R_1$$

$$V_- = (I_{RET} + I_{BJT}) * R_2$$


$$I_{IN} * R_1 = (I_{RET} + I_{BJT}) * R_2$$

$$I_{BJT} + I_{RET} = \frac{I_{IN} * R_1}{R_2}$$

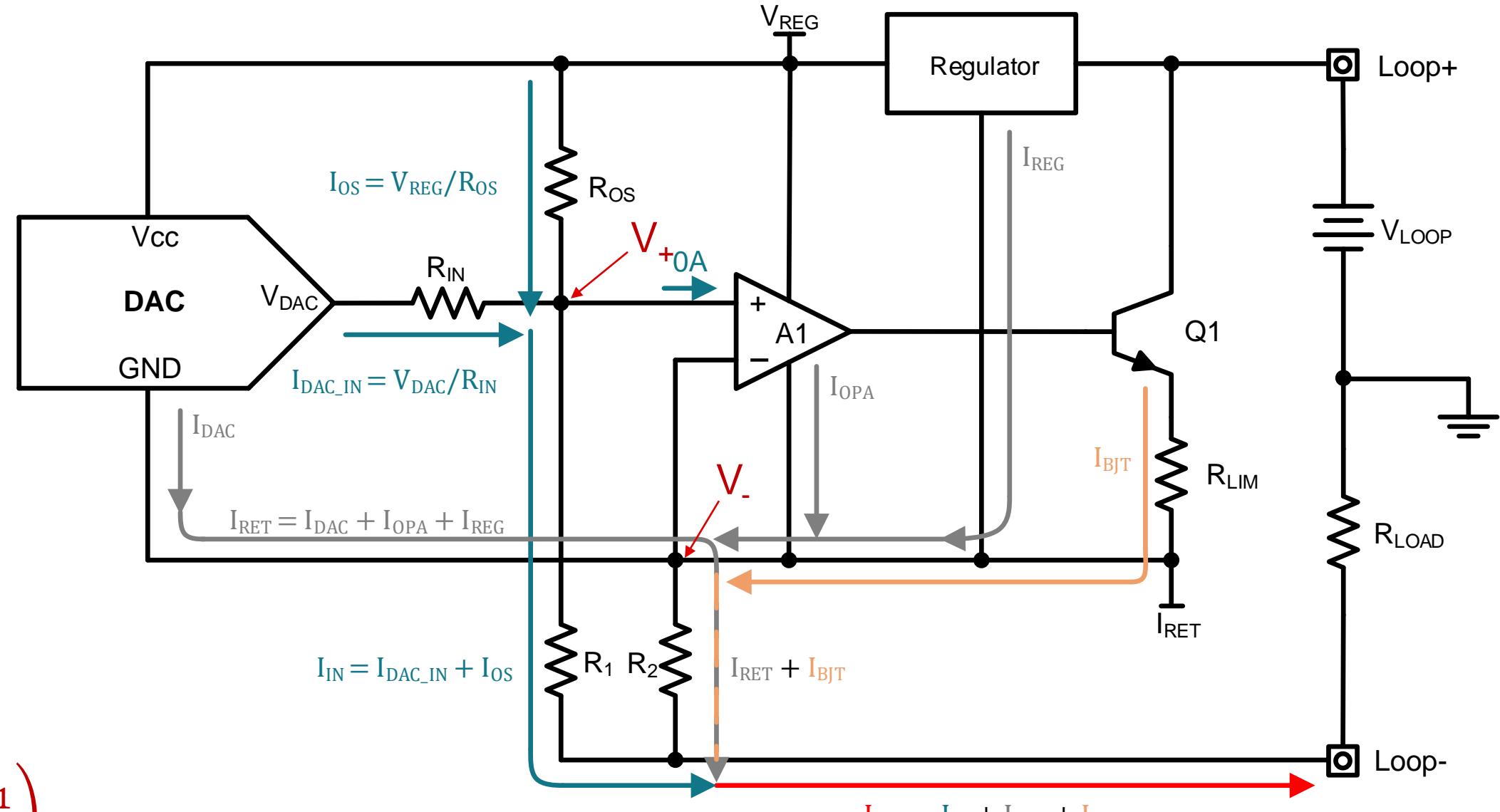
$$I_{OUT} = \left(\frac{V_{DAC}}{R_{IN}} + \frac{V_{REG}}{R_{OS}} \right) * \left(1 + \frac{R_1}{R_2} \right)$$



Transmitter input

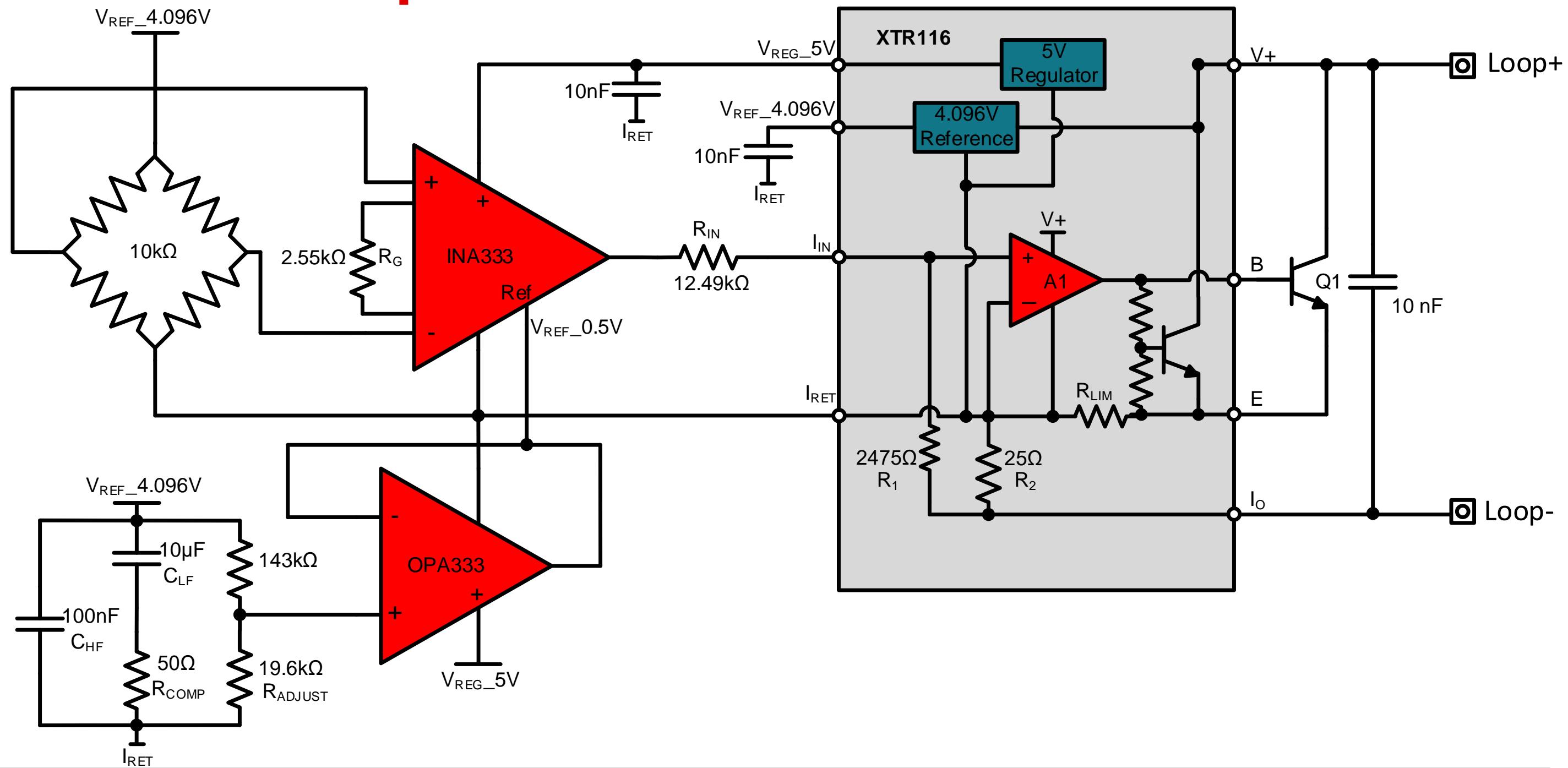

Transmitter input

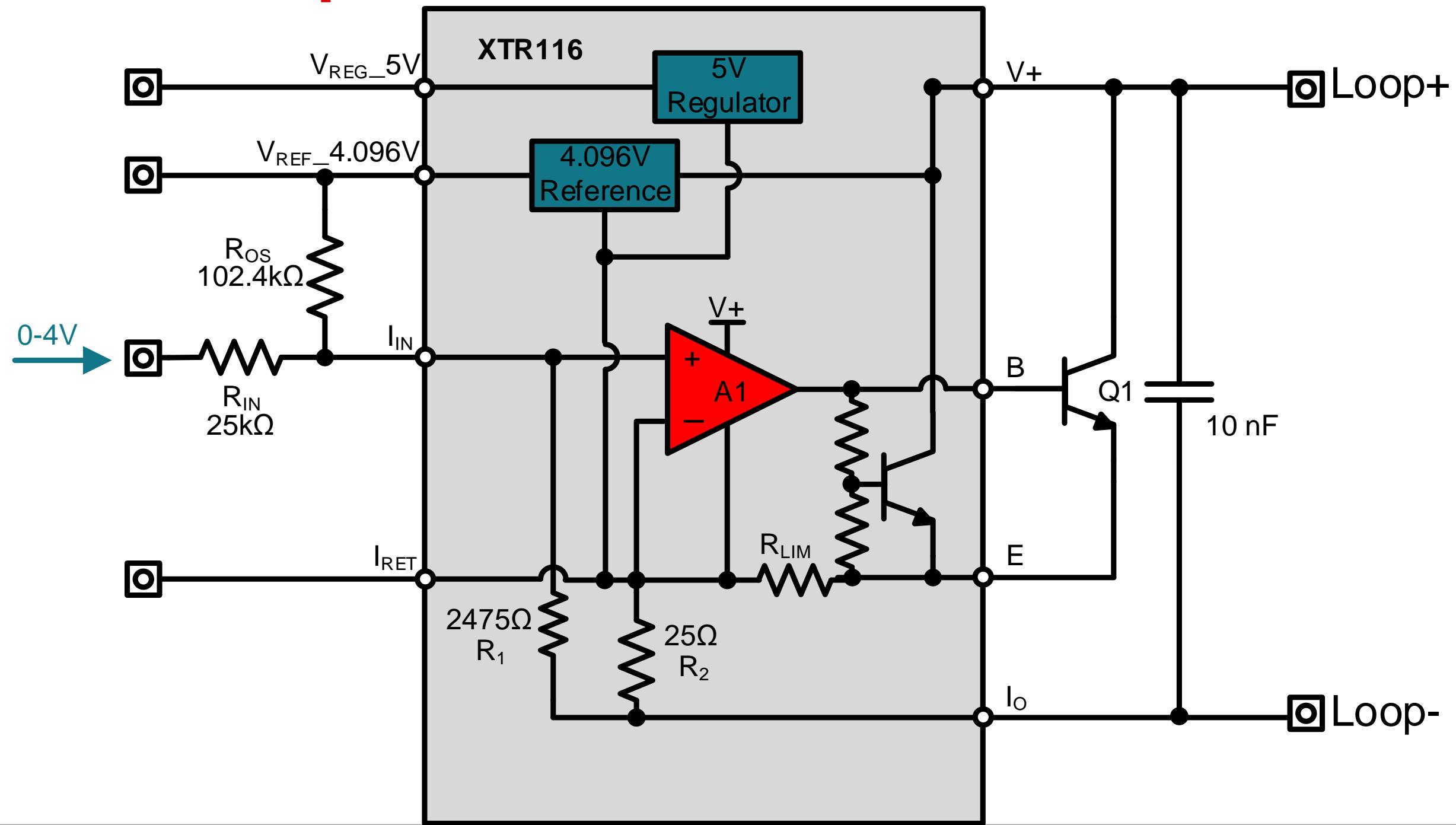

I_{RET}

$$I_{IN} = \left(I_{SOURCE} + \frac{V_{REF}}{R_{OS}} \right)$$


$$I_{OUT} = \left(I_{SOURCE} + \frac{V_{REF}}{R_{OS}} \right) * \left(1 + \frac{R_1}{R_2} \right)$$

$$V_{LOAD} = I_{OUT} * R_{LOAD}$$

$$V_+ = V_- = V_{R1} = V_{R2}$$

$$V_+ = V_{R2} = I_{IN} * R_1$$

$$V_{IRET} = V_{R2} + V_{LOAD}$$

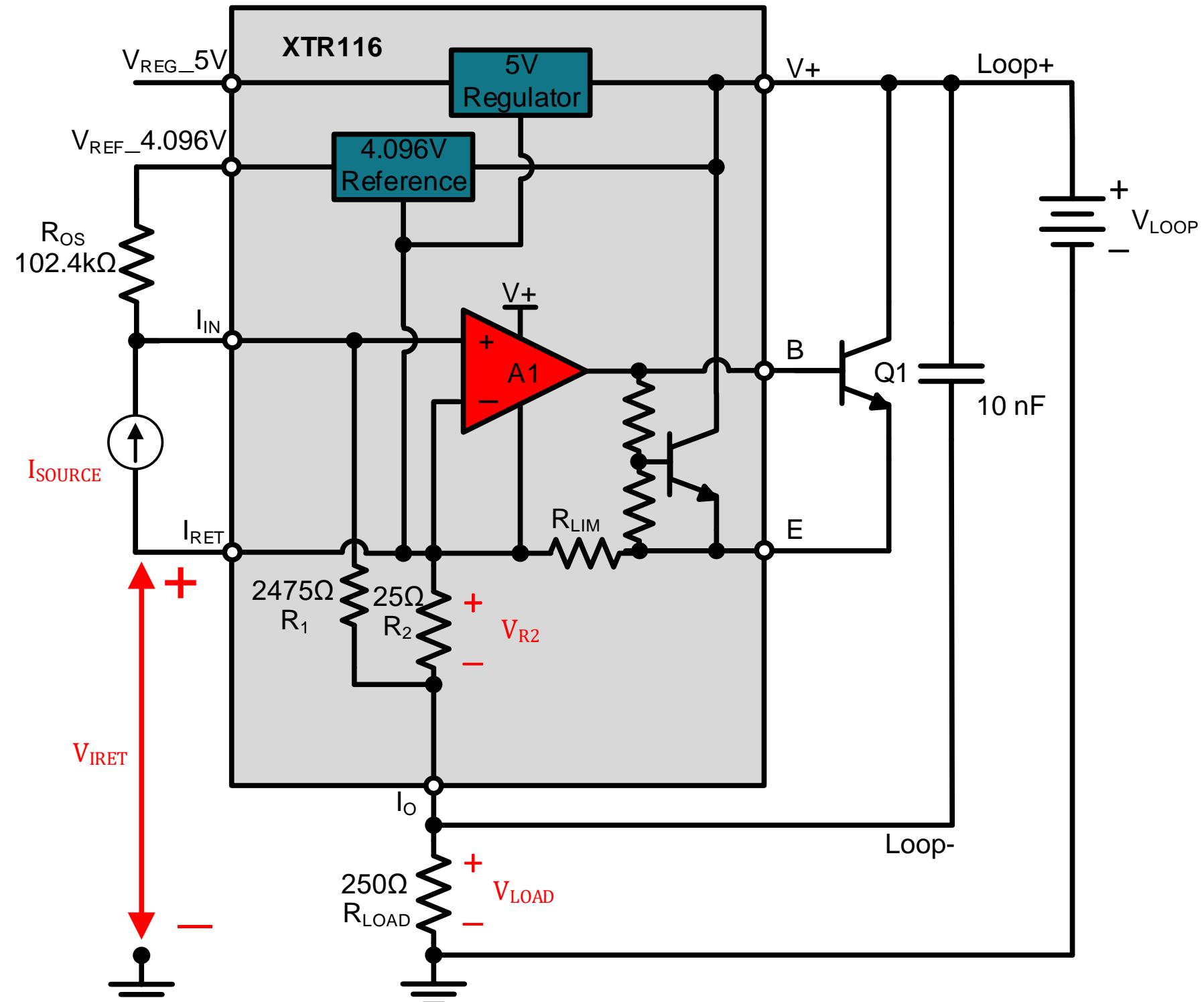

I_{RET}

$$I_{IN} = \left(I_{SOURCE} + \frac{V_{REF}}{R_{OS}} \right)$$

$$I_{IN} = \left(0A + \frac{4.096V}{102.4k\Omega} \right) = 40\mu A$$

$$I_{OUT} = \left(I_{SOURCE} + \frac{V_{REF}}{R_{OS}} \right) * \left(1 + \frac{R_1}{R_2} \right)$$

$$I_{OUT} = (40\mu A) * \left(1 + \frac{2475\Omega}{25\Omega} \right) = 4mA$$

$$V_{LOAD} = I_{OUT} * R_{LOAD}$$

$$V_{LOAD} = 4mA * 250\Omega = 1V$$


$$V_+ = V_- = V_{R1} = V_{R2}$$

$$V_+ = V_{R2} = I_{IN} * R_1$$

$$V_{R2} = 40\mu A * 2475\Omega = 0.099V$$

$$V_{IRET} = V_{R2} + V_{LOAD}$$

$$V_{IRET} = 0.099V + 1V = 1.099V$$

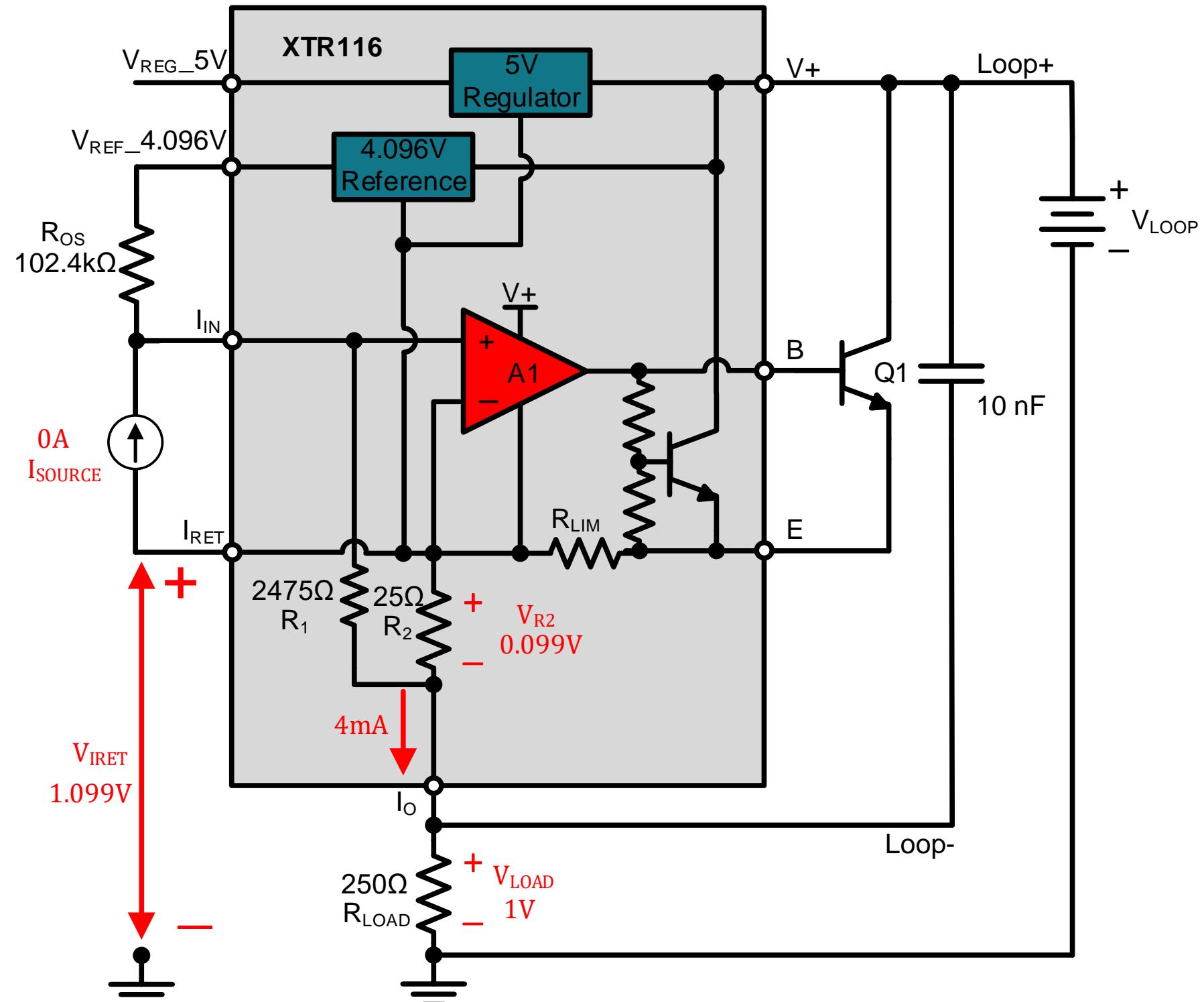

I_{RET}

$$I_{IN} = \left(I_{SOURCE} + \frac{V_{REF}}{R_{OS}} \right)$$

$$I_{IN} = \left(160\mu A + \frac{4.096V}{102.4k\Omega} \right) = 200\mu A$$

$$I_{OUT} = \left(I_{SOURCE} + \frac{V_{REF}}{R_{OS}} \right) * \left(1 + \frac{R_1}{R_2} \right)$$

$$I_{OUT} = (200\mu A) * \left(1 + \frac{2475\Omega}{25\Omega} \right) = 20mA$$

$$V_{LOAD} = I_{OUT} * R_{LOAD}$$

$$V_{LOAD} = 20mA * 250\Omega = 5V$$


$$V_+ = V_- = V_{R1} = V_{R2}$$

$$V_+ = V_{R2} = I_{IN} * R_1$$


$$V_{R2} = 200\mu A * 2475\Omega = 0.495V$$

$$V_{IRET} = V_{R2} + V_{LOAD}$$

$$V_{IRET} = 0.495V + 5V = 5.495V$$

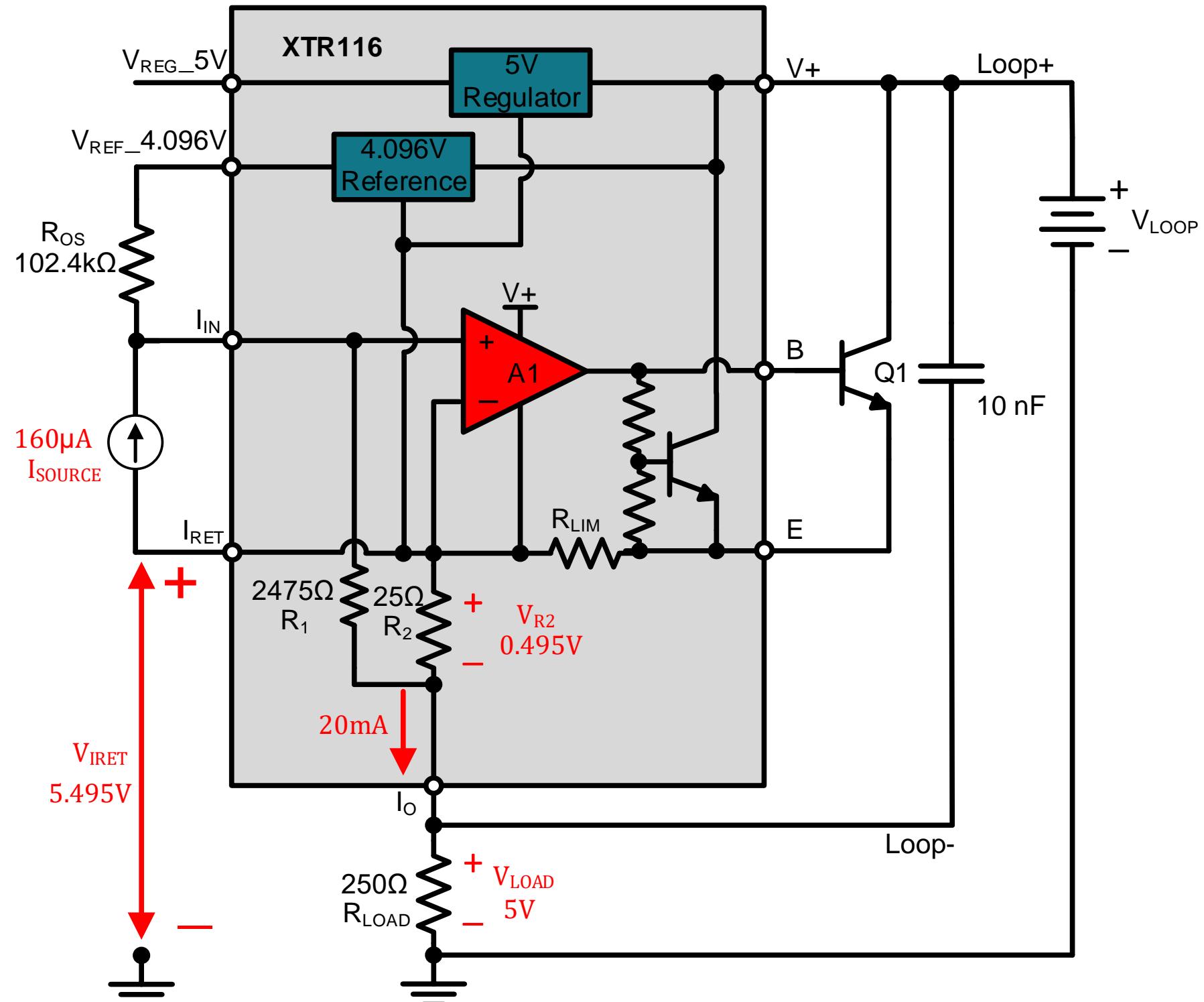


Compliance voltage

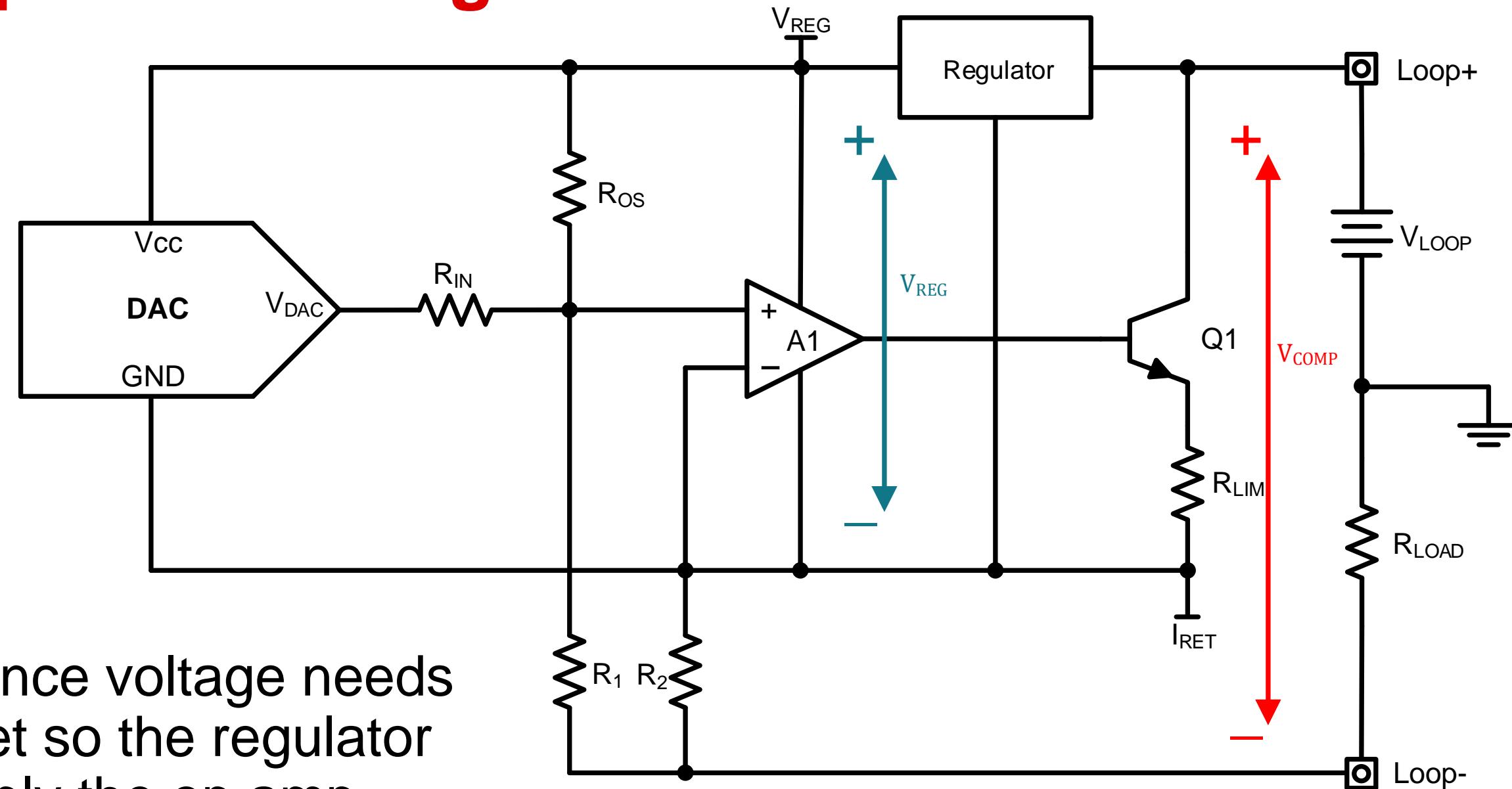

Compliance voltage needs to be met so the regulator can supply the op amp with enough voltage.

Compliance voltage

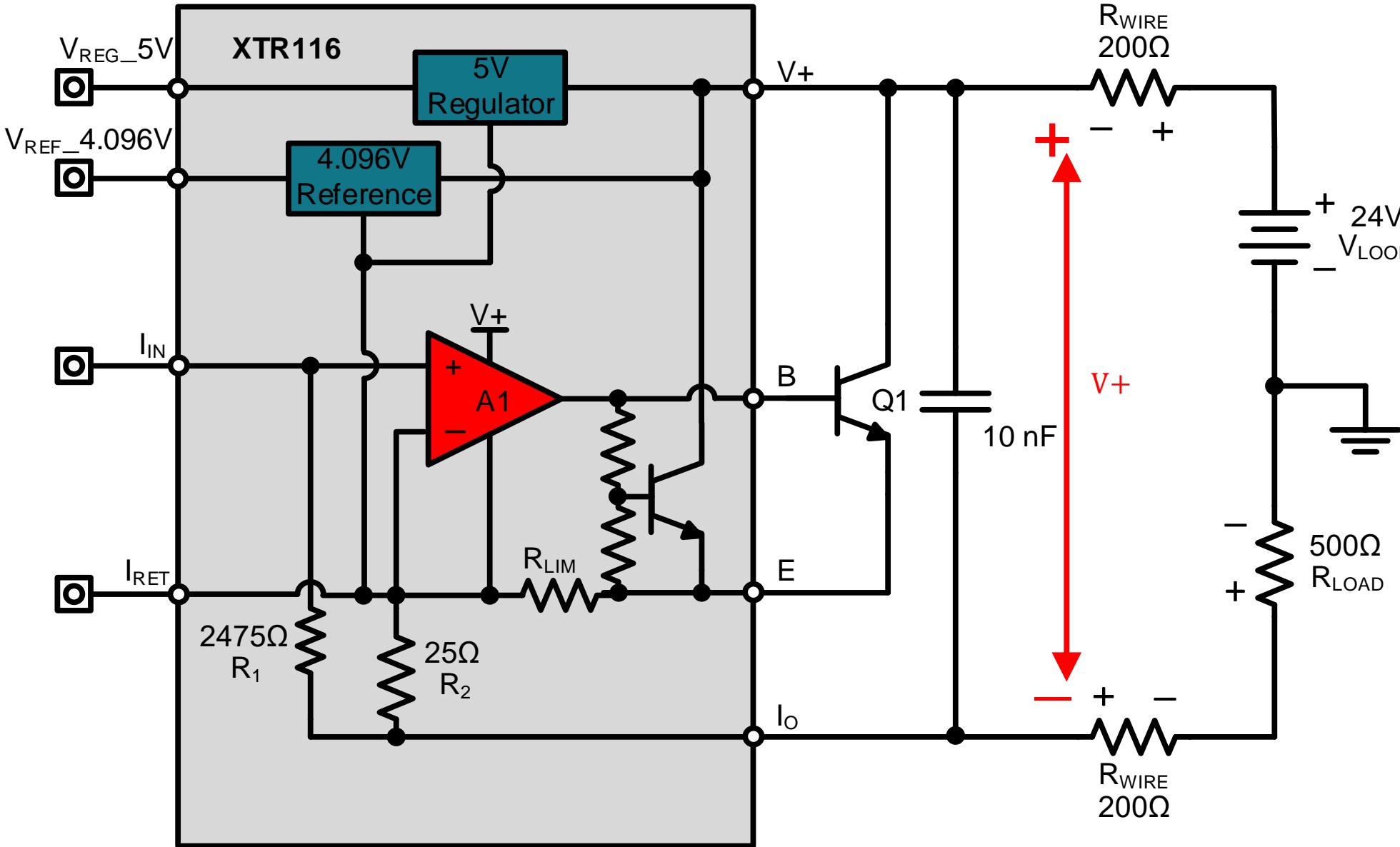

$$V_{LOOP} \geq V_{COMP} + I_{OUT_MAX} * R_{MAX}$$


$$V_+ = V_{LOOP} - I_{OUT_MAX} * R$$

$$V_+ = 24V - 20mA * 900\Omega = 6V$$

$$R_{MAX} = \frac{V_{LOOP} - V_{COMP}}{I_{OUT_MAX}}$$

$$R_{MAX} = \frac{24V - 7.5V}{20mA} = 825\Omega$$

4mA Current budget

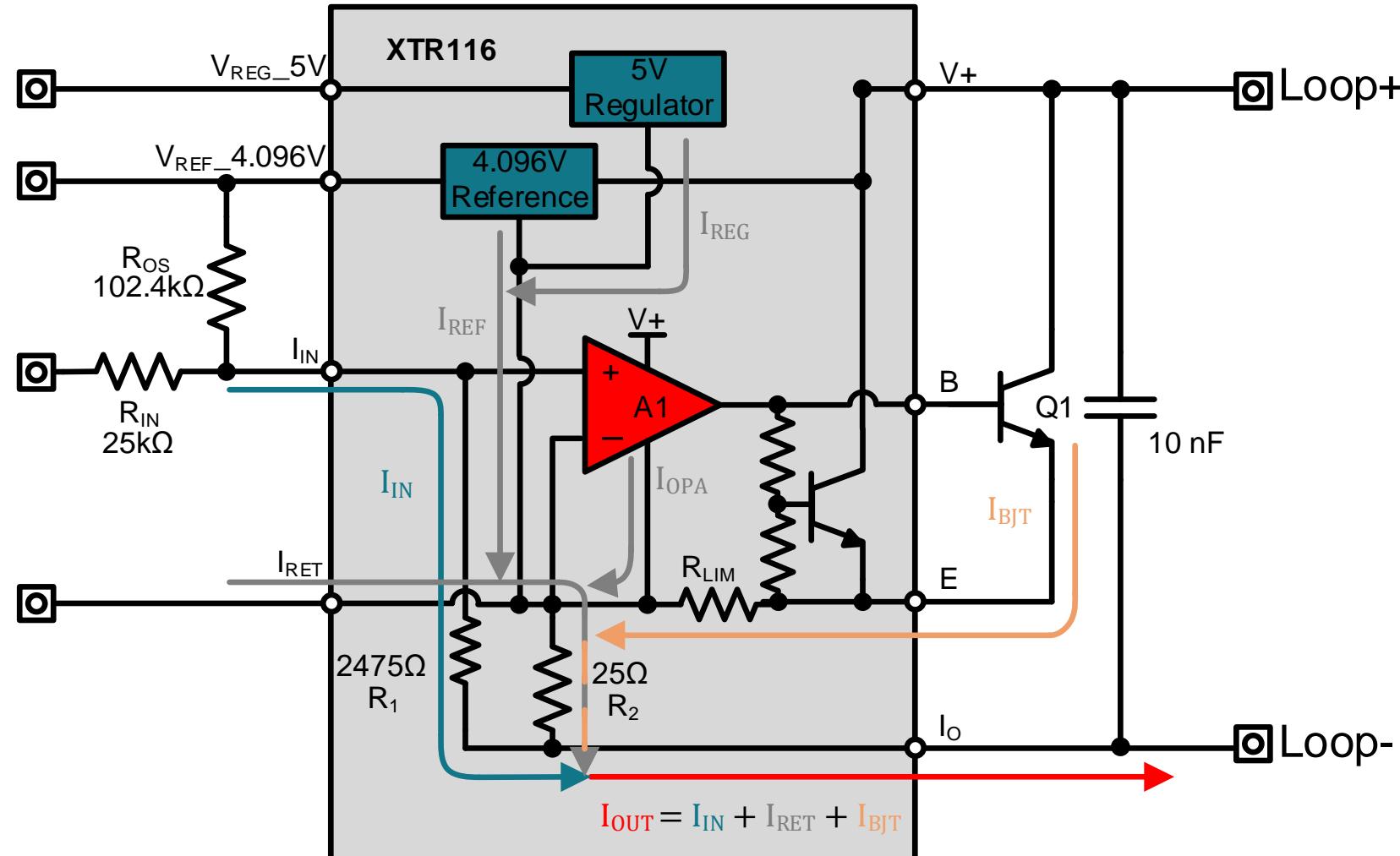


POWER SUPPLY	
Specified Voltage Range	V_+
Operating Voltage Range	
Quiescent Current	I_Q
Over Temperature	


$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$

MIN	TYP	MAX	
	+24		V
+7.5	130	+40	V
		200	μA
		250	μA


Input isolation

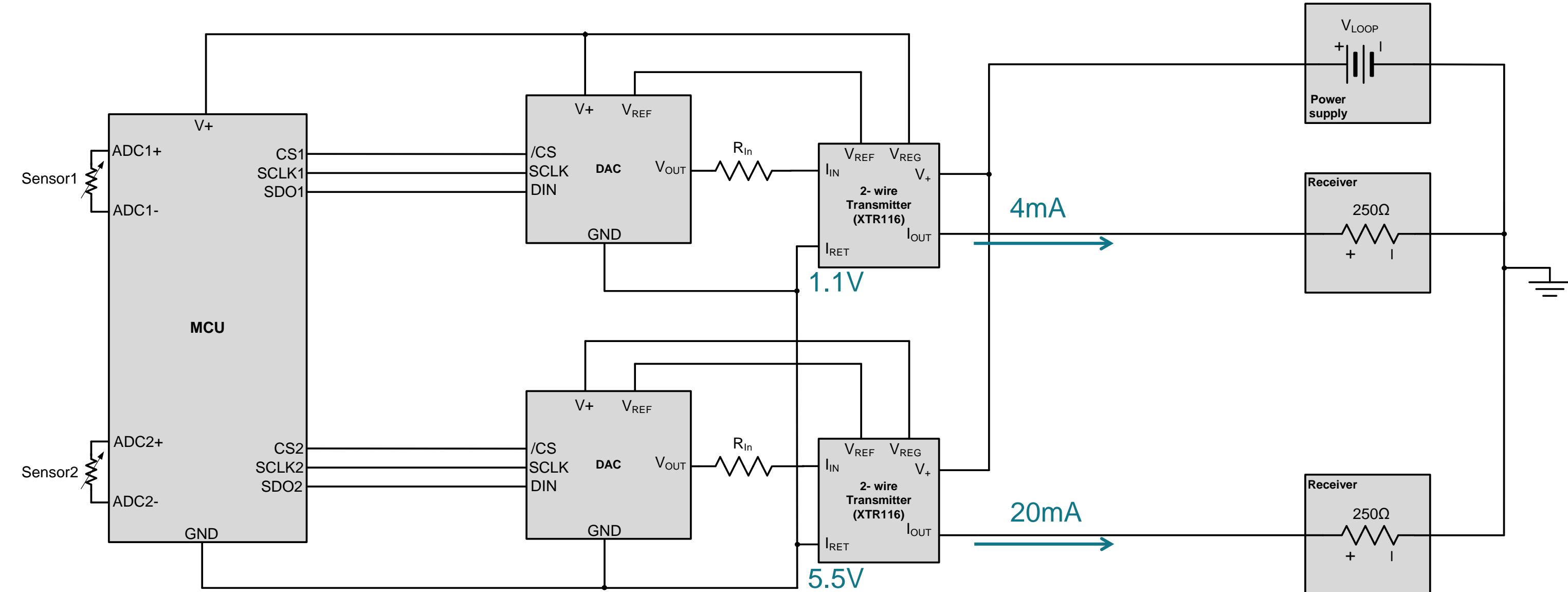

Input isolation

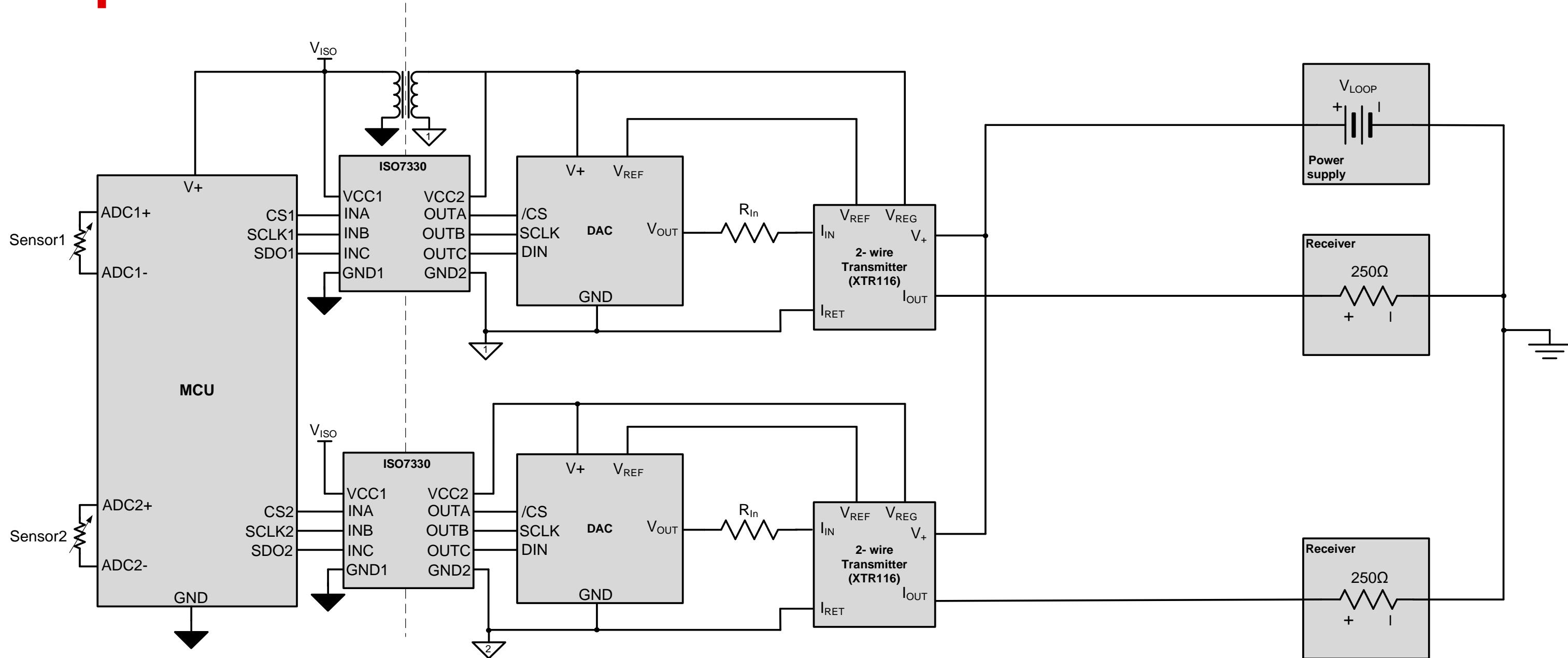

Input isolation

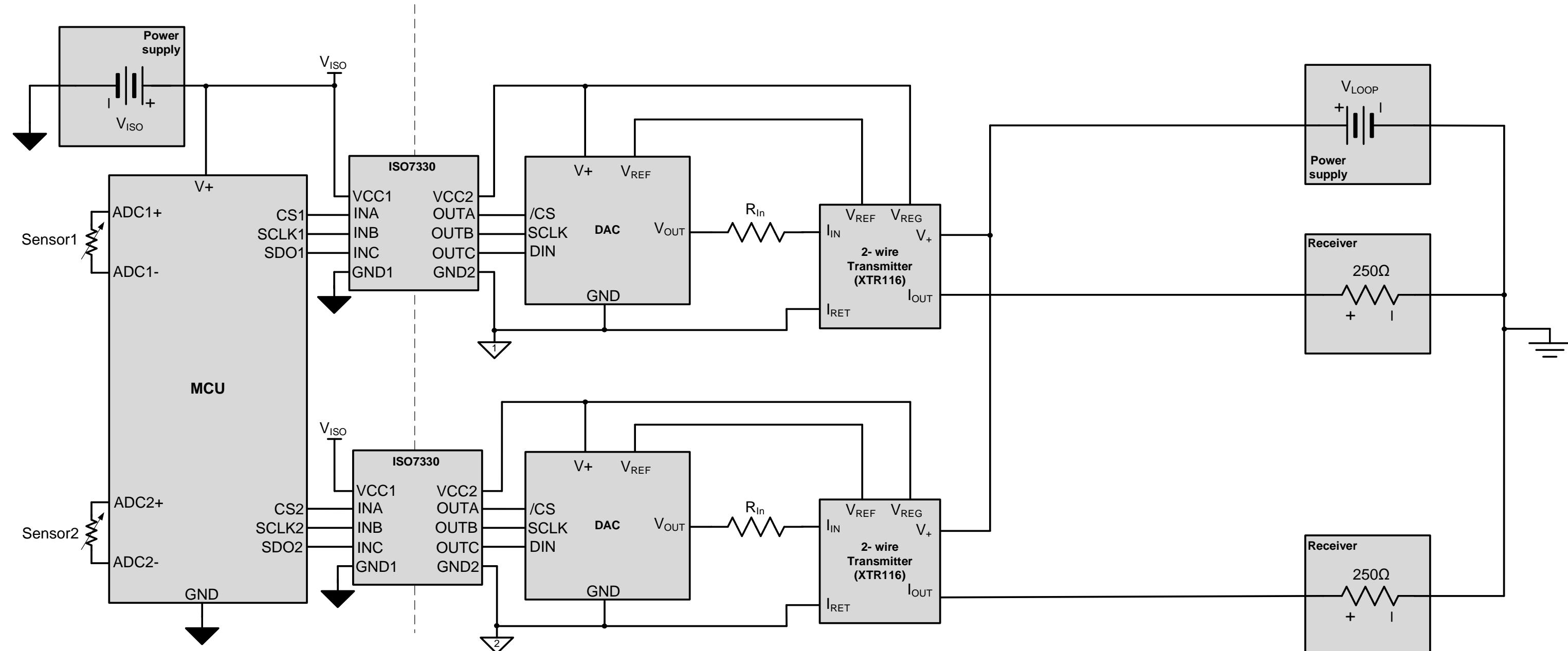

XTR parts

Part	Description	Loop Voltage (V)	Full-Scale Input Range	Reference	Regulator	Gain
XTR101	IA + Current Excitation	11.6-40	Settable	Current reference	-	Settable
XTR115	IIN to IOUT Converter. External Resistor Scales VIN to IIN	7.5-36	40µA to 200µA	2.5V	5V	100A/A
XTR116	IIN to IOUT Converter. External Resistor Scales VIN to IIN	7.5-36	40µA to 200µA	4.096V	5V	100A/A
XTR117	IIN to IOUT Converter. External Resistor Scales VIN to IIN	7.5-40	40µA to 200µA	-	5V	100A/A

XTR parts

Part	Description	Sensor Excitation	Loop Voltage (V)	Nonlinearity Correction	Regulator	Gain
XTR105	100Ω RTD Conditioner	Two 800µA	7.5-36	40:1 improvement	5.1V	Settable
XTR112	1kΩ RTD Conditioner	Two 250µA	7.5-36	40:1 improvement	5.1V	Settable
XTR106	Bridge Conditioner	5V and 2.5V	7.5-36	20:1 improvement	5.1V	Settable
XTR108	Smart Programmable RTD or Bridge Conditioner	Settable	7.5-36	40:1 improvement	5.1V	Settable

**Thanks for your time!
Please try the quiz.**

To find more Current Transmitter technical resources and search products, visit:

www.ti.com/amplifier-circuit/special-function/4-20ma-signal-conditioners.html

Quiz: 2-wire 4-20mA Transmitters

TI Precision Labs – Current Loop Transmitters

Presented by Katlynne Jones
Prepared by Katlynne Jones

Quiz: 2-wire 4-20mA Transmitters || Question

1. Which statement about a 2-wire transmitter is false?
 - a) The transmitter, sensor, and input circuitry must consume less than 4mA of current
 - b) I_{RET} cannot be grounded to V_{LOOP}
 - c) Input isolation can be used to connect multiple 2-wire transmitters in parallel
 - d) The V_{LOOP} voltage needs to be greater than the compliance voltage


Quiz: 2-wire 4-20mA Transmitters || Answer

1. Which statement about a 2-wire transmitter is false?
 - a) The transmitter, sensor, and input circuitry must consume less than 4mA of current
 - b) I_{RET} cannot be grounded to V_{LOOP}
 - c) Input isolation can be used to connect multiple 2-wire transmitters in parallel
 - d) **The V_{LOOP} voltage needs to be less than the compliance voltage**

Quiz: 2-wire 4-20mA Transmitters || Question

2. Given the 2-wire transmitter below, what is the gain of the transmitter if R1 is 1975Ω and R2 is 25Ω ?

- a) 10
- b) 40
- c) 80
- d) 100

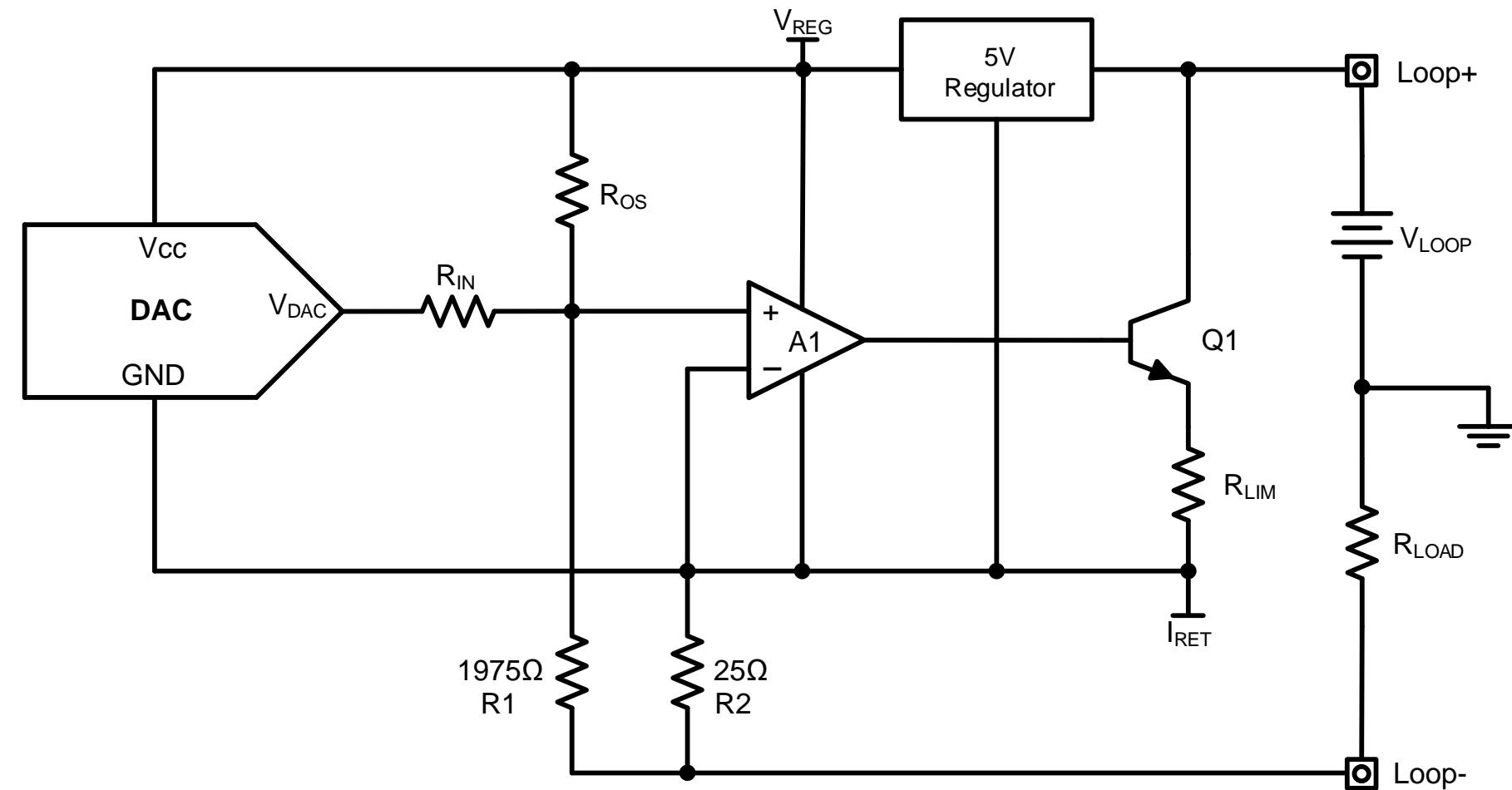


Quiz: 2-wire 4-20mA Transmitters || Answer

2. Given the 2-wire transmitter below, what is the gain of the transmitter if R1 is 1975Ω and R2 is 25Ω ?

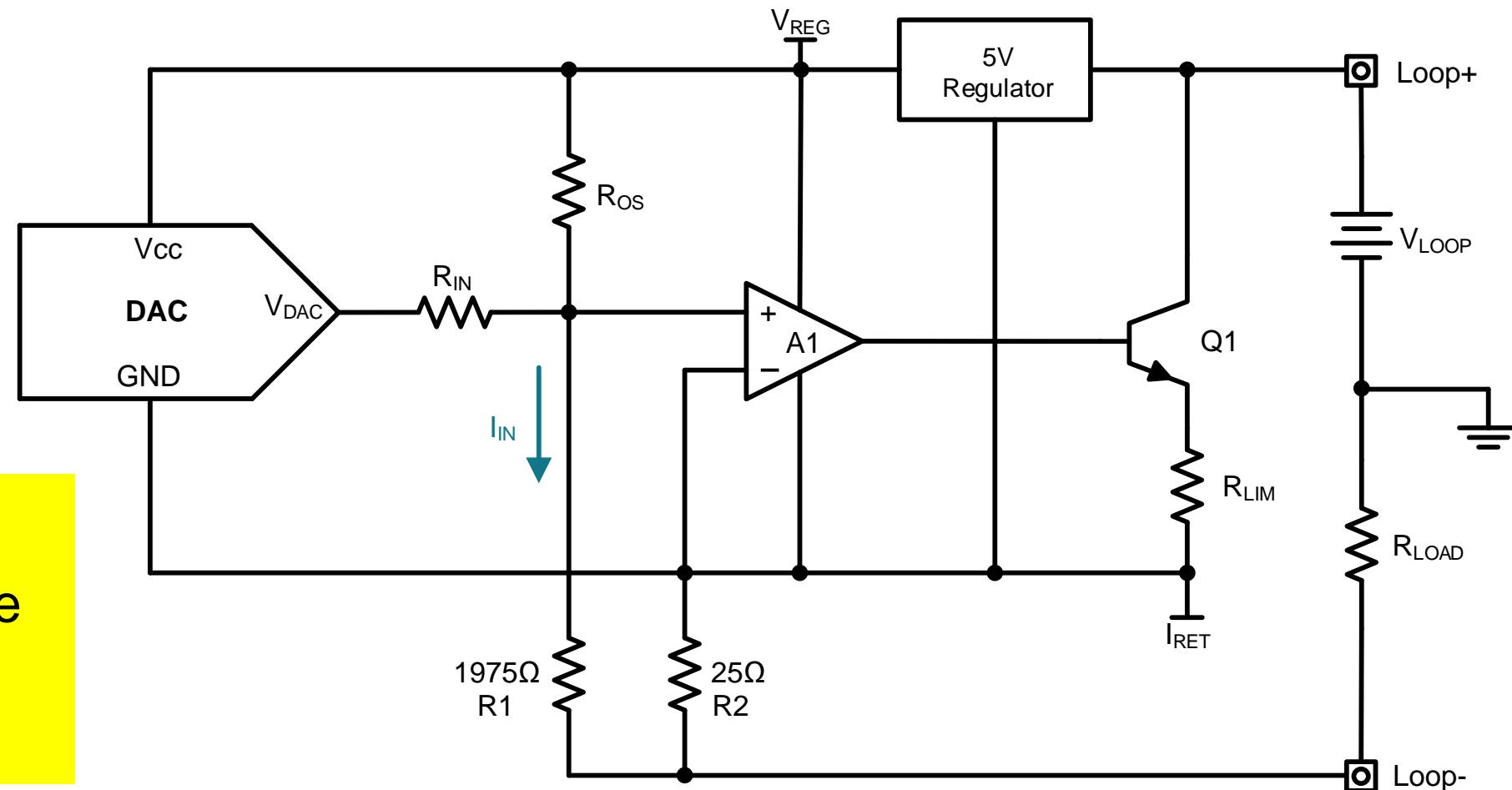- a) 10
- b) 40
- c) 80
- d) 100


The transfer function of this 2-wire transmitter is $I_{OUT} = I_{IN} * \left(1 + \frac{R_1}{R_2}\right)$. The gain is defined by $\left(1 + \frac{R_1}{R_2}\right)$.



Quiz: 2-wire 4-20mA Transmitters || Question

3. Given the 2-wire transmitter below, what value for R_{IN} and R_{OS} should be chosen to get an output of 4-20mA with V_{DAC} voltage of 0-5V?

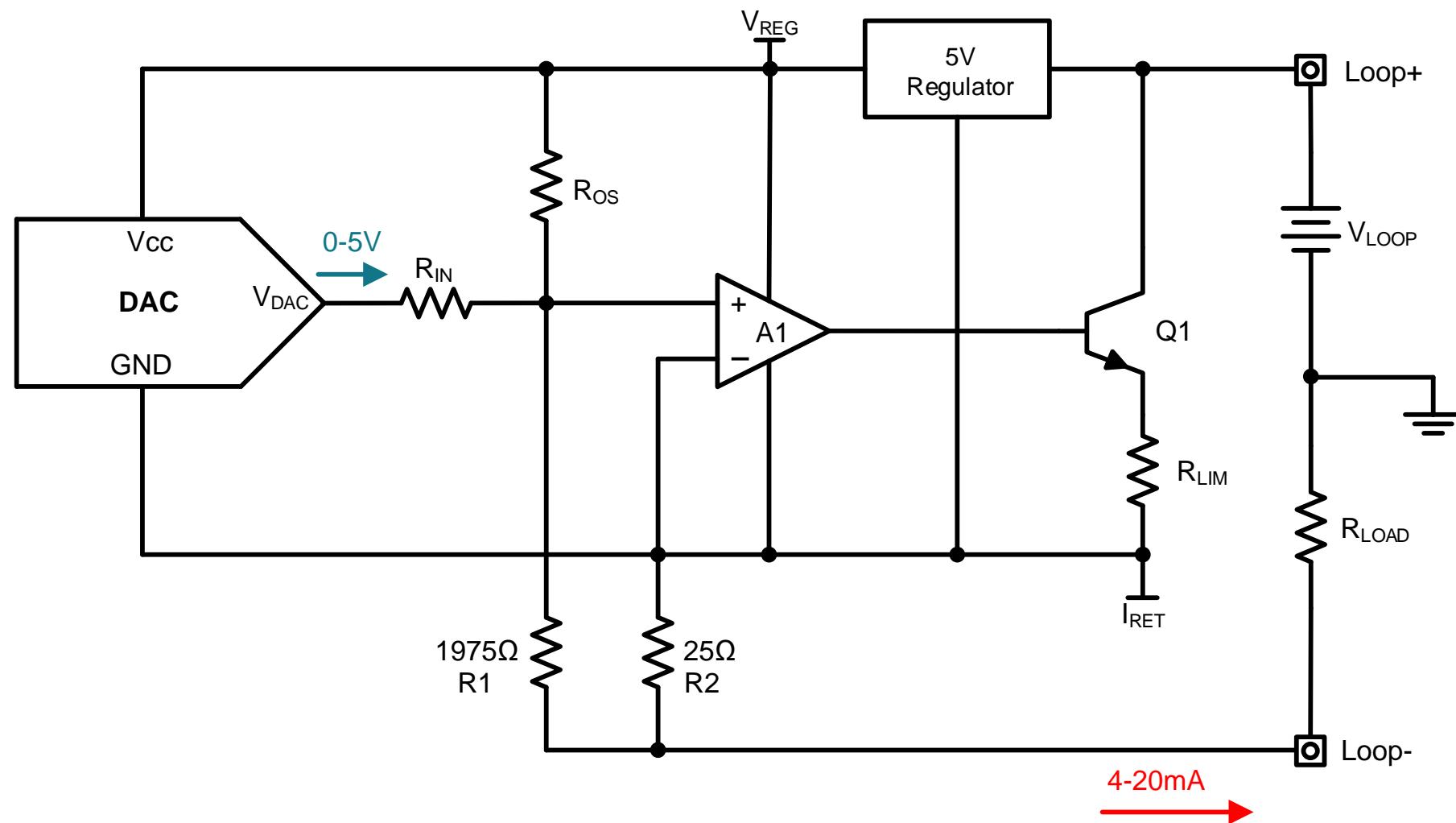- a) 5k Ω and 75k Ω
- b) 25k Ω and 100k Ω
- c) 30k Ω and 125k Ω
- d) 50k Ω and 150k Ω




Quiz: 2-wire 4-20mA Transmitters || Answer

3. Given the 2-wire transmitter below, what value for R_{IN} and R_{OS} should be chosen to get an output of 4-20mA with V_{DAC} voltage of 0-5V?

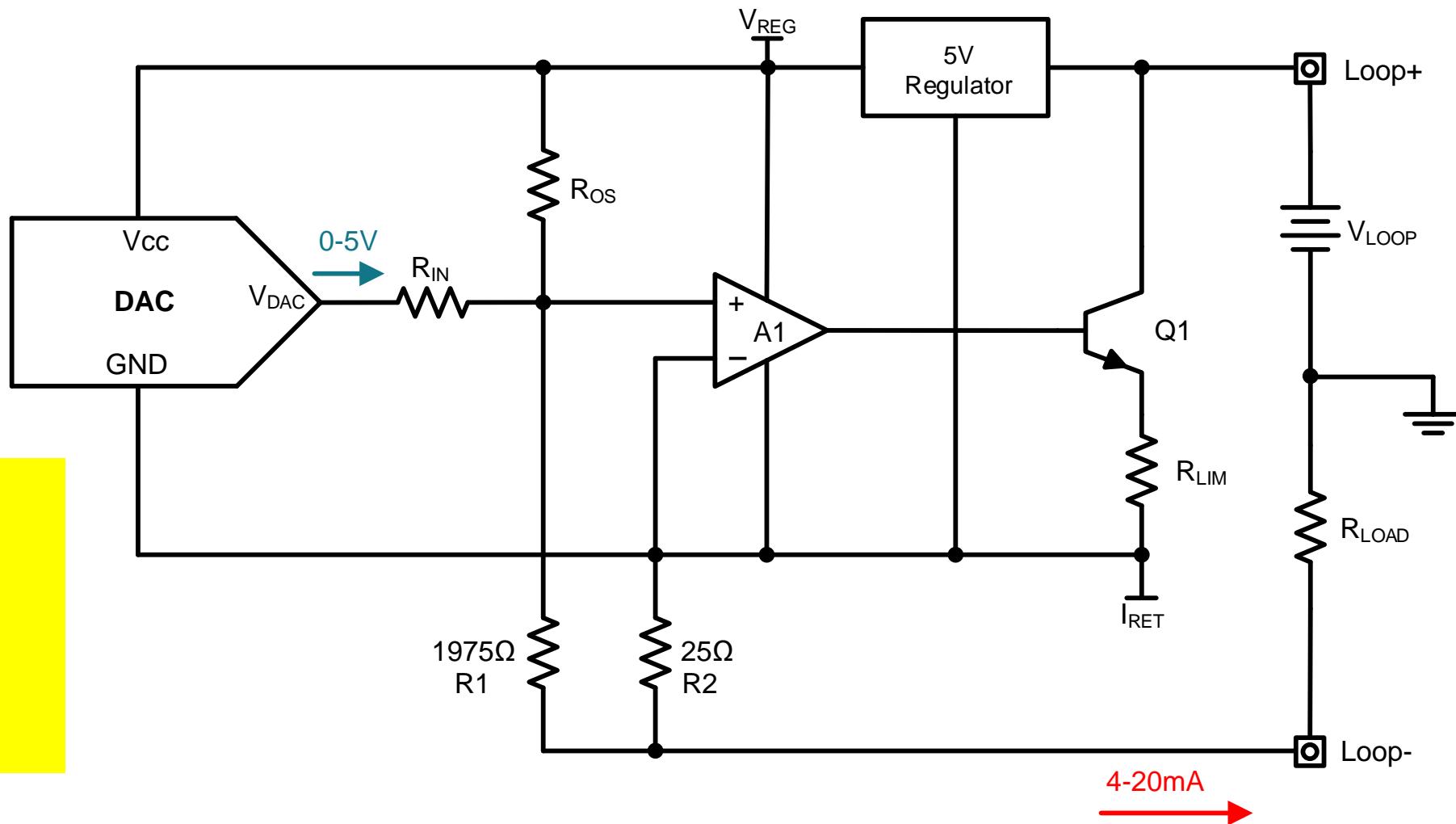- a) 5k Ω and 75k Ω
- b) 25k Ω and 100k Ω**
- c) 30k Ω and 125k Ω
- d) 50k Ω and 150k Ω


The input to this 2-wire transmitter is $I_{IN} = \left(\frac{V_{DAC}}{R_{IN}} + \frac{V_{REG}}{R_{OS}} \right)$. With a gain of 80 and a 5V regulator, the correct values for R_{IN} and R_{OS} are 25k Ω and 100k Ω .



Quiz: 2-wire 4-20mA Transmitters || Question

4. Due to the compliance voltage of the XTR116, what is the minimum V_{LOOP} that can be used if the wire resistance and load is as given in the figure and the expected transmitter output is 4-20mA.

- a) 10V
- b) 21V
- c) 36V
- d) 40V

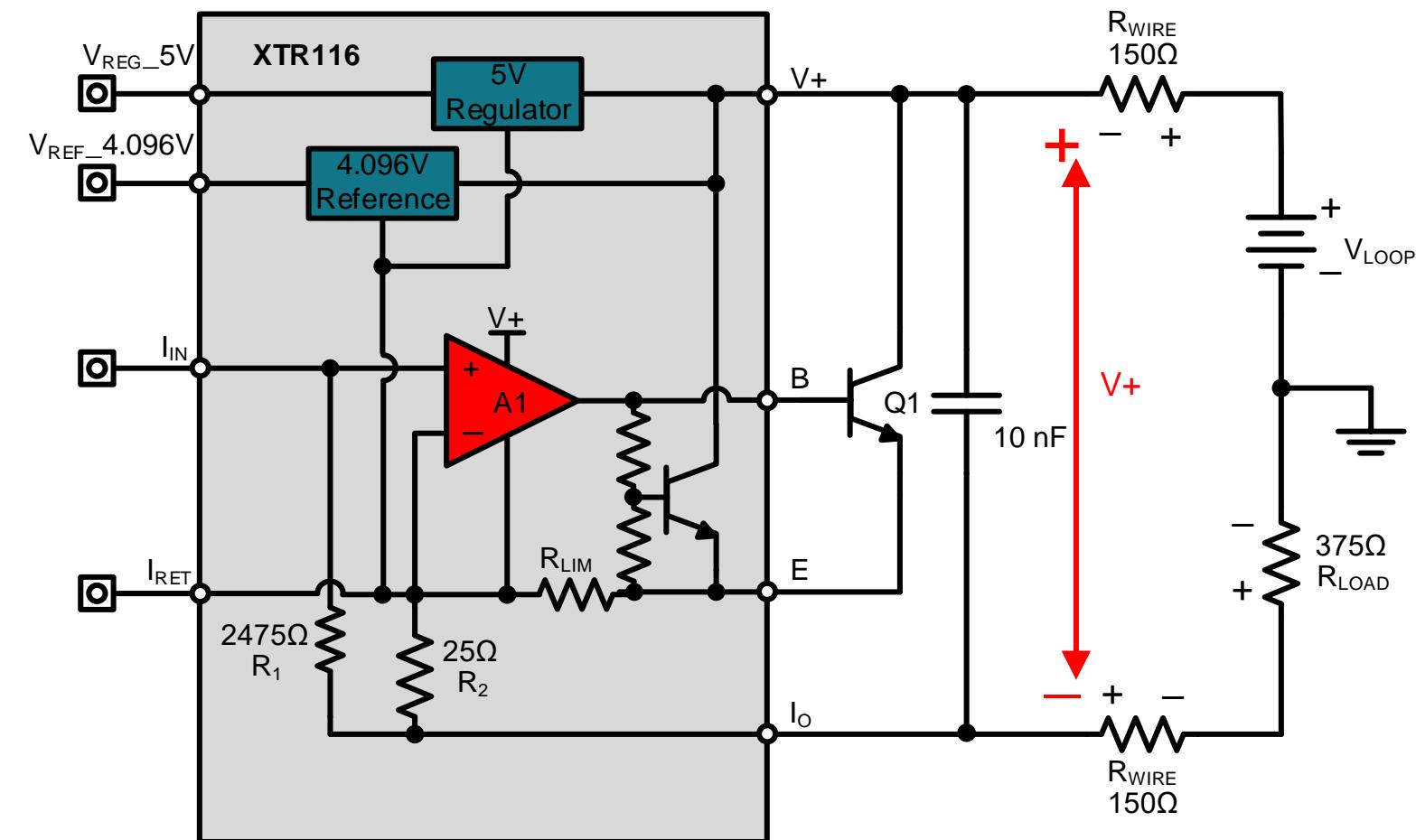

Quiz: 2-wire 4-20mA Transmitters || Answer

4. Due to the compliance voltage of the XTR116, what is the minimum V_{LOOP} that can be used if the wire resistance and load is as given in the figure and the expected transmitter output is 4-20mA.

- a) 10V
- b) 21V**
- c) 36V
- d) 40V


The XTR116 has a compliance voltage of 7.5V. This means that the VLOOP supply needs to be greater than the compliance voltage plus the max current and total resistance.

POWER SUPPLY	V+		MIN	TYP	MAX	*	*	*	*	*	*	V
			+7.5	+24	+36							
Specified Voltage Range				200	250	*	*	*	*	*	*	V
Quiescent Current				240	300							μA
Over Temperature, -40°C to +85°C												μA

Quiz: 2-wire 4-20mA Transmitters || Question

5. With a current input of 35 μ A and R_{OS} , and R_{LOAD} as shown in the figure, what is the voltage at I_{RET} referred to ground?

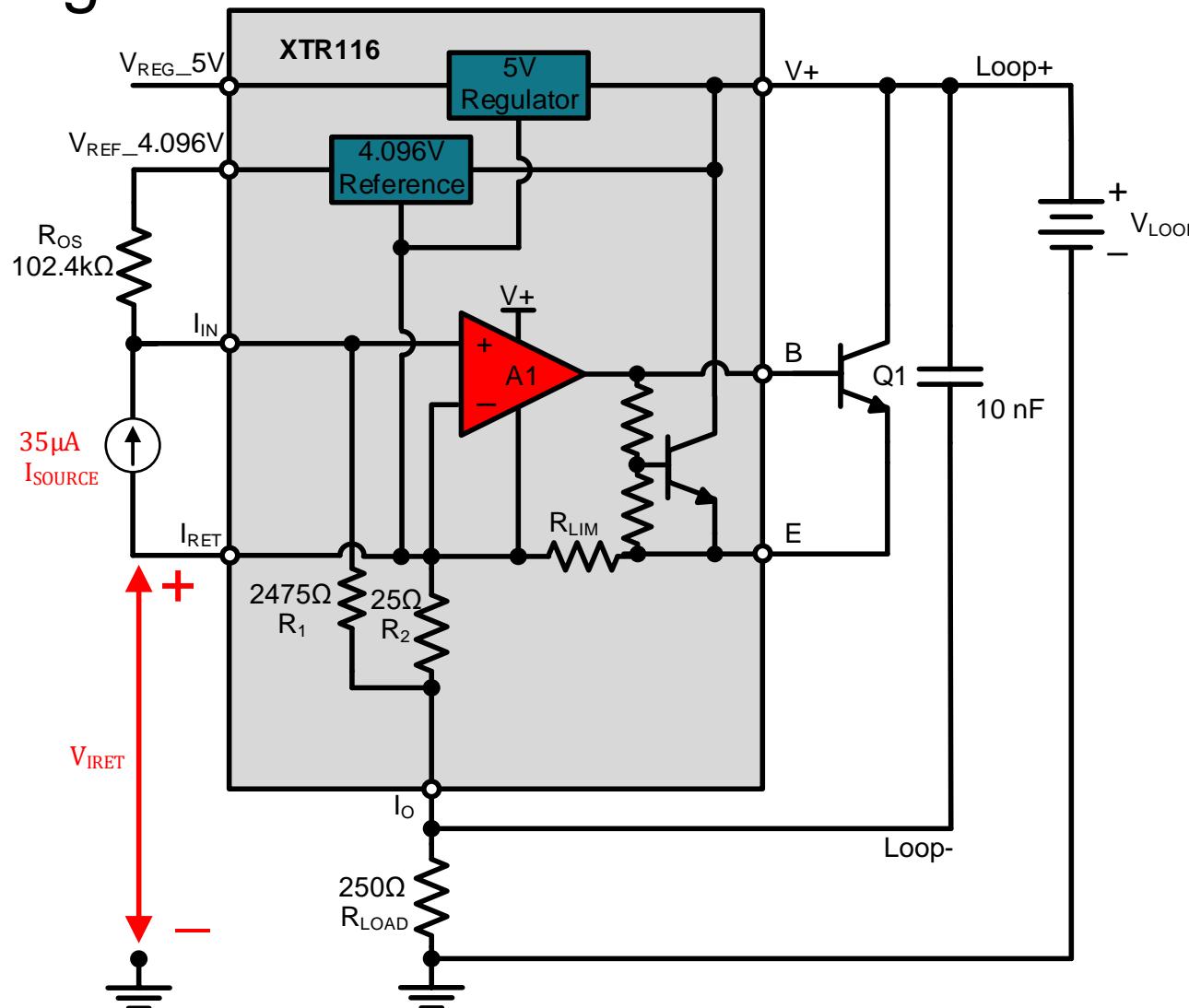- a) 1.65V
- b) 2.06V
- c) 3.79V
- d) 4.54V




Quiz: 2-wire 4-20mA Transmitters || Answer

5. With a current input of 35 μ A and R_{OS} , and R_{LOAD} as shown in the figure, what is the voltage at I_{RET} referred to ground?

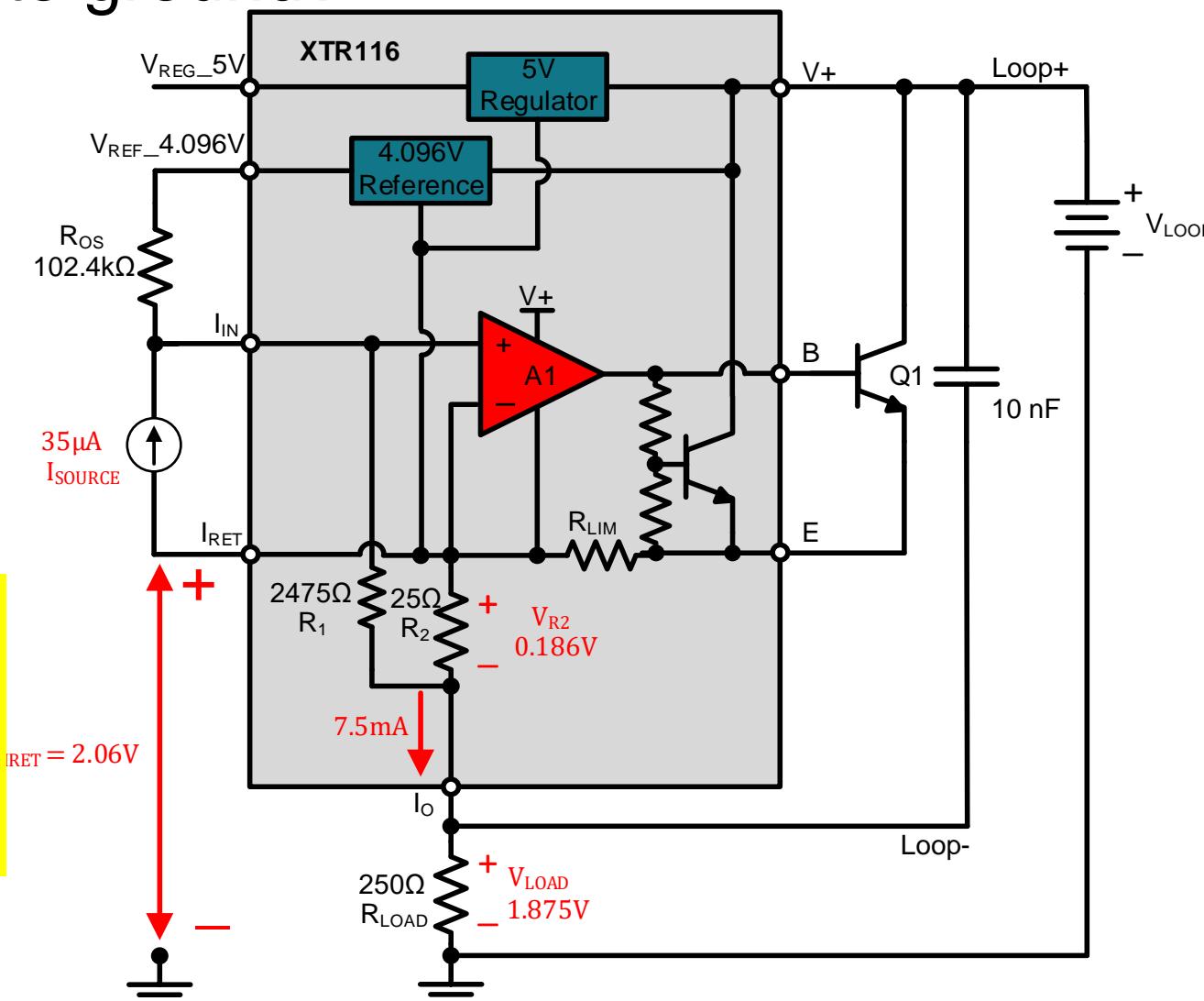- a) 1.65V
- b) 2.06V**
- c) 3.79V
- d) 4.54V

The voltage at I_{RET} is given by $V_{I_{RET}} = V_{R2} + V_{LOAD}$. V_{R2} is calculated to be 0.186V and V_{LOAD} is calculated to be 1.875V, so $V_{I_{RET}}$ is 2.06V



Thanks for your time!

To find more Current Transmitter technical resources and search products, visit:

<https://www.ti.com/amplifier-circuit/special-function/4-20ma-signal-conditioners.html>