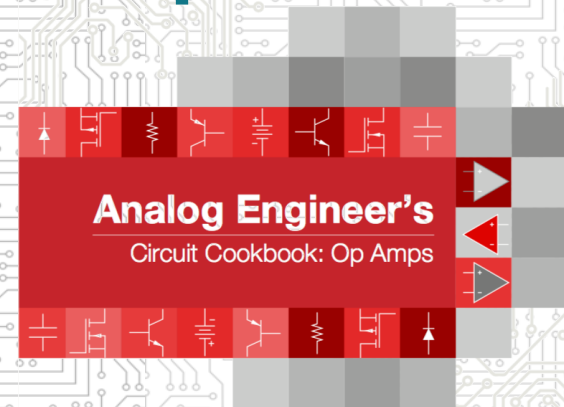


# How to Design Non-Inverting Microphone Pre-Amplifier Circuit


General Purpose Amplifiers

[www.ti.com/general-amps](http://www.ti.com/general-amps)

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)





# Circuit Description

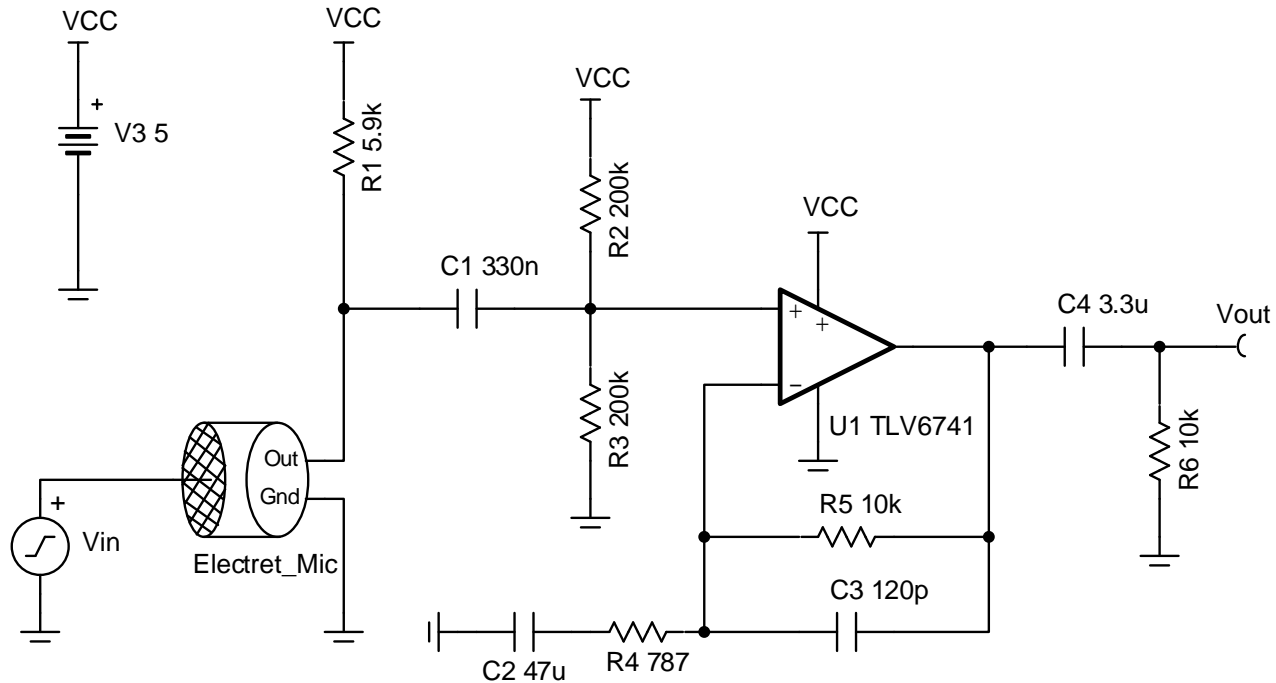

# Design Steps


Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

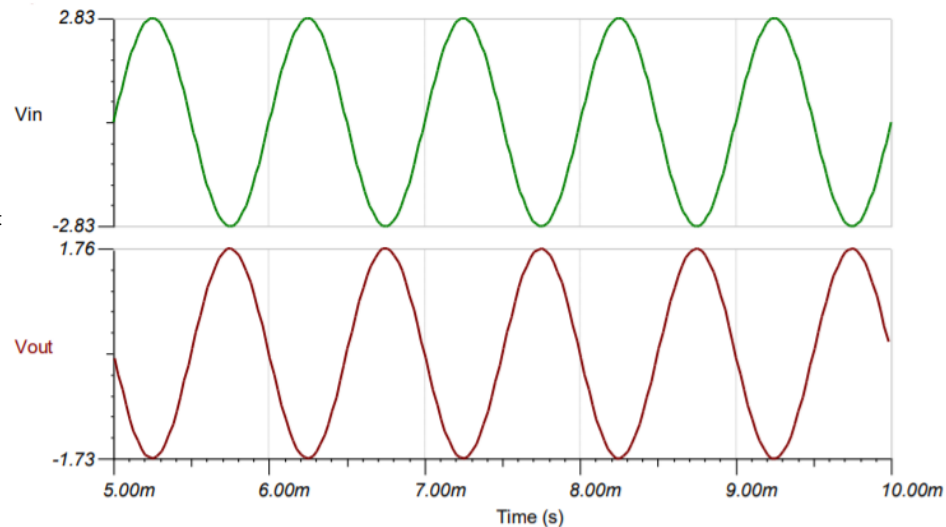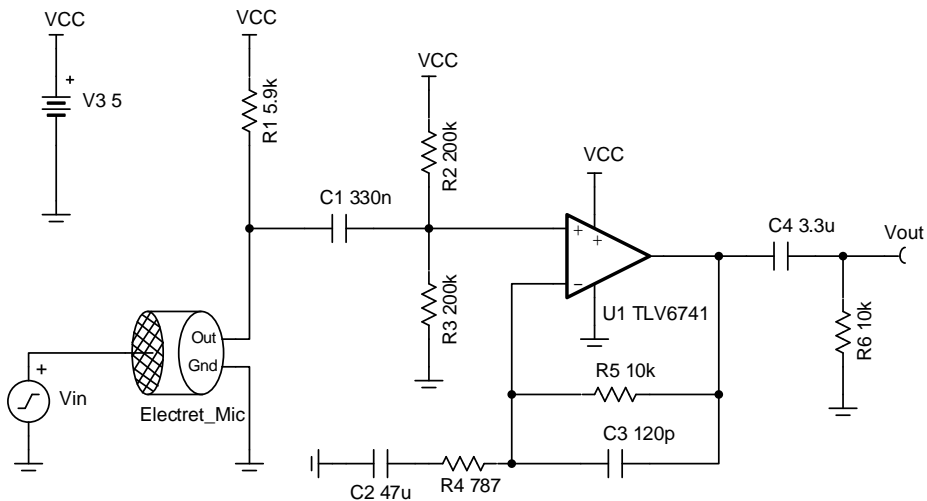

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)

# Design Steps


Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

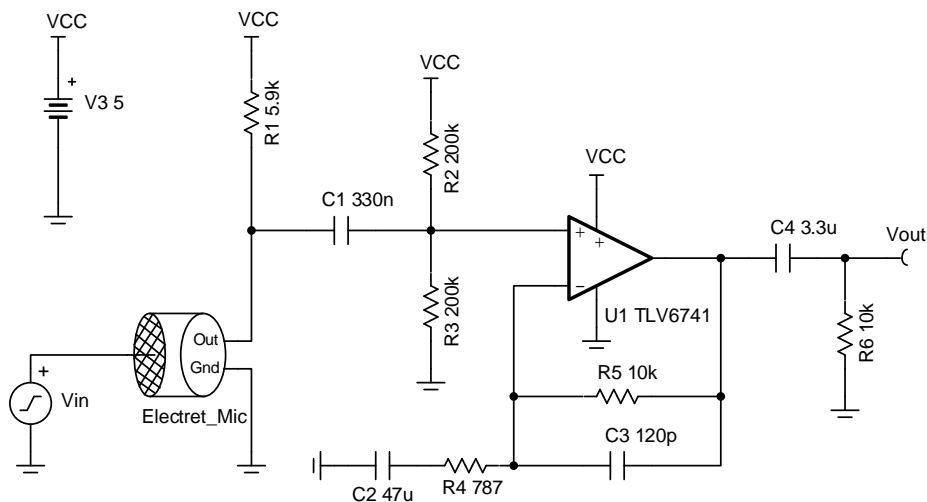

Microphone Parameter	Value
Sensitivity @94dB SPL (1Pa)	-35 dBV
Current Consumption (Max)	0.5mA
Impedance	2.2kΩ
Standard Operating Voltage	2Vdc

# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

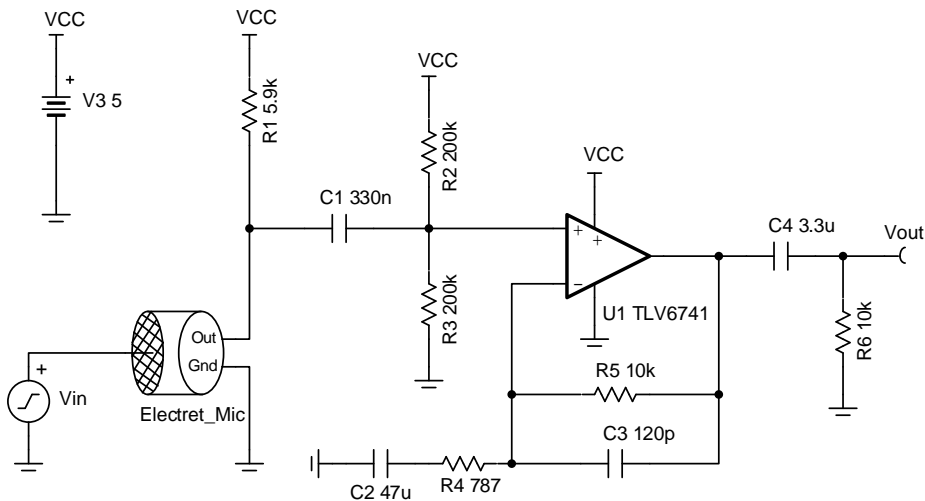


$$10^{\frac{-35dB}{20}} = 17.78 \frac{mV}{Pa}$$

$$\frac{17.78 \frac{mV}{Pa}}{2.2k\Omega} = 8.083 \frac{\mu A}{Pa}$$

$$I_{Max} = 8.083 \frac{\mu A}{Pa} \times 2Pa = 16.166\mu A$$

# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

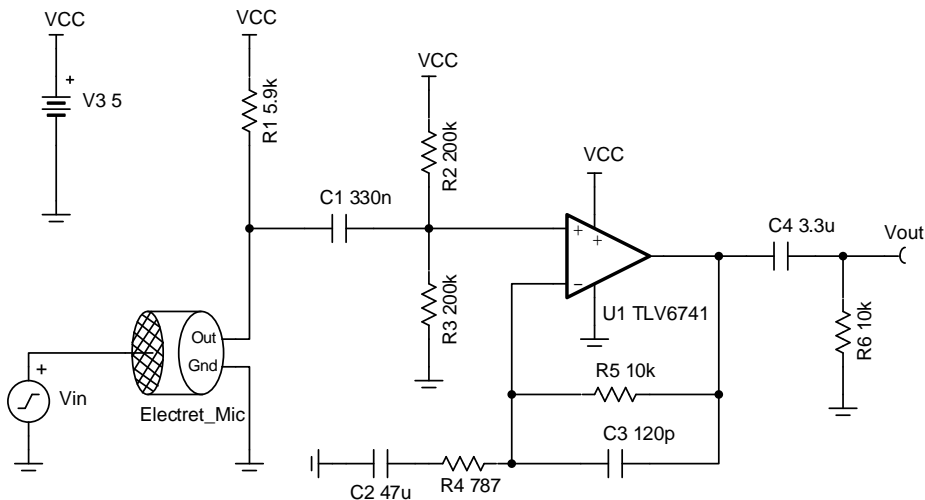


$$R_1 = \frac{V_{cc} - V_{mic}}{I_s}$$

$$R_1 = \frac{5V - 2V}{0.5mA} = 6k\Omega \approx 5.9k\Omega$$

# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

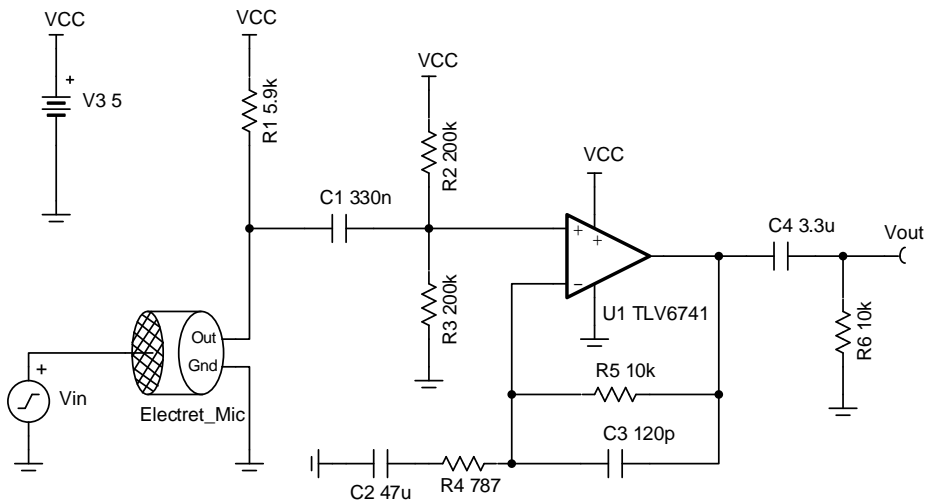


$$R_{eq} = R_2 || R_3 > 10 \times R_1$$

$$R_2 = R_3 = 200k\Omega$$

# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

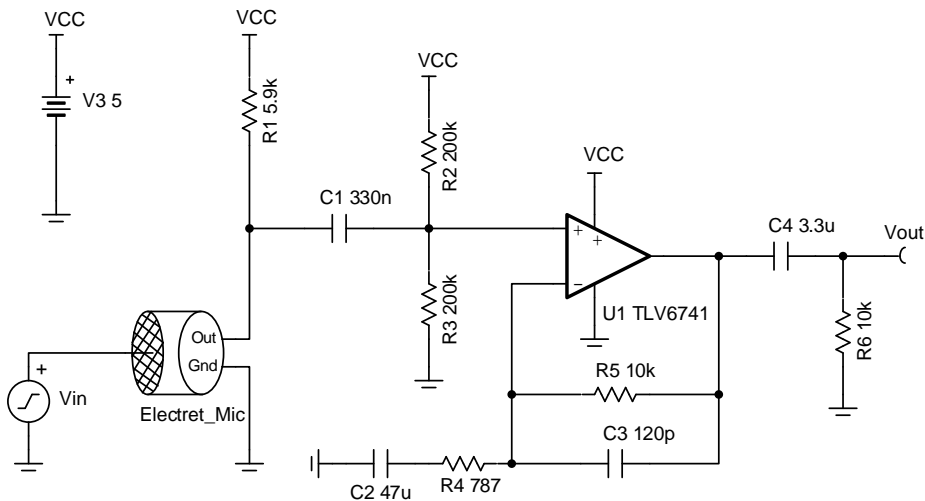

$$R_{in} = R_1 \parallel R_{eq} = 5.9k\Omega \parallel 100k\Omega = 5.571k\Omega$$


$$V_{in} = I_{max} \times R_{in}$$

$$V_{in} = 16.166\mu A \times 5.571k\Omega = 90.067mV$$



# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

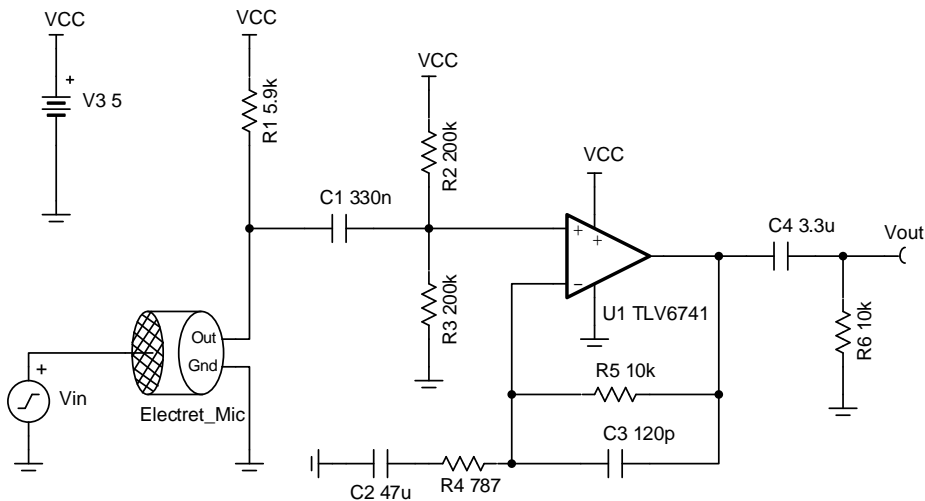

$$Gain = \frac{V_{outmax}}{V_{in}} = \frac{1.228V_{rms}}{90.067mV_{rms}} = 13.634 \frac{V}{V}$$


$$R_4 = \frac{R_5}{Gain - 1}$$

$$R_5 = 10k\Omega$$

$$R_4 = 791\Omega \approx 787\Omega$$

# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

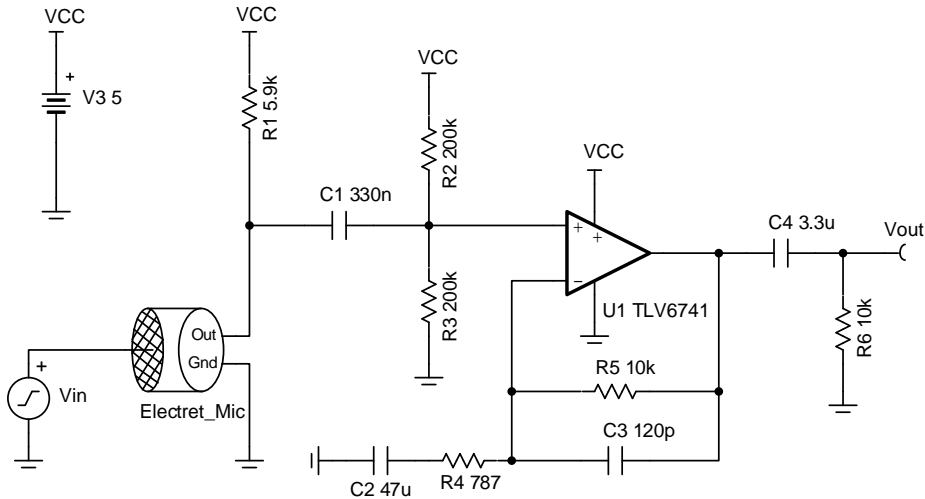

$$G_{pole1} = 10^{-0.5/3}$$

$$f_c = f \times \sqrt{\left(\frac{1}{G_{pole1}} - 1\right)} = 3.956\text{Hz}$$


$$C_1 = \frac{1}{2\pi \times R_{eq} \times f_c} = 0.402\mu\text{F} \approx 0.33\mu\text{F}$$

$$C_2 = \frac{1}{2\pi \times R_4 \times f_c} = 51.121\mu\text{F} \approx 47\mu\text{F}$$

$$C_4 = \frac{1}{2\pi \times R_6 \times f_c} = 4.023\mu\text{F} \approx 3.3\mu\text{F}$$

# Design Steps

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

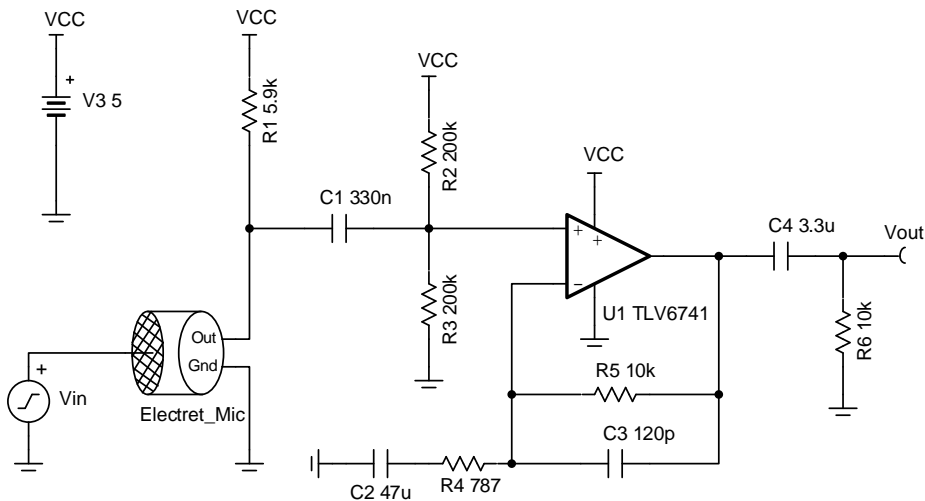

$$G_{pole2} = 10^{\frac{-0.1}{20}}$$



$$f_p = \frac{f}{\sqrt{\left(\frac{1}{G_{pole2}} - 1\right)}} = 131.044kHz$$

$$C_3 = \frac{1}{2\pi \times R_5 \times f_p} = 121.451pF \approx 120pF$$

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)



# AC Results

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

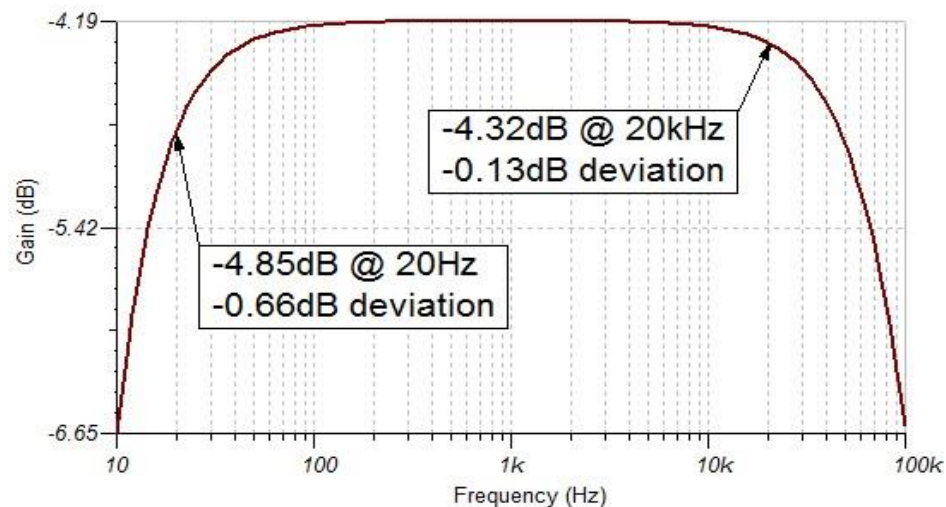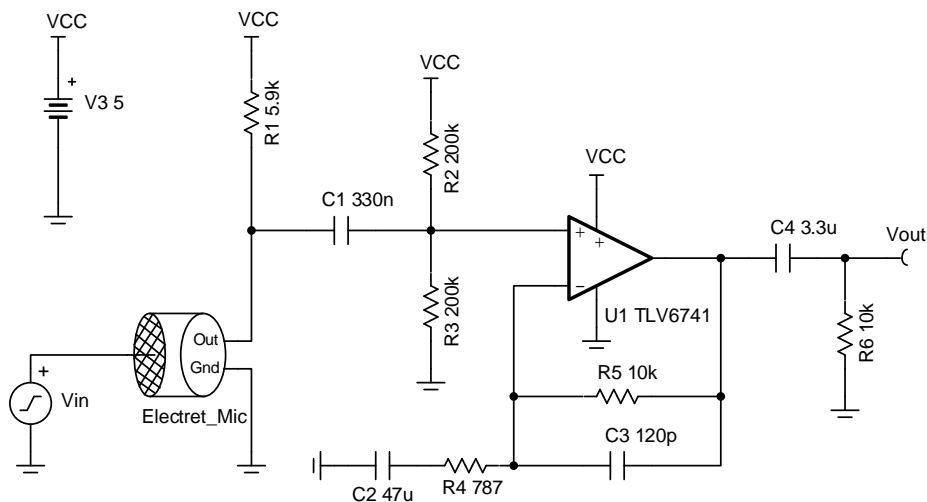

# Noise Results

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

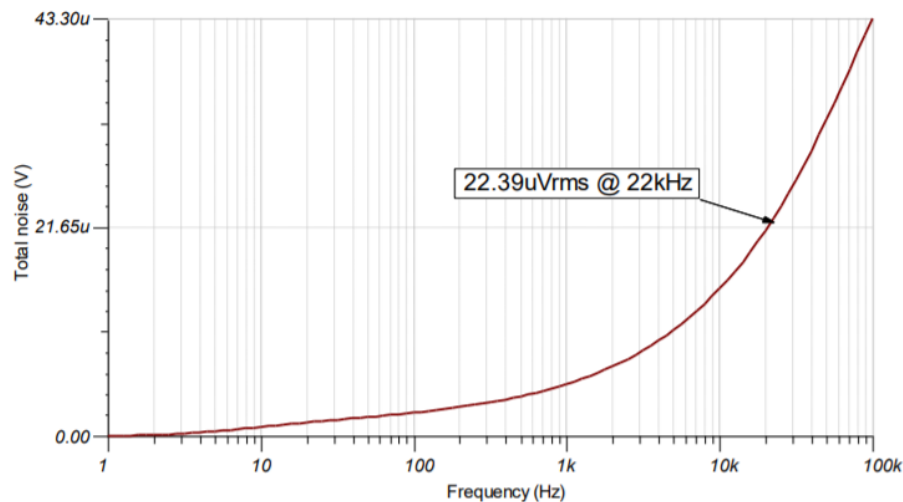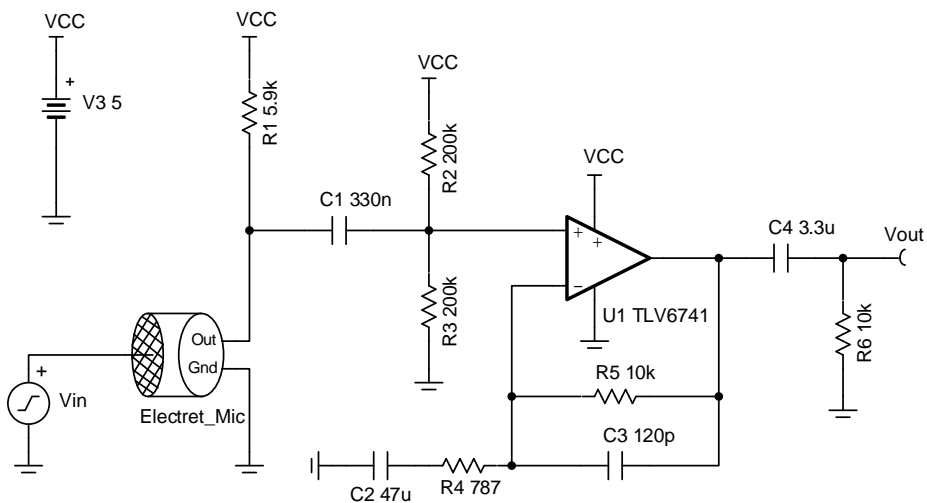


# Design Notes

Input Pressure (Max)	Output Voltage (Max)	Supply		Freq. Response Deviation	
100dB SPL (2Pa)	1.228V <sub>rms</sub>	V <sub>cc</sub>	V <sub>ee</sub>	@20Hz	@20kHz
		5V	0V	-0.5dB	-0.1dB

## Design Notes:

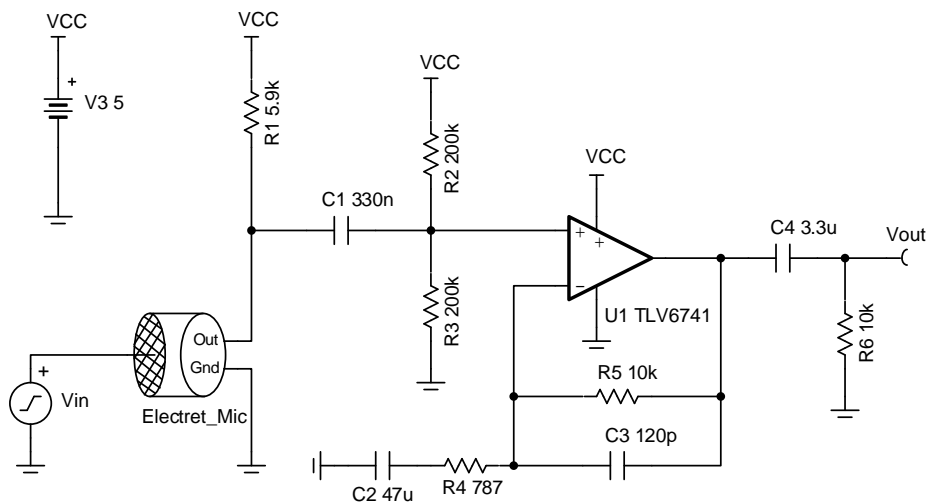1. Use low-K capacitors (tantalum, C0G, and so forth) and thin film resistors help to decrease distortion.
2. Use a battery to power this circuit to eliminate distortion caused by switching power supplies.
3. The common mode voltage is equal to the DC bias voltage plus any variation caused by the microphone output voltage. For op amps with a complementary pair input stage it is recommended to keep the common mode voltage away from the cross over region to eliminate the possibility of cross over distortion.



# Design Resources

## EE Cookbook: Op Amp

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)

Step-by-step circuit design of common op amp building block circuits.

## TI Designs

[www.TI.com/tidesigns](http://www.TI.com/tidesigns)

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

## Analog Engineer's Pocket Reference

[www.TI.com/analogrefguide](http://www.TI.com/analogrefguide)

PDF, iTunes app and hardcopy available  
PCB, analog, mixed signal design formulae  
Conversions, tables, equations

## TI Precision Labs

[www.TI.com/precisionlabs](http://www.TI.com/precisionlabs)

Quiz questions, problems, solutions  
Labs and evaluation module (EVM) available

## TINA-TI™ simulation software

[www.TI.com/tool/tina-ti](http://www.TI.com/tool/tina-ti)

Complete SPICE simulator DC, AC, transient, noise analysis  
Schematic entry and post-processor for waveform math

## DIYAMP-EVM

[www.TI.com/DIYAMP-EVM](http://www.TI.com/DIYAMP-EVM)

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

## The Signal

[www.TI.com/thesignal](http://www.TI.com/thesignal)

PDF, iTunes app and hardcopy available  
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

## Analog Wire Blog

[www.TI.com/analogwire](http://www.TI.com/analogwire)

Technical blogs written by analog experts  
Tips, tricks, and design techniques

## TI E2E™ Community

[www.TI.com/e2e](http://www.TI.com/e2e)

Support forums for all TI products

## Op Amp Parametric Quick Search

[www.TI.com/amplifiers](http://www.TI.com/amplifiers)

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

## Op Amp Parametric Cross-Reference

[www.TI.com/opampcrossreference](http://www.TI.com/opampcrossreference)

Find similar TI op amps using competitive part numbers

[www.ti.com/circuitcookbooks](http://www.ti.com/circuitcookbooks)



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)