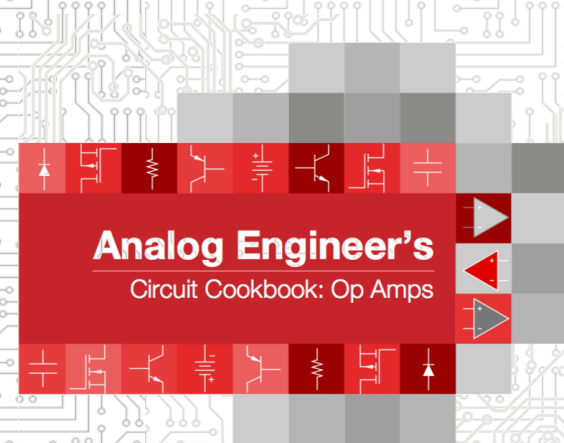


How to Design Inverting Amplifier Circuit


General Purpose Amplifiers

www.ti.com/general-amps

www.ti.com/circuitcookbooks




Circuit Description

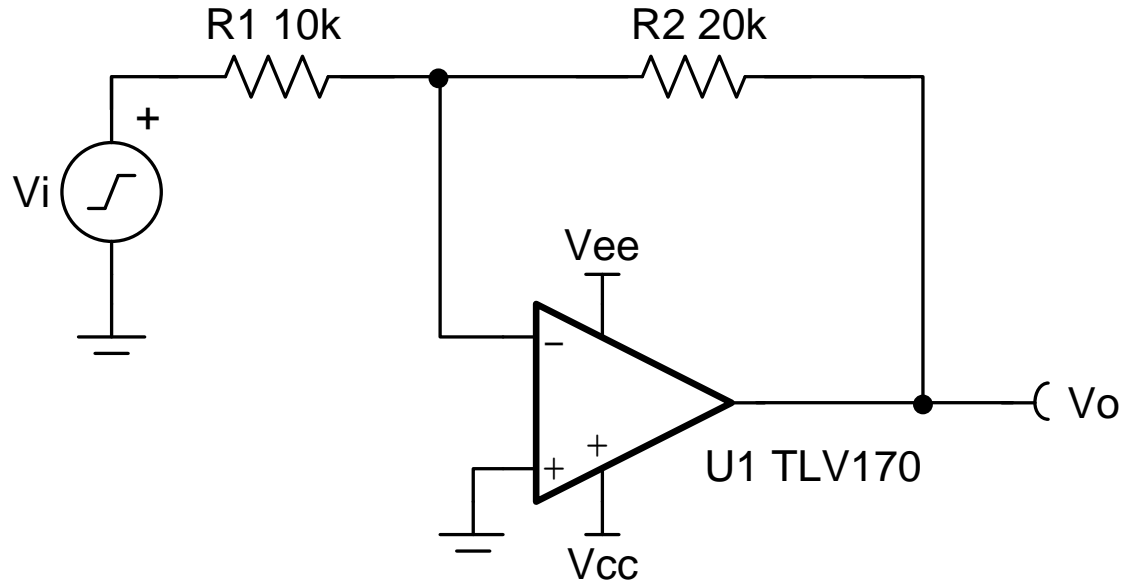

$$V_o = -\frac{R_2}{R_1} \times V_i$$

Design Steps


| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

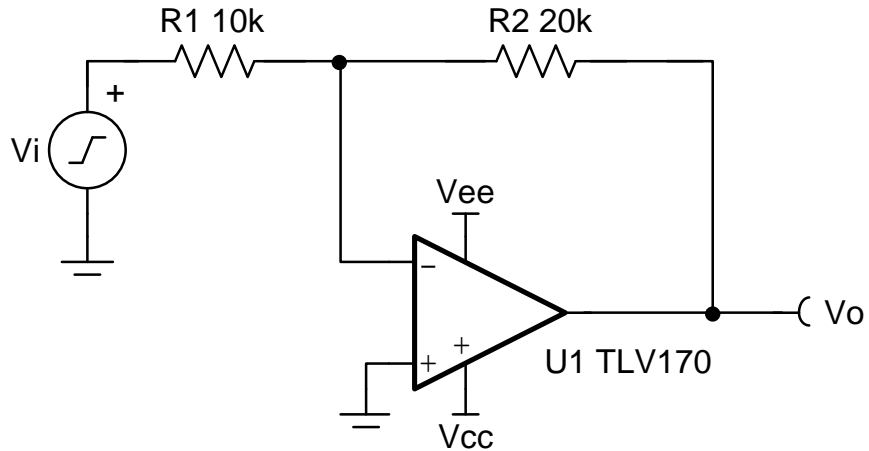

$$V_o = -\frac{R_2}{R_1} \times V_i$$

Design Steps

| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

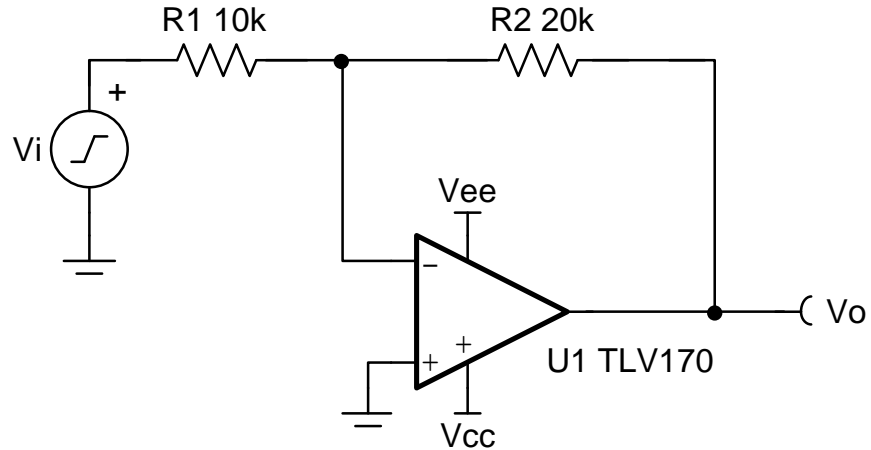


$$G = \frac{V_{oMax}}{V_{iMin}}$$

$$G = \frac{14V}{-7V} = -2V/V$$

Design Steps

| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

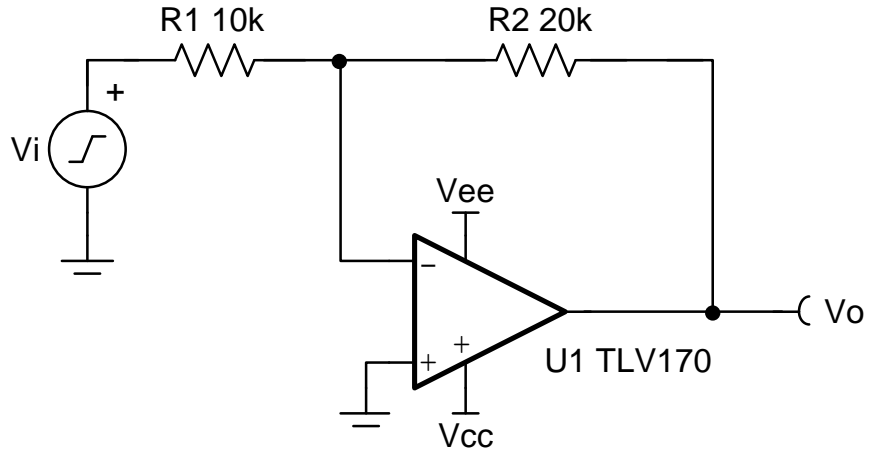

$$G = -\frac{R_2}{R_1}$$



$$R_2 = -G \times R_1 \rightarrow G \times R_1$$

$$R_1 = 10k\Omega$$

$$R_2 = 20k\Omega$$



DC Results

| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{CC} | V_{EE} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

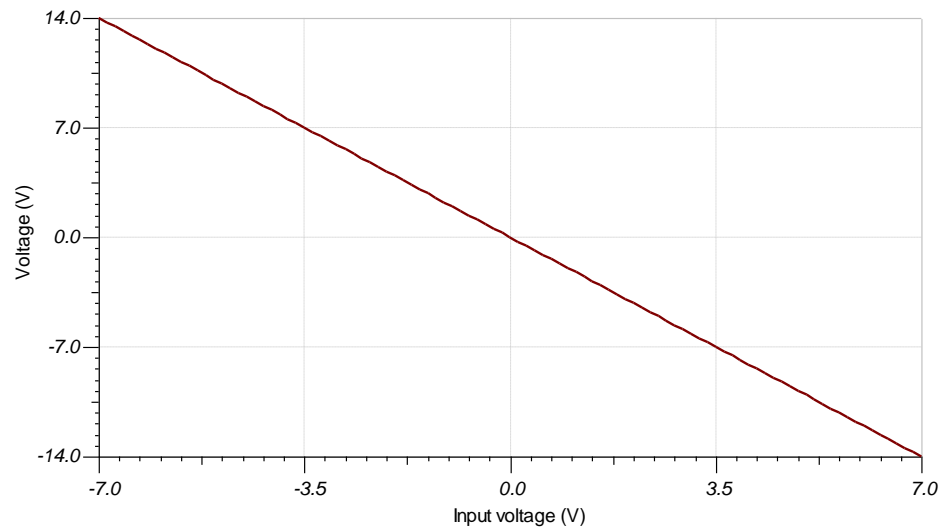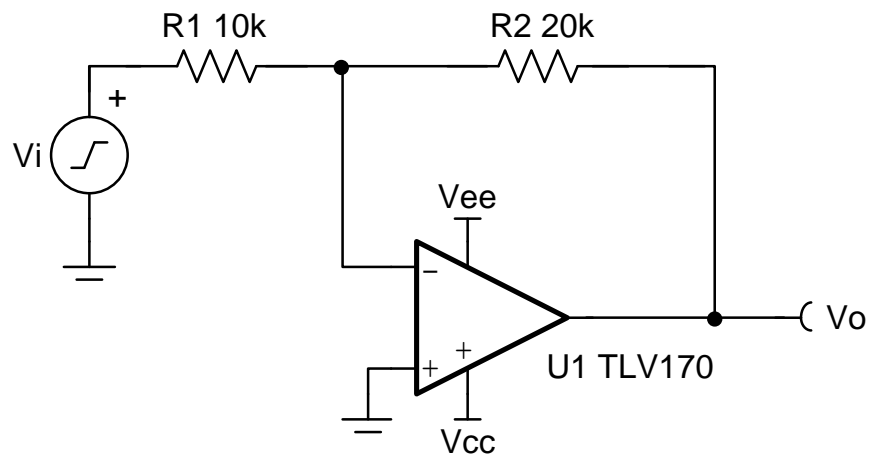



Transient Results

| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

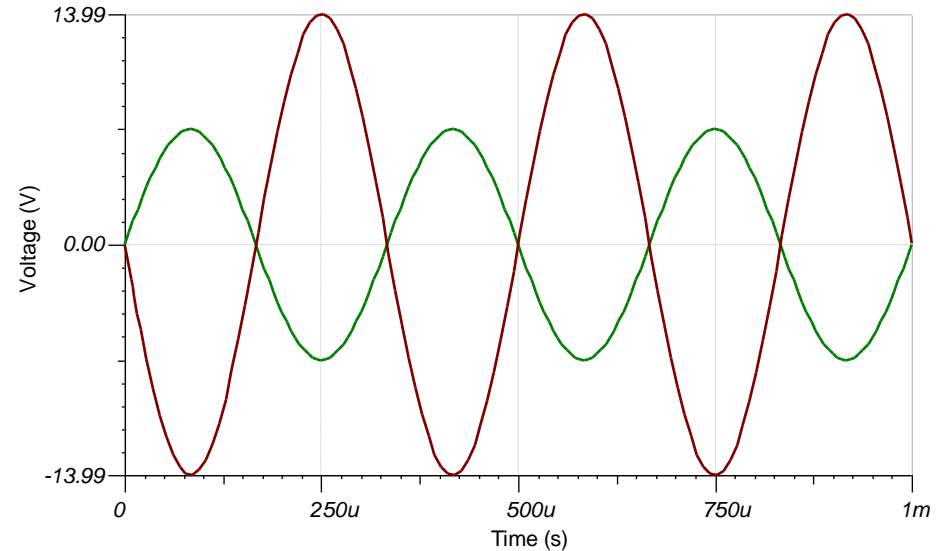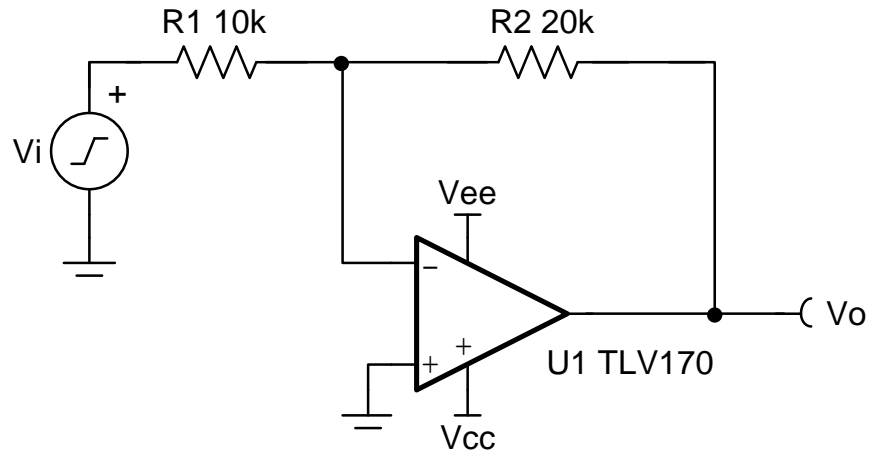


AC Results

| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

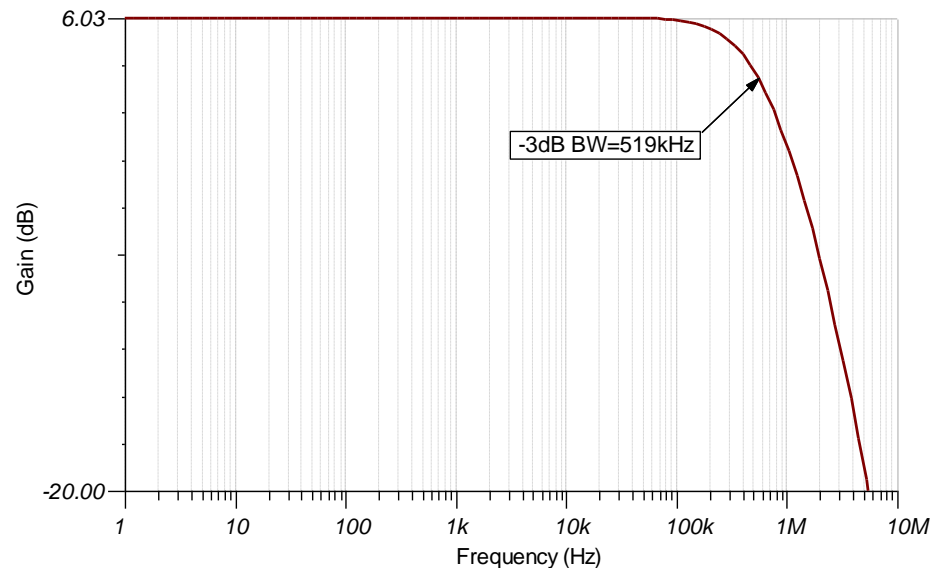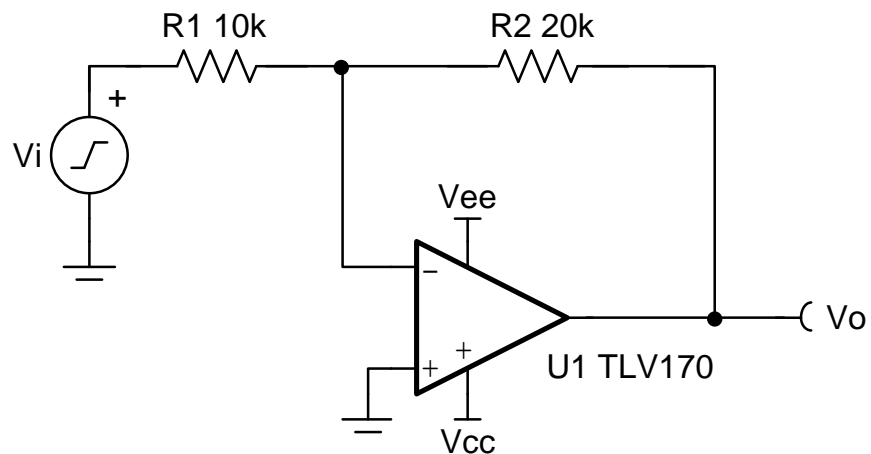

Design Notes

| Input | | Output | | Supply | | Freq. |
|------------|------------|------------|------------|----------|----------|-------|
| V_{iMin} | V_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | f |
| -7V | 7V | -14V | 14V | 15V | -15V | 3kHz |

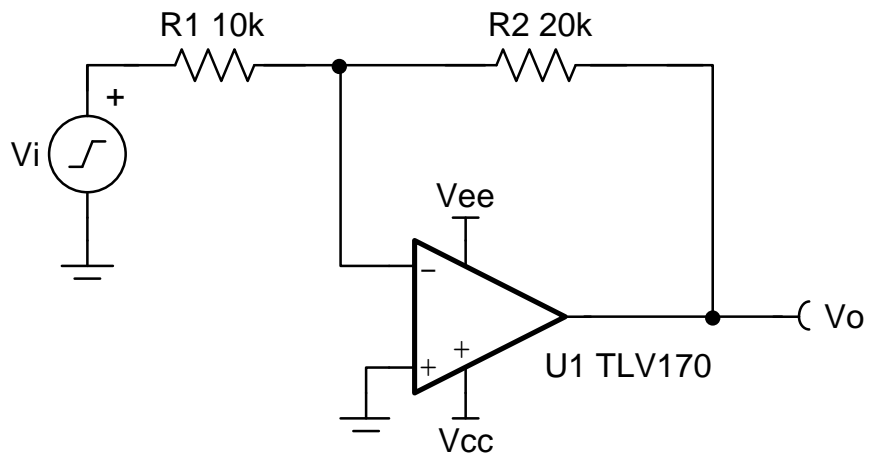

Design Notes:

1. Small-signal bandwidth is determined by the noise gain (or non-inverting gain) and op amp gain-bandwidth product (GBP). A capacitor in parallel with R2 helps filter the input and stabilize the circuit.
2. Large signal performance can be limited by slew rate. Therefore, check the maximum output swing versus frequency plot in the data sheet to minimize slew-induced distortion.
3. The common-mode voltage is equal to the voltage at the non-inverting input. In this circuit the common-mode voltage does not vary with input voltage.

Design Resources

EE Cookbook: Op Amp

www.ti.com/circuitcookbooks

Step-by-step circuit design of common op amp building block circuits.

TI Designs

www.TI.com/tidesigns

Ready-to-use reference designs with theory, calculations, simulations schematics, PCB files, bench test results

Analog Engineer's Pocket Reference

www.TI.com/analogrefguide

PDF, iTunes app and hardcopy available
PCB, analog, mixed signal design formulae
Conversions, tables, equations

TI Precision Labs

www.TI.com/precisionlabs

Quiz questions, problems, solutions
Labs and evaluation module (EVM) available

TINA-TI™ simulation software

www.TI.com/tool/tina-ti

Complete SPICE simulator DC, AC, transient, noise analysis
Schematic entry and post-processor for waveform math

DIYAMP-EVM

www.TI.com/DIYAMP-EVM

Evaluation module providing engineers with SC70, SOT23, SOIC packaging and 12 popular amplifier configurations

The Signal

www.TI.com/thesignal

PDF, iTunes app and hardcopy available
A compendium of blog posts on op amp design topics including offset voltage, input bias current, stability, noise and more

Analog Wire Blog

www.TI.com/analogwire

Technical blogs written by analog experts
Tips, tricks, and design techniques

TI E2E™ Community

www.TI.com/e2e

Support forums for all TI products

Op Amp Parametric Quick Search

www.TI.com/amplifiers

Search for precision, high-speed, general-purpose, ultra-low-power, audio and power op amps

Op Amp Parametric Cross-Reference

www.TI.com/opampcrossreference

Find similar TI op amps using competitive part numbers

www.ti.com/circuitcookbooks



© Copyright 2021 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)