

# Slew rate and bandwidth

TI Precision Labs – Current sense amplifiers

Presented by Kyle Stone


Prepared by Javier Contreras

# Slew rate and bandwidth

- In the **electrical characteristics** table:

FREQUENCY RESPONSE				
BW	Bandwidth	A1 versions, $C_{OUT} = 500$ pF	550	kHz
		A2 versions, $C_{OUT} = 500$ pF	440	
		A3 versions, $C_{OUT} = 500$ pF	400	
SR	Slew rate		4	V/ $\mu$ s

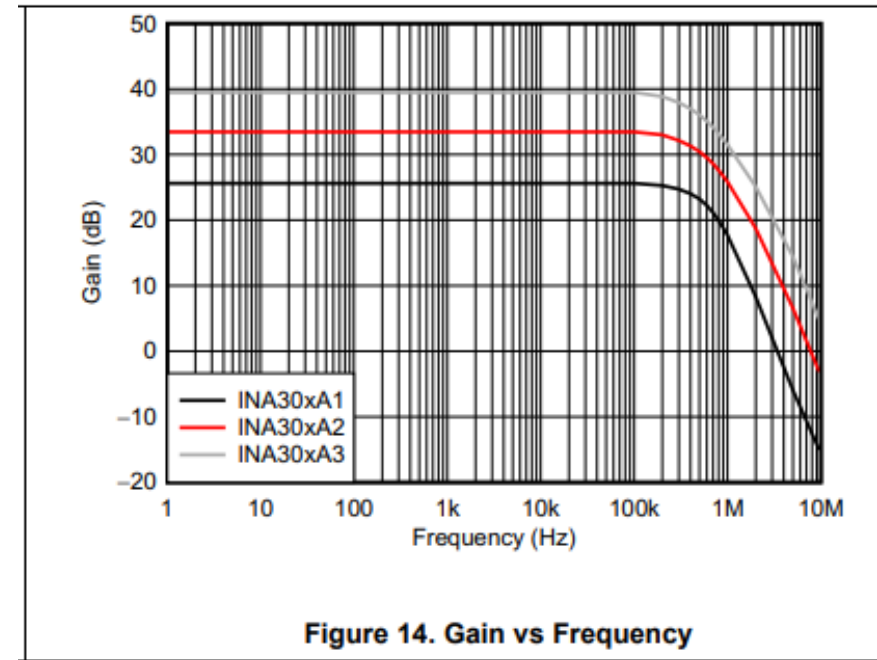- In the **typical characteristics** curves:





# Bandwidth




- In the **electrical characteristics table**:

BW	Bandwidth		
		A2 versions, $C_{OUT} = 500 \text{ pF}$	440 kHz
		A3 versions, $C_{OUT} = 500 \text{ pF}$	400 kHz

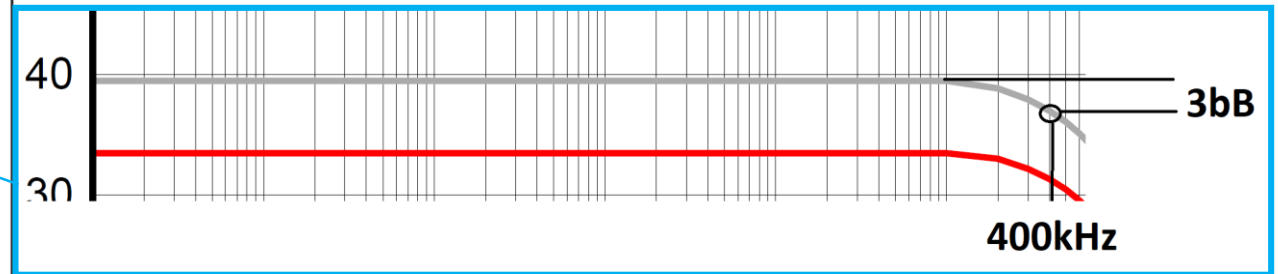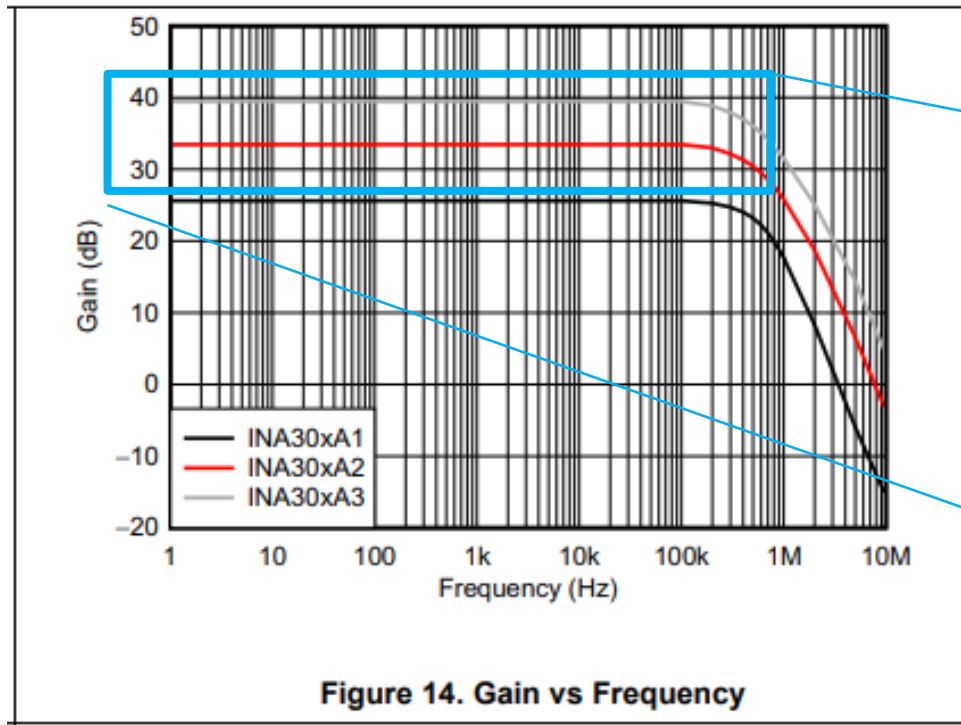- In the **typical characteristics curves**:



# Bandwidth simulation

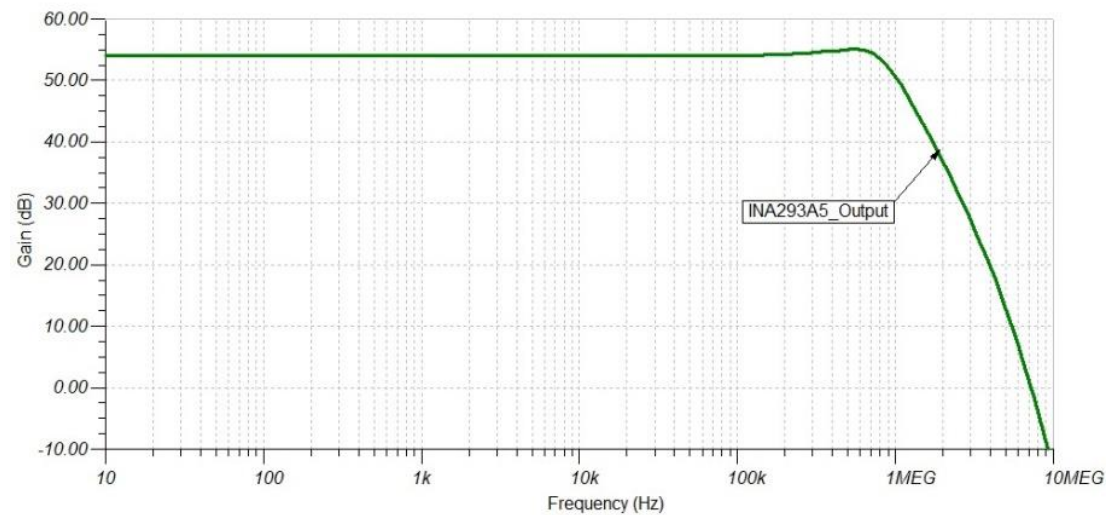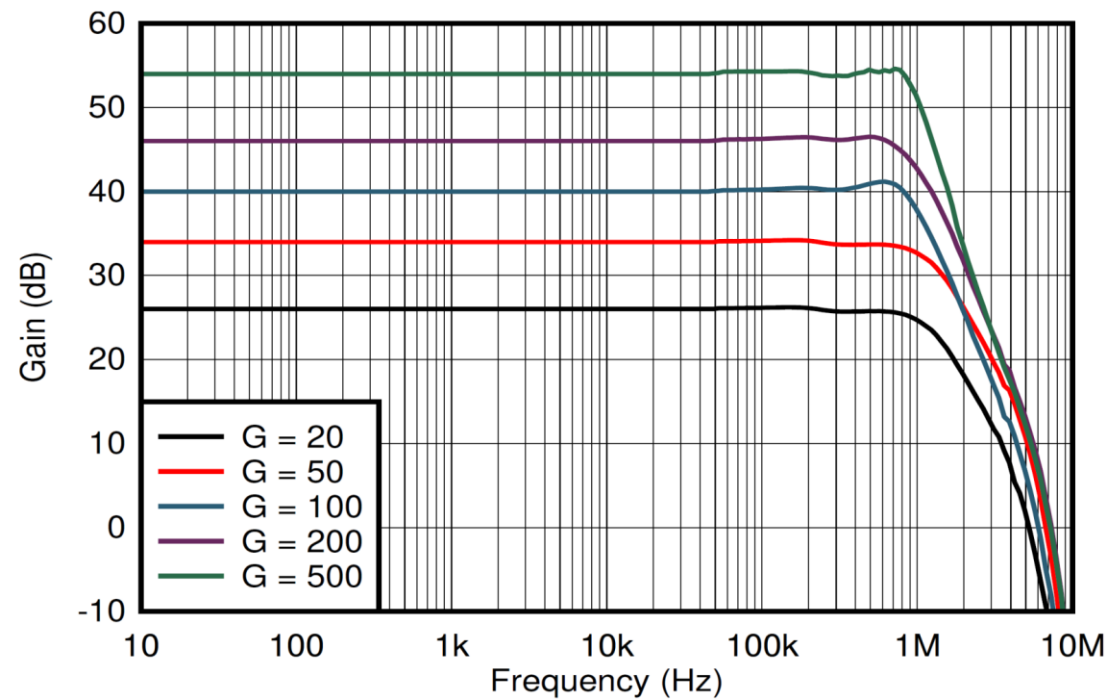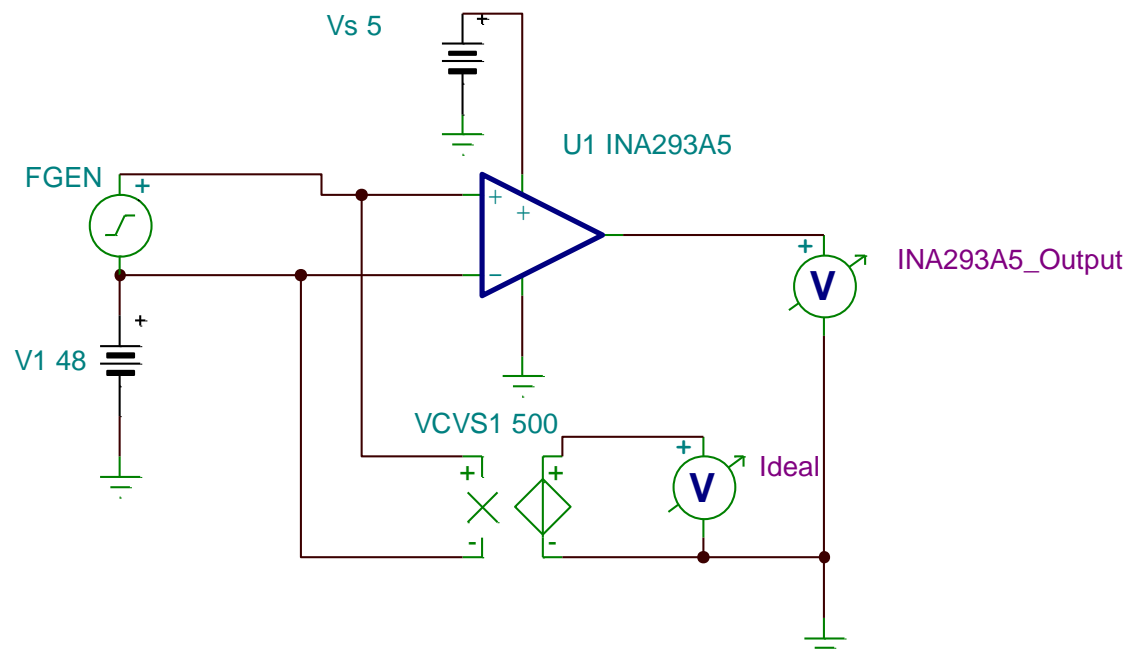


# Bandwidth small signal vs. large signal

$$\text{Max Slew Rate of a sine wave} = 2\pi \cdot F \cdot A$$


F= Frequency

A = Amplitude of sine wave

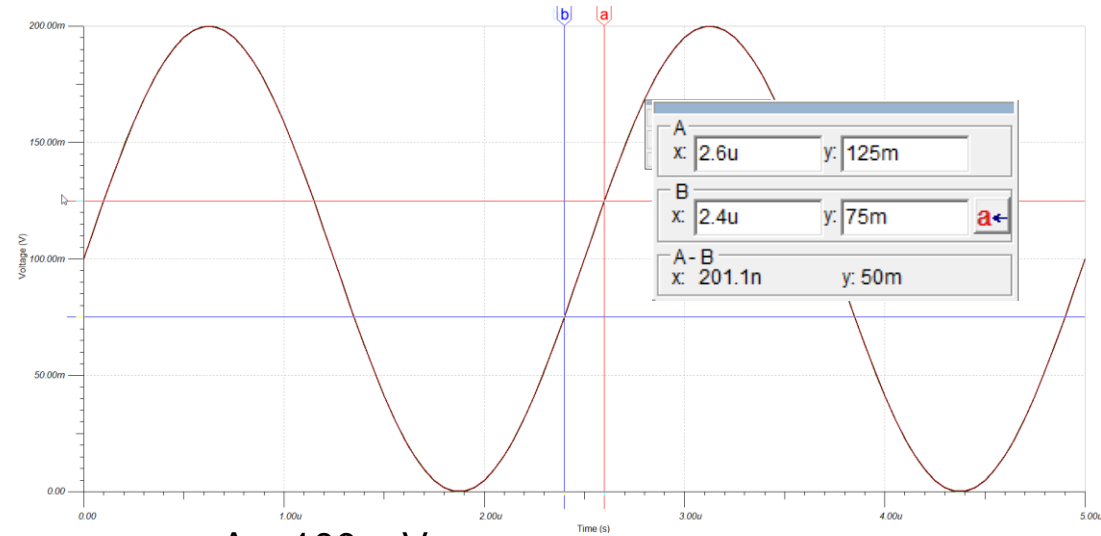

A = 100 mV  
 F = 400 kHz  
 Max slew rate  $\approx 0.25 \text{ V}/\mu\text{s}$

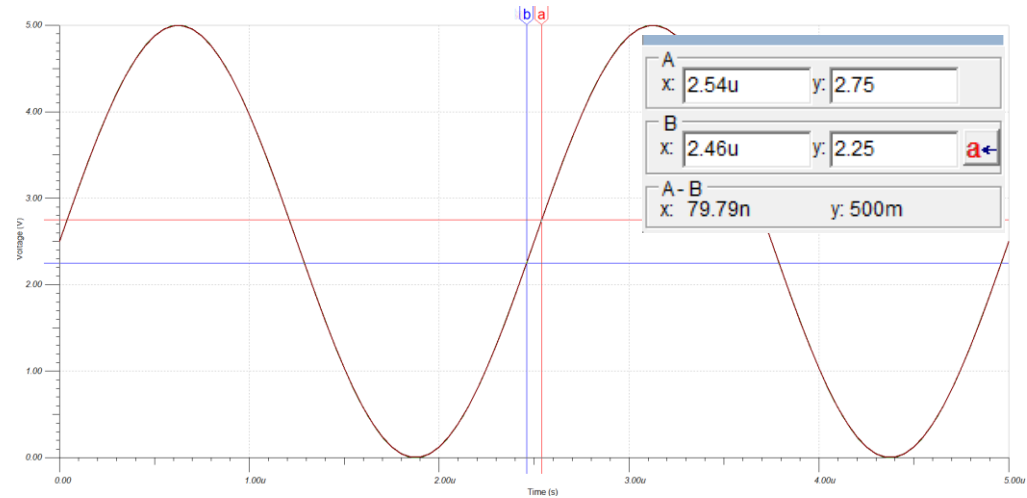
Graphical estimation  $\approx$   
 $0.05 \text{ V}/200 \text{ ns} \rightarrow 0.25 \text{ V}/\mu\text{s}$




A = 2.5 V  
 F = 400 kHz  
 Max slew rate  $\approx 6.28 \text{ V}/\mu\text{s}$

Graphical estimation  $\approx$   
 $0.5 \text{ V}/80 \text{ ns} \rightarrow 6.25 \text{ V}/\mu\text{s}$

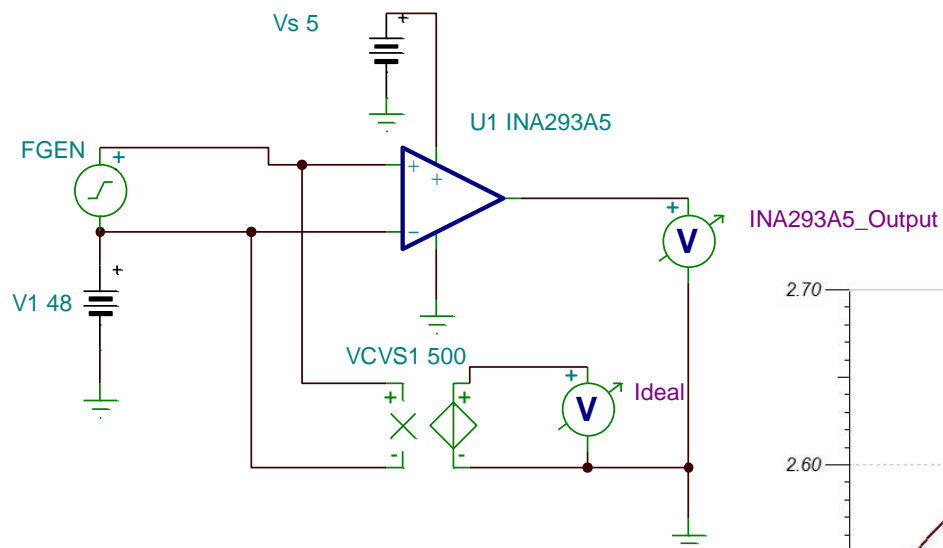
# Bandwidth small signal transient simulation



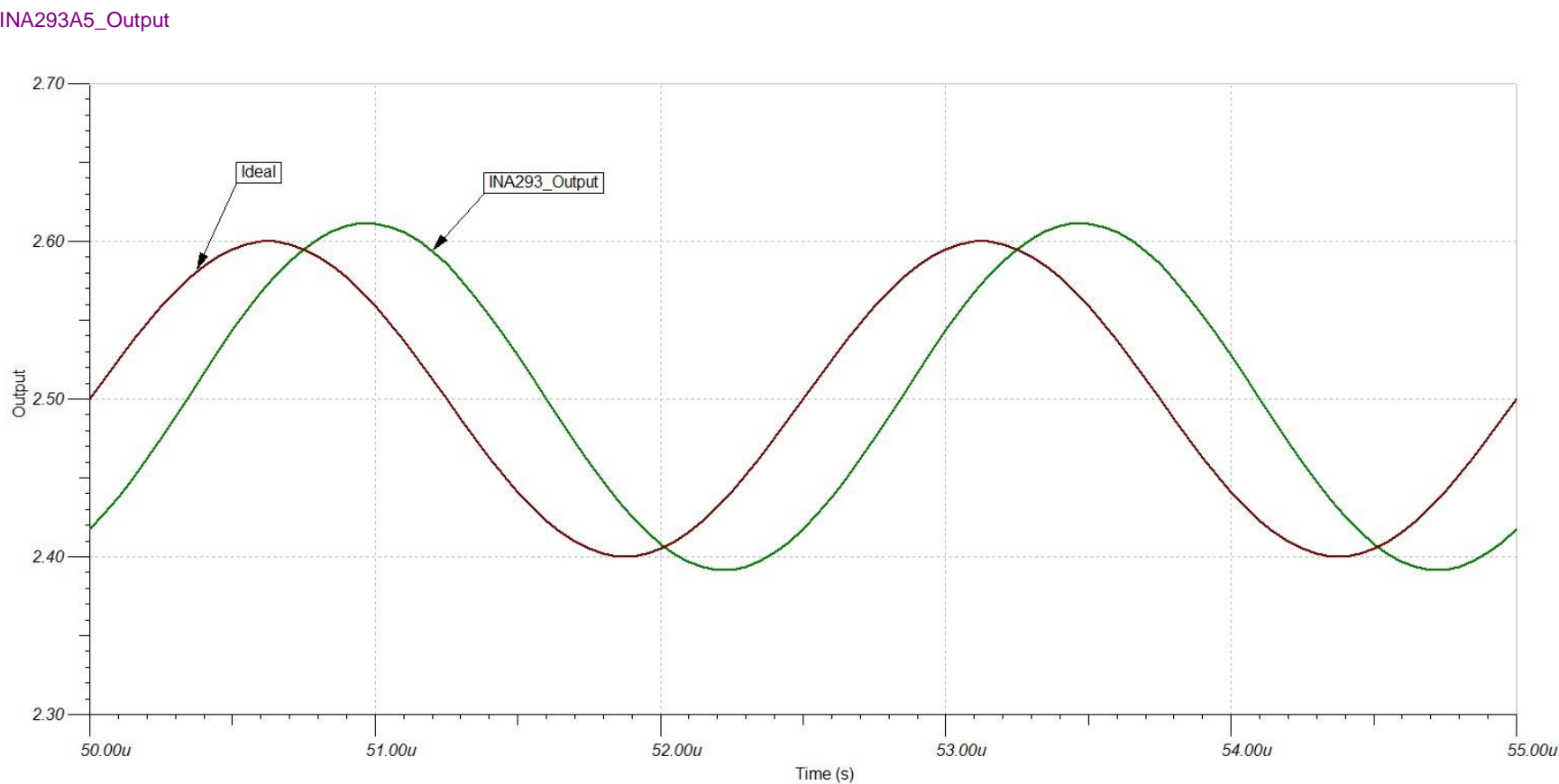
Input  
Sinewave  
200  $\mu$ V amplitude  
400 kHz



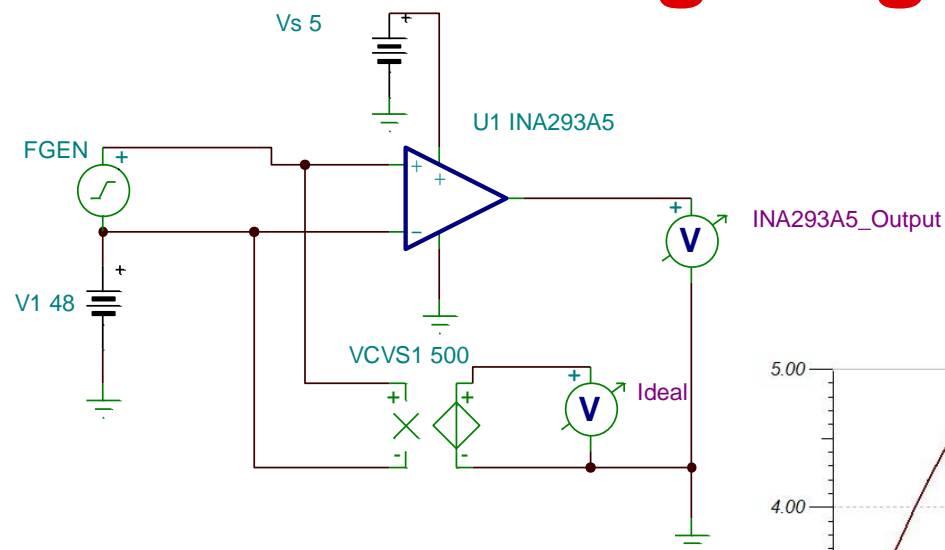
# Bandwidth large signal transient simulation



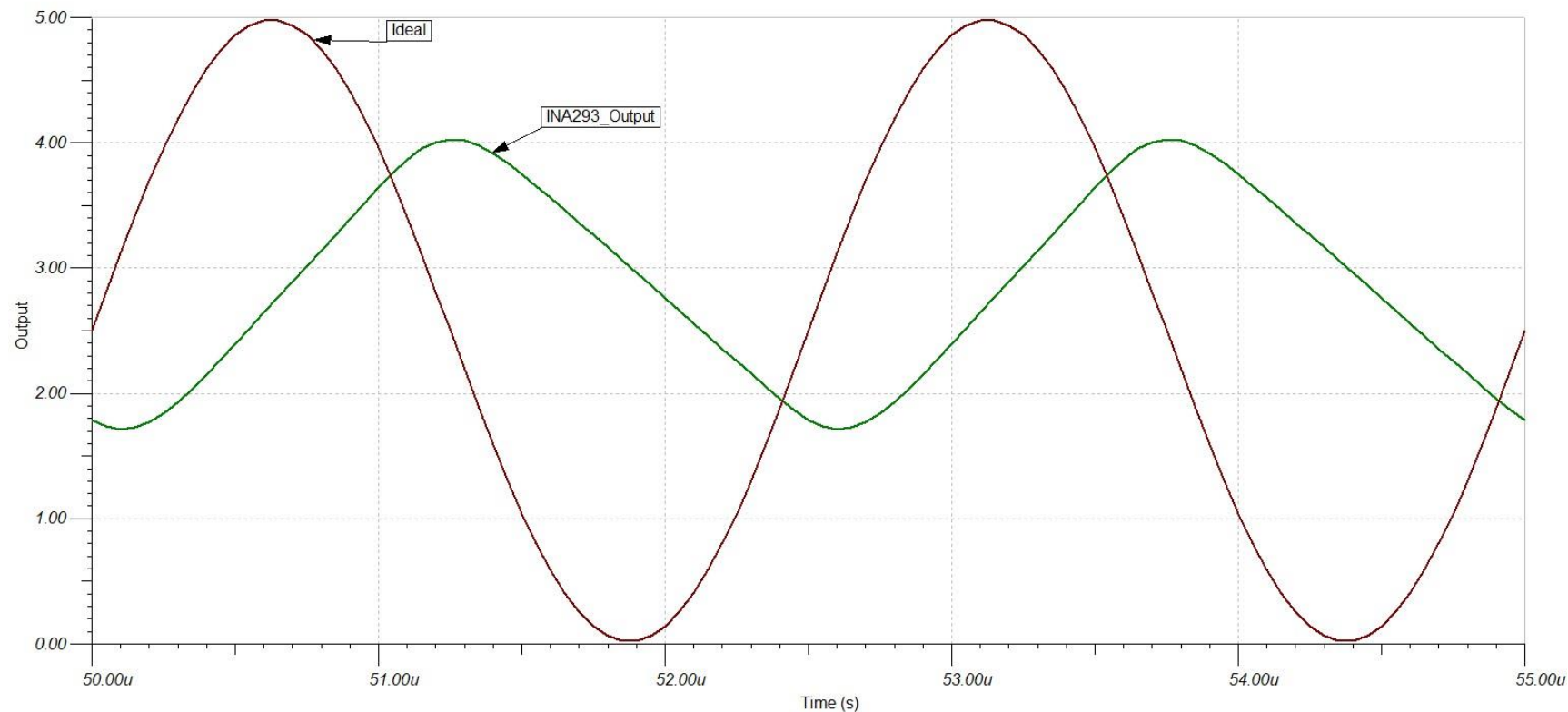Input  
Sinewave  
~5 mV amplitude  
400 kHz




# Slew rate

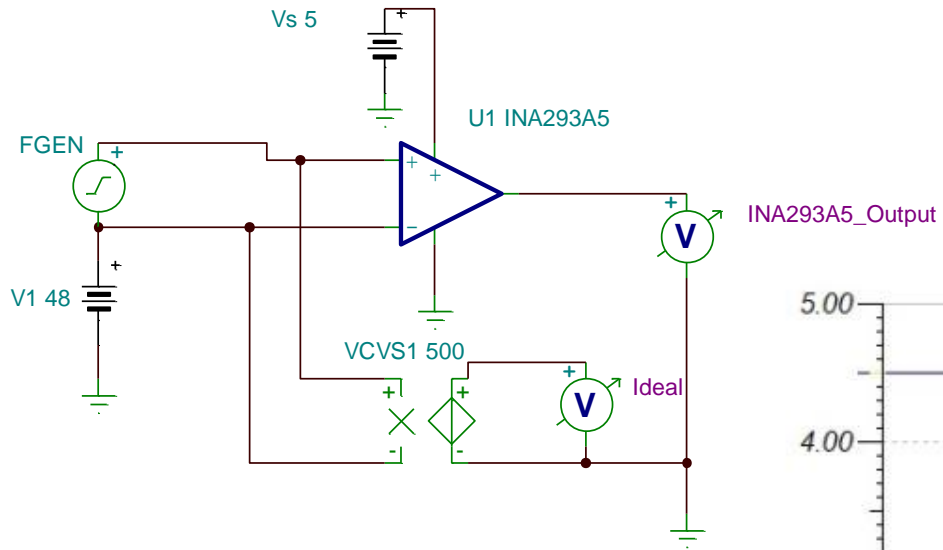

Input Step  
0.1 mV to 9.5 mV

Slew rate from simulation  
 $4 \text{ V} / 1.62 \mu\text{s} \rightarrow 2.47 \text{ V}/\mu\text{s}$

A	x: 5.4u	y: 500m
B	x: 7.02u	y: 4.5
A - B	x: -1.62u	y: -4

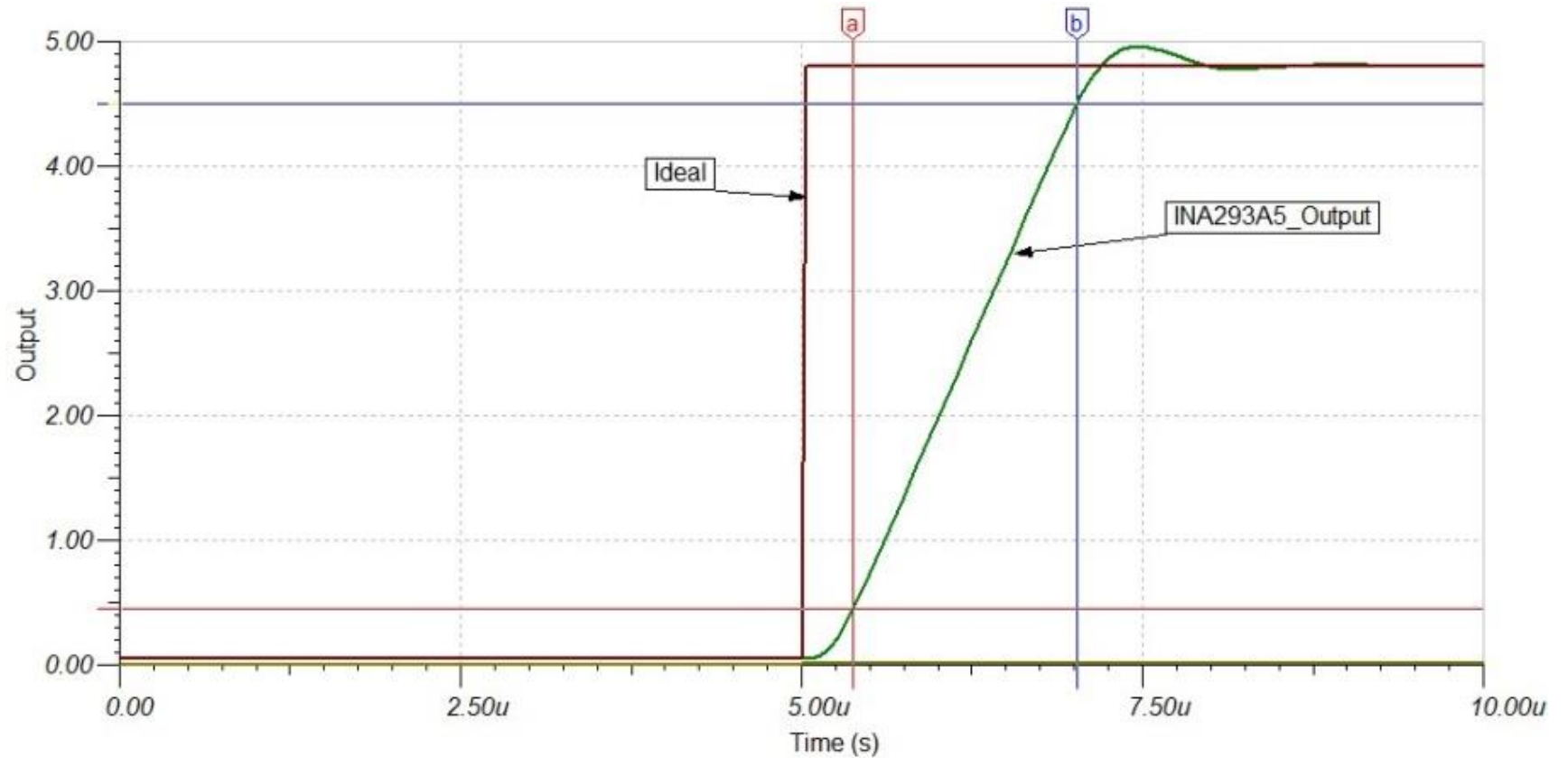



# Slew rate notes

- Slew rate measured in linear range of current sense amplifiers (CSA)
- Slew rate is not defined in non-linear range
- A device with a 0-V input could be considered having a negative input due to VOS for a unidirectional CSA
- Coming out of saturation requires time. Below is an example statement from the INA293:

## **8.2.2.1 Overload Recovery With Negative $V_{SENSE}$**

The INA293 is a unidirectional current sense amplifier that is meant to operate with a positive differential input voltage ( $V_{SENSE}$ ). If negative  $V_{SENSE}$  is applied, the device is placed in an overload condition and requires time to recover once  $V_{SENSE}$  returns positive. The required overload recovery time increases with more negative  $V_{SENSE}$ .

# Normally modeled behavior

- Linear range of the device
- Small signal AC bandwidth
- Slew rate in linear range

# Typical non-modeled behavior

- Outside of normal operating conditions.
- Overload recovery (non-linear)

**To find more current sense amplifier  
technical resources and search  
products, visit [ti.com/currentsense](https://ti.com/currentsense)**



© Copyright 2022 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.  
Use of this material is subject to TI’s **Terms of Use**, viewable at [TI.com](https://www.ti.com)