## Selecting an External Crystal TI Precision Labs – Microcontrollers

Presented by Henok Taffere Prepared by Brandon Fisher

## **External crystals**



- More accurate with less drift over operating conditions
- Lower power consumption than internal sources
- Long startup time
- Frequency is set by source
- Added system cost
- Needs special board layout considerations to operate properly

🤴 Texas Instruments

## **External crystal accuracy**

#### **Internal Oscillator Specification**

	PARAMETER	TEST CONDITIONS	Vcc	MIN TYP MAX	UNIT
I <sub>REFO</sub>	REFO oscillator current consumption	T <sub>A</sub> = 25°C	1.8 V to 3.6 V	3	μA
f <sub>REFO</sub>	REFO frequency calibrated	Measured at ACLK	1.8 V to 3.6 V	32768	Hz
	REFO absolute tolerance calibrated	Full temperature range	1.8 V to 3.6 V	±3.5%	
		T <sub>A</sub> = 25°C	3 V	±1.5%	

 $F_{RANGE} = 32768 \, Hz \, \pm 491.52 \, Hz$ 

#### **External Oscillator Specification**

ParametersMinTYPMAXUnitsFrequency Tolerance @ +25°C-10+10ppmNote: 
$$1 ppm = 0.0001\%$$

 $F_{RANGE} = 32768Hz \pm 0.33Hz$ 



3

# Accuracy stability and drift

Parameters	Conditions	Min	ТҮР	MAX	Units
Frequency		3.57		70.000	MHz
Frequency Tolerance	25°C			±30	ppm
Temperature Coefficient		-0.04	-0.03	-0.02	ppm/T <sup>2</sup>



Parameters	Conditions	Min	ТҮР	МАХ	Units	
Frequency	25°C			±30		
Tolerance	-10 ~ + 70 °C			±80	ррш	



### Crystals also drift over time, the rate at which they drift is often given as "Aging"

Parameter	МАХ	Units
Aging	±3	ppm/year

4

### Load capacitance

Parameters	MIN	ТҮР	МАХ	Units
Load Capacitance (C <sub>L</sub> )		12		pF



**Really:** 
$$C_L = \frac{C'_1 * C'_2}{C'_1 + C'_2}$$
 Where:  $C'_x = C_x + C_{Stray}$   
In most cases, we choose  $C_1 = C_2$ : **So:**  $C_L = \frac{C_1 + C_{Stray}}{2}$   
For this example:  
 $C_1 = C_2 = 22_{pF}$  if  $C_{stray} = 2pF$   
We can check if this is right:  
 $C_L = \frac{C_1 + C_{Stray}}{2} = \frac{22pF + 2pF}{2}$   
 $C_L = 12pF$ 



5

## **Equivalent series resistance**



Design Parameter	Higher ESR Crystal	Lower ESR Crystal
Safety Factor	Worse	中 Better
Startup Time	Worse	Better
Power Dissipation	Worse	🕂 Better
Peak Drive Level	Worse	📥 Better
Cost	🕂 Better	Worse
PCB Footprint	📥 Better	Worse

## **Equivalent series resistance**



How do you know how high of an ESR Value is too high?





To find more TI microcontroller technical resources and search products, visit **ti.com/Microcontrollers**.

