



Fully Differential Amplifiers - 1

TIPL 2021

TI Precision Labs: Op Amps


Prepared and Presented by Samir Cherian






Fully-differential Signals and Their Advantages


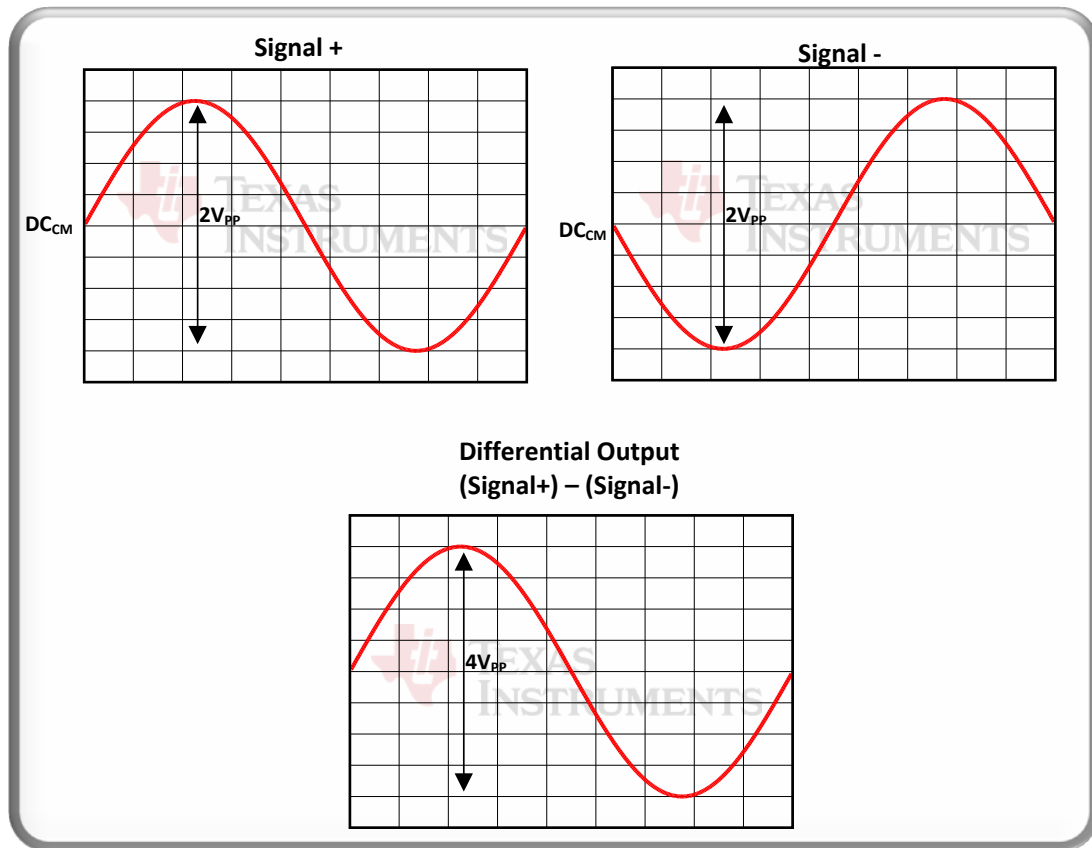
- Improved rejection of common-mode perturbations and noise.
- Improved even-order Harmonic Distortion performance.
- Improved dynamic range: 2x differential-output signal swing.




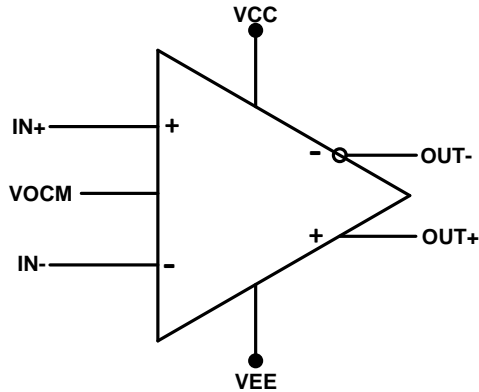
Fully-differential Amplifier (FDA): Introduction



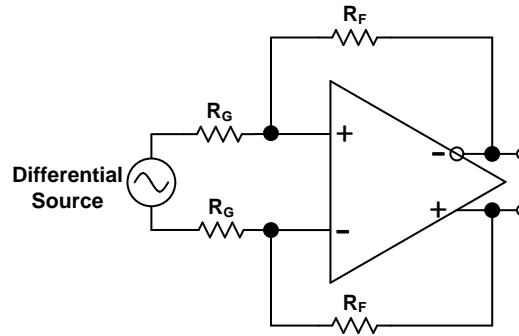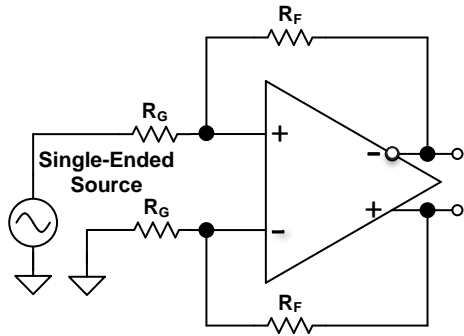- Converts single-ended input to differential output.
- Converts differential input to differential output.
- Independent common-mode and differential gain control allows for output common-mode level shift



FDA: Discrete-amplifier Realization

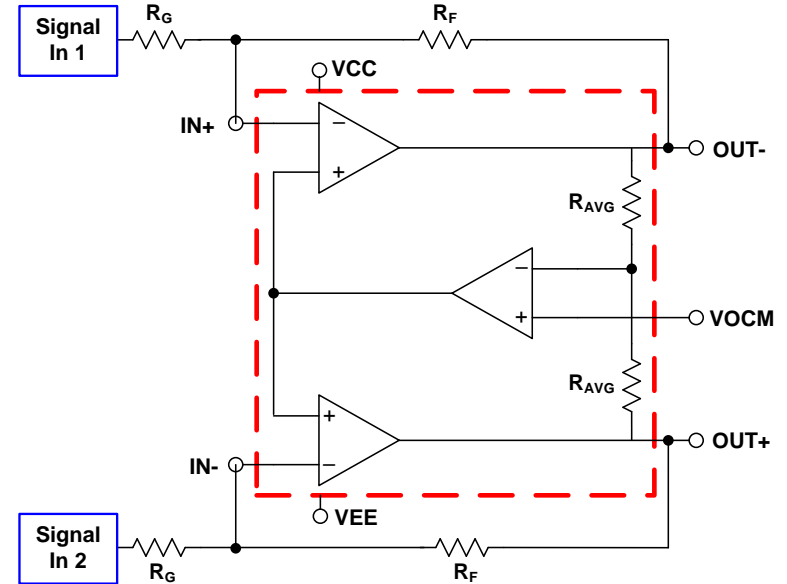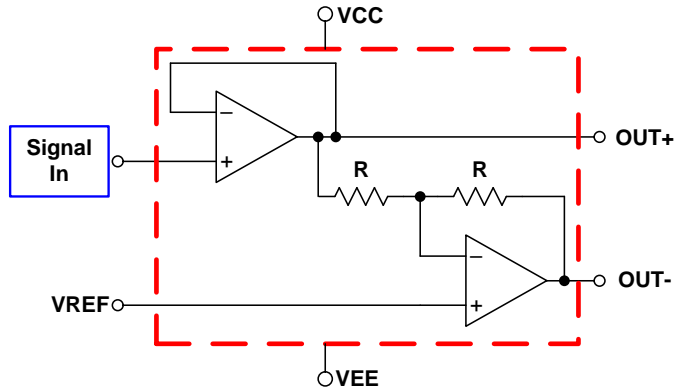


- High input impedance.
- Phase difference between inverting and noninverting outputs results in balance error.

$$E_{n_Out} = \sqrt{E_{n_Amp1}^2 + 4 \times E_{n_Amp2}^2}$$

- Integrated solution can offer lower noise for same power consumption and better matching for reduced balance error.


Integrated FDA: THS4551 Block Diagram

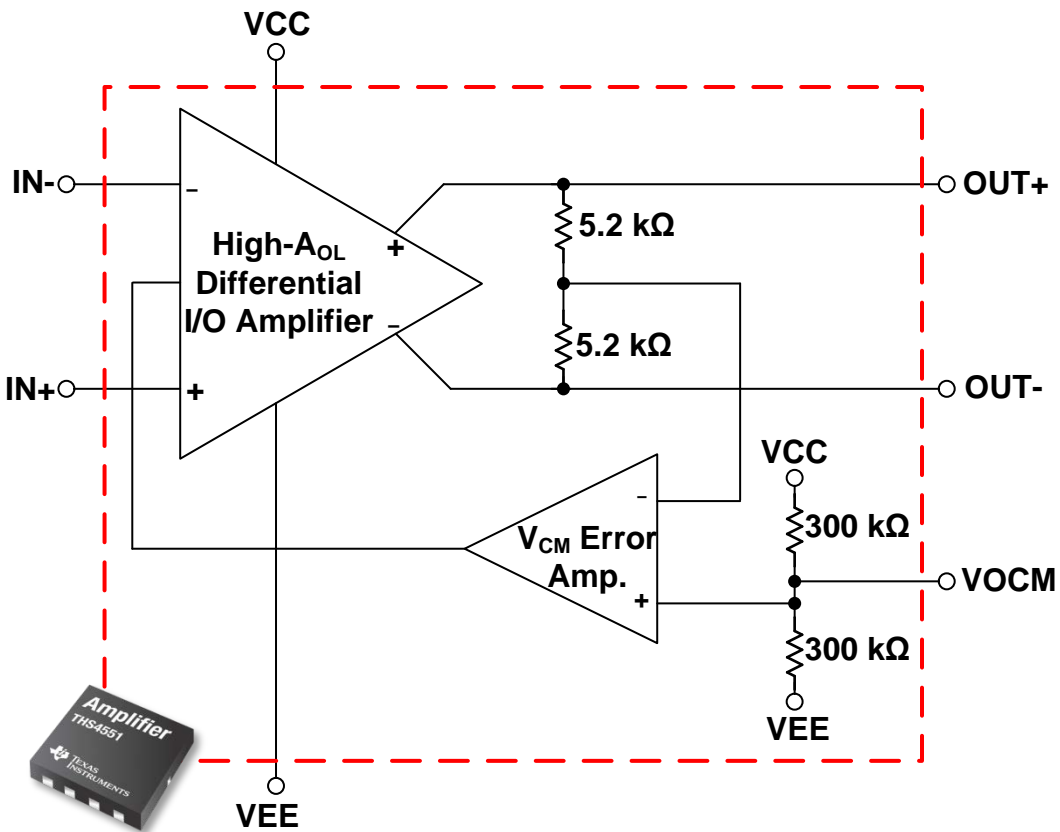

- Integrated fully-differential, high- A_{OL} amplifier.
- Integrated wide-bandwidth, common-mode feedback, error amplifier.
- Integrated resistors to detect the average output common-mode voltage.
- Integrated mid-supply, common-mode set resistors.


How an FDA Works: Rule 1 of 3

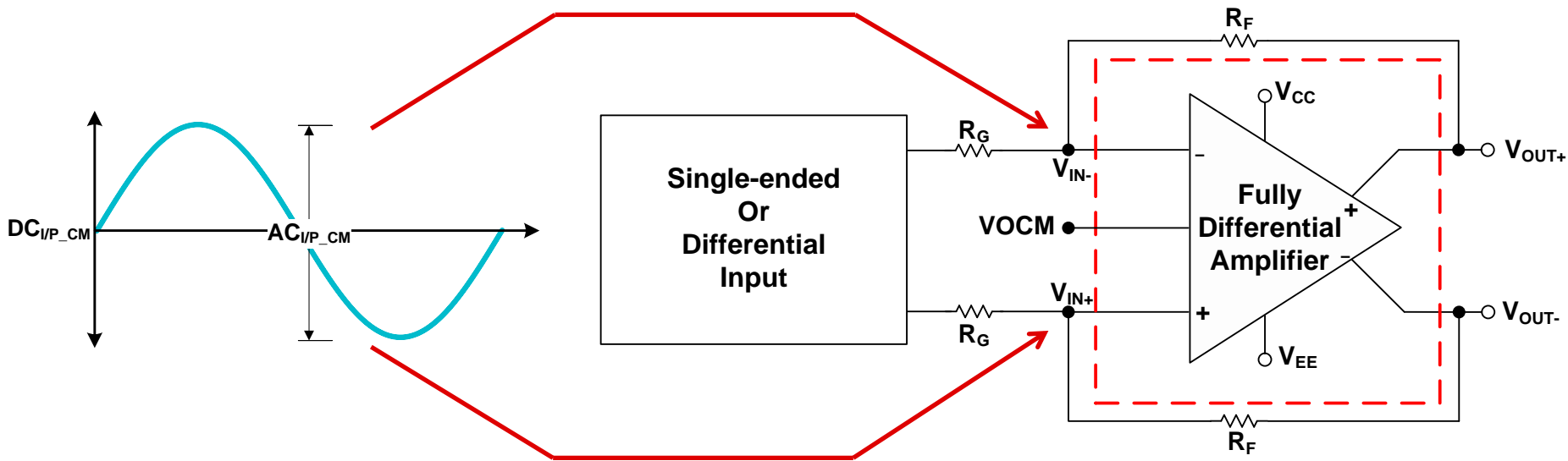There are Three Golden Rules that determine how an FDA works



- 1 The voltage (DC and AC) at the inputs track each other exactly, similar to an op-amp's virtual short across its inputs.

How an FDA Works: Rules 2 and 3

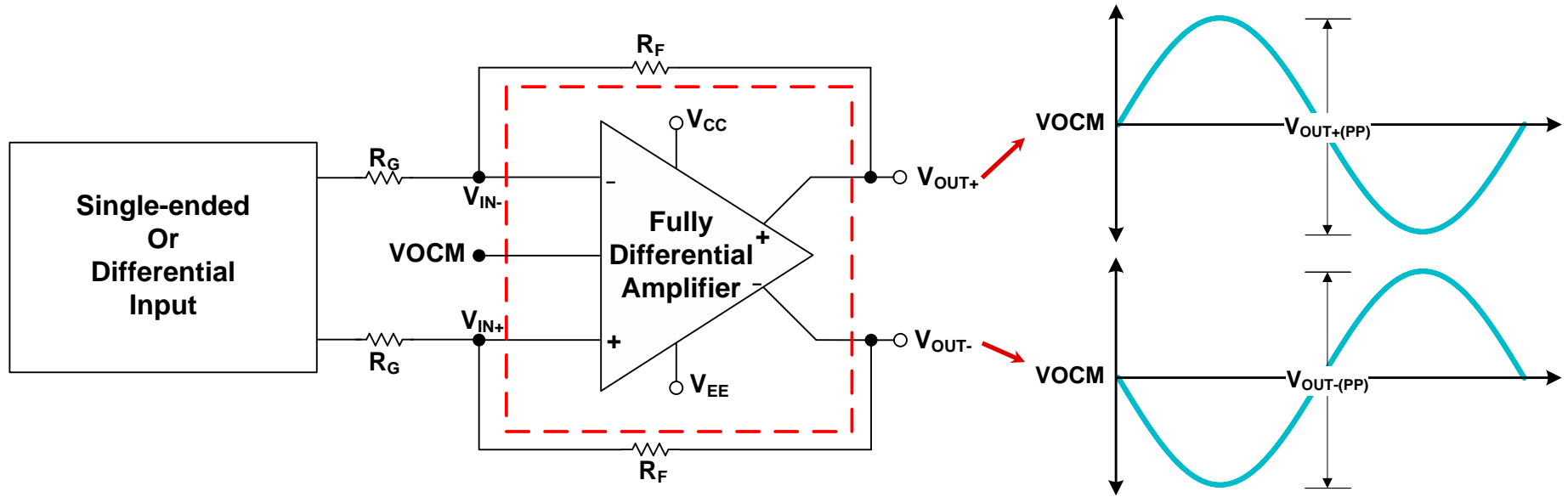

2 The two outputs are 180° out of phase, AND

3 The two outputs have the same DC offset voltage equal to $VOCM$.

$$V_{OUT+}(t) - V_{OCM} = -(V_{OUT-}(t) - V_{OCM})$$
$$V_{OCM} = \frac{V_{OUT+}(t) + V_{OUT-}(t)}{2}$$



©Copyright 2017 Texas Instruments Incorporated. All rights reserved.

This material is provided strictly “as-is,” for informational purposes only, and without any warranty.
Use of this material is subject to TI’s **Terms of Use**, viewable at TI.com


Fully Differential Amplifiers - 1

Exercises


TI Precision Labs: Op Amps

Questions

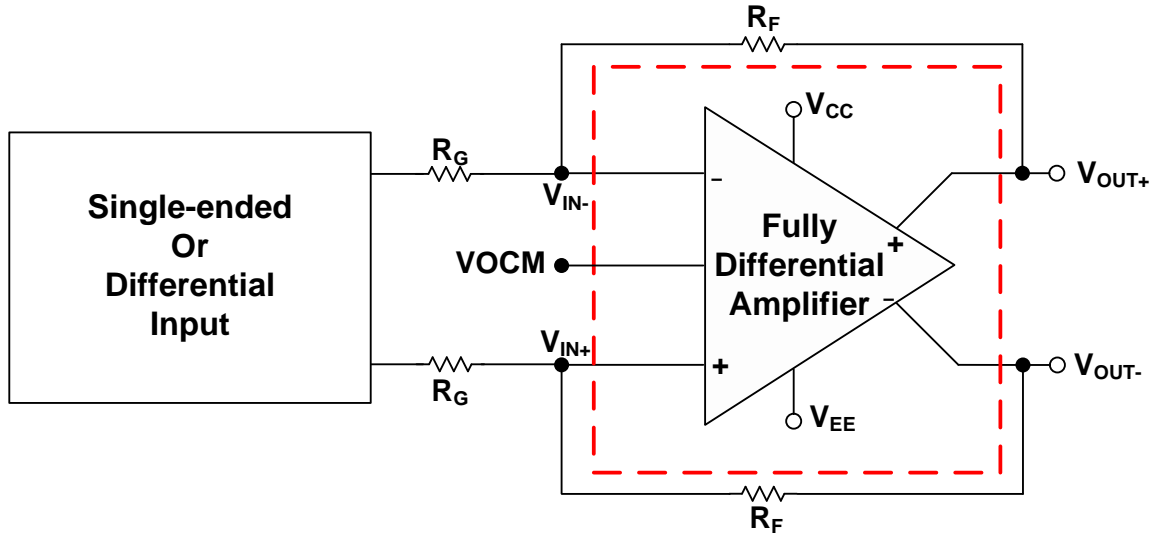1. An FDA circuit has $V_{OCM} = 3V$ and its instantaneous differential output is equal to $0.5V$.
What is the instantaneous voltage at V_{out+} and V_{out-} ?



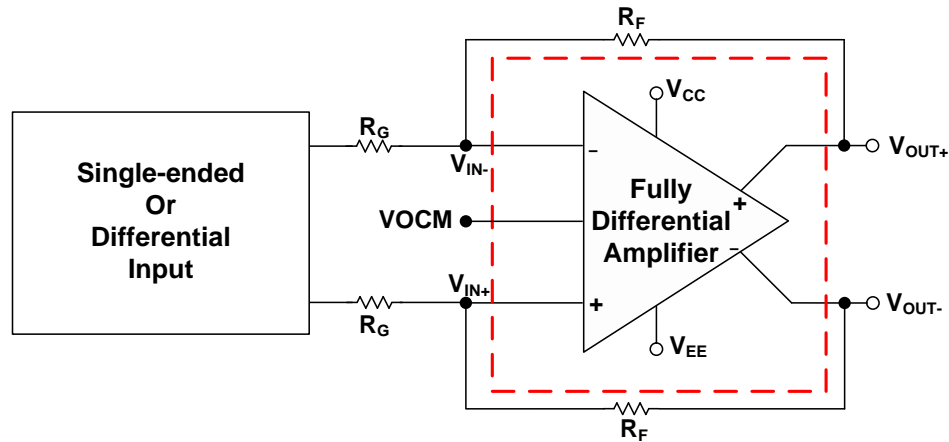2. An FDA circuit is setup as shown below. The desired VO_{CM} is equal to mid-supply which occurs by default due to the internal resistors. What would you change in the design in order to minimize the noise from the internal resistors.



3. An FDA is operating on 5V supplies and its outputs have the ability to swing rail-to-rail. What is the maximum differential output voltage of the FDA (assume a sinusoidal signal and VO_{CM} at mid-supply)?

Answers

1. An FDA circuit has $VOCM = 3V$ and its instantaneous differential output is equal to $0.5V$.
What is the instantaneous voltage at V_{out+} and V_{out-} ?

$VOCM$ by definition is the average of the two output voltages, so

$$VOCM = \frac{V_{OUT+}(t) + V_{OUT-}(t)}{2} = 3V$$


Also, the problem states that

$$V_{OUT+}(t) - V_{OUT-}(t) = 0.5V$$


Solving the above two equations gives V_{out+} and V_{out-} as $3.25V$ and $2.75V$ respectively.

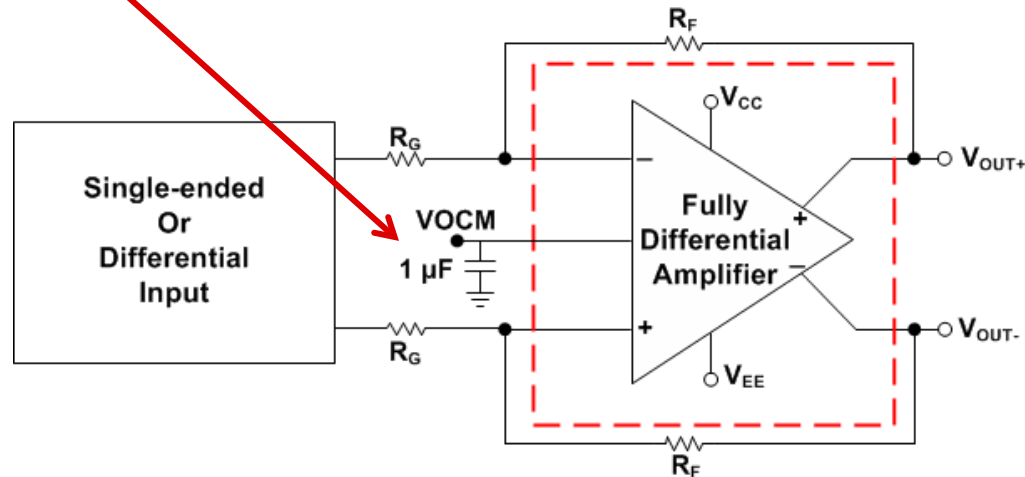2. An FDA circuit is setup as shown below. The desired VO_{CM} is equal to mid-supply which occurs by default due to the internal resistors. What would you change in the design in order to minimize the noise from the internal resistors.

Answer: Add a large external capacitor (1nF to 1μF) to the VO_{CM} pin. This will act as a low impedance path at high frequencies and shunt the noise from the internal resistors to GND.



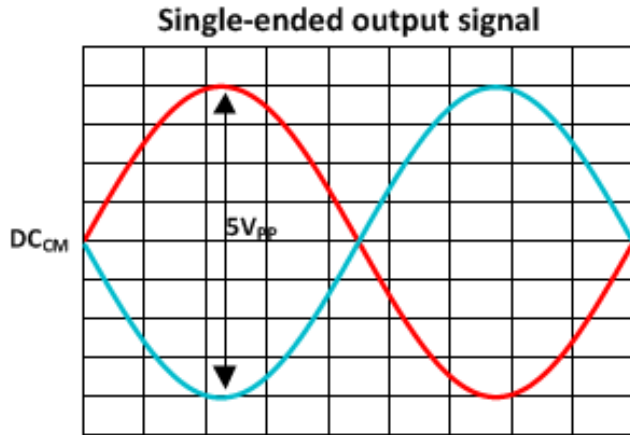3. An FDA is operating on 5V supplies and its outputs have the ability to swing rail-to-rail. What is the maximum differential output voltage of the FDA (assume a sinusoidal signal)?



Answer: Since each single-ended output signal can swing completely between the amplifiers supplies, each output's is capable of a $5V_{PP}$ swing.

Since the two outputs are 180° out of phase with each other the **Differential Output Swing = $2 * 5V_{PP} = 10V_{PP}$**