

Stability – 5

TIPL 1335

TI Precision Labs – Op Amps

Presented by Collin Wells


Prepared by Collin Wells, Art Kay, Ian Williams, and Tim Green

Prerequisites: Op Amp Bandwidth 1 – 3
(TIPL221 – TIPL1223)



Hello, and welcome to part five of the TI Precision Labs on op amp stability. The previous videos discussed the concepts involved in basic stability theory, as well as how to test and simulate for stability issues in SPICE and on the bench. This video will discuss why capacitive loads cause stability issues and will present the first capacitive load compensation technique using an isolation resistor.

 
Why Do Capacitive Loads Cause Instability?



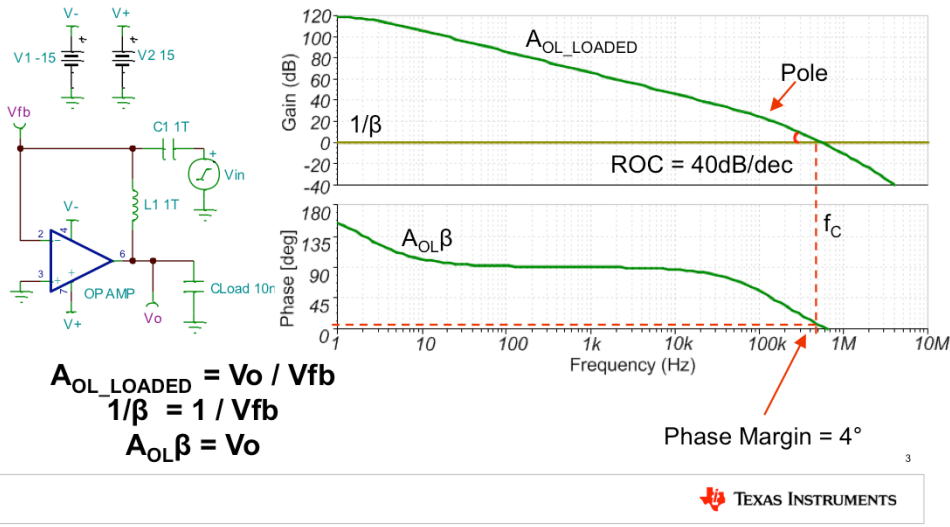Part 1 of the stability series discussed that the most common cause of stability issues in amplifier circuits is capacitance on the output. Some common circuits that frequently have large capacitive loads are voltage reference buffers, cable/shield drive circuits, and MOSFET drive circuits. In the case of the MOSFET and cable or shield drive circuits the capacitive load is not always immediately apparent, so be sure to examine if the output is connected to anything with parasitic capacitance.


Simulate the Effects of Output Capacitance

Run open-loop analysis on buffer circuit with capacitive load





Now that we know how to generate the open-loop curves of an op amp circuit, we can simulate the effects with a capacitive load to determine the issue. As the results show, the 10nF capacitive load results in a pole in the Aol curve which degrades the Aol*β phase to only 4 degrees at fc. Let's examine why this happens.

Capacitive Loads – Stability Theory

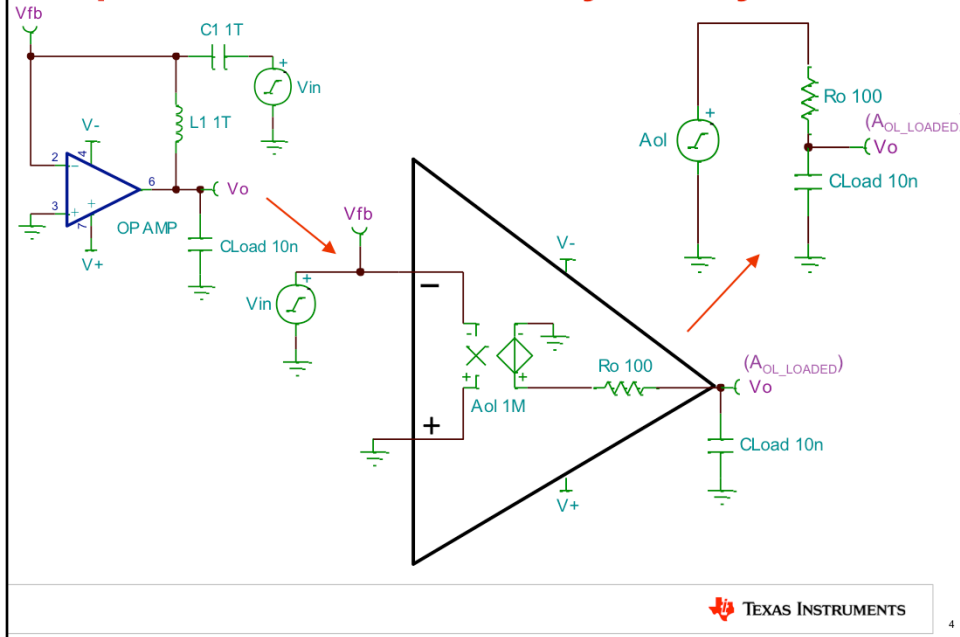

If we take a look at a simplified representation of the open-loop circuit, we see that the input signal passes through the Aol gain block and then the series open-loop output impedance, Ro , before reaching the op amp output, V_o . With a capacitor from $CLoad$ to GND on the output, the op amp Aol curve is loaded by the RC voltage divider formed from Ro and $CLoad$.

Capacitive Loads – Stability Theory

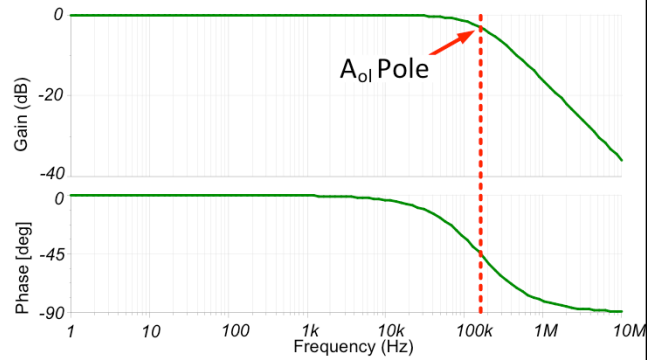 


Transfer Function: $V_{o} / V_{in} (s) = 1 / (1 + s * R_o * C_{LOAD})$

Pole Equation: $f_{POLE} = 1 / (2 * \pi * R_o * C_{LOAD})$


To understand the effects of the output load, the AC transfer function of the equivalent $R_o + C_{Load}$ circuit has been plotted here. The pole location can be calculated from the transfer function and is shown at the bottom of the slide.

Capacitive Loads – Stability Theory

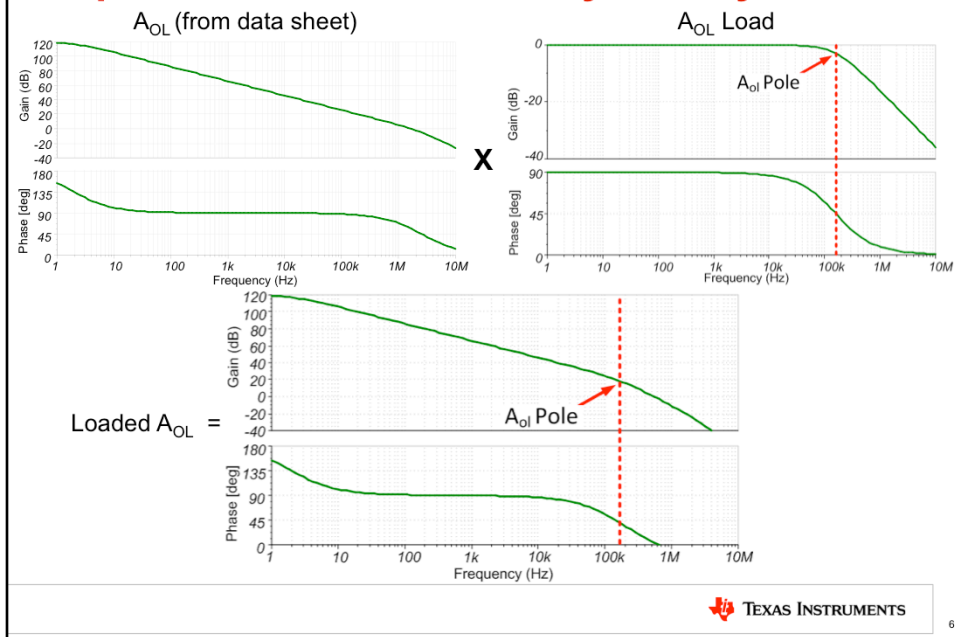

If the original op amp A_{OL} curve and the A_{OL} load curve are combined, the result is the loaded A_{OL} curve shown on the bottom. The A_{OL} pole from the interaction of R_o and C_{load} causes the A_{OL} curve to change to a -40dB / decade slope and reduces the unity-gain phase margin.

Compensation Method 1: R_{ISO}

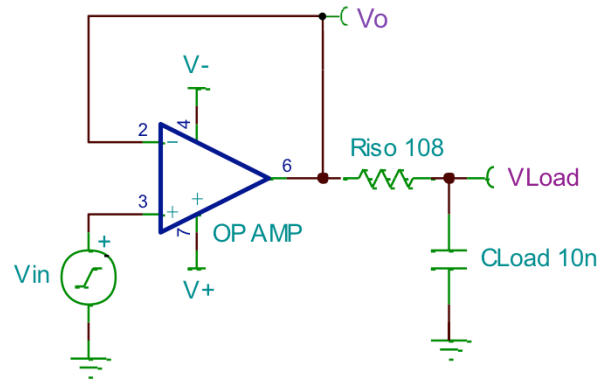


Now that we understand how a capacitive load contributes to circuit instability, we can introduce our first compensation technique, known as the Riso method.


The Riso method compensates the circuit by adding a zero to cancel the pole from the output impedance and capacitive load.

Method 1: R_{ISO} – Results

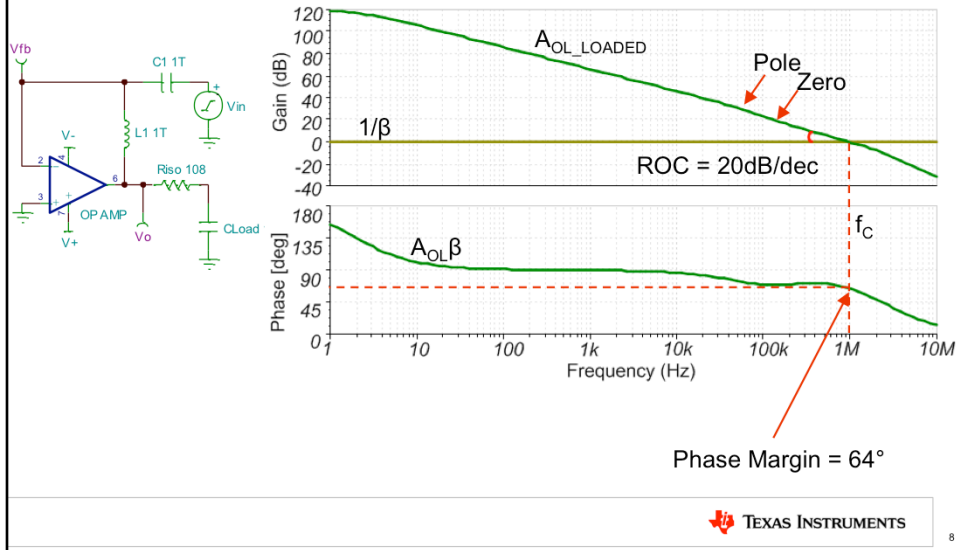Theory: Adds a zero to cancel the pole in loaded A_{OL}




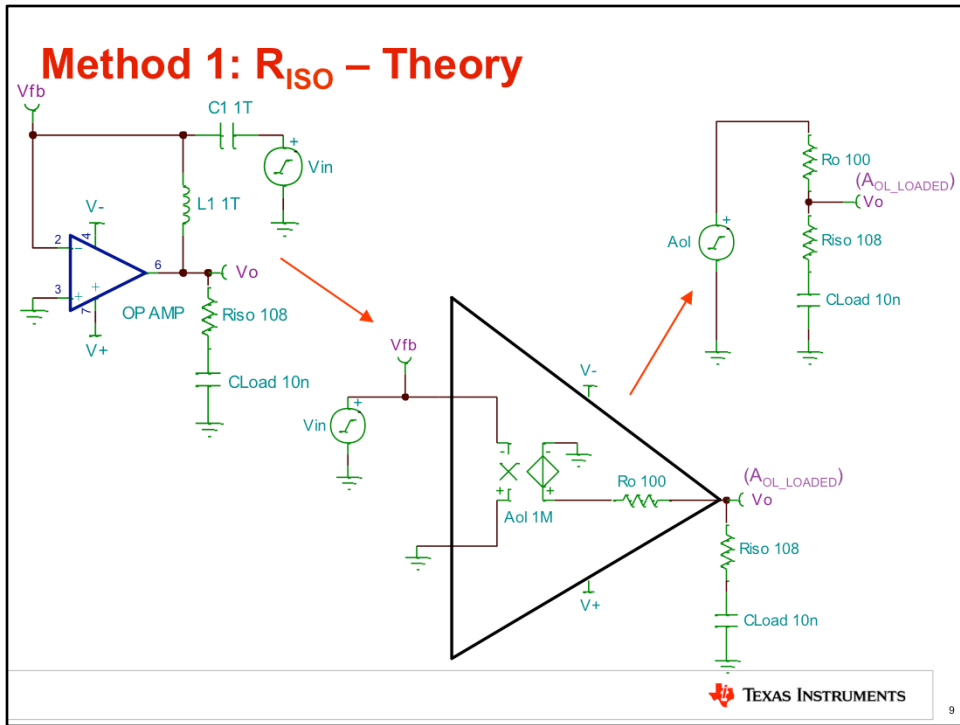Looking at the open-loop results from the “Riso” compensation method, a zero can be seen cancelling the pole from Riso and Cload. This results in a return to a 20dB/decade Aol slope and significantly improved phase margin.




We can examine the open-loop R_{ISO} circuit the same way we examined the capacitive load circuit. Once again the A_{OL} is loaded by an impedance divider, but this time both R_{ISO} and C_{Load} are on the bottom side of the divider and R_o is on the top side of the divider.

Resistor Divider Analogy

 
 
$$V_{O} / V_{IN} = R_{2} / (R_{2} + R_{1})$$



$$V_{O} / V_{IN} = Z_{2} / (Z_{2} + Z_{1})$$

$$V_{O} / V_{IN} = R_{ISO} + 1/s * C_{LOAD} / (R_{ISO} +$$



$$V_{O} / V_{IN} = 1 + s * R_{ISO} * C_{LOAD} / (1 + s * (R_{ISO} + R_{O}) * C_{LOAD})$$

← **Zero:** R_{ISO} & C_{LOAD}
← **Pole:** R_{O} , R_{ISO} , and C_{LOAD}



We can compare the Aol Load to a classic resistive voltage divider. Remember, the transfer function of a voltage divider is equal to the impedance of the bottom leg divided by the sum of both the top and bottom impedances. The same applies to the circuit with R_o , R_{iso} , and C_{load} , as shown on the right. R_o makes up Z_1 , the impedance of the top leg, while the series combination of R_{iso} and C_{load} make up Z_2 , the impedance of the bottom leg. The transfer function can be simplified to the form shown at the bottom-right. The numerator shows a zero dependent only on R_{iso} and C_{load} , both external circuit components, while the denominator shows a pole dependent on R_o , R_{iso} , and C_{load} .

Method 1: R_{ISO} – Theory

  

Transfer Function: $V_{o}/V_{in}(s) = \frac{1 + sR_{ISO} * C_{LOAD}}{1 + s*(R_{O} + R_{ISO}) * C_{LOAD}}$

Zero Equation: $f_{ZERO} = 1/2 * \pi * R_{ISO} * C_{LOAD}$


Zero: R_{ISO} & C_{LOAD}

Pole Equation: $f_{POLE} = 1/2 * \pi * (R_{O} + R_{ISO}) * C_{LOAD}$

Pole: R_{O} , R_{ISO} , and C_{LOAD}

The resulting Laplace transfer function for this circuit is shown here. Again, with a single “s” term in both the numerator and denominator it is clear that there is now both a pole and a zero in the transfer function. The equations for the pole and zero frequency can be calculated from the transfer function. Plotting the ac transfer function, you can see that the positive phase shift from the zero cancels the negative phase shift from the pole, causing a net phase shift of zero degrees.

Method 1: R_{ISO} – Theory

 

Adding the A_{ol} and A_{ol} load curves together as before, we can again see that the zero added by R_{ISO} cancels the pole in the A_{ol} curve and restores the unity-gain phase margin to an acceptable level for stability.

Method 1: R_{ISO} – Design

Design Steps:


- 1.) Find the zero frequency, f_{ZERO} , where $A_{OL_Loaded} = 20$ dB
- 2.) Calculate R_{iso} to set the zero at f_{ZERO}
This will yield between 60° and 90° degrees of phase margin

R_{ISO} Equation:

$$R_{iso} = 1/2 * \pi * f_{ZERO} * C_{LOAD}$$

$$R_{iso} = 1/2 * \pi * 146.5\text{kHz} * 10\text{n}$$

$$R_{iso} = \mathbf{108\Omega}$$

 


To design the R_{iso} circuit for a phase margin above 60 degrees, first find the frequency where the Loaded A_{ol} curve is equal to 20dB, $f(zero)$.

Then, to calculate the value of R_{iso} , use the equations shown on the left and plug in the values for C_{load} and $f(zero)$. An R_{iso} value of 108 ohms is the result in this case.



These steps will result in a phase margin between 60 and 90 degrees of phase margin depending on the op amp unity-gain phase margin and location of the A_{ol} pole.

Method 1: R_{ISO} – Design Summary

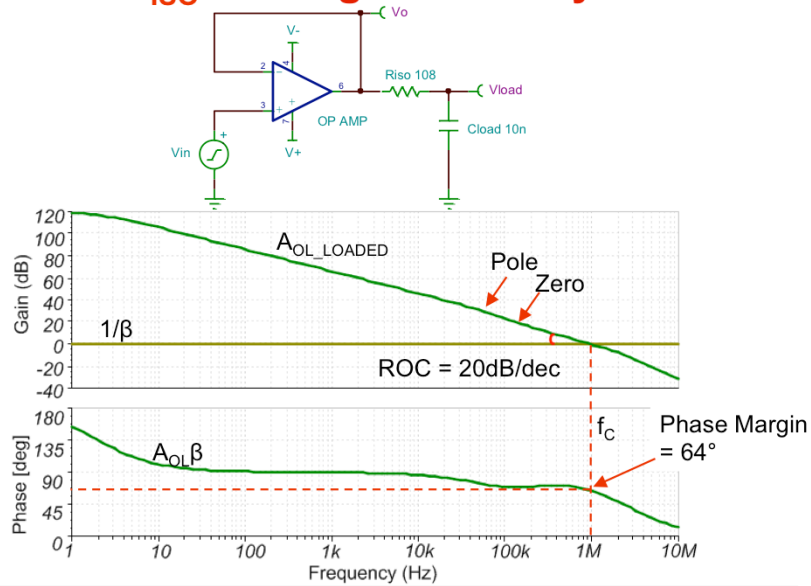


In summary, find the frequency where the loaded Aol curve equals 20dB and set the zero to that frequency by calculating the proper R_{iso} value. While the theory behind this is not shown here, if the zero frequency ends up greater than ~ 1.5 decades from the pole, the R_{iso} value should be increased to prevent the $A_{ol}\beta$ phase from dipping too low in the loop. If R_{iso} is equal to at least $R_o/34$, then the zero will be within 1.5 decades of the pole. If the circuit is not required to deliver larger output currents then consider increasing R_{iso} to be equal to or larger than R_o and the circuit will be stable under basically all capacitive loads.

Unstable vs. Stable Transient Results

  

No compensation - Unstable

 

Riso compensation - Stable




Comparing the transient response of the circuit both with and without Riso compensation, we can see the significant improvement by using Riso. Without Riso, the output of the circuit shows heavy overshoot and ringing.

Method 1: R_{ISO} – Disadvantage

Disadvantage:

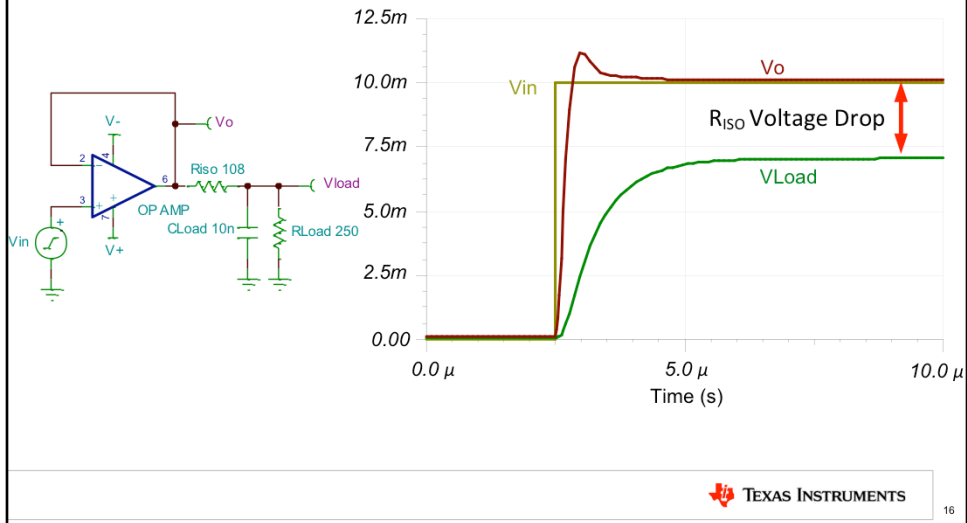
Voltage drop across R_{ISO} may not be acceptable for certain applications!



While the R_{iso} circuit is both simple to implement and design, it has a big disadvantage in precision circuits. The voltage drop from R_{iso} is dependent on the output current or output load, and may be significant compared to the desired signal. As shown here, a 10mV signal has over 3mV (30%) of error due to a 250 Ω output load.

**Thanks for your time!
Please try the quiz.**

17

 

In summary, this video discussed the theory behind why capacitive loads cause stability issues and presented a simple method to compensate for the capacitive load by placing a resistor between the amplifier output and capacitive load.

The next video will present a second capacitive load compensation technique that fixes the dc errors caused by the Riso circuit.

Thank you for your time! Please try the quiz to check your understanding of this video's content.

Stability 5

Multiple Choice Quiz

TI Precision Labs – Op Amps



Quiz: Stability 5

1. (T/F) Placing capacitive loads on the output of an op amp will generally cause stability issues.

- a. True
- b. False

2. The output capacitance causes issues because it interacts with the amplifier's:

- a. Open-Loop Gain
- b. Input Offset Voltage
- c. Open-Loop Output Impedance
- d. Feedback network

3. Output capacitance results in an additional _____ which degrades the phase margin.

- a. pole in the Aol curve
- b. zero in the Aol curve
- c. pole-zero pair in the Aol curve

Quiz: Stability 5

4. (T/F) The Riso compensation technique works by adding a zero to cancel the Aol pole from the capacitive load.

- a. True
- b. False

5. (T/F) The frequency of the zero in the Riso compensation method is based on the values of:

- a. Riso, Ro, Cload
- b. Riso, Cload
- c. Ro, Cload


6. (T/F) DC voltage errors due to the voltage drop across Riso are a disadvantage to the Riso compensation method.

- a. True
- b. False

Stability 5

Multiple Choice Quiz: Solutions

TI Precision Labs – Op Amps

 

Quiz: Stability 5

1. (T/F) Placing capacitive loads on the output of an op amp will generally cause stability issues.

- a. True
- b. False

2. The output capacitance causes issues because it interacts with the amplifier's:

- a. Open-Loop Gain
- b. Input Offset Voltage
- c. Open-Loop Output Impedance
- d. Feedback network

3. Output capacitance results in an additional _____ which degrades the phase margin.

- a. pole in the Aol curve
- b. zero in the Aol curve
- c. pole-zero pair in the Aol curve

Quiz: Stability 5

4. (T/F) The Riso compensation technique works by adding a zero to cancel the Aol pole from the capacitive load.

- a. True
- b. False

5. (T/F) The frequency of the zero in the Riso compensation method is based on the values of:

- a. Riso, Ro, Cload
- b. Riso, Cload
- c. Ro, Cload

6. (T/F) DC voltage errors due to the voltage drop across Riso are a disadvantage to the Riso compensation method.

- a. True
- b. False


Stability 5

Exercises


TI Precision Labs – Op Amps



 1. Compensate the amplifier circuit using an R_{ISO} resistor so the final circuit has at least 60° of phase margin.




1335 - Stability 5 - Problem 1.TSC

 

2. Compensate the amplifier circuit using an R_{ISO} resistor so the final circuit has at least 60° of phase margin.



1335 - Stability 5 - Problem 2.TSC

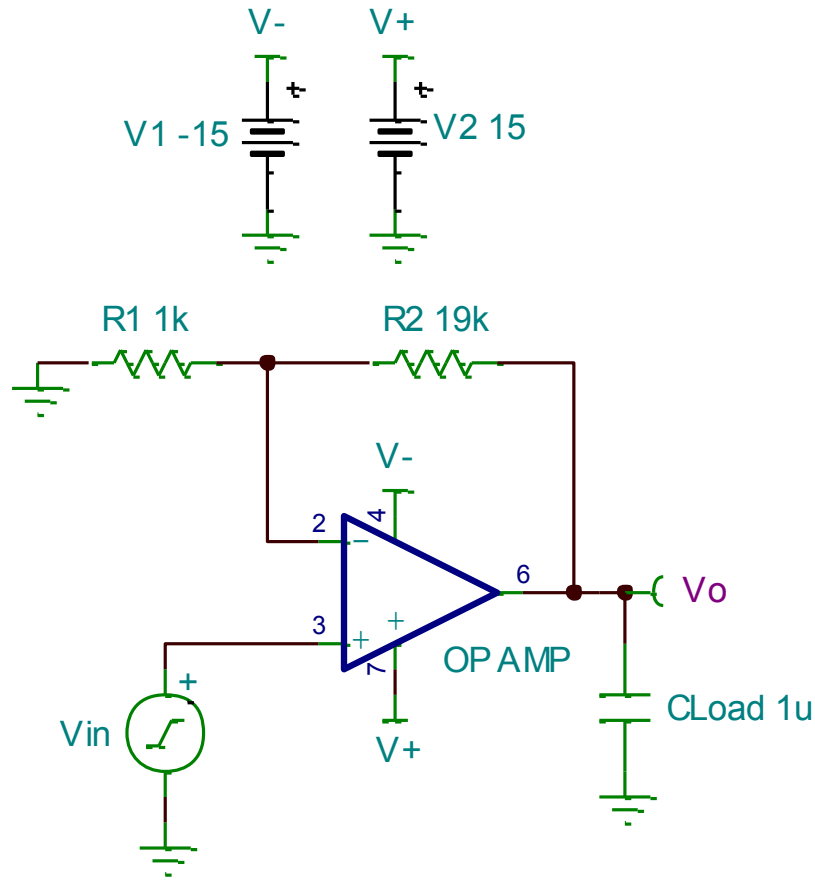



Stability 5

Solutions

TI Precision Labs – Op Amps





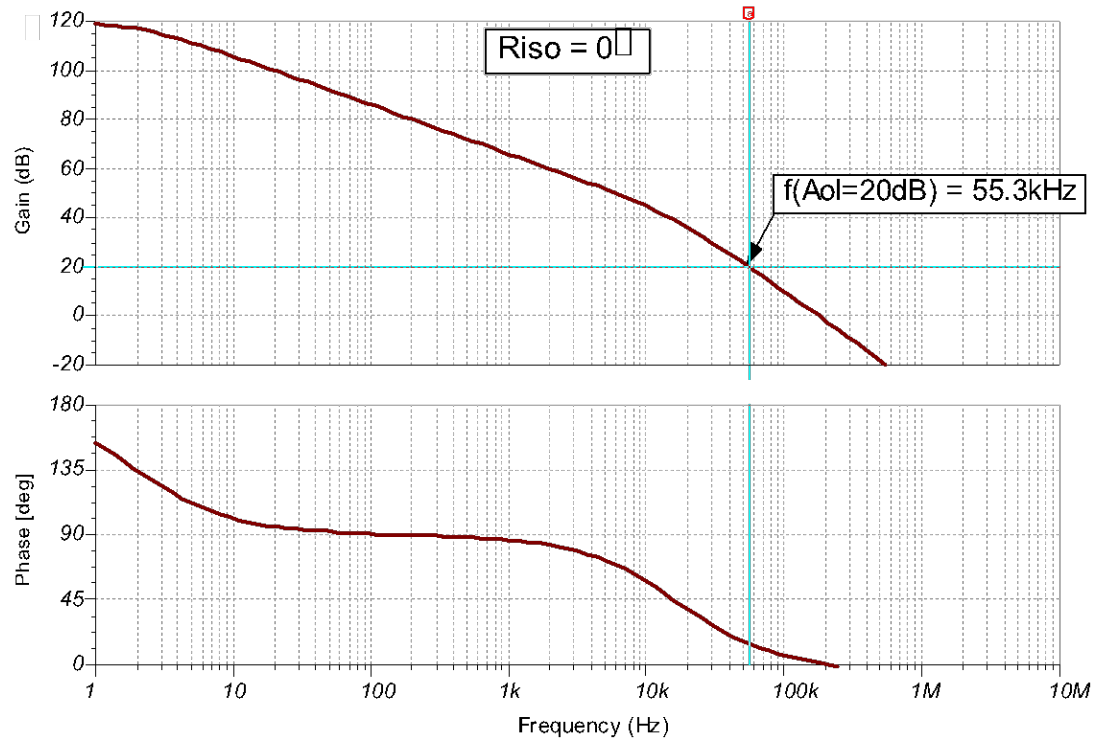 1. Compensate the amplifier circuit using an R_{ISO} resistor so the final circuit has at least 60° of phase margin.





1335 - Stability 5 - Problem 1 - Solution.TSC

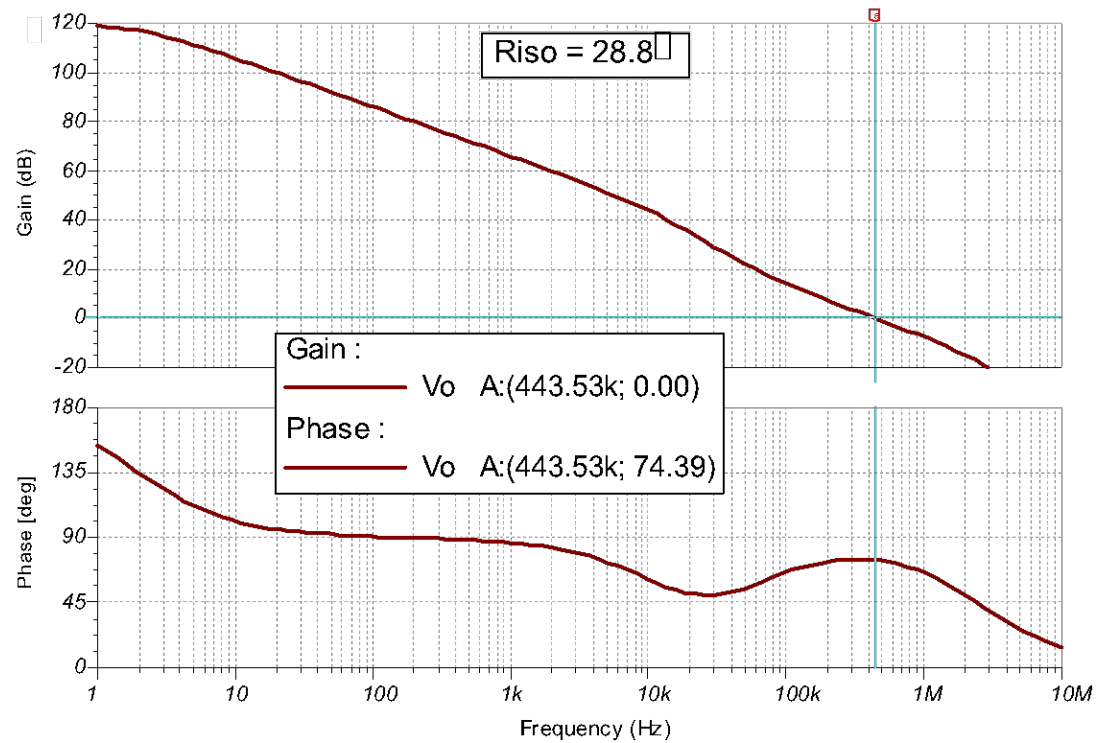 1. Simulate the percent overshoot and ac gain peaking for the following circuit. Based on these indirect measurements, what is the $A_oI\beta$ phase margin?



 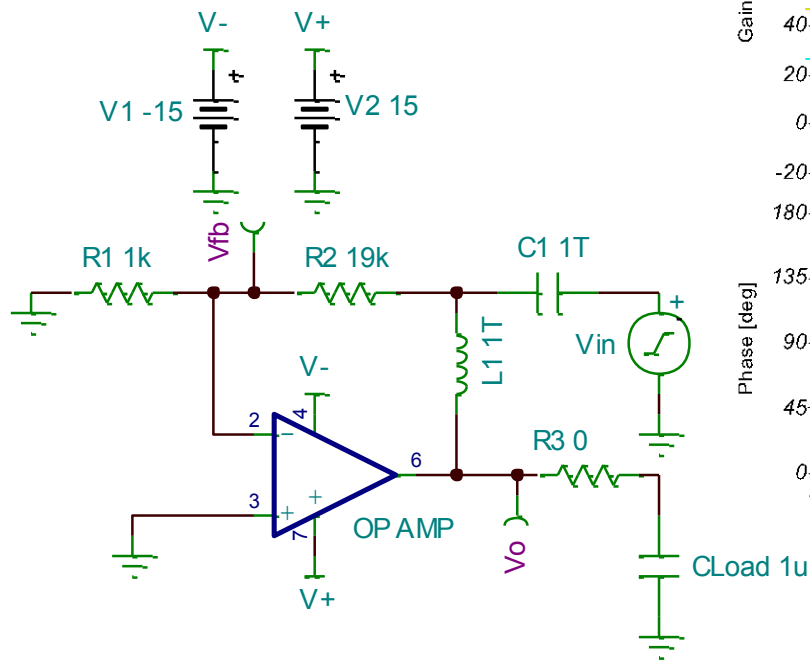2. Compensate the amplifier circuit using an R_{ISO} resistor so the final circuit has at least 60° of phase margin.



1335 - Stability 5 - Problem 2 - Solution.TSC

2. Compensate the amplifier circuit using an R_{ISO} resistor so the final circuit has at least 60° of phase margin.

