


# Driving a SAR ADC with a Fully Differential Amplifier

**TIPL 4103**  
**TI Precision Labs – ADCs**

Created by Luis Chioye, Art Kay, Samir Cherian


Presented by Peggy Liska

# Fully Differential Amplifier or FDA

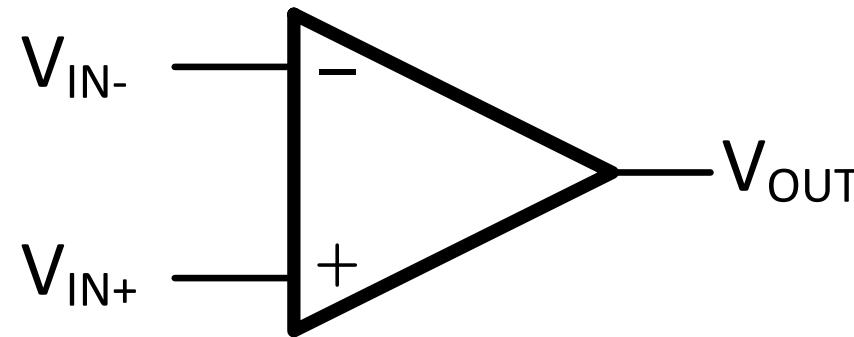
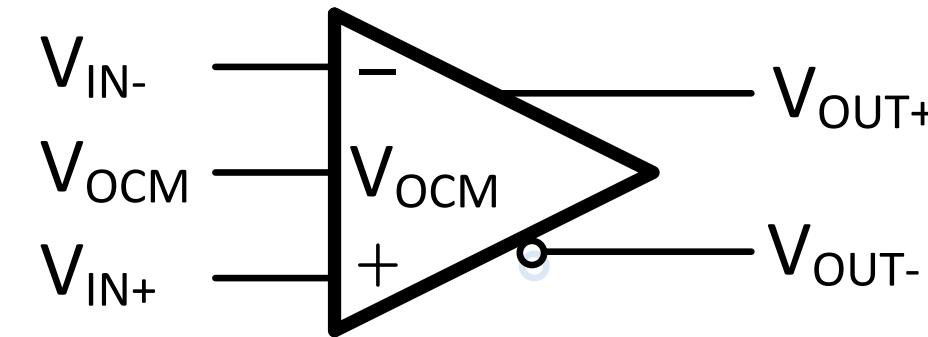
## Standard Operational Amplifier


- Differential in
- Single-ended out
- Output Common Mode is  $V_{OUT}$
- Single feedback paths




## Fully-Differential Amplifier

- Differential in
- Differential out
- Output Common-mode set by  $V_{OCM}$
- Multiple feedback paths
- Double the dynamic range of amplifier
- Even order harmonic distortion canceled

# Fully Differential Amplifier or FDA

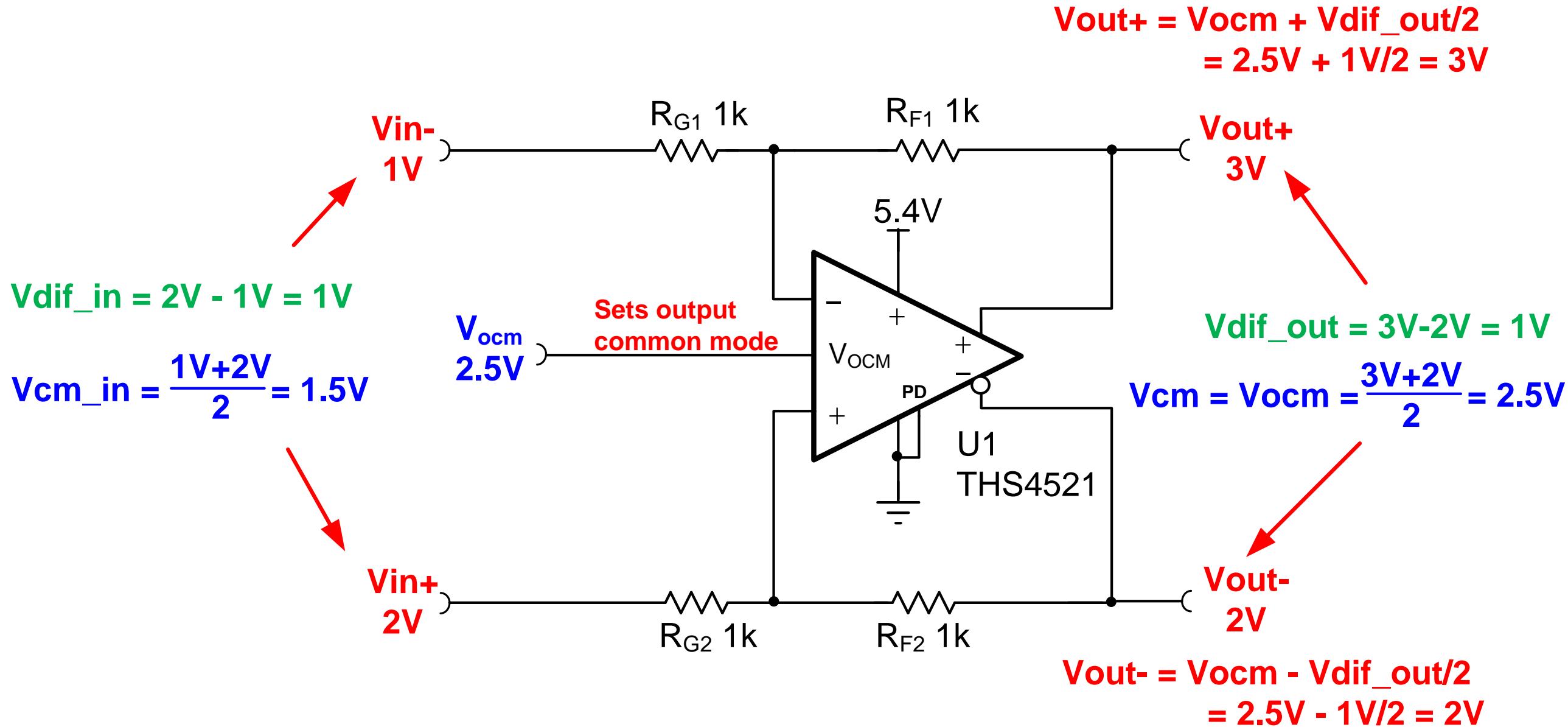


# Integrated FDA – THS4551 block diagram

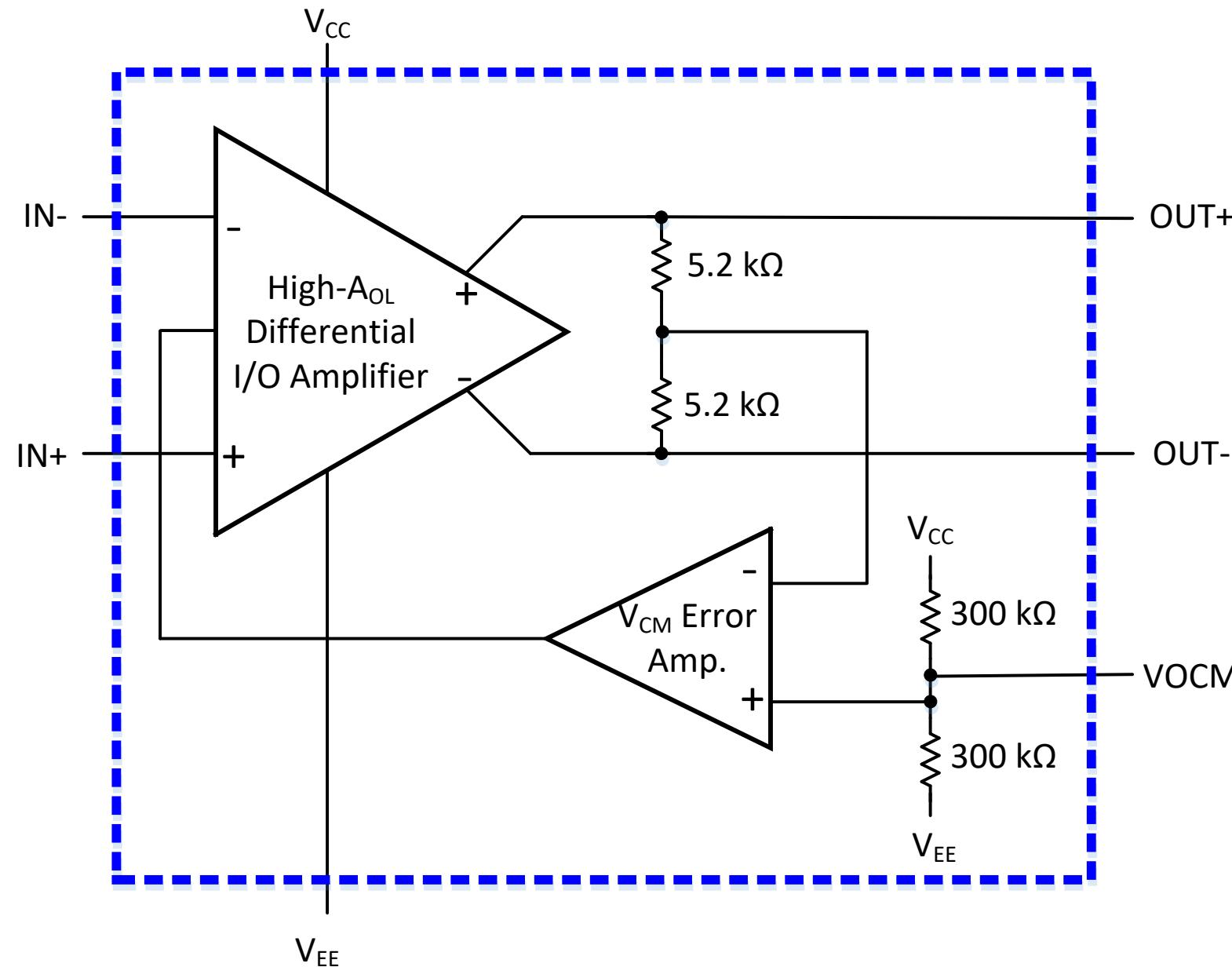

- Integrated fully-differential, high A<sub>OL</sub> amplifier
- Integrated wide-bandwidth, common-mode feedback, error amplifier
- Integrated resistors to detect the average output common-mode voltage
- Integrated mid-supply, common mode setting resistors


# FDA Distortion Considerations

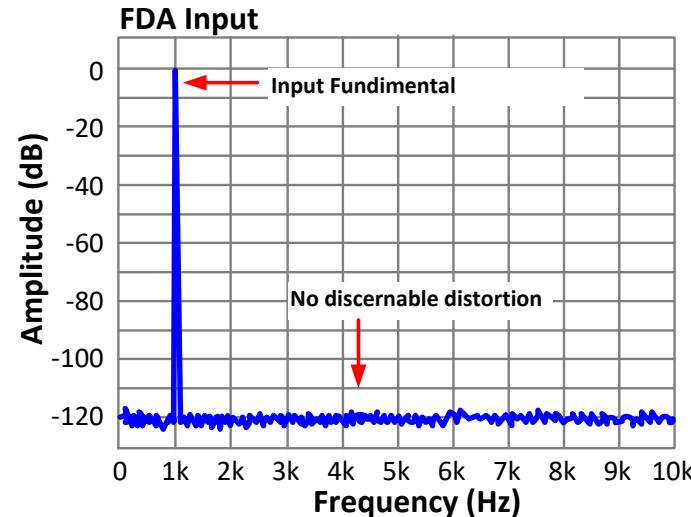

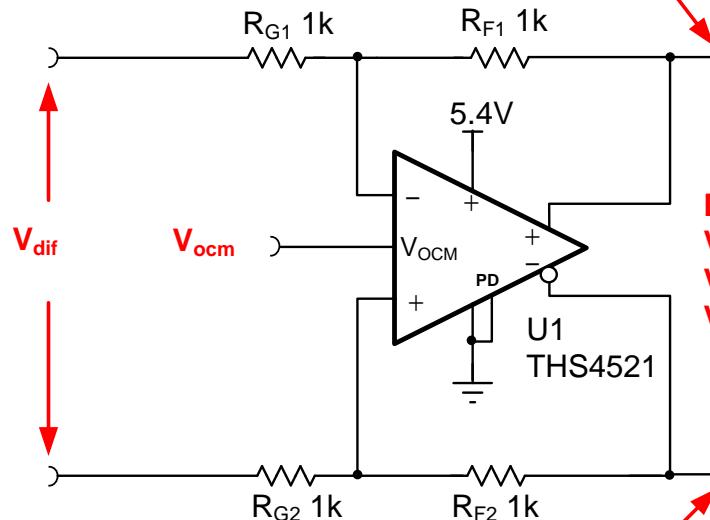**Non-Inverting Output**

$$g_a(x) = a_0 + a_1 \cdot x + a_2 \cdot x^2 + a_3 \cdot x^3 + a_4 \cdot x^4 + a_5 \cdot x^5 + \dots$$

$$V_{out\_pos} = a_0 + a_1 \cdot (V_{dif}) + a_2 \cdot (V_{dif})^2 + a_3 \cdot (V_{dif})^3 + a_4 \cdot (V_{dif})^4 + a_5 \cdot (V_{dif})^5 + \dots$$




**Inverting Output**

$$g_b(x) = b_0 + b_1 \cdot x + b_2 \cdot x^2 + b_3 \cdot x^3 + b_4 \cdot x^4 + b_5 \cdot x^5 + \dots$$

$$V_{out\_neg} = b_0 + b_1 \cdot (-V_{dif}) + b_2 \cdot (-V_{dif})^2 + b_3 \cdot (-V_{dif})^3 + b_4 \cdot (-V_{dif})^4 + b_5 \cdot (-V_{dif})^5 + \dots$$
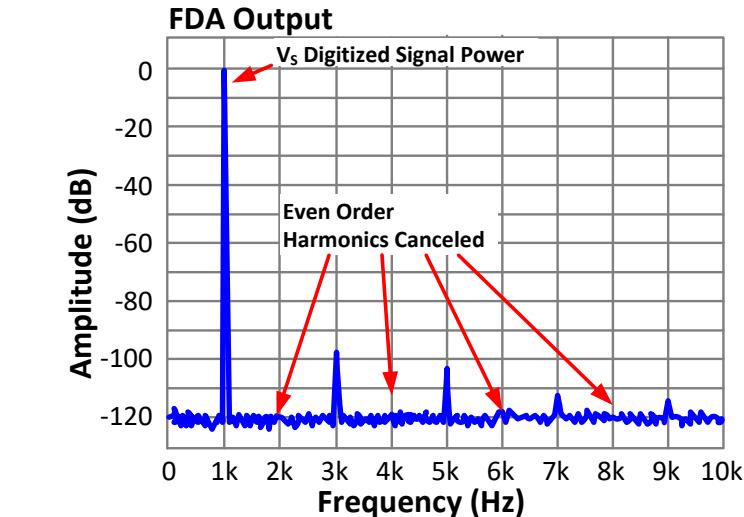
$$V_{out\_neg} = b_0 - b_1 \cdot (V_{dif}) + b_2 \cdot (V_{dif})^2 - b_3 \cdot (V_{dif})^3 + b_4 \cdot (V_{dif})^4 - b_5 \cdot (V_{dif})^5 + \dots$$






**Differential Output**

$$V_{out\_dif} = V_{out\_pos} - V_{out\_neg}$$




$$V_{out\_dif} = a_0 + b_0 + (a_1 + b_1) \cdot (V_{dif}) + (a_2 - b_2) \cdot (V_{dif})^2 + (a_3 + b_3) \cdot (V_{dif})^3 + (a_4 - b_4) \cdot (V_{dif})^4 + (a_5 + b_5) \cdot (V_{dif})^5 + \dots$$

$$V_{out\_dif} = a_0 + b_0 + (a_1 + b_1) \cdot (V_{dif}) + (a_2 - b_2) \cdot (V_{dif})^2 + (a_3 + b_3) \cdot (V_{dif})^3 + (a_4 - b_4) \cdot (V_{dif})^4 + (a_5 + b_5) \cdot (V_{dif})^5 + \dots$$

# FDA Distortion Considerations

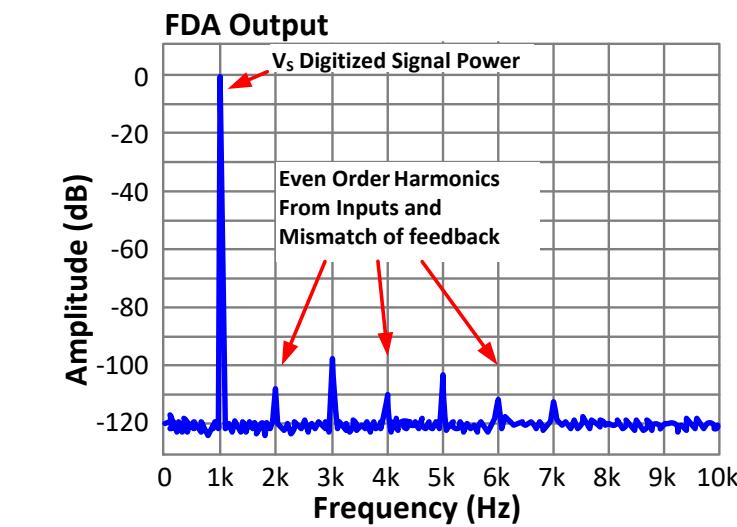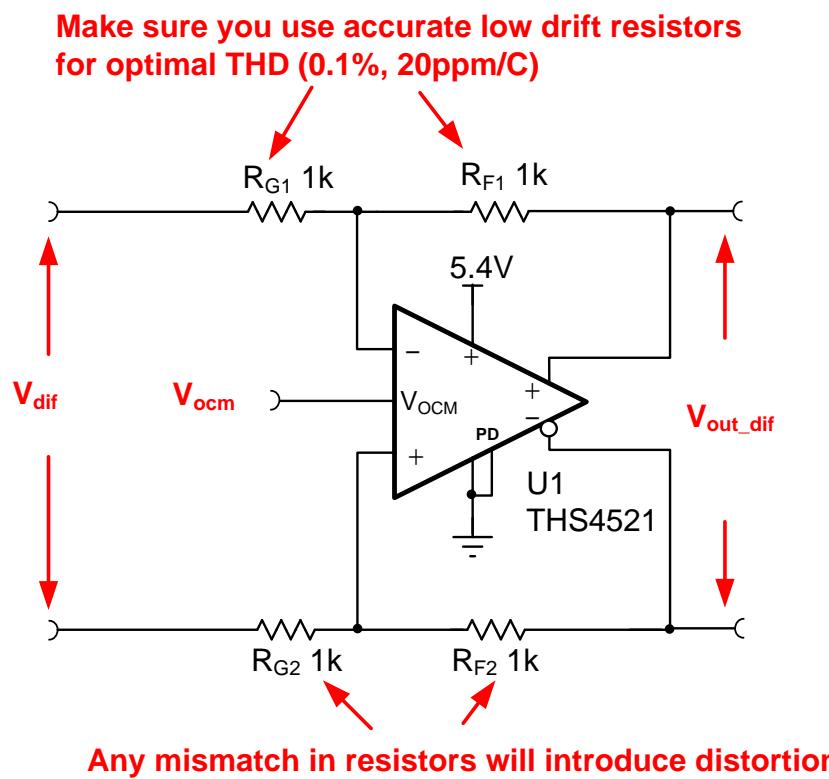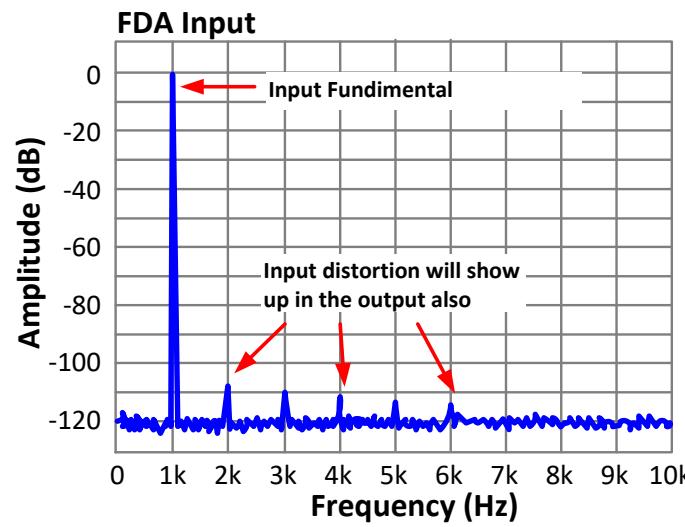
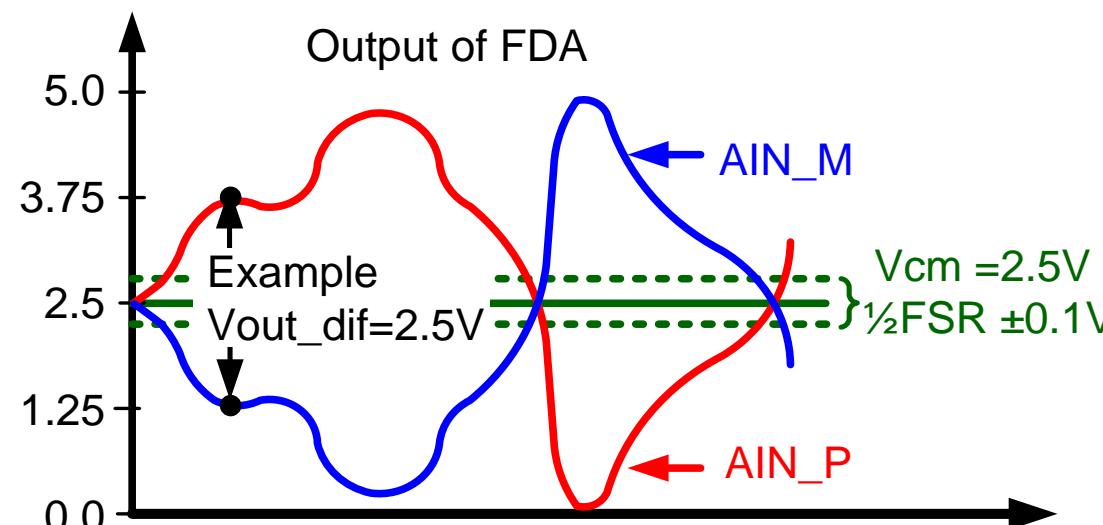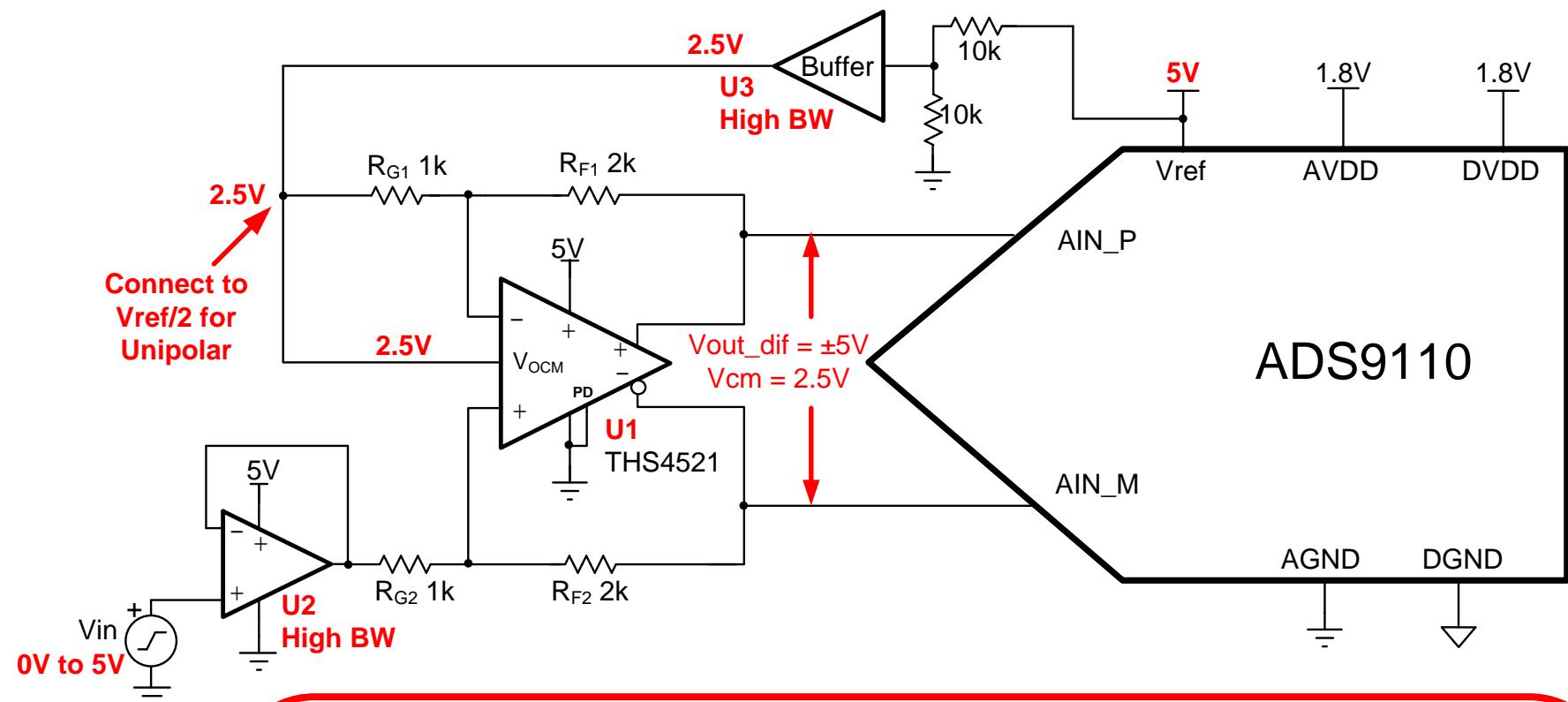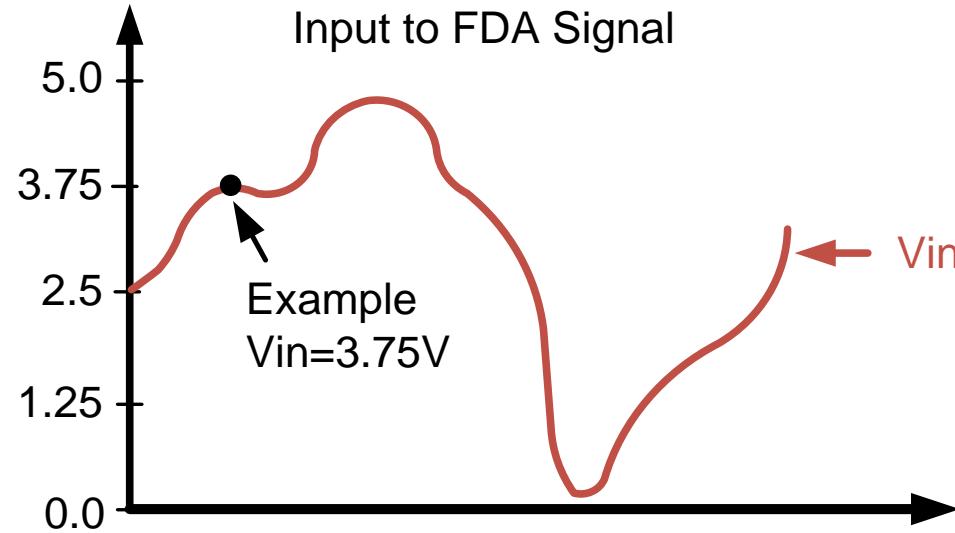
# FDA – Single Ended Unipolar to Differential



Equations for this Configuration

$$A_{vdif} = \frac{R_F}{R_G}$$

$$V_{OutP} = \left( \frac{A_{vdif}}{2} \right) \cdot (V_{in} - V_{OCM}) + V_{OCM}$$

$$V_{OutN} = -\left( \frac{A_{vdif}}{2} \right) \cdot (V_{in} - V_{OCM}) + V_{OCM}$$

$$V_{OutDif} = A_{vdif} \cdot (V_{in} - V_{OCM})$$

Example Calculation:  $V_{in} = 3.75V$




$$A_{vdif} = \frac{R_F}{R_G} = \frac{2k\Omega}{1k\Omega} = 2 V/V$$

$$V_{OutP} = \left( \frac{2}{2} \right) \cdot (3.75V - 2.5V) + 2.5V = 3.75V$$

$$V_{OutN} = -\left( \frac{2}{2} \right) \cdot (3.75V - 2.5V) + 2.5V = 1.25V$$

$$V_{OutDif} = 2 \cdot (3.75V - 2.5V) = 2.5V$$
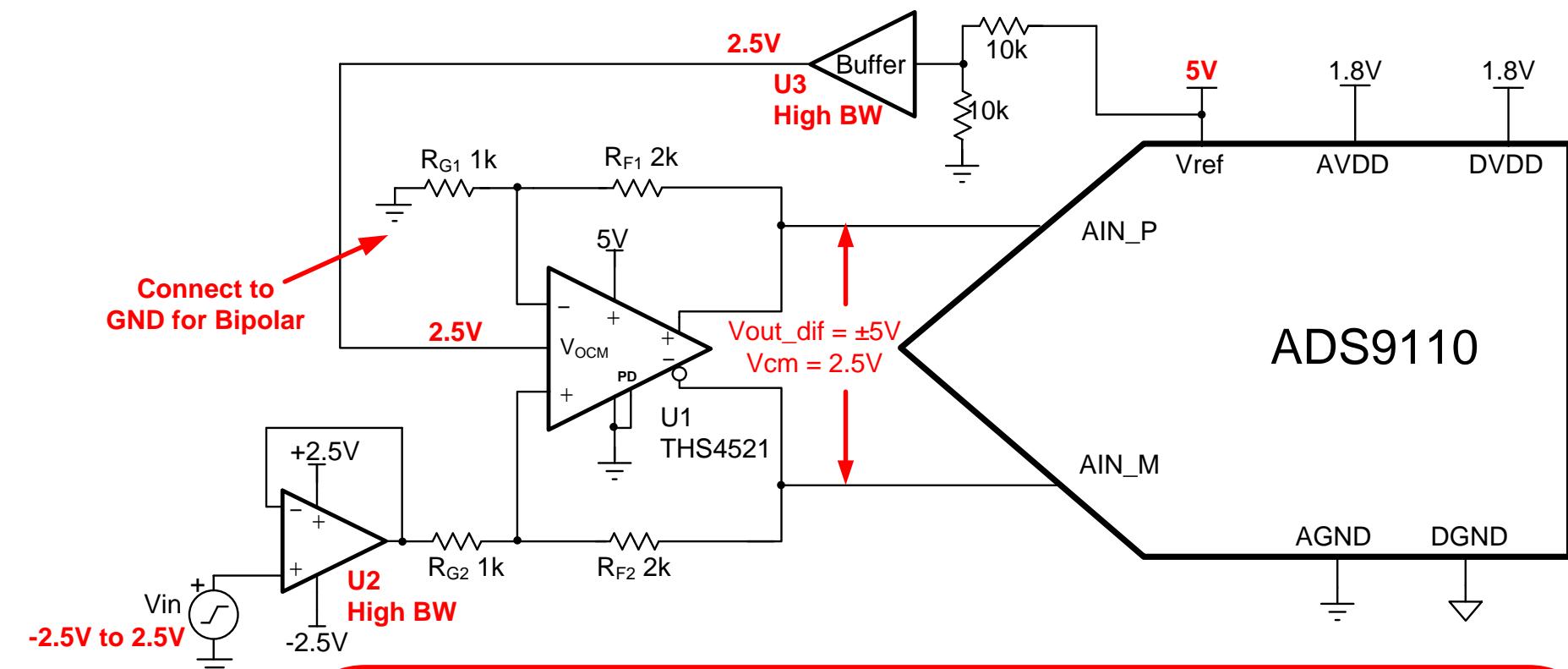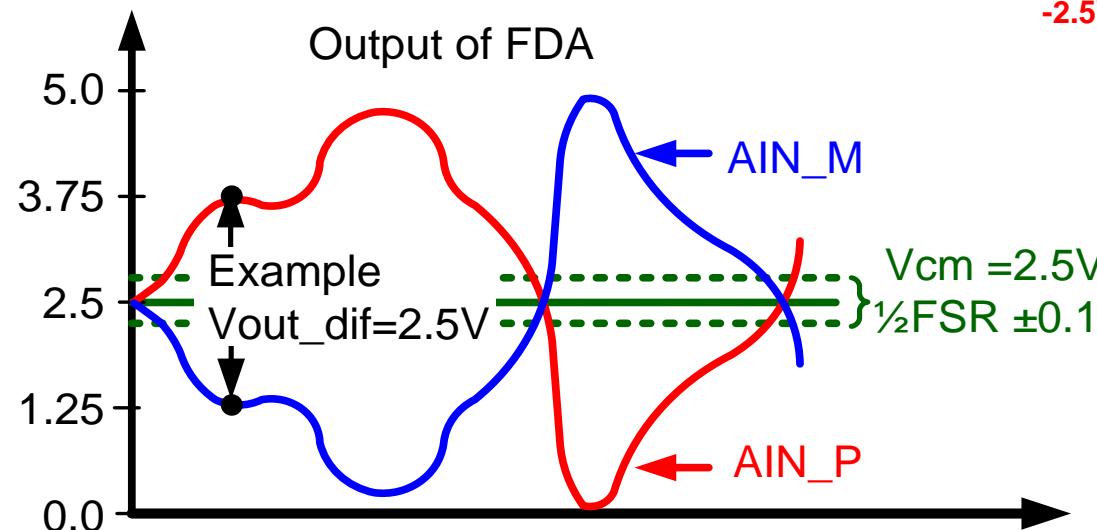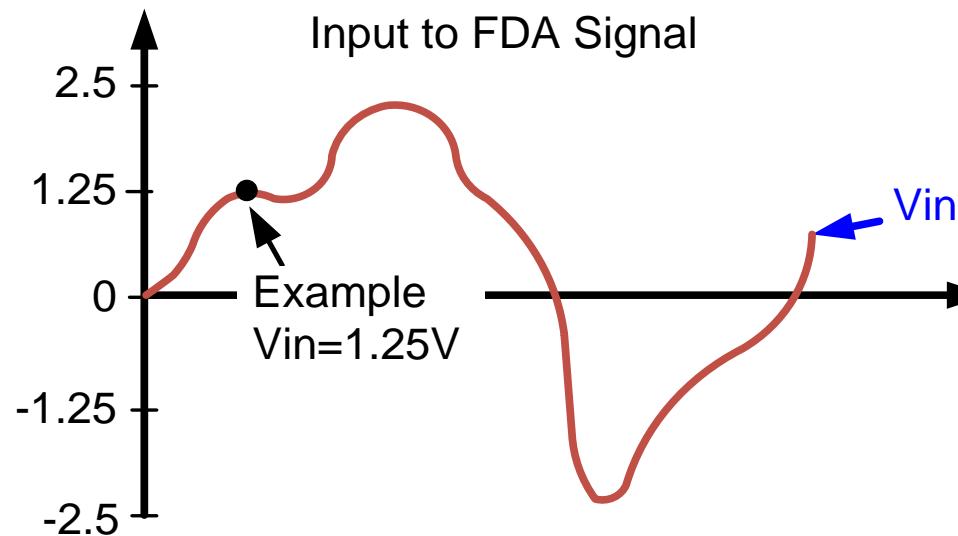
# FDA – Single Ended Bipolar to Differential



Equations for this Configuration

$$A_{vdif} = \frac{R_F}{R_G}$$

$$V_{OutP} = \left( \frac{A_{vdif}}{2} \right) \cdot (V_{in}) + V_{OCM}$$

$$V_{OutN} = -\left( \frac{A_{vdif}}{2} \right) \cdot (V_{in}) + V_{OCM}$$

$$V_{OutDif} = A_{vdif} \cdot (V_{in})$$

Example Calculation:  $V_{in} = 3.75V$




$$A_{vdif} = \frac{R_F}{R_G} = \frac{2k\Omega}{1k\Omega} = 2 V/V$$

$$V_{OutP} = \left( \frac{2}{2} \right) \cdot (1.25V) + 2.5V = 3.75V$$

$$V_{OutN} = -\left( \frac{2}{2} \right) \cdot (1.25V) + 2.5V = 1.25V$$

$$V_{OutDif} = 2 \cdot (3.75V - 1.25V) = 2.5V$$

# Improve Linear Range

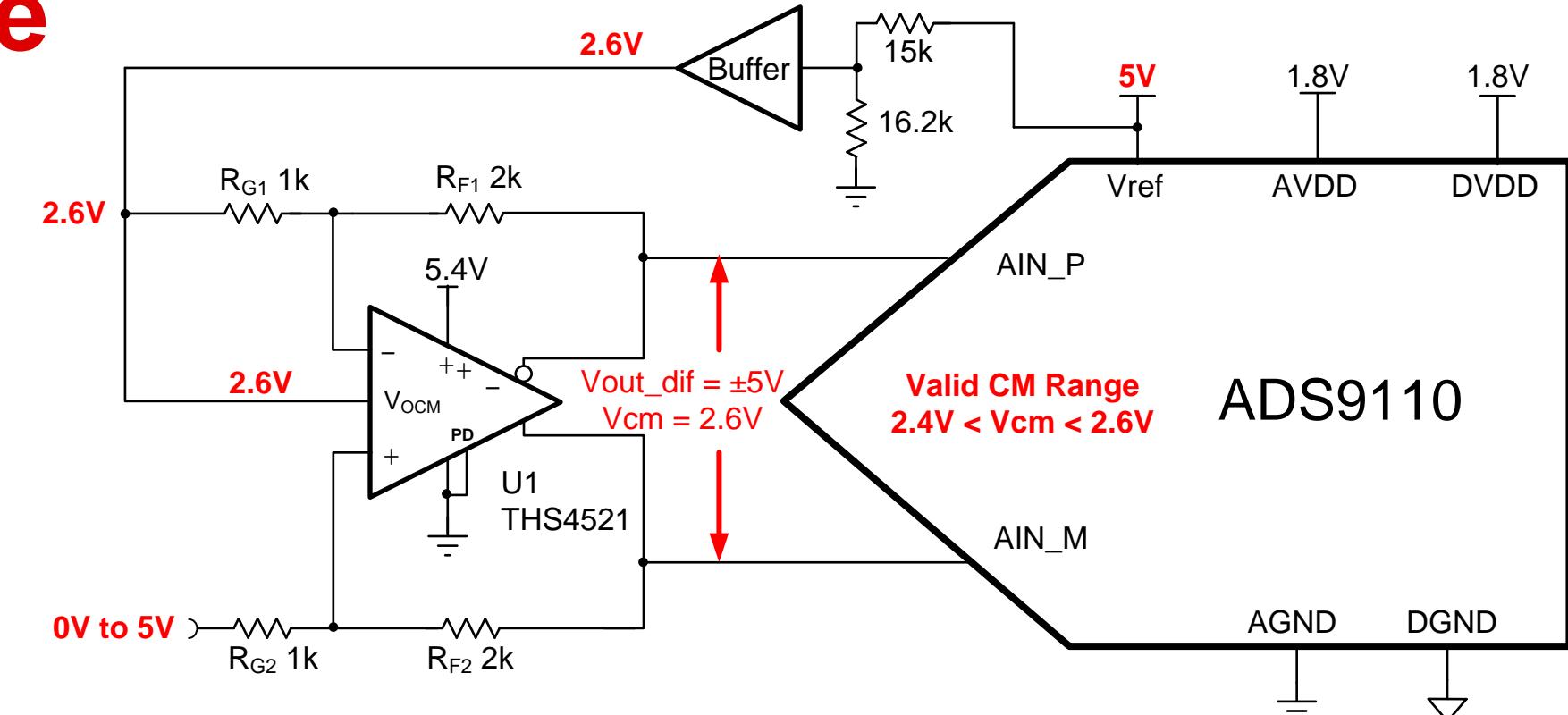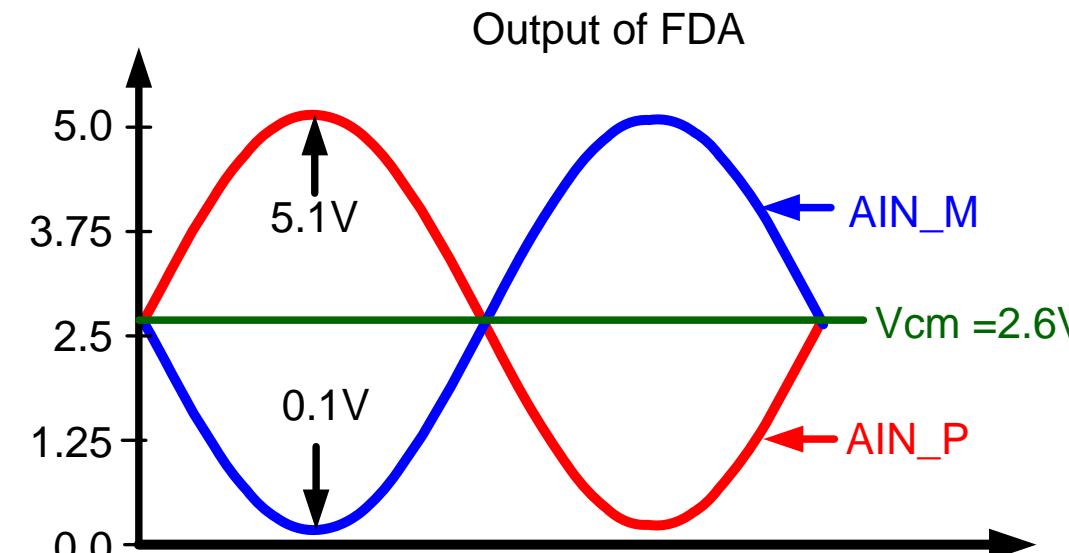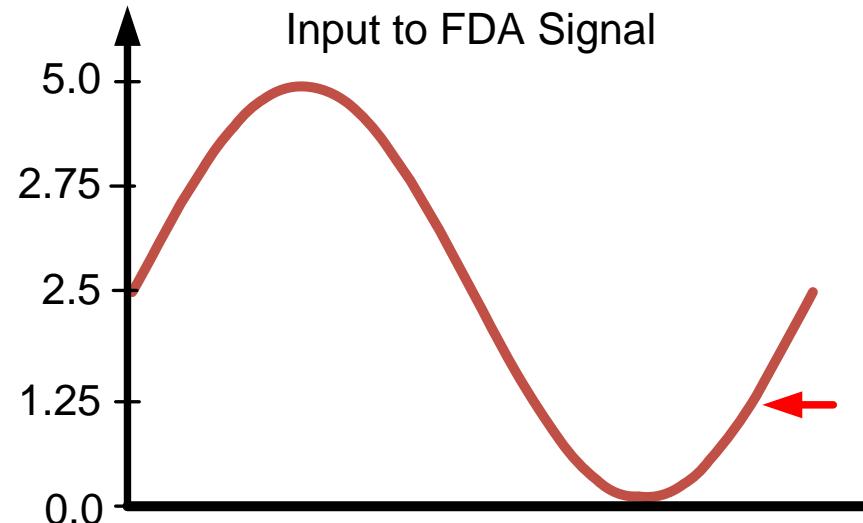

PARAMETER THS4521	MIN	TYP	MAX	UNIT
Output voltage low			$(V-) + 0.1$	V
Output voltage high		$(V+) - 0.3$	$(V+) - 0.25$	V

PARAMETER ADS9110	MIN	TYP	MAX	UNIT
Full-scale input voltage span	$-V_{ref}$		$V_{ref}$	V
Absolute Input voltage range	$AIN$ to GND	-0.1	$AVDD + 0.1$	V
Common-mode voltage range		$(V_{ref}/2) - 0.1$	$(V_{ref}/2) + 0.1$	V

**Thanks for your time!  
Please try the quiz.**

# Quiz: Driving a SAR ADC with a Fully Differential Amplifier

TIPL 4103

TI Precision Labs – ADCs

Created by Art Kay


# Quiz: Linear Range ADC + FDA

1. Design a FDA circuit topology to translate a single ended 0V to 1V, to 0V to 4V. Use THS4551, OPA320, and ADS9110 with a 4.096V reference. Will the output be linear over the full 0V to 1V signal range?
2. Design a FDA circuit topology to translate a single ended -0.1V to +0.1V, to 0V to 2.5V. Use THS4551, OPA320, and ADS9110 with a 2.5V reference. Will the output be linear over the full 0V to 1V signal range?
3. (T/F) Assume the input signal applied to an FDA has both even and odd order harmonics. The the FDA will cancel the even order harmonics.
4. (T/F) The V<sub>ocom</sub> pin can be directly connected to a voltage divider to set it's output common mode.

# Solutions

# Quiz: Linear Range ADC + FDA

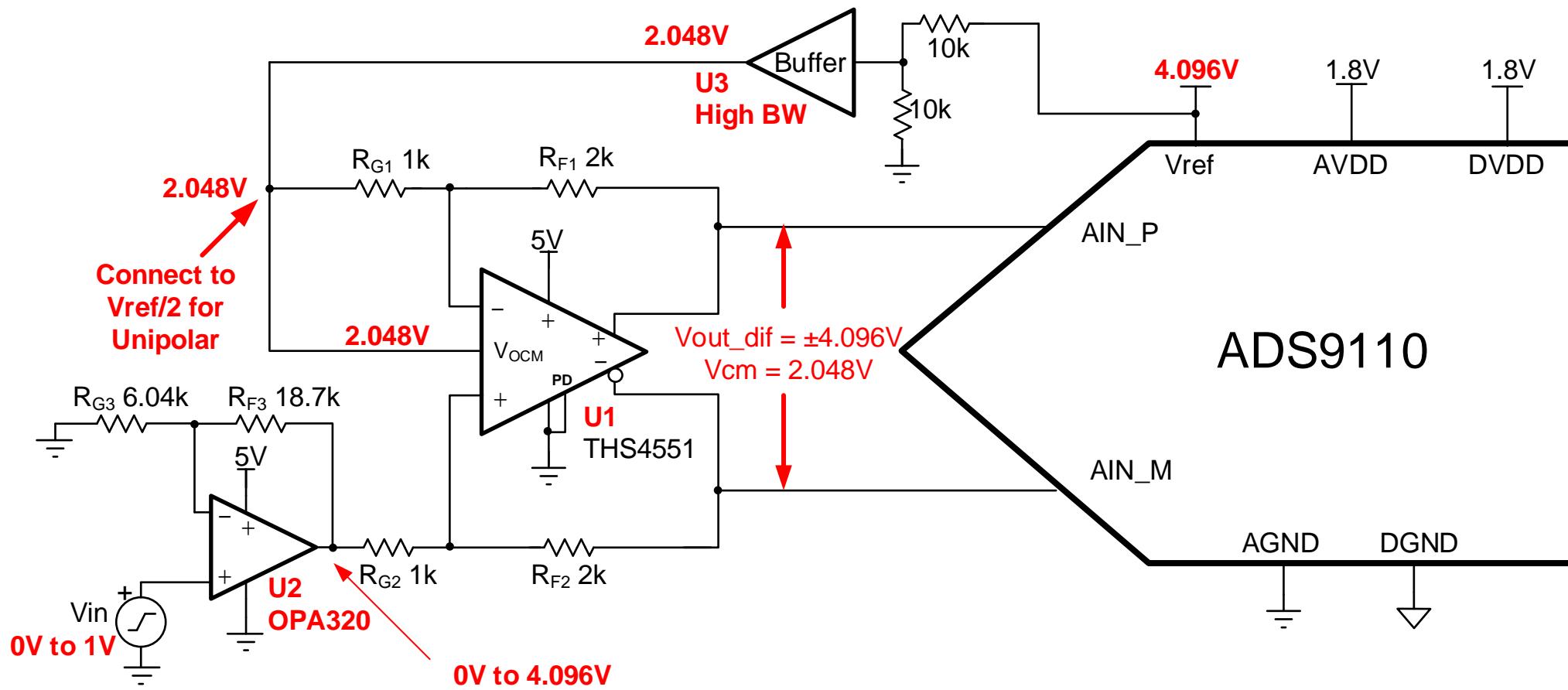1. Design a FDA circuit topology to translate a single ended 0V to 1V, to 0V to 4V. Use THS4551, OPA320, and ADS9110 with a 4.096V reference. Will the output be linear over the full 0V to 1V signal range?



Type	R <sub>f</sub> Non-Inverting 1.87k
R1	604
Target Gain (R <sub>f</sub> /R1)	4.096
Best Gain	4.096
Tolerance	Error(%) 0.1% E198
0.000647	
OK	Help


Analog engineer's calculator used to select U2 Feedback resistors

# Quiz: Linear Range ADC + FDA

## Problem 1: continued.

PARAMETER OPA320	TEST CONDITION	MIN	TYP	MAX	UNIT
<b>INPUT VOLTAGE</b>					
Common-mode voltage range	$V_{cm}$	(V-) - 0.1		(V+)+0.1	V
<b>OUTPUT</b>					
Voltage swing from both rails	$V_o$	RL = 10kΩ	10	20	mV
		RL = 2kΩ	25	35	
<b>OPEN-LOOP GAIN</b>					
Open-loop gain	$A_{OL}$	0.1 < $V_o < (V+)-0.1V$ , $R_L = 10k\Omega$	114	132	dB
		0.2 < $V_o < (V+)-0.2V$ , $R_L = 2k\Omega$	108	123	

Amplifier input range	-0.1V < $V_{cm}$ < 5.1V
Amplifier output range	0.02 < $V_o$ < 4.98V
Amplifier Linear Range	0.1 < $V_o$ < 4.9V
Worst Case Range	0.1 < $V_o$ < 4.9V

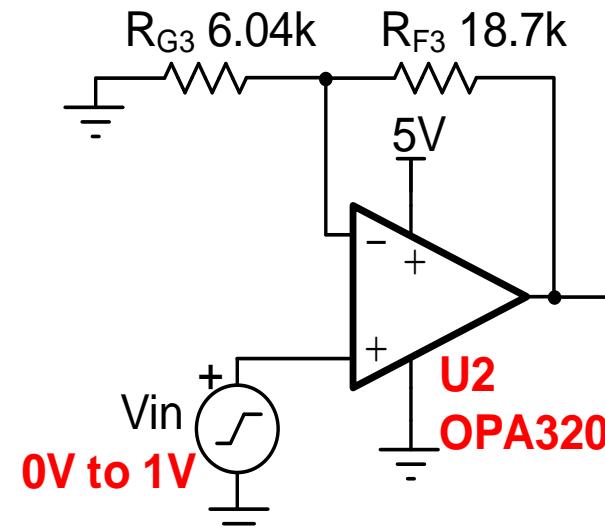




Target: 0V to 4.096V  
Linear range: 0.1V to 4.096V

# Quiz: Linear Range ADC + FDA

## Problem 1: continued.

PARAMETER THS4551	MIN	TYP	MAX	UNIT
Output voltage low		(V-) + 0.2	(V-) + 0.23	V
Output voltage high	(V+) - 0.23	(V+) - 0.2		V
Common mode input voltage low		(V-) + 0.2	(V-) - 0.1	V
Common mode input voltage high	(V+) - 1.2	(V+) - 1.1		V


input range	-0.1V < V <sub>cm</sub> < 3.8V
output range	0.23 < V <sub>O</sub> < 4.77V

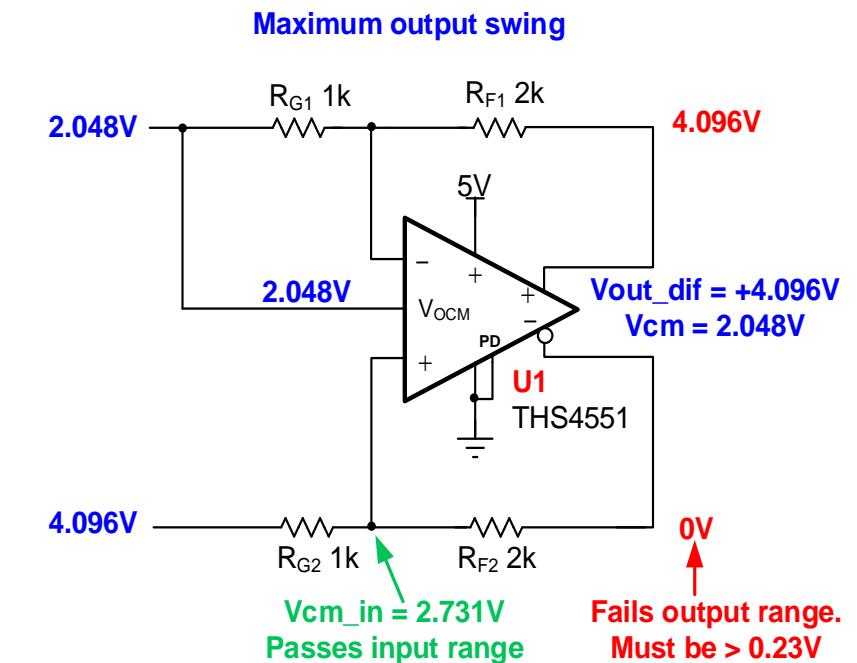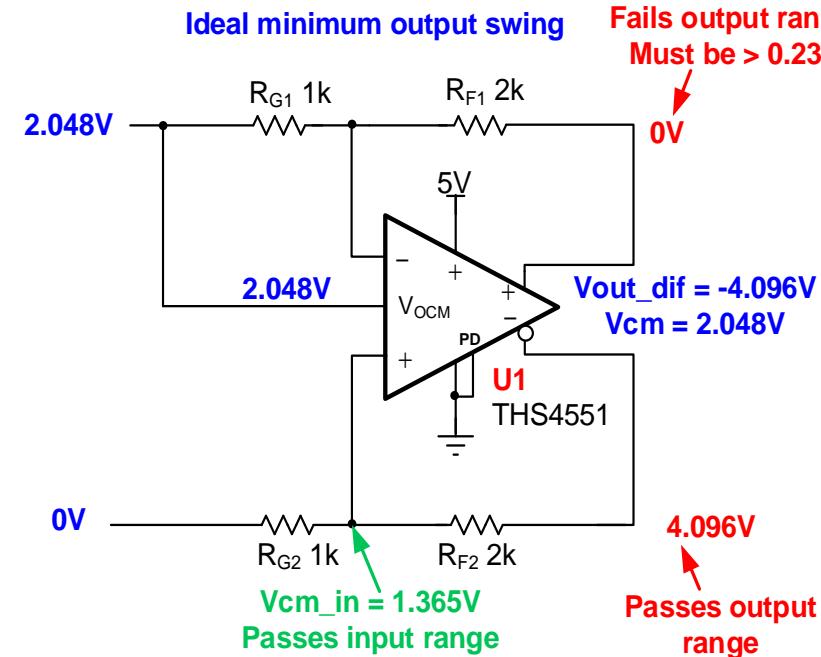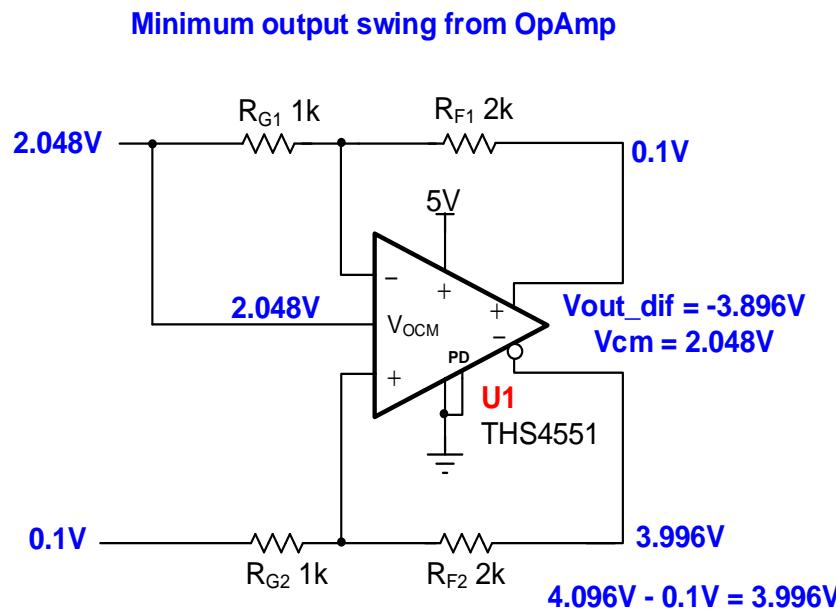

Note: The output swing low on the THS limits the range.

# Quiz: Linear Range ADC + FDA


Problem 1: continued.

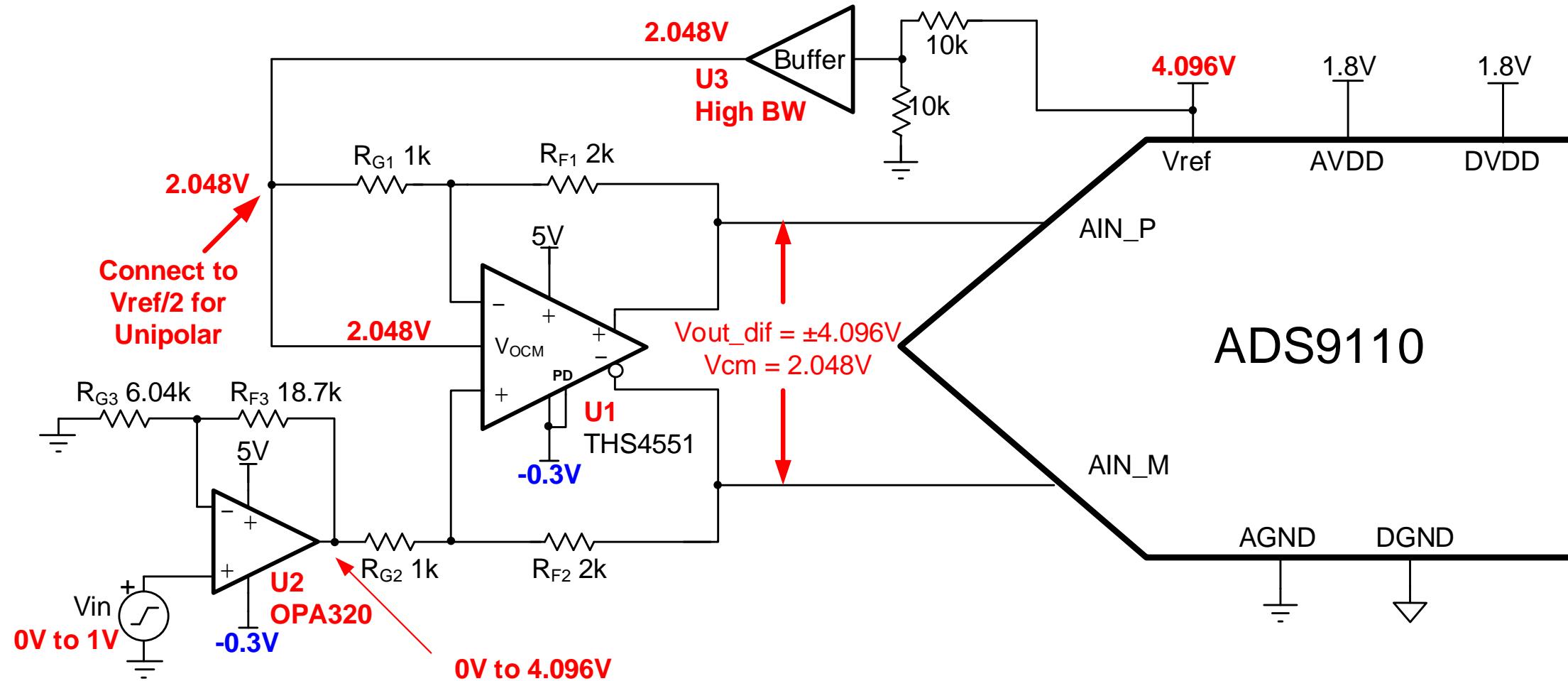

Note: One approach to avoiding the output swing limitation is a -0.3V negative supply.

# Quiz: Linear Range ADC + FDA

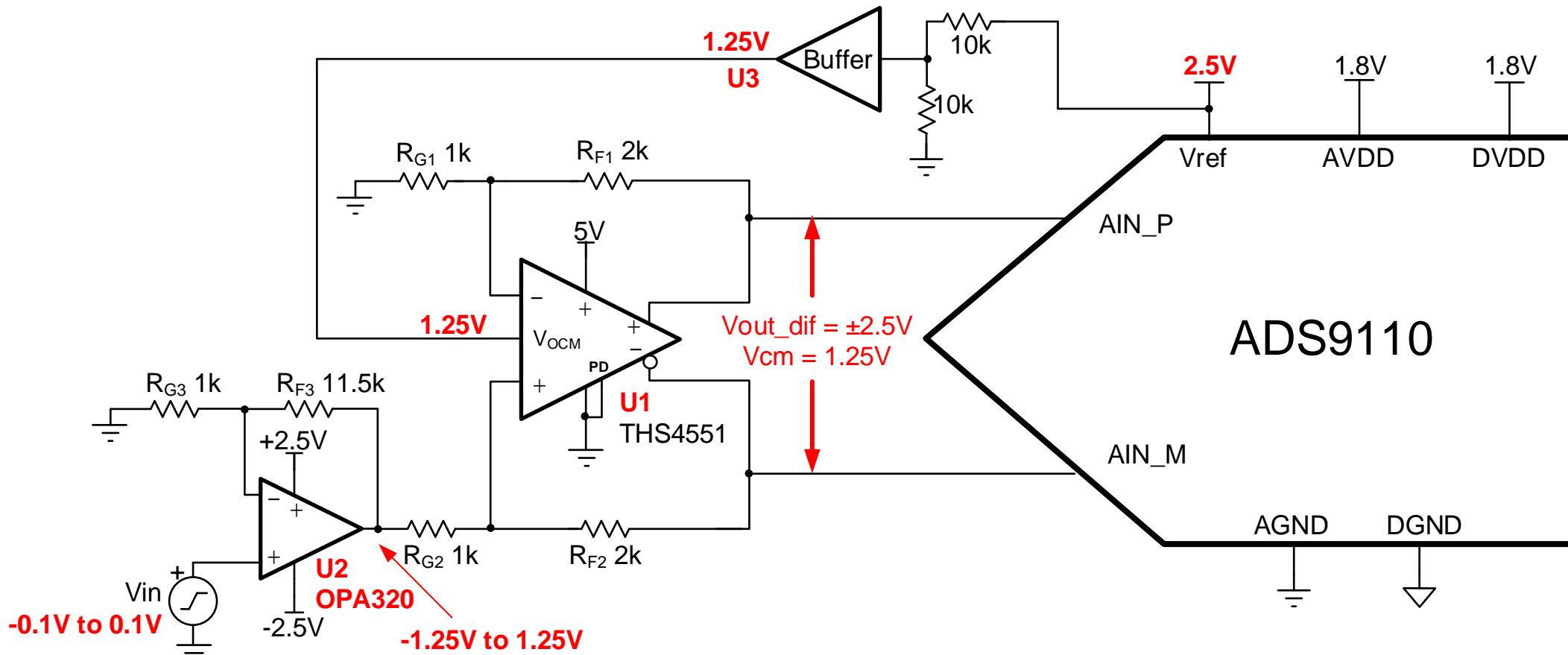2. Design a FDA circuit topology to translate a single ended -0.1V to +0.1V, to 0V to 2.5V. Use THS4551, OPA320, and ADS9110 with a 2.5V reference. Will the output be linear over the full 0V to 1V signal range?



Non-Inverting

1.15k

100

12.5

12.5

0.1% E198

OK

Help


Analog engineer's calculator used to select U2 Feedback resistors

# Quiz: Linear Range ADC + FDA

## Problem 2: continued.

PARAMETER OPA320	TEST CONDITION	MIN	TYP	MAX	UNIT
<b>INPUT VOLTAGE</b>					
Common-mode voltage range	$V_{cm}$	(V-) - 0.1		(V+)+0.1	V
<b>OUTPUT</b>					
Voltage swing from both rails	$V_o$	$RL = 10k\Omega$	10	20	mV
		$RL = 2k\Omega$	25	35	
<b>OPEN-LOOP GAIN</b>					
Open-loop gain	$A_{OL}$	$0.1 < V_o < (V+)-0.1V, R_L = 10k\Omega$	114	132	dB
		$0.2 < V_o < (V+)-0.2V, R_L = 2k\Omega$	108	123	

Amplifier input range	-2.6V < $V_{cm}$ < 2.6V
Amplifier output range	-2.48 < $V_o$ < 2.48V
Amplifier Linear Range	-2.4 < $V_o$ < 2.4V
Worst Case Range	-2.4 < $V_o$ < 2.4V

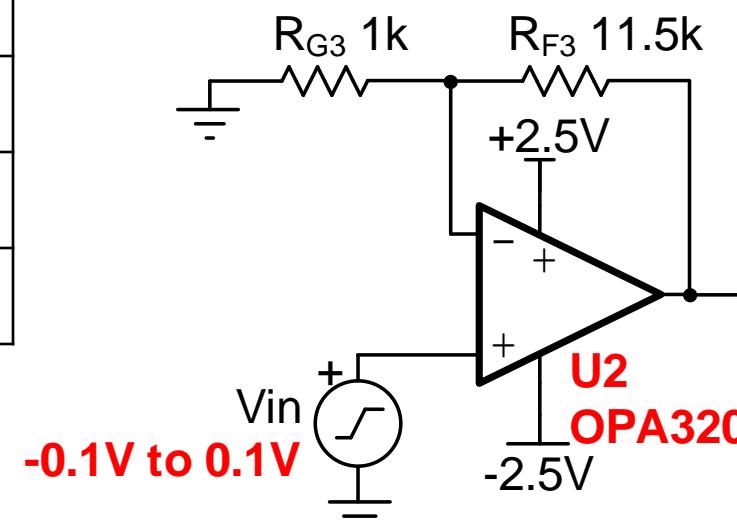



**Target:-1.25V to +1.25V**  
**Worst Case range: -2.4V to +2.4V**  
**Not limited**

# Quiz: Linear Range ADC + FDA

## Problem 2: continued.


PARAMETER THS4551	MIN	TYP	MAX	UNIT
Output voltage low		(V-) + 0.2	(V-) + 0.23	V
Output voltage high	(V+) - 0.23	(V+) - 0.2		V
Common mode input voltage low		(V-) + 0.2	(V-) - 0.1	V
Common mode input voltage high	(V+) - 1.2	(V+) - 1.1		V

input range	-0.1V < V <sub>cm</sub> < 3.8V
output range	0.23 < V <sub>O</sub> < 4.77V

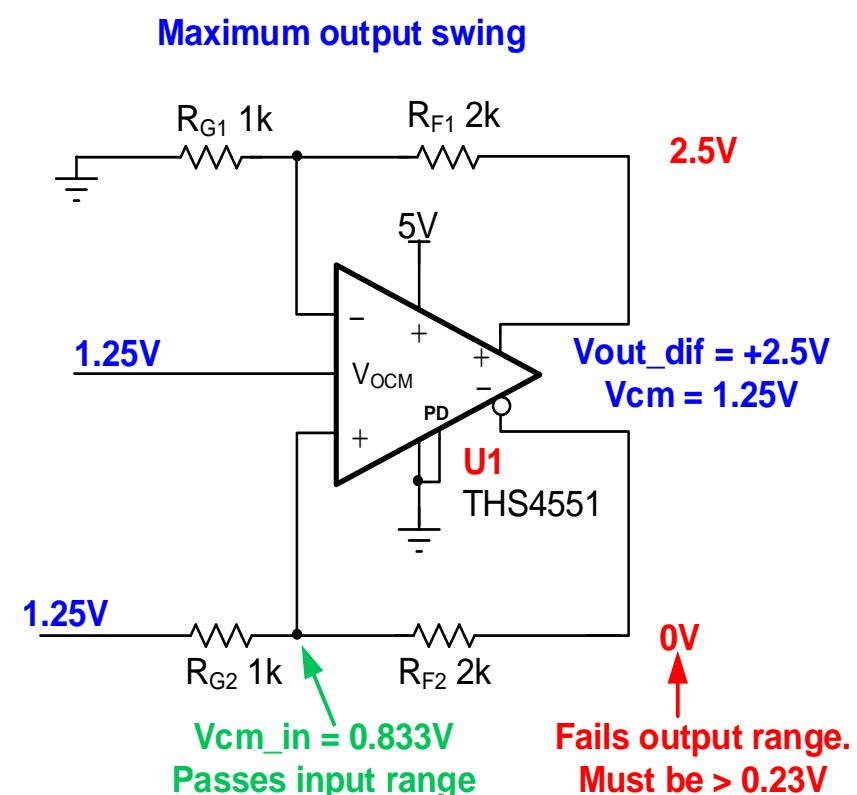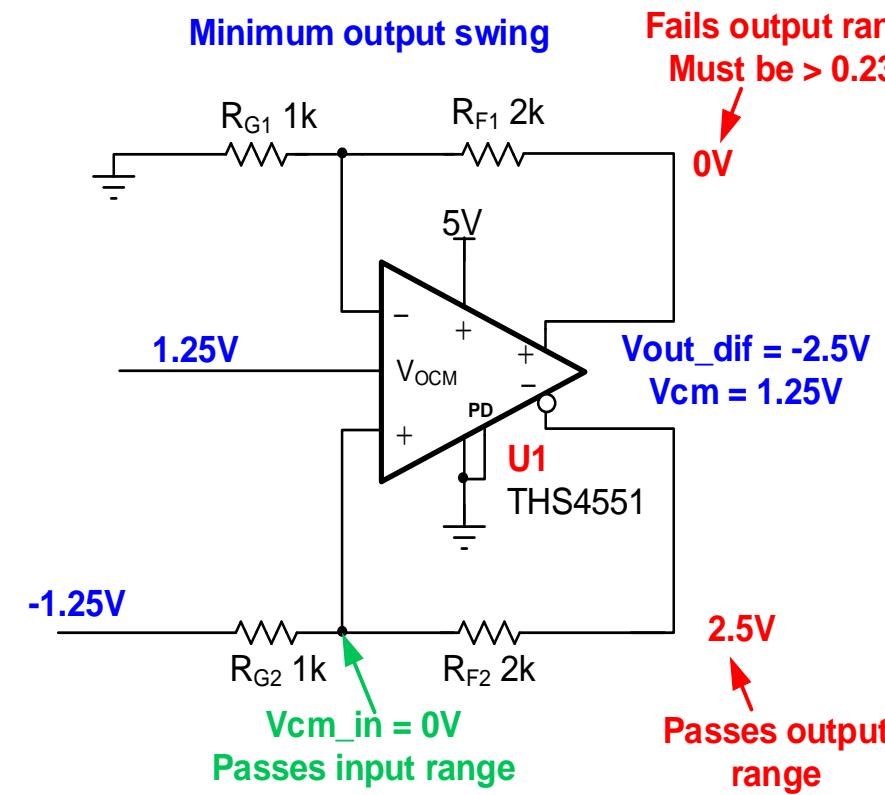

# Quiz: Linear Range ADC + FDA

Problem 2: continued.

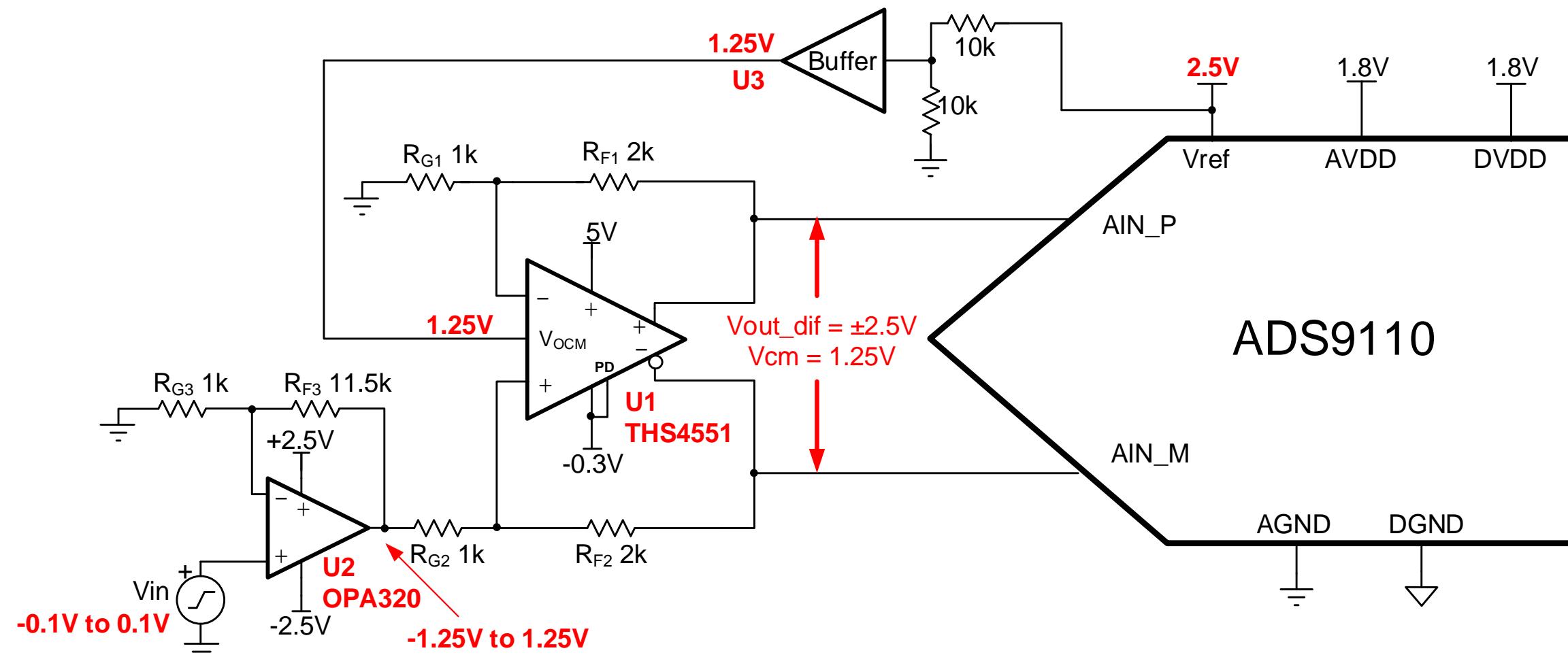

Note: One approach to avoiding the output swing limitation is a  $-0.3V$  negative supply.

# Quiz: Linear Range ADC + FDA

3. (**False**) Assume the input signal applied to an FDA has both even and odd order harmonics. The the FDA will cancel the even order harmonics.
4. (**False**) The Vocm pin can be directly connected to a voltage divider to set it's output common mode.