

Input & Output Limitations – 3

TIPL 1132

TI Precision Labs – Op Amps


Presented by Ian Williams

Prepared by Art Kay and Ian Williams


Prerequisites: Input & Output Limitations 1, 2

(TIPL 1130, TIPL 1131)

Real World Output Range

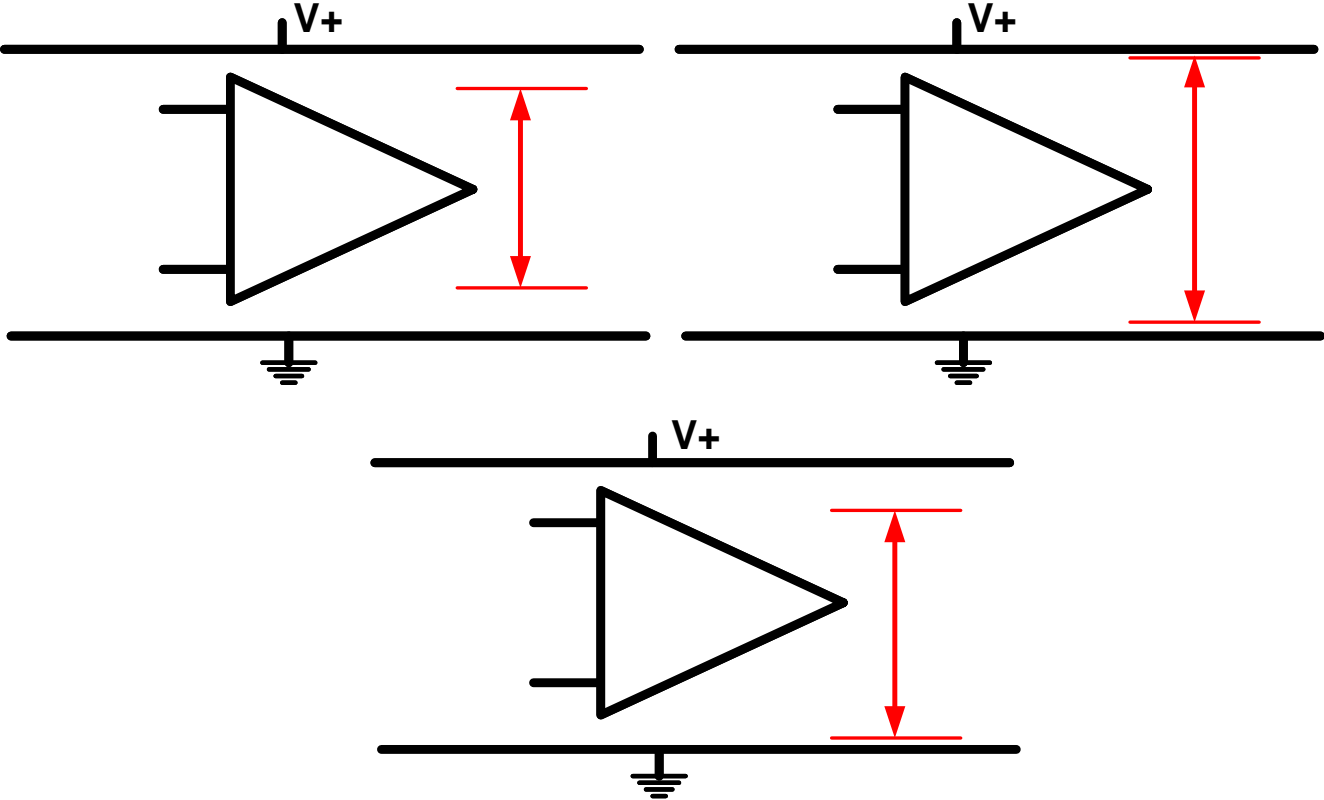

Classic Bipolar Output Stage

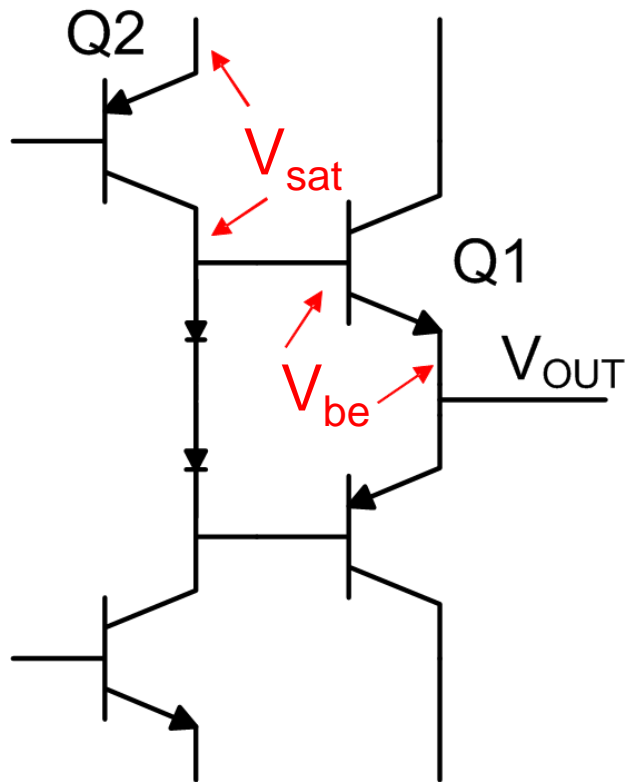


$$V_{OUT} \text{ swing headroom} = V_{sat} + V_{be}$$

Therefore,


$$V_{out_max} < +V_S - V_{sat} - V_{be}$$

$$V_{out_min} > -V_S + V_{sat} + V_{be}$$

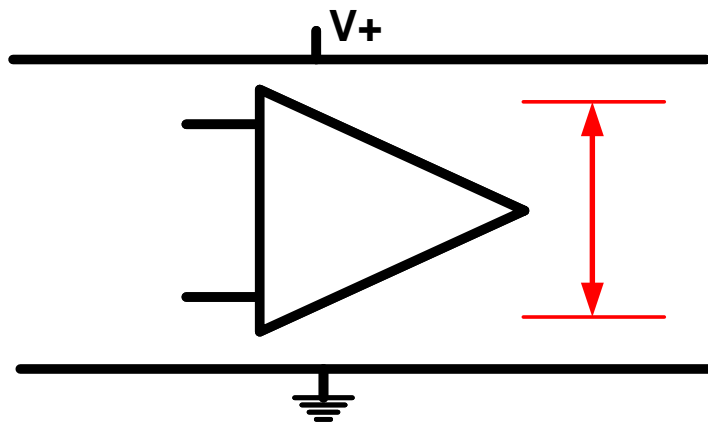


OPA827 – Classic Bipolar Output Stage

PARAMETER	CONDITIONS	STANDARD GRADE OPA827AI			UNIT
		MIN	TYP	MAX	
OUTPUT					
Voltage Output Swing	$R_L = 1k\Omega, A_{OL} > 120dB$	(V-)+3		(V+)-3	V
Over Temperature	$R_L = 1k\Omega, A_{OL} > 114dB$	(V-)+3		(V+)-3	V
Output Current	$ V_S - V_{OUT} < 3V$		30		mA
Short-Circuit Current			± 65		mA

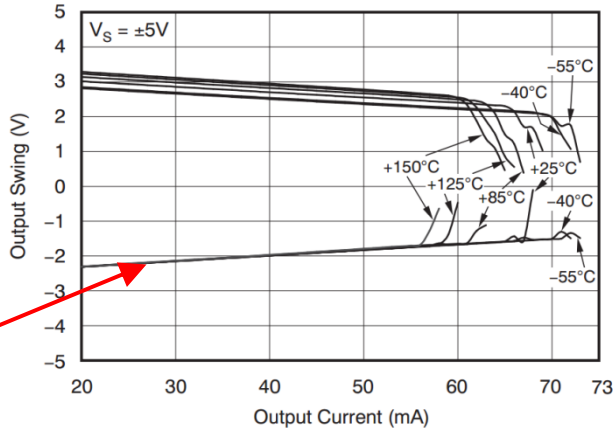

Output Saturated

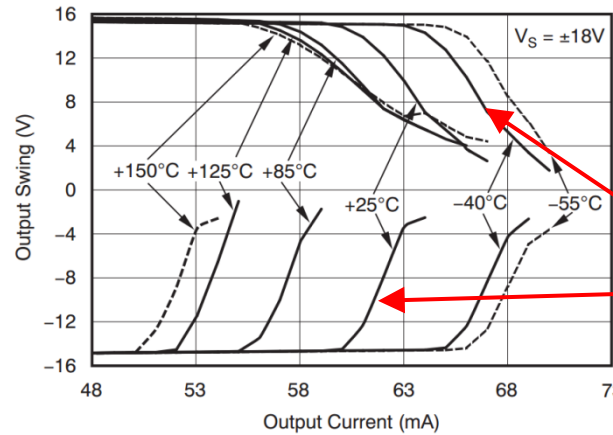

Short Circuit Protection

OPA827 – Classic Bipolar Output Stage

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNIT
OUTPUT					
Voltage Output Swing	$R_L = 1k\Omega, A_{OL} > 120dB$	$(V_-)+3$		$(V_+)-3$	V


Output Swing (Specs Table)

$$V_{OUT} \text{ swing} = 5V - 3V = \pm 2V$$


$$I_{OUT} = 2V / 1k\Omega = 2mA$$

Output Swing (Claw Curve)

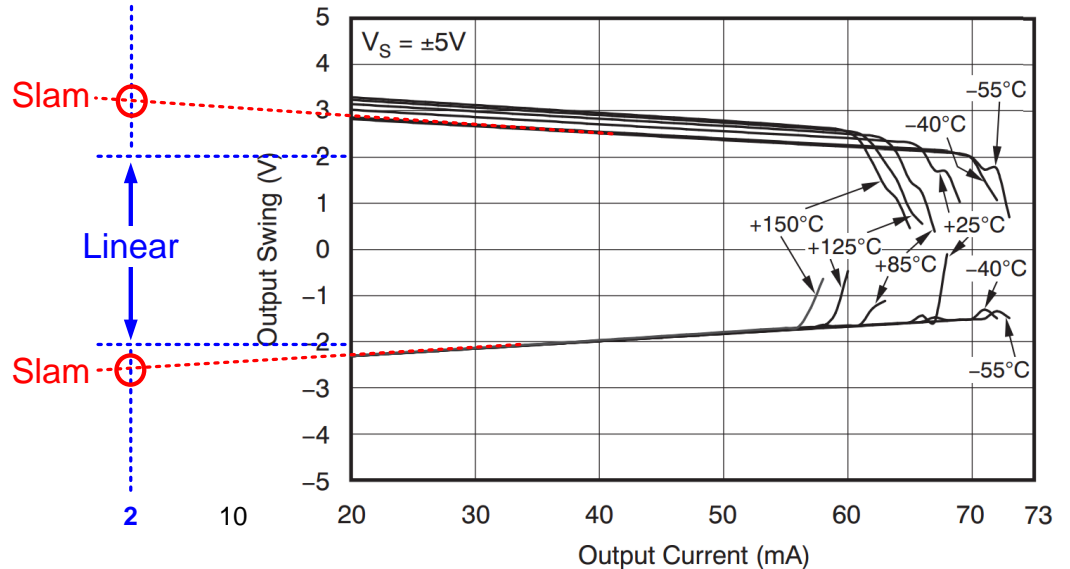
$$V_{OUT} \text{ swing} \approx \pm 3V \text{ (Slam @ 2mA)}$$



Claw Curve – Bipolar vs. CMOS

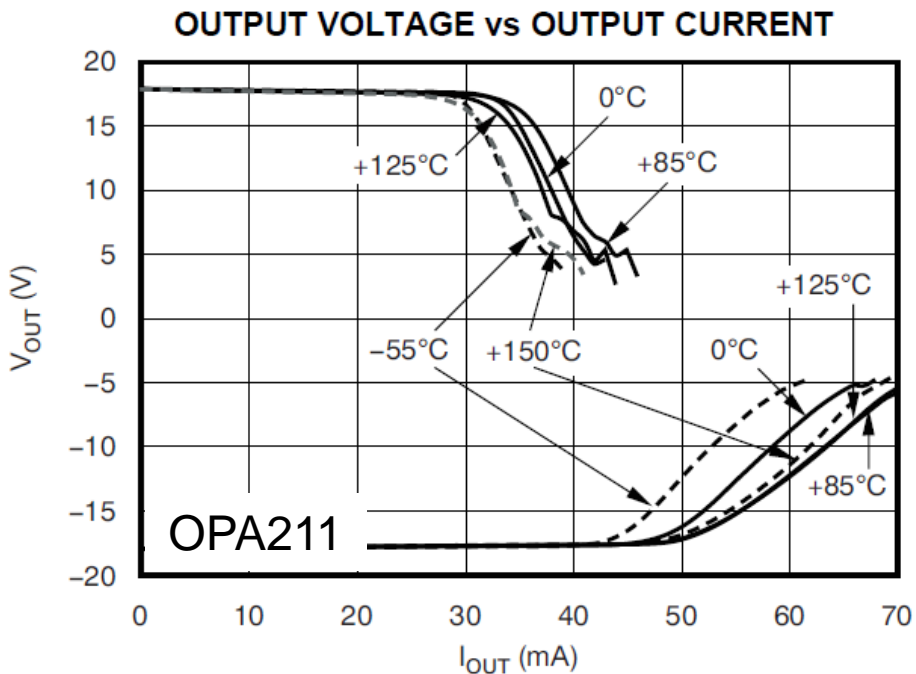


Bipolar

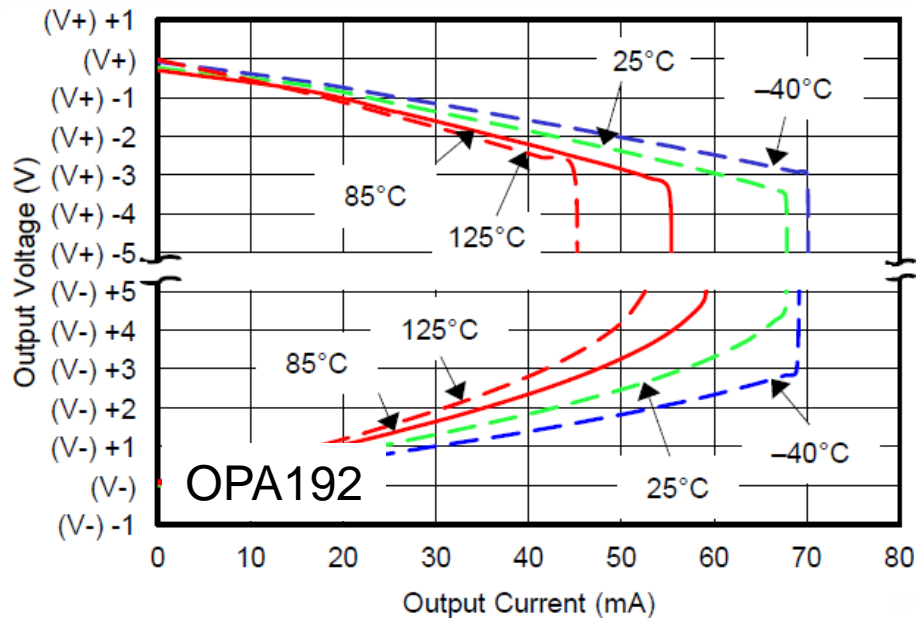


CMOS

Specs Table – Linear or Slam Voltage?


PARAMETER	CONDITIONS	MIN	TYP	MAX	UNIT
OUTPUT					
Voltage output swing from rail	No load		6	15	mV
	$R_L = 10\text{ k}\Omega$		220	250	mV
	$T_A = -40^\circ\text{C to } +125^\circ\text{C}$		310	350	mV
OPEN-LOOP GAIN					
A_{OL} Open-loop voltage gain	$(V^-) + 0.5\text{ V} < V_O < (V^+) - 0.5\text{ V},$ $R_L = 5\text{ k}\Omega$	110	120		dB
	$(V^-) + 0.5\text{ V} < V_O < (V^+) - 0.5\text{ V}$	120	130		dB

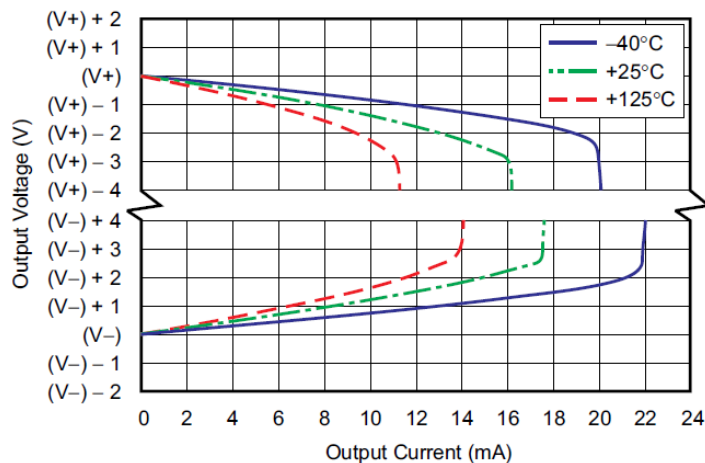

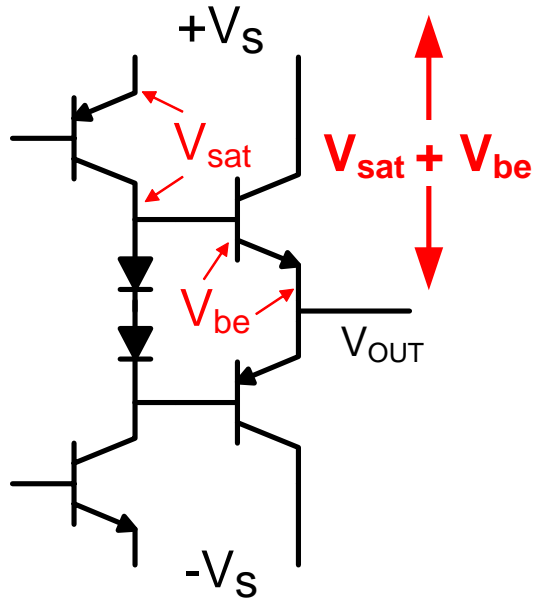Classic Bipolar vs. Rail-to-Rail Output Stage





Classic Bipolar

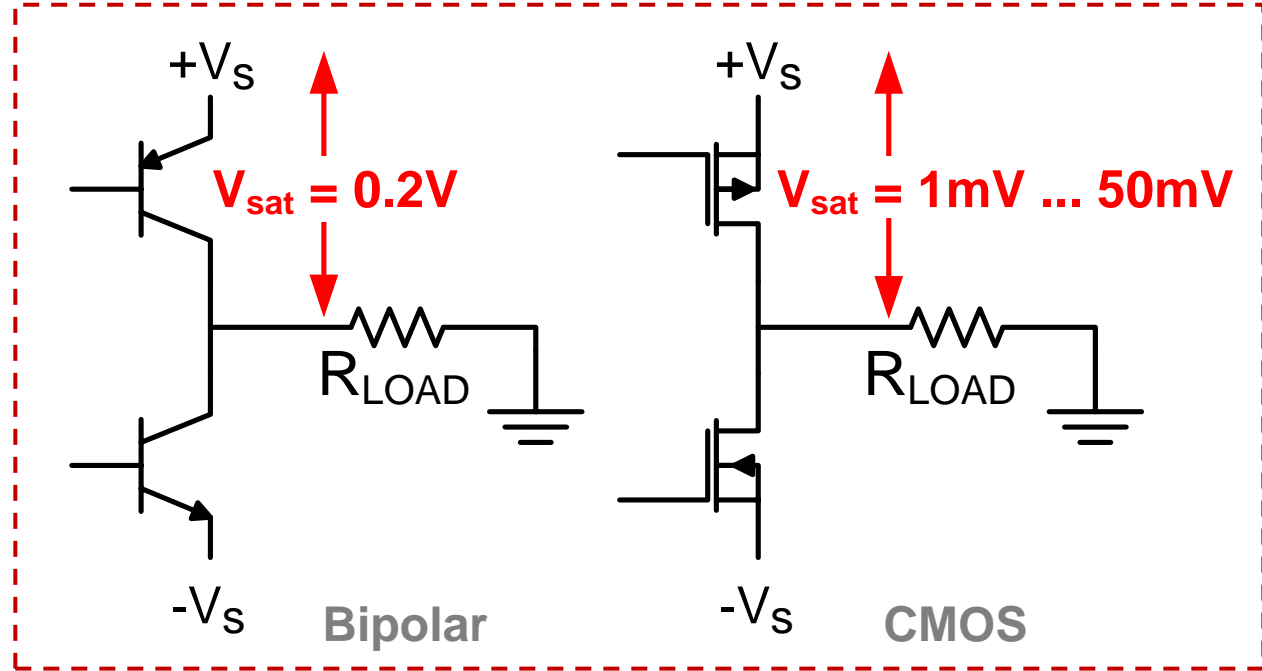



Rail-to-Rail

CMOS – Why No True Rail-to-Rail Output?

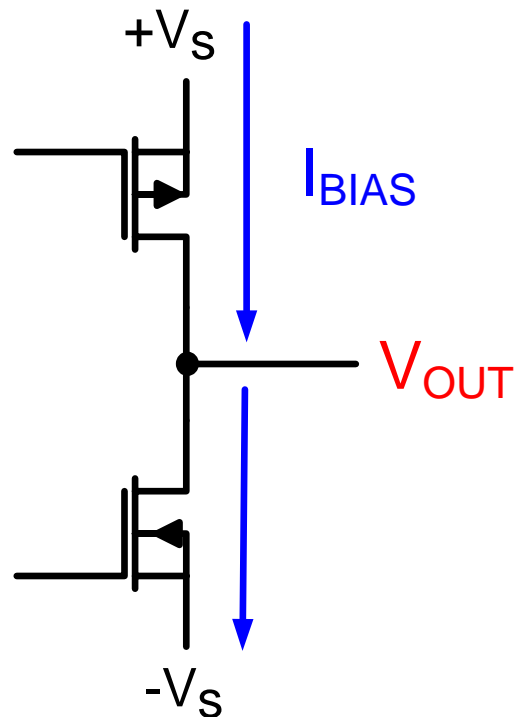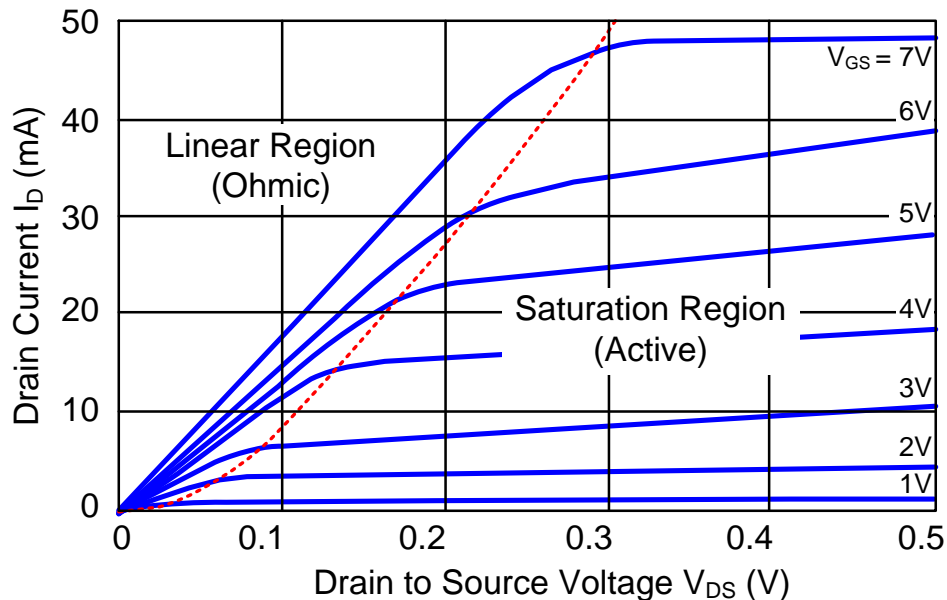

- Some minimum drain to source voltage is required!
- Increasing $I_D \rightarrow$ Increasing V_{GS}

Rail-to-Rail Output Stage vs. I_{OUT}

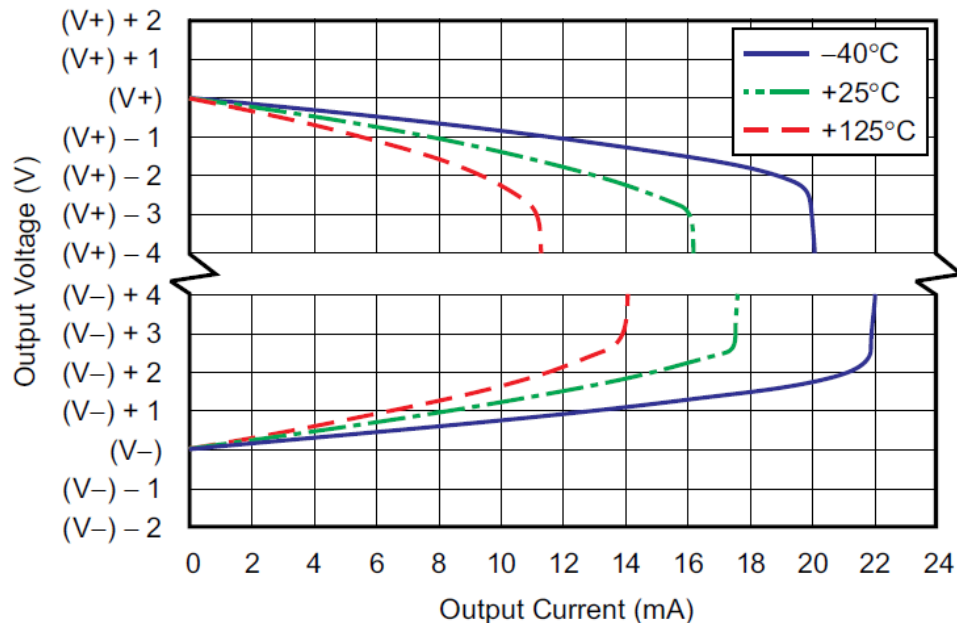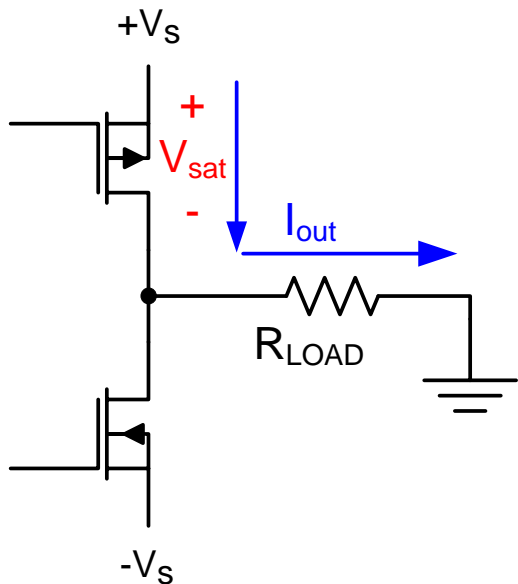


$$I_{out} = 0\text{mA}, V_{sat} \approx 0\text{V}$$


$$I_{out} = 8\text{mA}, V_{sat} \approx 1\text{V} (T = 25^\circ\text{C}) \rightarrow R_{out} = 125\Omega$$

$$I_{out} = 13\text{mA}, V_{sat} \approx 2\text{V} (T = 25^\circ\text{C}) \rightarrow R_{out} = 154\Omega$$


Rail-to-Rail Output Stage

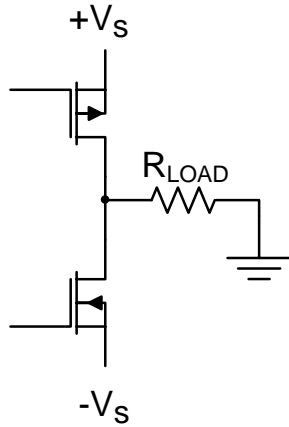

CMOS


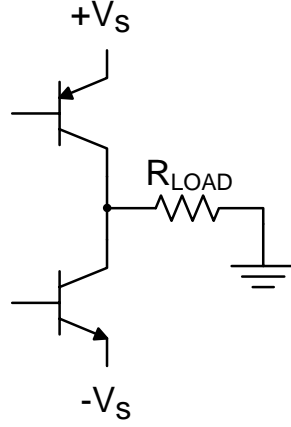


Bipolar

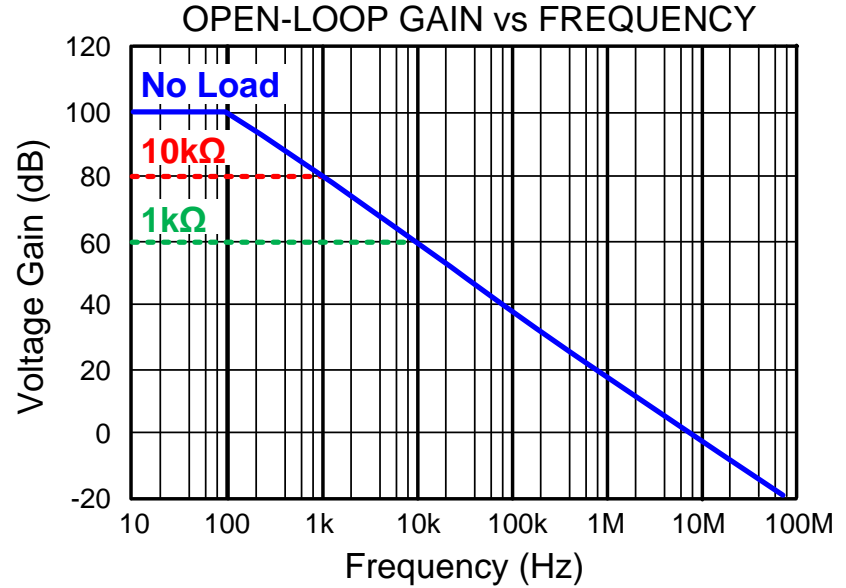

- R_{LOAD} affects A_{OL} and output swing
- $R_{out} = R_{LOAD} \parallel R_o$, where R_o = output resistance
- Gain in the last stage is set by R_{out} / g_m
- R_{out} decreases with loading

Output Short Circuit Current Limit

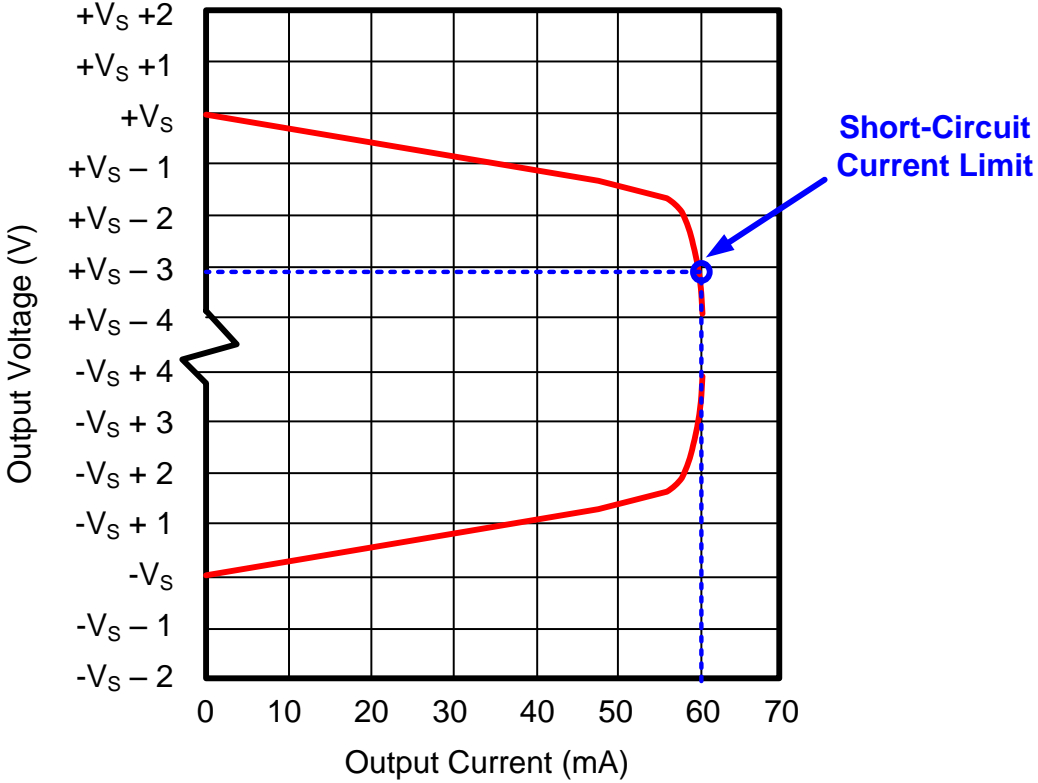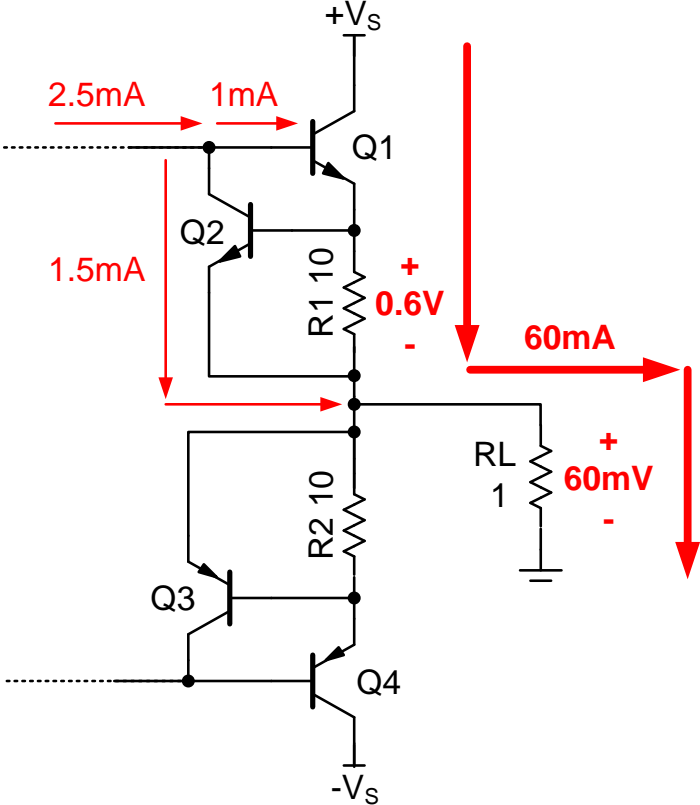


Short Circuit Limit – Specs Table vs. Curve

ELECTRICAL CHARACTERISTICS:

High-Voltage Operation, $V_S = \pm 4\text{ V to } \pm 18\text{ V}$ ($V_S = +8\text{ V to } +36\text{ V}$) (continued)

At $T_A = +25^\circ\text{C}$, $R_L = 10\text{ k}\Omega$ connected to $V_S / 2^{(1)}$, and $V_{CM} = V_{OUT} = V_S / 2^{(1)}$, unless otherwise noted.

PARAMETER	CONDITIONS	MIN	TYP	MAX	UNIT
OUTPUT					
Voltage output swing from rail	No load		6	15	mV
	$R_L = 10\text{ k}\Omega$		220	250	mV
	$T_A = -40^\circ\text{C to } +125^\circ\text{C}$		310	350	mV
I_{SC} Short-circuit current	Sinking		-18		mA
	Sourcing		+16		mA

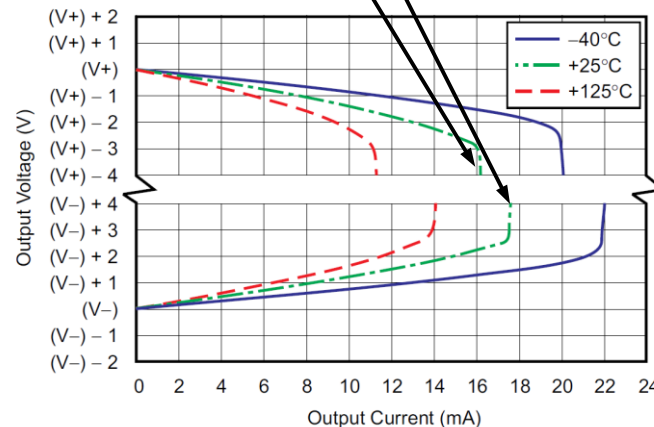

**Thanks for your time!
Please try the quiz.**


Input & Output Limitations – 3

Multiple Choice Quiz

TI Precision Labs – Op Amps


Quiz: Input & Output Limitations – 3

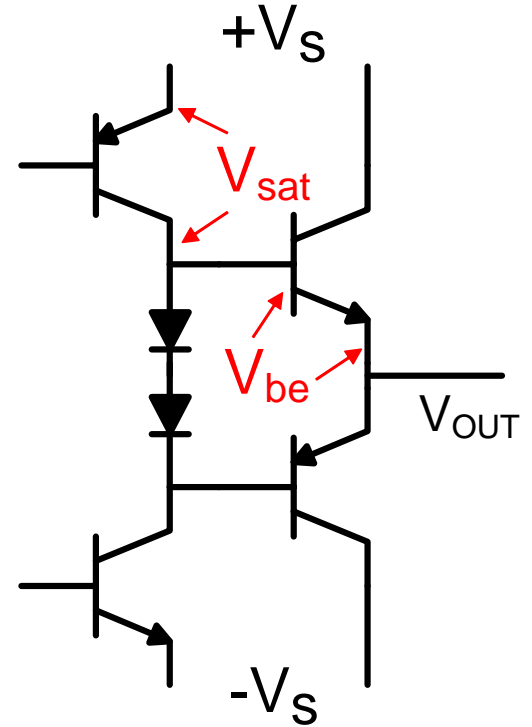1. The figure below shows a classic bipolar output stage. Which of the following is true?
 - a. This is a rail-to-rail output.
 - b. Connecting a load to the output will cause A_{OL} to shift.
 - c. The output swing limit will be about 1V from the supply rail.
 - d. The RF immunity for the op amp will be limited.





Quiz: Input & Output Limitations – 3

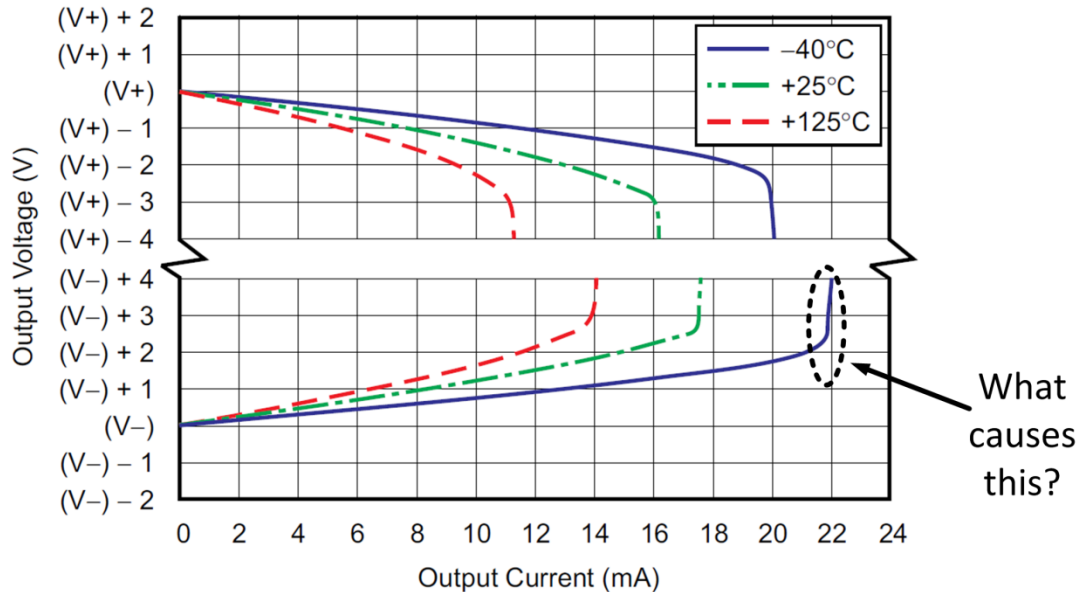2. In the claw curve below, the region at the end of the curve is circled. What causes this bend in the curve?
- The amplifier short circuit limit is turning on.
 - The resistance of the output transistors is causing voltage to decrease.
 - The amplifier is going into thermal overload.
 - The saturation and cutoff of the input stage is causing common mode limitations.



Quiz: Input & Output Limitations – 3

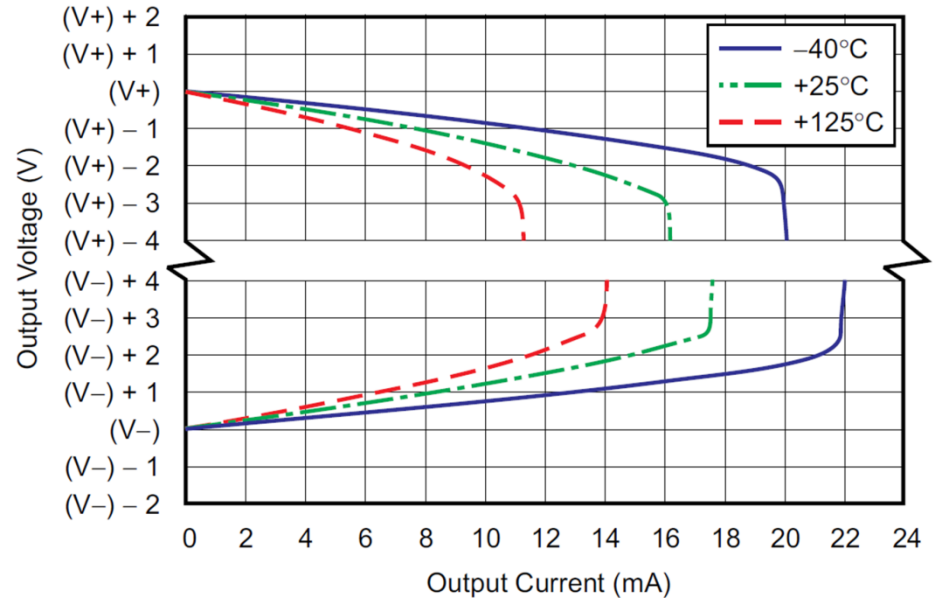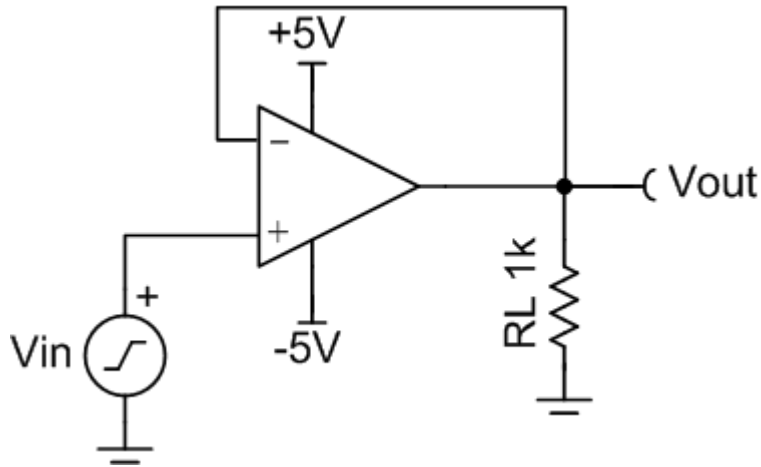3. For the circuit below, estimate the output swing (slam limit).
- a. $-4.9 < V_{out} < +4.9V$
 - b. $-4.2 < V_{out} < +4.0V$
 - c. $-3.5 < V_{out} < +3.5V$
 - d. $-3.0 < V_{out} < +3.0V$



Quiz: Input & Output Limitations – 3

4. (T/F) The claw curve represents the linear output swing range for an op amp vs. output current.
 - a. True
 - b. False


5. The DC A_{OL} for some amplifiers will be affected by loading. Which amplifier types are most susceptible to the effect?
 - a. Rail-to-rail
 - b. Classic bipolar

6. What output swing limitation would you expect with a bipolar rail-to-rail amplifier?
 - a. A few millivolts from the rail
 - b. 50mV from the rail
 - c. 300mV from the rail
 - d. 1V from the rail

7. (T/F) If the output is shorted to the negative supply, the short circuit limit will limit the output current and protect the device from damage.
 - a. True
 - b. False

Quiz: Input & Output Limitations – 3

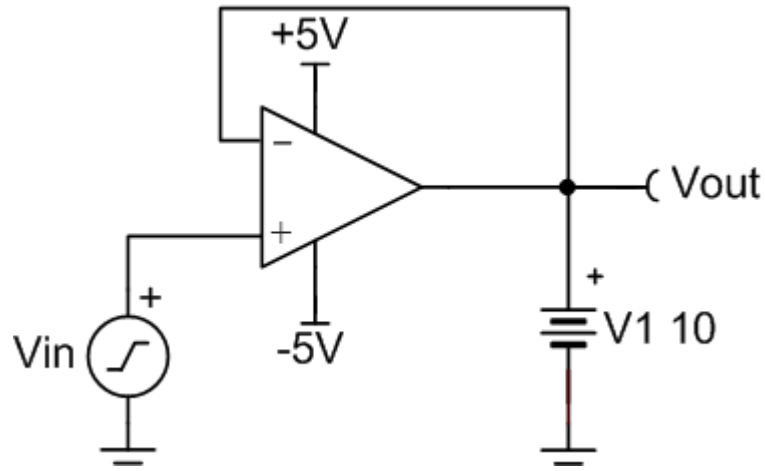8. The circuit's output is accidentally shorted to a 10V supply as shown below. Will the short circuit protection, prevent damage?
- a. Yes
 - b. No



Quiz: Input & Output Limitations – 3

9. Based on the data sheet excerpt below, at 125°C, the worst case linear output swing is _____.
- 30mV from the rail.
 - 50mV from the rail.
 - 70mV from the rail.
 - 100mV from the rail.

At $T_A = +25^\circ\text{C}$, $R_L = 10\text{ k}\Omega$ connected to $V_S / 2$, $V_{CM} = V_S / 2$, and $V_{OUT} = V_S / 2$, unless otherwise noted.

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
OPEN-LOOP GAIN					
A_{OL} Open-loop voltage gain	$(V_-) + 100\text{ mV} < V_O < (V_+) - 100\text{ mV}$, $R_L = 10\text{ k}\Omega$, $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$	106	130		dB
OUTPUT					
Voltage output swing from rail	$R_L = 10\text{ k}\Omega$		30	50	mV
	$R_L = 10\text{ k}\Omega$, $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$			70	mV
I_{SC} Short-circuit current			± 5		mA

Quiz: Input & Output Limitations – 3

10. For the data sheet excerpt below, the typical short circuit current is set to turn on at +30mA (sourcing) and -45mA (sinking). These limits are for room temperature only. How could you estimate the variation of short circuit current over temperature?
- $\pm 20\%$
 - $\pm 50\%$
 - Use the claw curves
11. For the data sheet excerpt below, the typical short circuit current is set to turn on at +30mA (sourcing) and -45mA (sinking). These limits indicate typical performance only. How could you estimate the worst case?
- $\pm 20\%$
 - $\pm 50\%$
 - Use the claw curves


PARAMETER	CONDITIONS	Standard Grade OPA211AI, OPA2211AI			High Grade OPA211I ⁽¹⁾			UNIT
		MIN	TYP	MAX	MIN	TYP	MAX	
OUTPUT								
Voltage Output	V_{OUT}	$R_L = 10k\Omega, A_{OL} \geq 114dB$	(V-) + 0.2		(V+) - 0.2	(V-) + 0.2	(V+) - 0.2	V
		$R_L = 600\Omega, A_{OL} \geq 110dB$	(V-) + 0.6		(V+) - 0.6	(V-) + 0.6	(V+) - 0.6	V
		$I_O < 15mA, A_{OL} \geq 110dB$	(V-) + 0.6		(V+) - 0.6	(V-) + 0.6	(V+) - 0.6	V
Short-Circuit Current	I_{SC}			+30/-45			+30/-45	mA

Input & Output Limitations – 3

Multiple Choice Quiz: Solutions
TI Precision Labs – Op Amps


Solutions: Input & Output Limitations – 3

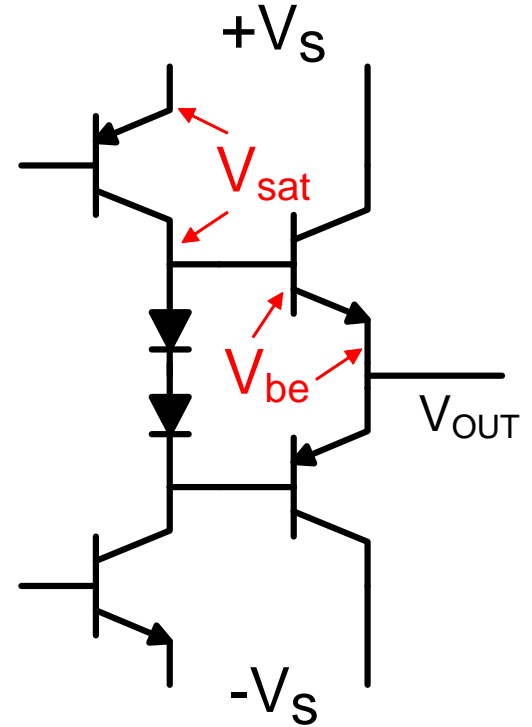1. The figure below shows a classic bipolar output stage. Which of the following is true?
 - a. This is a rail-to-rail output.
 - b. Connecting a load to the output will cause A_{OL} to shift.
 - c. The output swing limit will be about 1V from the supply rail.**
 - d. The RF immunity for the op amp will be limited.





Solutions: Input & Output Limitations – 3

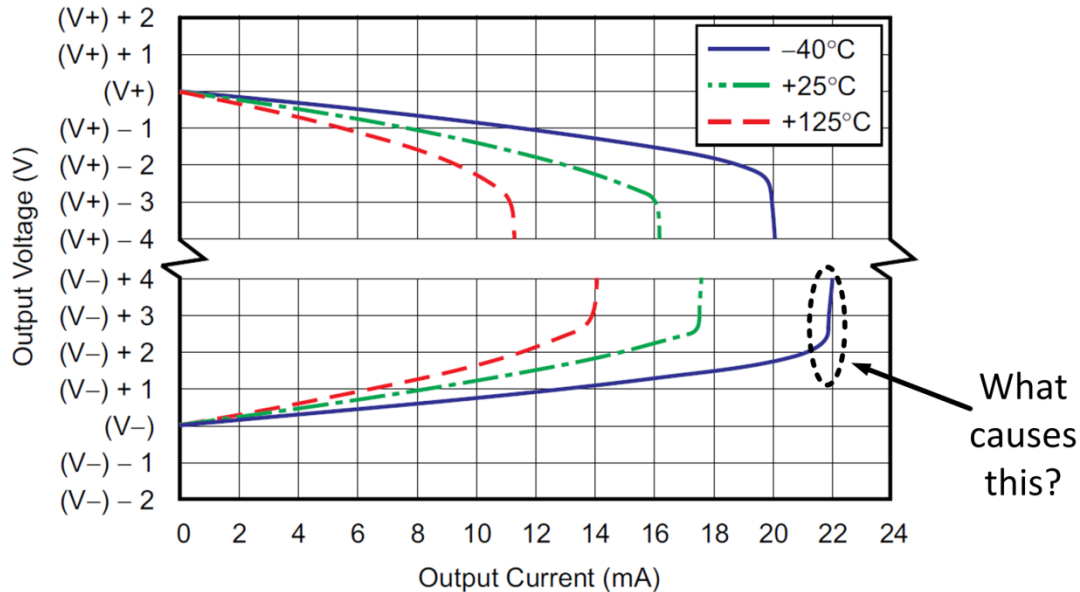2. In the claw curve below, the region at the end of the curve is circled. What causes this bend in the curve?
- The amplifier short circuit limit is turning on.
 - The resistance of the output transistors is causing voltage to decrease.
 - The amplifier is going into thermal overload.
 - The saturation and cutoff of the input stage is causing common mode limitations.



Solutions: Input & Output Limitations – 3

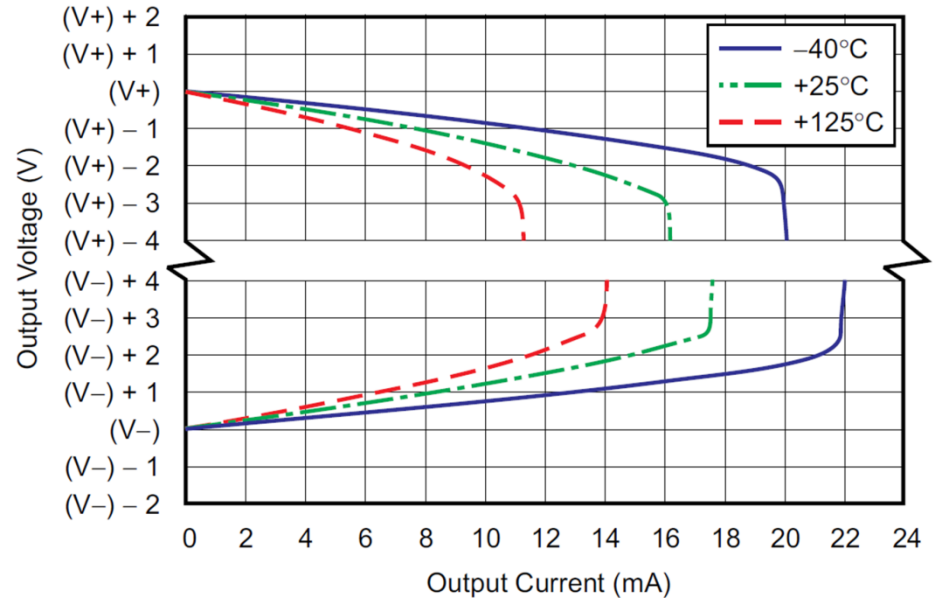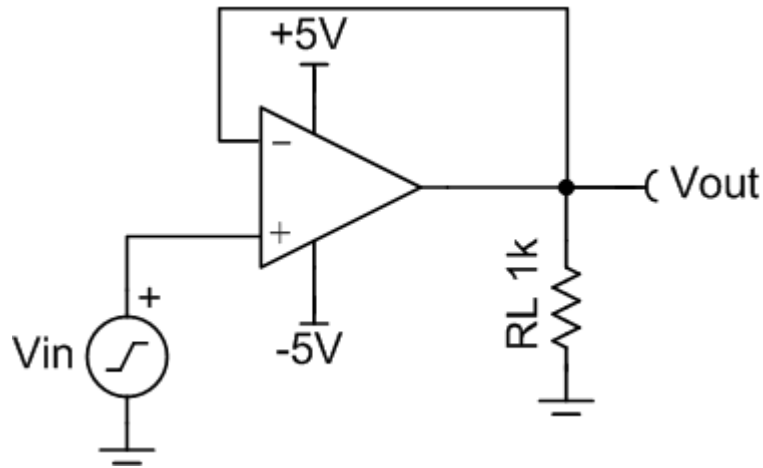3. For the circuit below, estimate the output swing (slam limit).
- a. $-4.9 < V_{out} < +4.9V$
 - b. $-4.2 < V_{out} < +4.0V$
 - c. $-3.5 < V_{out} < +3.5V$
 - d. $-3.0 < V_{out} < +3.0V$



Solutions: Input & Output Limitations – 3

4. (T/F) The claw curve represents the linear output swing range for an op amp vs. output current.
 - a. True
 - b. **False**


5. The DC A_{OL} for some amplifiers will be affected by loading. Which amplifier types are most susceptible to the effect?
 - a. **Rail-to-rail**
 - b. Classic bipolar

6. What output swing limitation would you expect with a bipolar rail-to-rail amplifier?
 - a. A few millivolts from the rail
 - b. 50mV from the rail
 - c. **300mV from the rail**
 - d. 1V from the rail

7. (T/F) If the output is shorted to the negative supply, the short circuit limit will limit the output current and protect the device from damage.
 - a. **True**
 - b. False

Solutions: Input & Output Limitations – 3

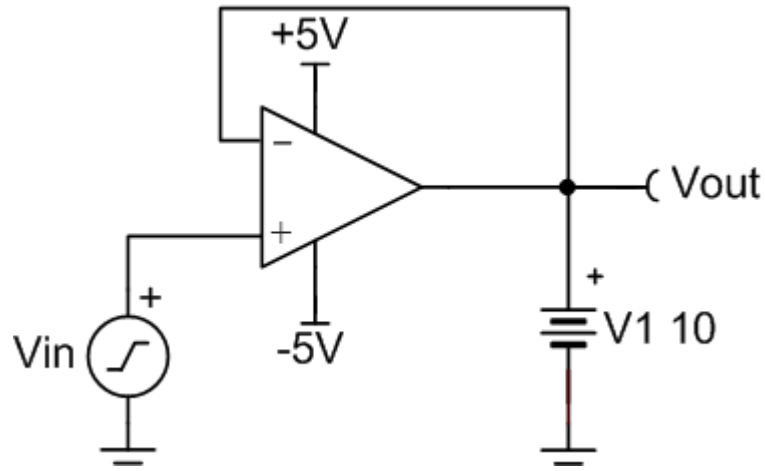8. The circuit's output is accidentally shorted to a 10V supply as shown below. Will the short circuit protection prevent damage?
- a. Yes
 - b. **No**



Solutions: Input & Output Limitations – 3

9. Based on the data sheet excerpt below, at 125°C, the worst case linear output swing is _____.
- 30mV from the rail.
 - 50mV from the rail.
 - 70mV from the rail.
 - 100mV from the rail.

At $T_A = +25^\circ\text{C}$, $R_L = 10\text{ k}\Omega$ connected to $V_S / 2$, $V_{CM} = V_S / 2$, and $V_{OUT} = V_S / 2$, unless otherwise noted.

PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
OPEN-LOOP GAIN					
A_{OL} Open-loop voltage gain	$(V_-) + 100\text{ mV} < V_O < (V_+) - 100\text{ mV}$, $R_L = 10\text{ k}\Omega$, $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$	106	130		dB
OUTPUT					
Voltage output swing from rail	$R_L = 10\text{ k}\Omega$		30	50	mV
	$R_L = 10\text{ k}\Omega$, $T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$			70	mV
I_{SC} Short-circuit current			± 5		mA

Solutions: Input & Output Limitations – 3

10. For the data sheet excerpt below, the typical short circuit current is set to turn on at +30mA (sourcing) and -45mA (sinking). These limits are for room temperature only. How could you estimate the variation of short circuit current over temperature?
- $\pm 20\%$
 - $\pm 50\%$
 - Use the claw curves
11. For the data sheet excerpt below, the typical short circuit current is set to turn on at +30mA (sourcing) and -45mA (sinking). These limits indicate typical performance only. How could you estimate the worst case?
- $\pm 20\%$
 - $\pm 50\%$
 - Use the claw curves

PARAMETER	CONDITIONS	Standard Grade OPA211AI, OPA2211AI			High Grade OPA211I ⁽¹⁾			UNIT
		MIN	TYP	MAX	MIN	TYP	MAX	
OUTPUT								
Voltage Output	V_{OUT} $R_L = 10k\Omega, A_{OL} \geq 114dB$ $R_L = 600\Omega, A_{OL} \geq 110dB$	$(V-) + 0.2$ $(V-) + 0.6$		$(V+) - 0.2$ $(V+) - 0.6$	$(V-) + 0.2$ $(V-) + 0.6$		$(V+) - 0.2$ $(V+) - 0.6$	V
Short-Circuit Current	I_{SC} $I_O < 15mA, A_{OL} \geq 110dB$	$(V-) + 0.6$	+30/-45	$(V+) - 0.6$	$(V-) + 0.6$	+30/-45	$(V+) - 0.6$	mA