

AN-2182 LM3466 Demonstration Board Reference Design

1 Introduction

The LM3466 integrates a linear LED driver for lighting systems that consist of multiple LED strings powered by a constant current power supply. The LM3466 equalizes the current provided by the supply in a pre-set ratio for each active LED string, where an active string is a fully turned on LED string, regardless of the number of strings connected to the supply or the forward voltage of each LED string. If any LED string opens during operation, the LM3466 automatically equalizes the supply current through all of the remaining active LED strings. As a result, the overall brightness of the lighting system is maintained even if some LED strings open during operation. The LM3466 consists of only linear circuitry so that the EMI of the application circuit is not deteriorated.

This application report details the design of an LM3466 evaluation board that drives five LED strings, each of which consists of 14 LEDs. The input current I_s (of the constant current power supply) is 1.75A such that the LED current is 0.35A per string. The evaluation board schematic, PCB layout, Bill of Materials, and circuit design procedures are shown. Typical performance and operating waveforms are also provided for reference.

2 Demonstration Board Schematic and PCB

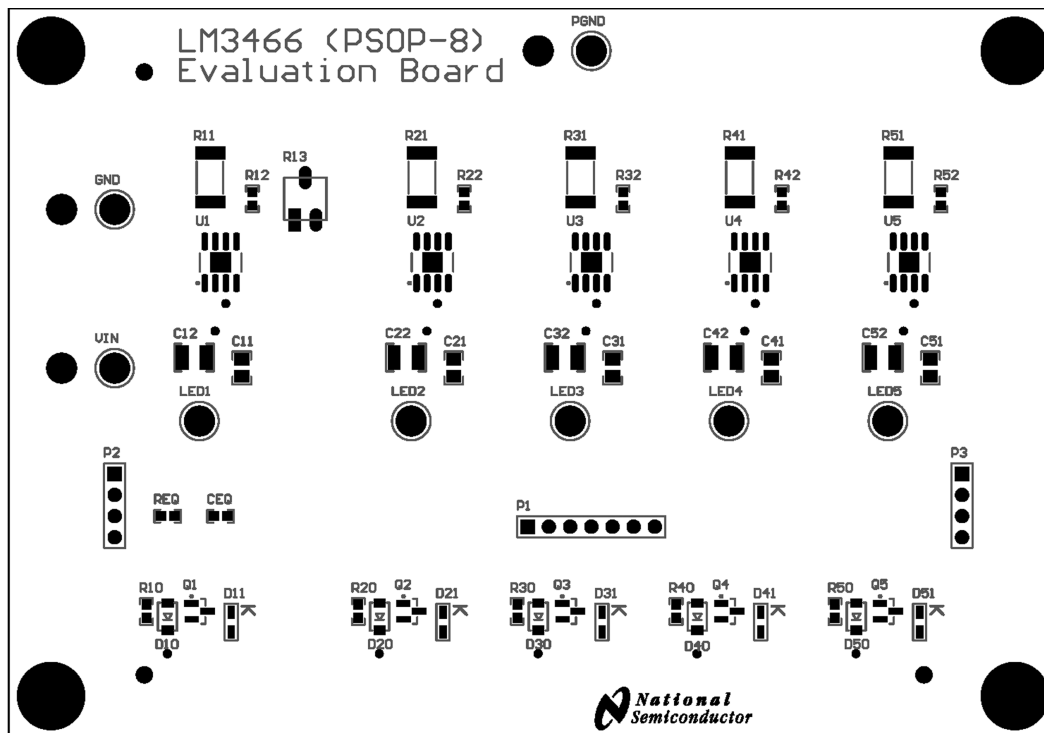


Figure 1. LM3466 Evaluation Board PCB Top Overlay

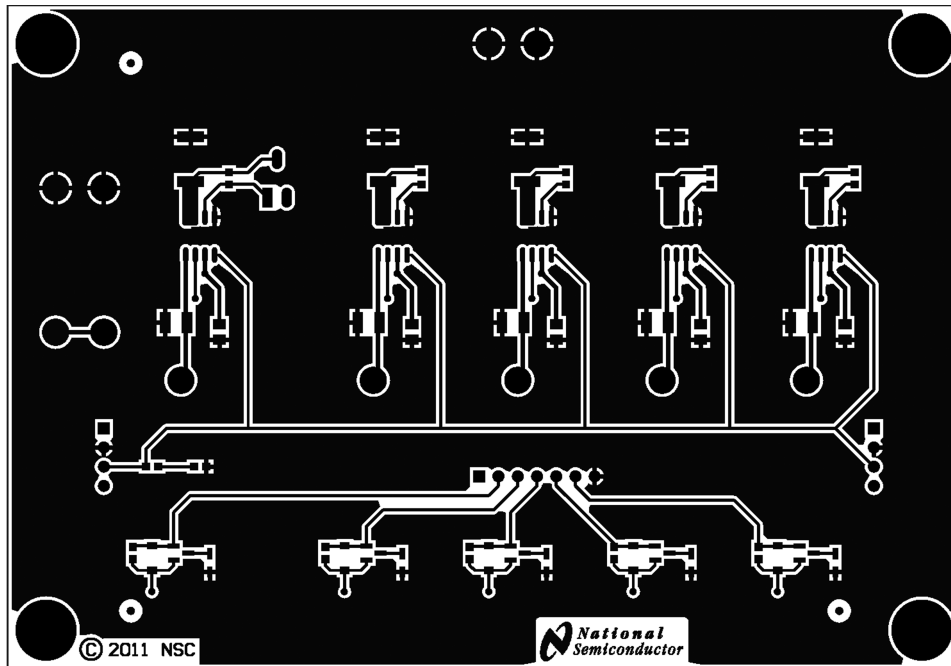


Figure 2. LM3466 Evaluation Board Top View

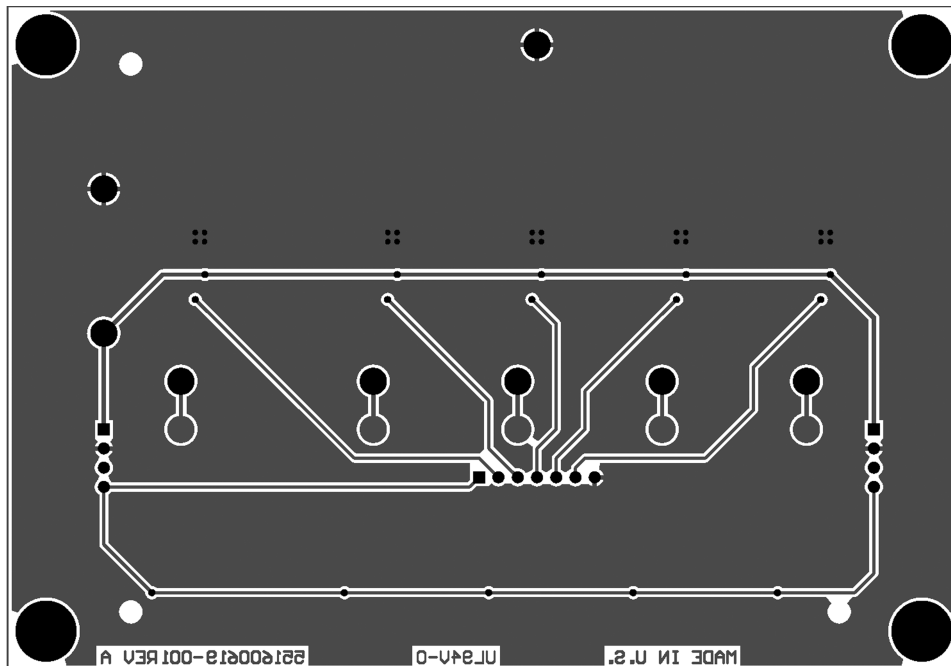


Figure 3. LM3466 Evaluation Board Bottom View

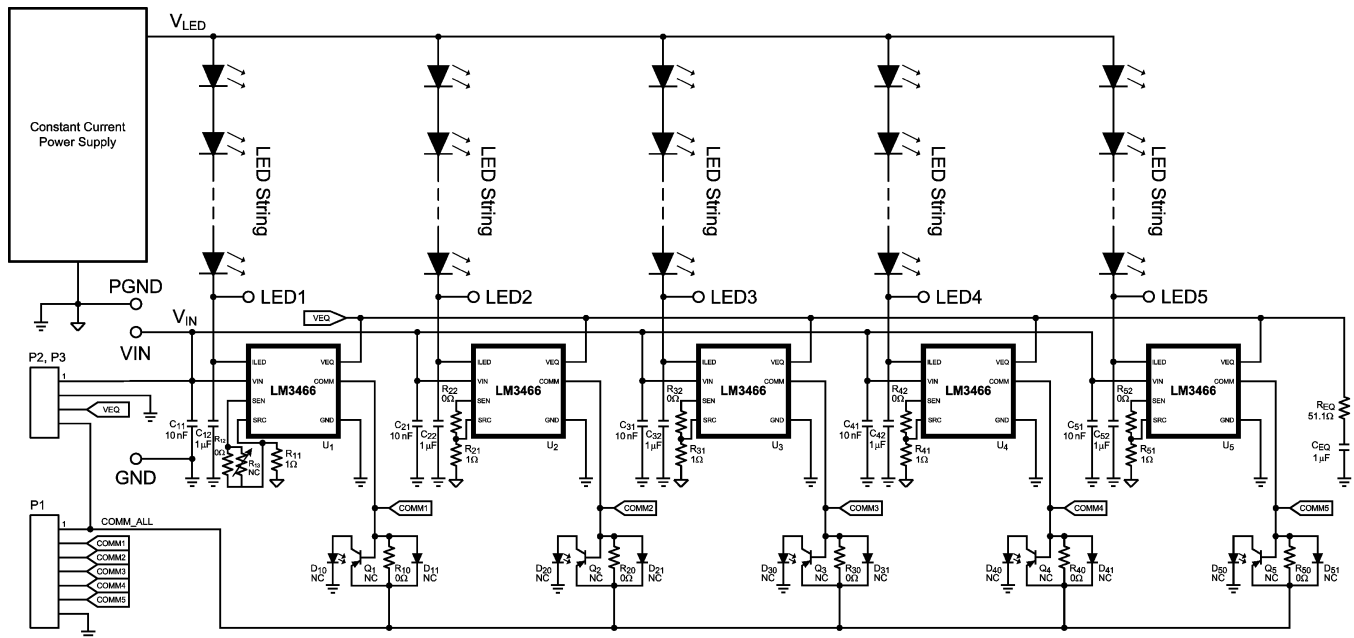


Figure 4. LM3466 Evaluation Board Schematic

Table 1. Evaluation Board Quick Setup Procedures

Step	Description	Notes
1	Connect a constant current power supply to VLED and PGND. The VIN terminal can be connected to VLED, or another voltage source ranged from 6 V to 70 V.	The supply current I_S is set to 1.75A, with a maximum output voltage of 48 V.
2	Connect five LED strings from VLED to LED1 to LED5 terminals.	Each LED string consists of 14 LEDs with a forward string voltage of lower than 48 V at 0.35A.
3	Turn on the power supply. The five LED strings are turned on and the current is 0.35A each.	The voltage on R11-R51 is 0.35 V.

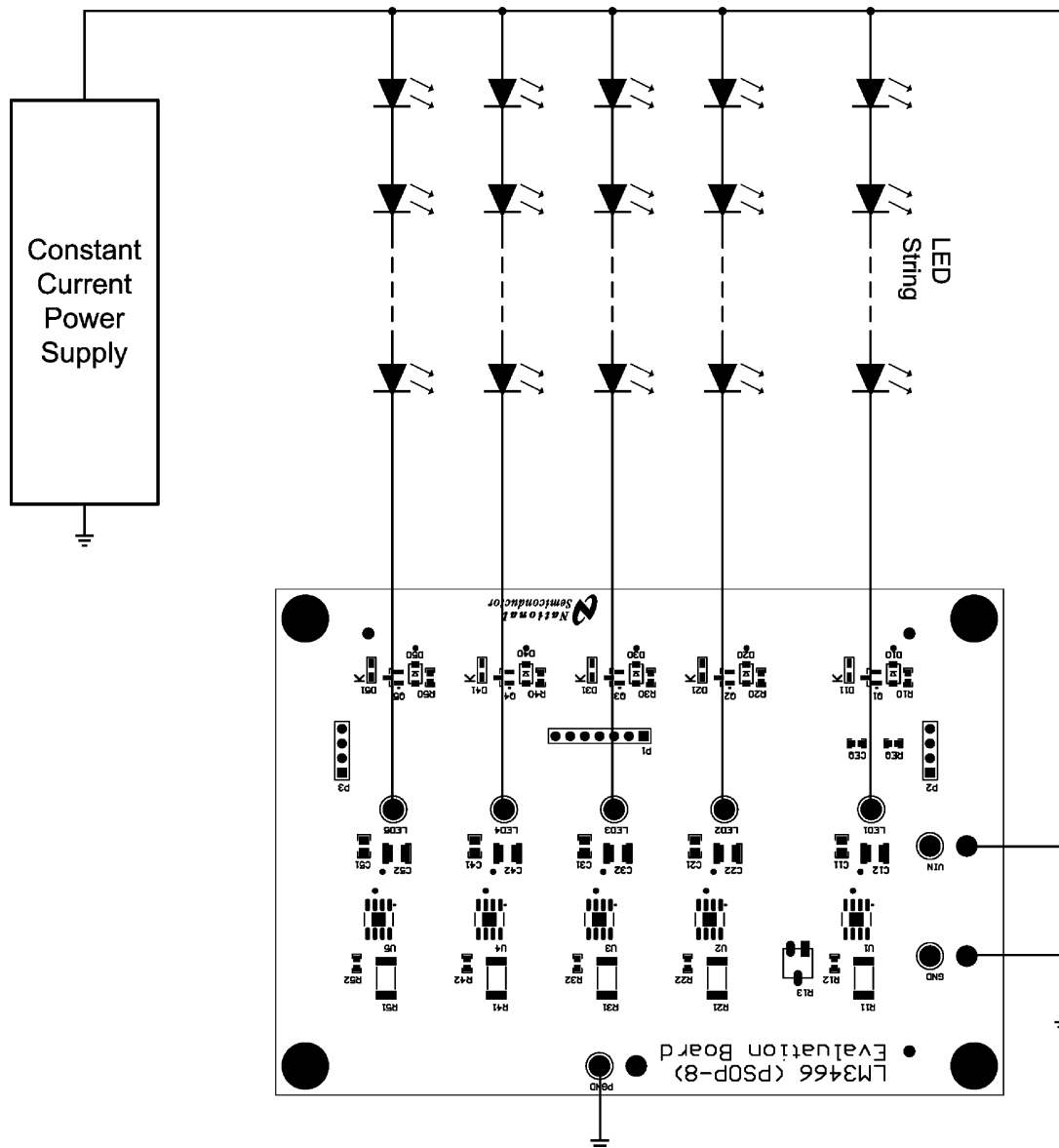


Figure 5. LM3466 Evaluation Board Connection Diagram

3 Design Procedure

The LM3466 evaluation board has 5 channels driving five LED strings powered by a constant current power supply ($I_S = 1.75A$). It is expected that the current of every LED string is 0.35A. From the schematic (see Figure 4), each channel consists of an LM3466 (U_i), a sense resistor (R_{i1}), and two capacitors (C_{i1} and C_{i2}), where $i = 1$ to 5. An RC circuit connecting the VEQ pin to ground is required for the whole circuit. The above components are determined as follows.

Step 1: Determine the sense resistor

The current provided by the constant current power supply is equalized through each channel in a pre-set ratio determined by the sense resistor R_{i1} . This LM3466 evaluation board is designed so that the current of each channel is the same, the sense resistor of each channel is designed to be the same. It is recommended that the nominal voltage of the SEN pin V_{SEN} should be around 0.3 V. Therefore, R_{i1} is selected to be 1 Ω . As a result, V_{SEN} should be 0.35 V if the LED current is 0.35A.

Step 2: Determine the capacitors

C_{i1}: A high quality ceramic capacitor for decoupling should be connected from the VIN pin to ground. In this LM3466 evaluation board, a 100 V, 0.01 μ F ceramic capacitor is used.

C_{i2}: If the cable connecting the LED string and the evaluation board is long, the parasitic inductance of the cable may generate noise. If this happens, a high quality ceramic capacitor should be connected between the ILED pin and ground. In this LM3466 evaluation board, a 100V, 1 μ F ceramic capacitor is used.

Step 3: Determine other components

R_{EQ} and **C_{EQ}**: The VEQ pins of all LM3466 are shorted together and then connected to ground through R_{EQ} and C_{EQ} for normal operation. Only one R_{EQ} and one C_{EQ} are required for one lighting system. It is recommended that R_{EQ} be 51.1 Ω and C_{EQ} be 1 μ F.

Step 4: Optional circuit for fault reporting

For simplicity, the COMM pins of all LM3466 can be shorted directly to a common bus COMM_ALL for normal operation (R_{i0} = 0 Ω). If fault reporting upon LED string open of a corresponding channel is required, an optional circuit can be used to connect the COMM pin of each LM3466 to COMM_ALL. Since the COMM pin pulls low during LED string open, the small signal LED in the optional circuit shown in Figure 6 will light during a fault.

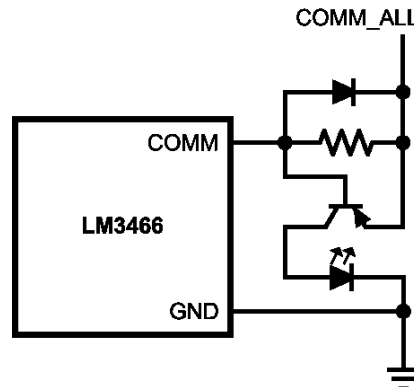


Figure 6. Optional COMM Circuit

4 PC Board Layout

To minimize the effect of noise, the ground connections of the LM3466 and the sense resistor R_{i1} should be closed. Good heat dissipation helps optimize the performance of the LM3466. The ground plane should be used to connect the exposed pad of the LM3466, which is internally connected to the LM3466 die substrate. The area of the ground plane should be extended as much as possible on the same copper layer above and below the LM3466. Using numerous vias beneath the exposed pad to dissipate heat of the LM3466 to another copper layer is also a good practice.

5 Bill of Materials

Item	Part Number	Mfg name	Part Description	Qty	Ref Designator(s)	Size
1	GRM21BR72A103KA01L	MuRata	CAP, CERM, 0.01 μ F, 100V, \pm 10%, X7R, 0805	5	C11, C21, C31, C41, C51	0805
2	GRM32ER72A105KA01L	MuRata	CAP, CERM, 1 μ F, 100V, \pm 10%, X7R, 1210	5	C12, C22, C32, C42, C52	1210
3	GRM188R71A105KA61D	MuRata	CAP, CERM, 1 μ F, 10V, \pm 10%, X7R, 0603	1	CEQ	0603
4	1502-2	Keystone Electronics	Terminal, Turret, TH, Double	8	GND, LED1, LED2, LED3, LED4, LED5, PGND, VIN	
5	CRCW06030000Z0EA	Vishay-Dale	RES, 0 Ω , 5%, 0.1W, 0603	10	R10, R12, R20, R22, R30, R32, R40, R42, R50, R52	0603
6	CRCW25121R00FKEG	Vishay	RES, 1.00 Ω 1W 1% 2512	5	R11, R21, R31, R41, R51	2512
7	CRCW060351R1FKEA	Vishay-Dale	RES, 51.1 Ω , 1%, 0.1W, 0603	1	REQ	0603
8	LM3466/NOPB	Texas Instruments	Simple Linear LED driver for Multi-Channel LED Systems	5	U1, U2, U3, U4, U5	SO PowerPAD -8

6 Typical Performance and Waveforms

All curves and waveforms are taken at $I_S = 1.75A$ with the evaluation board and $T_A = 25^\circ C$, unless otherwise specified.

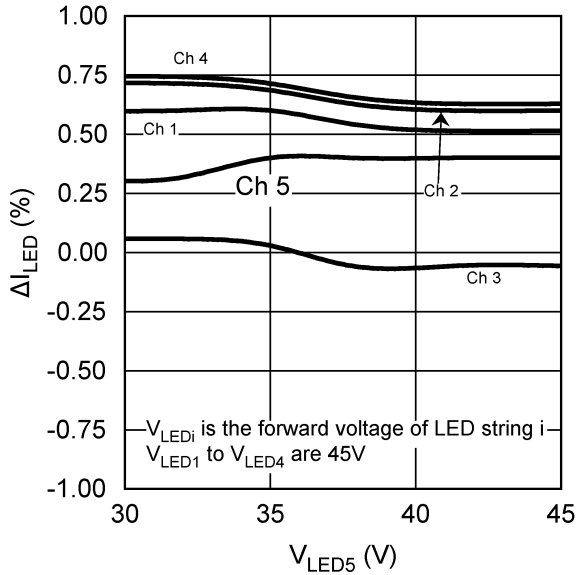


Figure 7. Current Regulation vs V_{LED}

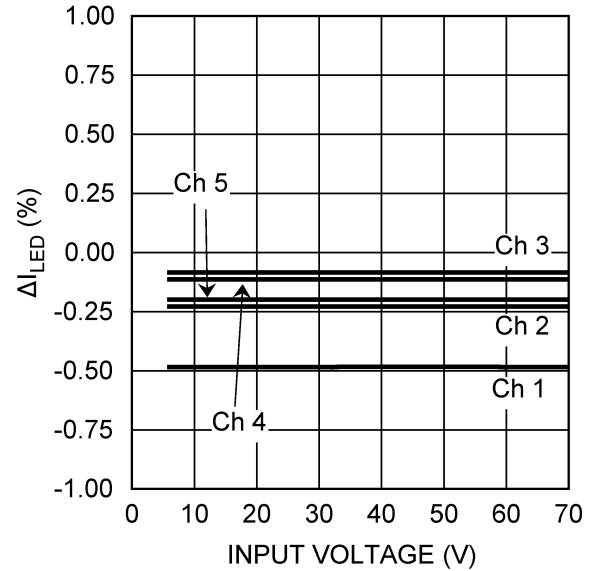


Figure 8. Current Regulation vs Input Voltage

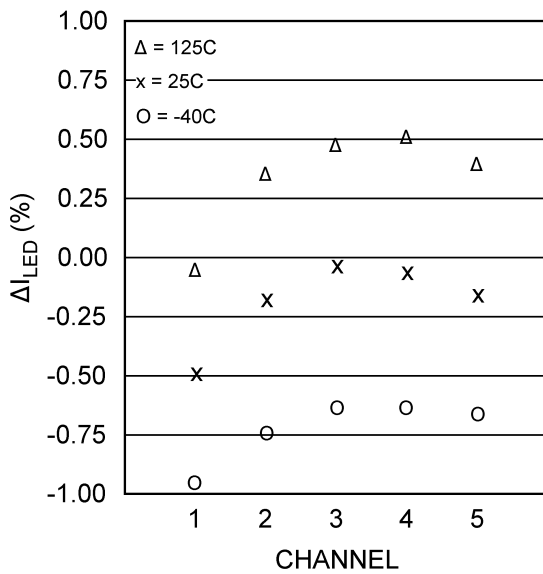


Figure 9. Current Regulation (Channel to Channel) vs Temperature



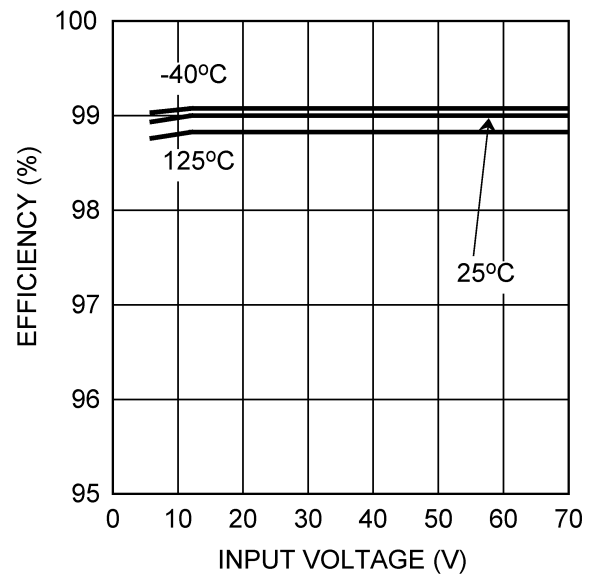


Figure 10. Efficiency vs Input Voltage

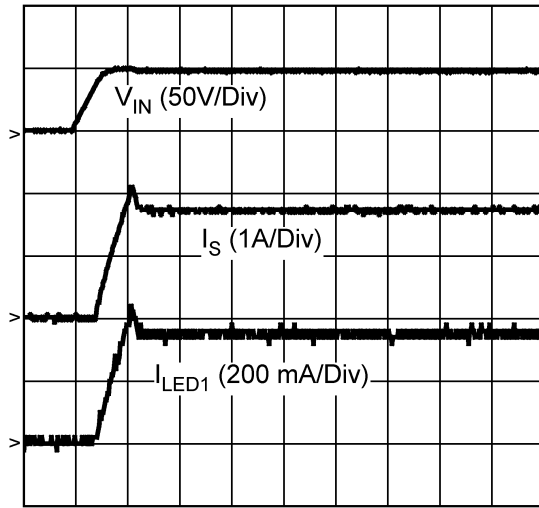

TIME (20 ms/DIV)
Figure 11. Power Up

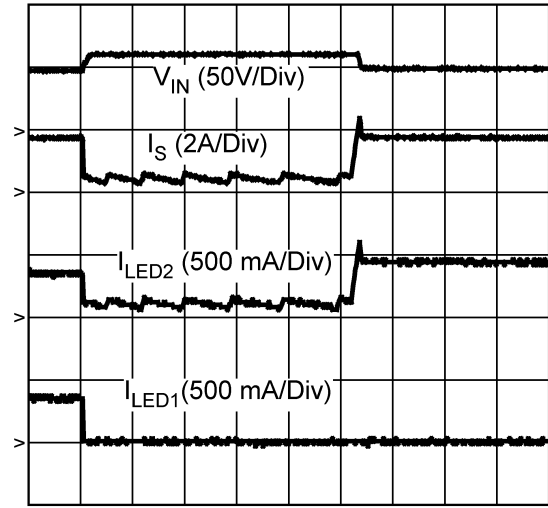

TIME (100 ms/DIV)
Figure 12. LED String Disconnect

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Applications Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Automotive and Transportation	www.ti.com/automotive
Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Video and Imaging	www.ti.com/video

TI E2E Community

e2e.ti.com