

## TI Designs

# 12V to 24V, 27A Brushed DC Motor Reference Design



### TI Designs


TI Designs provide the foundation that you need including methodology, testing and design files to quickly evaluate and customize the system. TI Designs help **you** accelerate your time to market.

### Design Resources

<a href="#">TIDA-00620</a>	Design Folder
<a href="#">DRV8701</a>	Product Folder
<a href="#">MSP430G2553</a>	Product Folder
<a href="#">CSD18540Q5B</a>	Product Folder
<a href="#">LMT86DCKT</a>	Product Folder
<a href="#">Understanding IDRIVE and TDRIVE</a>	Tools Folder
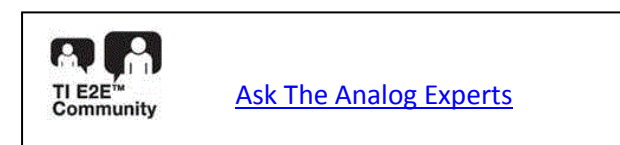
### Design Features


- 343 Watt RMS Power Stage With MSP430G2553 Control Scheme
- Tested to Operate with 18 Volt External Battery
- Delivers up to 27.47 A<sub>RMS</sub> Continuous Motor Current With No External Heat Sinking or Air Flow Aids
- Dual Layer, Small PCB Form Factor of 76.3 mm by 38.1 mm
- Utilizes TI's 60 V N-Channel NexFETs With an R<sub>DS</sub> of 1.8 mΩ Packaged In a SON 5-mm x 6-mm footprint
- User Configurable Gate Drive Current Allows for Ease in Adapting to Custom MOSFET Selection



### Featured Applications

- Industrial Brushed-DC Motors
- Robotics
- Power Tools
- Handheld Vacuum Cleaners
- Home Automation
- Industrial Pumps and Valves

### Block Diagram

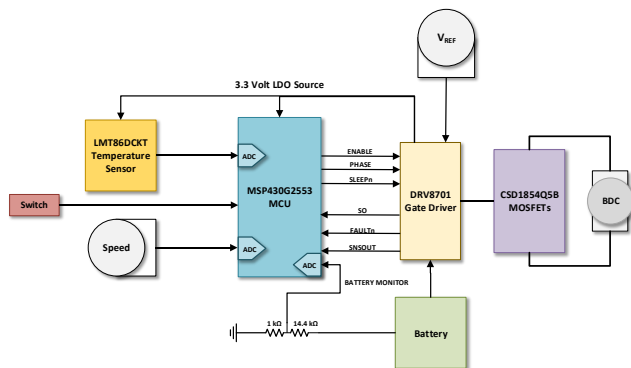

### Board Image



## 1 Key System Specifications

PARAMETER	SPECIFICATION			DETAILS
Max PCB Temperature	Maximum PCB temperature measured during motor load testing	127.7° C		See <a href="#">Section 8.7</a>
Maximum PCB Current	Maximum amount of current run through PCB during motor load testing	27.47 A		See <a href="#">Section 8.7</a>
3.3V LDO	Typical sustained 3.3 V supply measured on DVDD pin of DRV8701	3.3 V		See <a href="#">Section 8.1</a>
4.8 V LDO	Typical sustained 4.8 V supply measured on AVDD pin of DRV8701	4.8 V		See <a href="#">Section 8.1</a>
Current Limiting	Limiting current supplied to motor using VREF voltage measurement			See <a href="#">Section 8.5</a>
Dead Time	Forcibly injected settling time between when opposite signals on the same side of the H-Bridge change state	380 ns		See <a href="#">Section 8.3</a>
Direction Switch Debounce	Direction toggle switch routed through MSP430G2553 to debounce the state change prior to being routed to the DRV8701			See <a href="#">Section 8.4</a>
Sense Amplifier Voltage	Amplifies the voltage drop across the sense resistor at the base of the H-Bridge and is measured on SO pin of DRV8701			See <a href="#">Section 8.6</a>
Thermal Information	No motor load current of 2.85 Amps and maximum load current of 27.47 Amps	36.6° C	127.7° C	See <a href="#">Section 8.7</a>
RMS Motor Power	No load at 2.85 Amps and maximum load at 27.47 Amps	28.25 W	343.4 W	See <a href="#">Section 8.8</a>
IDRIVE	68 kΩ to AVDD Pin setting Source Current and Sink Current	150 mA	300 mA	See <a href="#">Section 2.4</a>
Microcontroller	Texas Instruments MSP430G2553 programmed in circuit using a four wire SPI interface			See <a href="#">Section 4.7</a>
MOSFETs	Four Texas Instruments N-Channel 60 V NexFETs			See <a href="#">Section 4.10</a>
Driver	Texas Instruments DRV8701 Brushed DC Motor Driver			See <a href="#">Section 4.6</a>

**Figure 1. Key System Specifications**

## 2 System Description


Brushed motors are a relatively popular option for motor designs because of their low price and simple control scheme. A brushed motor has a wire-wound rotor and permanent magnet stator. The commutation of the motor is achieved using conductive rings that are connected to the rotor using brushes that scrape against the commutator rings. This allows the direction of current through the motor to change based on the orientation of the brushes and different commutation rings. Utilizing an H-Bridge allows for easy direction and speed control changes to be applied quickly and efficiently to the brushed DC motor.

An electronic drive is required to control the motor currents in a brushed DC motor. The electronic drive circuit consists of:

- A power stage with two-phase inverter meeting the required power capability
- Microcontroller to implement the motor speed commands and fault handling
- Current sensing for motor startup / stall protection
- Gate driver for controlling the two-phase inverter
- Power supply for microcontroller and other low voltage devices


### 2.1 PWM and Phase Control

In a BDC motor, a simple Pulse Width Modulation (PWM) signal can be used to control the speed of the rotor. As the duty cycle of the PWM signal changes the average voltage delivered to the motor is varied allowing for different rotor speeds without burning up power through a resistive potentiometer. The direction of the motor is then controlled using a two-phase inverter that allows the direction of current supplied to the motor to be changed quickly using four independently controlled MOSFETs as shown in **Figure 2** below.

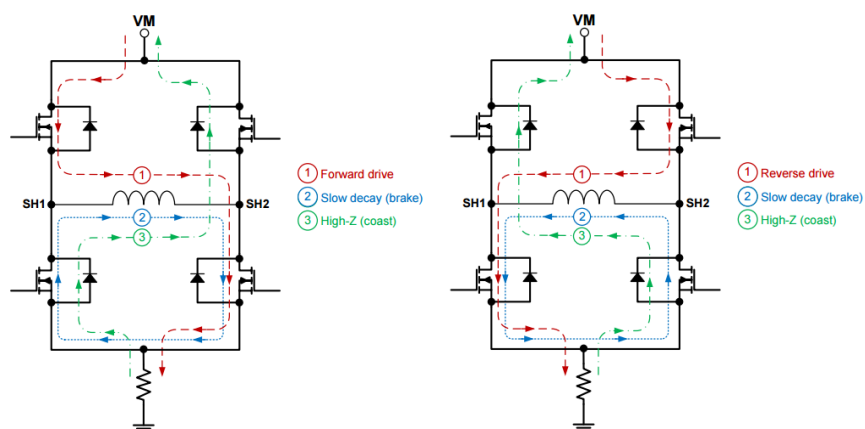

**Figure 2. Two-Phase Inverter Current Directions**

The PWM signals used to control the motor are generated using the MSP430G2553. By sampling the wiper voltage of the Speed potentiometer and comparing that sample to Timer\_A of the MSP430 a PWM signal with varying duty cycle and a constant switching frequency is created as shown in **Figure 3** below.

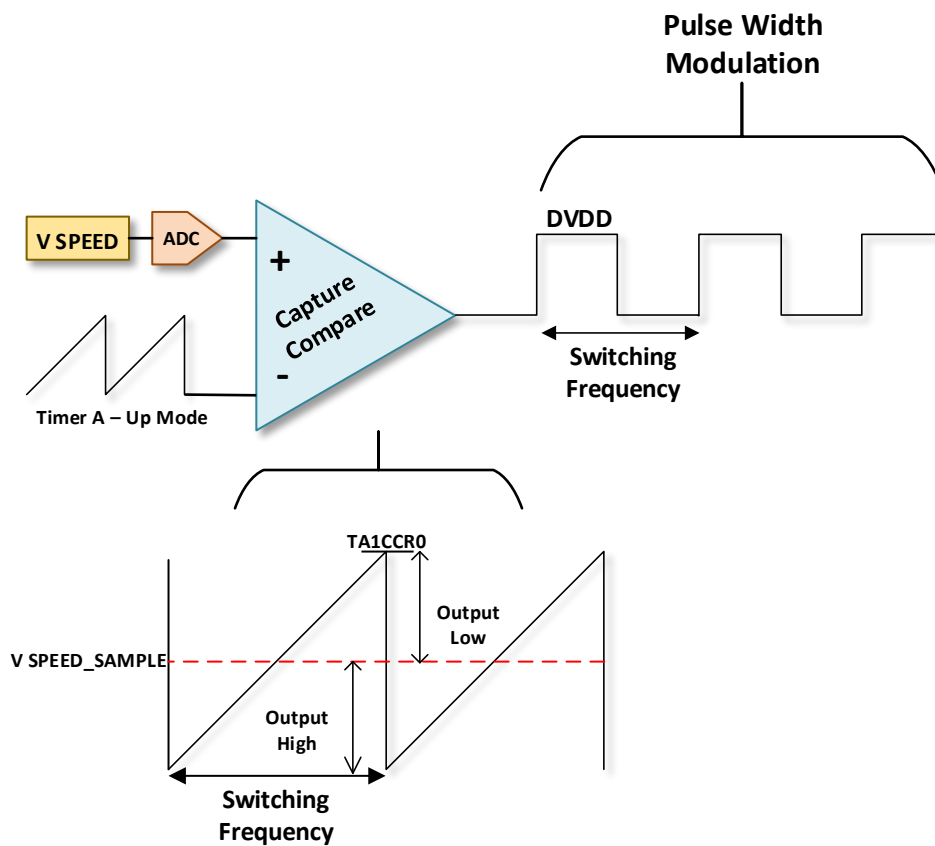


**Figure 3. MSP430G2553 PWM Timer\_A Scheme**

## 2.2 Current Chopping Using $V_{REF}$

To control the current through the motor a sense resistor is placed at the base of the H-Bridge between the source of both low side MOSFETs and ground. An internal operational amplifier in the DRV8701 is then connected across the sense resistor and ground enabling the driver to measure the voltage drop and amplify it by a scaling factor  $A_V$  to generate a larger amplitude value. This voltage is referred to as  $V_{SO}$  and is compared to the voltage set on the  $V_{REF}$  pin; if  $V_{SO}$  is greater than or equal to  $V_{REF}$  the bridge stops generating gate signals until the voltage has dropped below  $V_{REF}$ , if  $V_{SO}$  is less than  $V_{REF}$  the bridge will continue to generate gate signals.  $V_{SO}$  relates to the current running through the motor using **Equation 1**:

$$V_{SO} = A_V * (I_{DRIVE} * R_{SENSE}) \quad (1)$$

In the event that  $V_{SO}$  is greater than or equal to  $V_{REF}$  the output of the SNSOUT Pin is pulled low to indicate a driver fault and the DRV8701 is current chopping the gate signals. While  $V_{SO}$  is less than  $V_{REF}$  the output of the SNSOUT pin can be pulled logic high using an external pull up resistor indicating that the device is operating in a typical drive current state. An example of a driving current scheme with current chopping is shown in **Figure 4** below.

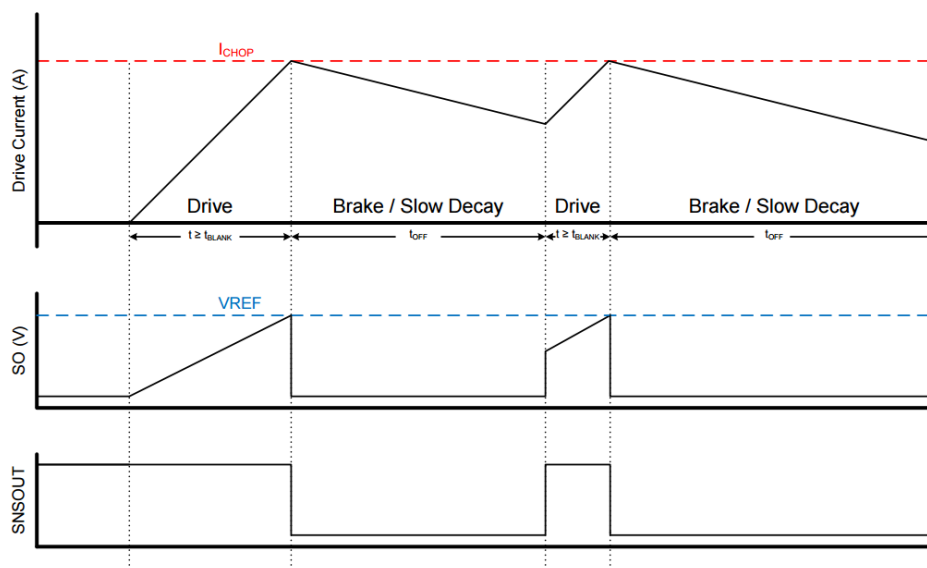


**Figure 4. IDRIVE Current Chopping**

In **Figure 4** above the motor is being initially driven and the current draw from the supply increases. Once the voltage measured across the sense resistor ( $V_{SO}$ ) is equal to or greater than  $V_{REF}$  the SNSOUT Pin is pulled low and the output gate signals are cut off for the remainder of that PWM switching interval. On the next PWM switching interval the induction of the motor still retains some of the current run through the motor on the last drive cycle resulting

in the driver spending a smaller amount of time driving the motor before  $V_{SO}$  is equal to  $V_{REF}$  and the gate signals to the bridge are cut off.

## 2.3 IDRIVE

Using the DRV8701 to provide gate signals to the MOSFETs in the two-phase inverter allows for the selection of  $I_{SINK}$  and  $I_{SOURCE}$  currents using the IDRIVE settings. The goal in controlling  $I_{SOURCE}$  and  $I_{SINK}$  is to tune the amount of current supplied to the gates of the four MOSFETs in the H-Bridge and achieve the desired slew rate between active and saturated regions without supplying excess current to the device. If the slew rate of the MOSFETs is too low the device will spend too much time in the Miller Region shown in **Figure 5** below.

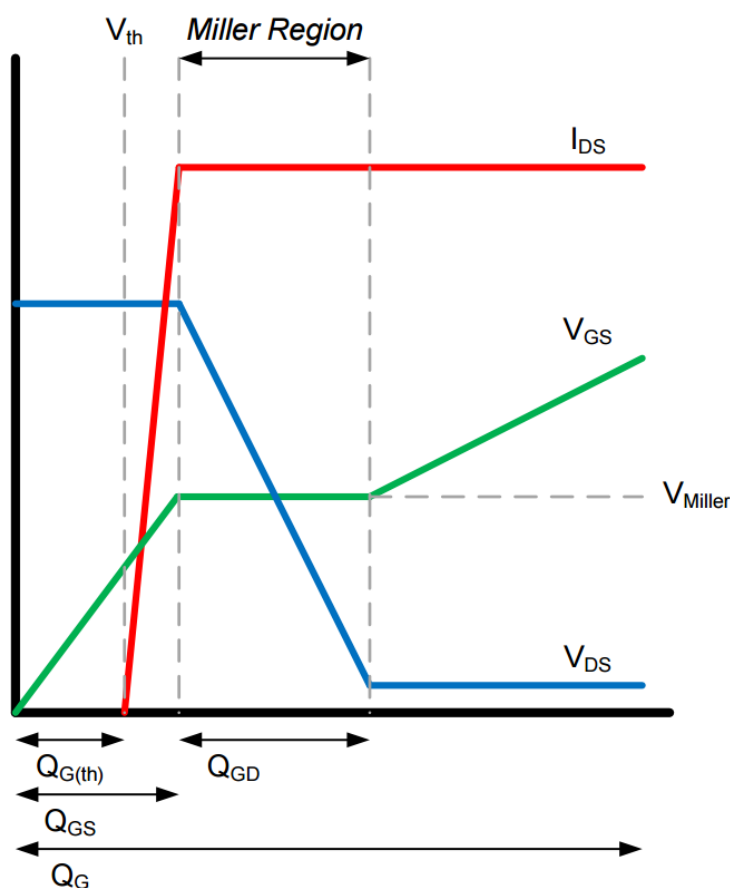

**Figure 5. Miller Region of Typical MOSFET**

While the device is operating in the Miller region the  $R_{DS}$  value of the MOSFET is changing from  $R_{DS\_OFF}$  to  $R_{DS\_ON}$  while the current is kept constant. Having a higher resistance as a large amount of current runs through the device results in the generation of heat for the period of time the device is operated in the Miller region. Properly matching the  $I_{SINK}$  and  $I_{SOURCE}$  currents to the gate capacitances of the selected MOSFETs generates a faster slew rate which results in less time spent in the Miller region and less heat dissipated through the device.

### 3 Block Diagram

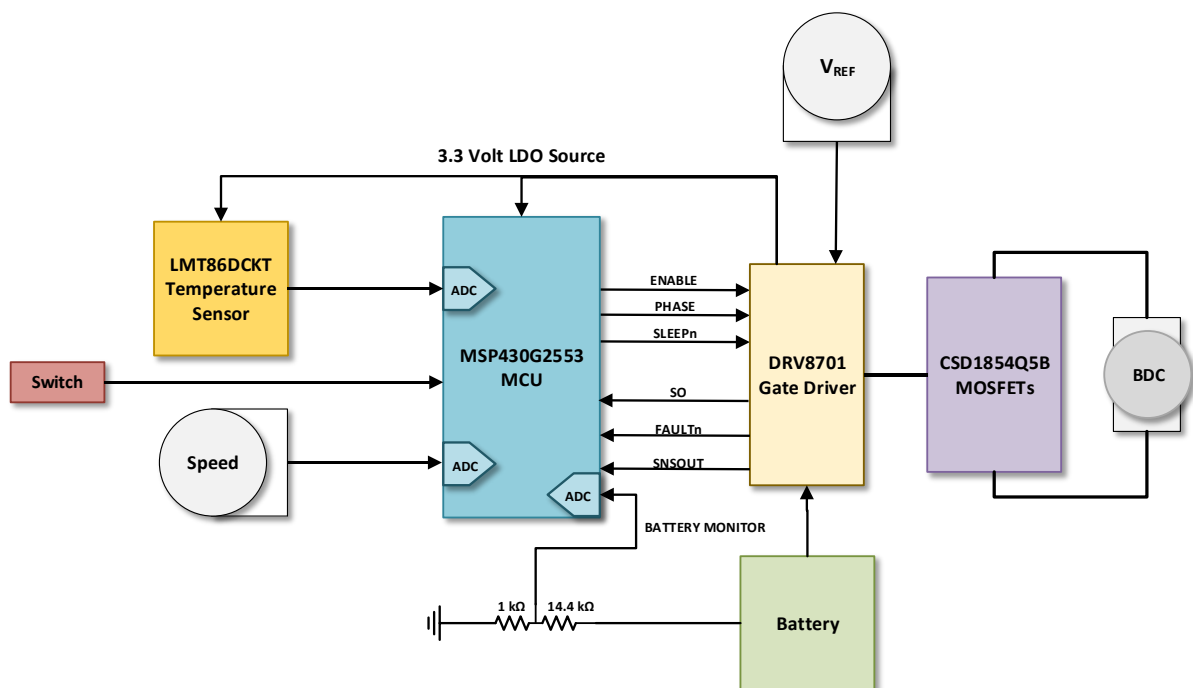


Figure 6. System Block Diagram

#### 3.1 Highlighted Products

##### 3.1.1 DRV8701ERGER

The DRV8701 is a single H-bridge gate driver that uses four external N-channel MOSFETs oriented in a two-phase inverter to drive one bidirectional brushed DC motor. The Phase / Enable (DRV8701E) control scheme allows simple interfacing to microcontroller circuits. An internal sense amplifier allows for adjustable current control using an external sense resistor. The gate driver includes the ability to control the winding current using fixed off-time PWM current chopping. The DRV8701 drives both high- and low-side FETs with 9.5-V VGS gate drive sourced from an integrated charge pump. The gate drive current for all external FETs can be configured with a single external resistor on the IDRIVE pin.

##### 3.1.2 MSP430G2553IPW20

The MSP430G2553 is an ultra-low-power microcontroller that consists of many different device features. Some of these features include five different low-power modes, a 16-bit RISC CPU, 16-bit registers, and constant generators. Using the Digitally Controlled Oscillator (DCO) the MSP430G2553 can wake up from low-power modes in less than 1  $\mu$ s.

### 3.1.3 [CSD18540Q5B](#)

---

The CSD18540Q5B is a 60 V N-Channel MOSFET with an  $R_{DS}$  rating of 1.8 m $\Omega$ . The device is desired for power conversion applications because of its design for minimized losses and small SON 5-mm  $\times$  6-mm footprint.

### 3.1.4 [LMT86DCKT](#)

---

The LMT86DCKT is a precision CMOS temperature sensor that utilizes an analog output voltage that is linearly and inversely proportional to temperature. This device can operate down to a 2.2 V supply with 5.4  $\mu$ A making it an ideal device to use with battery operated applications.



## 4 System Design Theory

### 4.1 Board Layout

The PCB created for this application has two stages; the power stage and the control stage. The control stage consists of the MSP430G2553 and the DRV8701 along with the  $V_{\text{SPEED}}$  and  $V_{\text{REF}}$  potentiometers and direction microswitch. To flash the MSP430 with firmware changes a JTAG header is included to allow for SPI-by-wire in-circuit flashing. The power stage on this board includes four NexFETs, two 470 $\mu\text{F}$  bulk capacitors,  $R_{\text{SENSE}}$ , and a 30 A / 60 V fuse. This board was printed with 2 oz. copper and approximately 93% of the board was poured with copper.

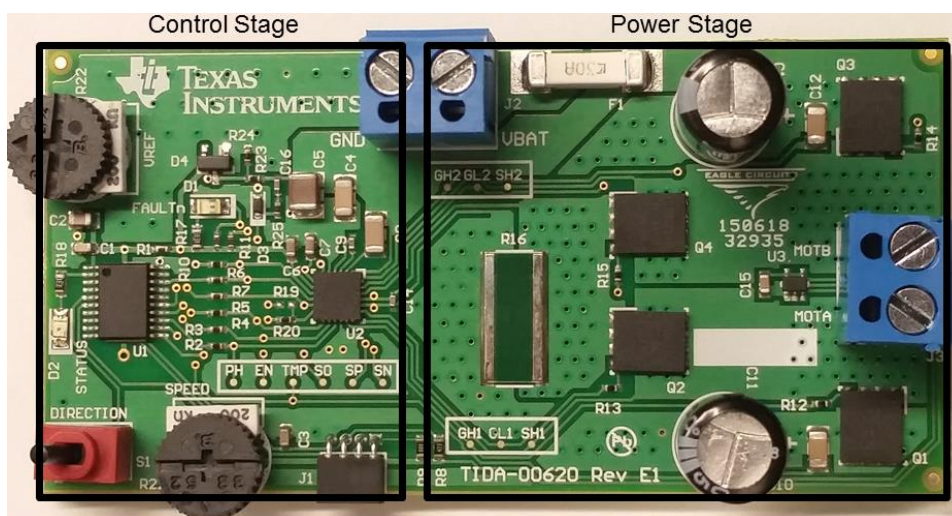


Figure 7. Board Stage Layout


The power stage takes up a large footprint on this board because the copper planes on the PCB are used to dissipate the heat generated by the sense resistor and four power MOSFETs instead of using an external finned heat sink. Each of these planes has a large number of vias linking the top plane with the bottom plane to help with current flow and move heat to the bottom plane to help with dissipation. The four NexFET MOSFETs have a  $R_{\text{DS\_ON}}$  of 1.8 m $\Omega$  and the maximum amount of sustained current drawn in testing this PCB design was 27.47 Amps. Using equation 2 and 3 below each active MOSFET was dissipating approximately 1.358 Watts of power while the sense resistor was dissipating approximately 3.773 Watts.

$$P_{\text{MOSFET\_DISSIPATED}} = (27.47 \text{ A})^2 \times 1.8 \text{ m}\Omega = 1.358 \text{ Watts} \quad (2)$$

$$P_{\text{RSENSE\_DISSIPATED}} = (27.47 \text{ A})^2 \times 5 \text{ m}\Omega = 3.773 \text{ Watts} \quad (3)$$

## 4.2 Battery Monitoring Layout

Battery Monitoring in this application is achieved using a voltage divider to scale the voltage present on the Vbat monitor trace to a value safe for the ADC of the MSP430G2553 to sample and continuously monitor. The two diodes provide external paths for conditions where the voltage is too large or reversed in polarity. In the case of an overvoltage condition the diode connected between the Vbat monitor trace and DVDD will start conducting. The 13.3 k $\Omega$  resistor will be in series with the current path and limit the amount of current allowed to flood in to the DVDD rail. This condition would be superseded by the MSP430G2553 flagging the voltage and pulling down the SLEEPn pin, thus causing the DRV8701 to shut off and stop the LDO producing 3.3 V on DVDD. If the polarity of the battery were to be flipped the diode connected between Vbat monitor and ground would conduct and stop the reverse current condition from causing harm throughout the VM current path.

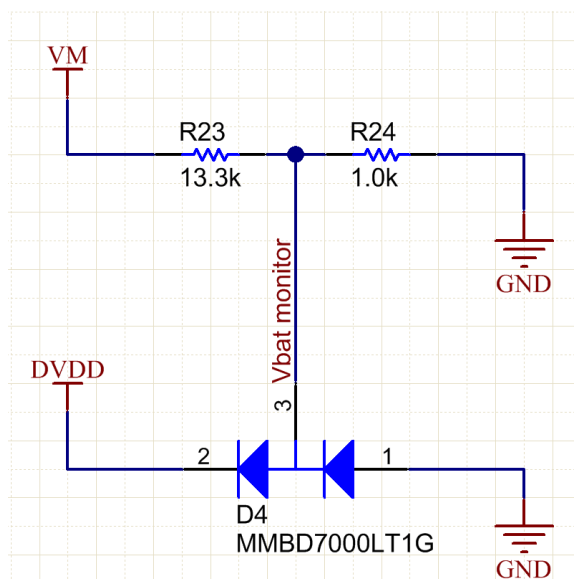

**Figure 8. Battery Monitoring**

### 4.3 SLEEPn Pin Startup

Once the device has been successfully powered on the RC circuit below will begin charging up from the  $V_M$  supply while the zener diode holds the voltage to 3.3V for the duration of the charge time of the RC circuit formed by  $C_{16}$  and  $R_{25}$ . The charge time before the RC circuit voltage drops below the zener voltage is calculated using **Equation 4** below.

$$t_{\text{STARTUP}} = -(\ln(V_{\text{ZENER}} / V_M)) * R_{25} * C_{16} = -(\ln(3.3 \text{ V} / 18 \text{ V})) * 1 \text{ k}\Omega * .47 \mu\text{F} = 797.33 \mu\text{s} \quad (4)$$

During this time the DVDD LDO is turned on in the DRV8701 driver allowing for the MSP430G2553 to be powered on. As soon as the MSP430G2553 is powered on the GPIO pin connected to SLEEPn is pulled high for the duration of the devices operation.

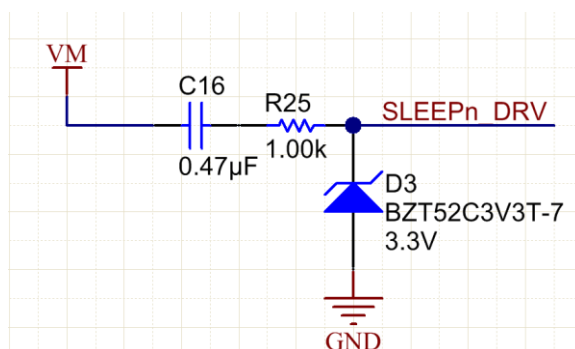


Figure 9. SLEEPn Pullup Pin

### 4.4 Temperature Sensor

The temperature sensor is placed between the two legs of the H-Bridge to allow for the most direct measurements of temperature between the four bridge MOSFETs. Placing the temperature sensor here allows for real time temperature interrupts that the driver would not be able to detect. This device outputs an analog voltage that is then measured using the MSP430G2553's ADC and if an internal interrupt is flagged as an over temperature condition the PWM output of the microcontroller is stopped until the temperature has dropped.


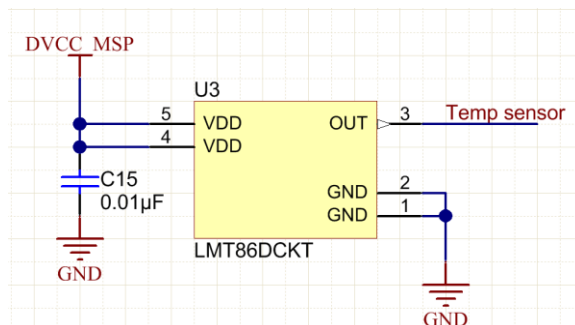


Figure 10. Temperature Sensor Schematic

## 4.5 H-Bridge


The N-Channel NexFET MOSFETs are used in each of the four switching positions in the H-Bridge as shown in **Figure 11** below.  $0\ \Omega$  resistors are placed between the gate of each MOSFET and gate drive pins of the DRV8701 to allow for each MOSFET to be disconnected from the driver by quickly removing the resistor. Connections to the sense amplifier pins of the DRV8701 are tied to the drain and source of each corresponding MOSFET within the bridge to aid the driver in measuring  $V_{DS}$  of each of the four MOSFETs.  $R_{SENSE}$  also has a dedicated sense amplifier that allows the DRV8701 to monitor the voltage drop across  $R_{SENSE}$  and use this value to monitor the motor current. By measuring  $V_{DS}$  of each MOSFET the DRV8701 can protect against over current events and will flag a fault condition when  $V_{DS}$  is above 800 mV.

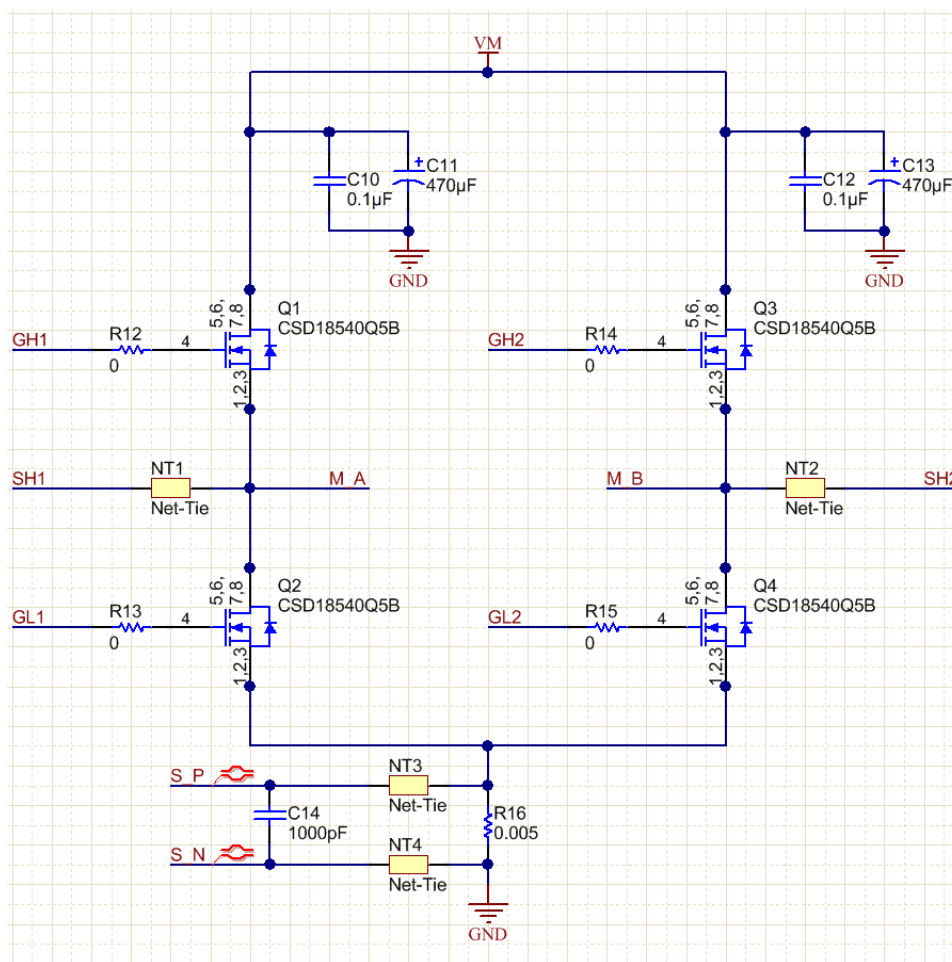

**Figure 11. H-Bridge Schematic**

## 4.6 DRV8701


The DRV8701 schematic below in **Figure 12** illustrates the placement of stabilization capacitors connected to the outputs of each LDO regulator and the DRV8701 supply voltage  $V_M$ . Both the 3.3 V and 4.8 V internal regulators are Low-Dropout (LDO) regulators which result in switching transients that need to be properly stabilized in order for the output voltage rail to be usable by other devices. The supply voltage  $V_M$  is tied to both a large bulk capacitor  $C_5$  and a smaller capacitor  $C_4$ . This rail requires a large bulk capacitance close to the DRV8701 because it is shared with the switching components of the H-Bridge, meaning it is susceptible to possible voltage drooping that could damage the driver.

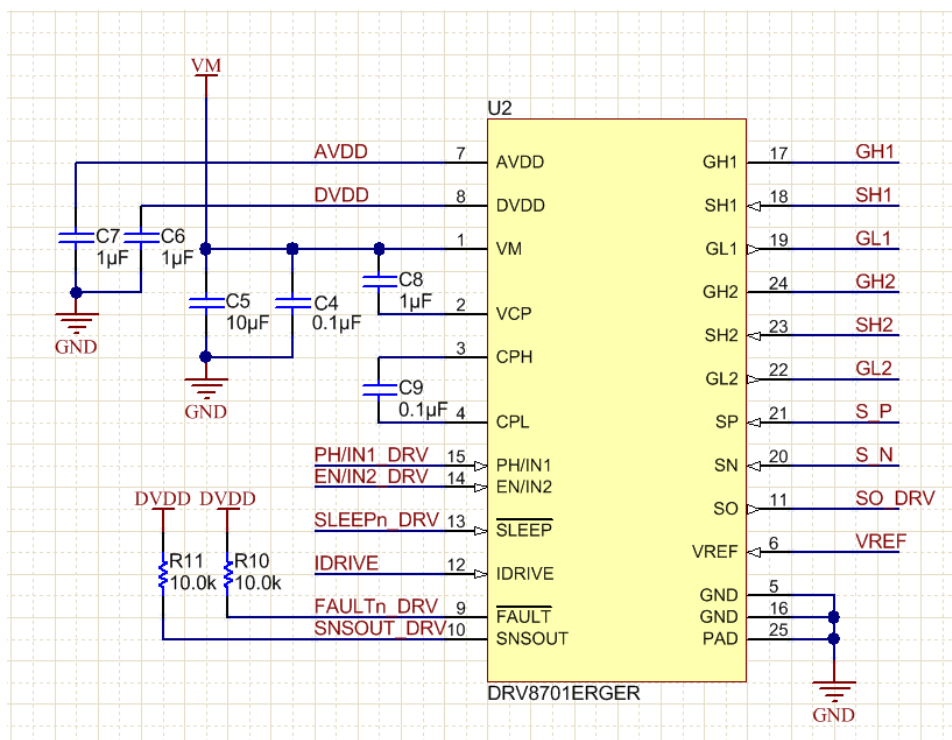

**Figure 12. DRV8701 Schematic**

## 4.7 MSP430G2553

Shown below in **Figure 13** is the schematic for the MSP430G2553 placement. Two capacitors are placed on the power pin DVCC\_MSP to allow for adequate transient filtering prior to the input pin of the device. This allows for any sudden and momentary drop in supply voltage to be filtered out of the rail prior to being supplied to the MSP430G2553. This configuration of the device does not need to utilize any external crystal oscillators or other peripheral timing connections. The supply voltage for the MSP430G2553 is sourced from the 3.3 V LDO of the DRV8701 and the devices are connected together using a 0 Ω resistor allowing for quick disconnection of the power rail in the event that the user wants to externally power the MSP430G2553.

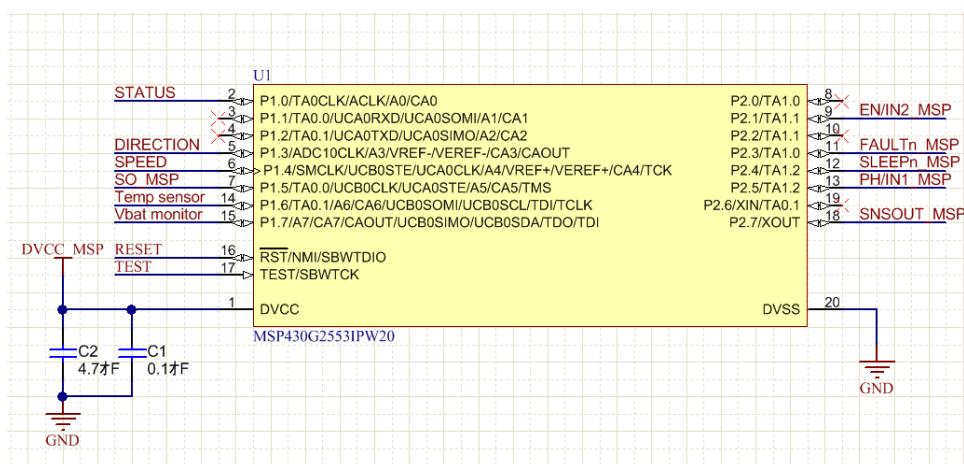

**Figure 13. MSP430G2553 Schematic**

## 4.8 R<sub>SENSE</sub> Placement

Placing R<sub>SENSE</sub> in an isolated position at the center of the board allows for the device to dissipate heat without harming other discrete devices in close proximity to it. The value of R<sub>SENSE</sub> in this design is 5 mΩ and it is rated for 6 W. The maximum current pulled through the board during testing was 27.47 Amps, meaning this resistor dissipated 3.77 Watts during that time. R<sub>SENSE</sub> ties the two low side FETs of the H-Bridge to ground so the device has to be able to sink continuous current while the motor is spinning in either direction. This continuous flow of current through the resistor results in the need for a large ground pour directly adjacent to the device to allow for an unimpeded path for current flow and adequate heat dissipation.

## 4.9 Bulk Capacitors

A result of using a Pulse Width Modulated scheme for motor control is sudden current draw from the supply voltage V<sub>M</sub>. In order to compensate for this sudden change in current the bulk capacitors are placed very close to the high side voltage supply rails to help stabilize any resulting voltage sag in V<sub>M</sub>. Stray inductance present in the supply lines will result in a slowed response in changing current which will momentarily pull down the voltage on V<sub>M</sub>. Having the Bulk Capacitors properly placed will cushion this short period of voltage sagging.

#### 4.10 MOSFET Selection

---

For this reference design the 60 Volt N-Channel NexFETs were selected because they have a relatively low  $R_{DS\_ON}$  for this applications design constraints with power throughput. If the user were interested in running the board at lower power / very low current specifications and would like to achieve a much smaller footprint, the Texas Instruments 30 V N-Channel FemtoFET MOSFET could be selected. This device has an  $R_{DS\_ON}$  of approximately 90 m $\Omega$  but resides in an ultra-small 0402 case footprint, which would result in a significant board reduction for a lower power solution. For a higher power solution with a larger footprint, the Texas Instruments 100 V N-Channel NexFET could be selected. This device has an  $R_{DS\_ON}$  of 6.4 m $\Omega$  but can handle up to 110 Amps of continuous current at 25°C.



## 5 Getting Started Hardware

### 5.1 Control Overview

A labeled diagram of the different inputs and outputs on the TIDA-00620 board are shown below. The blue terminal blocks are used to screw down wires connecting the external power supply and motor wire leads to the contacts on the PCB board. To flash the firmware on the MSP430G2553 the SPI-Bi-Wire header can be connected to a TI Launch Pad using a 4 wire header soldered to the Launch Pad board.

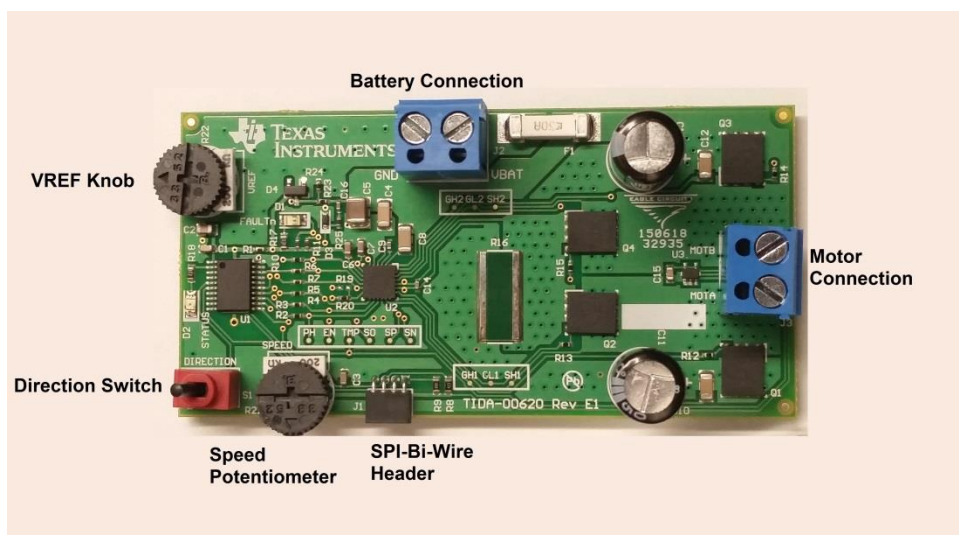


Figure 14. Labeled Board Interface

### 5.2 Initial Power On

This design can be operated anywhere between 12 and 24 Volts without causing any problems with the internal components. When connecting the power source to the board make sure the battery terminals are connected correctly to the VBAT (+ Battery Terminal) and GND (- Battery Terminal) correctly. Once power is applied if the MSP430G2553 has powered on and is generating control signals correctly the green status LED will turn on and stay on.


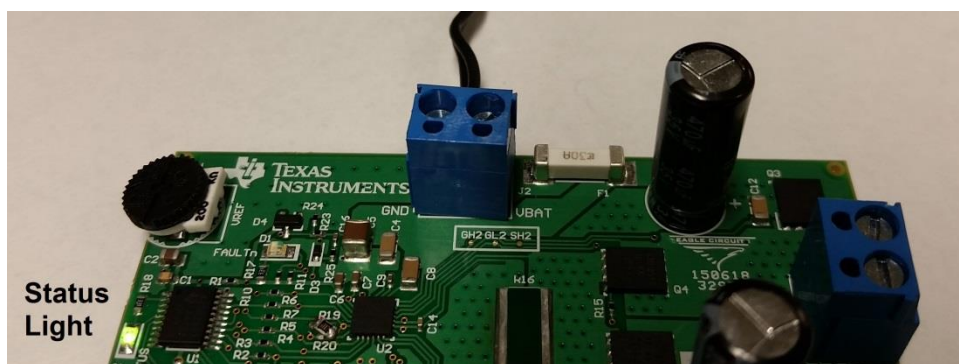


Figure 15. Status LED

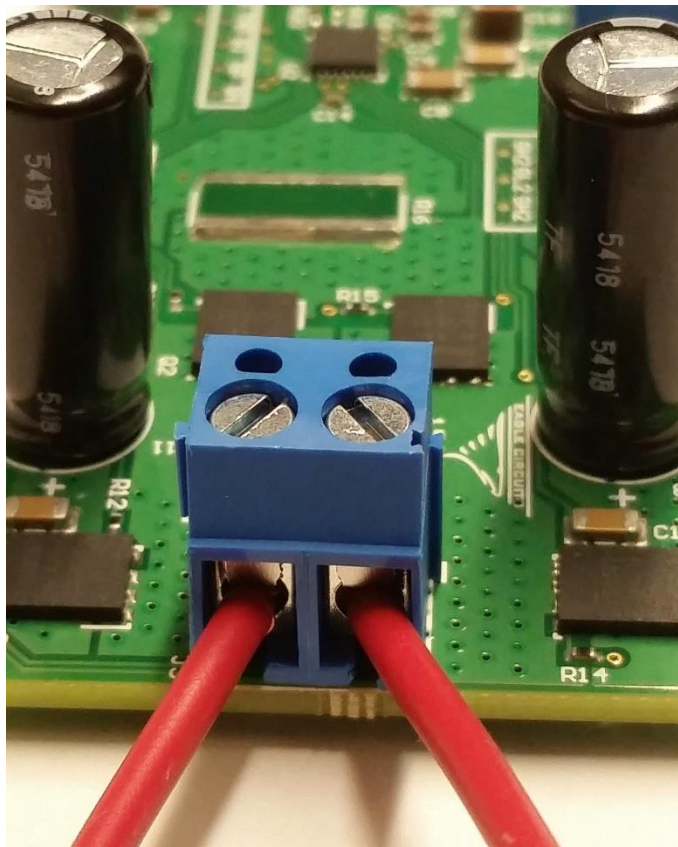

### 5.3 Motor Connection

To connect the motor to the PCB the blue terminal block located on the right side of the board can be used to connect the motor. For this connection the wires in the terminals dictate the direction the motor will spin and the datasheet for each motor can be referenced to determine which motor terminal will result in a specific driving direction. The motor wires can be placed in each terminal using a flat head screw driver to tighten down the terminal block onto the bare wire as shown in **Figure 16** below.



**Figure 16. Motor Terminal Connections**

---

## 6 Getting Started Firmware

---

### 6.1 Watch Dog Timer Control and DCO Initialization

---

The first thing the firmware will do upon startup is initialize global variables and function calls. The firmware will then disable the Watch Dog Timer and calibrate the Digitally Controlled Oscillator (DCO) to run at 8 MHz. This clock speed allows the MSP430G2553 to have the desired resolution / operating speed for all of the DCO sourced timers and ADC samples.

```
#include <msp430g2553.h>

int Speed;
int Temp;
int Battery_Voltage;

void Speed_Pole();
void Temp_Monitor();
void Battery_Monitor();

void main(void)
{
    WDTCTL = WDTPW + WDTHOLD;    // Stop Watch Dog Timer

    DCOCTL = CALDCO_8MHZ; // Calibrate DCO to 8 MHz as opposed to default 1 MHz
    BCSCTL1 = CALBC1_8MHZ;
```

### 6.2 SLEEPn Pin Pull Up

---

Next pin 2.4 of the MSP430G2553 is immediately initialized and pulled high. This pin is in charge of keeping the DRV8701 awake and on. When  $V_M$  is initially applied the Zener circuit shown in **Section 4.3** above will wake up the driver for a short period of time which enables the LDO to power up the MSP430. Eventually the RC time constant of the Zener circuit will drop below the required logic high voltage and the DRV8701 will go back to sleep, meaning the MSP430 must take control of this pin upon initial power up and hold it high to keep the 3.3 V LDO operating.

```
P2DIR |= BIT4;           // Set Direction of P2.4 as output
P2SEL &= (~BIT4);       // Set P2.4 as GPIO
P2OUT |= BIT4;          // Set state of P2.4 to high
```

## 6.3 Low Power Mode Wakeup Timer

Once the sleep pin has been pulled high the firmware then enables and initializes Timer A0 which is used to wake the device up from low power mode and poll the user inputs every 1 ms. The timer is configured in Up Mode, meaning it will continuously count up to the value set in TA0CCR0. From the previously initiated DCO clock speed of 8 MHz, register TA0CCR0 is set to 8000 because it will take the microcontroller approximately 1 ms to count to that value using this clock speed. The 1 ms interrupt time is chosen for this application because this allows the microcontroller to significantly reduce its power consumption while still operating at a reasonable speed for human perception of the changes in input states.

```
TA0CCTL0 = CCIE;           // CCR0 interrupt enabled
TA0CTL = TASSEL_2 + MC_1;  // SMCLK, upmode
TA0CCR0 = 8000;           // Trigger interrupt once every 1 ms (8000 / 8MHz = 1ms)
P1OUT &= 0x00;           // Clear Registers
P1DIR &= 0x00;
```

## 6.4 Pin Initializations

With the system crucial pins and timers set the device now enters into initializing the desired GPIO pins for setting the states of the various inputs and outputs. These include the speed potentiometer, direction switch, FAULTn pin, Phase pin, Enable pin, Temperature sensor, and Battery Monitor.

```
P1DIR &= (~BIT3);         // Set Direction of P1.3
P1SEL &= (~BIT3);         // Set P1.3 as a GPIO Pin
P2DIR |= (BIT1+BIT5);     // Set Pin 2.1 and 2.5 as outputs
P2DIR &= ~BIT3 + ~BIT7;   // Set Pin 2.3 and 2.7 as an input
P2SEL |= BIT1;           // Route TA1.1 to output pin
P2SEL &= (~BIT7)+(~BIT5)+(~BIT3); // Set Pin 2.7, 2.5, 2.3 as GPIO
P2REN |= BIT3 + BIT7;    // Assign Pull Up Resistor to P2.3 and P2.7
```

## 6.5 PWM Timer Control

In order to control the speed the motor is spinning at a PWM signal must be generated. To do this the MSP430G2553 utilizes Timer\_A initialized to run in Up Mode where the timer will continuously count from 0 to the value set in register TA1CCR0 and then reset to 0. The value set in the TA1CCR0 register is 255, which results in a switching frequency of 31.372 kHz with the 8 MHz clock speed previously selected. Ideally the switching frequency selected should be greater than 20 kHz so that the PWM will not make an audible sound in the motor.

```
TA1CCR0 = 255;           // PWM Period, maximum value for Timer A1(8 MHz/255 = 31.372 kHz)
TA1CCTL1 = OUTMOD_7;    // CCR1 reset/set
TA1CTL = TASSEL_2 + MC_1; // Chooses SMCLK and Up Mode
```

## 6.6 Analog to Digital Converter Initialization

Once the PWM timer has been initialized the firmware then initiates the analog to digital converter connected to pin 1.4, or the  $V_{\text{SPEED}}$  connection from the Speed potentiometer. The ADC is configured to sample this voltage and convert the sample based on the 3.3 V supply voltage to the device. The result from this conversion is then stored in memory and written to the Speed variable.

```
ADC10CTL0 = ADC10SHT_3 | ADC100N;
ADC10CTL1 = INCH_4;
ADC10AE0 = BIT4;
ADC10CTL0 |= ENC + ADC10SC;
while (ADC10CTL1 & ADC10BUSY);
Speed = ADC10MEM;
```

## 6.7 Status Light and Low Power Mode

Once all of the required timers and pins are properly configured the last thing the firmware will do in the main function is set the green LED status light to turn on. After this is completed the device then shuts off all other timers except the SMCLK which is sourced from the initial 8 MHz DCO and any general interrupts. This means that after this line in the firmware the device will simply sit and count up to TA1CCR0 for the PWM signal and TA0CCR0 where the interrupt service routine shown in **Section 6.11** begins.

```
P1DIR |= BIT0;
P1SEL &= (~BIT0);
P1OUT |= BIT0; // Set state of P1.0 to high (Status Light)

_BIS_SR(CPUOFF + GIE); // Enter LPM0 with interrupts
}
```

## 6.8 Speed\_Pole Function

After initializing all of the static states of timers and pins in the MSP430G2553 the firmware then defines the Speed\_Pole function. This function momentarily stops the ADC, changes the input pin to pin 1.4, takes a sample and writes that sample to the global Speed variable.

```
void Speed_Pole(void)
{
    ADC10CTL0 &= ~ENC;
    ADC10CTL1 = INCH_4;
    ADC10AE0 = BIT4;
    ADC10CTL0 |= ENC + ADC10SC;
    while (ADC10CTL1 & ADC10BUSY);
    Speed = ADC10MEM;
}
```

## 6.9 Battery\_Monitor Function

The Battery\_Monitor function is the next function to be initialized by the firmware. This function stops the ADC, changes the input pin to pin 1.7, samples the voltages and writes that value to the Battery\_Voltage variable. This variable is then compared to two different values, 217 and 620. These values correspond to the voltage range available for use with this reference design and are calculated using the Battery Monitoring circuit in **Section 4.2** above. The battery voltages allowable using this function are shown in **Equation 5** and **Equation 6** below.

$$V_{\text{BATT\_MONITOR\_LOWER}} = (217 / (2^{10} - 1)) * 3.3 * 14.4 = 10.08 \text{ Volts} \quad (5)$$

$$V_{\text{BATT\_MONITOR\_UPPER}} = (620 / (2^{10} - 1)) * 3.3 * 14.4 = 28.8 \text{ Volts} \quad (6)$$

If the battery voltage for this design is dipped below 10.08 V or above 28.8 V the MSP430 will pull the SLEEPn pin of the DRV8701 low, thus disabling the 3.3 V LDO and shutting down the entire control / driver system. The board can be restarted by reapplying the correct voltage based on the above calculations.

```
void Battery_Monitor(void)
{
    ADC10CTL0 &= ~ENC;
    ADC10CTL1 = INCH_7;
    ADC10AE0 = BIT7;
    ADC10CTL0 |= ENC + ADC10SC;
    while (ADC10CTL1 & ADC10BUSY);
    Battery_Voltage = ADC10MEM;

    if (Battery_Voltage < 217 || Battery_Voltage > 620){
        P2OUT &= ~BIT4;        // Set state of P2.4 to low, putting DRV8701 to sleep
    }
    else{
    }
}
```

## 6.10 Temp\_Monitor Function

The last function that is initialized in the firmware is the Temp\_Monitor function. This function stops the ADC and reconfigures it to sample from pin 1.6. The value converted from pin 1.6 is then written to the Temp variable and compared to a static amount of 202. The 202 value corresponds to a voltage amount of 651.16 mV, which using the temperature tables found in the LMT86DCKT datasheet is approximately 130° C measured at the temperature sensor. If the voltage drops below this value that means the sensor is greater than 130° C so the firmware then writes a zero to the speed variable which will cause the PWM signal sent to the driver to stop until the temperature sensor has dropped below this temperature.

```

void Temp_Monitor(void)
{
    ADC10CTL0 &= ~ENC;
    ADC10CTL1 = INCH_6;
    ADC10AE0 = BIT6;
    ADC10CTL0 |= ENC + ADC10SC;
    while (ADC10CTL1 & ADC10BUSY);
    Temp = ADC10MEM;

    if (Temp < 202) {
        Speed=0;
    }
    else{
    }
}
  
```

## 6.11 Timer A Interrupt Service Routine

Once Timer A has reached the value stored in TA0CCR0 an interrupt service routine is entered and the MSP430G2553 will awake from low power mode. In this interrupt service routine the Direction pin (P1.3) is poled and if it is high the MSP430 sets the state of the Phase pin (P2.5) to be high and if P1.3 is low, P2.5 is set low. In this service routine the three functions defined above are called and the value stored in the Speed variable is normalized to fit in the 8 Bit TA1CCR1 register. Once these processes are completed the interrupt service routine is complete and the MSP430G2553 goes back into low power mode.


```

#pragma vector=TIMER0_A0_VECTOR
__interrupt void Timer_A (void)
{
    if((P1IN & BIT3) == BIT3){ // If P1.3 is pulled high then pull Pin 2.5 high
        P2OUT |= BIT5; // Set State of Pin 2.5 as high
    }
    else{ // If P1.3 is initially pulled low then pull Pin 2.5 low
        P2OUT &= (~BIT5); // Set state of Pin 2.5 as low
    }
    Battery_Monitor();
    Speed_Pole();
    Temp_Monitor();
    TA1CCR1 = (Speed/4); // Normalize 10BitADC Speed Value to 8Bit Timer A Register and
                        // write to TA1CCR1 Register
}
  
```

## 7 Test Setup

### 7.1 Block Diagram of Load Testing

The load test determines the thermal characteristics and current carrying capabilities of this design's power stage. **Figure 17** shows the load testing setup used for this reference design.

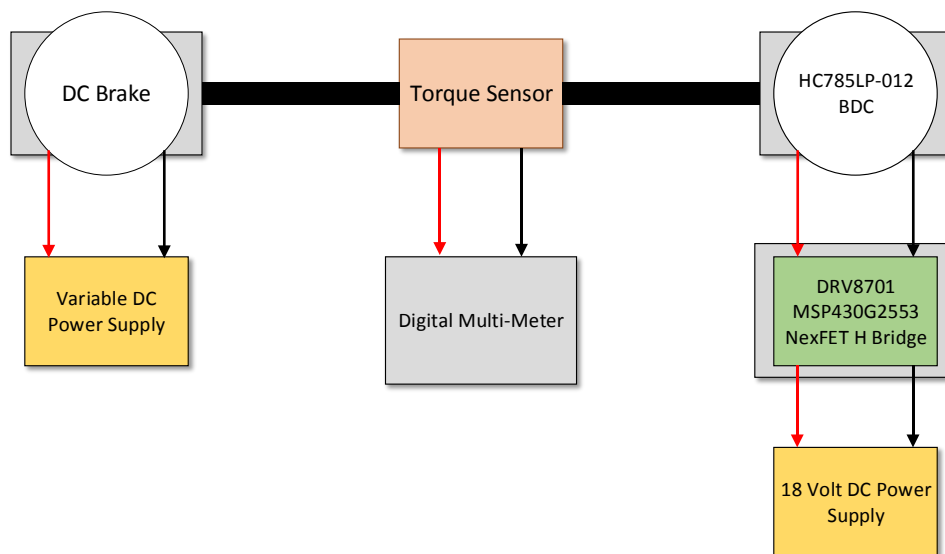

**Figure 17. Load Test Diagram**

The motor shaft is connected to a DC brake through a torque sensor. The brushed DC Motor is rated to deliver a shaft torque of 148.10 mNm at 19.99 Amps and 18310 RPM. The motor is loaded by means of a DC brake controlled by a variable DC supply. The speed of the motor is kept constant and the voltage supplied to the variable DC brake was incrementally increased to adjust the load needed to be produced by the DC motor. The motor supply current was incremented in 1 Amp intervals and the resulting torque reading from the torque sensor as well as maximum PCB temperature measured using a thermal camera were recorded. The RMS power delivered to the motor was also recorded by measuring the RMS current supplied to the motor and multiplying that by the RMS voltage measured across the motor terminals. The supply voltage ( $V_M$ ) for the driver was kept at a constant 18 Volts. No exhaust fans or heat sinks were used for the maximum PCB temperature measurements.

## 7.2 Load Test Fixture

For the load testing of the TIDA-00620 board an aluminum test fixture was used to hold the DC Motor, Torque Sensor, and DC Brake. The fixture had a center channel bored through the center of the aluminum block which allowed for mounting L brackets holding the motor and brake aligned with each other. The Torque sensor was mounted at an offset from this center channel to accommodate the spindle of this device to be in line with the motor and brake. Flexible couplings were then used to attach the spindle of the motor to the left torque sensor spindle and the right spindle of the torque sensor to the brake spindle. These flexible couplings allow for any slight offset in alignment to be accounted for without overly stressing the mounting brackets of each device. Each of the devices shown in **Figure 18** below were connected to a respective control device as shown in **Figure 17** in Section 7.1.

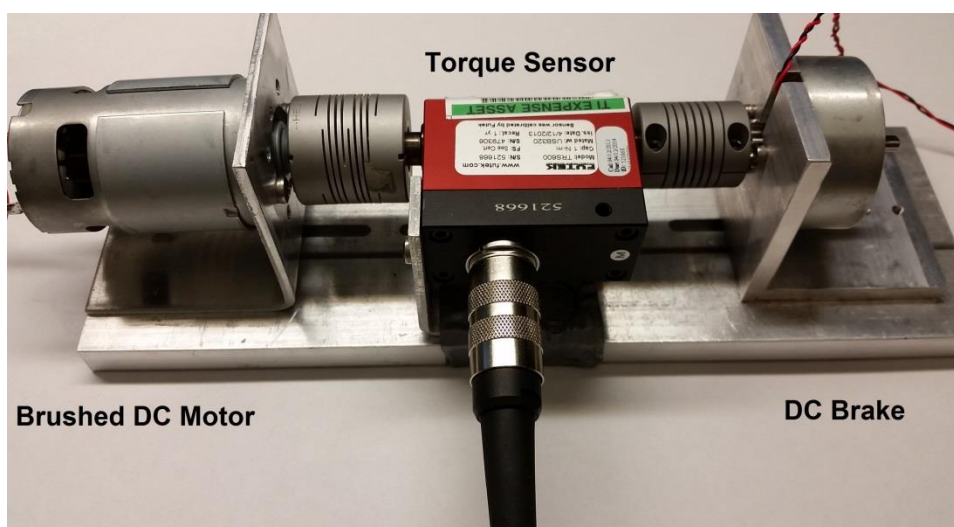


Figure 18. DC Motor / Torque Sensor / DC Brake Test Fixture



## 8 Test Data

### 8.1 DRV8701 Integrated 3.3 V and 4.8 V Low Drop-Out Regulators

**Figure 19** below shows the 3.3 V generated by the onboard LDO in the DRV8701 connected to DVDD pin. **Figure 20** shows the 4.8 V generated by the second onboard LDO in the DRV8701 connected to AVDD pin.

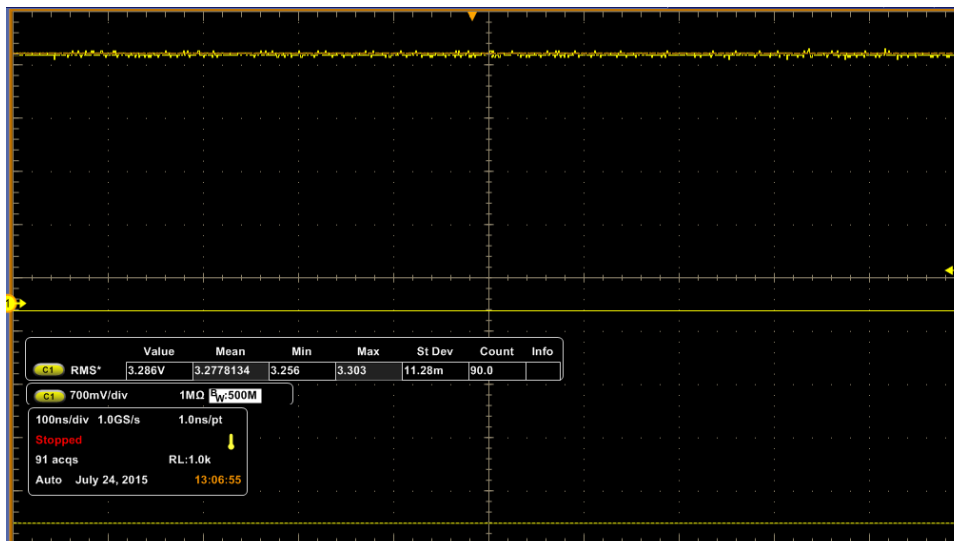


Figure 19. LDO Output Voltage of 3.3 V

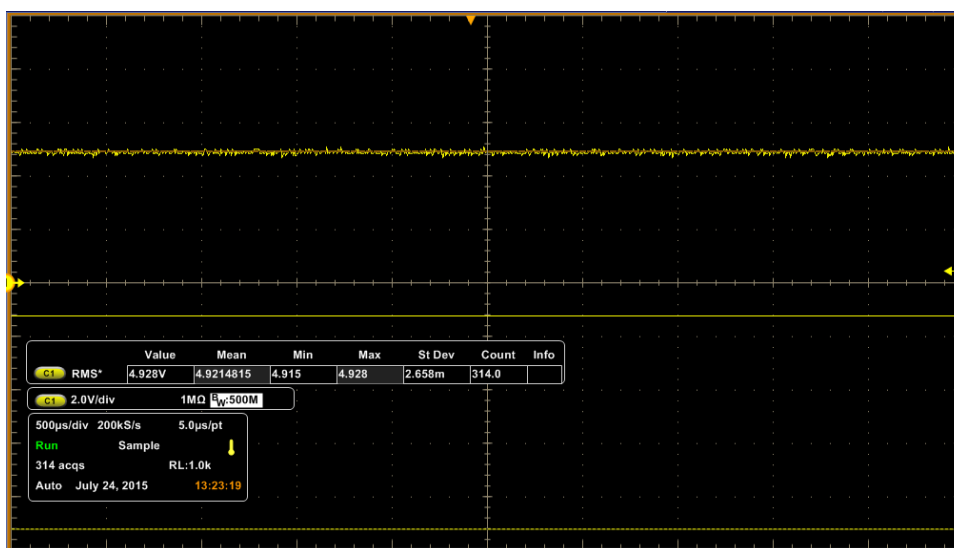


Figure 20. LDO Output Voltage of 4.8 V

## 8.2 PWM Speed Control Using $V_{\text{SPEED}}$ Reference

To Control the speed of the motor a PWM signal is generated by the MSP430G2553 based on the voltage level set by the SPEED potentiometer ( $V_{\text{SPEED}}$ ) connected between DVDD and Ground. The wiper pin of the potentiometer is sampled and compared to TIMER\_A of the MSP430. While the sampled  $V_{\text{SPEED}}$  is greater than the timer value the PWM output is high and while it is less than the timer the PWM output is low. The result is a varying duty cycle of the PWM signal based on the voltage measured at the speed potentiometer. The duty cycle of the PWM signal can be calculated using **Equation 7** below:

$$\%\_Duty\_Cycle = (V_{\text{SPEED}}/DVDD) * 100 \quad (7)$$

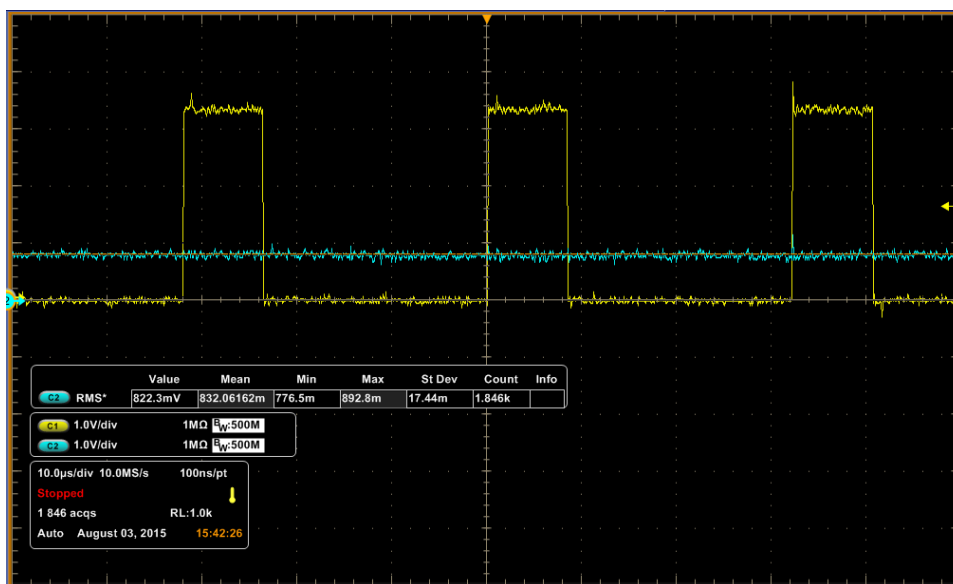


Figure 21. Resulting PWM Output with  $V_{\text{SPEED}} = 822 \text{ mV}$

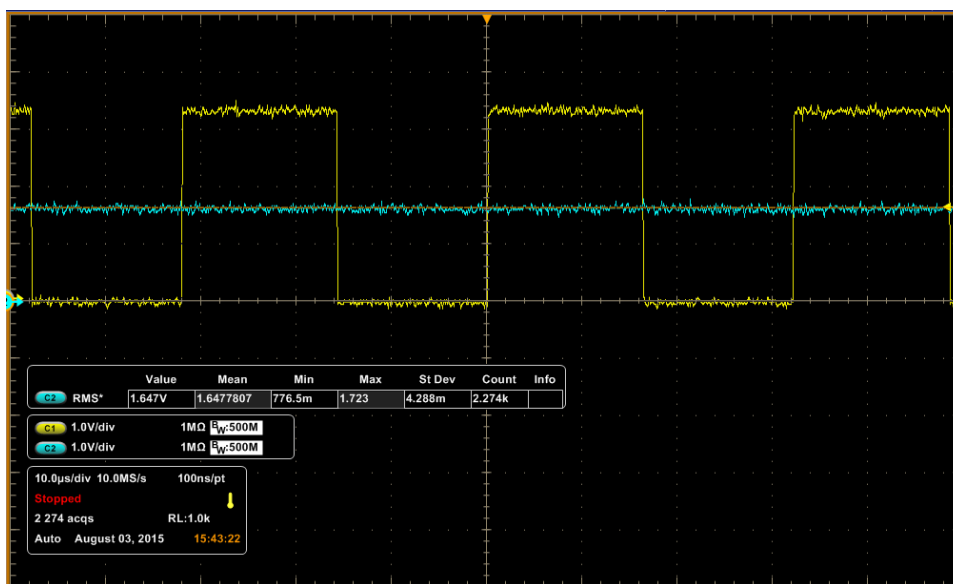


Figure 22. Resulting PWM Output with  $V_{\text{SPEED}} = 1.647 \text{ V}$

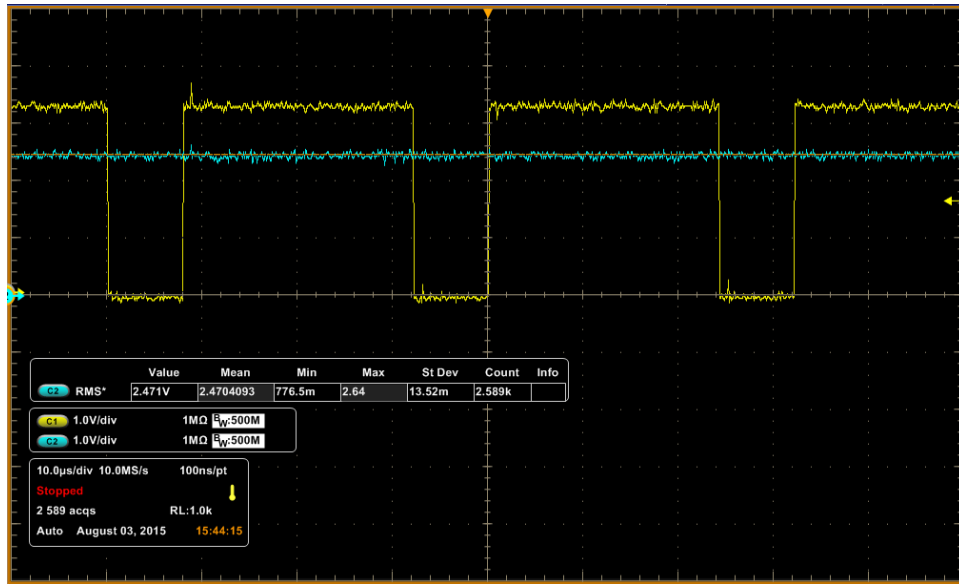


Figure 23. Resulting PWM Output with  $V_{\text{SPEED}} = 2.471 \text{ V}$

### 8.3 Inserted Dead Time

**Figure 24** shows the low side and high side gate signals from the same leg of the external H-Bridge. When the high side MOSFET is not active the low side MOSFET turns on to recirculate current through the motor and the other low side MOSFET which is also held on. In order to prevent shoot through on the same side of the bridge 380 ns of dead time is forcibly inserted by the DRV8701 as shown in **Figure 25**.

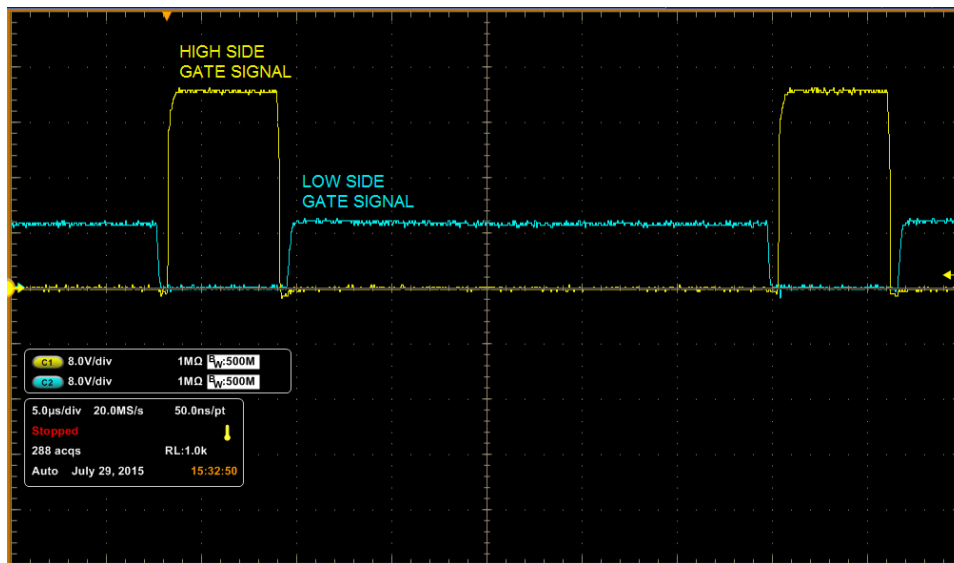


Figure 24. Complimentary High Side and Low Side Gate Signals

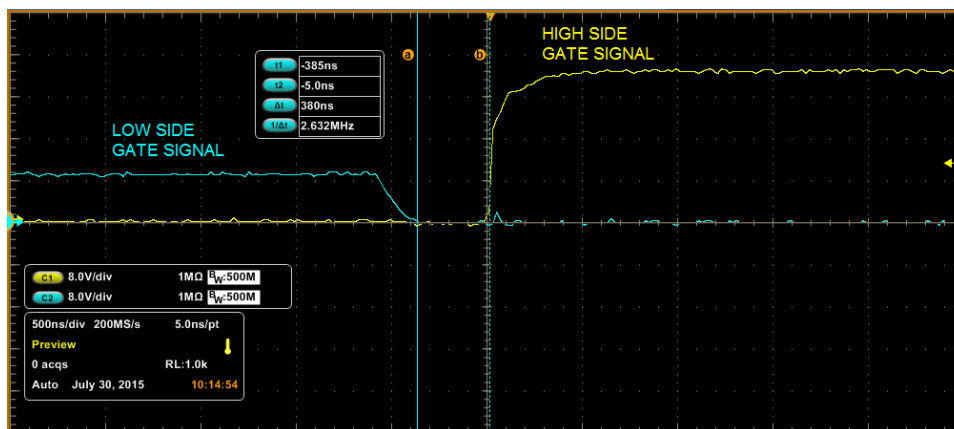


Figure 25. DRV8701 Inserted 380 ns Dead Time

## 8.4 Direction Pin De-bounce

One of the added benefits of using the MSP430G2553 as a control interface is the ability to debounce the phase switch input by periodically polling the state of the switch as opposed to constantly sampling. Instead of a short period of voltage chopping the state of the phase pin can be changed smoothly and quickly, as illustrated in **Figure 26** below.



Figure 26. Phase State Change of MSP430G2553

## 8.5 Current Chopping Using $V_{REF}$ Reference

The DRV8701 uses  $V_{REF}$  to set the value at which current chopping will occur by monitoring the voltage drop across  $R_{SENSE}$  and amplifying the voltage by a scaling factor  $A_V$ . The value of current at which chopping will begin can be calculated using **Equation 8** below:

$$I_{CHOP} = (V_{REF} - V_{OFFSET}) / (R_{SENSE} * A_V) \quad (8)$$

An example of a typical startup current spike is shown in Figure 9. An example of current chopping based on a  $V_{REF}$  value of 1.07 V and the same startup condition is shown in **Figure 28**.

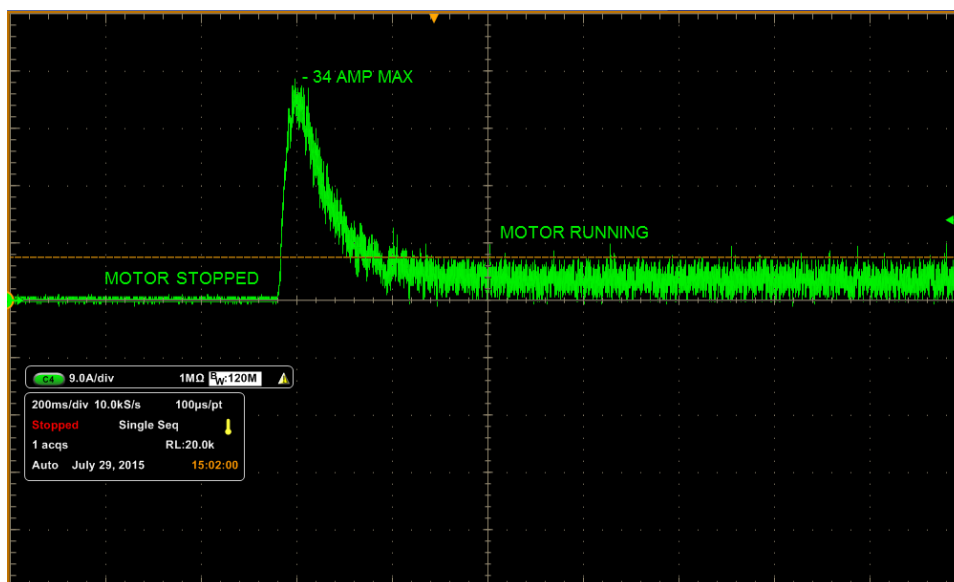


Figure 27. Startup Motor Current Spike

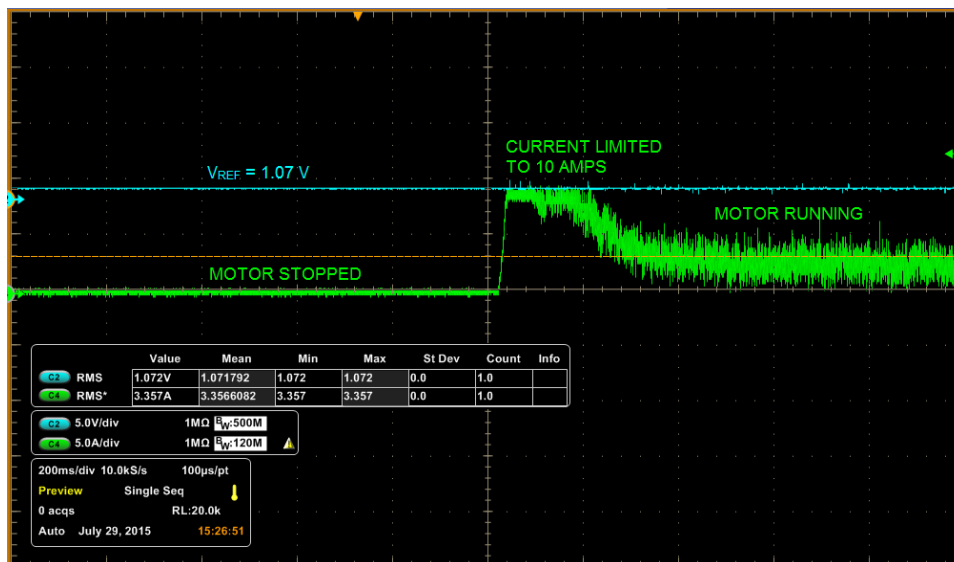


Figure 28. Startup Motor Current With Current Chopping

## 8.6 Sense Amplifier Output as Motor Current Increases

The output of the sense amplifier measuring the voltage across  $R_{SENSE}$  can be viewed on the SO pin of the DRV8701.  $V_{SO}$  increases based as on the amount of time the motor is being driven for as shown in **Figure 29** below. When the output of the sense amplifier is measured to be equal to  $V_{REF}$  the DRV8701 will begin to limit the current running through the bridge until  $V_{SO}$  has dropped below  $V_{REF}$ . An example of  $V_{SO}$  increasing as the current through  $R_{SENSE}$  increases is shown in **Figure 30** below.

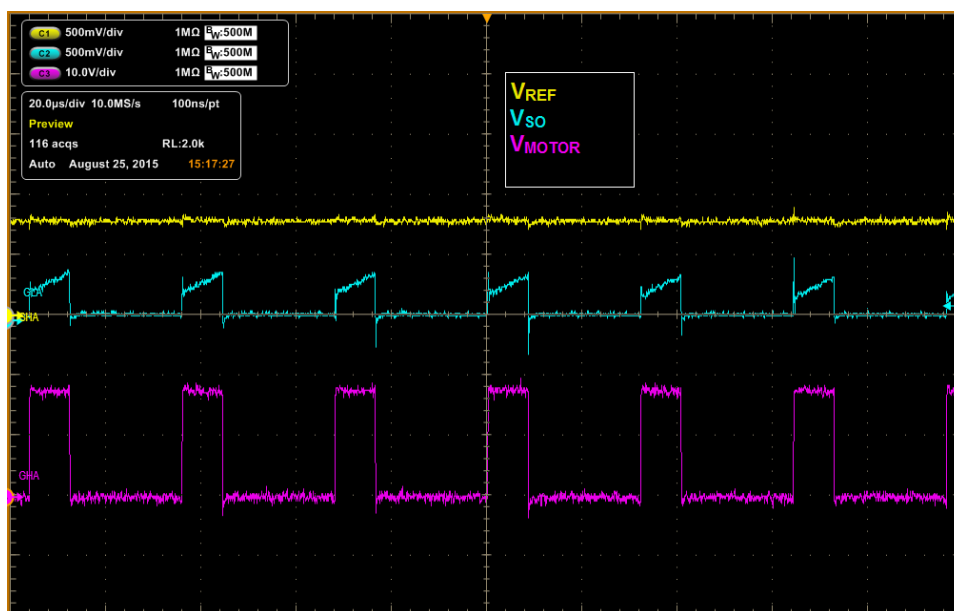


Figure 29.  $V_{SO}$  Increasing With PWM High Time


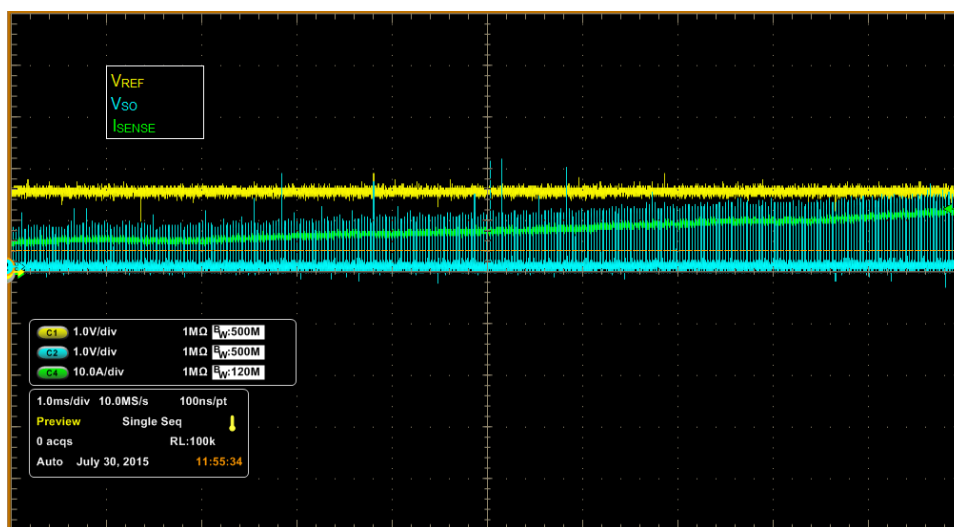



Figure 30.  $V_{SO}$  Increasing With  $I_{SENSE}$  Until  $V_{REF}$  Is Reached

## 8.7 Load Testing Thermal Data

Figures 31 through Figure 37 illustrate the maximum thermal point on the PCB as the current delivered to the motor was increased. The thermal images were captured in 5 Amp intervals, with the initial current delivered to the motor at 2.85 Amps and the final current delivered to the motor at 27.47 Amps. For each current interval the driver was operated for 10 seconds then shut off and allowed to cool down to room temperature (Approximately 20° C) before the next current level was tested.

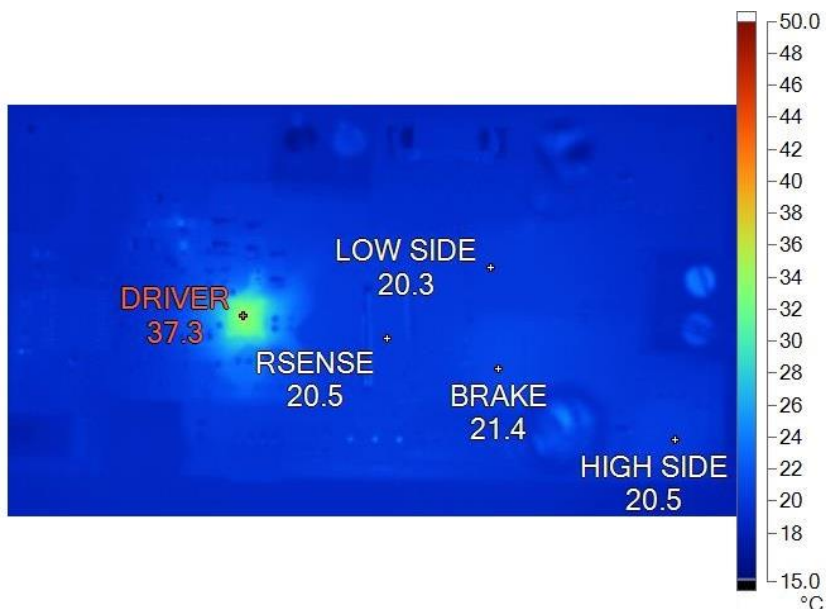

**Figure 31. 2.85 Amps Continuous Current, 5.18 m-Nm Load**

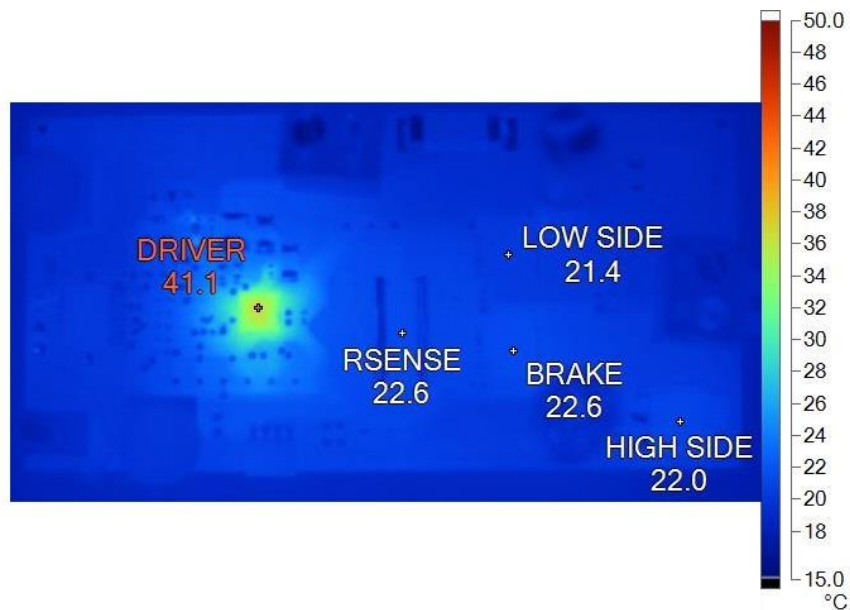

**Figure 32. 5.14 Amps Continuous Current, 23.24 m-Nm Load**



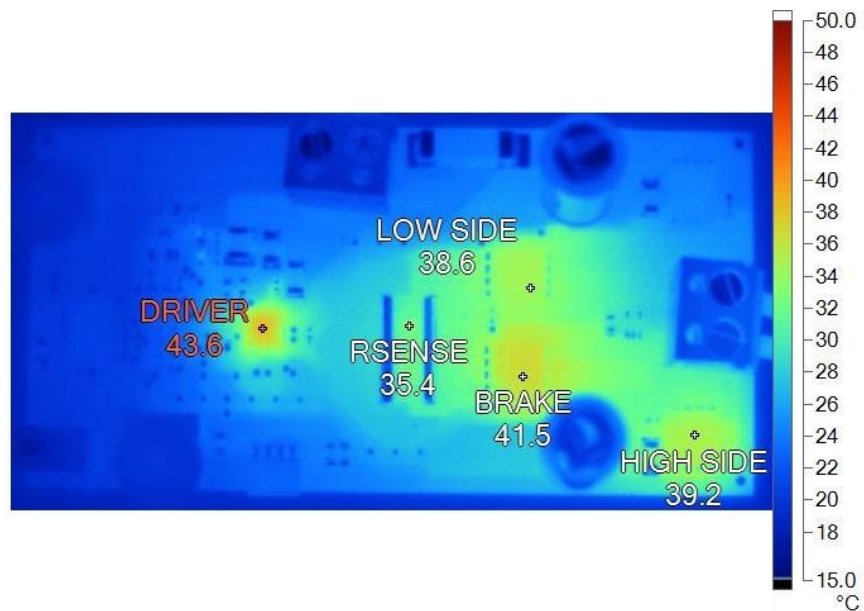


Figure 33. 10.17 Amps Continuous Current, 62.86 m-Nm Load

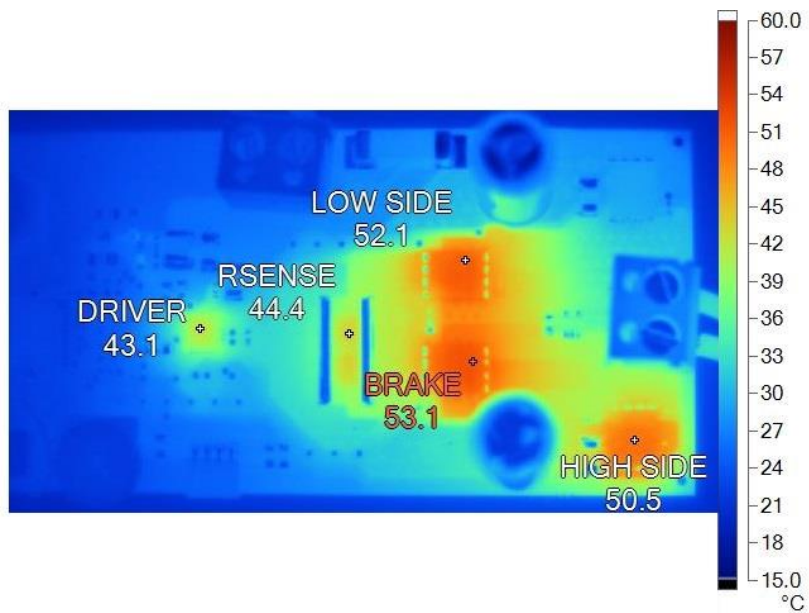


Figure 34. 15.46 Amps Continuous Current, 98.04 m-Nm Load

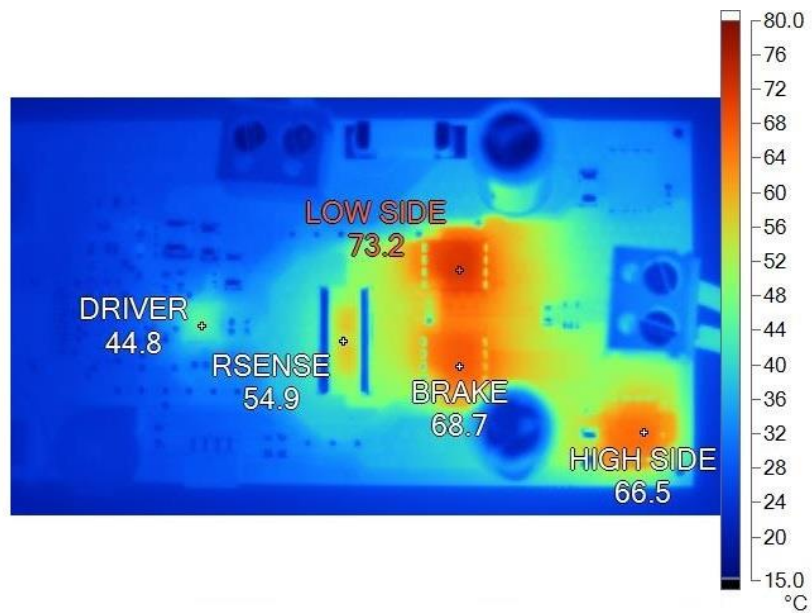


Figure 35. 20.49 Amps Continuous Current, 130.64 m-Nm Load

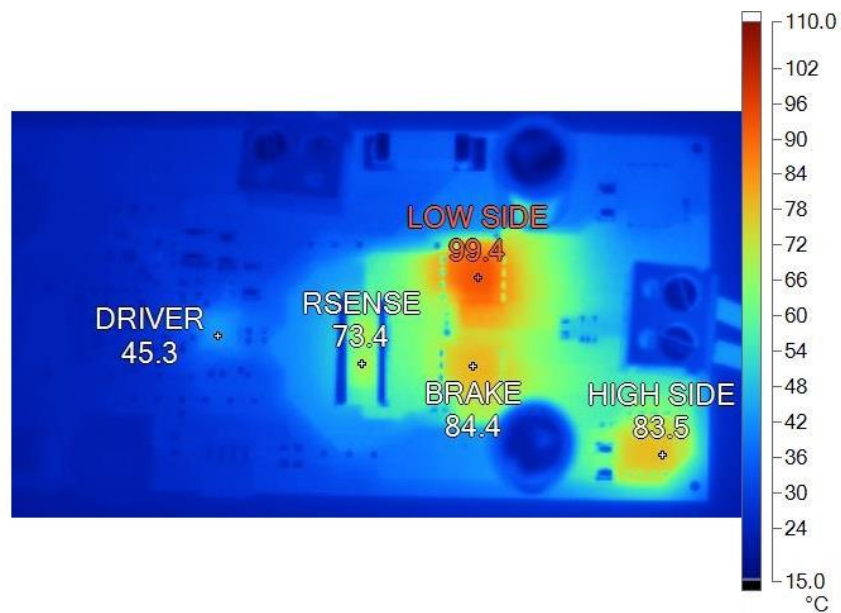


Figure 36. 25.47 Amps Continuous Current, 162.90 m-Nm Load

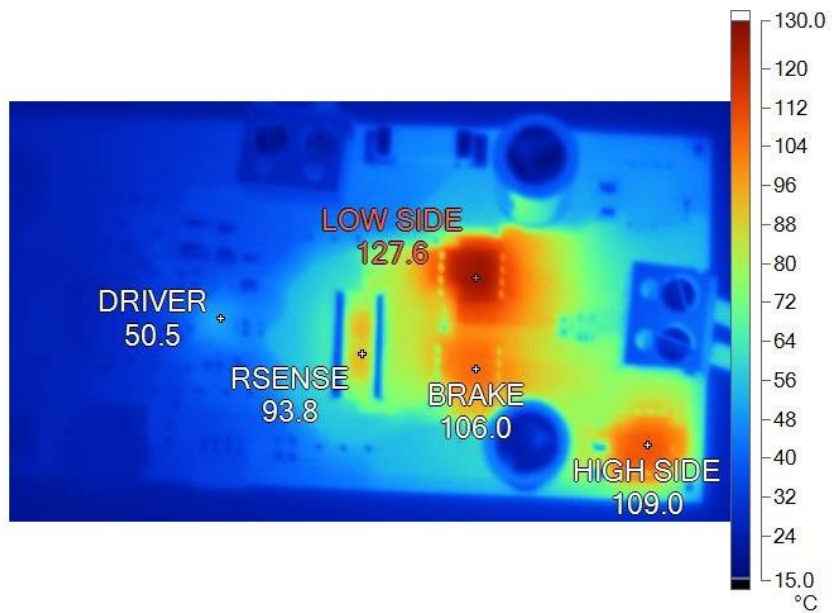



Figure 37. 27.47 Amps Continuous Current, 180.62 m-Nm Load

## 8.8 Temperature vs. Power Data

The RMS power delivered to the motor versus the maximum PCB temperature in degrees Celsius is shown in **Figure 38** below. The current supplied to the motor was measured using a current probe clamped to one of the cables connecting the motor to the terminal blocks of the PCB. An oscilloscope probe was then placed across the terminals of the motor and the voltage supplied to the motor was measured. Both current and voltage were measured and the RMS values were calculated for the 10 second testing interval for each torque load. To calculate the RMS power for each testing interval the equation below was used:

$$P_{RMS} = I_{RMS} * V_{RMS} \tag{9}$$

The calculated RMS power in Watts versus the maximum PCB temperature in degrees Celsius for each 10 second test interval is graphed in **Figure 38** below.

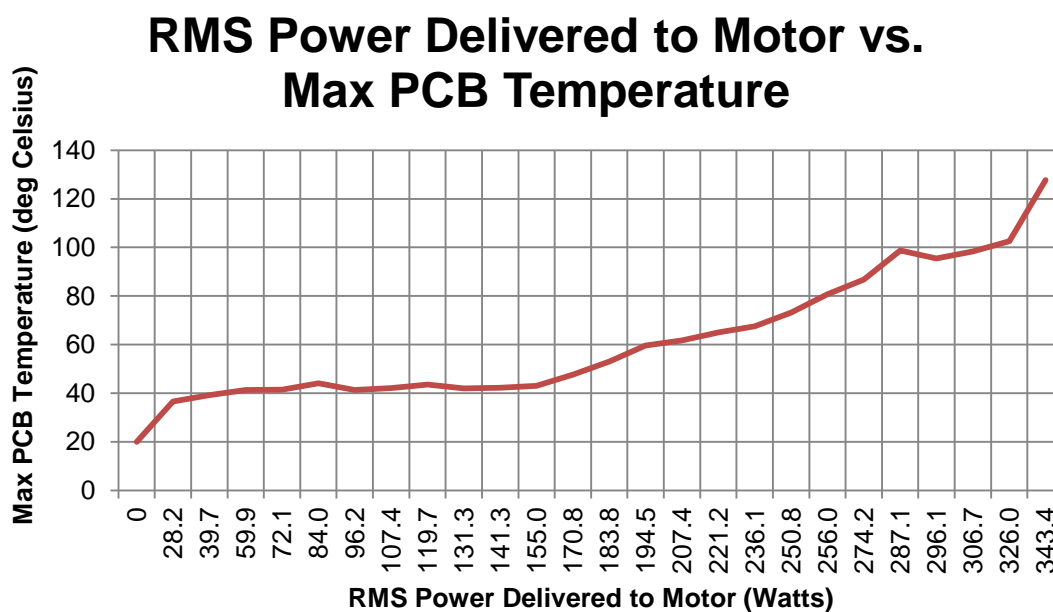

**Figure 38. RMS Powered Delivered to Motor vs. Max PCB Temp**

The device testing stopped at 127.6° C after the last 10 second interval because the recommended maximum temperature for operation is 125.0° C so the device was raised above this threshold for a very short period of time at the end of the last load test. If the device were to be operated at a higher power range it could safely deliver a larger power output if the amount of time it was operated for were significantly decreased.

## 8.9 All Collected Load Test Data

All of the collected test data is shown in **Table 2** below. All of the data below was collected by connecting the reference design PCB to a Brushed DC Motor that spun a DC Brake and torque sensor in line with the motor shaft. The motor speed was kept constant while the torque resisting the motor turning was increased to draw more current from the power supply and through the board. For each test interval the PCB was allowed to cool down to room temperature before the load test began. This allowed for all of the thermal data to be exemplary of how the board would perform delivering the rated power amount to the motor from a startup state.

RMS Motor Voltage (Volts)	RMS Motor Current (Amps)	DC INPUT POWER (Watts)	MAX PCB TEMP (°C)	MOTOR SHAFT TORQUE (Nm)
0.00	0.00	0	0	0.000
9.90	2.85	28.25	36.6	0.005
9.89	4.01	39.66	39.2	0.020
11.66	5.14	59.93	41.3	0.023
11.71	6.16	72.13	41.5	0.031
11.67	7.20	83.98	44.1	0.038
11.80	8.15	96.21	41.3	0.046
11.79	9.11	107.43	42.1	0.054
11.77	10.17	119.70	43.6	0.063
11.83	11.10	131.31	42	0.070
11.72	12.06	141.34	42.3	0.075
11.94	12.98	154.98	43.1	0.080
12.00	14.23	170.76	47.7	0.090
11.89	15.46	183.82	53.1	0.098
11.94	16.29	194.50	59.7	0.105
11.86	17.49	207.43	61.8	0.112
11.95	18.51	221.19	65.1	0.117
12.06	19.58	236.13	67.6	0.126
12.24	20.49	250.80	73.2	0.131
11.94	21.44	255.99	80.7	0.138
11.98	22.89	274.22	86.8	0.147
12.17	23.59	287.09	98.7	0.151
12.11	24.45	296.09	95.5	0.161
12.04	25.47	306.66	98.4	0.163
12.33	26.44	326.01	102.6	0.169
12.50	27.47	343.38	127.7	0.181


**Table 2. Collected Load Test Data Between 2.85 – 27.47 A**

The voltage and current delivered to the motor are represented as RMS values because the H-Bridge is supplying PWM signals to the motor, meaning a peak value for either voltage or current would only show how the supply is operating during a driving period of each PWM frame. A more realistic figure for power delivered to the motor is the RMS value which is reported showing the average power delivered over the 10 second test interval.


## 9 Design Files

### 9.1 Schematics


#### 9.1.1 MSP430G2553

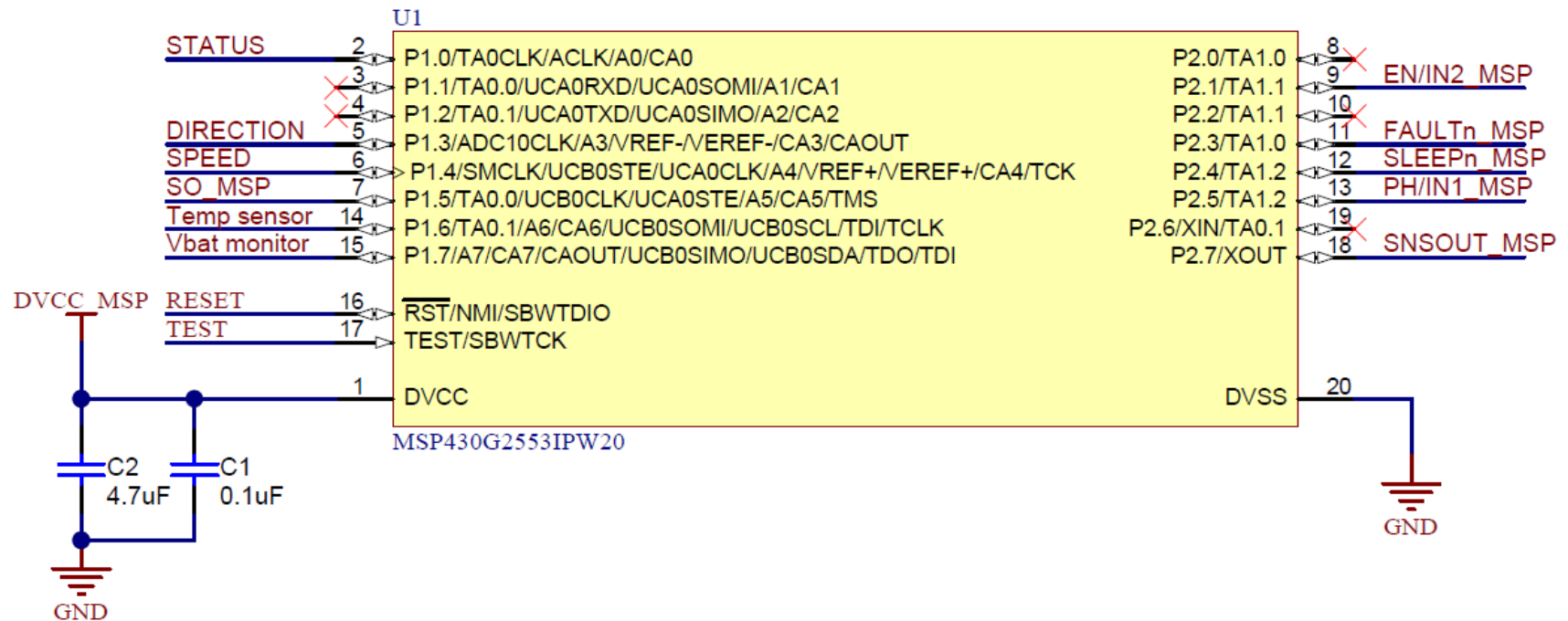

## 9.1.2 DRV8701

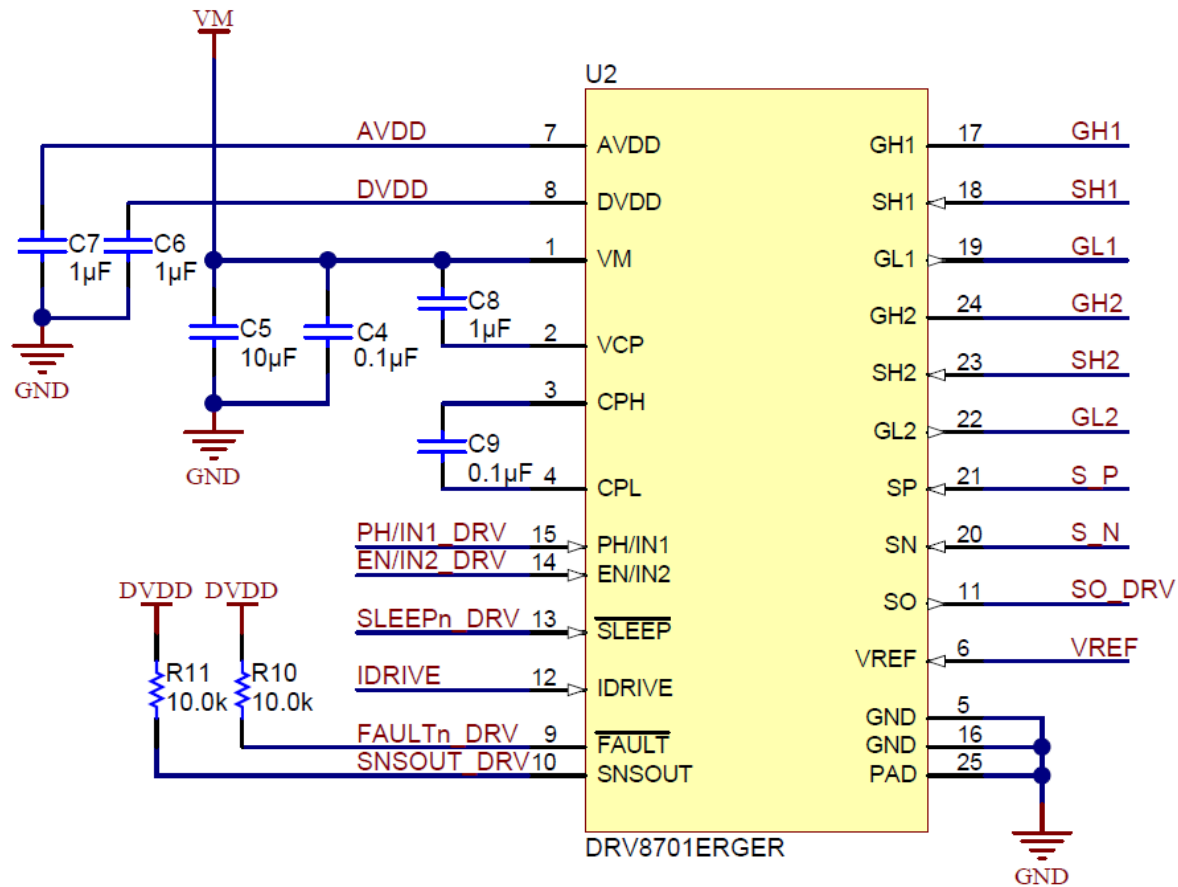


### 9.1.3 H-Bridge

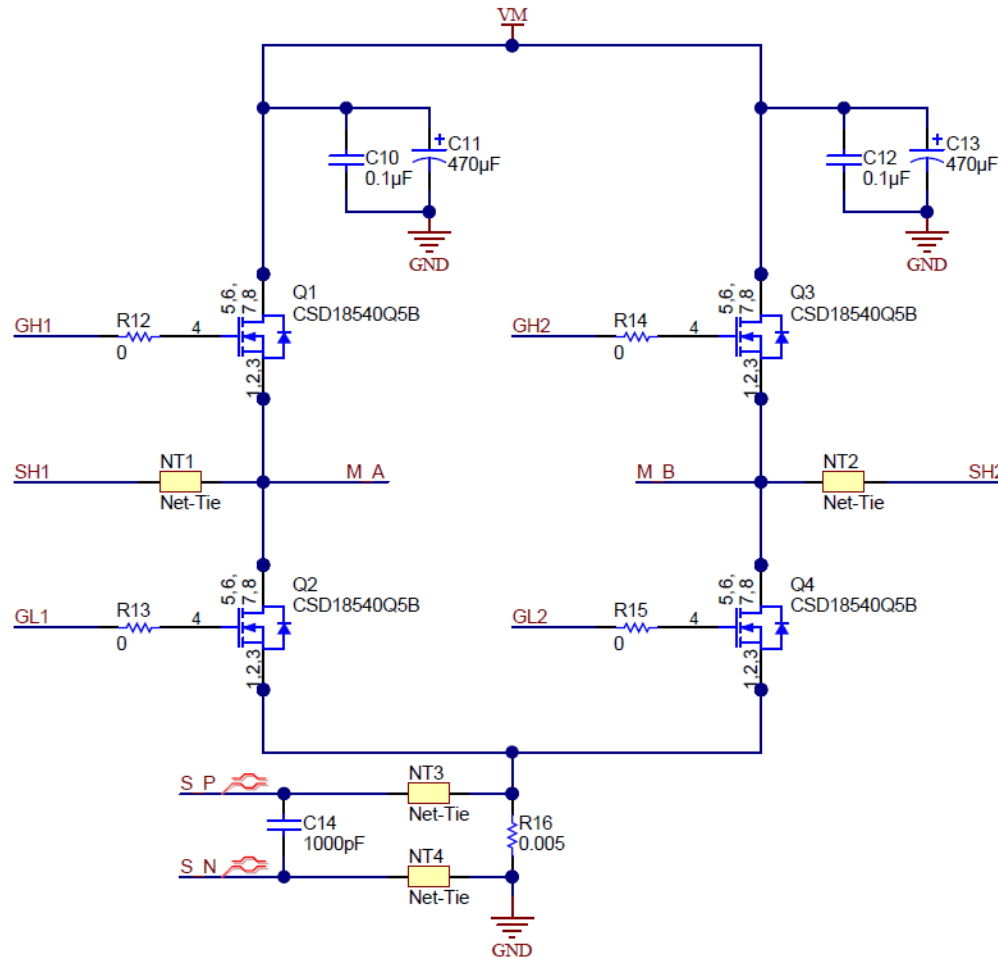





## 9.1.4 Protection

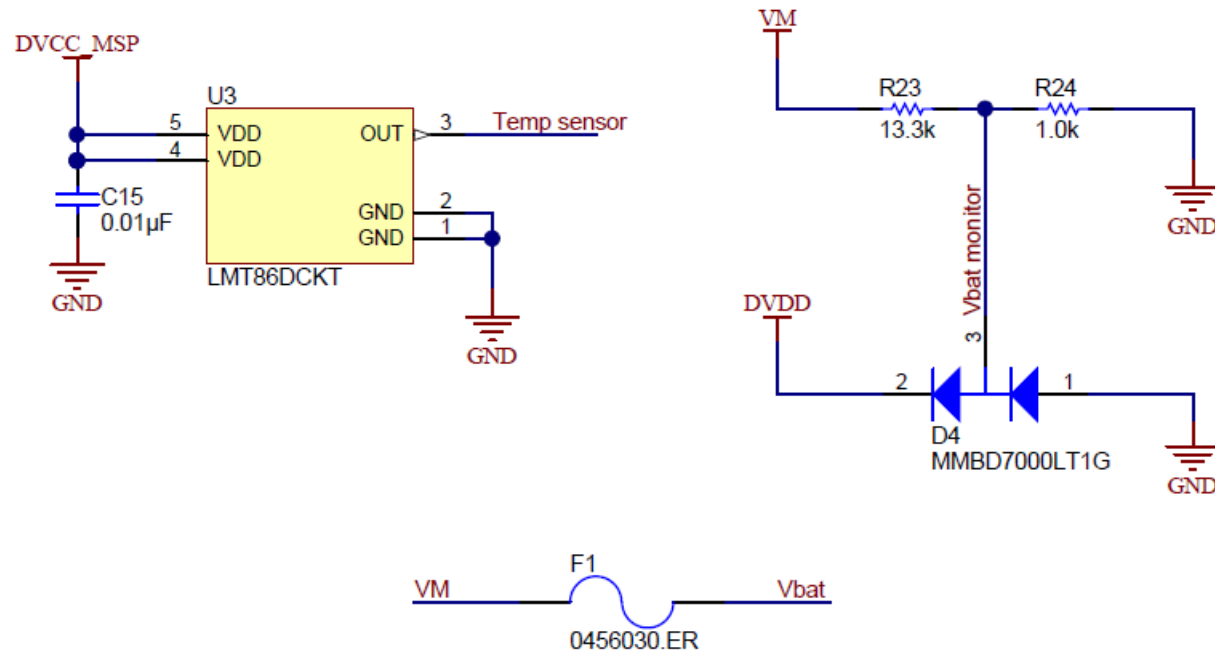


### 9.1.5 Speed + Direction

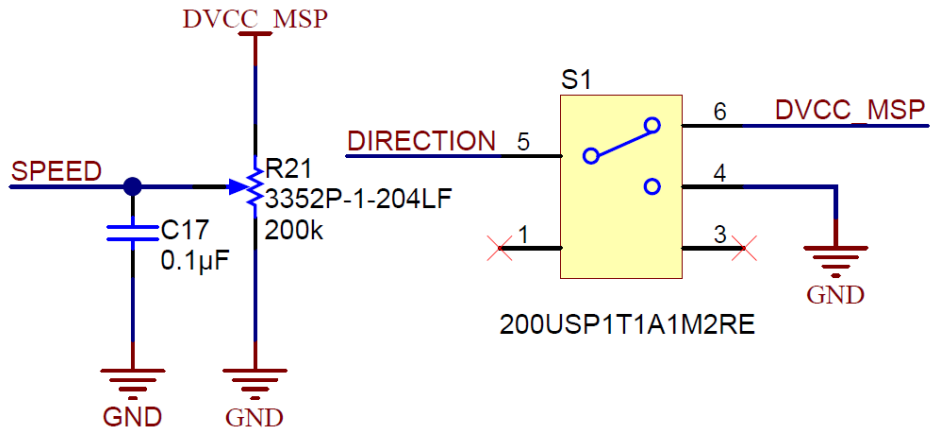


### 9.1.6 Sleep RC Time

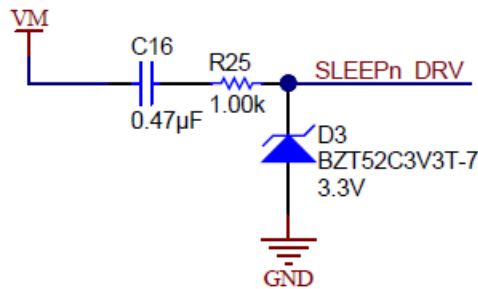


### 9.1.7 Fault + Status LEDs

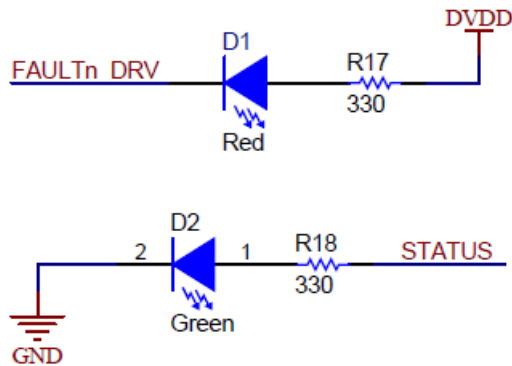

### 9.1.8 SPI Header

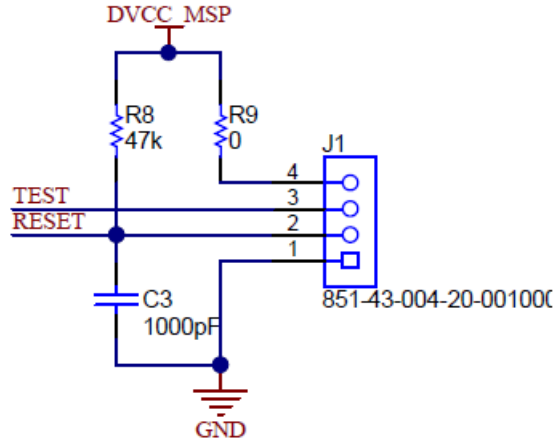

### 9.1.9 MSP430 – DRV8701 Connections

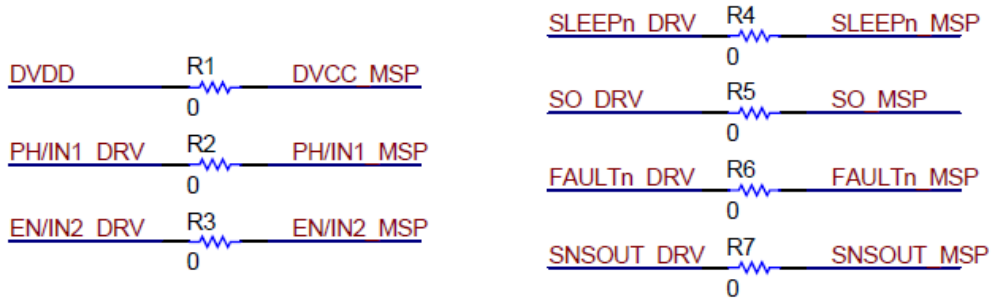


### 9.1.10 Terminal Block Connections




### 9.1.11 I Drive



### 9.1.12 V<sub>REF</sub> Pot

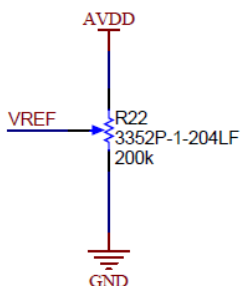

### 9.1.13 Test Points

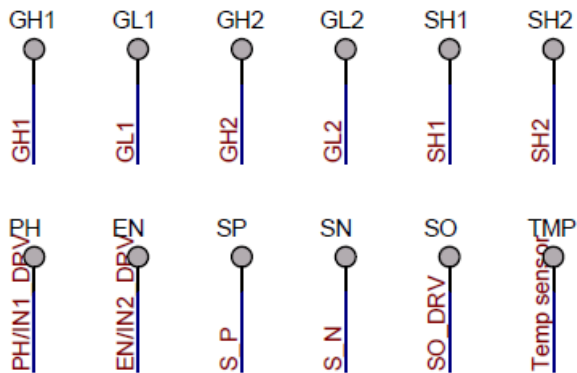

## 9.2 Bill of Materials



# Bill of Materials

TIDA-00620

Item	Qty	Reference	Value	Part Description	Manufacturer	Manufacturer Part Number	PCB Footprint
1	1	!PCB		Printed Circuit Board	Any	TIDA-00620	
2	1	C1	0.1uF	CAP, CERM, 0.1uF, 10V, +/- 10%, X7R, 0603	Kemet	C0603C104K8RACTU	0603
3	1	C2	4.7uF	CAP, CERM, 4.7uF, 10V, +/- 20%, X7R, 0805	TDK	C2012X7R1A475M	0805
4	1	C3	1000pF	CAP, CERM, 1000pF, 16V, +/-10%, X7R, 0603	MuRata	GRM188R71C102KA01D	0603
5	3	C4, C10, C12	0.1uF	CAP, CERM, 0.1 uF, 50 V, +/- 10%, X7R, 1206	MuRata	GRM319R71H104KA01D	1206
6	1	C5	10uF	CAP, CERM, 10 uF, 50 V, +/- 10%, X7R, 1210	MuRata	GRM32ER71H106KA12L	1210
7	2	C6, C7	1uF	CAP, CERM, 1 uF, 6.3 V, +/- 10%, X5R, 0603	MuRata	GRM188R60J105KA01D	0603
8	1	C8	1uF	CAP, CERM, 1 uF, 16 V, +/- 10%, X7R, 1206	MuRata	GRM319R71C105KAA3D	1206
9	1	C9	0.1uF	CAP, CERM, 0.1 uF, 16 V, +/- 10%, X7R, 0402	MuRata	GRM155R71C104KA88D	0402
10	2	C11, C13	470uF	CAP, AL, 470 uF, 35 V, +/- 20%, 0.03 ohm, TH	Panasonic	EEU-FR1V471LB	RCAP, 8x20mm

11	1	C14	1000pF	CAP, CERM, 1000pF, 16V, +/-10%, X7R, 0402	MuRata	GRM155R71C102KA01D	0402
12	1	C15	0.01uF	CAP, CERM, 0.01 $\mu$ F, 6.3 V, +/- 10%, X7R, 0603	MuRata	GRM188R70J103KA01D	0603
13	1	C16	0.47uF	CAP, CERM, 0.47 $\mu$ F, 10 V, +/- 10%, X5R, 0402	MuRata	GRM155R61A474KE15D	0402
14	1	C17	0.1uF	CAP, CERM, 0.1 $\mu$ F, 16 V, +/- 10%, X7R, 0402	MuRata	GCM155R71C104KA55D	0402
15	1	D1	Red	LED, Red, SMD	Lite-On	LTST-C170KRKT	LED_0805
16	1	D2	Green	LED, Green, SMD	Lite-On	LTST-C171GKT	LED_0805
17	1	D3	3.3V	Diode, Zener, 3.3 V, 300 mW, SOD-523	Diodes Inc.	BZT52C3V3T-7	SOD-523
18	1	D4	100V	Diode, Switching, 100 V, 0.2 A, SOT-23	ON Semiconductor	MMBD7000LT1G	SOT-23
19	1	F1		Fuse, 30 A, 72 V, SMD	Littelfuse	0456030.ER	10.1x3.12mm
20	3	FID1, FID2, FID3		Fiducial mark. There is nothing to buy or mount.	N/A	N/A	Fiducial
21	1	J1		SOCKET .050" GRID SIP 4 POS R/A, TH	Mill-Max	851-43-004-20-001000	R/A 4x1 receptacle
22	2	J2, J3		Terminal Block, 5 mm, 2x1, Tin, TH	Würth Elektronik	691 101 710 002	Terminal Block, 5 mm, 2x1, TH
23	4	Q1, Q2, Q3, Q4	60V	MOSFET, N-CH, 60 V, 28 A, SON 5x6mm	Texas Instruments	CSD18540Q5B	SON 5x6mm
24	11	R1, R2, R3, R4, R5, R6, R7, R12, R13, R14, R15	0	RES, 0, 5%, 0.063 W, 0402	Vishay-Dale	CRCW04020000Z0ED	0402
25	1	R8	47k	RES, 47k ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW060347K0JNEA	0603
26	1	R9	0	RES, 0 ohm, 5%, 0.1W, 0603	Vishay-Dale	CRCW06030000Z0EA	0603

27	2	R10, R11	10.0k	RES, 10.0 k, 1%, 0.1 W, 0402	Panasonic	ERJ-2RKF1002X	0402
28	1	R16	0.005	RES, 0.005, 1%, 6 W, 4320_WIDE	Susumu Co Ltd	KRL11050-C-R005-F-T1	4320_WIDE
29	2	R17, R18	330	RES, 330, 1%, 0.1 W, 0603	Yageo America	RC0603FR-07330RL	0603
30	2	R21, R22	200k	Trimmer, 200 K, 0.5 W, TH	Bourns	3352P-1-204LF	Thumbwheel Trimmer
31	1	R23	13.3k	RES, 13.3 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW040213K3FKED	0402
32	1	R24	1.0k	RES, 1.0 k, 5%, 0.063 W, 0402	Vishay-Dale	CRCW04021K00JNED	0402
33	1	R25	1.00k	RES, 1.00 k, 1%, 0.063 W, 0402	Vishay-Dale	CRCW04021K00FKED	0402
34	1	S1		Switch, SPDT, On-On, 2 Pos, TH	E-Switch	200USP1T1A1M2RE	Switch, 7x4.5mm
35	1	U1		16 MHz Mixed Signal Microcontroller with 16 KB Flash, 512 B SRAM and 24 GPIOs, -40 to 85 degC, 20-pin SOP (PW), Green (RoHS & no Sb/Br)	Texas Instruments	MSP430G2553IPW20	PW0020A
36	1	U2		H-Bridge Gate Driver, RGE0024F	Texas Instruments	DRV8701ERGER	RGE0024F
37	1	U3		Analog Temperature Sensors with Class-AB Output, DCK0005A	Texas Instruments	LMT86DCKT	DCK0005A
38	0	R19	68k	RES, 68 k, 5%, 0.063 W, 0402	Vishay-Dale	CRCW040268K0JNED	0402
39	0	R20	0	RES, 0, 5%, 0.063 W, 0402	Vishay-Dale	CRCW04020000Z0ED	0402

## 9.3 PCB Layout Recommendations

### 9.3.1 Layout Prints

To download the Layout Prints for each board, see the design files at <http://www.ti.com/tool/DESIGNNUMBER>

TOP SILKSCREEN

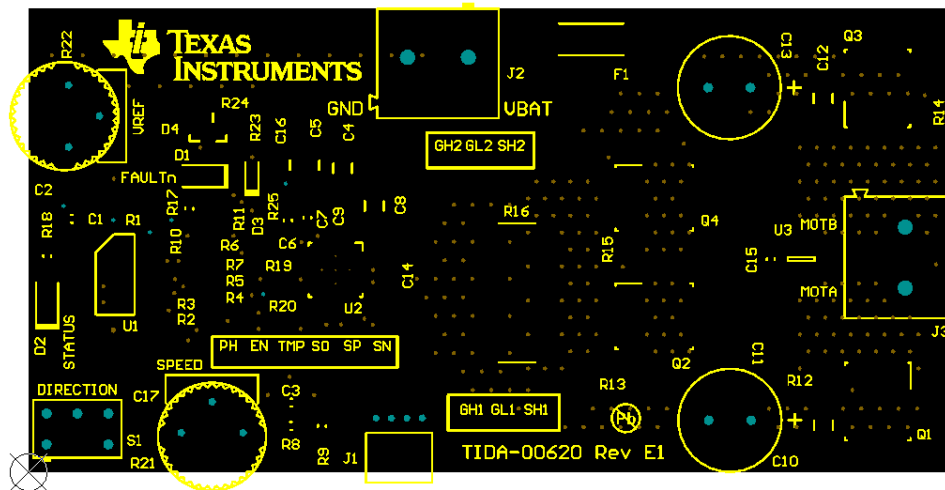


Figure 39. Top Silkscreen

TOP SOLDER MASK

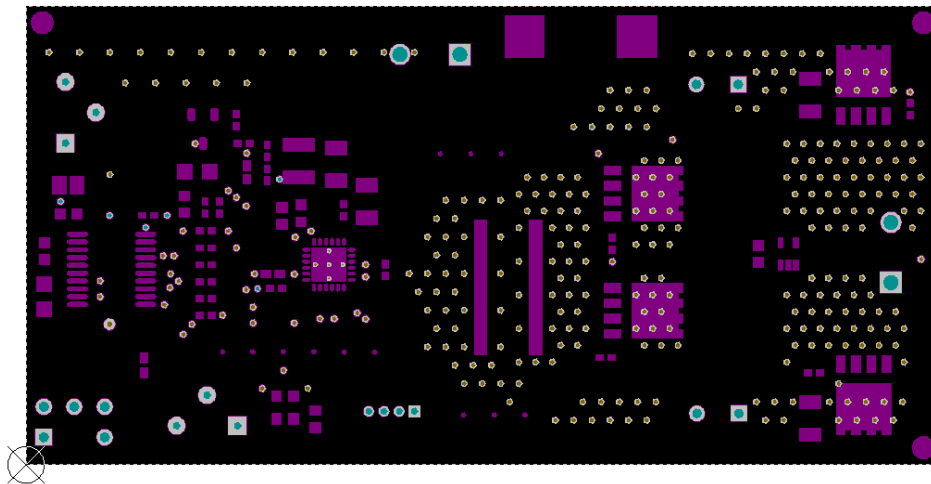


Figure 40. Top Solder Mask



TOP LAYER

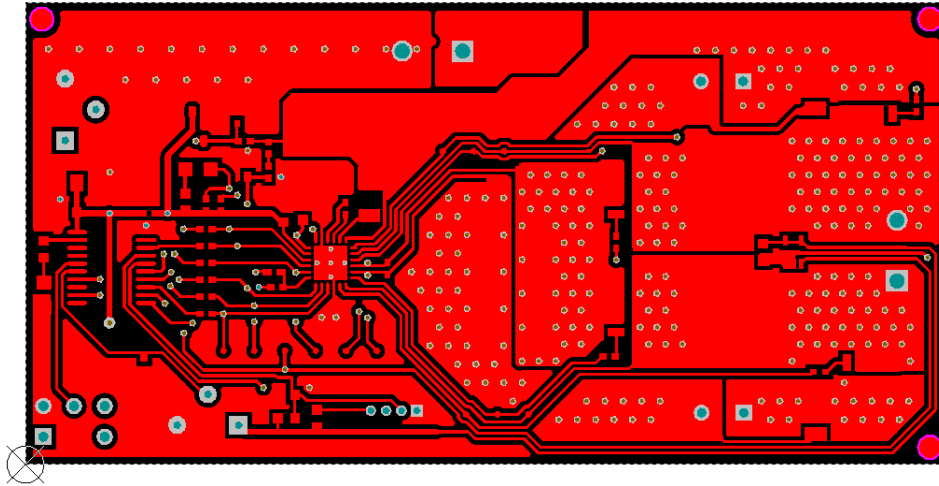


Figure 41. Top Layer

BOTTOM LAYER

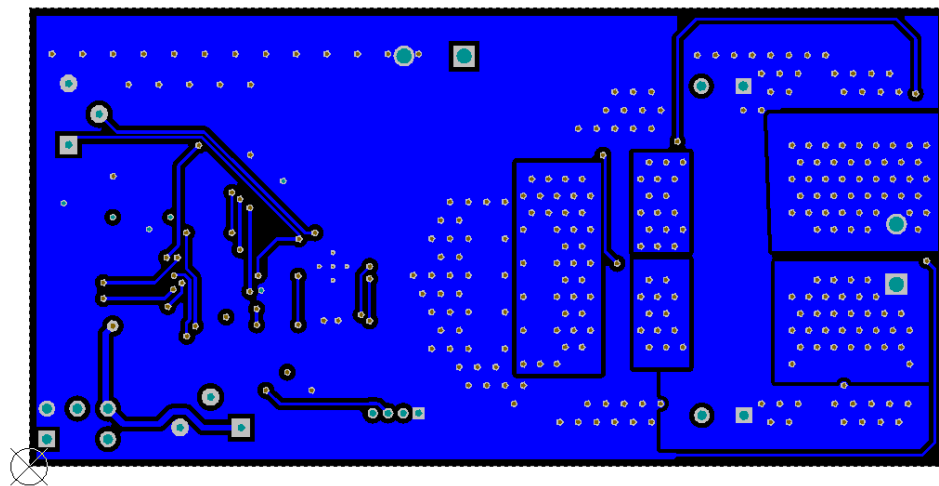


Figure 42. Bottom Layer

BOTTOM SOLDER MASK

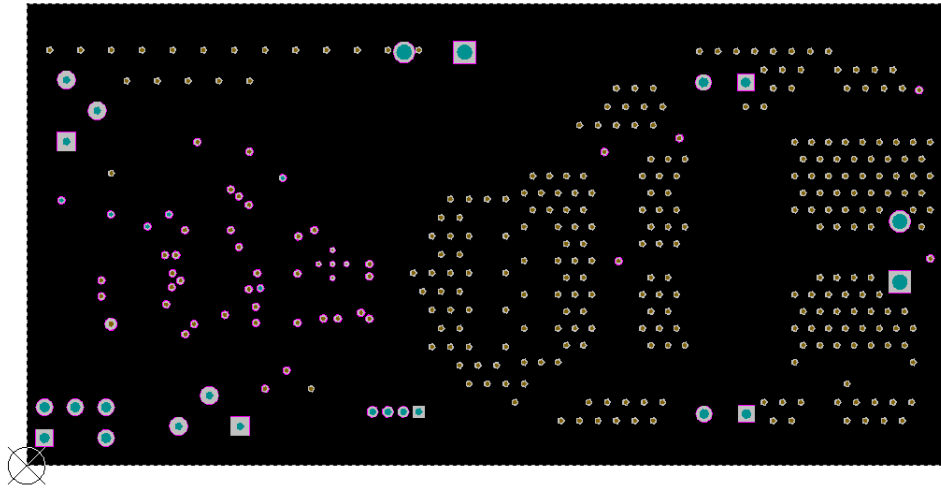


Figure 43. Bottom Solder Mask

BOTTOM SILKSCREEN

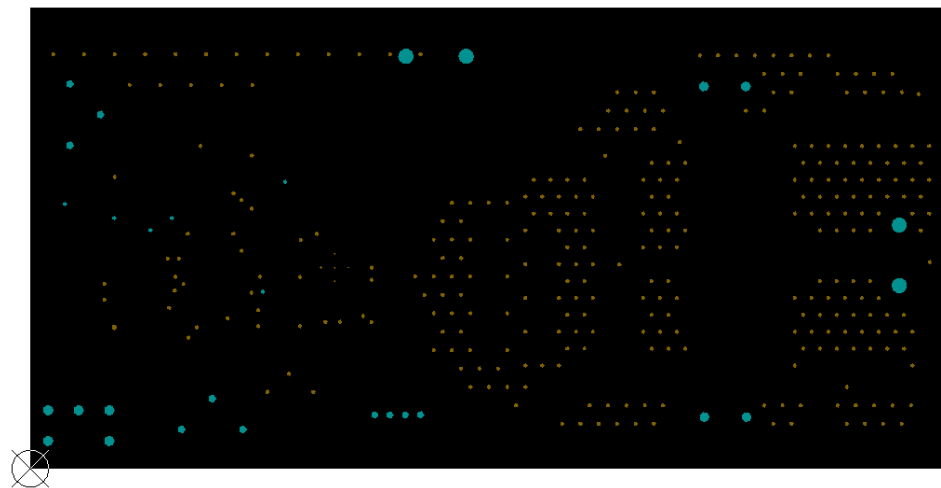


Figure 44. Bottom Silkscreen

MECHANICAL DIMENSIONS

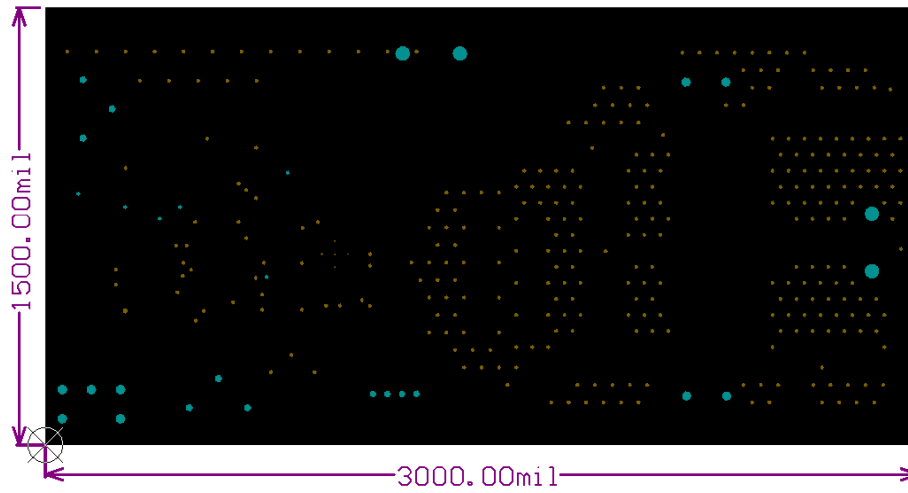


Figure 45. Mechanical Dimensions

## 9.4 Altium Project

To download the Altium project files for each board, see the design files at

<http://www.ti.com/tool/DESIGNNUMBER>

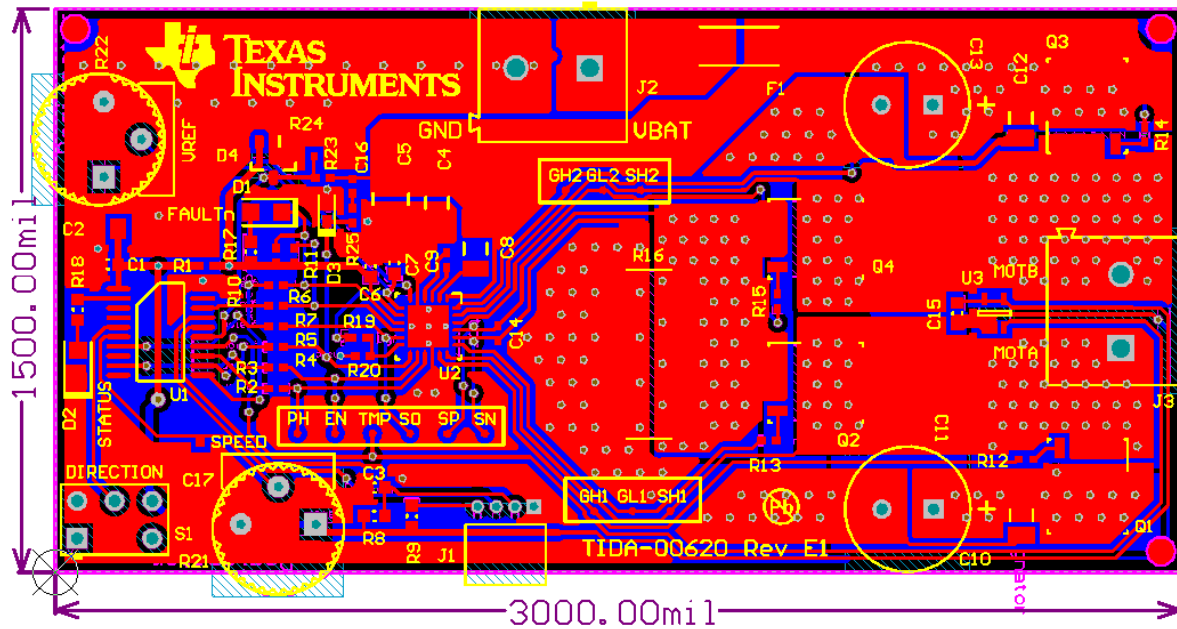


Figure 46. All Layers

## 9.5 Layout Guidelines

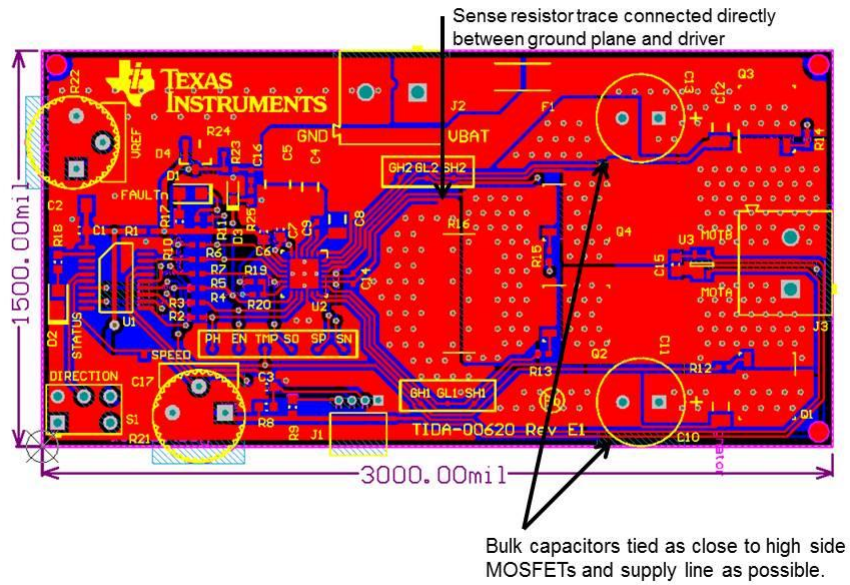


Figure 47. Top Design Guide

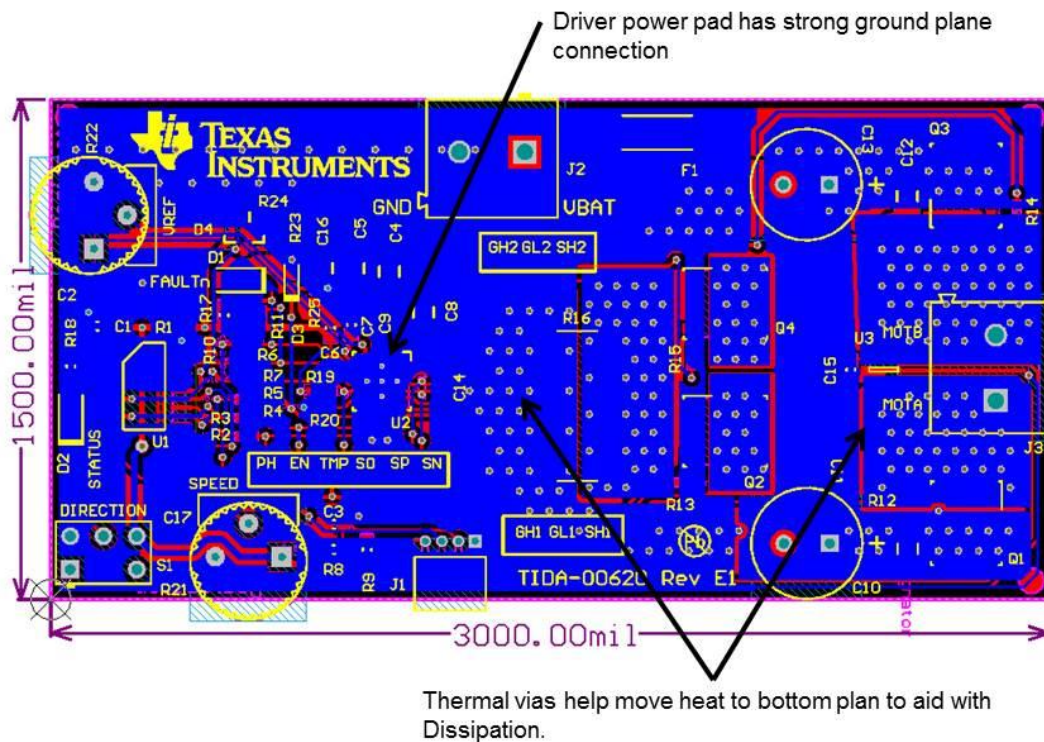


Figure 48. Bottom Design Guide



## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.