

# HIGH VOLTAGE SEMINAR

SUTEJ REDDY CHALLA  
HIGH VOLTAGE CONTROLLERS

DRIVING SiC MOSFETS IN AUXILIARY  
POWER SUPPLIES



# Content


- **Block diagram of end equipment with high-voltage bias power**
- Flyback topology candidate comparison
- Design considerations of SiC flyback control circuitry
- Summary

# SiC material properties + power system benefits

## Intrinsic material properties

Property	Definition	Si	GaN	SiC – 4H
$E_G$ (eV)	Bandgap energy	1.12	3.4	3.2
$E_{BR}$ (MV/cm)	Critical field breakdown voltage	0.3	3.3	3.5
$v_s$ ( $\times 10^7$ cm/s)	Saturation velocity	1.0	2.5	2.2
$\mu$ ( $\text{cm}^2/\text{V}\cdot\text{s}$ )	Electron mobility	1400	990-2000	900
$\lambda$ (W/cm.K)	Thermal conductivity	1.3	1.5	4.5


## Properties leading to system benefits

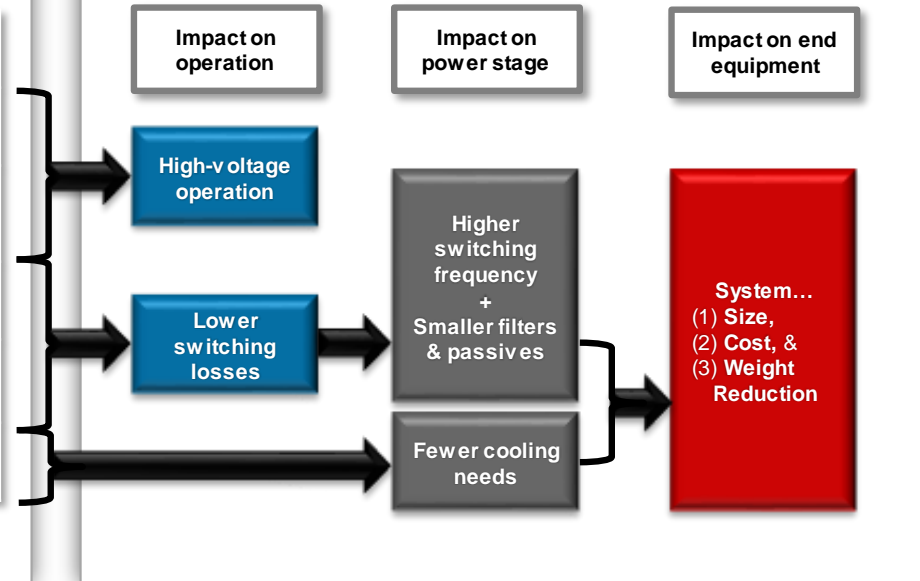

# Aux power supplies in central PV inverter
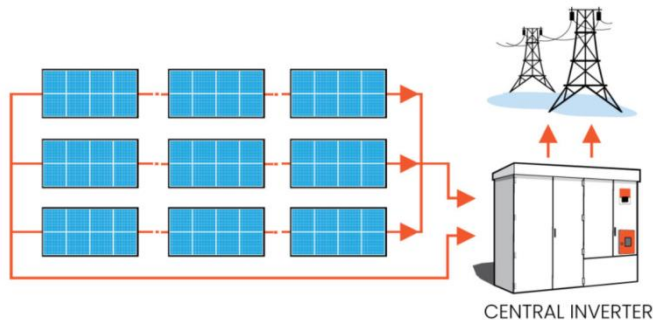
## Where:


- Typical power levels of 20 W to 150 W
- Operating input voltage range: 1000 V to 1500 V DC



## Why SiC?

- Higher VDS rating (1700 V SiC)
- High efficiency

## SiC Flyback Converter

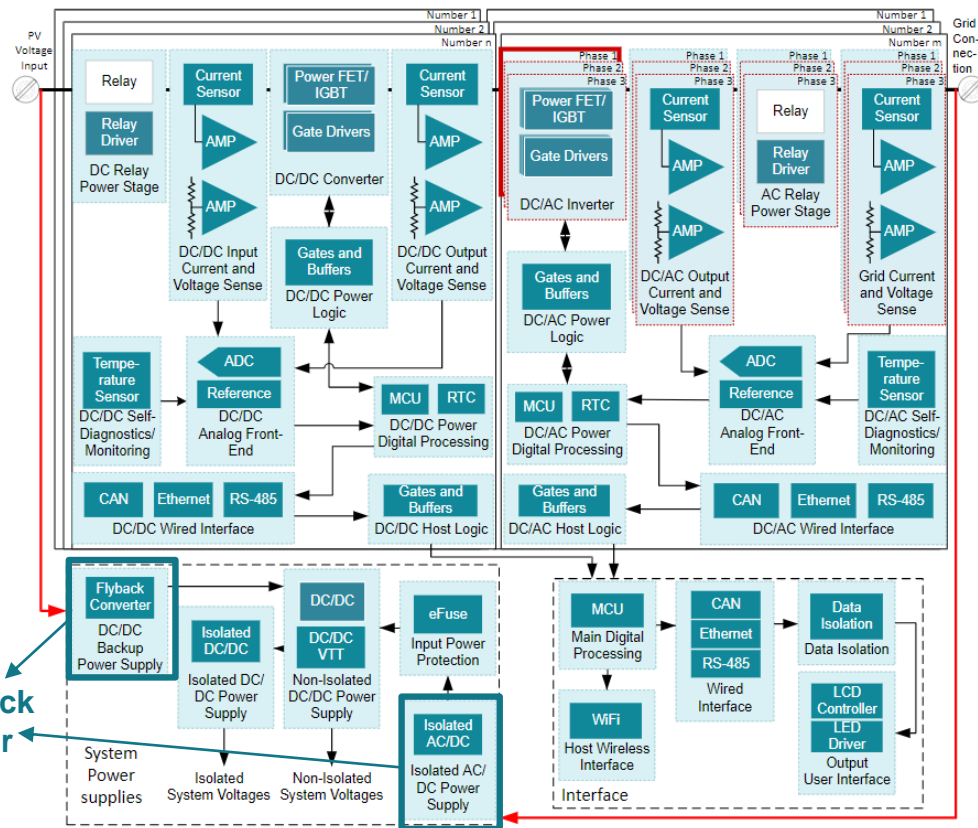

# Aux power supply of electricity meter


- **Where:**

- Typical power levels of 15 W – 20 W
- Operating input voltage range: 300 V to 950 V DC



- **Why SiC?**

- Higher VDS rating

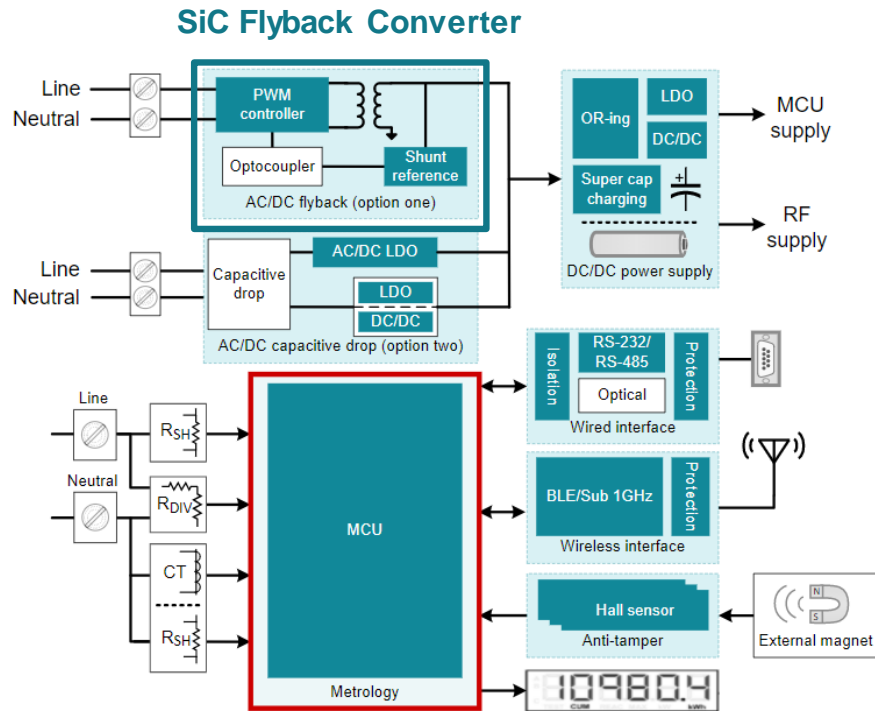


# Aux power supply in AC motor drive

## Where:


- Typical power levels of 20 W – 60 W
- Operating input voltage range:

Grid voltage	Input voltage range
200 vac, 3phase	100 V – 400 V
380 – 480 vac, 3phase	200 V – 820 V
525-690 vac, 3phase	300 V – 1130 V

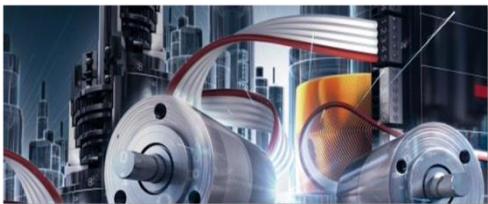
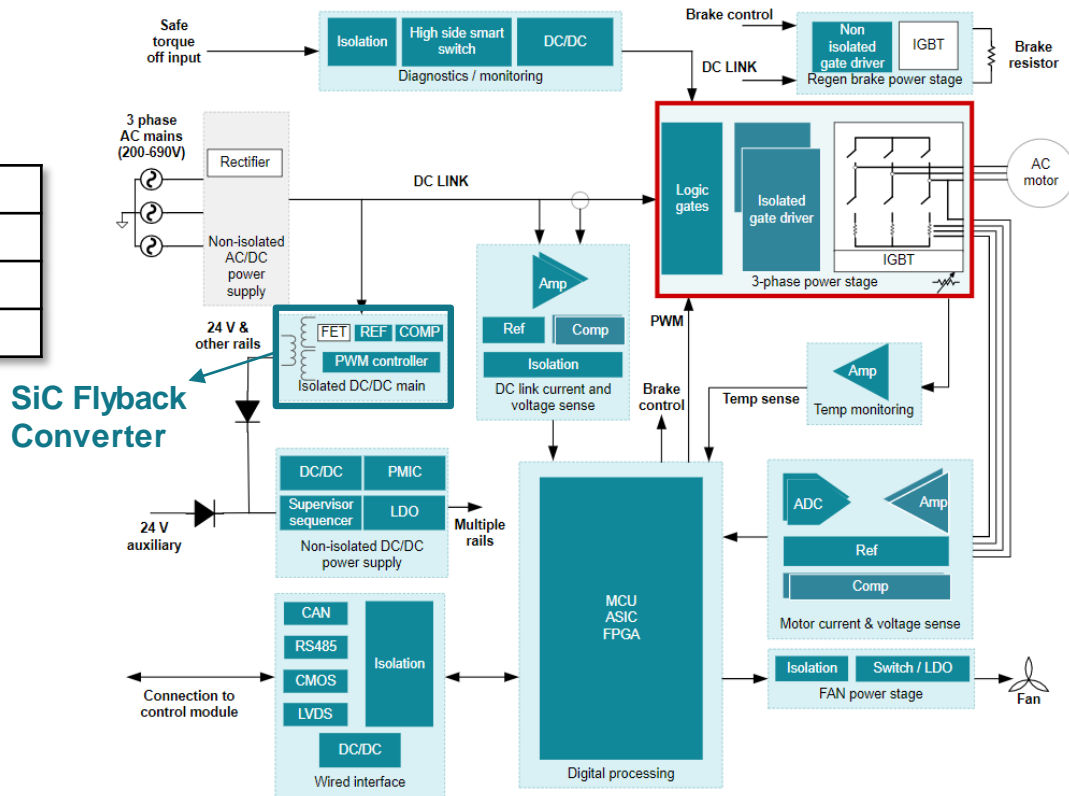
## Why SiC?


- Higher VDS rating
- Removal of heatsink






# Traction inverter bias power supply configurations


## Case 1

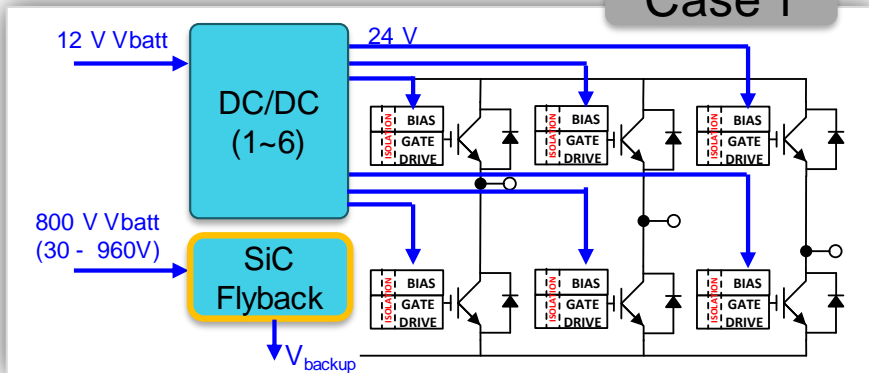


## Case 2

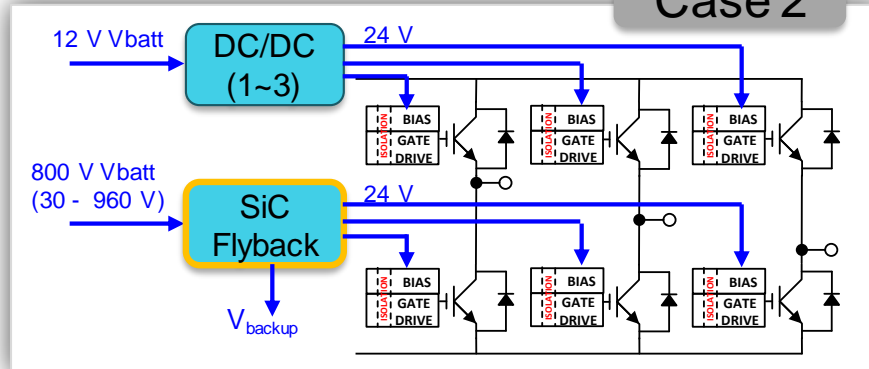

## Case 3

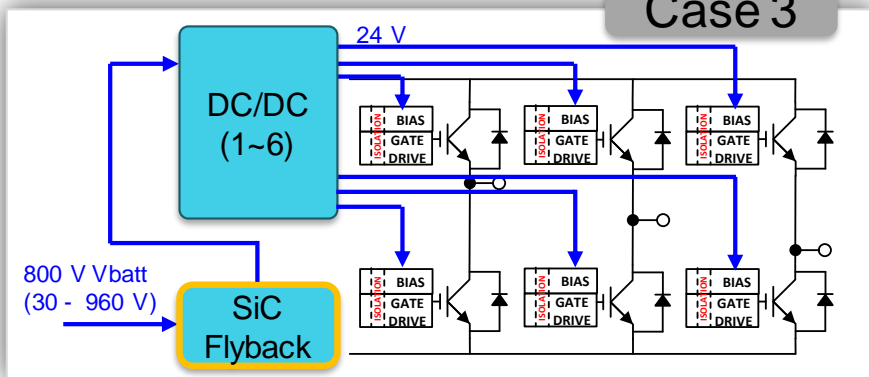

## Case 4


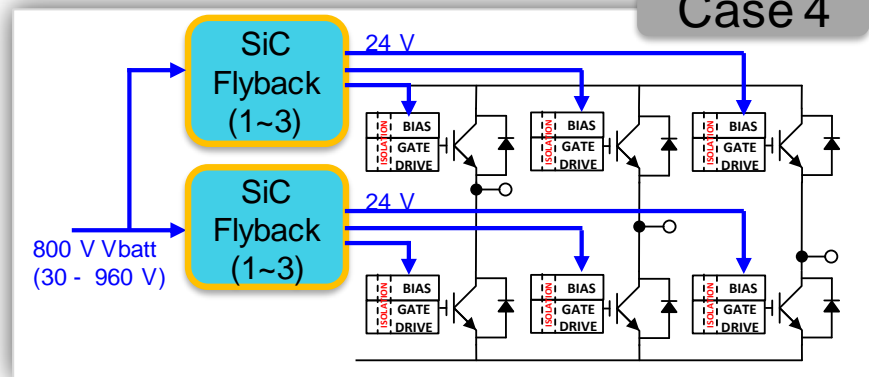




# Content

- Block diagram of end equipment with high-voltage bias power
- **Flyback topology candidate comparison**
- Design considerations of SiC flyback control circuitry
- Summary
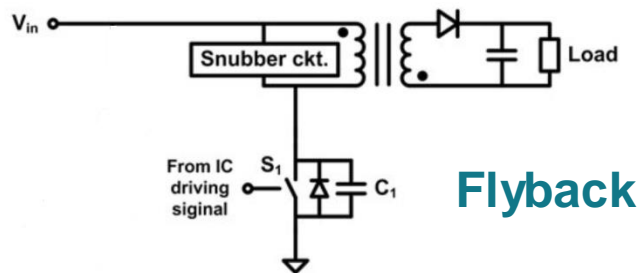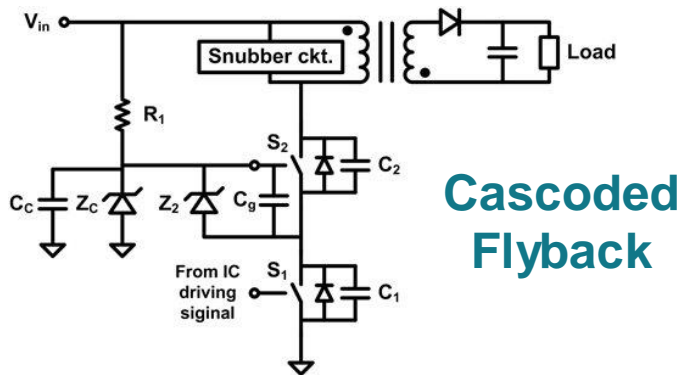
# Flyback Topology Candidate: Loss Comparison





Specifications: 800-V  $V_{in}$  to 15  $V_{out}$ .  $P_{out} = 60$  W,  $f_{sw} = 140$  kHz, CCM,  $T_J = 125^\circ\text{C}$ ,  $T_A = 105^\circ\text{C}$

	<b>Cascoded Si Flyback</b> (900 V, 1.2 $\Omega$ , IPD90R1K2C3ATMA1 x 2)	<b>SiC Flyback</b> (1700 V, 1.2 $\Omega$ , SCT2H12NY)
<b>Conduction Loss</b>	0.304 W for $R_{ds(on)}$ at $125^\circ\text{C} = 2.1 \Omega \times 2$	0.124 W $R_{ds(on)}$ at $125^\circ\text{C} = 1.71 \Omega$
<b>Turn-on Loss</b>	0.84 W for 0-500V $E_{oss}$ (0.42W x 2)	1.14 W for 0-1000V $E_{oss}$
<b>Gate Driving Loss</b>	0.176 W for 0-15V gate drive (88mW x 2)	0.035 W for 0-18V gate drive
<b>Sum</b>	1.62 W (not including gate clamp loss of cascade switch)	1.3 W


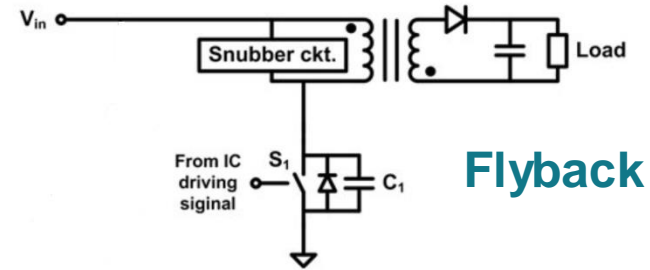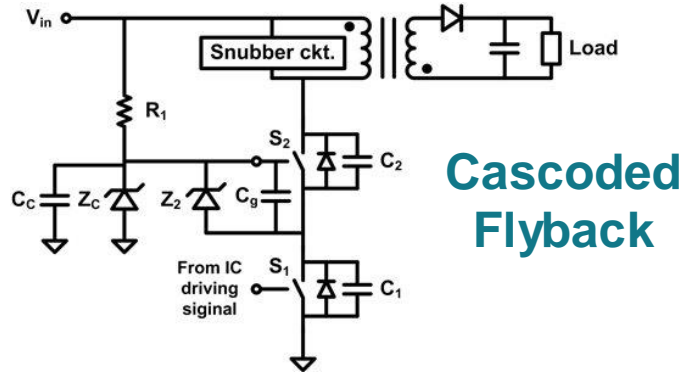
# Flyback Topology Comparison: BOM Difference



	<b>Cascoded Si Flyback</b> (900 V, 1.2 Ω, IPD90R1K2C3ATMA1 x 2)	<b>SiC Flyback</b> (1700 V, 1.2 Ω, SCT2H12NY)
<b>MOSFET</b>	\$0.2 x 2 = \$0.4	\$1.0 x 1 = \$1.0
<b>Gate Clamp</b>	342V, 1.1 A, TVS diode: \$0.15 x 2 = \$0.3 HV resistor stack 470kΩ, 0.1W: \$~0.01 x 5 = \$0.05 Clamp Capacitors 100pF, 500V, X7R: \$0.05 x 2 = \$0.1	0
<b>Heatsink</b>	513201B02500G: \$0.5 x 2 = \$1.0	513201B02500G: \$0.5 x 1 = \$0.5
<b>Sum</b>	\$1.85	\$1.5

# TIDA-01505 (SiC Flyback) Automotive 40V-1000Vin, 15Vout, 60W Flyback Reference Design for 800-V Battery System

## Design Features


- Wide-Vin isolated Flyback DC/DC converter over the Ultra wide input voltage range of 40 V to 1000 V DC, up to 1200 V transient.
- Regulated output voltage 15 V (<5% regulation) and output current up to 4 A.
- SiC MOSFET solution with high voltage rating, low gate charge and fast switching transients.
- SiC gate driver adaption from an integrated MOSFET gate driver utilizing center-tapped transformer.
- Constant switching frequency with duty cycle range from 15% to 80%.
- Current mode control with cycle-to-cycle over current limitation.
- Automotive Grade 1 qualified Transformer with Reinforced isolation (tested at 5.7 kV High-Pot).

## Tools & Resources


- **TIDA-01505 Tools Folder**
- **Test Data/Design Guide**
- **Design Files:** Schematics, BOM and BOM Analysis, Design Files
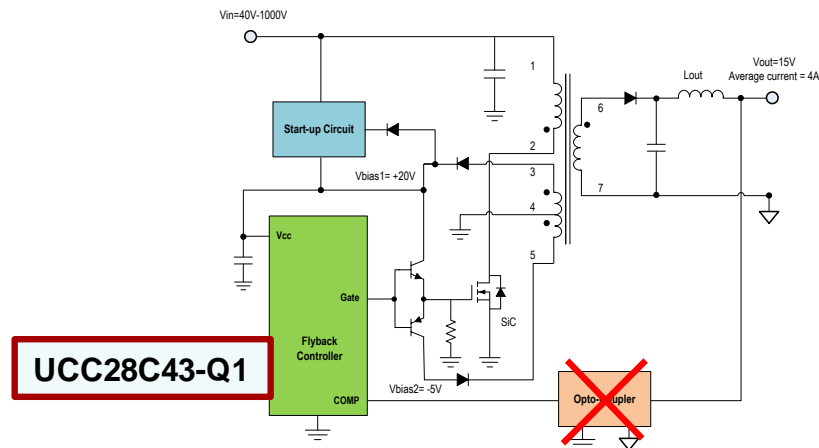
## Design Benefits


- Designed for isolated unidirectional power supplies in HEV/EV Traction Inverter systems.
- Support regenerative braking with the minimum start-up voltage of 40V.
- Extendable to higher voltage and higher power range.
- Automotive Grade 1 qualified Transformer with Reinforced isolation.



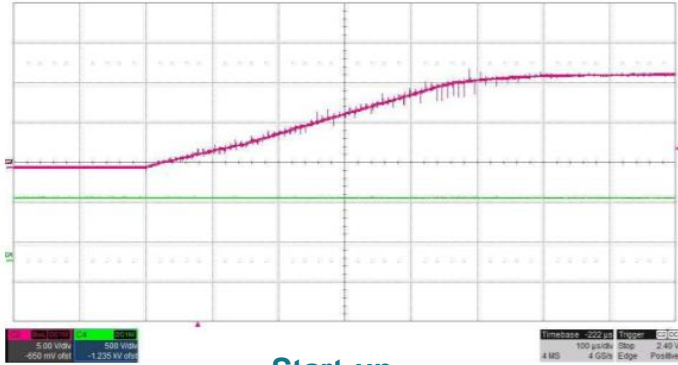
# Experimental Results of TIDA-01505 (SiC Flyback)




Start-up

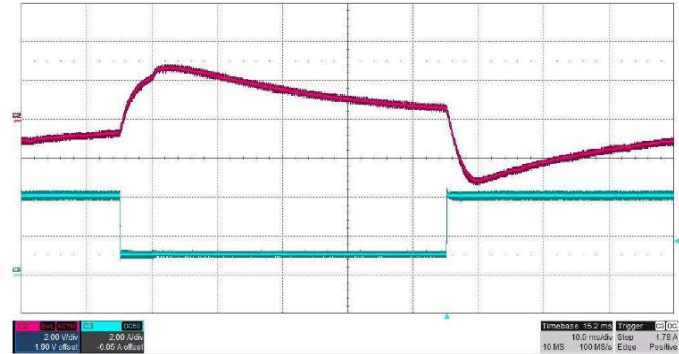

Load transient response

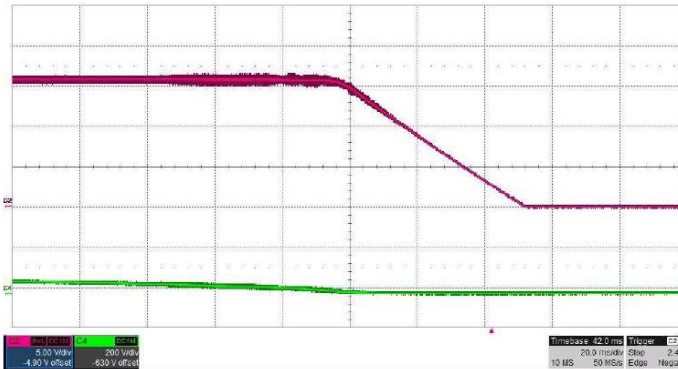

Shutdown

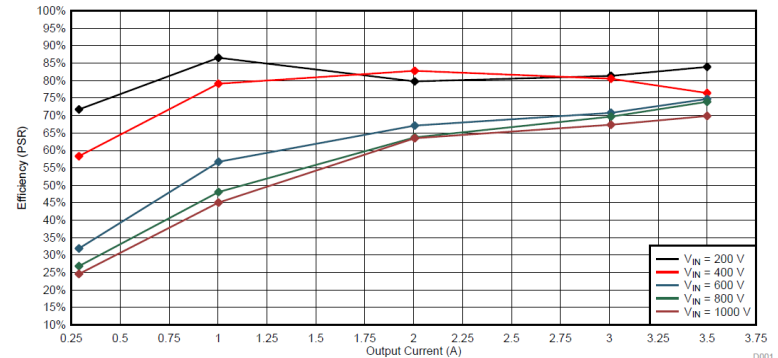

Measured efficiency

# Content

- Block diagram of end equipment with high-voltage bias power
- Flyback topology candidate comparison
- **Design considerations of SiC flyback control circuitry**
- Summary

# General purpose PWM controllers

Parameter	UCC28C4x	UCC280x UCC2813-x	UC284xA TL284xB	UC284x TL284x
Process technology	<b>BiCMOS</b>	BiCMOS	Bipolar	Bipolar
Absolute maximum VDD	<b>20 V</b>	12 V	30 V	30 V
Supply current at 50 khz	<b>2.3 mA</b>	0.5 mA	11 mA	11 mA
Startup current	<b>50 <math>\mu</math>A</b>	0.1 mA	0.5 mA	1 mA
Over-current propagation delay	<b>50 ns</b>	100 ns	150 ns	150 ns
Reference voltage accuracy	<b><math>\pm 1\%</math></b>	$\pm 2\%$	$\pm 2\%$	$\pm 2\%$
E/A reference accuracy	<b><math>\pm 25</math> mV</b>	$\pm 60$ mV	$\pm 80$ mV	$\pm 80$ mV
Maximum operating frequency	<b>1 MHz</b>	1 MHz	500 kHz	500 kHz
Output rise/fall times	<b>35 ns</b>	44 ns	50 ns	50 ns
UVLO turn-on accuracy	<b><math>\pm 1.0</math> V</b>	$\pm 1.2$ V	$\pm 1.5$ V	$\pm 1.5$ V


**UC284x, TL284x, UCC280x, UCC2813-x, UCC28C4x are all P2P parts.**

## Improvements provide:

- Greatly reduced power requirement
- Eliminates bootstrap supply
- Fewer external components
- Lower junction temperature
- Reduced stress during faults
- No current sense R/C filter networks
- Faster response to faults
- Higher frequency operations




# Aux power supply using UCCx8C4y

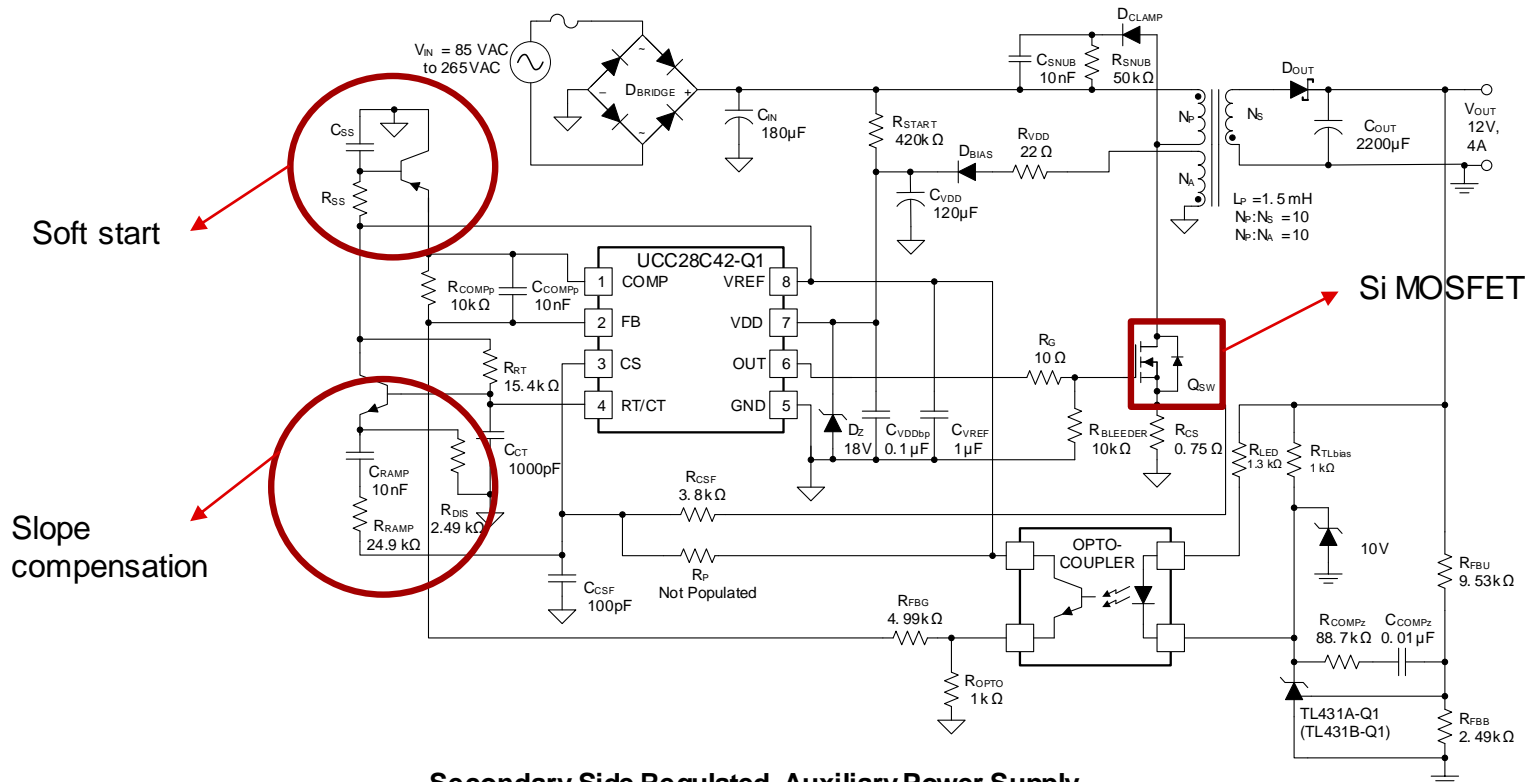


Copyright © 2016, Texas Instruments Incorporated

# PWM Controller requirements for driving SiC MOSFET

Ultra high-voltage (1700 V)	High-voltage (1200 V)	Mid-voltage (650 V to 900 V)
<b>Vgs Max Recommended: 20V</b> Cree C2M1000170D Rohm SCT2H12NY Littelfuse LSIC1MO170E	<b>Vgs Max Recommended: 20V</b> STmicro SCT10N120 Microsemi MSC080SMA120J	<b>Vgs Max Recommended: 18V</b> Rohm SCT3120AL STmicro SCTH35N65G2V
<b>Vgs Max Recommended: 15V</b> Infineon IMBF170R1K0M1	<b>Vgs Max Recommended: 18V</b> Infineon IMW120R350M1H  <b>Vgs Max Recommended: 15V</b> Cree C3M0350120J	<b>Vgs Max Recommended: 15V</b> Onsemi NTB020N090SC1 Cree E3M0280090D

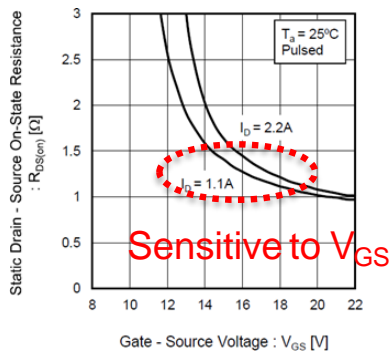

Rohm 1700 V, 1.0Ω SiC MOSFET

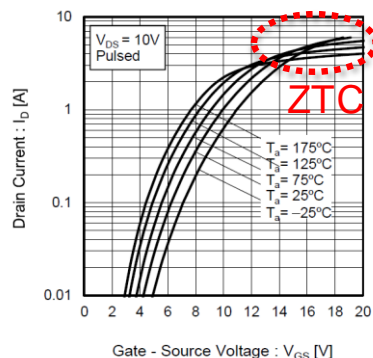

- High sensitivity of SiC FET on-resistance calls for
  - Less variation in controller output voltage
- High zero temp-co voltage of SiC FET calls for
  - Higher UVLO-off threshold from controller
- Commercial off-the-shelf SiC FET Vgs Max rating varies from manufacturer to manufacturer
  - Controller VDD has to be > 20V
- Requires clamped voltage at the output of the controller
  - Multiple clamp options for different Vgs ratings







# Summary

- Silicon MOSFETs are not desirable in high-voltage auxiliary power supplies due to their poor figure of merit and high cost
- Single-switch flyback with SiC MOSFET is the preferred topology for high-voltage auxiliary power supplies
- SiC MOSFETs allow greater system-level benefits, such as low cost, small size and high efficiency
- Gate drive of SiC MOSFET needs careful consideration:
  - SiC MOSFET on-resistance is highly sensitive to the gate voltage
  - Driving SiC MOSFET with insufficient voltage leads to thermal runaway
- GP PWM controllers along with necessary external components, such as comparator/LDO/gate driver, can drive SiC MOSFETs reliably and efficiently in high-voltage auxiliary power supplies


**Thank you**

# Backup




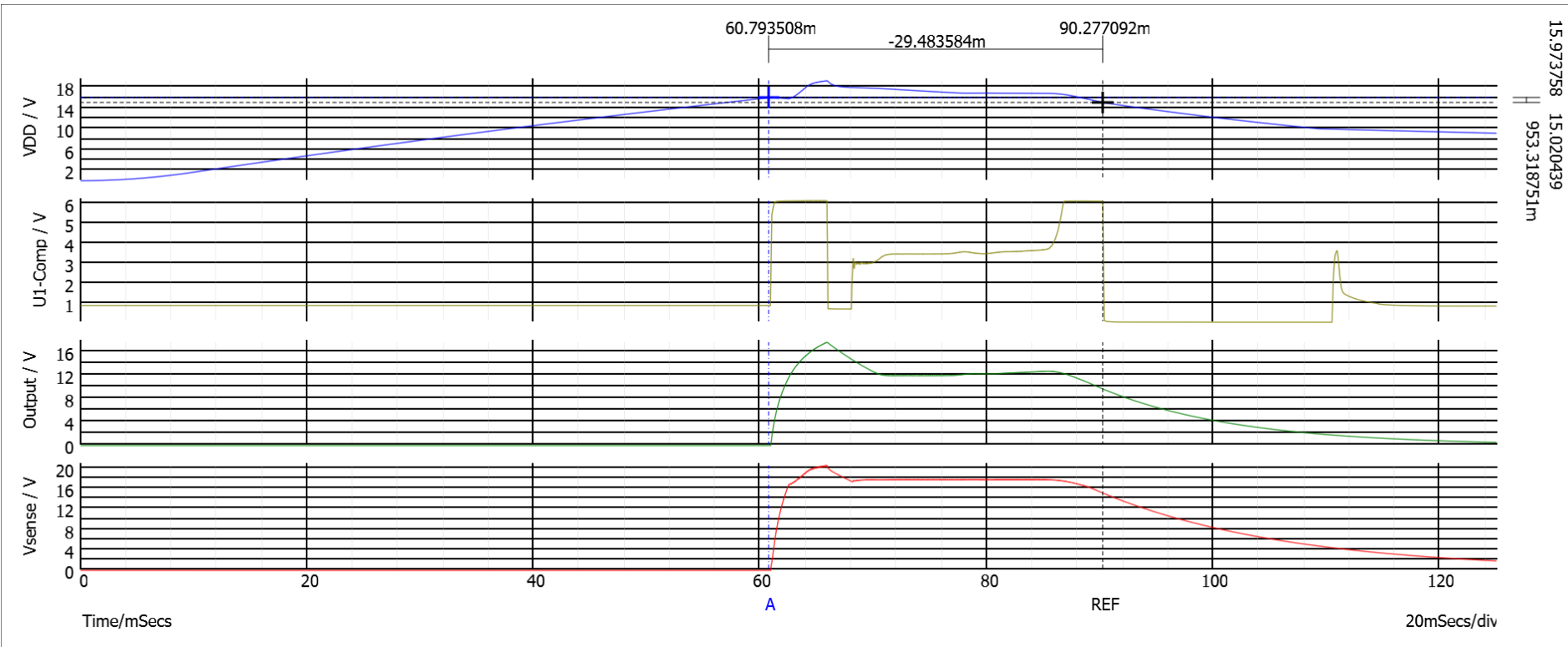
# SIMetrix simulation with external UVLO comparator





**©2021 Texas Instruments Incorporated. All rights reserved.**

The material is provided strictly "as-is" for informational purposes only and without any warranty.  
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated