

TI Designs: TIDA-01421

センサレス位置測定用の車載ブラシ付きモータのリプル・カウンタのリファレンス・デザイン



概要

最新の自動車に搭載されている小型モータは進化を続けており、各モータで駆動するシート、ウィンドウ、スライド・ドア、ミラー、リフト・ゲートなどの位置を記憶する需要が高まっています。既存のソリューションは、モータ本体に取り付けられた複数の磁気センサを利用して、モータ制御モジュールにフィードバック・ループを提供しています。センサレス手法は既存のソリューションに冗長性を提供し、場合によってはセンサを取り付けたモータは不要になります。インラインの電流センス信号コンディショニング回路の実装により、センサレス手法はますます広く使用されるようになってきています。このデザインでは、位置測定を制御する多くの車載用モータ・システム向けに簡単に変更できるソリューションを紹介します。

リソース




- TIDA-01421 デザイン・フォルダ
- INA240-Q1 プロダクト・フォルダ
- TLV2316-Q1 プロダクト・フォルダ
- LMV7275-Q1 プロダクト・フォルダ

特長

- 多くのDCモータ・ソリューション用に構成可能
- インラインのモータ電流センシングに対応できる、広い同相入力範囲
- 標準的な9V~18Vのバッテリー電源で動作
- MSP430™ LaunchPad™ 開発キットと簡単に接続でき、インターフェイスとデジタル・キャプチャが可能
- 高精度のテスト用ソリューション

アプリケーション

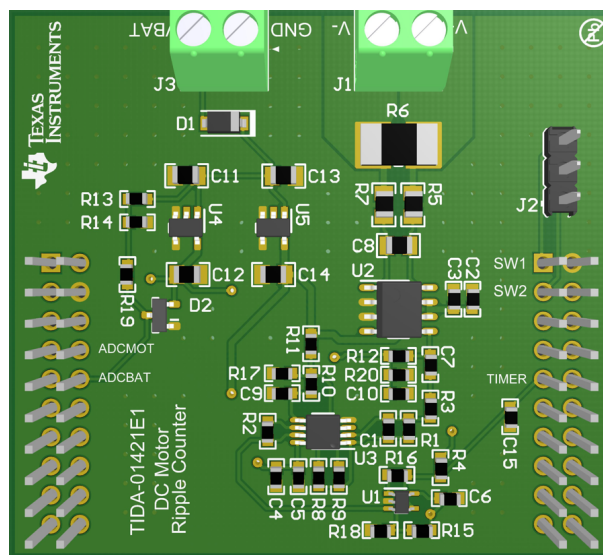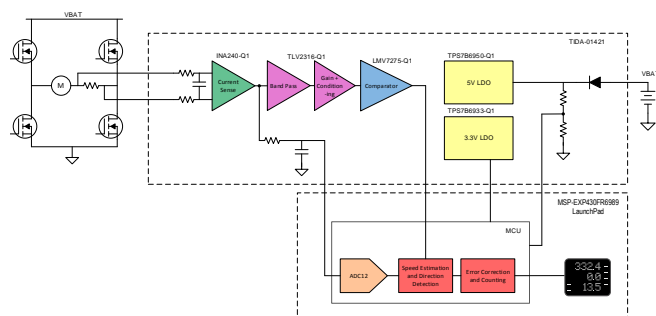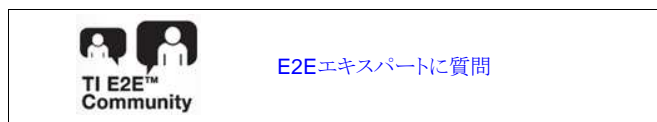- メモリ・シート
- パワー・ウィンドウ
- リフト・ゲートとパワー・トランク
- サイド・ミラー





使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE (重要な注意事項)をご参照くださいますようお願いいたします。

1 System Description

Motor position memory is being applied in more areas of the automotive vehicle including configuration and comfort settings for different driver profiles as well as diagnostics for more efficient and smarter control of the motor. The demand for more cost-efficient and easily-configurable solutions for many different motor types has increased. For example, the seats in a vehicle can feature many axes of movement and ergonomic adjustment all controlled by individual motors. Existing memory solutions for these seats require motors with magnetic Hall-effect sensors plus the additional extra wiring for each sensor. Sensorless position measurement reduces the requirement for this many sensors and wiring by sensing the in-line motor current at the seat control module itself.

A sensorless approach is possible for brushed DC motors due to the effect that the back-electromagnetic force (BEMF) has on the motor current seen entering the motor. As the motor rotates, the impedance seen by the BEMF periodically changes due to the nature of the DC motor brushes making contact with multiple poles of the motor and effectively shorting some of the motor windings. This change in impedance changes the measured current in a very periodic pattern proportional to the actual speed of the motor.

This system provides a way to measure this varying in-line motor current, filter and condition the resultant signal, then provide a 3.3-V digital logic level series of rising and falling edges for a digital processor to count and analyze for accuracy and feedback to the main motor controller. With some simple changes in current sense resistor values, gain settings, and filter bandwidths, this solution can quickly be modified for use with many small motor systems.


1.1 Key System Specifications

表 1. Key System Specifications

PARAMETER	SPECIFICATIONS
Normal power supply operating range	9 V to 18 V
Common mode input range	-4 V to 80 V
Operating ripple frequency range	100 Hz to 1.3 kHz
Maximum motor current	±16 A

2 System Overview

2.1 Block Diagram

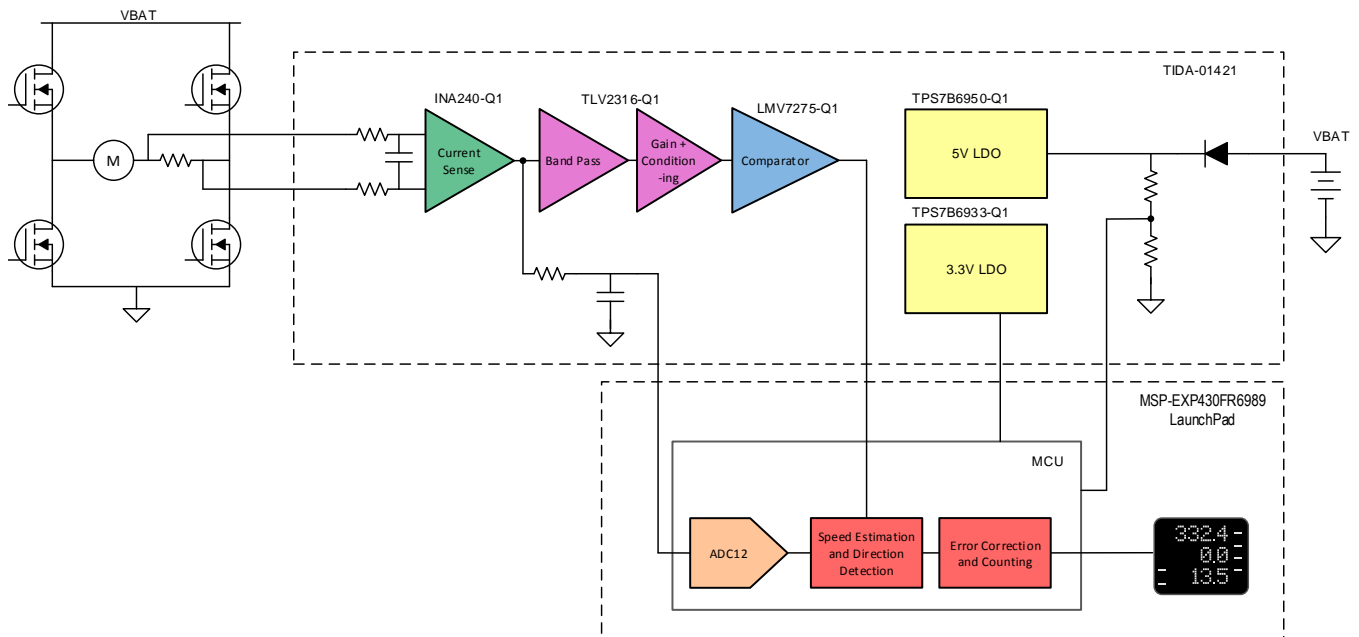

2.2 Highlighted Products

2.2.1 INA240-Q1

The INA240-Q1 is a wide common-mode range, high-accuracy, bidirectional current shunt monitor. With a -4V to 80V common-mode range, the device can sense within all typical operating voltage ranges for a DC motor application as well as be protected from typical automotive overvoltage and undervoltage fault conditions. The device features a very large common mode rejection ratio of 120dB, providing an accurate, low noise measurement even in speed controlled, PWM driven motor solutions. The accuracy and drift performance of this device allow for minimal error when measuring the motor ripples. The device can operate from a single supply from 2.7 V to 5.5 V.

2.2.2 TLV2316-Q1

The TLV2316-Q1 is a dual, low-voltage, rail-to-rail general-purpose operational amplifier. The robust design provides ease-of-use to the circuit designer: a unity-gain stable, integrated radio frequency (RF) and electromagnetic interference (EMI) rejection filter, no phase reversal in overdrive condition, and high electrostatic discharge protection. This dual operational amplifier (op amp) is utilized for the two-stage signal conditioning before the output comparator.

2.2.3 LMV7275-Q1

The LMV7275-Q1 is a single rail-to-rail input low-power comparator and features an open-drain output for correct level shifting to interface with a typical 3.3-V microcontroller (MCU) GPIO. The tiny SC-70 package is ideal for low-voltage, low-power, and space-critical designs.

2.2.4 TPS7B69-Q1

The TPS7B69-Q1 is a family of high-voltage, low quiescent current low-dropout linear regulators (LDOs) available in both 3.3-V and 5-V output options. The LDOs power all of the devices on this design, but also provide the necessary 3.3 V to power an MCU.

2.3 System Design Theory

The current measured in-line with the brushed motor has both a large-amplitude, very-low frequency DC component and a small-amplitude, high-frequency AC component. Both of these components must be considered when choosing the correct configuration for this design.

The total current seen in-line with the motor can be solved in 式 1 as:

$$I_{\text{MOTOR}} = \frac{(V_{\text{ARMATURE}} - V_{\text{BEMF}})}{R_{\text{ARMATURE}}} \quad (1)$$

where,

- V_{ARMATURE} is the DC voltage applied across the motor armatures,
- V_{BEMF} is the BEMF generated by the motor during operation,
- R_{ARMATURE} is the equivalent series resistance seen between the armatures.

The DC-component current is the main source driving the inductive load of the motor. The motor load varies widely depending on the necessary torque to drive the mechanical motor assembly. In high-torque automotive applications like windows and seats, the steady-state current delivered to these loads can be in the range of 10 A to 20 A.

The AC-component current is created by the sinusoidal BEMF generated by the motor, as well as the periodic changes in motor coil impedance due to the motor brushes shorting adjacent commutator poles. The amplitude and frequency of this component also varies both on the mechanical load on the motor and the design of the motor itself. This AC component contains the ripple that the user should measure and is directly proportional to the actual motor speed. Every ripple corresponds to a commutator pole rotation across the armature brushes. The total sub-divisions of a full rotation can be captured by knowing the total number of poles in the motor.

2.3.1 PCB Size and Form Factor

The design includes daughtercard jumpers for connection to an MSP430™ LaunchPad™ to easily interface with an MCU for ripple counting. This requirement is responsible for the necessary 2 in of width on the PCB, after which all other layout considerations were made. The final board design is 2.1 in × 1.9 in after making all the necessary design considerations. The PCB is two-sided and components are only placed on the top side.

The total PCB area is much less in a production design because the large connectors for the battery, in-line motor sense, and the MSP430 LaunchPad jumpers are not necessary. The local linear regulators on the board are likely to be shared with other components on the motor driver controller assembly. The current sense, signal conditioning, comparator devices, and associated passive components on this design were kept as close together as possible to minimize the board space they use, which indicates a typical production-design use case.

2.3.2 Current Sense Amplifier Stage

The total motor current can be measured by sensing on the low side of the driver bridge, or in-line with the motor. Sensing current on the low side introduces additional impedances and layout concerns to retain accuracy of the ripple signal. Additionally, to measure ripples in both directions, low-side sensing requires a sensing amplifier on both sides of the full bridge, which increases the total component count. When measuring in-line with the motor, bidirectional measurement with a single device is possible. However, there are design concerns that must be made to ensure an accurate output for the signal conditioning stage.

The MOSFET bridge driving the motor in an automotive application is typically powered directly by the automotive battery. The typical supply range of the battery is 9 V to 14 V; however, some typical automotive conditions can lead to operating voltages of 6 V to 40 V. Note that, when choosing a current sense amplifier, it must be able to withstand common-mode voltages across this entire range to prevent functional damage to the device. The INA240-Q1 has a very-wide common mode range of -4 V to 80 V, which is very capable of withstanding all the possible common-mode conditions expected for the design.

The INA240-Q1 can also be biased to provide a bidirectional output to measure both motor rotational directions. The output stage of the INA240-Q1 utilizes two reference pins, REF1 and REF2, to bias the output. By tying REF2 to the supply voltage V+ and REF1 to ground, the output of the INA240-Q1 rests at the mid-supply rail voltage. In this application, the supply voltage is 5 V; therefore, depending on the motor direction, the output is between 0 V to 2.5 V or 2.5 V to 5 V. This output voltage can be calculated in 式 2 as:

$$V_{OUT} = I_{MOTOR} \times R_{SENSE} \times GAIN + 2.5 V \tag{2}$$

The maximum current to be sensed can be used to choose the correct value for the sense resistor. For this design, a maximum of 16 A has been chosen. With the INA240-Q1 gain of 50 V/V and 4.9 V as the maximum output voltage, R_{SENSE} can be solved in 式 4 by using the previous 式 2:

$$R_{SENSE} = \frac{(4.9 V - 2.5 V)}{(16 A \times 50 V/V)} = 3 m\Omega \tag{4}$$

The sense resistor must be sized properly for handling a very large amount of power. A size 2512 resistor rated for 3 W has been chosen for this design.

A simple common-mode RC input filter can be used at the input of the INA240-Q1 device to reduce the noise generated by high-frequency motor brush and potential PWM switching noise.

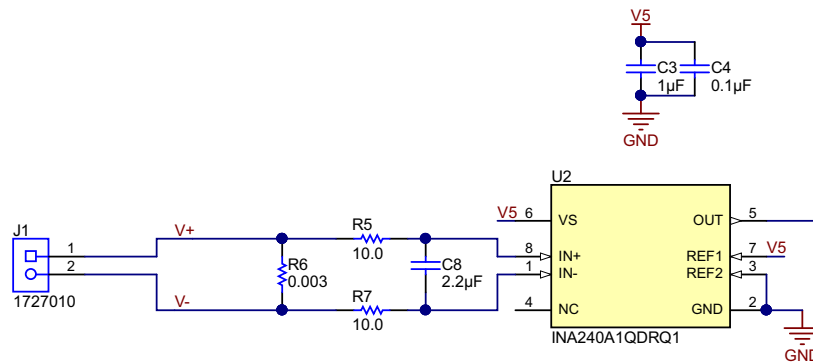


図 1. Schematic of Current Sense Amplifier Stage

2.3.3 Band-Pass Filter Stage

The output of the current sense amplifier is filtered with an active band-pass filter to look at the motor ripple signal and remove additional noise and the DC-component variance. The ripple frequency that must be measured largely depends on the typical rotations per minute (RPM) of the motor and the total number of commutator poles. For this design, the filter is limited to about 100 Hz to 1.3 kHz. An inverting amplifier topology has been used to allow for biasing before the next amplifier stage. The simple TLV2316-Q1 has been chosen for its low-voltage operation and rail-to-rail input. Standard op-amp design guidelines pertaining to power supply decoupling and layout considerations are followed.

Figure 2 shows a schematic of the band-pass filter stage.

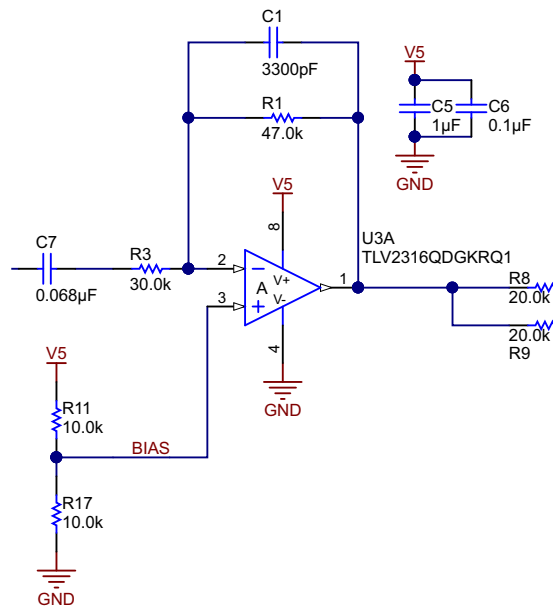


Figure 2. Schematic of Band-Pass Filter Stage

2.3.4 Differential Amplifier for DC-Bias Adjustment

The main goal for the signal conditioning amplifier stages is to generate a clean, low-noise AC signal that can be measured by the final comparator to generate a 0-V to 3.3-V square wave with a switching frequency equal to the motor ripple frequency. Biasing the sinusoidal ripple waveform around the comparator reference point is the preferred method for generating this square wave. The previous filter stage starts this process but the specific filter requirements and operating frequency range lead to some additional necessary steps in the design to ensure proper biasing for the comparator stage.

The high-pass portion of the previous filter stage is configured to approximately 100 Hz, which requires a fairly large RC filter to achieve. This filter also generates a huge time constant that shows its effects on the signal during the very large initial spike in motor current at start-up. This current spike is large enough and slow enough to not be filtered out by the high-pass circuit, and the value for the RC time-constant means that the low-frequency DC component of the signal does not settle to a resting point very quickly. The motor begins to turn during this current spike and ripples are generated. The comparator misses multiple ripples for counting if this change in the effective DC-bias point of the signal is left to remain.

Figure 3 shows the initial spike in current (yellow waveform) and the resultant signal after the differential amplifier stage (green waveform).

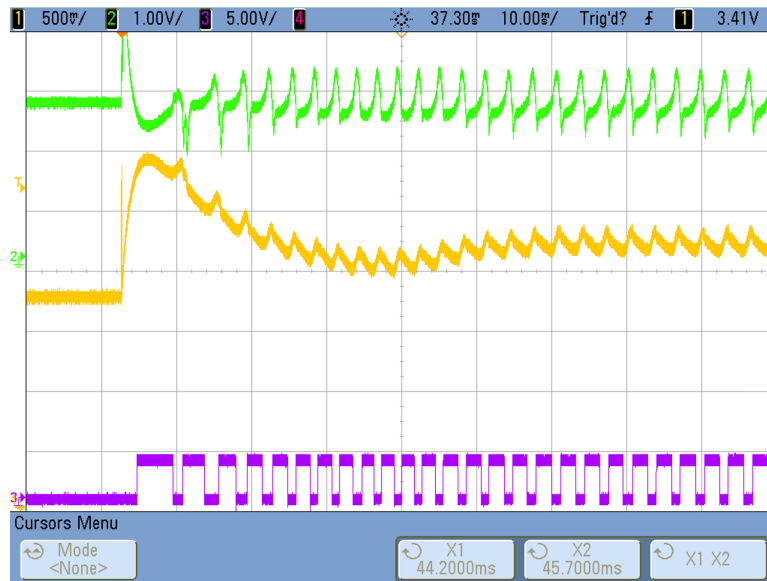


図 3. Oscilloscope Image of Initial Current Spike

This low-speed, high-amplitude current spike is removed from the signal with the unique use of a differential amplifier stage. The output of the band-pass filter is used for both the positive and negative inputs of the amplifier, but one side of the amplifier is very slightly filtered with a low-pass RC filter. This small RC filter causes a very slight phase shift and attenuation of the ripple signal, but has very little effect on the large DC-bias spike. The common mode essentially stays the same on both inputs and is negated by the amplifier. The phase and amplitude difference between the AC signals on both inputs leads to a differential output retaining the ripple frequency component. A very large differential gain of 55 V/V provides a large signal swing of the signal difference and a DC re-biasing around 2.5 V allows the output of this stage to have a very clean and consistent bias point for the signal being measured by the comparator.

図 4 shows the schematic for the differential amplifier stage of the signal chain. The BIAS signal comes from the resistor divider used to bias the previous band-pass filter stage.

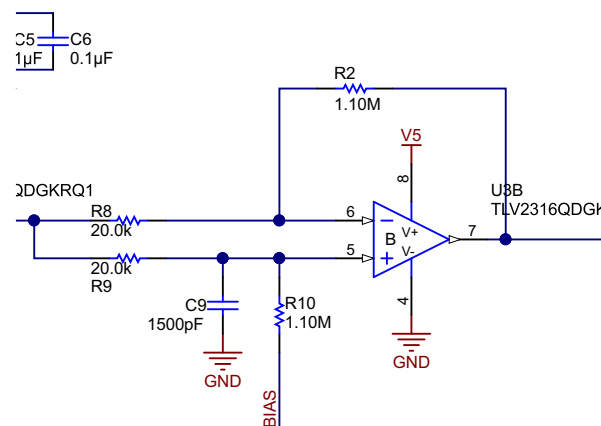


図 4. Schematic of Differential Amplifier Stage

2.3.5 Comparator Stage

The comparator stage of the design generates the final 0- to 3.3-V signal used by the MCU for counting. An open-drain output device has been chosen to create the proper 3.3-V levels for input into a typical MCU GPIO. An inverting hysteresis topology (see 図 5) has been utilized to reduce the effects of noise on the input of the comparator.

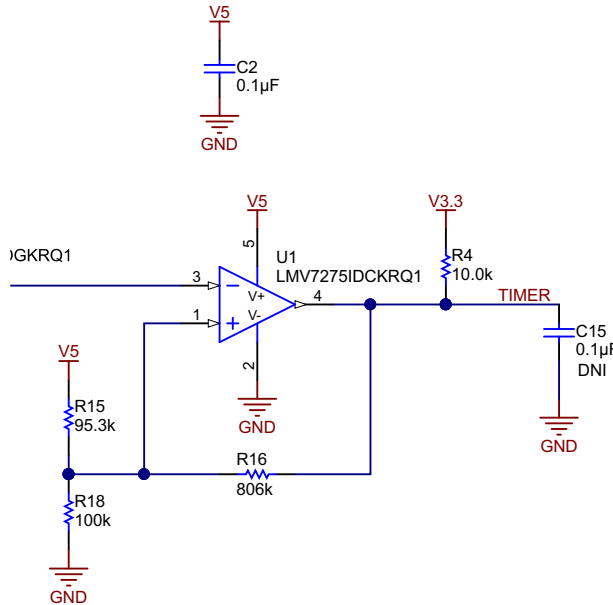


図 5. Schematic of Comparator Stage

For an inverting open-drain topology, the DC thresholds with hysteresis can be determined in 式 5 and 式 6 as:

$$V_{TL} = \left((R_{18} \parallel R_{16}) \times \frac{V_{CC}}{((R_{18} \parallel R_{16}) + R_{15})} \right) + \left((R_{15} \parallel R_{18}) \times \frac{V_{OL}}{((R_{15} \parallel R_{18}) + R_{16})} \right) \tag{5}$$

$$V_{TH} = \left((R_{18} \parallel R_{16}) \times \frac{V_{CC}}{((R_{18} \parallel R_{16}) + R_{15})} \right) + \left((R_{15} \parallel R_{18}) \times \frac{V_{OH}}{((R_{15} \parallel R_{18}) + R_{16})} \right) \tag{6}$$

For this application, the $V_{OL} = 0\text{ V}$ causes a slight offset to the centering of the main biasing point for the comparator. Because the AC signal is centered around 2.5 V, the comparator reference point in combination with the feedback resistor is adjusted to allow the V_{TL} and V_{TH} to be centered around 2.5 V as well.

2.3.6 Motor Power Supply and Current Monitoring

This design includes both the power supply and motor current as the output pin on the LaunchPad jumpers for additional monitoring and control. These pins can be used to recognize faults like overvoltage and overcurrent conditions and can also be used to help correct for errors in the ripple counter.

The battery voltage measures directly after the reverse protection diode. This voltage is then scaled down to meet the input range of a typical 3.3-V MCU. For this design, normal operation is considered 9 V to 18 V, so 18 V is scaled to equal 3 V. Overvoltage conditions can still be monitored up to 19.7 V for the configured voltage divider. Protection diodes and a current limiting resistor have been added on this line to protect the MCU from damage if the battery voltage exceeds 19.7 V. A resistor divider at the output of the current sense amplifier is used to attenuate the signal to meet the maximum 3.3-V input requirements of the MCU ADC.

Assorted mechanical effects on the motor, including brush noise and unusual loading conditions, can cause unwanted effects on the measured signal current. These effects can lead to excessive false or missed triggering of the output comparator. Error correction can be performed in the MCU relying on basic estimations of the motor speed, which are based on the power supply voltage and motor DC current. The motor speed can then be translated to a proportional ripple frequency and compared to the actual ripple frequency. Comparing the estimated ripple frequency to the actual frequency allows for smart error correction of the running ripple count.

Use 式 7 and the frequency-dependent equation for the BEMF voltage to estimate the motor speed:

$$V_{BEMF} = \omega \times K_e \tag{7}$$

where,

- ω is the motor speed,
- K_e is the motor constant (taken from the data sheet of the motor).

Replacing V_{BEMF} in the previous and solving for ω leads to 式 8:

$$\omega = \frac{V_{ARMATURE} - (I_{MOTOR} \times R_{ARMATURE})}{K_e} \tag{8}$$

$R_{ARMATURE}$ and K_e are known parameters of the motor. $V_{ARMATURE}$ is the motor supply voltage and I_{MOTOR} is the motor DC current, which are both values that can be captured by the MCU ADC. The motor current value can also be used to infer the direction of the output for adding or subtracting counts from the total during operation.

図 6 shows the circuitry used to monitor these signals.

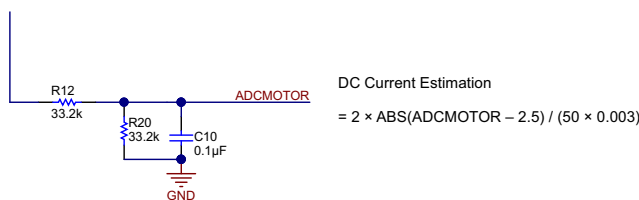


図 6. Schematic of Monitoring Connections (A)

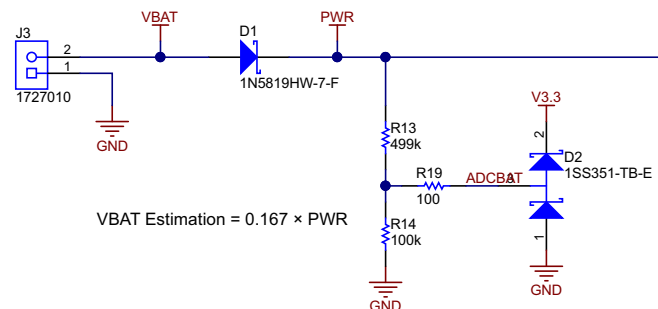



図 7. Schematic of Monitoring Connections (B)

2.3.7 3.3-V and 5-V Regulators

This design uses two linear dropout regulators (LDO) for the necessary 3.3- and 5-V voltage supply. These devices have a wide input voltage for operation and protection for the entire possible battery voltage range and all possible fault conditions.

The only design consideration to make for these devices is sizing the capacitors. The data sheet recommends that the input capacitor be larger than 0.1 μF and the output capacitor should be between 2.2 μF and 100 μF . A 4.7- μF value was used as the input capacitor and 2.2 μF was used as an output capacitor on both devices.

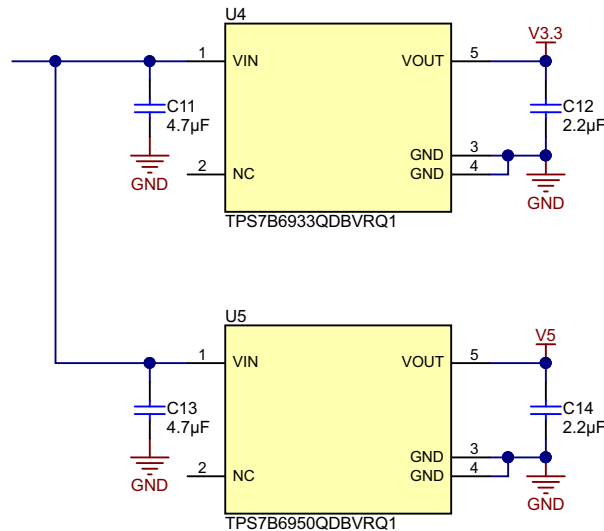☒ 8 shows the configuration of these LDOs.



☒ 8. Schematic of LDO Configuration

2.3.8 LaunchPad™ Connectors

To interface with a typical MSP430 Launchpad, the appropriate 20-pin jumpers are used. The following signals are tied to these jumpers:

- 3.3 V for powering the MSP430
- Output of the comparator tied to one of the timer counter pins of the MSP430 for both counting of the ripples and to use the TimerB peripheral to measure the frequency of the ripples for error correction
- Battery supply (ADCBAT) and DC motor current (ADCMOTOR) for both error correction and fault detection
- Two GPIO connections tied to jumper J2 for general purpose use, such as button press signals to detect motor direction

The specific pinout is chosen based on the featured peripherals of the MSP-EXP430FR6989. This board is chosen for very basic functional tests of design from a digital standpoint.

☒ 9 shows the schematic connections to the LaunchPad jumpers.

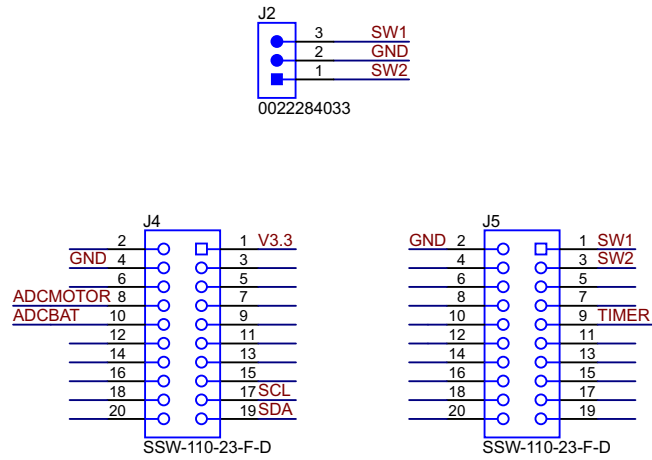


図 9. Schematic of MSP430™ LaunchPad™ Jumper Configuration

3 Getting Started Hardware

The larger 20-pin connectors J4 and J7 can interface with a typical MSP430 LaunchPad. The MSP-EXP430FR6989 was used for testing of the design to allow the ripple count to be output to the onboard LCD screen of the LaunchPad.

Jumper J3 provides a connection for a power supply. Jumper J1 is the connection to place the current sense amplifier in-line with the motor. The final jumper, J2, is a simple connection to the LaunchPad GPIOs for button-press detection or other triggering. 表 2 lists details on all the connections.

表 2. Table of all Jumper Connections

JUMPER	PURPOSE
J1	In-line motor current sense connection
J3	Battery power supply connection
J2	MSP430™ GPIO connection for button press, triggering, and so forth
J4, J7	MSP-EXP430FR6989 LaunchPad™ connectors

図 10 shows a rendering of the top side of the PCB and 図 11 shows the PCB attached to the LaunchPad.

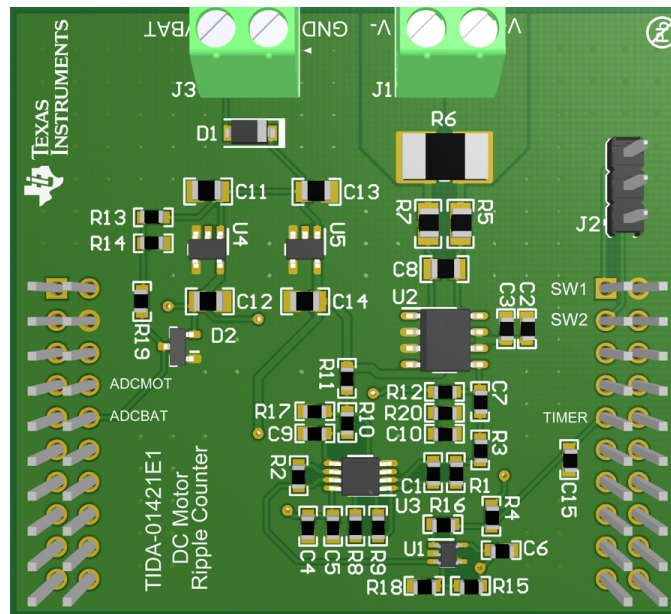


図 10. 3D Rendering of Top Side PCB

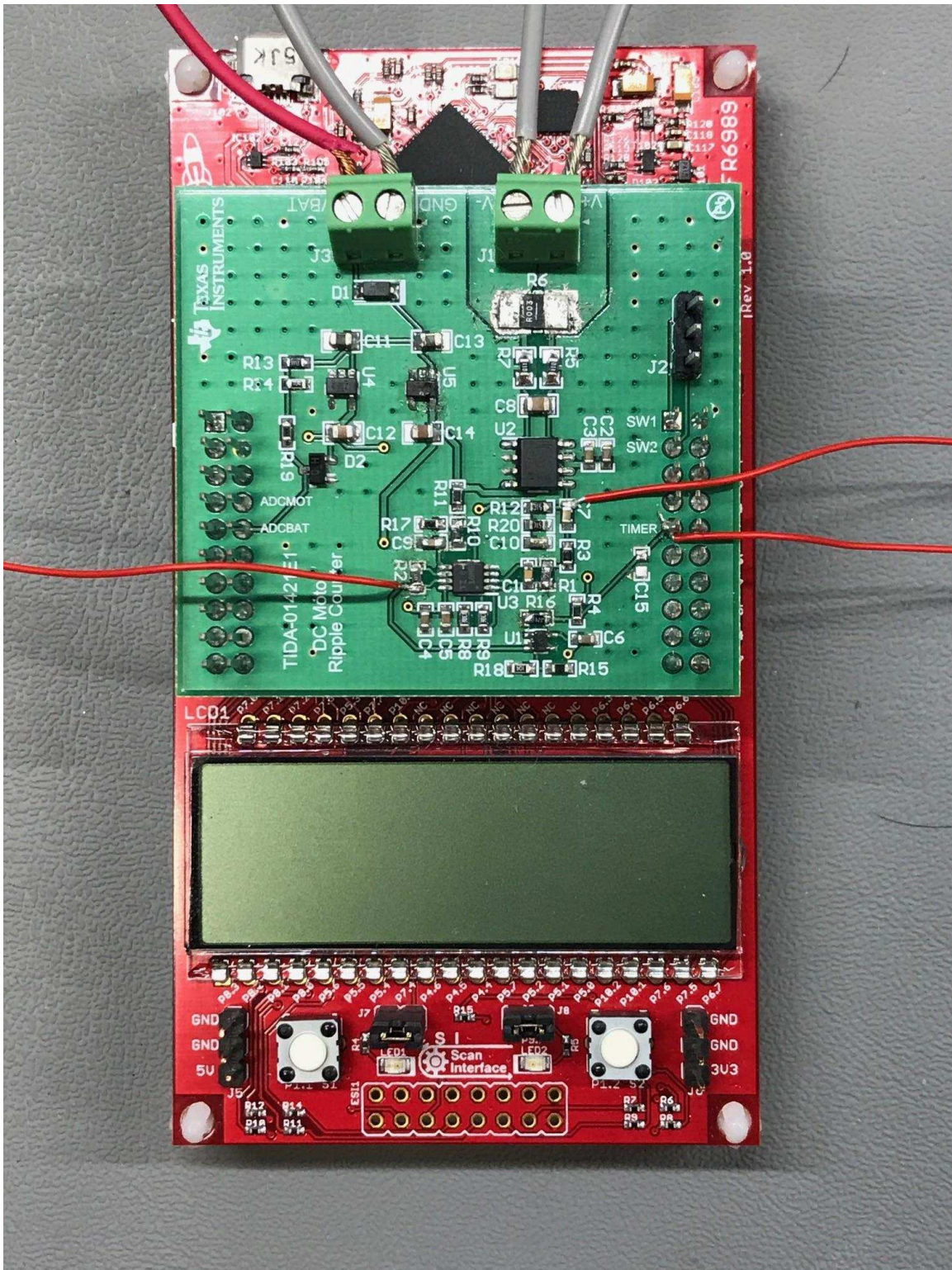


図 11. TIDA-01421 Attached to MSP-EXP430FR6989 LaunchPad™

4 Testing and Results

This design was tested in conjunction with the motor driver design of TIDA-01330, a two-axis seat motor driver design. For testing, this board drove the motors on a standard car seat assembly. The ripple counter design was inserted in-line with the motor driver output for both the forward-backward axis as well as the up-down axis motors.

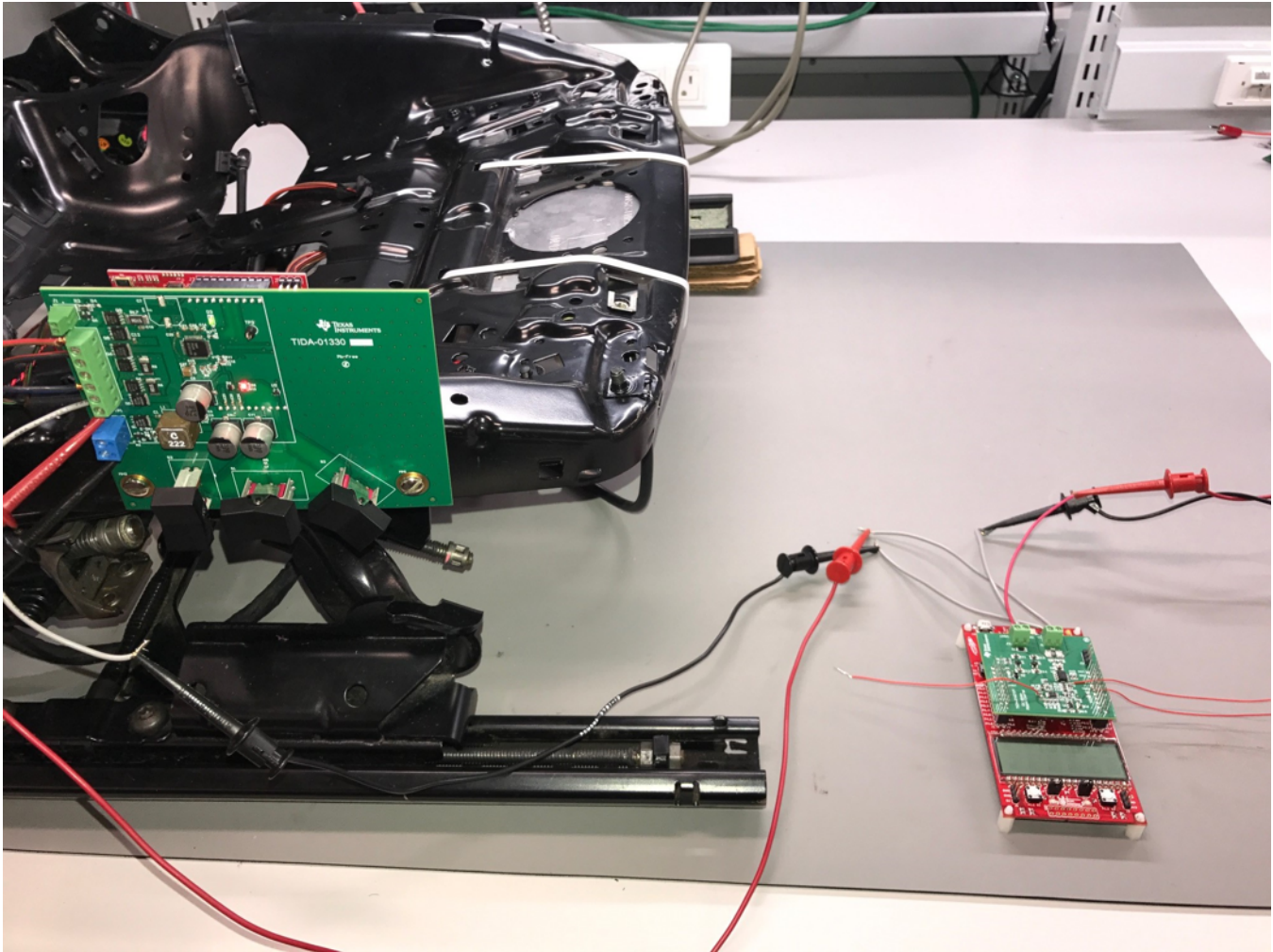


図 12. Test Setup of TIDA-01421 Tested in Combination of Automotive Seat Assembly and TIDA-01330

4.1 Forward-Backward Motor Operation

In all of the following results, the yellow waveform is the output of the INA240-Q1, the green waveform is the output of the differential-amplifier stage, and the purple waveform is the output of the comparator.

4.1.1 Normal Operation at 12 V

The initial tests show the results of the ripple counter when measuring the forward-backward motor at 12 V.

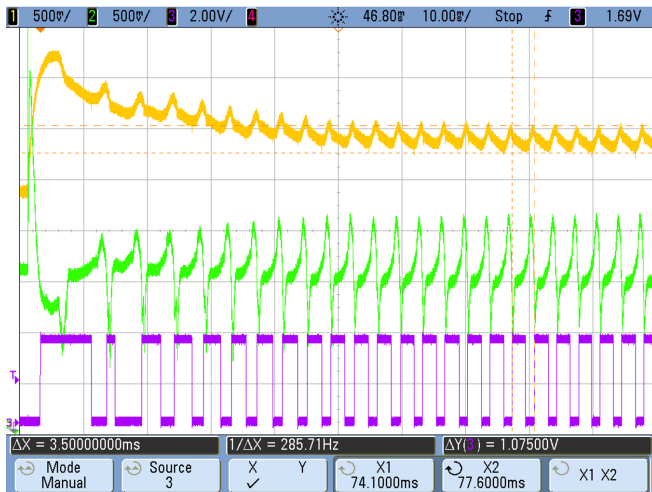


図 13. Forward Motor Operation at 12 V

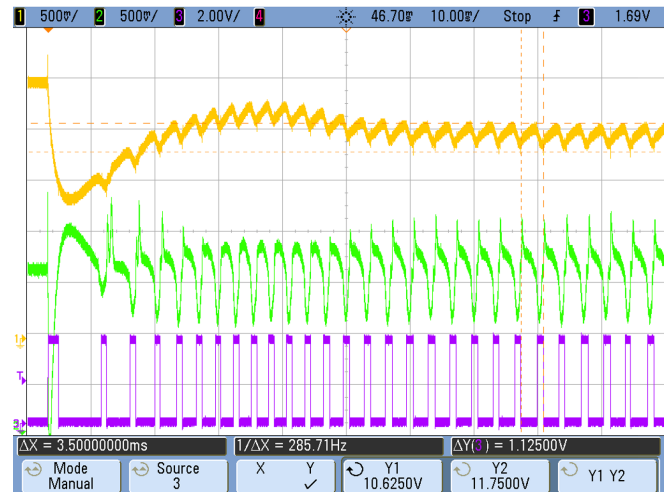


図 14. Backward Motor Operation at 12 V

4.1.2 Operation at 9 V and 18 V

The next set of results show the change in motor speed based on a change in the motor supply voltage at 9 V and 18 V.

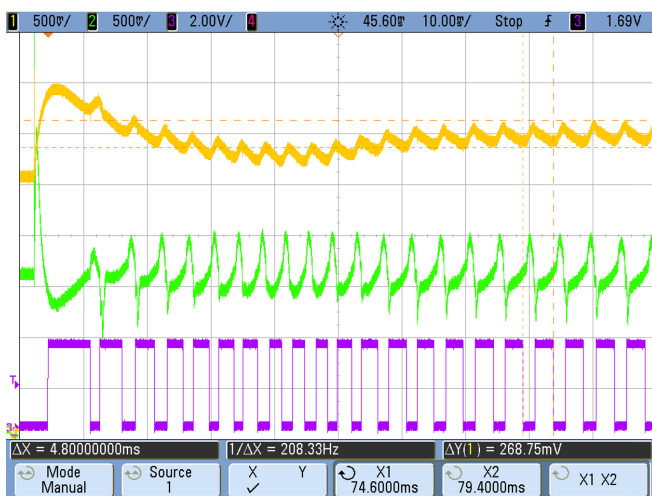


図 15. Forward Motor Operation at 9 V


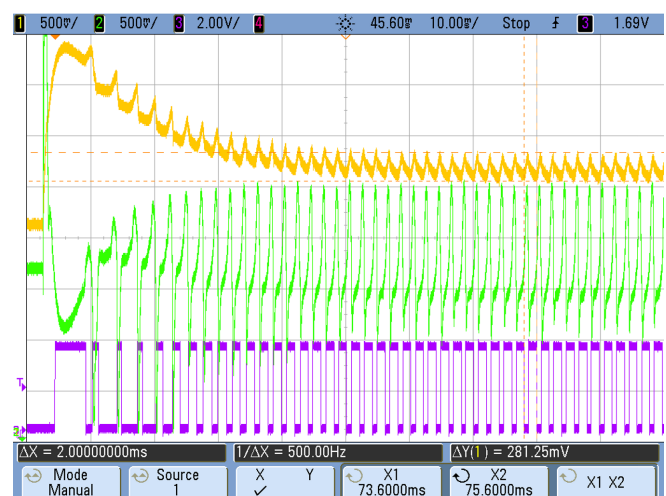



図 16. Forward Motor Operation at 18 V

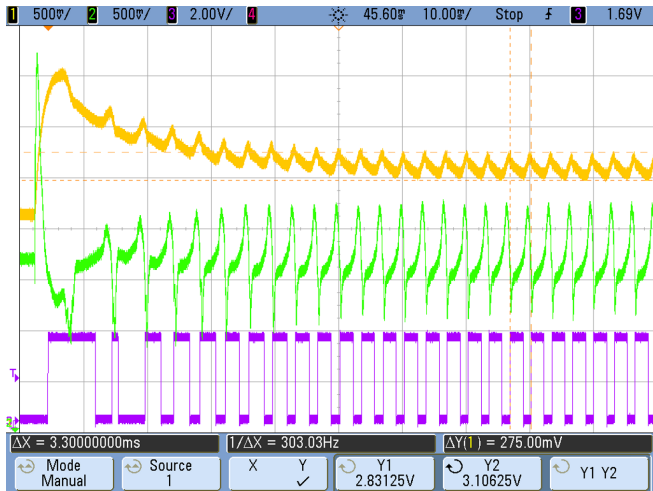4.1.3 Operation With Added Weight on Seat Assembly


The final set of results show the effects of adding 60 pounds of additional weight on the seat assembly to increase torque on the motor.



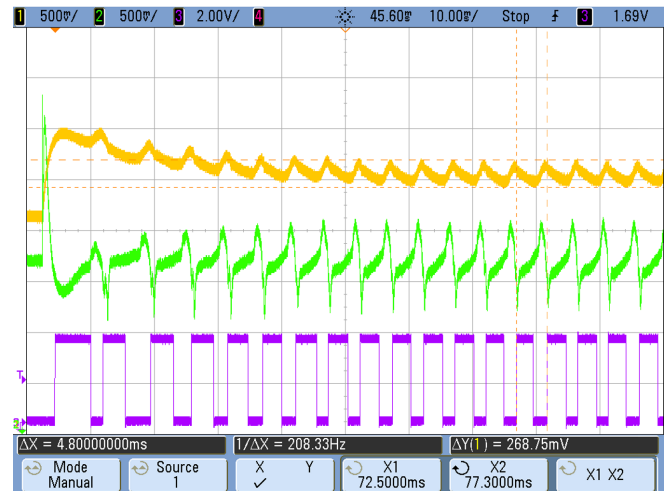17. Forward Motor Operation at 12 V With 60 Pounds of Added Weight



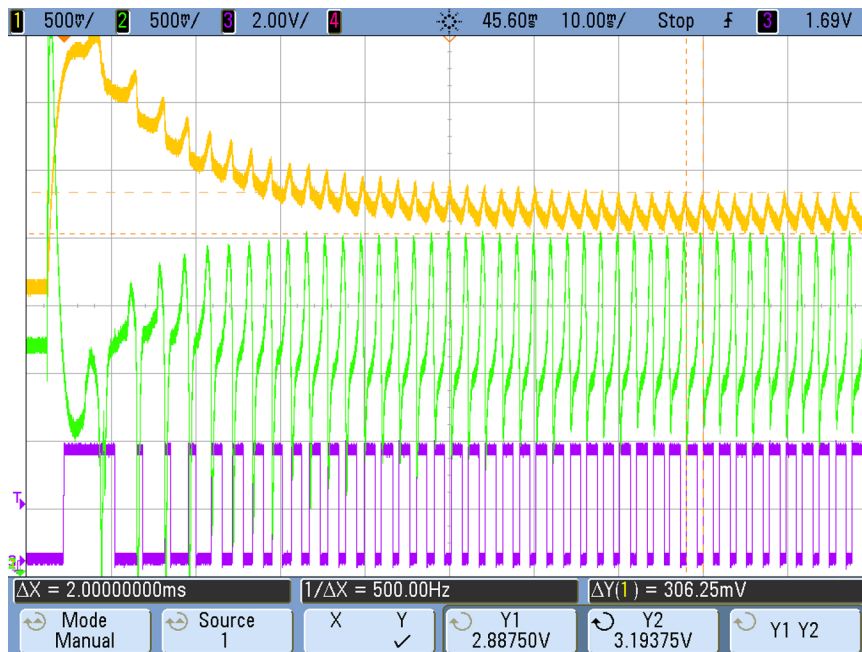18. Forward Motor Operation at 9 V With 60 Pounds of Added Weight



19. Forward Motor Operation at 18 V With 60 Pounds of Added Weight

4.2 Up-Down Motor Operation

4.2.1 Normal 12-V Operation

The initial tests show the performance of the ripple counter when measuring the up-down motor at 12 V.

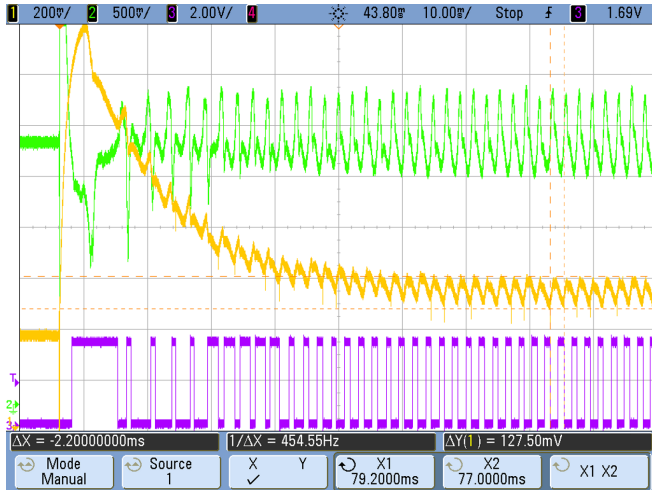


図 20. Upward Motor Operation at 12 V

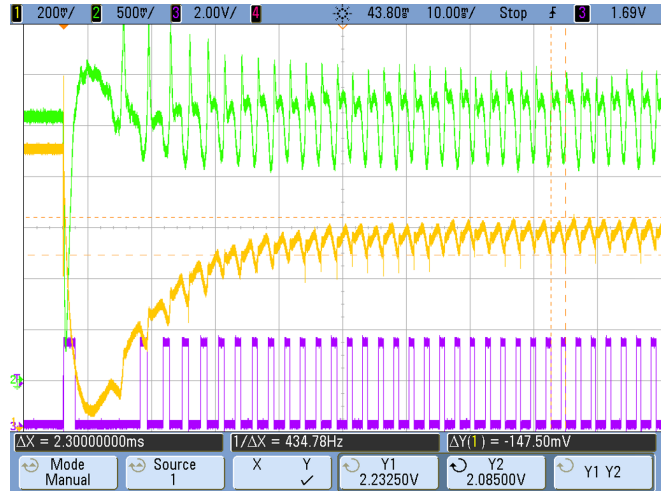


図 21. Downward Motor Operation at 12 V

4.2.2 Operation at 9 V and 18 V

The next set of results show the change in motor speed based on a change in motor supply at 9 V and 18 V.

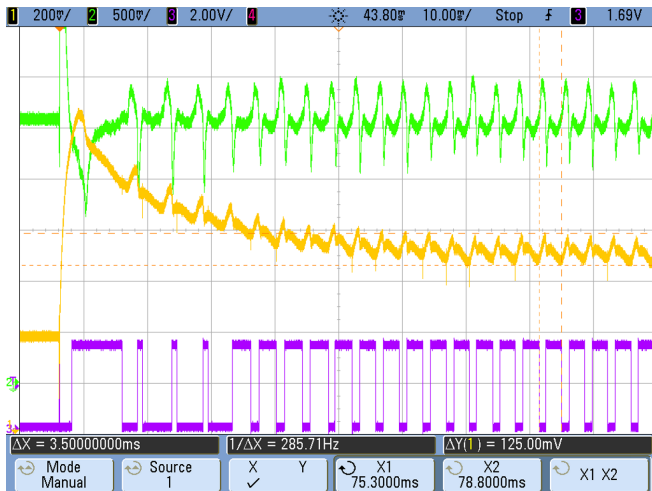


図 22. Upward Motor Operation at 9 V


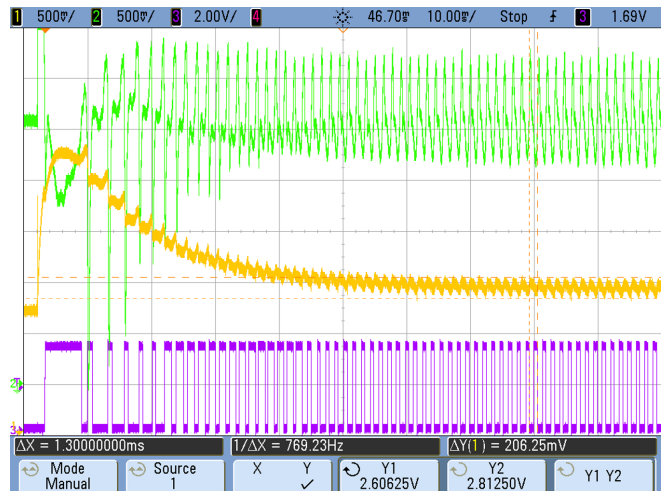



図 23. Upward Motor Operation at 18 V

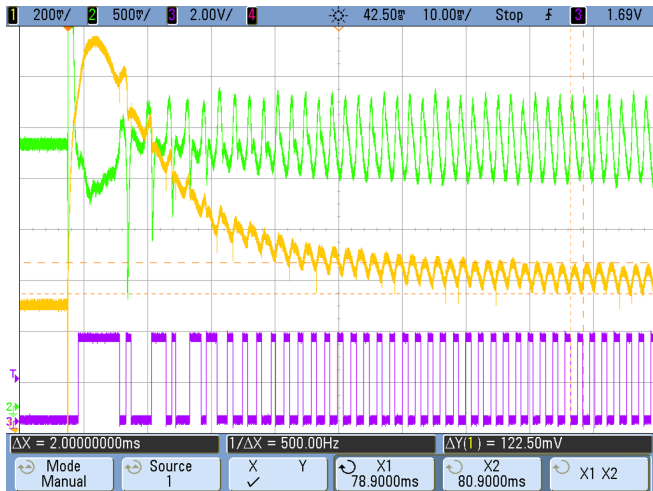4.2.3 Operation With Added Weight on Seat Assembly


The final set of results show the effects of adding 60 pounds of additional weight on the seat assembly to increase torque on the motor.



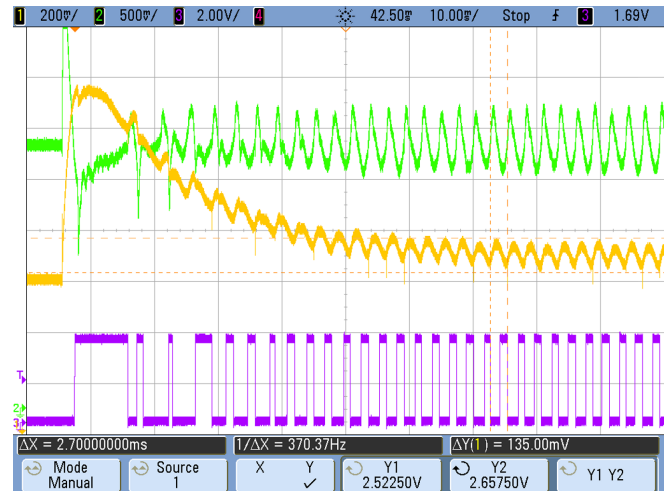24. Upward Motor Operation at 12 V With 60 Pounds of Added Weight



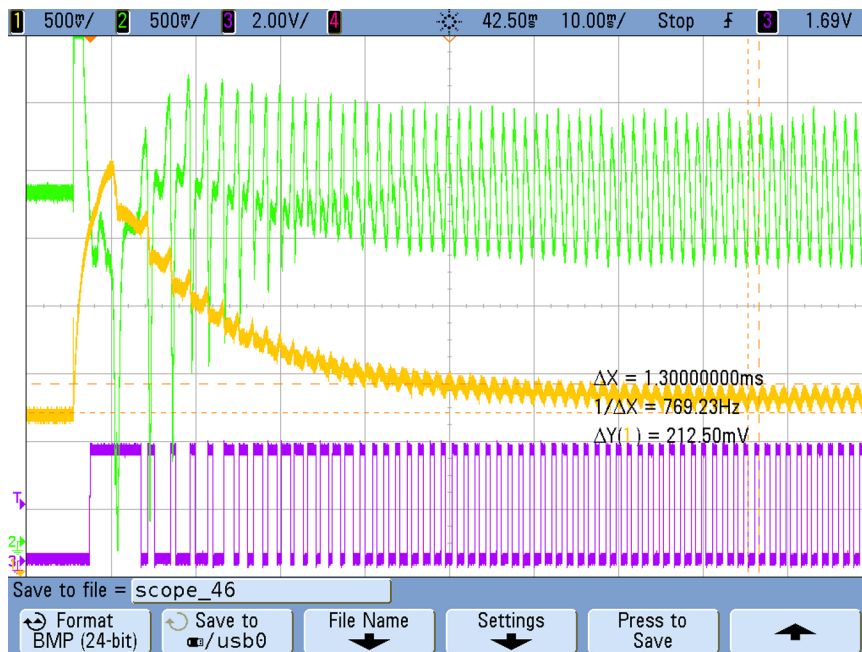25. Upward Motor Operation at 9 V With 60 Pounds of Added Weight



26. Upward Motor Operation at 18 V With 60 Pounds of Added Weight

5 Design Files

5.1 Schematics

To download the schematics, see the design files at [TIDA-01421](#).

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01421](#).

5.3 PCB Layout Recommendations

5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01421](#).

5.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01421](#).

5.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01421](#).

5.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01421](#).

6 Software Files

To download the software files, see the design files at [TIDA-01421](#).

7 商標

MSP430, LaunchPad are trademarks of Texas Instruments.
すべての商標および登録商標はそれぞれの所有者に帰属します。

改訂履歴

資料番号末尾の英字は改訂を表しています。その改訂履歴は英語版に準じています。

2017年7月発行のものから更新

Page

-
- all instances of INA282-Q1 to INA240-Q1 変更 3
-

TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関係する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに合意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任がお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的での、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または黙示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジーまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものでもありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、もしくは、TIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的にかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、続発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する黙示の保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁済または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際の、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知らされていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかったために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/sampterms.htm>)についてのTIの標準条項が含まれますが、これらに限られません。