

TI Designs: TIDA-01608

シャント抵抗とI²Cインターフェイスを内蔵した絶縁電流検出のリファレンス・デザイン



概要

この検証済みのデザインは、数百ボルトを搬送するバス上の電流を正確に測定できます。このデザインは、広い高電圧入力範囲の要件から、太陽光およびサーバー・アプリケーションを対象としています。このデザインは、INA260電流シャント・モニタと内蔵のシャント抵抗を使用して電流を測定し、2つのP82B96双方向バッファを使用してI²C通信を実行し、ISOW7842を使用して絶縁電流測定を行います。INA260は同相電圧が36Vに制限されているため、ISOW7842を使用してデザインのINA260側をフロートさせ、高いバス電圧を測定できるようにしています。

リソース

TIDA-01608	デザイン・フォルダ
INA260	プロダクト・フォルダ
ISOW7842	プロダクト・フォルダ
P82B96	プロダクト・フォルダ

特長



- 高電圧バス(±1kV)の電流測定
- 絶縁電力
- I²Cとの互換性
- マイクロコントローラへの強化デジタルI²C絶縁
- 1%のシステム精度

アプリケーション

- 太陽光インバータ
- ソーラー・コンバイナー・ボックス
- サーバー電源
- サーバー・インフラストラクチャ



[E2Eエキスパートに質問](#)

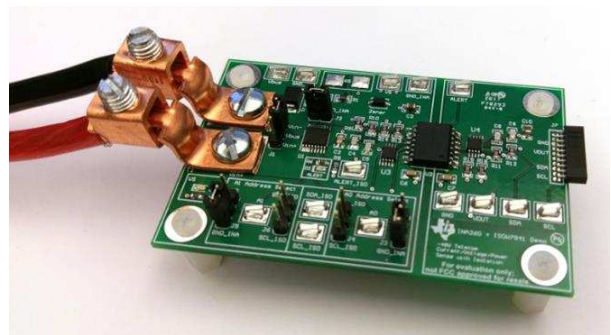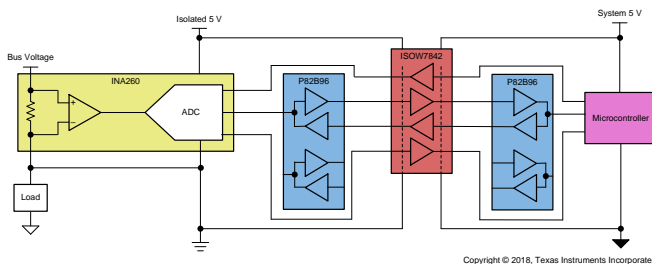

使用許可、知的財産、その他免責事項は、最終ページにあるIMPORTANT NOTICE(重要な注意事項)をご参照くださいますようお願いいたします。英語版のTI製品についての情報を翻訳したこの資料は、製品の概要を確認する目的で便宜的に提供しているものです。該当する正式な英語版の最新情報は、www.ti.comで閲覧でき、その内容が常に優先されます。TIでは翻訳の正確性および妥当性につきましては一切保証いたしません。実際の設計などの前には、必ず最新版の英語版をご参照くださいますようお願いいたします。

1 System Description

At the time of this writing, TI current shunt monitors can only measure high-side configured bus voltages up to 80 V and down to –16 V. Measurement of a bus voltage beyond these ranges requires a difference amplifier solution, low-side implementation, or isolated amplifiers. The goal of this reference design is to provide a solution to measure current and power on high-voltage buses with high accuracy without the need for more expensive isolated topologies. Some of the applications that can benefit from this design are solar energy and servers.

With the rapid worldwide market growth in solar energy, innovation continues to drive inverter design. Modern inverters must have a proven reliability across various grid types, while increasing conversion efficiency and integrating new safety and control features. Photovoltaic (PV) installations tied to the grid are usually built with arrays of modules connected in series to string inverters. For large-array installations with a capacity greater than 10 kW, a solar central inverter performs the conversion of the variable DC power of the PV cells to AC power. Multiple string inputs are combined at the DC input of the central inverter. After the DC combination, each combined input proceeds through voltage and current sensing subsystems, individual DC/DC converters, and individual DC/AC converters. For PV arrays with a power capacity greater than 50 kW, combining the PV strings into a high-voltage DC bus before the inverter is necessary. This system is known as a solar combiner box. This reference design lets designers evaluate the current on this high-voltage DC bus, and it can be used as reference for solar combiner box applications.

A server computer is a computing system designated to run a specific application or applications for extended periods of time and often with minimal human interference. Although servers can be built from commodity computer components, dedicated servers use specialized hardware for optimal reliability. Special, redundant, uninterruptible power supplies are required to ensure no loss of data is experienced during a power failure. The isolated DC/DC power stage of the server power supply is the main power converter stage. This stage is required to convert the high-voltage DC bus obtained at the output of power factor correction (PFC) to the usable 12- or 48-V (or other) output. This power stage is capable of handling a wide input range and delivering consistent high power at a high efficiency. This reference design assists designers with evaluating the power efficiency of their application.

1.1 Key System Specifications


表 1. Key System Specifications

PARAMETER	DESCRIPTION	SPECIFICATIONS
Bus voltage	Working bus voltage range	±1 kV
Isolation	Isolation capability range	≥ 1 kV
Measurements	What the system can measure and report	Shunt voltage and current
Communication	System communication protocol	I ² C compatible
Operating temperature	–40°C to 85°C (limited by P82B96 operating range)	–40°C to 85°C (limited by P82B96 operating range)
INA260 accuracy	Current shunt monitor accuracy	±1% error

2 System Overview

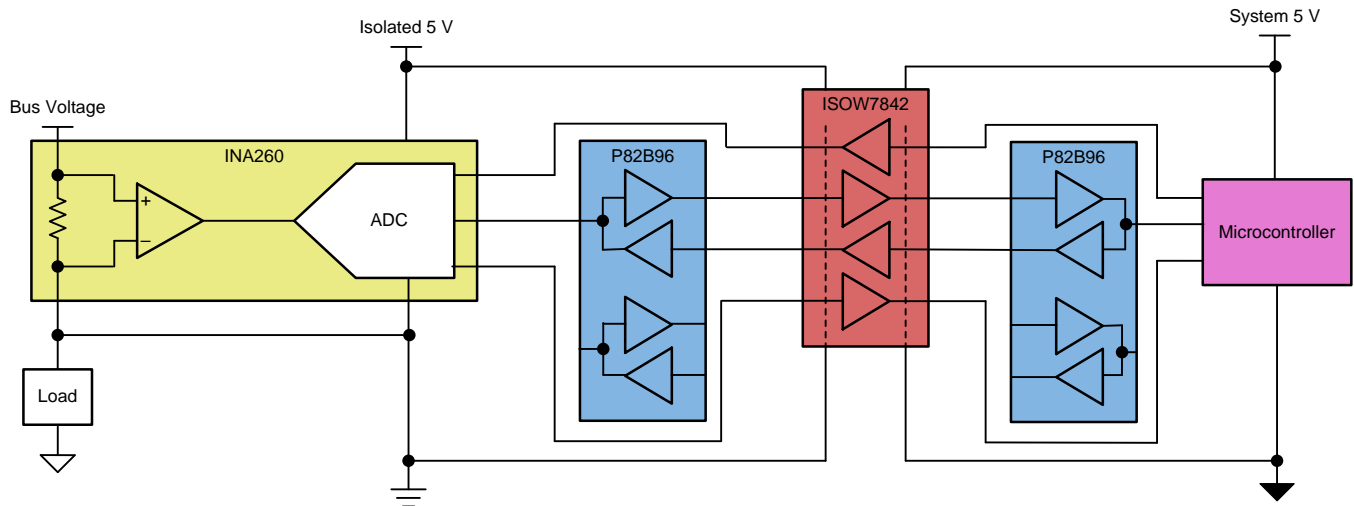2.1 Block Diagram

shows the basic block diagram of the design, which comprises four stages. The first stage (yellow) uses a current shunt monitor, INA260, to measure the load current. The second stage (red) uses a digital isolator, ISOW7842, to provide the required 1-kV working voltage isolation between the current sensing circuit and the MCU. The third stage (blue) incorporates two bus buffer devices, P82B96. These devices support bidirectional data transfer between the I²C bus at different voltage levels. The fourth stage (pink) uses the TI SM-USB-DIG Platform and INA260EVM software to display the data collected by the INA260 device.



Copyright © 2018, Texas Instruments Incorporated

図 1. TIDA-01068 Block Diagram

2.2 Highlighted Products

2.2.1 INA260

The INA260 is a digital-output, current, power, and voltage monitor with an I²C- and SMBus™-compatible interface with an integrated precision shunt resistor. This monitor enables high-accuracy current and power measurements and overcurrent detection at common-mode voltages that can vary from 0 V to 36 V, independent of the supply voltage. The device is a bidirectional, low- or high-side, current-shunt monitor that measures current flowing through the internal current-sensing resistor. The integration of the precision current-sensing resistor provides calibration-equivalent measurement accuracy with ultra-low temperature drift performance and ensures that an optimized Kelvin layout for the sensing resistor is always obtained. The INA260 features up to 16 programmable addresses on the I²C-compatible interface. The digital interface allows programmable alert thresholds, analog-to-digital converter (ADC) conversion times, and averaging. To facilitate ease of use, an internal multiplier enables direct readouts of current in amperes and power in watts. The device operates from a single 2.7-V to 5.5-V supply, drawing 310 μA (typical) of supply current. The INA260 is specified over the operating temperature range between -40°C and +125°C and is available in the 16-pin TSSOP package.

2.2.2 ISOW7842

The ISOW784x is a family of high-performance, quad-channel reinforced digital isolators with an integrated high-efficiency power converter. The integrated DC/DC converter provides up to 650 mW of isolated power at high efficiency and can be configured for various input and output voltage configurations. These devices eliminate the need for a separate isolated power supply in space-constrained isolated designs. The ISOW784x family of devices provide high electromagnetic immunity and low emissions while isolating CMOS or LVCMOS digital I/Os. The signal-isolation channel has a logic input and output buffer separated by a silicon dioxide (SiO₂) insulation barrier, whereas, power isolation uses on-chip transformers separated by thin film polymer as insulating material. Various configurations of forward and reverse channels are available. If the input signal is lost, the default output is high for the ISOW784x devices and low for the devices with the F suffix. These devices help prevent noise currents on a data bus or other circuits from entering the local ground and interfering with or damaging sensitive circuitry. Through innovative chip design and layout techniques, electromagnetic compatibility of the ISOW784x family of devices has been significantly enhanced to ease system-level electrostatic discharge (ESD), electrical fast transient (EFT), surge, and emissions compliance. The high efficiency of the power converter allows operation at a higher ambient temperature. The ISOW784x family of devices is available in a 16-pin SOIC wide-body (SOIC-WB) DWE package.

2.2.3 P82B96

The P82B96 device is a bus buffer that supports bidirectional data transfer between an I²C bus and a range of other bus configurations with different voltage and current levels. One of the advantages of the P82B96 is that it supports longer cables or traces and allows for more devices per I²C bus because it can isolate bus capacitance such that the total loading (devices and trace lengths) of the new bus or remote I²C nodes are not apparent to other I²C buses (or nodes). The restrictions on the number of I²C devices in a system due to capacitance, or the physical separation between them, are greatly improved.

2.3 System Design Theory

2.3.1 First Stage: Current Sensing

This reference design requires the use of a current shunt monitor with a wide common-mode range; high accuracy; ability to report current; and the capability to perform I²C interface communication. The chosen current shunt monitor for this application is INA260. This device not only has the accuracy to achieve the design goals, but also features a precise, low-drift, 2-mΩ internal current-sensing resistor to allow for precision measurements. The integrated current-sensing resistor ensures measurement stability over temperature as well as simplifying printed-circuit board (PCB) layout difficulties common in high-precision, current-sensing measurements. The INA260 is internally calibrated to ensure that the current-sensing resistor and current-sensing amplifier are both precisely matched to one another. For this application, the shunt resistor is on the high side of the load, and directly measures the current flowing into the load from each input.

The INA260 functions as a digital current and power monitor when the circuit is designed such that the voltage on the bus is measured with respect to load ground, because load current \times bus voltage = power. However, the INA260 silicon only supports 36 V on the bus voltage input; so, the device cannot directly measure higher voltages for the power calculation. A resistor divider can occasionally be used to obtain a divided-down bus voltage measurement (as is the case in [TIDA-00313](#)) so that the power can be calculated and linearly scaled back up by the I²C master microprocessor. An example of operation would be measuring a 100-V bus rail, divided down by a series of 300-k Ω and 100-k Ω resistors to effectively reduce the bus voltage by a factor of 4, so that the 100-V rail would measure as 25 V, which is beneath the 36-V silicon limit.

Use of this resistor divider for measurement also requires that the integrated shunt resistor be placed in the low-side configuration, wherein the INA260 device ground and the load ground are connected, and the shunt is between the load and the ground. For reference, a high-side-connected shunt would be placed between the bus rail and the load. There are reasons to do both high- and low-side implementations and one of the drawbacks of using a low-side configuration is that the load is not directly grounded. This reference design uses a low-side implementation with a key adjustment—the shunt is placed on the high side of the INA260 and the device ground is attached to IN–, between the shunt and the load. Normally, this configuration does not work because the system grounds are eventually connected, and at that point, both sides of the load would be shorted to the same node and the circuit would not function. In this design, adding the ISOW7842 creates an isolation barrier with a generated, isolated-supply voltage to power the INA260 device. Because of this isolation, the device ground and load ground are no longer connected together elsewhere on the board, and the circuit continues to operate as expected.

2.3.2 Second Stage: Digital Isolation

This reference design requires that a device provide up to 1.0-kV isolation between the current sense amplifier and the MCU because the INA260 bus voltage is limited from 0 V to 36 V. The chosen digital isolator is ISOW7842. Using the ISOW7842 allows the designer to essentially float the INA260 side of the design, which facilitates isolated current measurement. Because the supply for the INA260 is generated by the ISOW7842, the circuit is not that different from a digital multimeter being powered by a battery, which can be inserted into a circuit to measure current at various voltage levels regardless of the system ground. The isolation of the ISOW7842 is not infinite, but rather limited by the size of the package and the breakdown voltage of air. A good general rule is that, for each millimeter of separation, the gap can isolate a transient voltage of 1 kV. This fact means that the air in a 1-mm gap between two conductors breaks down and conducts when the difference in potentials is 1 kV. A 2-mm gap requires a 2-kV surge to break down, and so forth. The minimum dimensions of the ISOW7842 package allow for, at most, a 8-mm gap; so this circuit can survive a surge of up to 8 kV.

Transient survivability and working voltages are not the same; the working voltage is substantially lower than the allowable transient. A circuit must be designed with attention to both creepage and clearance distances to provide good isolation. Clearance is essentially the shortest distance through the air between two conductors. Creepage is more planar because it is the shortest distance along the surface of a solid, insulating material (like a PCB), between two conductors. The creepage will always be equal to or less than the clearance, depending on the packaging of components in a circuit. Creepage can be artificially increased by adding a slot or hole between the conductors, which creates a longer path along the surface for current to travel. However, the clearance can only be increased by adding more non-air, insulating material between the conductors. This design provides 8 mm of clearance. For more information on this PCB layout, see [5.3](#).

2.3.3 Third Stage: I²C Buffers

This design requires a bus buffer that supports bidirectional data transfer between the MCU (and I²C master) and the ISOW7842 and between the INA260 and the ISOW7842. The P82B96 is the device chosen for this task. The device operates from 2 V to 15 V and provides an excellent way to convert the bidirectional SDA signal into two opposing unidirectional signals to transmit data across the ISOW7842 barrier device. The SCL line is unidirectional and is sourced only by the I²C master, and the INA260 ALERT signal is sourced only by the INA260, so additional bidirectional signal path conversions are not required, which is why the second signal converter on the P82B96 is not used in this design. The SCL and ALERT signals transmit across the barrier device directly.

2.3.4 Fourth Stage: TI SM-USB-DIG Platform and INA260EVM Software

The SM-USB-DIG platform is a general-purpose data acquisition system that is used on several different TI evaluation modules and designs. The primary control device of the SM-USB-DIG platform is the TUSB3210. The TUSB3210 is an 8052 MCU that has a built-in USB interface. The MCU receives information from the host computer that it interprets into power, I²C, serial peripheral interface (SPI), and other digital input and output (I/O) patterns. During the digital I/O transaction, the MCU reads the response of any device connected to the I/O interface. The response from the device is sent back to the PC, where it is interpreted by the host computer. The software used to read the current measurements is the INA260EVM software.

3 Hardware, Software, Testing Requirements, and Test Results

3.1 Required Hardware and Software

3.1.1 Hardware

The contents of the reference design kit are as follows:

- TIDA-01608 board
- USB SM-DIG Platform PCB
- USB extender cable

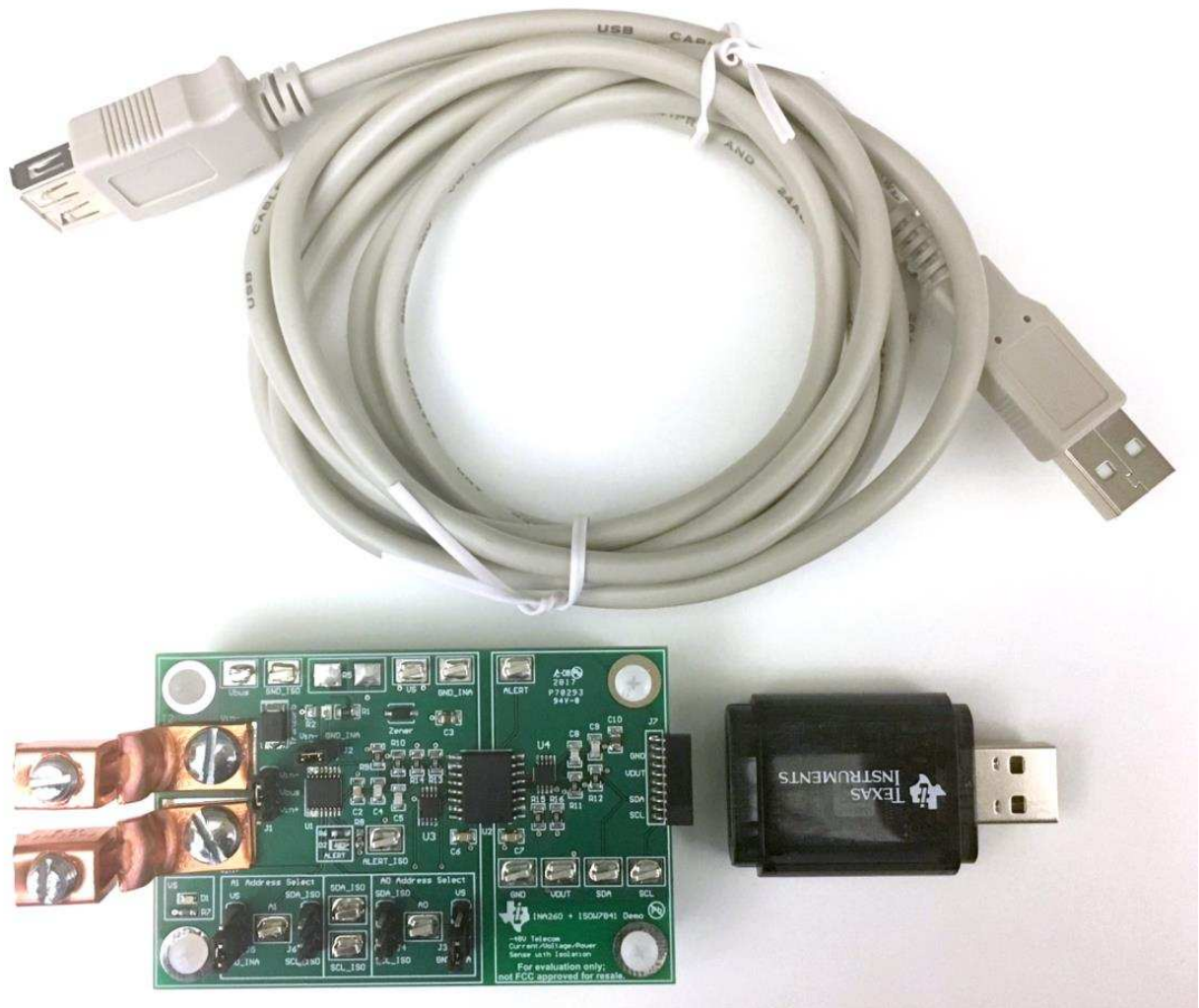


図 2. Required Hardware for TIDA-01608 Evaluation

3.1.2 Software

The INA260EVM GUI and TI SM-USB-DIG are used to interpret the data output from the board. For more information on how to use the INA260EVM software, see [INA260EVM-PDK User's Guide](#).


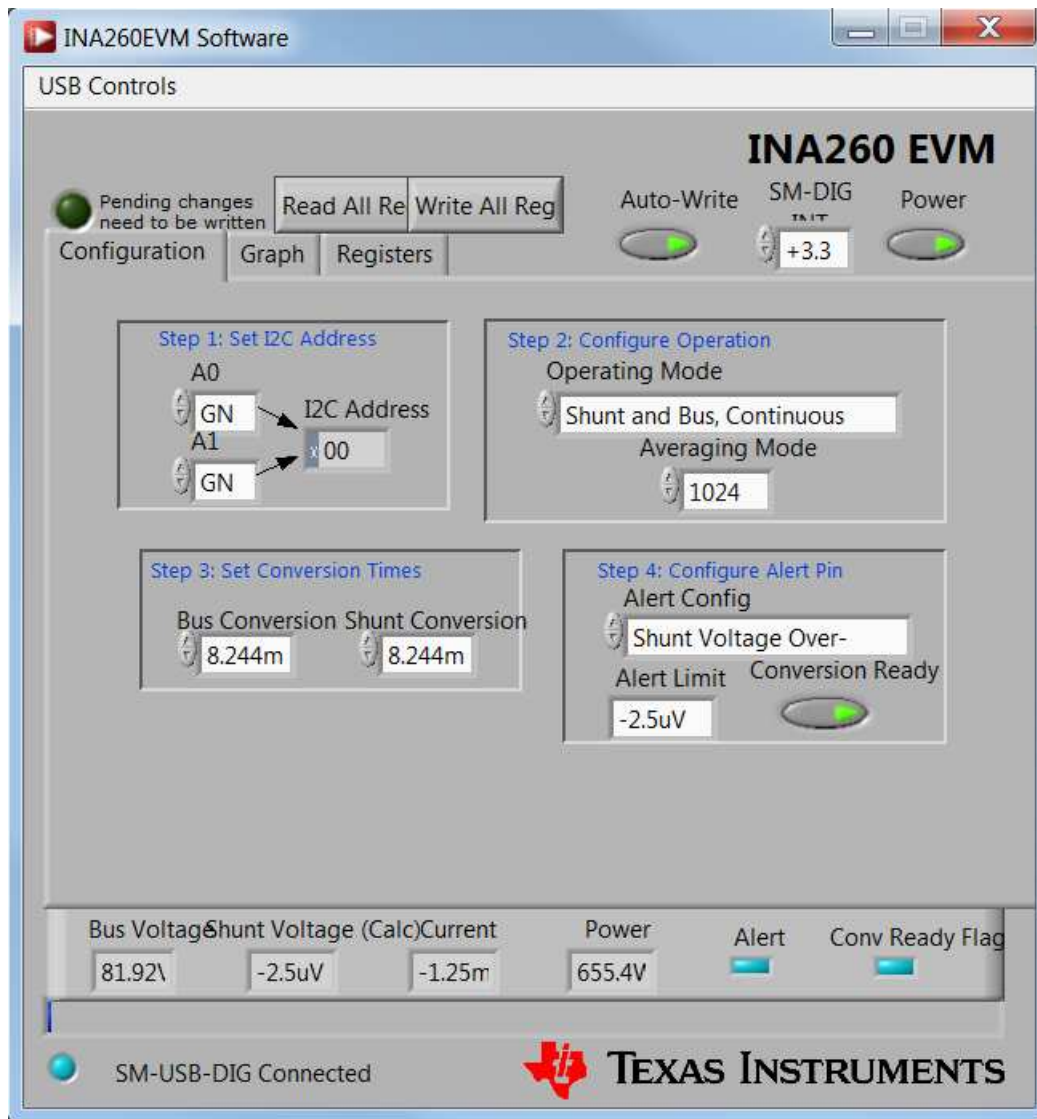


図 3. INA260EVM GUI

4 Testing and Results

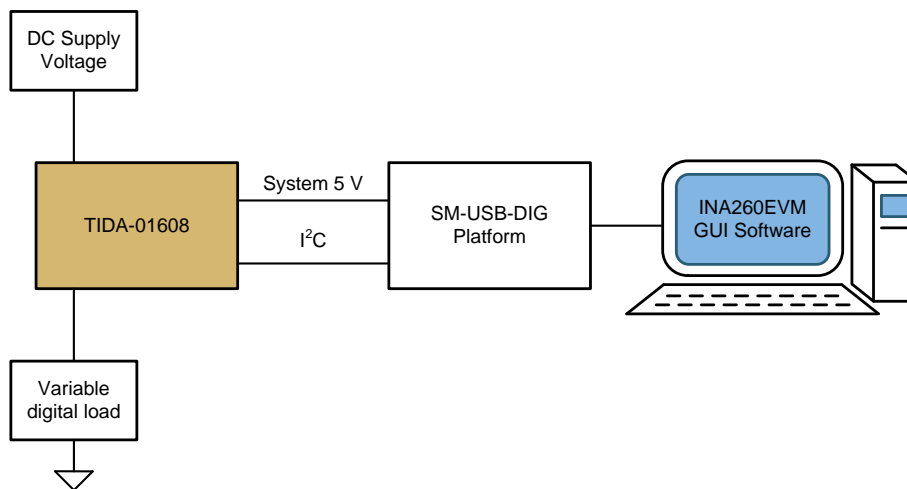4.1 Test Setup

A power supply (E3612A) and a variable digital load (PLZ334W) were used to simulate the DC bus connected to a load. The DC voltage was connected to the T1 terminal (VIN+) and the variable digital load was connected to the T2 terminal (VIN-) of the TIDA-01608 board. The TI SM-USB-DIG provides the 5-V supply voltage to power the TIDA-01608 board. The INA260EVM GUI software is used to collect the sensed current data and a DC multimeter is used to monitor the DC voltage corresponding to the voltage sense measurement. 図 4 shows a block diagram of the test setup. Due to limitations of the equipment, the full ± 1 -kV capable range of this design was not tested; a range from 1 V to 120 V was used for concept validation.



Copyright © 2018, Texas Instruments Incorporated

図 4. Test Setup

4.2 Test Results

4.2.1 Data Collected With Common-Mode Voltage $V_{CM} = 60$ V and Load Current $I_L = 50$ mA to 500 mA

For this test, the data was collected by sweeping the load current from 0 mA to 500 mA with a constant supply voltage of 60 V. The load current value was compared to the current value read by the INA260EVM software. 表 2 shows the collected data.

表 2. $V_{CM} = 60$ V, Load Current $I_L = 50$ mA to 500 mA

VOLTAGE (V)	NOMINAL CURRENT (A)	ACTUAL CURRENT (A)	CURRENT MEASURED GUI (A)	ERROR (%)
60	0.050	0.0540	0.0538	0.4630
60	0.100	0.1020	0.1023	0.2941
60	0.150	0.1530	0.1525	0.3268
60	0.200	0.2040	0.2034	0.2941
60	0.250	0.2540	0.2533	0.2756
60	0.300	0.3040	0.3032	0.2632
60	0.350	0.3540	0.3530	0.2825
60	0.400	0.4040	0.4029	0.2723
60	0.450	0.4560	0.4548	0.2632
60	0.500	0.5000	0.5012	0.2400

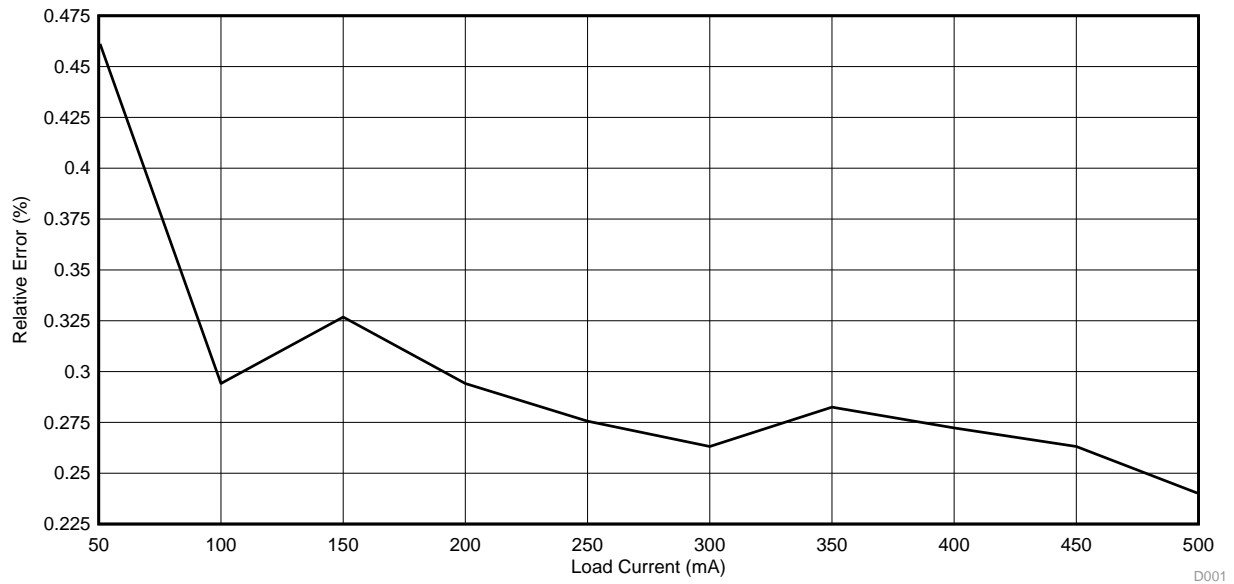


図 5. Measured Relative Error With $V_{CM} = 60V$, Load Current $I_L = 50 \text{ mA}$ to 500 mA

4.2.2 Data Collected With Common-Mode Voltage $V_{CM} = 120 \text{ V}$ and Load current $I_L = 50 \text{ mA}$ to 250 mA

For this test, the data was collected by sweeping the load current from 0 mA to 250 mA with a constant supply voltage of 120 V. The load current value was compared to the current value read by the INA260EVM software. 表 3 shows the collected data.

表 3. $V_{CM} = 120 \text{ V}$, Load Current $I_L = 50 \text{ mA}$ to 250 mA

VOLTAGE (V)	NOMINAL CURRENT (A)	ACTUAL CURRENT (A)	CURRENT MEASURED GUI (A)	ERROR (%)
120	0.025	0.0260	0.02625	0.9615
120	0.050	0.0540	0.05375	0.4630
120	0.075	0.07625	0.07625	0.3289
120	0.100	0.1040	0.10380	0.1923
120	0.125	0.1260	0.12500	0.7937
120	0.150	0.1490	0.14870	0.2013
120	0.175	0.176	0.17620	0.1136
120	0.200	0.2030	0.20360	0.29557
120	0.225	0.2260	0.22630	0.1327
120	0.250	0.2490	0.24870	0.1205

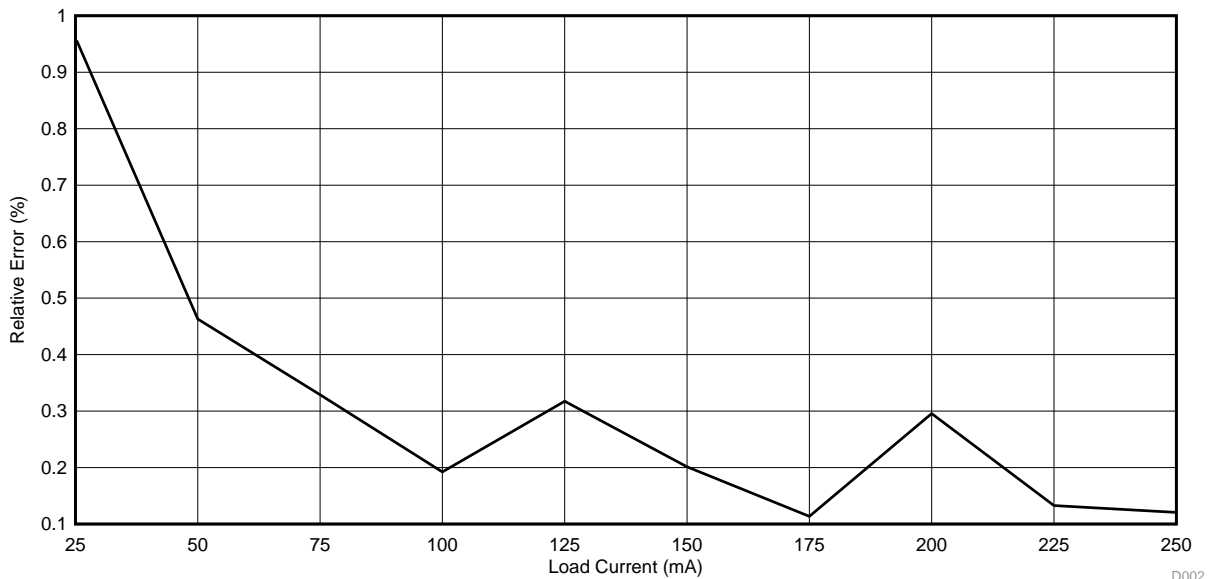



図 6. Measured Relative Error With $V_{CM} = 120\text{ V}$, Load Current $I_L = 50\text{ mA}$ to 250 mA

4.2.3 Data Collected With Common-Mode Voltage $V_{CM} = 1\text{ V}$ and Load Current $I_L = 1\text{ A}$ to 15 A

The data was collected by sweeping the load current from 0 A to 15 A with a constant supply voltage of 1 V. The load current value was compared to the current value read by the INA260EVM software. 表 4 shows the collected data.

表 4. $V_{CM} = 1\text{ V}$ and Load Current $I_L = 1\text{ A}$ to 15 A

VOLTAGE (V)	NOMINAL CURRENT (A)	ACTUAL CURRENT (A)	CURRENT MEASURED GUI (A)	ERROR (%)
1	1	1.00300	1.002	0.0997
1	2	2.00500	2.007	0.0998
1	3	3.00040	2.998	0.0800
1	4	3.99992	3.996	0.0980
1	5	4.9998	4.995	0.0960
1	6	6.00000	5.994	0.1000
1	7	7.00000	6.994	0.0857
1	8	8.00000	7.993	0.0875
1	9	9.00020	8.992	0.0911
1	10	10.00080	9.992	0.0880
1	11	11.00100	10.99	0.0100
1	12	12.00100	11.99	0.0917
1	13	13.00200	12.99	0.0923
1	14	14.00260	13.99	0.0900
1	15	15.00380	14.98	0.1920

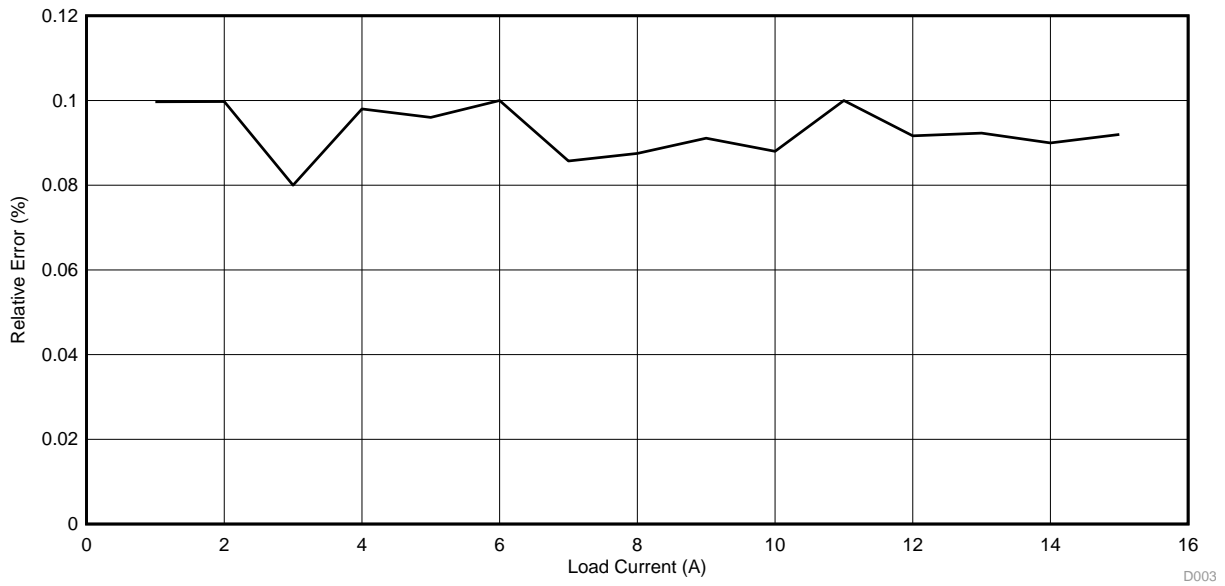

☒ 7. Measured Relative Error With $V_{CM} = 1\text{ V}$ and Load Current $I_L = 1\text{ A}$ to 15 A

5 Design Files

5.1 Schematics

To download the schematics, see the design files at [TIDA-01608](#) .

5.2 Bill of Materials

To download the bill of materials (BOM), see the design files at [TIDA-01608](#) .

5.3 PCB Layout Recommendations

Design for isolation requires attention to the clearance between low and high voltages on the PCB. With this layout, the ISOW7842 straddles the isolation barrier. The pins on the body of the package are the closest conductors with the highest voltage potential difference, which is 8 mm. The breakdown of air is 1 kV/mm, so for high-voltage surges, the isolation level is 8 kV. For continuous working voltage levels, the maximum potential difference with an 8-mm separation is only 1414 V at DC.

If the planes under the ISOW7842 device come closer together than the pins, then this voltage level is reduced. For example, a 3-mm gap would only survive a surge of 3 kV and would only support a continuous working voltage of 424 V at DC.

5.3.1 Layout Prints

To download the layer plots, see the design files at [TIDA-01608](#) .

5.4 Altium Project

To download the Altium project files, see the design files at [TIDA-01608](#) .

5.5 Gerber Files

To download the Gerber files, see the design files at [TIDA-01608](#) .

5.6 Assembly Drawings

To download the assembly drawings, see the design files at [TIDA-01608](#) .

6 Software Files

To download the software files, see the design files at [TIDA-01608](#) .

7 Related Documentation

1. Texas Instruments, [-48-V Telecom Current, Voltage, and Power Sense With Isolation Reference Design](#)
2. Texas Instruments, [Reference Design for 1200-V, Isolated, I2C, High-Side Current Sensing](#)
3. Texas Instruments, [600-V Unidirectional Curr/Volt/Power Monitoring for Solar Smart Combiner Box](#)
4. Texas Instruments, [INA260EVM-PDK User's Guide](#)

7.1 商標

SMBus is a trademark of Intel Corporation.

8 About the Authors

JASON BRIDGMON, MAYRIM VERDEJO, and MITCH MORSE are Applications Engineers at Texas Instruments (TI), where they work primarily with current and magnetic sensing products. Jason received bachelor of science degrees in electrical and computer engineering at the University of Denver. Mayrim received her bachelor of science degree from the University of Puerto Rico, Mayagüez with an emphasis on digital signal processing. Mitch received his bachelor's degree from Utah State University in Electrical Engineering.

TIの設計情報およびリソースに関する重要な注意事項

Texas Instruments Incorporated ("TI")の技術、アプリケーションその他設計に関する助言、サービスまたは情報は、TI製品を組み込んだアプリケーションを開発する設計者に役立つことを目的として提供するものです。これにはリファレンス設計や、評価モジュールに関係する資料が含まれますが、これらに限られません。以下、これらを総称して「TIリソース」と呼びます。いかなる方法であっても、TIリソースのいずれかをダウンロード、アクセス、または使用した場合、お客様(個人、または会社を代表している場合にはお客様の会社)は、これらのリソースをここに記載された目的にのみ使用し、この注意事項の条項に従うことに合意したものとします。

TIによるTIリソースの提供は、TI製品に対する該当の発行済み保証事項または免責事項を拡張またはいかなる形でも変更するものではなく、これらのTIリソースを提供することによって、TIにはいかなる追加義務も責任も発生しないものとします。TIは、自社のTIリソースに訂正、拡張、改良、およびその他の変更を加える権利を留保します。

お客様は、自らのアプリケーションの設計において、ご自身が独自に分析、評価、判断を行う責任がお客様にあり、お客様のアプリケーション(および、お客様のアプリケーションに使用されるすべてのTI製品)の安全性、および該当するすべての規制、法、その他適用される要件への遵守を保証するすべての責任をお客様のみが負うことを理解し、合意するものとします。お客様は、自身のアプリケーションに関して、(1) 故障による危険な結果を予測し、(2) 障害とその結果を監視し、および、(3) 損害を引き起こす障害の可能性を減らし、適切な対策を行う目的での、安全策を開発し実装するために必要な、すべての技術を保持していることを表明するものとします。お客様は、TI製品を含むアプリケーションを使用または配布する前に、それらのアプリケーション、およびアプリケーションに使用されているTI製品の機能性を完全にテストすることに合意するものとします。TIは、特定のTIリソース用に発行されたドキュメントで明示的に記載されているもの以外のテストを実行していません。

お客様は、個別のTIリソースにつき、当該TIリソースに記載されているTI製品を含むアプリケーションの開発に関連する目的でのみ、使用、コピー、変更することが許可されています。明示的または黙示的を問わず、禁反言の法理その他どのような理由でも、他のTIの知的所有権に対するその他のライセンスは付与されません。また、TIまたは他のいかなる第三者のテクノロジーまたは知的所有権についても、いかなるライセンスも付与されるものではありません。付与されないものには、TI製品またはサービスが使用される組み合わせ、機械、プロセスに関連する特許権、著作権、回路配置利用権、その他の知的所有権が含まれますが、これらに限られません。第三者の製品やサービスに関する、またはそれらを参照する情報は、そのような製品またはサービスを利用するライセンスを構成するものではなく、それらに対する保証または推奨を意味するものでもありません。TIリソースを使用するため、第三者の特許または他の知的所有権に基づく第三者からのライセンス、もしくは、TIの特許または他の知的所有権に基づくTIからのライセンスが必要な場合があります。

TIのリソースは、それに含まれるあらゆる欠陥も含めて、「現状のまま」提供されます。TIは、TIリソースまたはその仕様に関して、明示的か暗黙的にかかわらず、他のいかなる保証または表明も行いません。これには、正確性または完全性、権原、続発性の障害に関する保証、および商品性、特定目的への適合性、第三者の知的所有権の非侵害に対する黙示的保証が含まれますが、これらに限られません。

TIは、いかなる苦情に対しても、お客様への弁済または補償を行う義務はなく、行わないものとします。これには、任意の製品の組み合わせに関連する、またはそれらに基づく侵害の請求も含まれますが、これらに限られず、またその事実についてTIリソースまたは他の場所に記載されているか否かを問わないものとします。いかなる場合も、TIリソースまたはその使用に関連して、またはそれらにより発生した、実際の、直接的、特別、付随的、間接的、懲罰的、偶発的、または、結果的な損害について、そのような損害の可能性についてTIが知らされていたかどうかにかかわらず、TIは責任を負わないものとします。

お客様は、この注意事項の条件および条項に従わなかったために発生した、いかなる損害、コスト、損失、責任からも、TIおよびその代表者を完全に免責するものとします。

この注意事項はTIリソースに適用されます。特定の種類の資料、TI製品、およびサービスの使用および購入については、追加条項が適用されます。これには、半導体製品(<http://www.ti.com/sc/docs/stdterms.htm>)、評価モジュール、およびサンプル(<http://www.ti.com/sc/docs/sampterms.htm>)についてのTIの標準条項が含まれますが、これらに限られません。