

## ***DC-Coupling Between Differential LVPECL, LVDS, HSTL, and CM***

*Kal Mustafa / Chris Sterzik*
*High Performance Analog*

### **ABSTRACT**

This report describes various methods of interfacing different logic levels. The focus is dc-coupling between the following differential signaling: LVPECL (low-voltage positive-referenced emitter coupled logic), LVDS (low-voltage differential signals), HSTL (high-speed transceiver logic), and CML (current-mode logic). The report discusses sixteen various interface cases between the aforementioned differential signaling levels.

### **Contents**

<b>1</b>	<b>AC-Coupling</b> .....	<b>2</b>
	1.1 LVPECL.....	3
	1.2 LVDS .....	7
	1.3 CML .....	11
	1.4 HSTL .....	13
<b>2</b>	<b>References</b> .....	<b>15</b>

### **Figures**


Figure 1.	Input and Output Parameters .....	2
Figure 2.	LVPECL to LVPECL.....	3
Figure 3.	LVPECL to LVPECL.....	4
Figure 4.	LVPECL to LVDS .....	4
Figure 5.	LVPECL to LVDS .....	5
Figure 6.	LVPECL to CML.....	5
Figure 7.	LVPECL to CML Converter .....	6
Figure 8.	LVPECL to HSTL .....	6
Figure 9.	LVDS to LVPECL .....	7
Figure 10.	LVDS to LVPECL .....	8
Figure 11.	LVDS to LVDS Without On-Chip Termination .....	8
Figure 12.	LVDS to LVDS With On-Chip Termination.....	9
Figure 13.	LVDS to CML Converter.....	9
Figure 14.	LVDS to HSTL.....	10
Figure 15.	CML to LVPECL Translator.....	11
Figure 16.	CML to LVDS .....	11
Figure 17.	CML to CML .....	12
Figure 18.	CML to HSTL.....	13
Figure 19.	HSTL to LVPECL Converter.....	13
Figure 20.	HSTL to LVDS.....	14
Figure 21.	HSTL to CML Translator .....	14
Figure 22.	HSTL to HSTL.....	15

### **Tables**

Table 1.	Typical LVPECL, LVDS, HSTL, and CML Outputs.....	2
Table 2.	Typical LVPECL, LVDS, CML, and HSTL Input Levels.....	2
Table 3.	Interface Table.....	3

## 1 AC-Coupling

DC-coupling is used in a system when there is a need for a wide bandwidth, or when dc-unbalanced code is used. Both interfaces must have the same ground potential on the same board or system. DC-coupling directly connects the components together without any coupling capacitors. Among the advantages of dc-coupling are: simple board design, no dc-wander issues, and it is useful in all coded-data streams including SONET and NRZ data applications. One disadvantage of dc-coupling is that it requires careful power supply design. Figure 1, Table 1, and Table 2 provide the I/O levels for these differential signals.

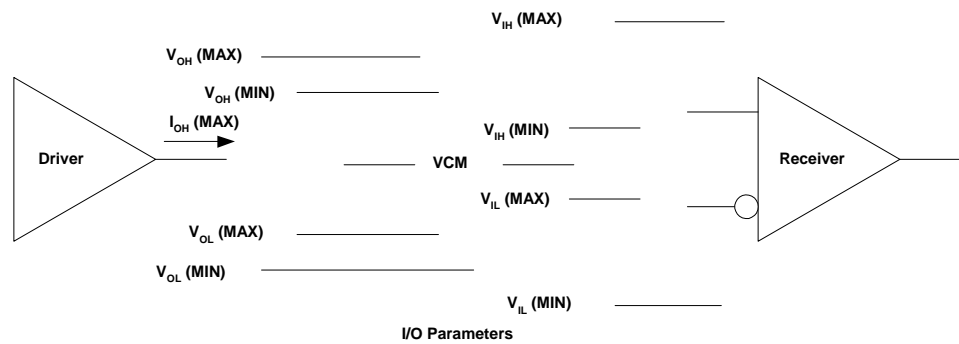

**Figure 1. Input and Output Parameters**

**Table 1. Typical LVPECL, LVDS, HSTL, and CML Outputs**

Output	LVPECL	LVDS	HSTL	CML
$V_{OH}$ (Min)	2.275 V	1.249	$V_{DDQ}^1 - 0.4$	$V_{CC}^2$
$V_{OL}$ (Max)	1.68 V	1.252	0.4	$V_{CC} - 0.4$ V

**Table 2. Typical LVPECL, LVDS, CML, and HSTL Input Levels**

Input	LVPECL	LVDS	HSTL	CML
$V_{IH}$ (Min)	2.135 V	1.249	$V_{Ref} + 0.2$	$V_{CC}$
$V_{Ref}$ or VCM	2	1.2	0.75	$V_{CC} - 0.2$ V
$V_{IL}$ (Max)	1.825 V	1.252	$V_{Ref} - 0.2$	$V_{CC} - 0.4$ V
$V_{ID}$ (Min)	310 mV	200 mV	400 mV	400 mV

<sup>1</sup>  $V_{DDQ} = 1.5$  V  $\pm 10\%$

<sup>2</sup>  $V_{CC} = 3.3$  V  $\pm 10\%$

Table 3. Interface Table

		TO			
FROM		LVPECL	LVDS	CML	HSTL
	LVPECL	See <a href="#">Figure 3</a>	See <a href="#">Figure 4</a> or <a href="#">Figure 5</a>	See <a href="#">Figure 6</a> or <a href="#">Figure 7</a>	See <a href="#">Figure 8</a>
	LVDS	See <a href="#">Figure 9</a> or <a href="#">Figure 10</a>	See <a href="#">Figure 11</a> or <a href="#">Figure 12</a>	See <a href="#">Figure 13</a>	See <a href="#">Figure 14</a>
	CML	See <a href="#">Figure 15</a>	See <a href="#">Figure 16</a> or	See <a href="#">Figure 17</a>	See <a href="#">Figure 18</a>
	HSTL	See <a href="#">Figure 19</a>	See <a href="#">Figure 20</a>	See <a href="#">Figure 21</a>	See <a href="#">Figure 22</a>

### 1.1 LVPECL


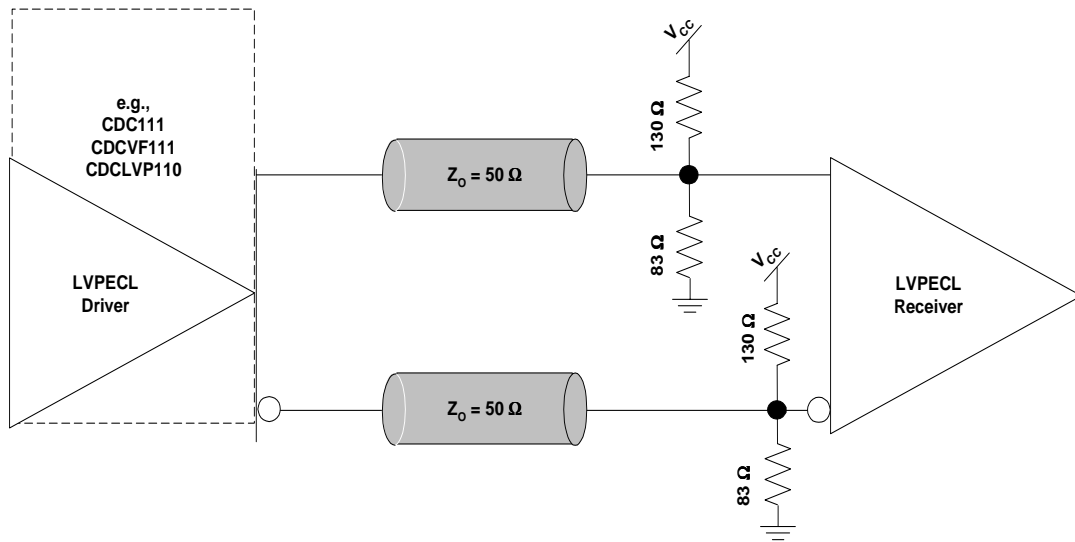



Figure 2. LVPECL to LVPECL

PECL and LVPECL are normally terminated though 50 Ω to (V<sub>CC</sub> - 2 V). Most systems normally do not have dual power supplies of both 3.3 V and 1.3 V; therefore Figures 2 and Figure 3 show alternative methods to terminate LVPECL output signals. The pullup and pulldown combination terminates the 50-Ω transmission line and establish the LVPECL common-mode voltage of 2 V at the receiver.

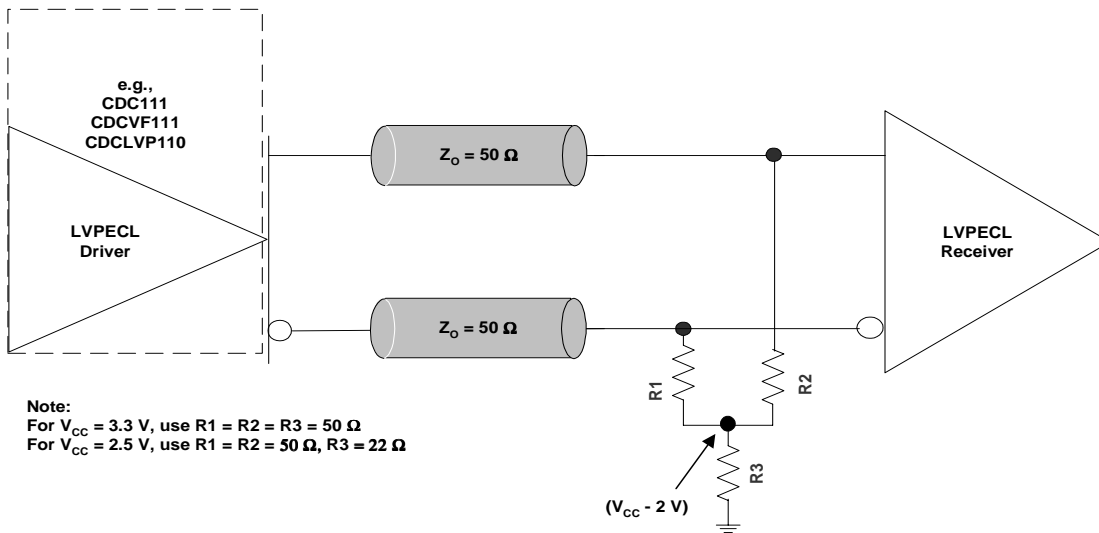

**Figure 3. LVPECL to LVPECL**

The Y-termination in Figure 3 is another alternative to LVPECL termination where a VTT supply is not readily available. This scheme saves one resistor over the scheme in Figure 2.

 

**Figure 4. LVPECL to LVDS**

The  $33\text{-}\Omega$  resistor is usually required when the LVPECL output is too high for the LVDS receiver input stage. For the LVDS receivers listed above, it is not required and Figure 5 is recommended.

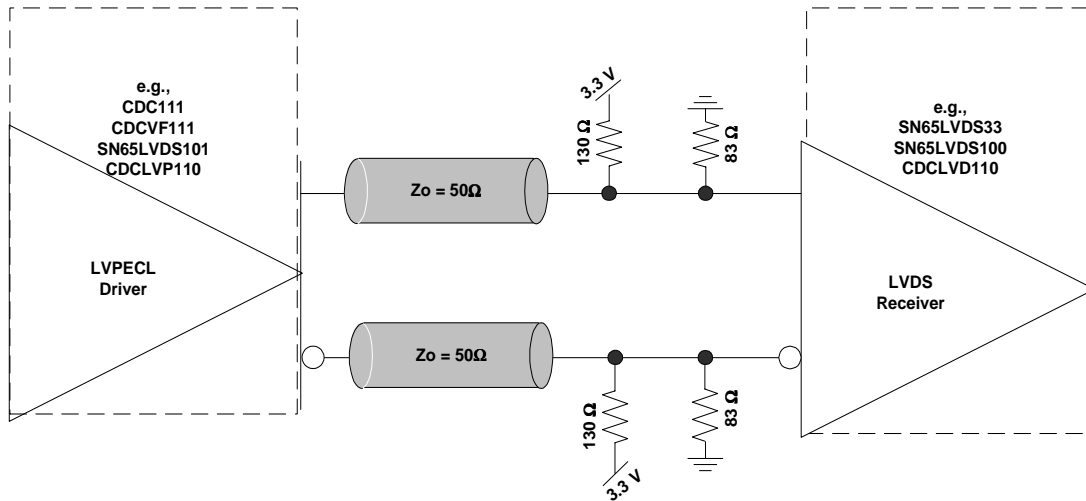


Figure 5. LVPECL to LVDS

Most LVDS receivers are capable of accepting LVPECL signals and it is not necessary to attenuate the LVPECL signal prior to the LVDS receiver. This is due to the wide common-mode range of the LVDS receivers listed above.


 



Figure 6. LVPECL to CML

The most widely used method of translating from LVPECL to CML is through ac-coupling. AC-coupling is recommended for dc-balanced signals. AC-coupling generates base-line wander in high-speed serial data transmission such as SONET and NRZ encoded data (non dc-balanced). Therefore, dc-coupling is recommended for such data streams. For detailed derivation, see the SCAA056.

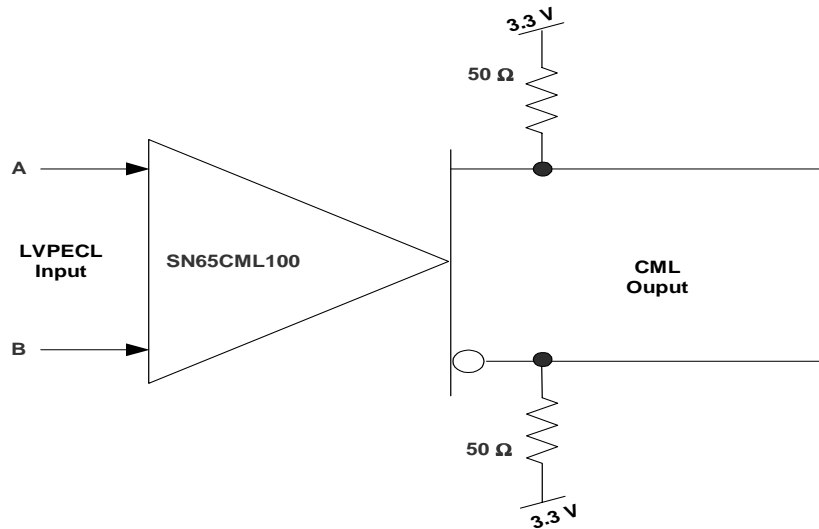

**Figure 7. LVPECL to CML Converter**

 The SN65CML100, in Figure 7, can be used as an LVPECL to CML converter. The 50- $\Omega$  pullup resistors are required to bias the SN65CML100 outputs as well as terminate the transmission line. In most cases, the two 50- $\Omega$  resistors are included in the CML receiver input stage and therefore are not required.




**Note:**  
 For  $V_{CC} = 3.3\text{ V}$ , use  $R1 = 127\ \Omega$ ,  $R2 = 35\ \Omega$ ,  $R3 = 48\ \Omega$   
 For  $V_{CC} = 2.5\text{ V}$ , use  $R1 = 100\ \Omega$ ,  $R2 = 40\ \Omega$ ,  $R3 = 60\ \Omega$

**Figure 8. LVPECL to HSTL**


## 1.2 LVDS

The resistors R1 in parallel with (R2+R3) should match the characteristic impedance ( $Z_o = 50 \Omega$ ) of the transmission line. At point Y in Figure 8, the ratio of R3 to the sum of (R1+R2+R3) should be chosen to set the HSTL common-mode voltage ( $V_{CM} = 0.75 \text{ V}$ ). At point X, the LVPECL common-mode voltage is 2 V, which is the voltage across R1 compared to the sum of all three resistors (R1+ R2+R3).

 


**Figure 9. LVDS to LVPECL**

The Thevenin equivalent of the 83  $\Omega$  and 130  $\Omega$ , in Figure 9, matches the 50- $\Omega$  transmission line impedance as well as sets the common-mode voltage ( $V_{CM} = 2 \text{ V}$ ) for the LVPECL receiver.

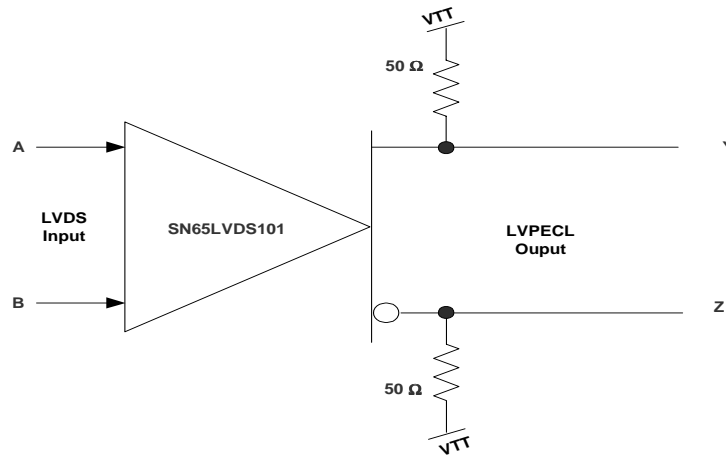

**Figure 10. LVDS to LVPECL**

The SN65LVDS101, in Figure 10, can be used as an LVDS to LVPECL converter. The 50- $\Omega$  pullup resistors are required to bias and terminate the LVPECL outputs to VTT ( $V_{CC} - 2\text{ V}$ ). If the termination voltage, VTT is not available then, the Thevenin equivalent of the 83  $\Omega$  and 130 $\Omega$ , as in Figure 9 is recommended.

 

**Figure 11. LVDS to LVDS Without On-Chip Termination**



Figure 11 is the most commonly used termination for LVDS signals. The 100-Ω external resistor terminates the differential impedance of the transmission line assuming the LVDS receiver does not include an on-chip termination. The designer could also replace the 100-Ω termination with two 50-Ω resistors and tie the mid-point with a capacitor (10 nF) to GND in order to terminate any unbalanced noise within the differential transmission line as well as correct for line-length mismatches.

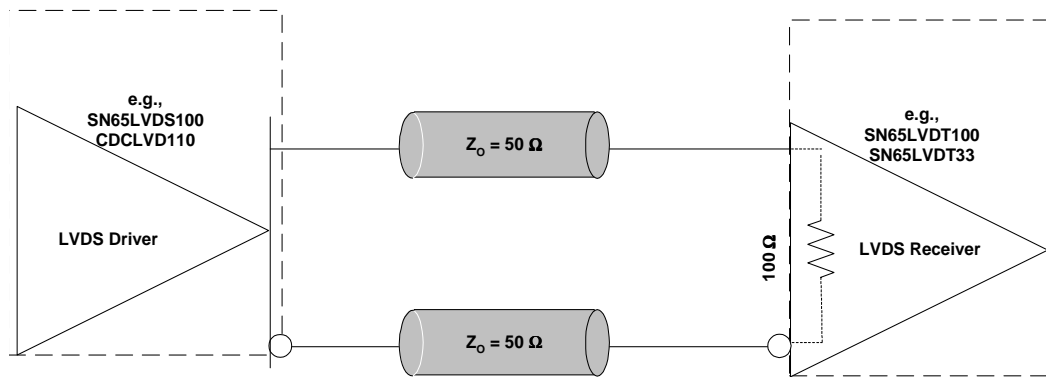


Figure 12. LVDS to LVDS With On-Chip Termination

In Figure 12, the LVDS receiver includes a 100-Ω on-chip resistor; therefore no external termination is needed.


 


Figure 13. LVDS to CML Converter

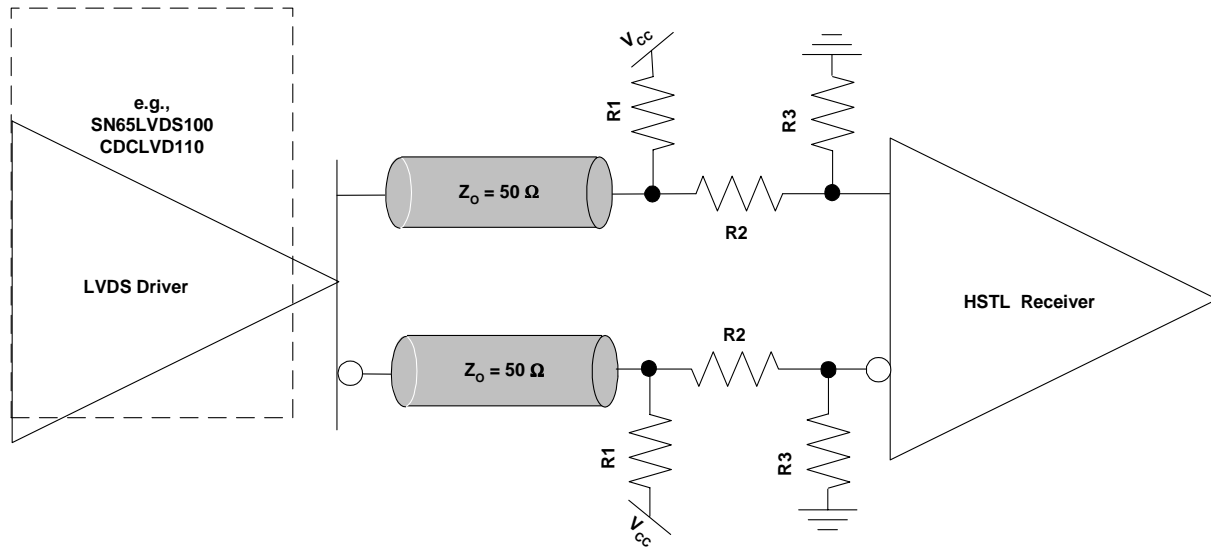Most CML receivers have  $50\ \Omega$  included on their input stage and external termination is not required. The  $50\text{-}\Omega$  pullup resistors are required to bias the SN65CML100 and terminate the transmission line.



**Note:**

For  $V_{CC} = 3.3\ \text{V}$ , use  $R_1 = 140\ \Omega$ ,  $R_2 = 30\ \Omega$ ,  $R_3 = 50\ \Omega$

For  $V_{CC} = 2.5\ \text{V}$ , use  $R_1 = 100\ \Omega$ ,  $R_2 = 36\ \Omega$ ,  $R_3 = 60\ \Omega$

**Figure 14. LVDS to HSTL**

At the output of the LVDS driver, the ratio of  $(R_2+R_3)$  to the sum of all three resistors  $(R_1+R_2+R_3)$  is the same ratio of  $V_{CM} = 1.2\ \text{V}$  to  $V_{CC}$ . The ratio of  $R_3$  to the sum  $(R_1+R_2+R_3)$  must be equal to the ratio  $0.75: V_{CC}$ . Furthermore;  $R_1 // (R_2+R_3)$  should match the transmission line impedance,  $Z_0 = 50\ \Omega$ . Solving these equations result in the values as in Figure 14 for  $V_{CC}$  of 3.3 and 2.5 respectively.

1.3 CML

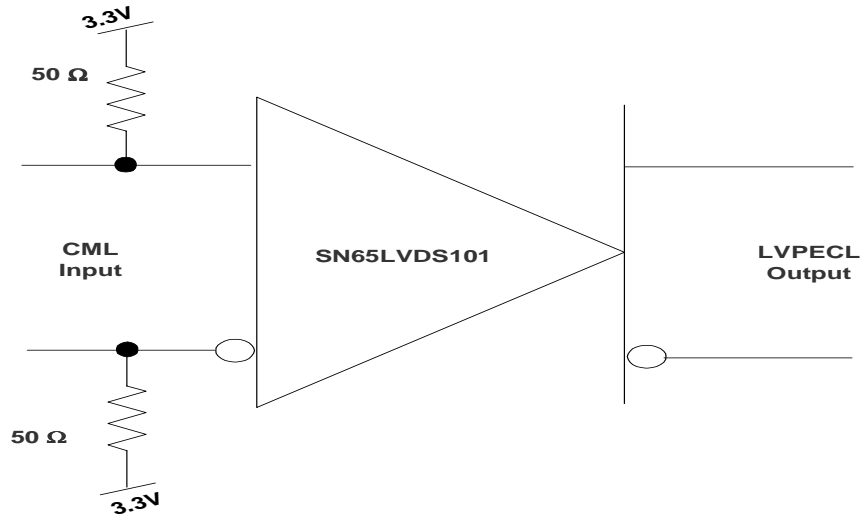


Figure 15. CML to LVPECL Translator

Commonly, ac-coupling is recommended when driving LVPECL with CML. The SN65LVDS101 has a wide common-mode range and can accept CML while providing an LVPECL output.


 


Figure 16. CML to LVDS

Generally, ac-coupling is recommended when driving LVDS receiver with CML. If the LVDS receiver has a wide common-mode range that can accept a CML input (common-mode range must go to  $V_{CC}$  rail), then a dc-coupled connection is a direct connection. The 50- $\Omega$  pullup resistors are required to bias the SN65CML100 and terminate the transmission line.

 

**Figure 17. CML to CML**

If both the CML driver and receiver have the same  $V_{CC}$  supply voltage and on-chip pullup resistors, then a direct connection can be made without external components. If the output stage does not provide an internal 50- $\Omega$  pullup resistor (TLK1501), then 50- $\Omega$  pullup resistors are required at the transmitter output or at the receiver input. The 50- $\Omega$  pullup resistors (see Figure 17) could also be moved to the receive end instead. In addition to the 50- $\Omega$  pullup at the source, a 100- $\Omega$  line end termination could be implemented at the receiver to terminate the line-impedance at both ends of the link.

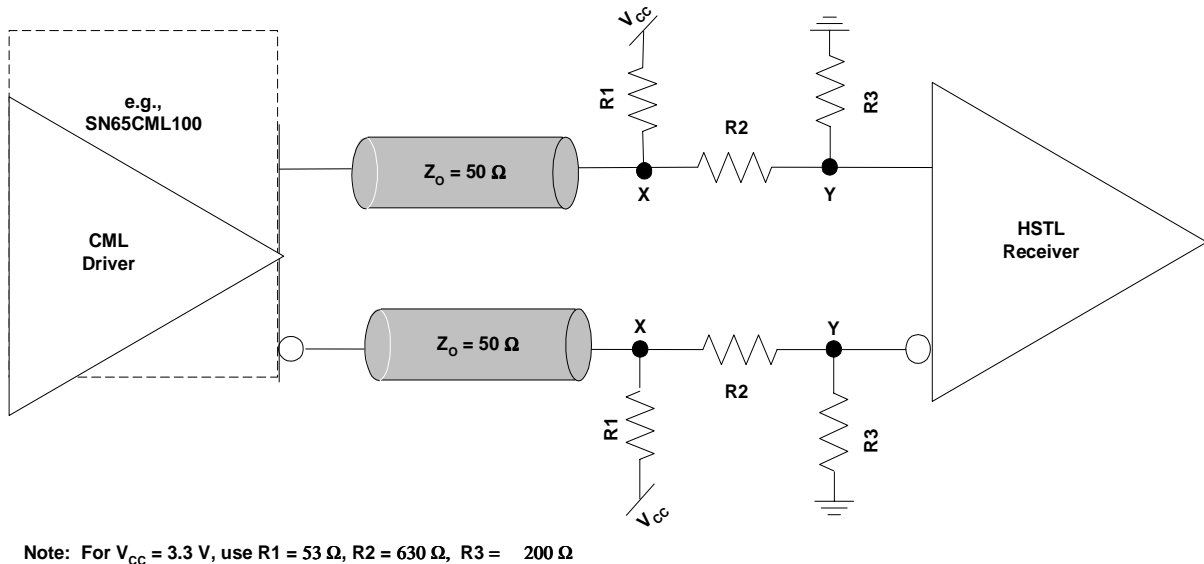


Figure 18. CML to HSTL

In Figure 18, the resistor network R1, R2, and R3 provides proper termination. The network also provides level shifting from CML to HSTL. Using the I/O tables, the following equations are used to solve for R1, R2, and R3. First,  $(R2+R3)/(R1+R2+R3) = 3.1/3.3$ . Second,  $R3/(R1+R2+R3) = 0.75/3.3$ . Finally,  $R1 \parallel (R2+R3) = Z_0 = 50\ \Omega$ .

## 1.4 HSTL


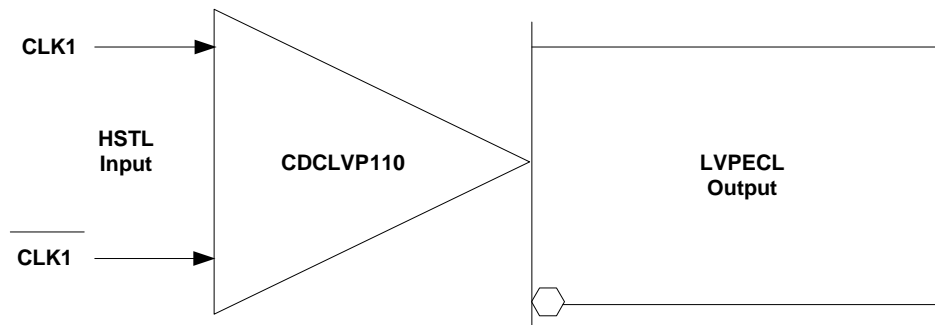


Figure 19. HSTL to LVPECL Converter


The CDCLVP110 in Figure 14 has dual inputs for either HSTL (CLK1 pair is optimized for HSTL levels) or LVPECL inputs (CLK0 pair accepts LVPECL). In both cases, the CDCLVP110

provides LVPECL outputs.

 


**Figure 20. HSTL to LVDS**

HSTL signals are usually terminated to ( $V_{TT} = V_{ref} = 0.75\text{ V}$ ). Since most LVDS compatible receivers accept a 200-mV signal swing anywhere between 0 V and 2.4 V; then the HSTL signal is well within the LVDS receiver input range. The typical HSTL signal swing is 400 mV (minimum), 1.1 V (maximum) this amplitude is compatible with the LVDS receiver. The SN65LVDS100 requires a 3.3-V supply, while the CDCLVD110 is 2.5-V LVDS driver/receiver.

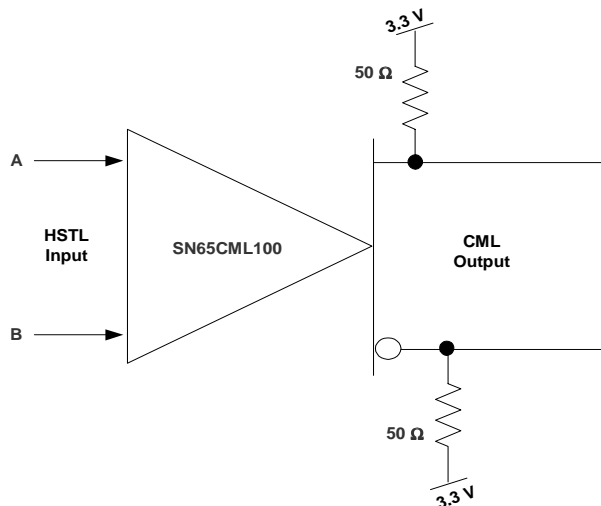

**Figure 21. HSTL to CML Translator**

The wide common-mode inputs range (0 V to 2.4 V) of the SN65CML100 accepts HSTL levels. The 50- $\Omega$  resistors are required to bias the SN65CML100 and terminate the transmission line impedance.

 

**Figure 22. HSTL to HSTL**

HSTL signals are usually terminated  $50\text{-}\Omega$  to VTT (typically  $V_{TT} = 0.75\text{ V}$ ). When VTT is not available, an alternative is a  $100\text{-}\Omega$  differential termination.

## 2 References

1. AC-Coupling between LVPECL, LVDS, CML, and HSTL, Texas Instruments application report, (SCAA059)
2. *Interfacing Between LVPECL, LVDS, and CML*, Texas Instruments application report, (SCAA056)
3. *Interfacing Differential Logic With LVDS Receivers*, Texas Instruments application report, (SLLA101)
4. *Clock Distribution Circuits (CDC)*, Texas Instruments CDC data book, (SCAD004)
5. CDCLVD110 data sheet, Texas Instruments, (SCAS684)
6. CDCLVP110 data sheet, Texas Instruments, (SCAS683)
7. SN65CML100 data sheet, Texas Instruments, (SLLS547)
8. SN65LVDS100 data sheet, Texas Instruments, (SLLS516A)
9. CDC111 data sheet, Texas Instruments, (SCAS321)
10. CDCVF111 data sheet, Texas Instruments, (SCAS670)
11. *Interfacing Between LVPECL, VML, CML, and LVDS Levels*, Texas Instruments application report, (SLLA120)
12. TLK2501 data sheet, Texas Instruments, (SLLS427)
13. TLK1501 data sheet, Texas Instruments, (SLLS458)

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

### Mailing Address:

Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265