

Designing UCC28250 as a Secondary Side Control for Output Turn-On with a Pre-Bias Condition

Hong Huang and Steven Tumas

Power-Supply Control Products

ABSTRACT

This application note addresses the considerations for using the [UCC28250](#) as a secondary side controller. With voltage mode control, the UCC28250 can be used in a design that produces smooth turn-on performance with an output pre-bias condition. The design guidelines are summarized from various performance tests and examined particularly on a 100-W, dc-dc half bridge converter. This converter is designed for telecom input of 36 V to 75 V and an output voltage of 3.3 V. This document provides test results based on these guidelines, and also offers some test results that demonstrate the outcomes when the guidelines are not followed. Additional design details and test results can be found in [the user's guide](#) for the [UCC28250EVM-564](#). For primary side control with the UCC28250, it is recommended to refer the [UCC28250EVM-501 user's guide](#).

Contents

1	Two Feedback Loops of UCC28250	2
2	Design Guidelines	3
3	Case Comparisons: Designs That Do and Do Not Follow the Design Guidelines	3
4	Conclusion	7
5	References	7

List of Figures

1	Two Feedback Loops of UCC28250	2
2	Case 1: HB Loop Compensation Bode Plots of HB Loop-Gain.....	4
3	Case 1 V_{OUT} Turn-on with Pre-Bias Condition.....	5
4	Case 2-1: Chattering Observed During V_{OUT} Turn-On.....	6
5	Case 2-2: Observed Undershoot and Chattering During V_{OUT} Turn-on with Pre-Bias Condition	7

1 Two Feedback Loops of UCC28250

Figure 1 illustrates the architecture of the UCC28250. This advanced pulse-width modulation (PWM) controller has two feedback loops, both of which sense the output voltage (V_{OUT}) for control.

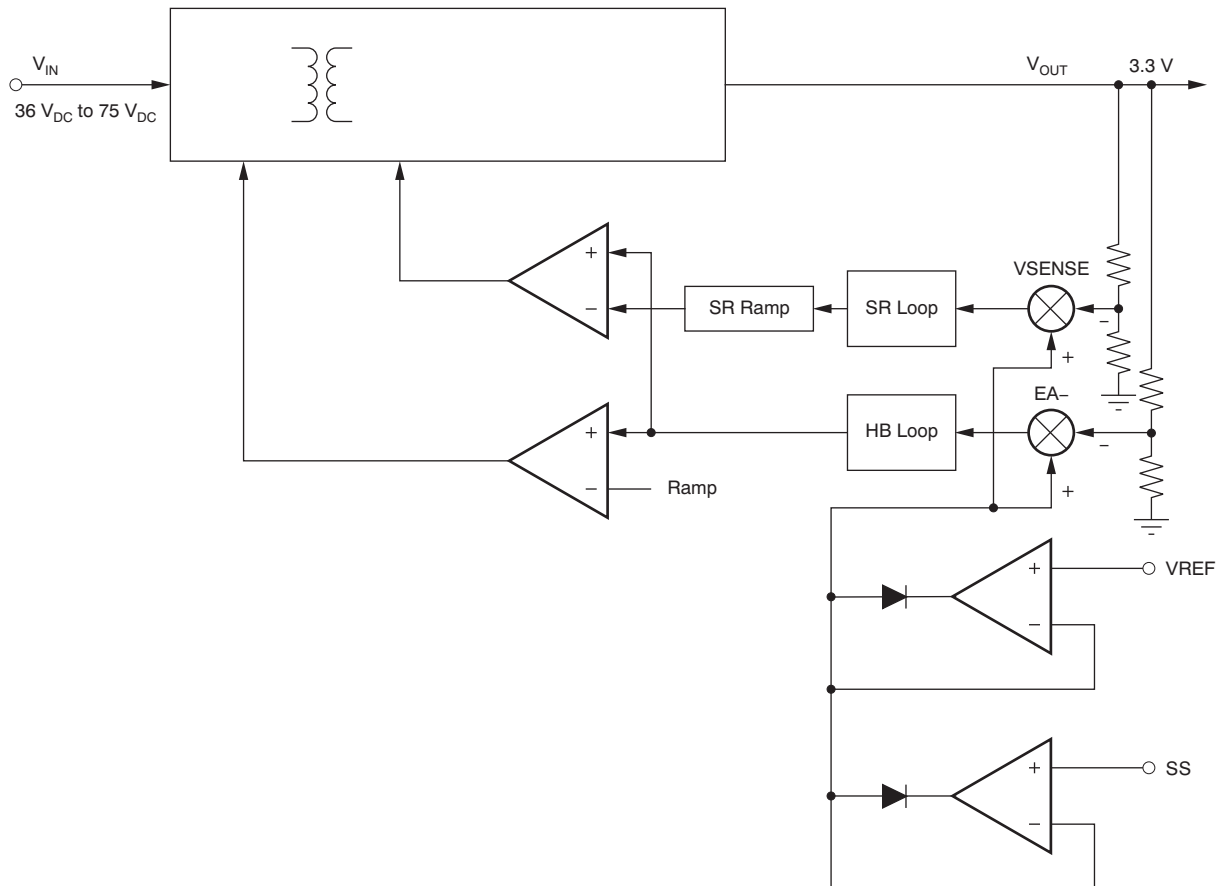


Figure 1. Two Feedback Loops of UCC28250

The loop with the sensed signal fed into VSENSE is called the *SR loop*. The loop with the sensed signal fed into EA- is called the *HB loop*. The SR loop is internally configured; that is, its internal parameters cannot be accessed externally except for the VSENSE pin feedback voltage divider; we also use VSENSE to represent this point, which is also known as the VSENSE feedback set-point. The HB loop is the standard feedback control loop that can be configured externally, such as when using the well-known Type III compensation technique in a voltage-mode control loop. To achieve a smooth turn-on with a pre-bias condition for V_{OUT} , the two loops can be designed following the suggested guidelines presented in [Section 2](#).

2 Design Guidelines

These design guidelines are based on various performance tests using the UCC28250 to make a secondary side control with the requirement of a smooth V_{OUT} turn-on with a pre-bias condition.

1. The voltages on the VSENSE pin and on the EA– pin should meet the relationship defined by [Equation 1](#):

$$V_{SENSE} = (1.05 \text{ to } 1.15) \times V_{EA-} \quad (1)$$

2. The output filter $L_O \times C_O$ double-pole frequency should be designed with the relationship of the switching frequency, f_{SW} , as shown in [Equation 2](#):

$$f_{LC} \leq \frac{f_{SW}}{40} \quad (2)$$

with the output capacitor equivalent series resistance (ESR) zero frequency, f_{ESR_Z} :

$$f_{ESR_Z} > 10 \times f_{LC}$$

3. Bode plots of the HB loop-gain crossover frequency should be obtained with [Equation 3](#):

$$f_C = (0.05 \text{ to } 0.1) \times f_{SW} \quad (3)$$

with a phase margin not less than 45 degrees.

4. The loop-gain for the HB Loop should be designed close to 60 dB at 1 Hz.

3 Case Comparisons: Designs That Do and Do Not Follow the Design Guidelines

3.1 Case 1: UCC28250EVM-564 V_{OUT} Turn-on with Pre-Bias Condition

Case 1-1: Using the UCC28250EVM-564

Using the UCC28250EVM-564 with the specified design values:

- SR loop with VSENSE = 1.710 V and HB loop with EA– = 1.648 V
This configuration makes VSENSE = $1.037 \times V_{EA-}$, or slightly lower than the recommendation from the guideline defined by [Equation 1](#).
- Output filter double-pole frequency, $f_{LC} = 4.73$ kHz; switching frequency $f_{SW} = 200$ kHz
These values make $f_{LC} \leq f_{SW}/40$, which follows the recommendation of [Equation 2](#).

NOTE: Any further increases in the output capacitance should continue to meet the stated guidelines, and good V_{OUT} turn-on performance can be maintained. However, when reducing the capacitance or inductance, you must ensure that the guidelines are followed.

- The HB loop-gain Bode plots are shown in Figure 2. The results show that $f_c = 11.5$ kHz with a phase margin of 59 degrees, which follows the guideline of Equation 3.

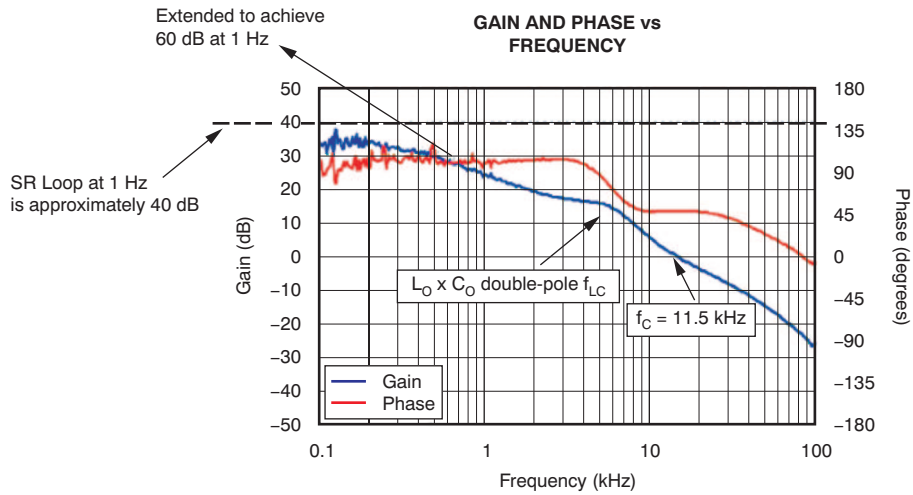


Figure 2. Case 1: HB Loop Compensation Bode Plots of HB Loop-Gain

- Based on the Bode plots, the extrapolated gain magnitude at 1 Hz is greater than 60 dB, in accordance with the [fourth design guideline](#).
- Soft-start time is approximately 12 ms with a soft-start capacitance of 0.1 μ F. Note that excessively long soft-start times can affect the actual device performance.

Case 1-2: Test Results

Figure 3 shows the output voltage (V_{OUT}) turn-on performance with regulation 3.3 V and pre-bias of 2.98 V. Based on Figure 3, the V_{OUT} turn-on is smooth and shows a monotonic rise; that is, there is no undershoot (ditch) or overshoot during the V_{OUT} turn-on from the pre-bias value to the final regulation value. Note that in Figure 3, EN represents the Enable signal.

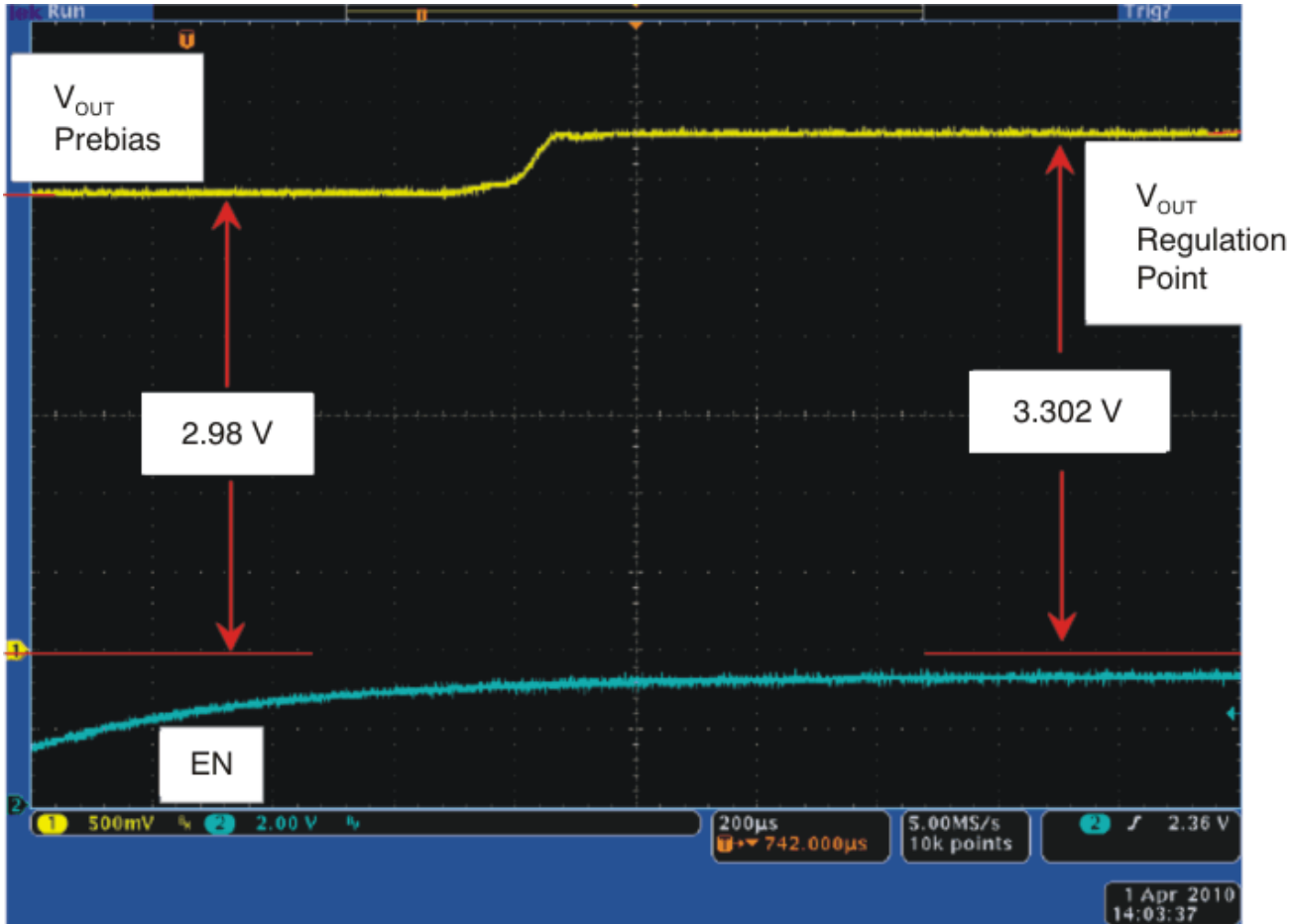


Figure 3. Case 1 V_{OUT} Turn-on with Pre-Bias Condition

3.2 Case 2: Output Filter $L_o \times C_o$ Does Not Follow the Guidelines

- $L_o = 0.5 \mu\text{H}$, $C_o = 100\mu\text{F}$, and $f_{\text{sw}} = 150 \text{ kHz}$.
This configuration generates a value of $f_{\text{LC}} = 22.5 \text{ kHz}$, which does not follow the guideline defined in Equation 2.
- The HB loop-gain crossover frequency setup at $f_c = 25 \text{ kHz}$.
This value does not follow the guideline shown in Equation 3.
- These two violations result in a V_{OUT} turn-on with chattering observed, as shown in Figure 4.

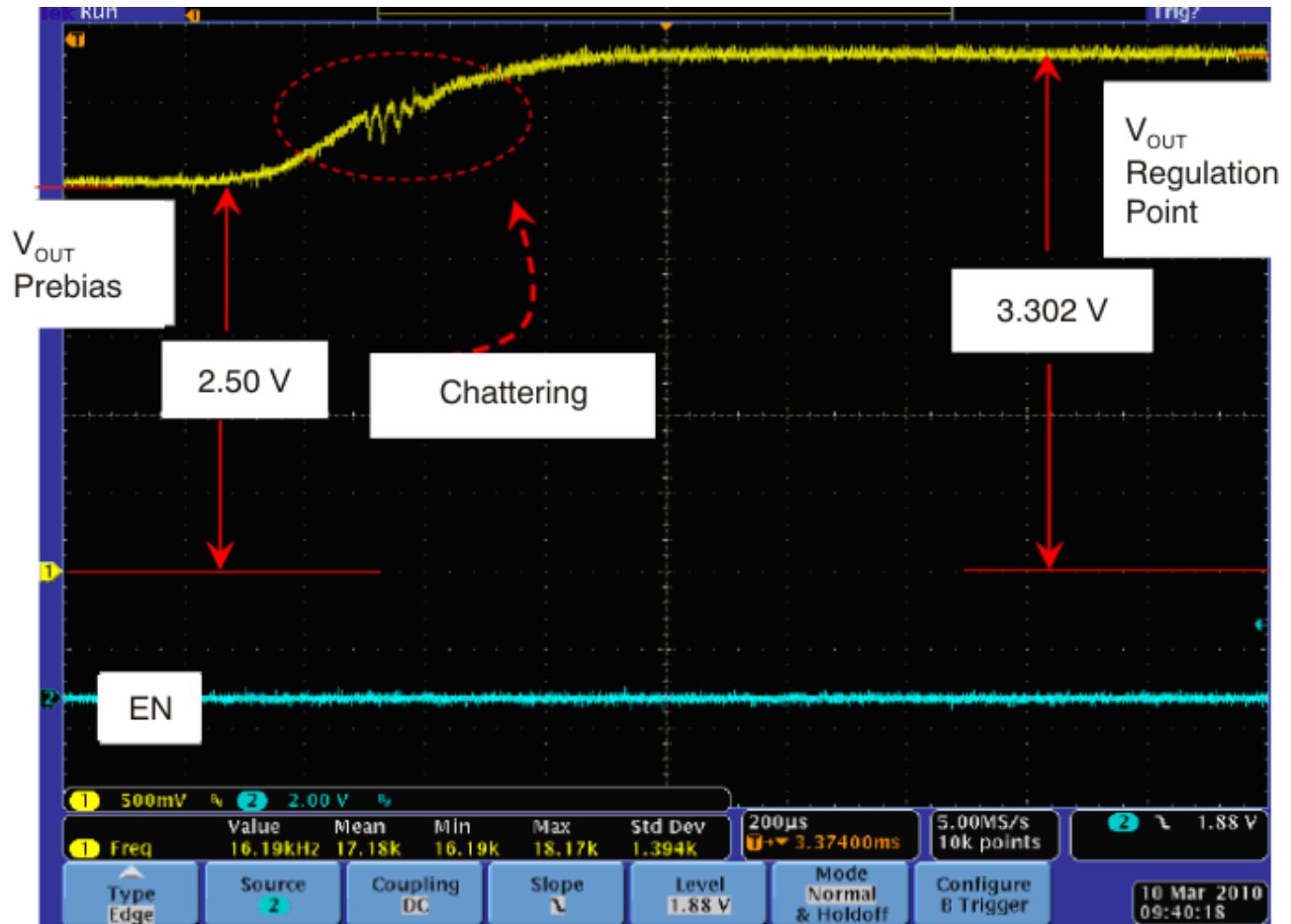


Figure 4. Case 2-1: Chattering Observed During V_{OUT} Turn-On

- The chattering may become a severe ditch (that is, an undershoot) when higher degrees of violations are present, as shown in Figure 5.

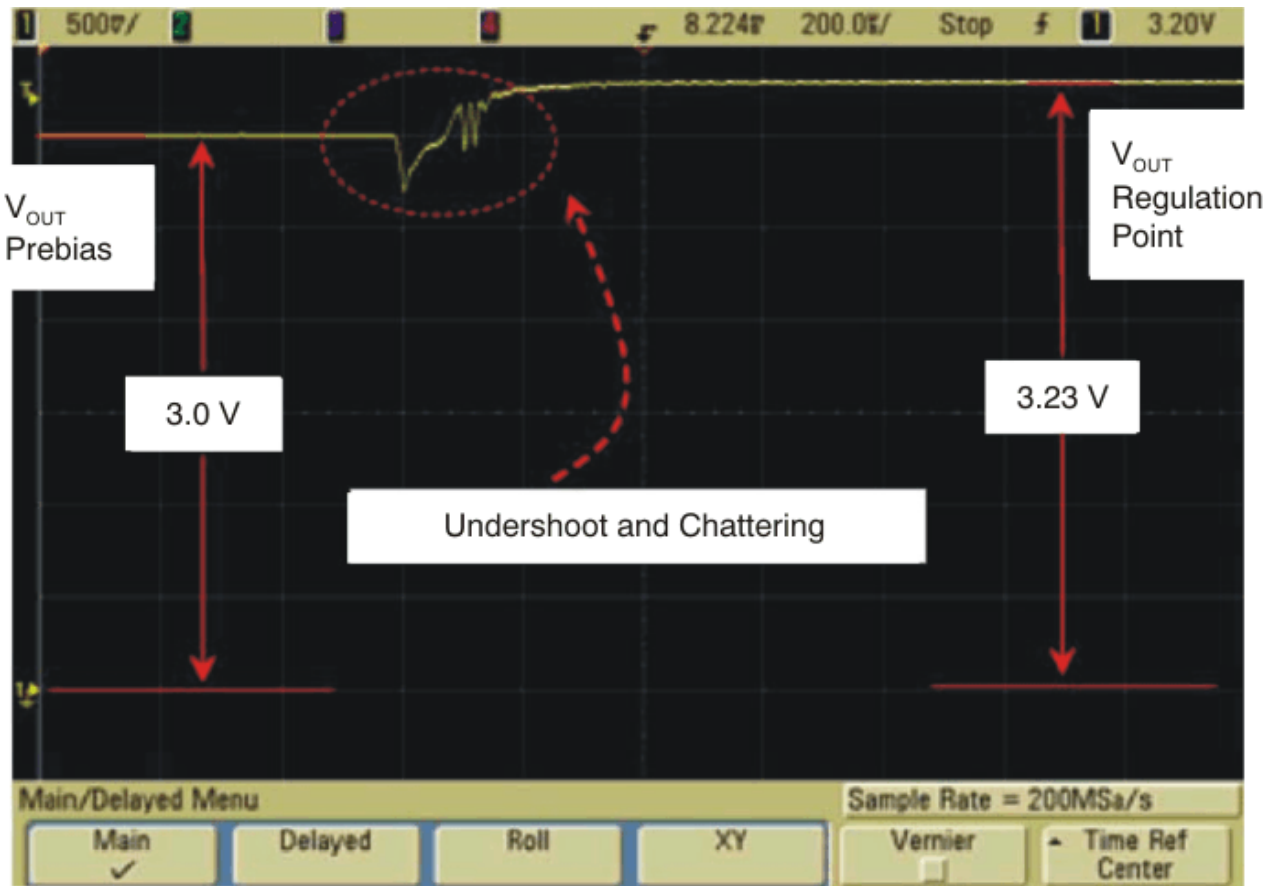


Figure 5. Case 2-2: Observed Undershoot and Chattering During V_{OUT} Turn-on with Pre-Bias Condition

4 Conclusion

In this note, four design guidelines are presented in order to design the UCC28250 as a secondary side control for output voltage turn-on with a pre-bias condition. These guidelines are obtained from various tests and clearly demonstrate the effectiveness of designing with the UCC28250 PWM controller. These suggestions are recommended in order to achieve smooth and monotonic output turn-on with a pre-bias condition.

5 References

The following documents are available for download from the TI website at www.ti.com.

- UCC28250 product data sheet. Literature number [SLUSA29](#).
- UCC28250EVM-501 evaluation module user guide. Literature number [SLUU429](#).
- UCC28250EVM-564 evaluation module user guide. Literature number [SLUU441](#).

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DLP® Products	www.dlp.com	Communications and Telecom	www.ti.com/communications
DSP	dsp.ti.com	Computers and Peripherals	www.ti.com/computers
Clocks and Timers	www.ti.com/clocks	Consumer Electronics	www.ti.com/consumer-apps
Interface	interface.ti.com	Energy	www.ti.com/energy
Logic	logic.ti.com	Industrial	www.ti.com/industrial
Power Mgmt	power.ti.com	Medical	www.ti.com/medical
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Space, Avionics & Defense	www.ti.com/space-avionics-defense
RF/IF and ZigBee® Solutions	www.ti.com/lprf	Video and Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless-apps

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2010, Texas Instruments Incorporated