

# Using TLC5940 With Higher LED Supply Voltages and Series LEDs

Brian Butterfield


PMP - Portable Power

## ABSTRACT

This application report describes how to accommodate higher LED supply voltages and increase the number of series LEDs that the TLC5940 can drive.

## 1 Introduction

The TLC5940 drives 16 LED channels with each channel able to drive a number of series LEDs. The number of series LEDs the TLC5940 can drive is dictated by the available LED supply voltage, and the voltage rating of the OUTx pins. However, in applications where higher LED supply voltages are necessary, such as when driving many series LEDs, a MOSFET placed in series with the OUTx pin and series LED(s) can be used to widen the range of applications where the TLC5940 can be used. [Figure 1](#) shows a typical circuit describing the inserted series MOSFET.

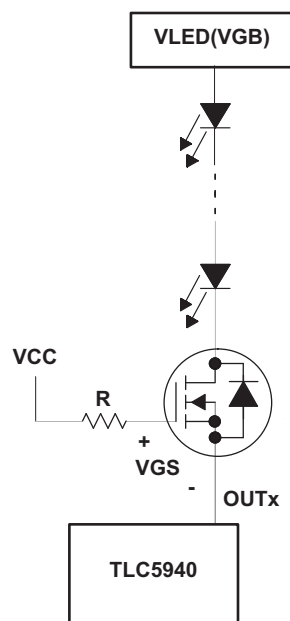

**Figure 1. Typical TLC5940 OUTx Circuitry With Series N-Channel MOSFET**

## 2 Application

With a MOSFET in this configuration, the number of series LEDs and the maximum allowable LED supply voltage depends on the voltage rating of the series n-channel MOSFET. The MOSFET isolates the LED cathode from the 17-V rated OUTx pin and limits the maximum voltage on the OUTx pin to the voltage just below the voltage applied to the gate of the MOSFET, which is  $V_{CC}$  in this example. This worst case occurs when the LED channel is off. During turnoff, the parasitic board capacitances cause the voltage at


OUTx to float up just high enough so that  $V_{CC}$  minus OUTx is less than the MOSFET's turnon threshold,  $V_{GS(th)}$ , which turns the MOSFET off. To restate, under these conditions, the voltage on the OUTx pin is less than  $V_{CC}$ , but greater than  $V_{CC} - V_{GS(th)}$ . When the LEDs are on and the OUTx channel sinks current, the TLC5940 pulls the OUTx pin low, such that  $V_{GS}$  is slightly larger than  $V_{CC} - V_{GS(th)}$  by the amount necessary for the MOSFET to pass the current satisfying OUTx. In either case, with LED(s) on or off, the OUTx pin always has a voltage less than  $V_{CC}$ . The voltage on the MOSFET drain equals the LED drive voltage ( $V_{LED}$ ) minus the forward voltage drop across the LEDs ( $V_f$ ) for the given current and temperature. [Figure 2](#), [Figure 3](#), and [Figure 4](#) illustrate this.

[Figure 2](#) shows the drain-to-source voltage across the MOSFET,  $V_{ds}$ , which is measured at the cathode of the LED and at the OUTx pin (blue and green trace, respectively). Without the series MOSFET, the OUTx pin voltage would be equal to the LED's cathode voltage, the blue trace. With a 5-V LED supply voltage, there is no danger to the TLC5940, and the series MOSFET is not required. The voltage difference between the pink and blue traces depicts the forward voltage drop across one LED, which varies when LED current changes.



**Figure 2. One LED With 5-V LED Supply Voltage, LED Current (Yellow),  $V_{GB}$  (Pink), Voltage on MOSFET's Drain (Blue), and Voltage on MOSFET's Source, or on OUTx Pin (Green).**

[Figure 3](#) shows a similar plot of traces as in [Figure 2](#) but with a 25-V LED supply voltage. Again, the figure shows the MOSFET  $V_{ds}$ , voltage difference between the cathode of the LED and OUTx pin (blue and green trace, respectively), this time protecting the TLC5940. Without the series MOSFET, the OUTx pin voltage would be equal to the LED's cathode voltage, the blue trace, and would violate the absolute maximum ratings for the device.

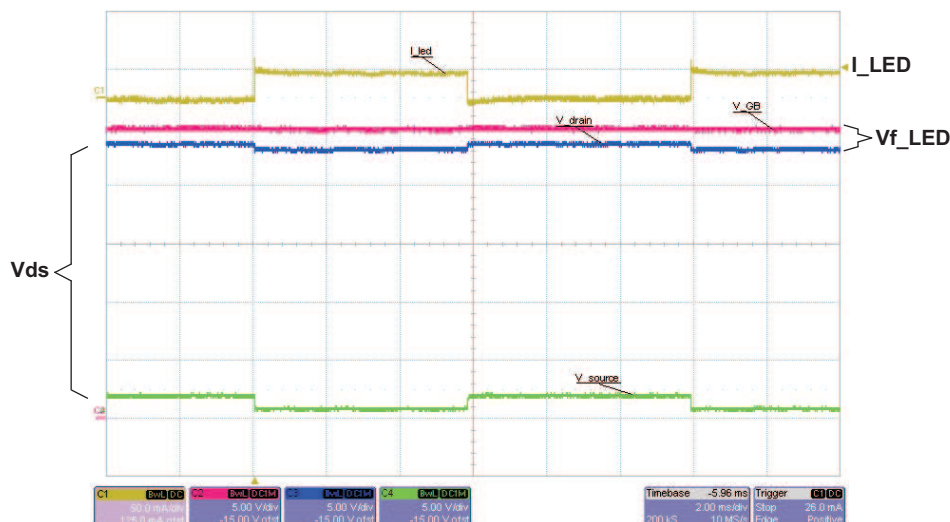


**Figure 3. One LED With 25-V LED Supply Voltage, LED Current (Yellow), V\_GB (Pink), Voltage on MOSFET’s Drain (Blue), and Voltage on MOSFET’s Source, or on the OUTx Pin (Green).**

Figure 4 shows similar traces as those in Figure 2 and Figure 3 but now with 24 series red LEDs driven by a 50-V LED supply voltage. When the driver is off and no current is flowing, the voltage across the LEDs is 29 V. Even though the driver is off, the LEDs have a forward voltage drop due to leakage currents that flow through them. The voltage on the OUTx pin is 2 V, which is greater than  $V_{CC} - V_{GS(th)}$ , or greater than  $3.3\text{ V} - 1.5\text{ V} = 1.8\text{ V}$ . This also means that  $V_{GS}$ , which is  $V_{CC} - V_{OUTx} = 3.3\text{ V} - 2\text{ V} = 1.3\text{ V}$ , is less than  $V_{GS(th)} = 1.5\text{ V}$ . The MOSFET’s drain-to-source voltage is  $V_{LED} - V_f - V_{OUTx} = 50\text{ V} - 29\text{ V} - 2\text{ V} = 19\text{ V}$ . When the driver is on,  $V_{OUTx}$  drops so that the MOSFET’s VI curve satisfies the condition to allow 20 mA of drain current. The voltage across the LEDs is now 39 V. The voltage on the OUTx pin is  $V_{CC} - V_{GS@I_{drain}=I_{sink}}$ , or  $3.3\text{ V} - 2.3\text{ V} = 1\text{ V}$ . The MOSFET’s drain-to-source voltage is  $V_{LED} - V_f - V_{OUTx} = 50\text{ V} - 39\text{ V} - 1\text{ V} = 10\text{ V}$ . The conditions in Figure 2, Figure 3, and Figure 4, show that the voltage on OUTx depends on the LED supply voltage and  $V_{GS(th)}$ , yet never goes above  $V_{CC}$ . See Table 1 for clarification.

**Table 1. Summary of Voltages When LEDs Are On and Off**

$V_{CC} = 3.3\text{ V}$ , $V_{GS(th)} = 1.5\text{ V}$	LEDs Off	LEDs On
I_LED	0 mA	25 mA
V_GB (LED supply)	50 V	50 V
V_drain	21 V	11 V
V_f_LED (LED forward voltage)	29 V	39 V
V_source=V_outx	2 V	1 V
V_gs	1.3 V ( $<V_{GS(th)}$ )	2.3 V ( $>V_{GS(th)}$ )
V_ds (drain-to-source voltage)	19 V	10 V

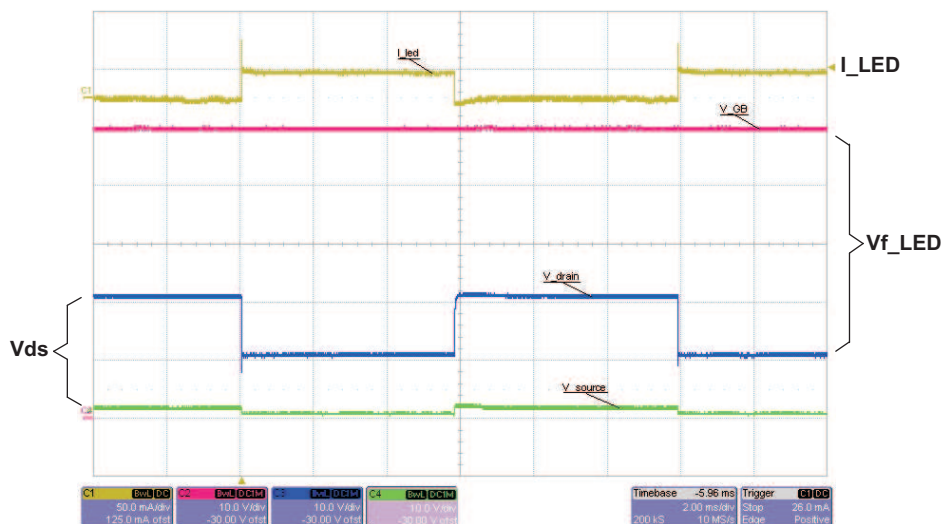

**Figure 4. 24 LEDs With 50-V LED Supply Voltage, LED Current (Yellow), V<sub>GB</sub> (Pink), Voltage on MOSFET’s Drain (Blue), and Voltage on MOSFET’s Source, or on OUTx Pin (Green).**

Figure 2, Figure 3, and Figure 4 show that the MOSFET drain-to-source voltage changes in relation to the voltage necessary to keep the OUTx pin below V<sub>CC</sub>. The MOSFET drain-to-source voltage also changes in direct relation with the voltage necessary to keep the corresponding LED current equal to the sinking current. Because of this buffering effect of the MOSFET, the OUTx pins are protected from being damaged. This allows for higher LED supply voltages and allows for more series LEDs. The figures also show that the number of LEDs a TLC5940 OUTx channel can drive, or the maximum LED supply voltage limit, is determined by MOSFET ratings.

Another consideration, which is not clearly evident in the figures, is the speed of the MOSFET. During testing, it was observed that a fast MOSFET can cause oscillations. Adding a series 100-Ω gate resistor slowed the MOSFET’s response and eliminated oscillations.

### 3 Alternate Solution

An alternate solution to the MOSFET used in the previous circuit is to use a NPN transistor and a base resistor. Typically, this alternate solution is more cost-effective, but with the trade-off of lower LED current accuracy. The lower accuracy is a result of the regulated current being the transistor base current in addition to the LED current. The base resistor should be sized small enough to allow the maximum LED current to pass from collector to emitter, but large enough to minimize base current, and to effectively provide LED overcurrent protection. The base resistor can be sized using the following guidelines.

$$\frac{(V_{CC} - V_{BE})\beta}{I_{LED\_OC}} < R < \frac{(V_{CC} - V_{BE})\beta}{I_{LED\_max}}$$

where I<sub>LED\_max</sub> is the maximum LED current and I<sub>LED\_OC</sub> is the LED overcurrent limit, recommended to be set 20% to 30% greater than I<sub>LED\_max</sub>.

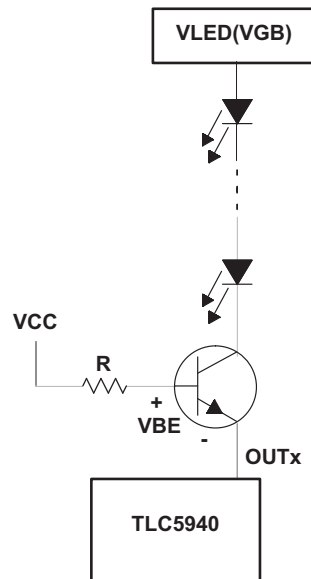


Figure 5. Typical TLC5940 OUTx Circuitry With Series NPN Transistor

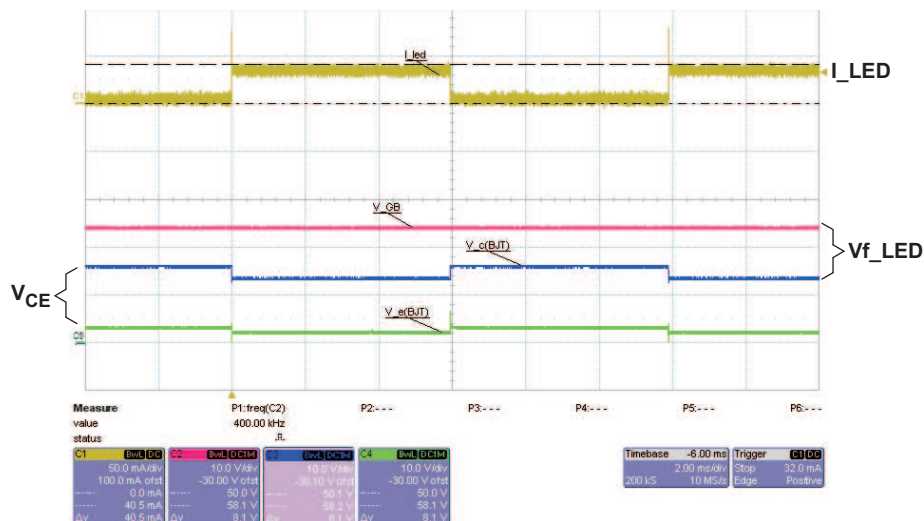


Figure 6. Six LEDs With 24-V LED Supply Voltage, LED Current (Yellow), V<sub>GB</sub> (Pink), Voltage on BJT's Collector (Blue), and Voltage on BJT's Emitter, or on the OUT<sub>x</sub> Pin (Green).

Similar to the MOSFET solution, Figure 6 shows that the number of LEDs a TLC5940 OUT<sub>x</sub> channel can drive, or the maximum LED supply voltage limit, is determined by NPN transistor ratings.

#### 4 Conclusion

With one N-channel MOSFET, or one NPN transistor plus one base resistor, placed in series with the OUT<sub>x</sub> pin of the TLC5940 and series LED(s), the TLC5940 can be used with higher LED supply voltages and to drive more series LEDs.

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

<b>Products</b>		<b>Applications</b>	
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>	Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>	Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>	Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>	Digital Control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>	Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>	Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>	Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>	Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Low Power Wireless	<a href="http://www.ti.com/lpw">www.ti.com/lpw</a>	Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
		Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2007, Texas Instruments Incorporated