

**Test Data
For PMP9291
2/5/2014**



Table of Contents

| | |
|---|----|
| 1. Design Specifications | 3 |
| 2. Circuit Description..... | 3 |
| 3. PMP9291 Board Photos | 4 |
| 4. Thermal Data..... | 6 |
| 5. Efficiency and Line/Load Regulation | 7 |
| 5.1 Efficiency Chart | 7 |
| 5.2 Efficiency Comparison between PMP9291 (Synchronous Secondary) and PMP9354 (Non-Synchronous Secondary)..... | 8 |
| 5.3 Efficiency and Line/Load Regulation Data | 9 |
| 5.4 Line and Load Regulation | 10 |
| 5.5 Line and Load Regulation Comparison between Self-Driven Synchronous Rectification and Diode (Non-Synchronous) Rectification | 11 |
| 5.6 Line and Load Regulation Comparison between Self-Driven Synchronous Rectification and Diode (Non-Synchronous) Rectification (Zoomed in to light load range) | 12 |
| 6 Waveforms..... | 13 |
| 6.1 Load Transient Response | 13 |
| 6.2 Startup | 16 |
| 6.3 Output Voltage Ripple and Switch Node Voltage | 22 |
| 7 Short Circuit Testing..... | 28 |

1. Design Specifications


| | |
|--|---|
| Vin | 10.8VDC to 13.2VDC (12VDC Nominal) |
| Vout | 5VDC |
| Iout | 0.3A Max. |
| Approximate Switching Frequency | ≈240KHz |

2. Circuit Description


PMP9291 is an Isolated Flybuck Converter using a synchronous buck regulator with Self-Driven Synchronous Rectification on the Secondary Side. The design accepts an input voltage of 10.8Vin to 13.2Vin and provides an isolated output of 5Vout capable of supplying a maximum of 0.3A of current to the load. This design was built on a 4-layer PCB. The secondary-side self-driven synchronous rectification offers benefits of higher efficiency, no need for pre-load, and much lower output voltage tolerances ($4.916V_{out} \pm 3.1\%$ over entire line and load range) without the need for opto-coupler and discrete voltage reference. A comparison of output voltage regulation over line and load between this design and an analogous non-synchronous flybuck converter (PMP9354) are given and compared in Sections 5.5 and 5.6. The design uses a readily-available off-the-shelf VERSA-PAC series transformer.

3. PMP9291 Board Photos

Board Dimensions: 2" x 2.7"

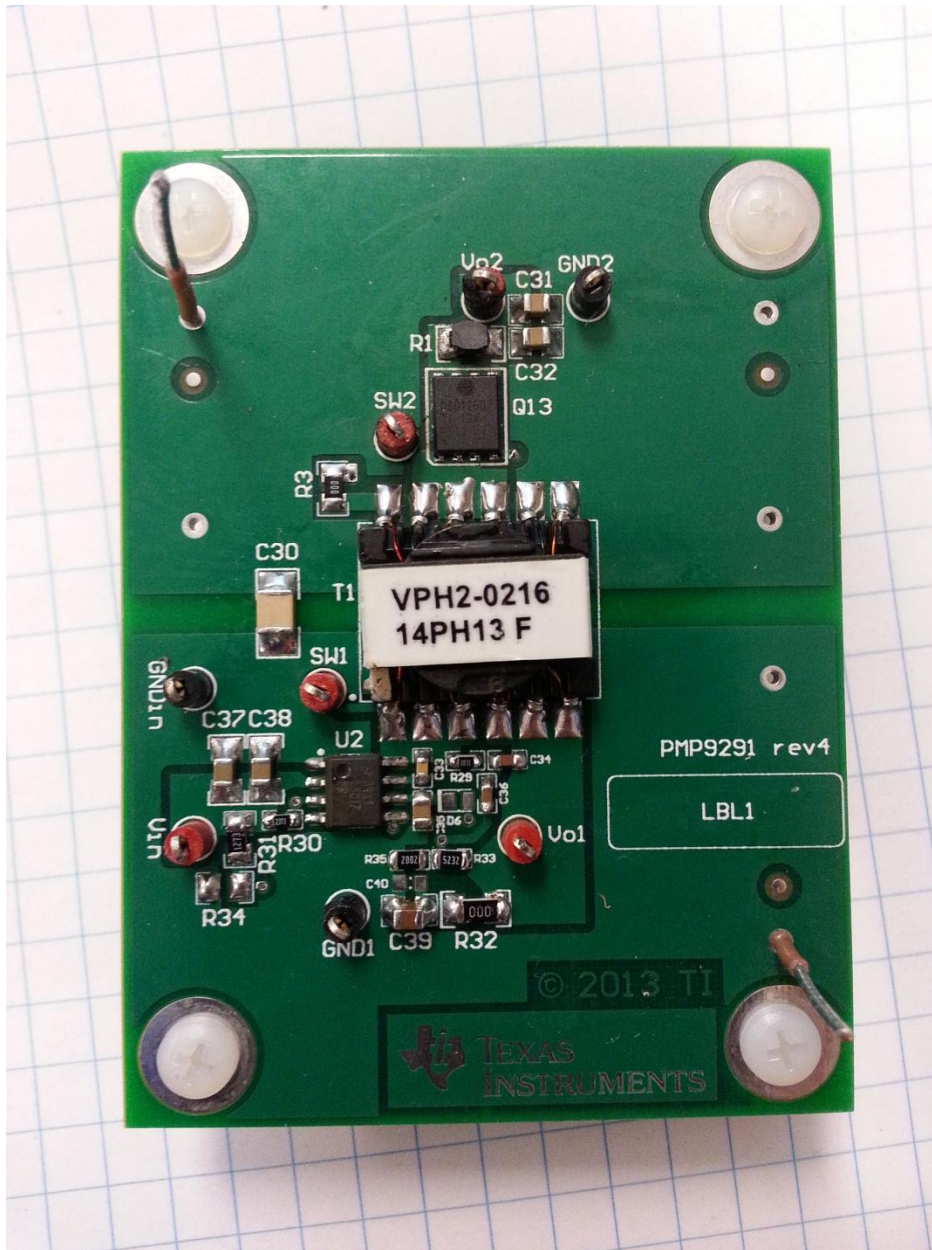


Board Photo (Top)

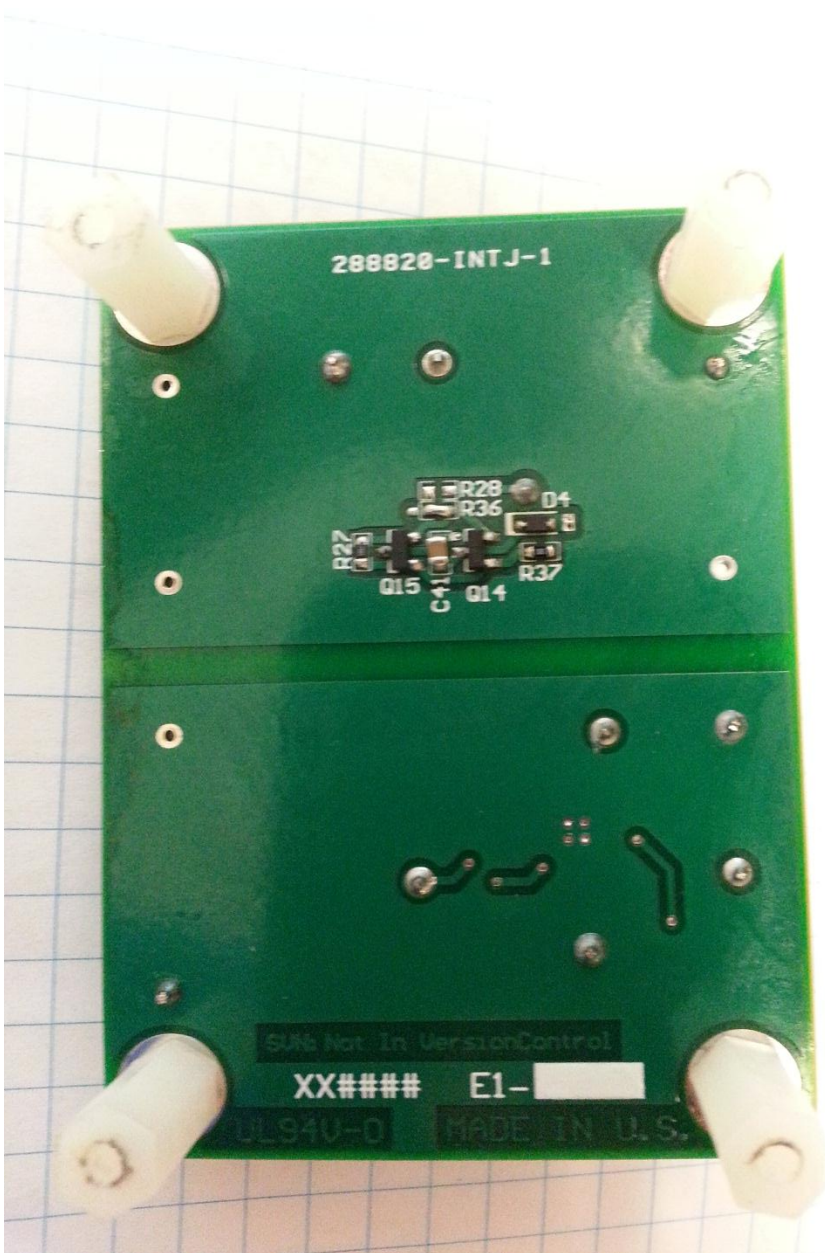

Board Photo (Bottom)


4. Thermal Data

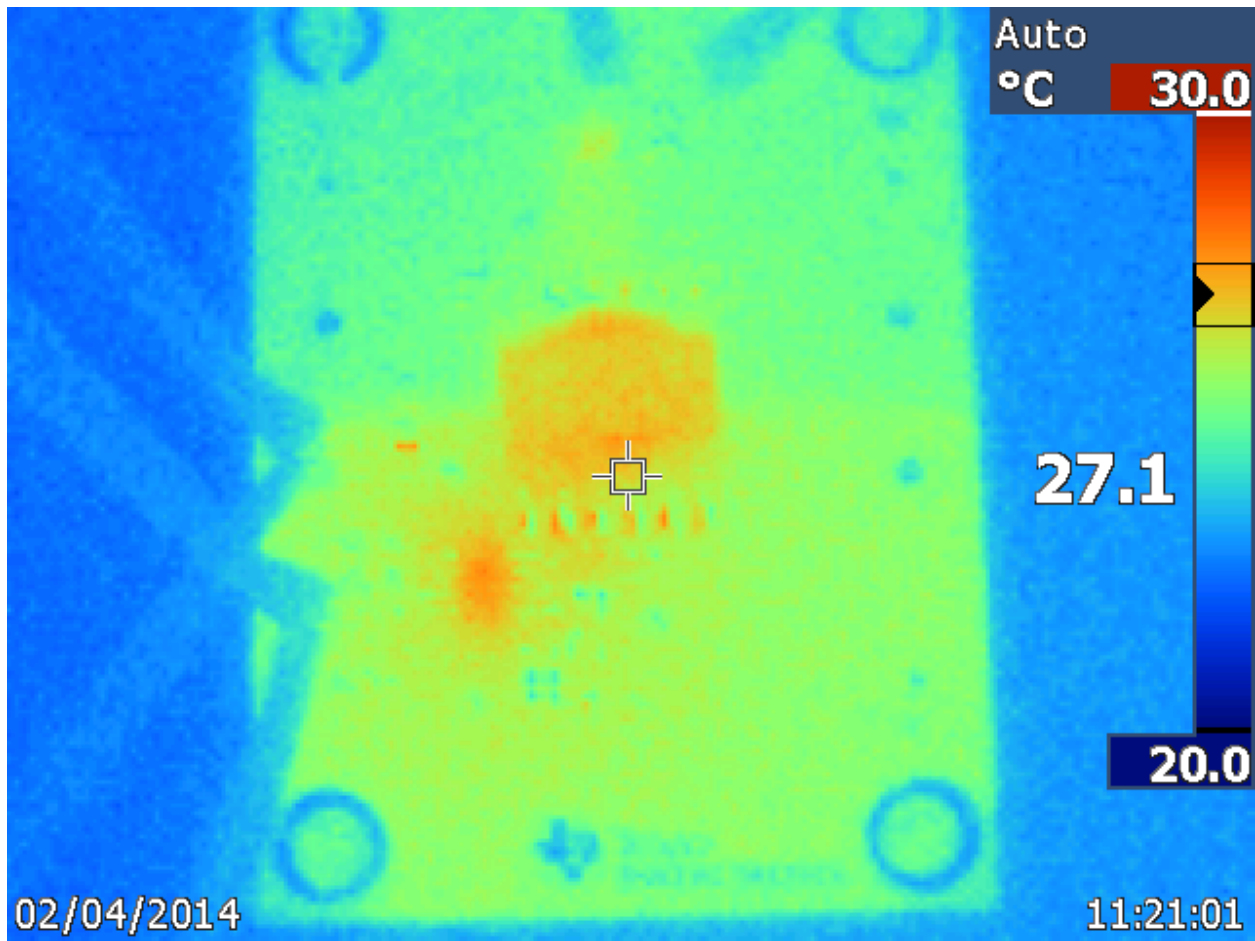


IR thermal image taken at steady state with 12Vin and 0.3A load (no airflow)

5. Efficiency and Line/Load Regulation

5.1 Efficiency Chart

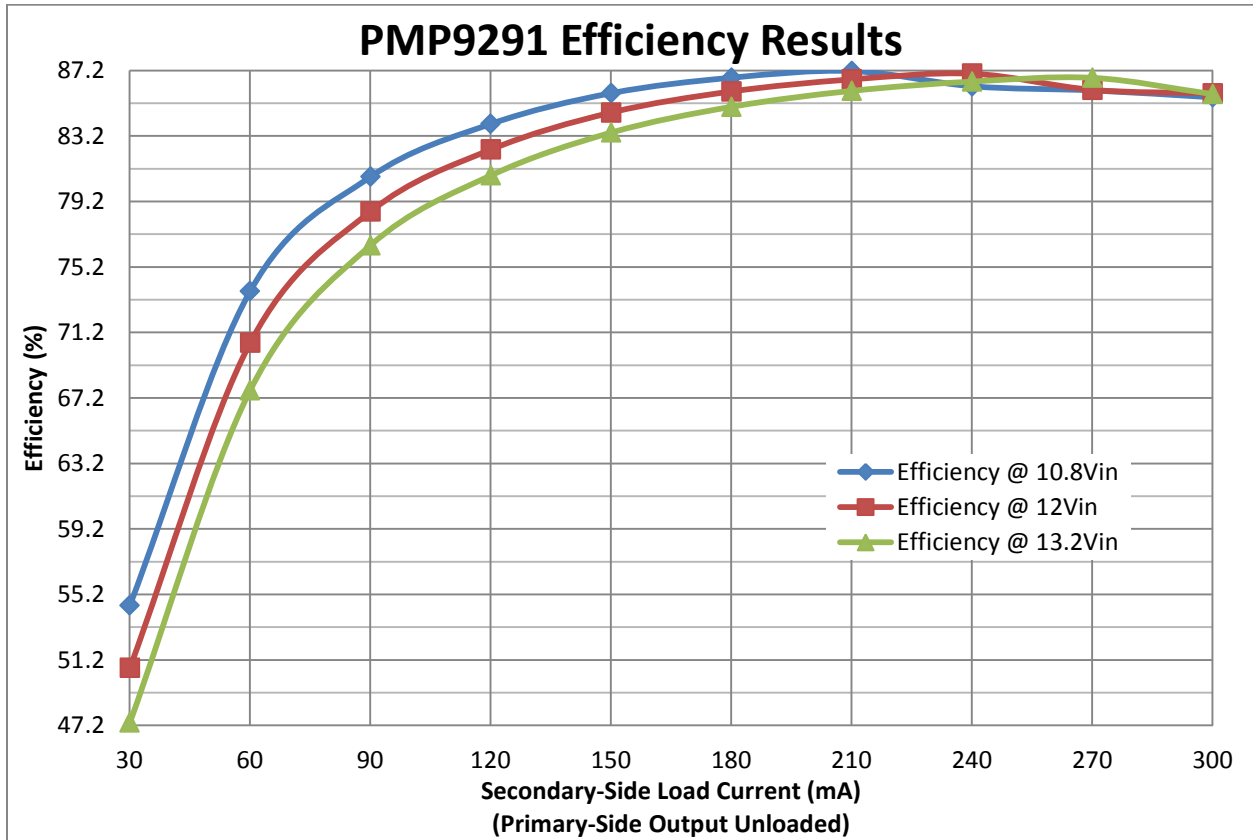

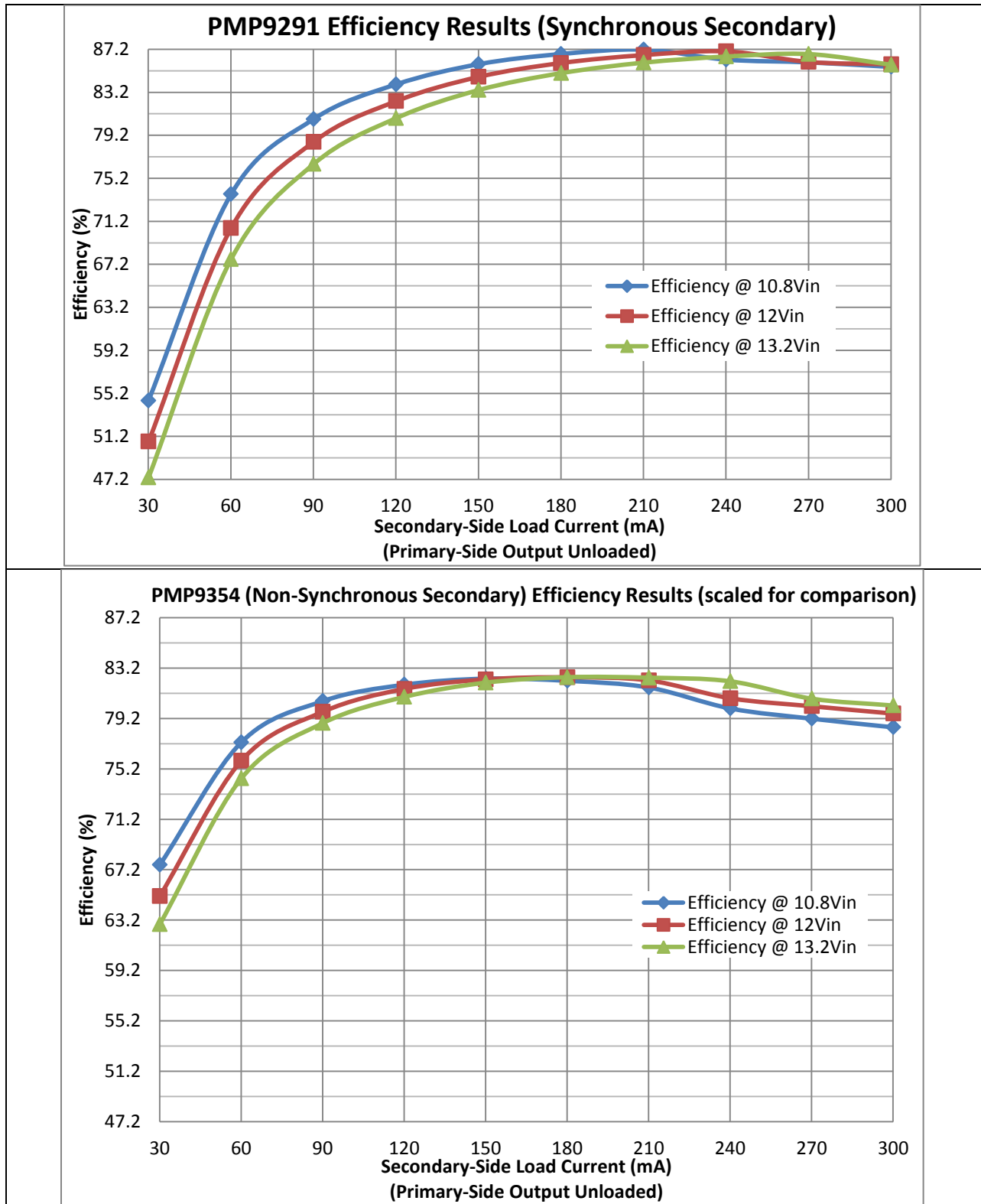
5.2 Efficiency Comparison between PMP9291 (Synchronous Secondary) and PMP9354 (Non-Synchronous Secondary)




5.3 Efficiency and Line/Load Regulation Data

| Vin (V) | Iin (mA) | Vout (V) | Iout (mA) | Pin (W) | Pout (W) | Efficiency (%) |
|---------|----------|----------|-----------|---------|----------|----------------|
| 10.80 | 13.271 | 4.9788 | 0 | 0.1433 | 0.0000 | |
| 10.80 | 25.338 | 4.974 | 29.992 | 0.2736 | 0.1492 | 54.5 |
| 10.80 | 37.43 | 4.9663 | 59.996 | 0.4042 | 0.2980 | 73.7 |
| 10.80 | 51.216 | 4.9583 | 90.008 | 0.5530 | 0.4463 | 80.7 |
| 10.80 | 65.507 | 4.9475 | 119.992 | 0.7073 | 0.5937 | 83.9 |
| 10.80 | 79.887 | 4.9336 | 150.03 | 0.8625 | 0.7402 | 85.8 |
| 10.80 | 94.497 | 4.9173 | 180 | 1.0202 | 0.8851 | 86.8 |
| 10.80 | 109.32 | 4.8984 | 210.02 | 1.1802 | 1.0288 | 87.2 |
| 10.80 | 125.72 | 4.8772 | 240.01 | 1.3574 | 1.1706 | 86.2 |
| 10.80 | 140.41 | 4.8273 | 270.03 | 1.5160 | 1.3035 | 86.0 |
| 10.80 | 154.71 | 4.7636 | 300.02 | 1.6704 | 1.4292 | 85.6 |
| Vin (V) | Iin (mA) | Vout (V) | Iout (mA) | Pin (W) | Pout (W) | Efficiency (%) |
| 12.00 | 14.07 | 5.026 | 0 | 0.1688 | 0.0000 | |
| 12.00 | 24.777 | 5.0227 | 30.013 | 0.2972 | 0.1507 | 50.7 |
| 12.00 | 35.575 | 5.0194 | 59.998 | 0.4268 | 0.3012 | 70.6 |
| 12.00 | 47.875 | 5.0151 | 90.001 | 0.5744 | 0.4514 | 78.6 |
| 12.00 | 60.822 | 5.0088 | 119.997 | 0.7297 | 0.6010 | 82.4 |
| 12.00 | 73.89 | 5.0006 | 150.03 | 0.8865 | 0.7502 | 84.6 |
| 12.00 | 87.157 | 4.9907 | 180 | 1.0455 | 0.8983 | 85.9 |
| 12.00 | 100.575 | 4.9783 | 210.02 | 1.2065 | 1.0455 | 86.7 |
| 12.00 | 114.06 | 4.9602 | 240 | 1.3683 | 1.1904 | 87.0 |
| 12.00 | 128.52 | 4.912 | 270.01 | 1.5419 | 1.3263 | 86.0 |
| 12.00 | 141.66 | 4.86 | 300.02 | 1.6994 | 1.4581 | 85.8 |
| Vin (V) | Iin (mA) | Vout (V) | Iout (mA) | Pin (W) | Pout (W) | Efficiency (%) |
| 13.20 | 14.689 | 5.0688 | 0 | 0.1939 | 0.0000 | |
| 13.20 | 24.312 | 5.0663 | 29.993 | 0.3208 | 0.1520 | 47.4 |
| 13.20 | 34.024 | 5.0642 | 59.997 | 0.4490 | 0.3038 | 67.7 |
| 13.20 | 45.109 | 5.0615 | 90 | 0.5953 | 0.4555 | 76.5 |
| 13.20 | 56.921 | 5.0575 | 119.995 | 0.7512 | 0.6069 | 80.8 |
| 13.20 | 68.858 | 5.0526 | 150.01 | 0.9087 | 0.7579 | 83.4 |
| 13.20 | 80.998 | 5.046 | 180.01 | 1.0688 | 0.9083 | 85.0 |
| 13.20 | 93.285 | 5.0382 | 210.02 | 1.2310 | 1.0581 | 86.0 |
| 13.20 | 105.41 | 5.0145 | 240.01 | 1.3910 | 1.2035 | 86.5 |
| 13.20 | 117.309 | 4.9736 | 270.01 | 1.5480 | 1.3429 | 86.8 |
| 13.20 | 130.7 | 4.9305 | 300 | 1.7248 | 1.4792 | 85.8 |


5.4 Line and Load Regulation

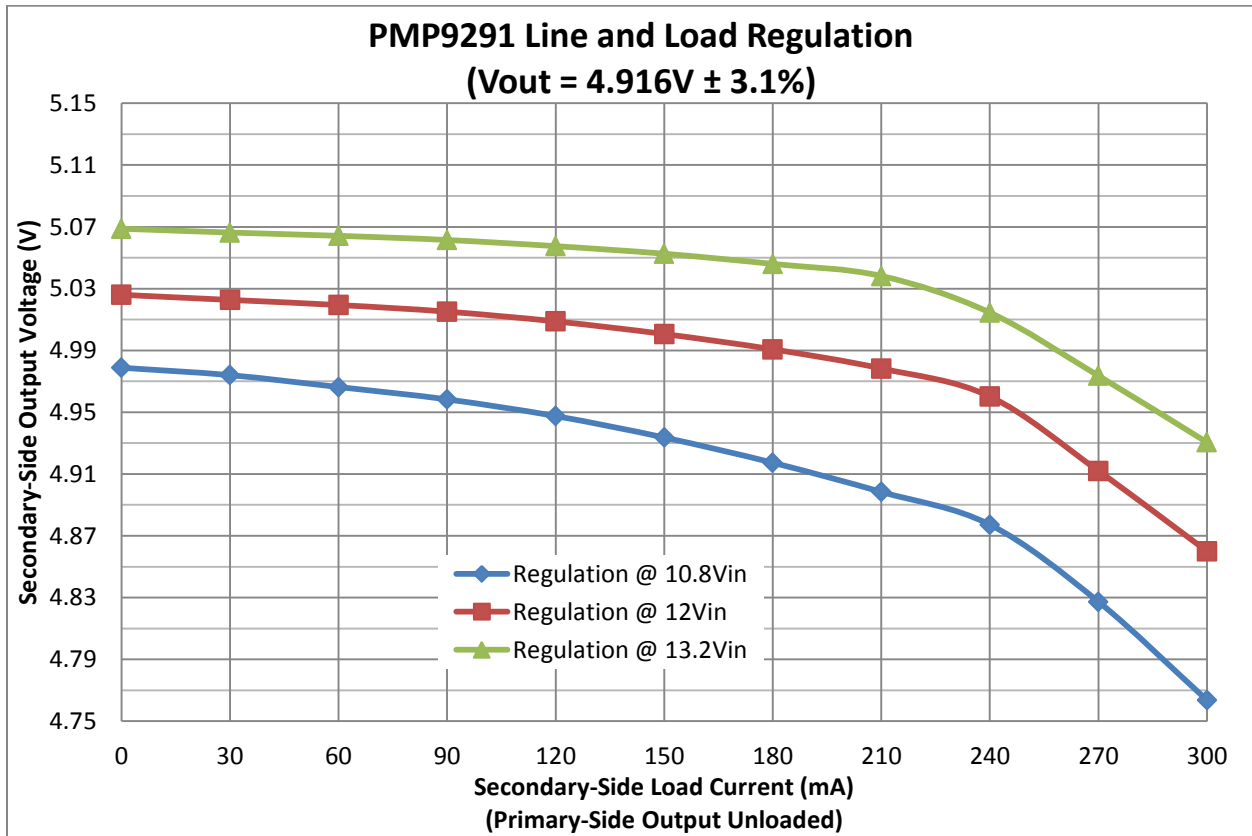

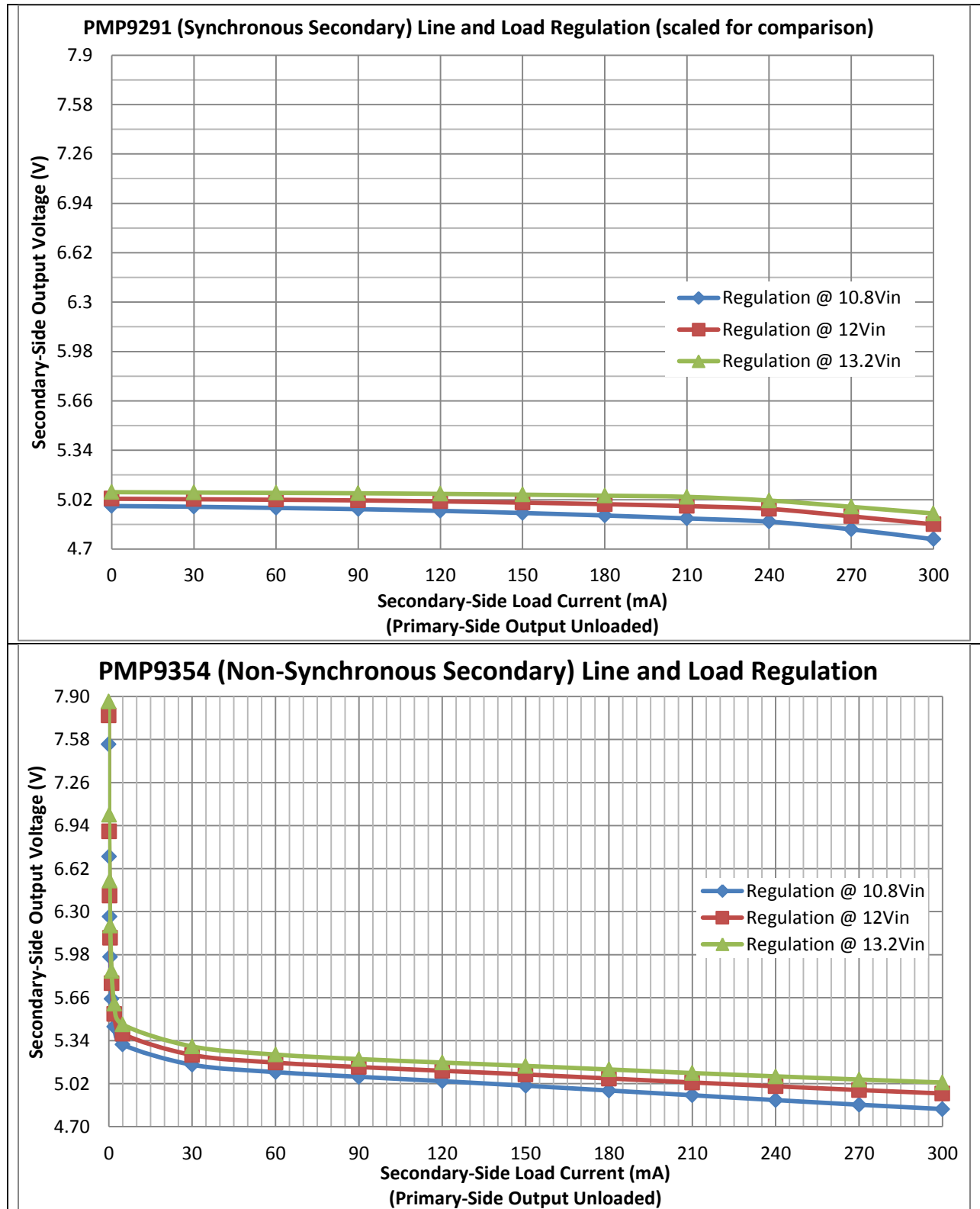5.5 Line and Load Regulation Comparison between Self-Driven Synchronous Rectification and Diode (Non-Synchronous) Rectification




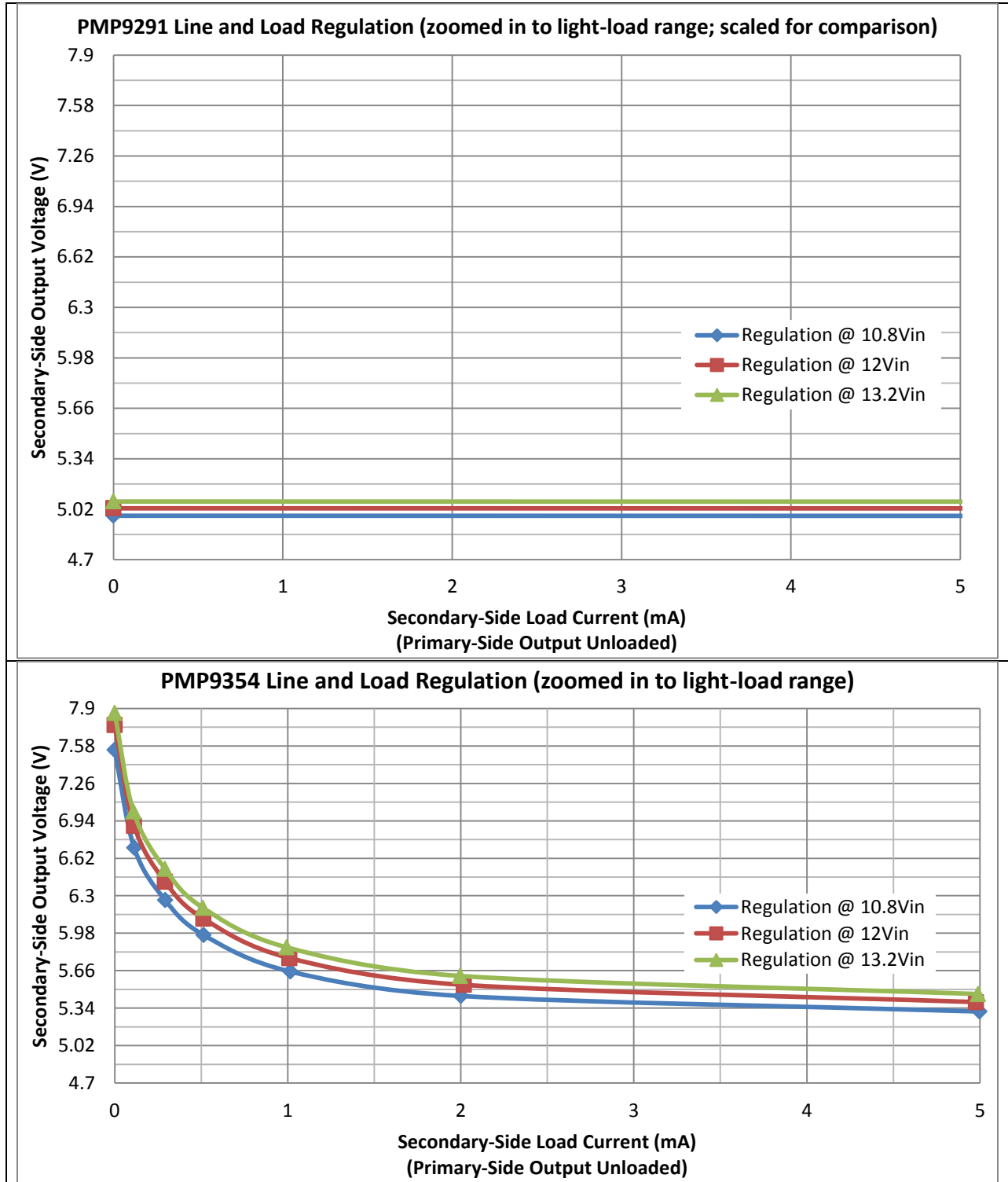5.6 Line and Load Regulation Comparison between Self-Driven Synchronous Rectification and Diode (Non-Synchronous) Rectification (Zoomed in to light load range)




6 Waveforms


6.1 Load Transient Response

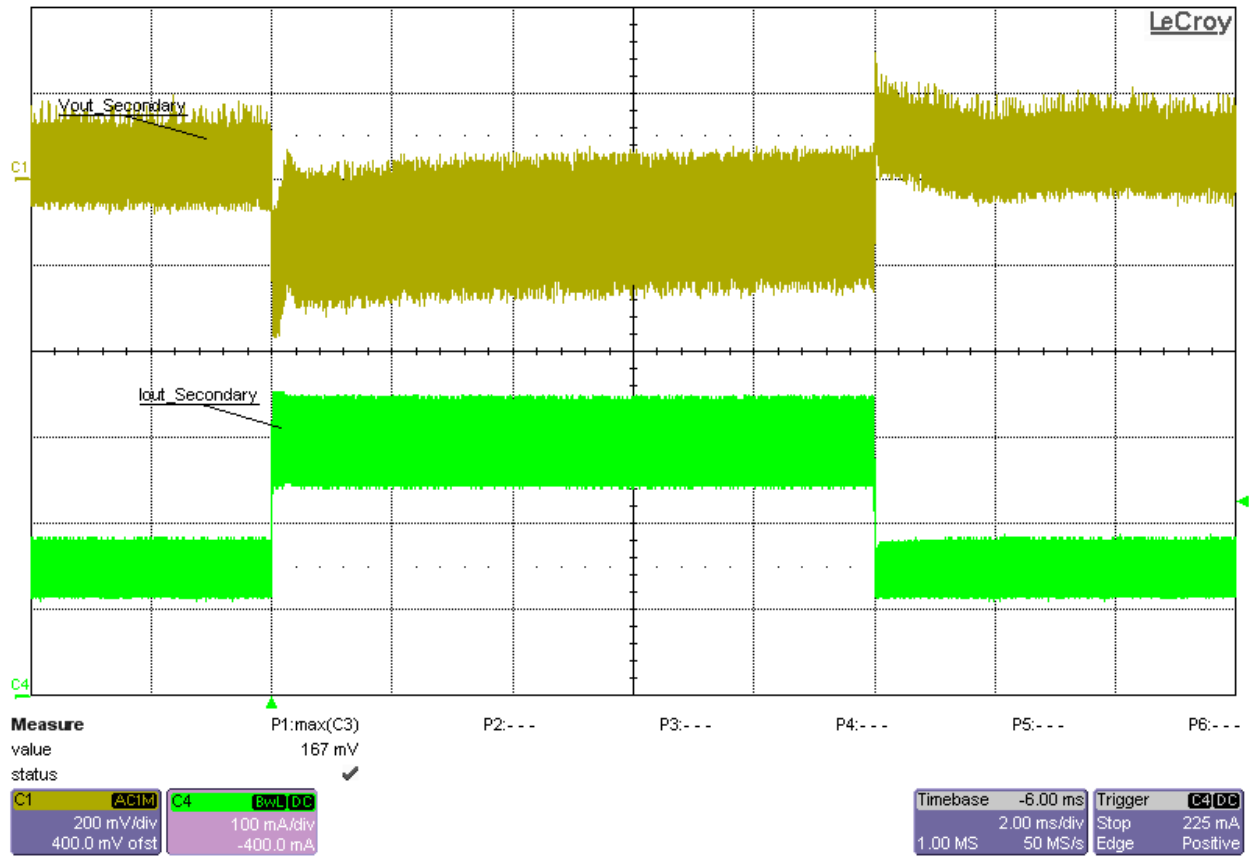

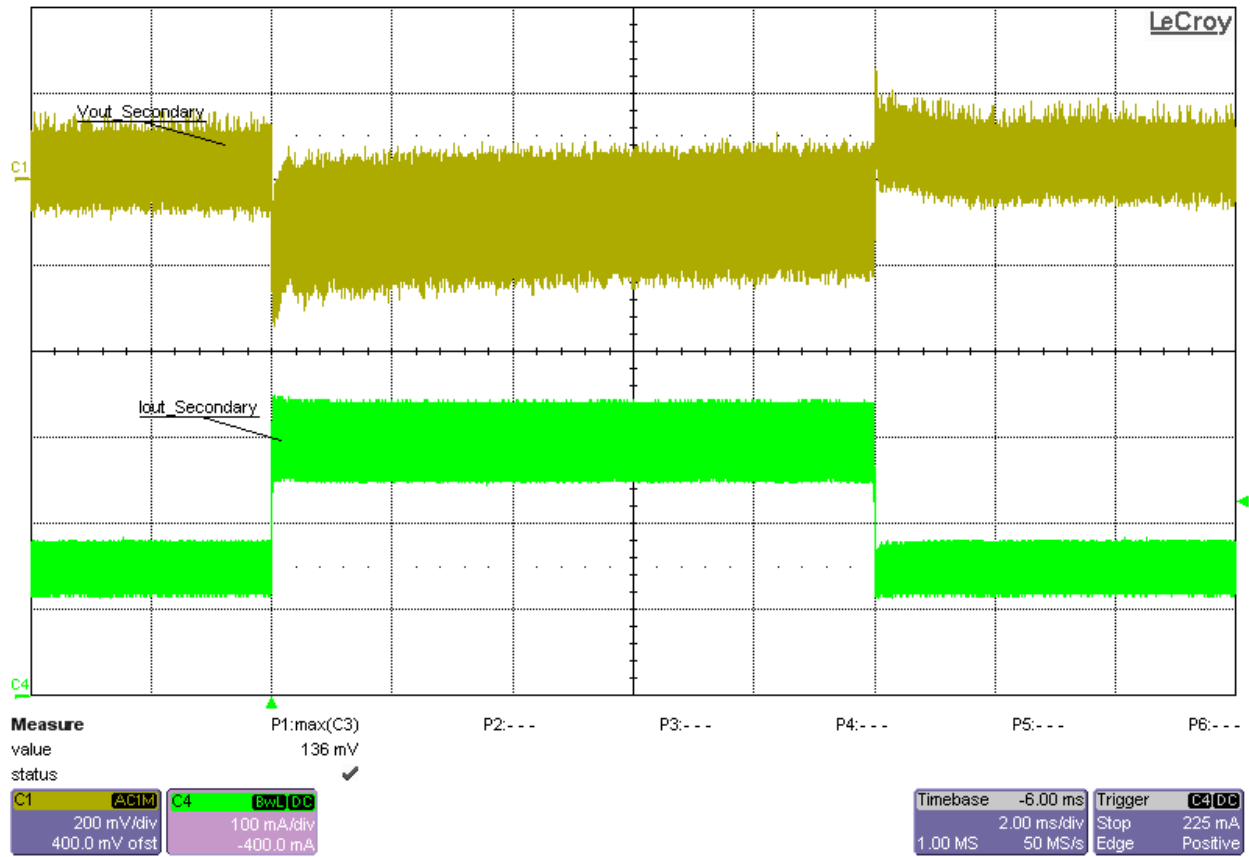Load Transient Response at 10.8V_{in} and 50%-to-100% (150mA-to-300mA) Load Step




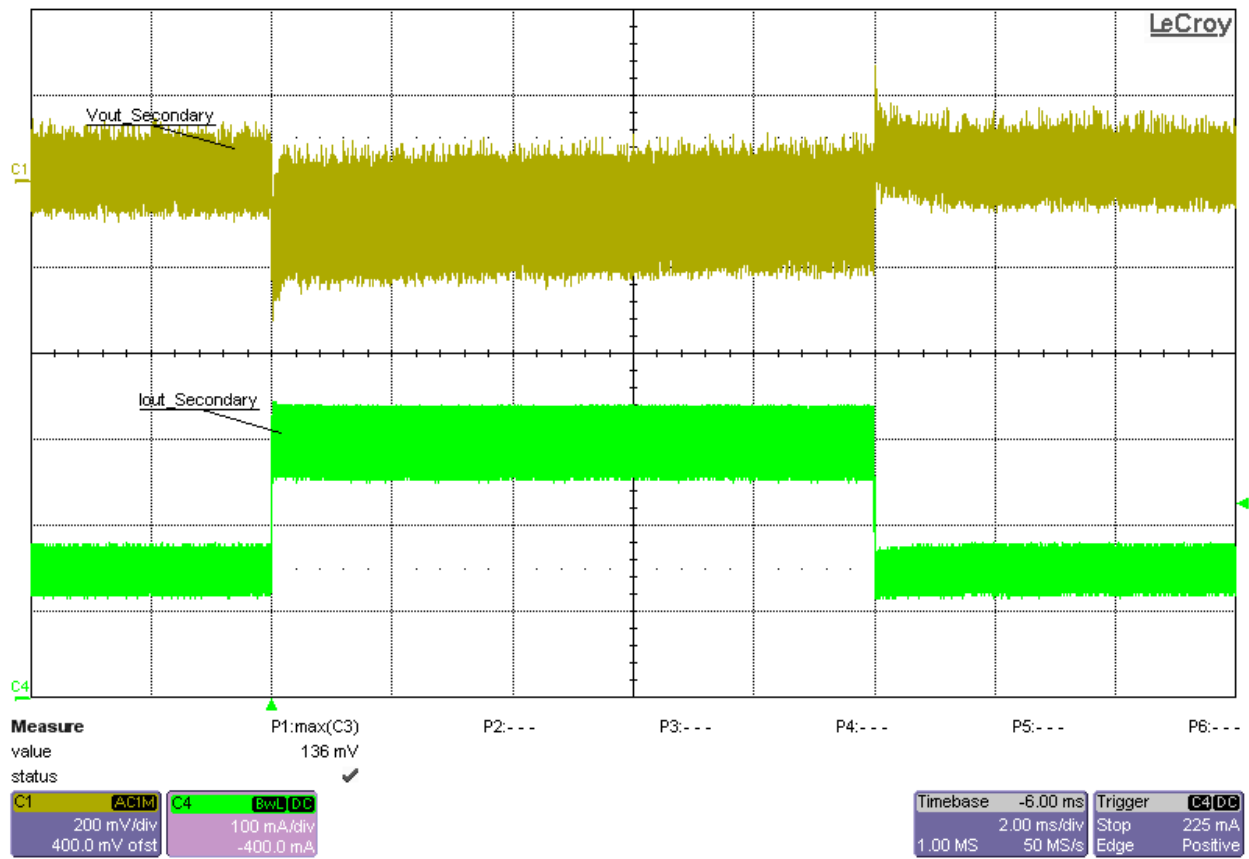Load Transient Response at 12Vin and 50%-to-100% (150mA-to-300mA) Load Step




Load Transient Response at 13.2Vin and 50%-to-100% (150mA-to-300mA) Load Step


6.2 Startup

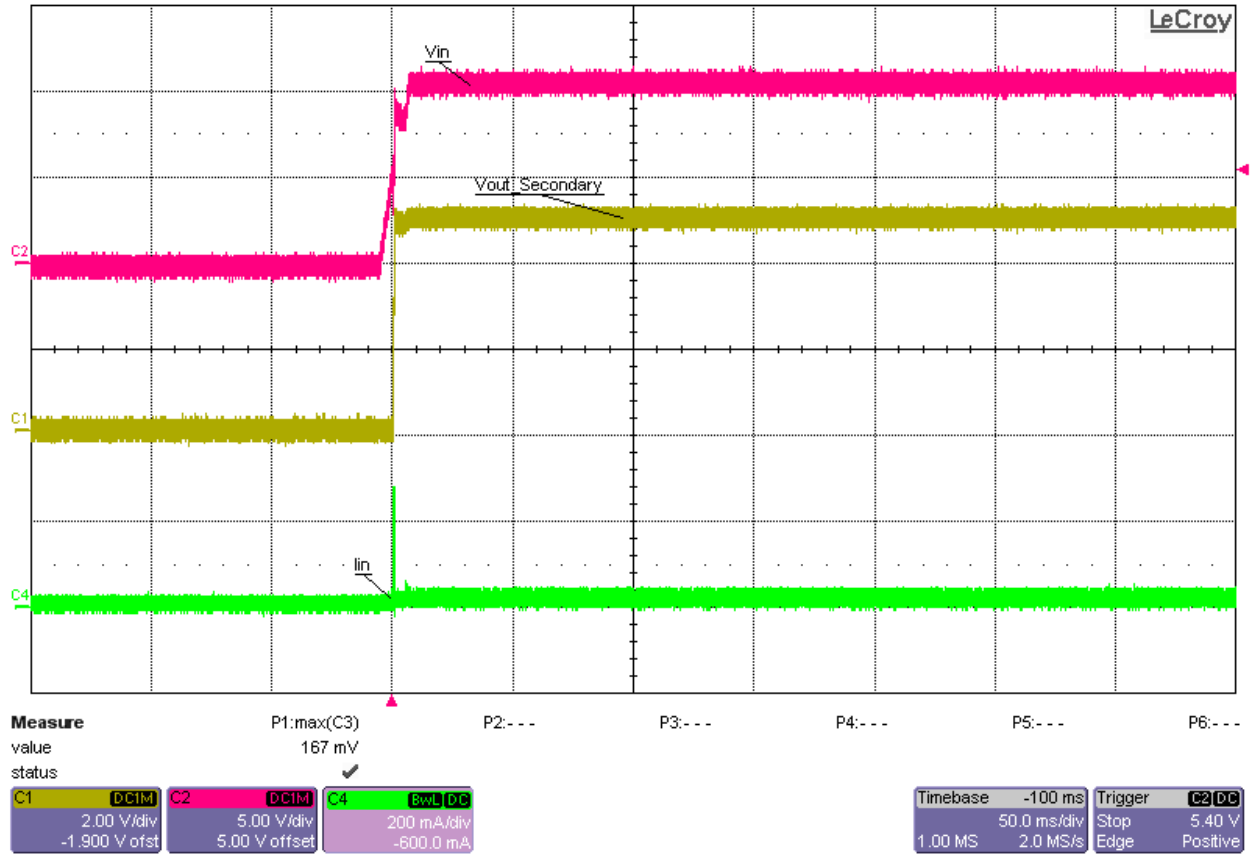


Startup into No Load at 10.8Vin

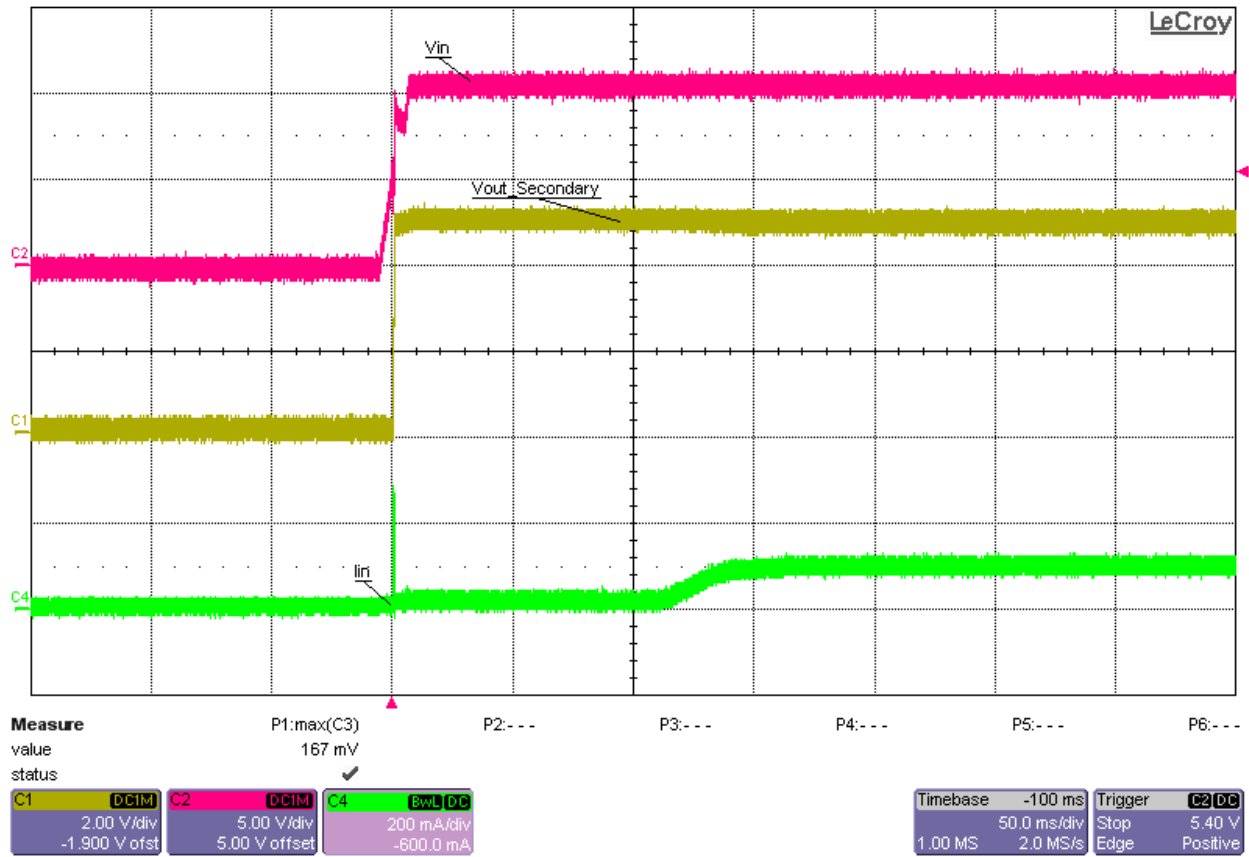

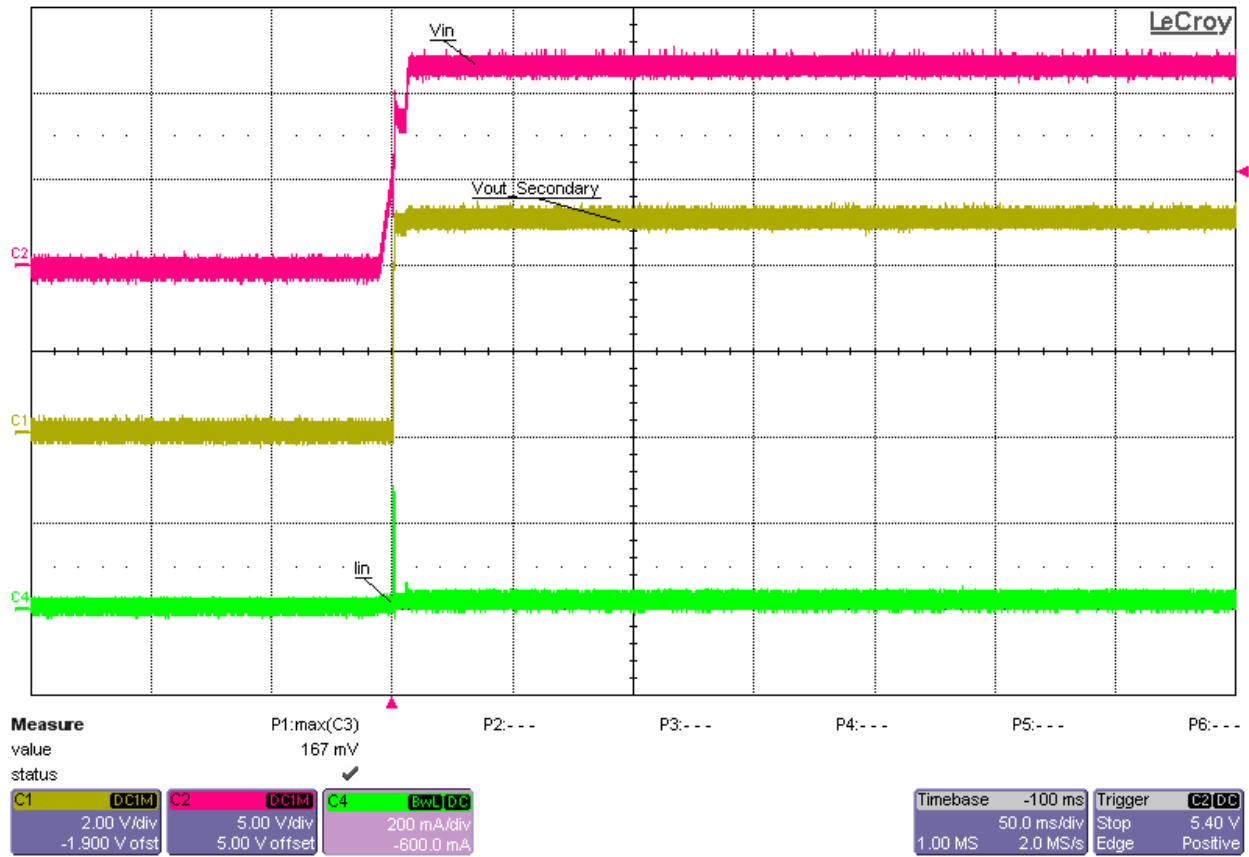
Startup into Full (300mA) Resistive Load at 10.8Vin




Startup into No Load at 12Vin

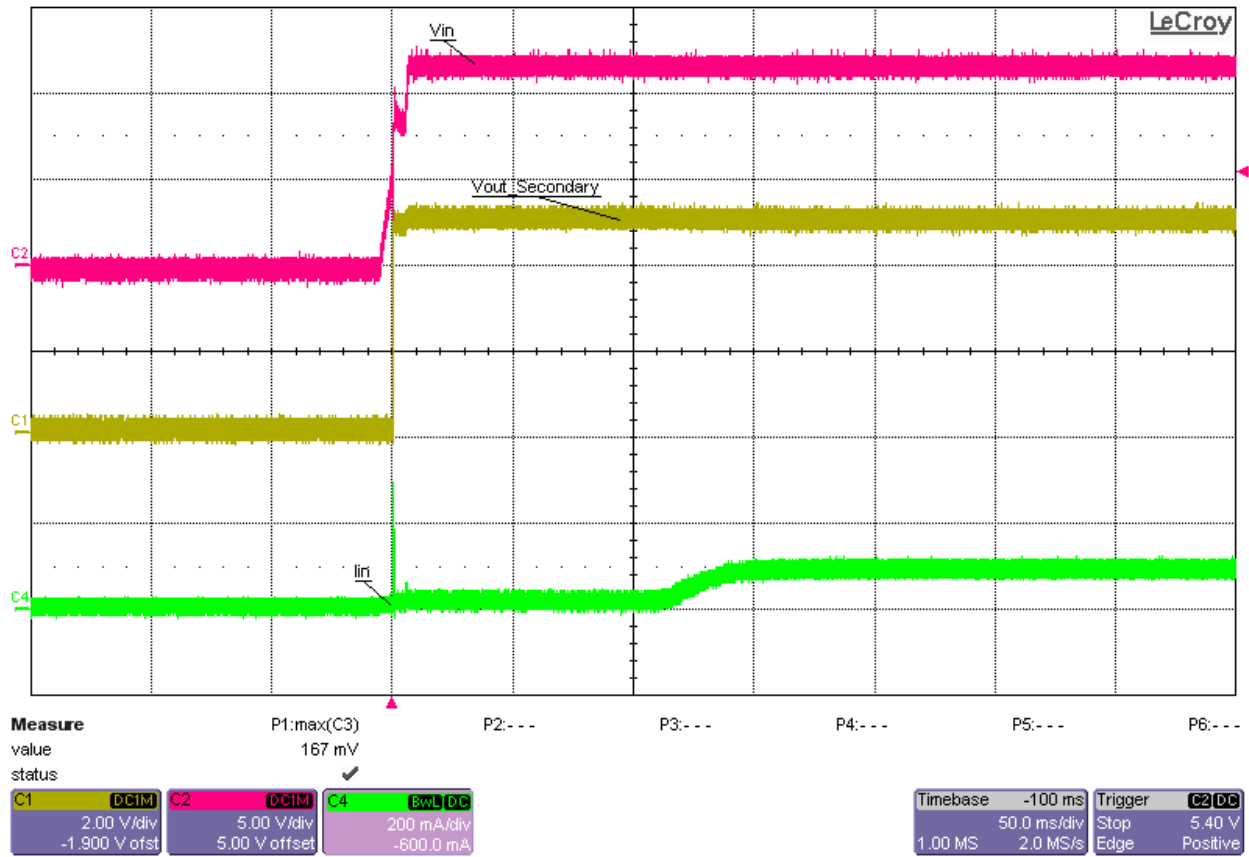

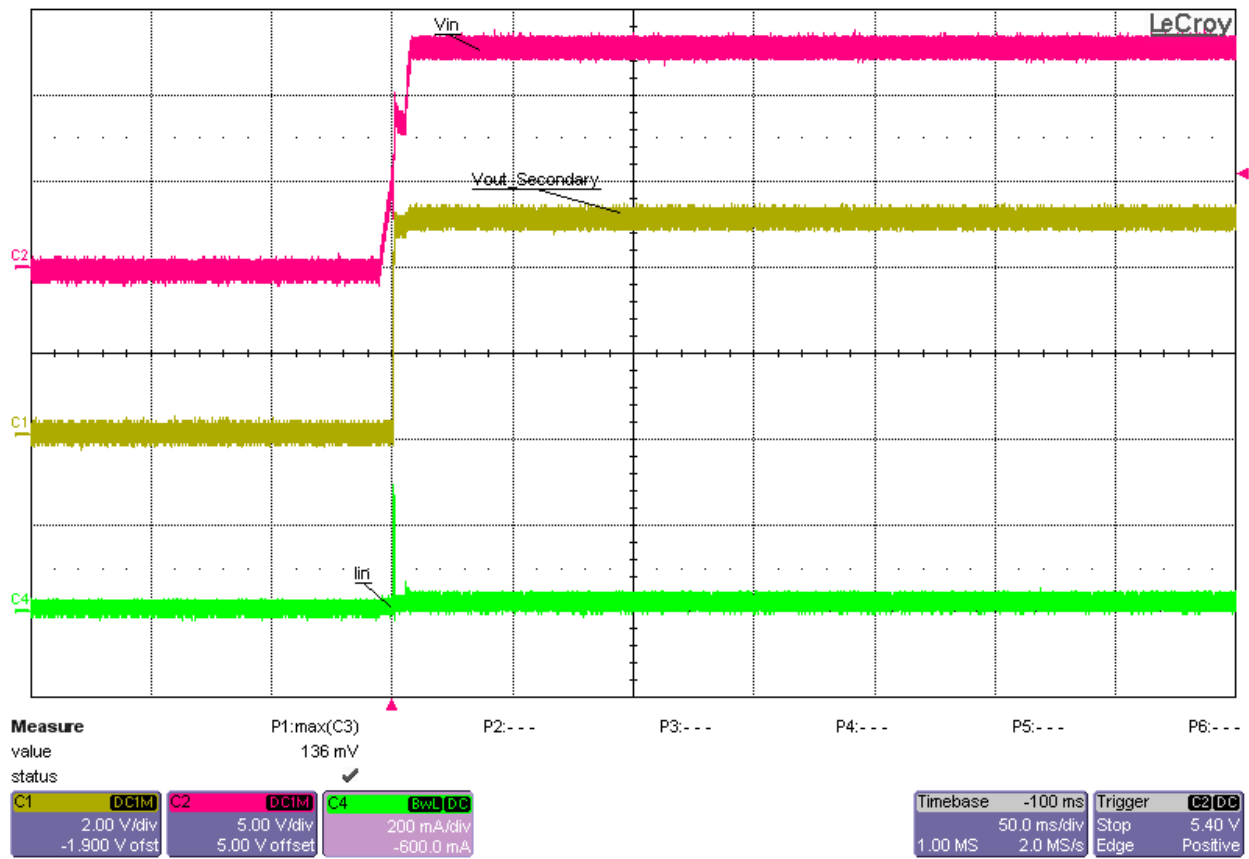Startup into Full (300mA) Resistive Load at 12Vin




Startup into No Load at 13.2Vin

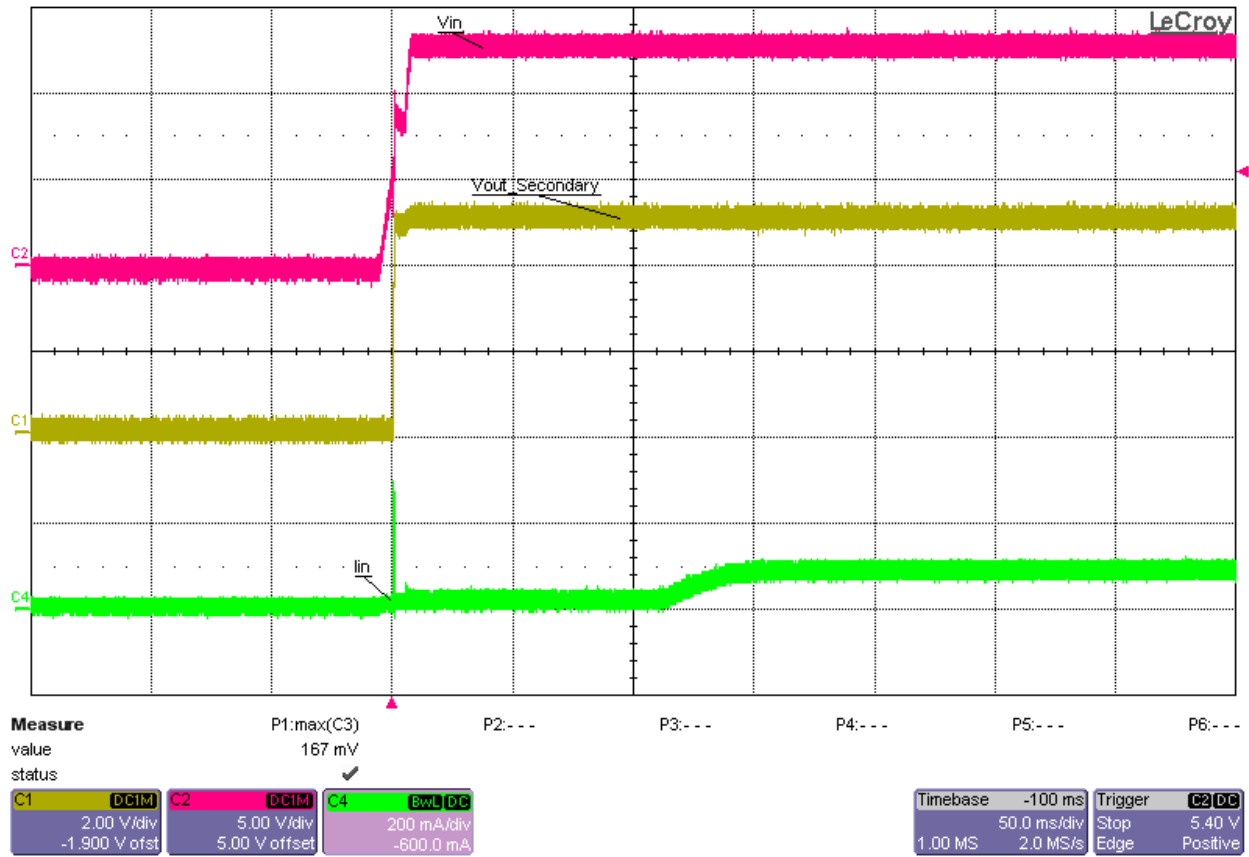


Startup into Full (300mA) Resistive Load at 13.2Vin

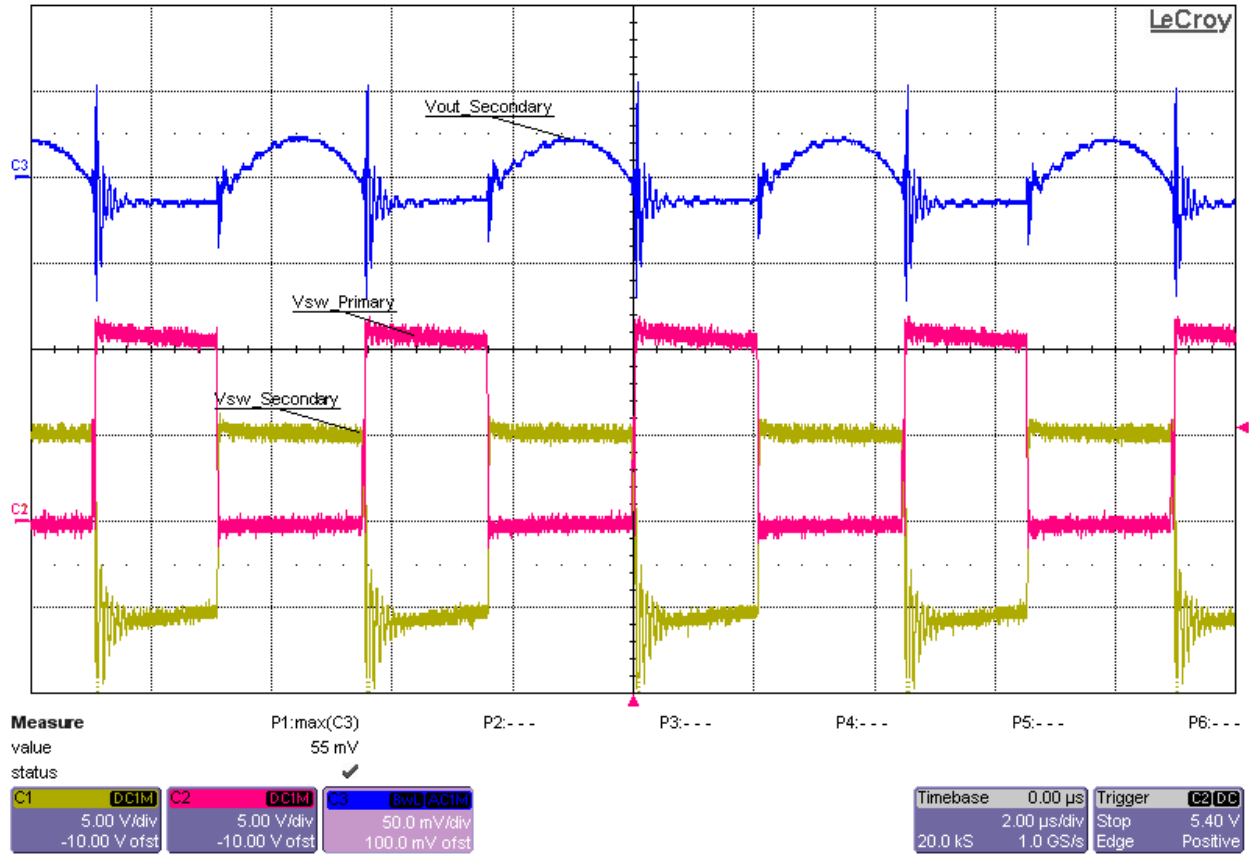6.3 Output Voltage Ripple and Switch Node Voltage




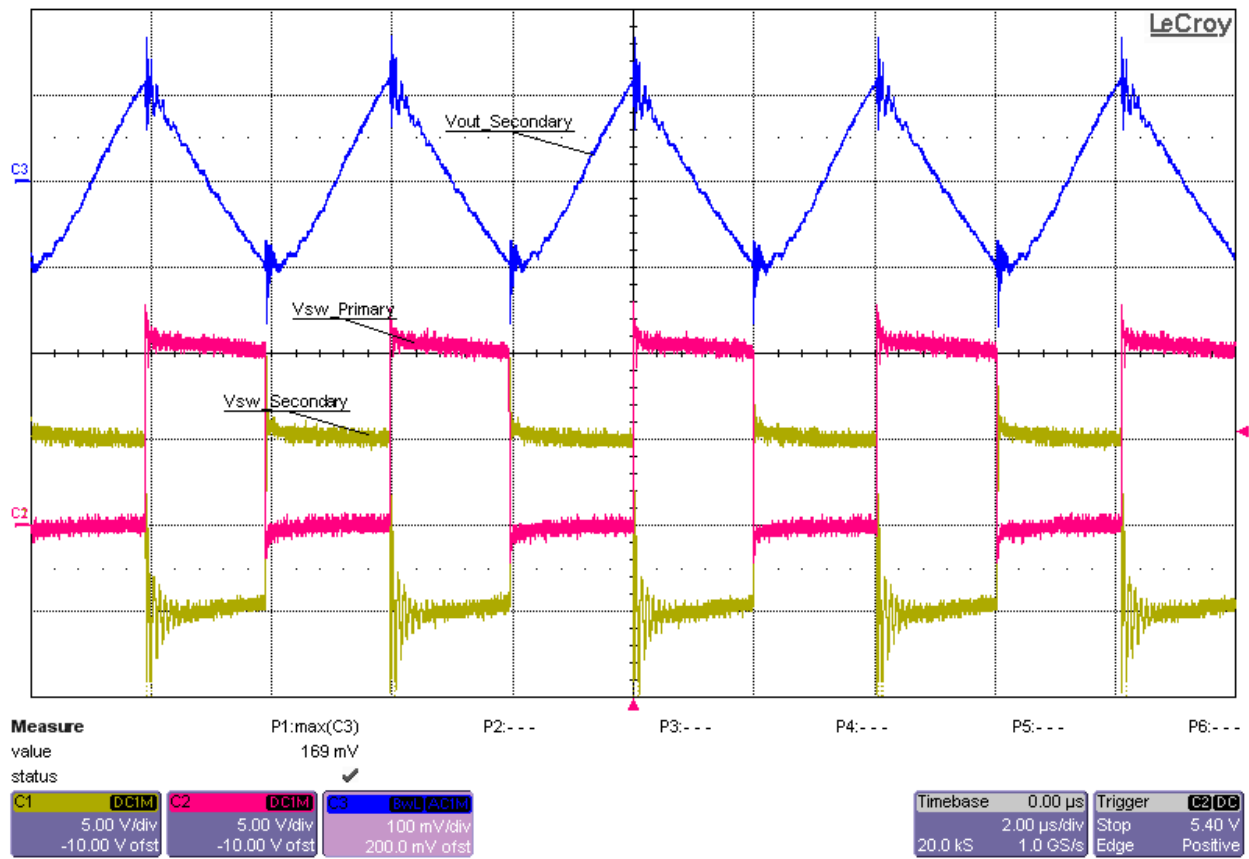Switch Node and Secondary-Side Output Voltage Ripple at 10.8Vin and No Load ($V_{ripple} \approx 43mV_{p-p}$)




Switch Node and Secondary-Side Output Voltage Ripple at 10.8Vin and Full (300mA) Load

(Vripple \approx 230mVp-p)

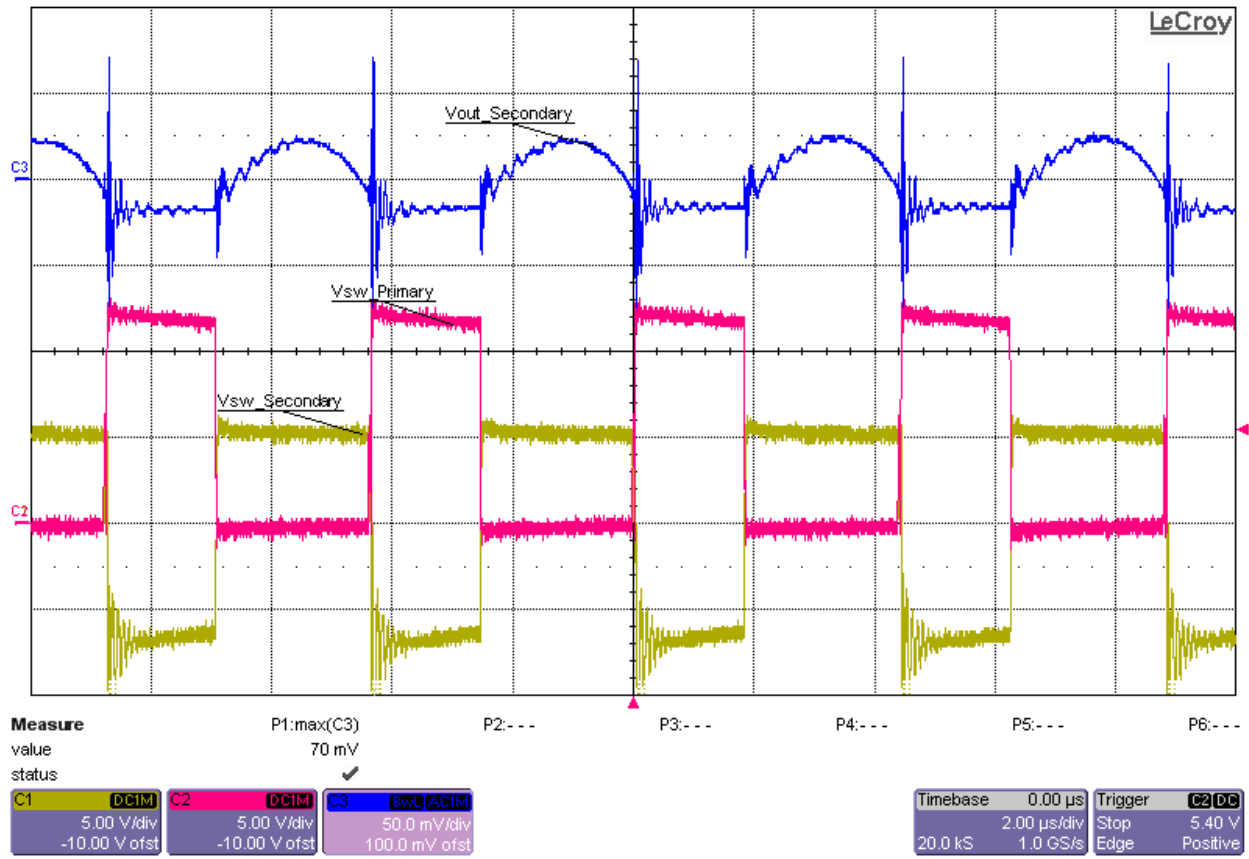


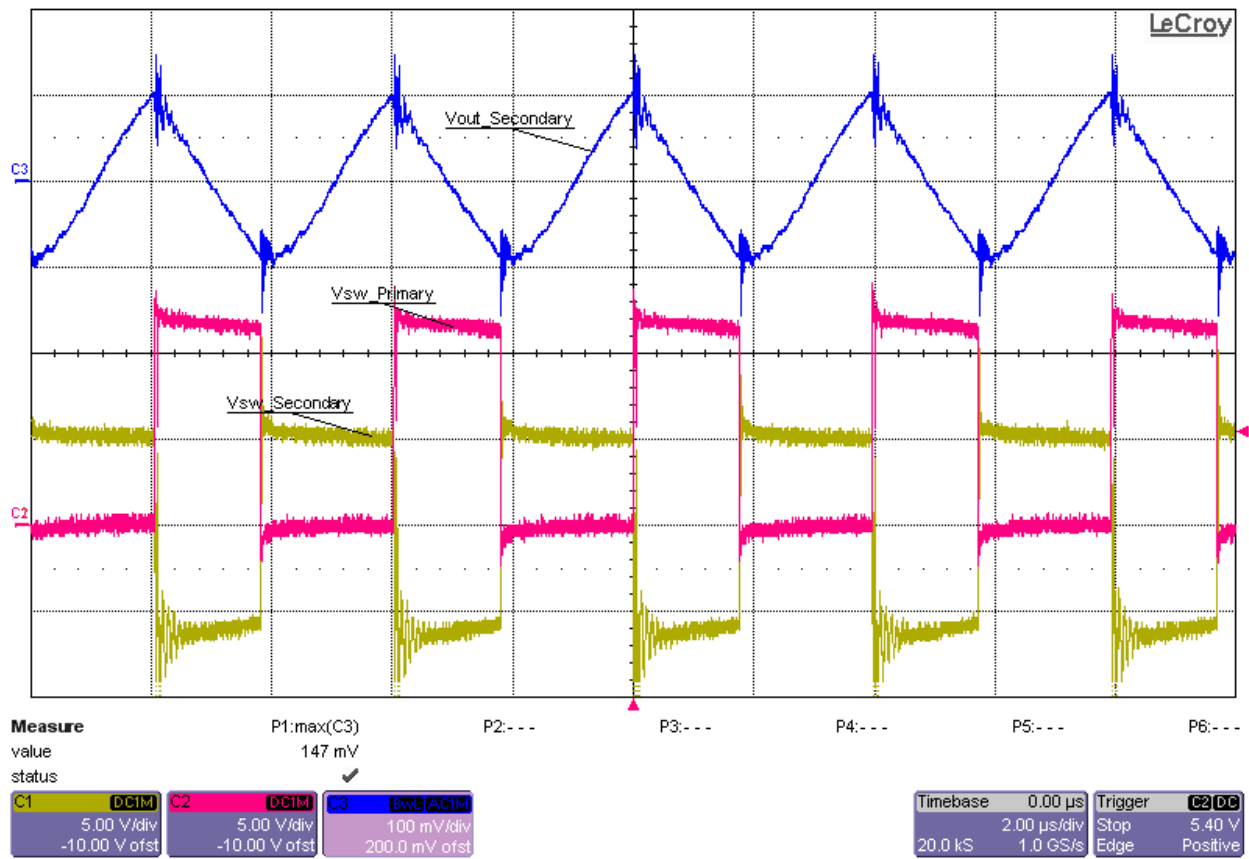Switch Node and Secondary-Side Output Voltage Ripple at 12Vin and No Load ($V_{ripple} \approx 45mV_{p-p}$)




Switch Node and Secondary-Side Output Voltage Ripple at 12Vin and Full (300mA) Load

(Vripple \approx 200mVp-p)

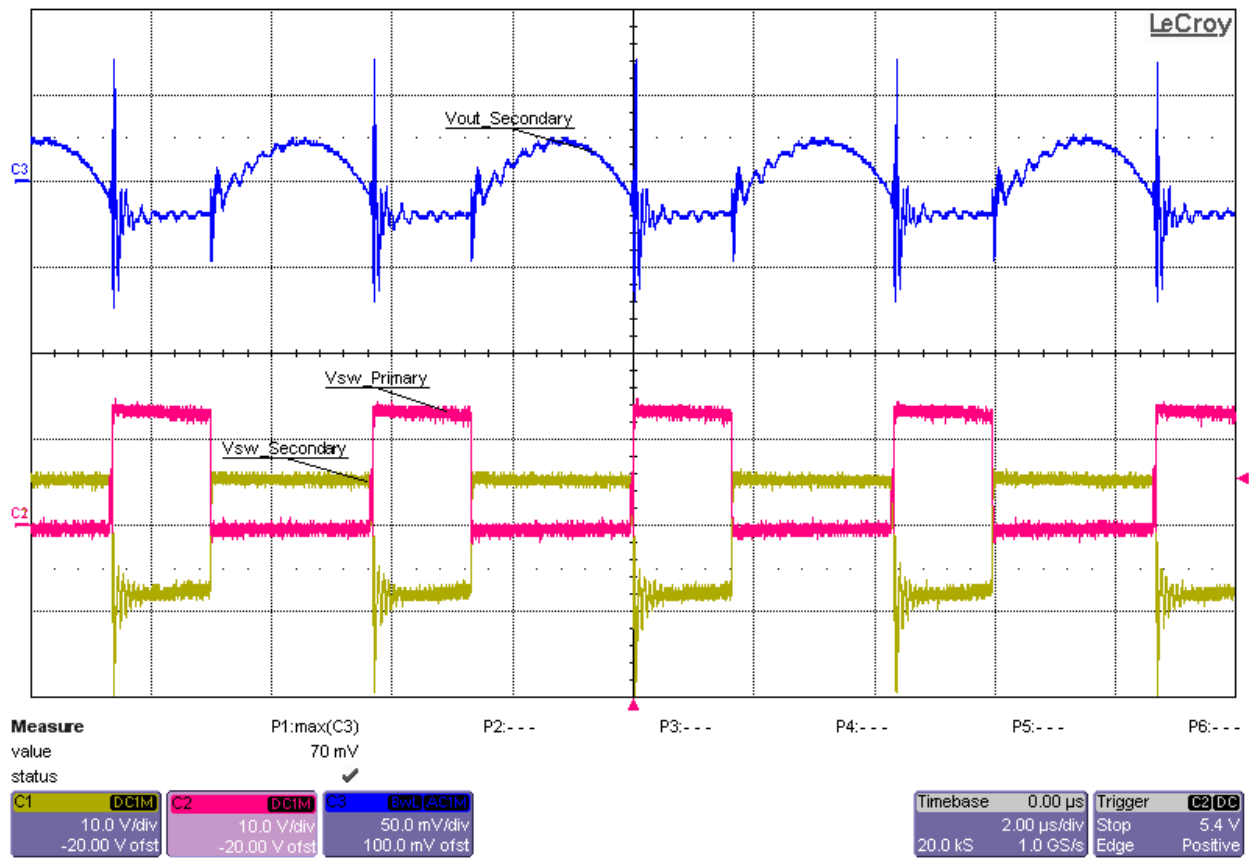

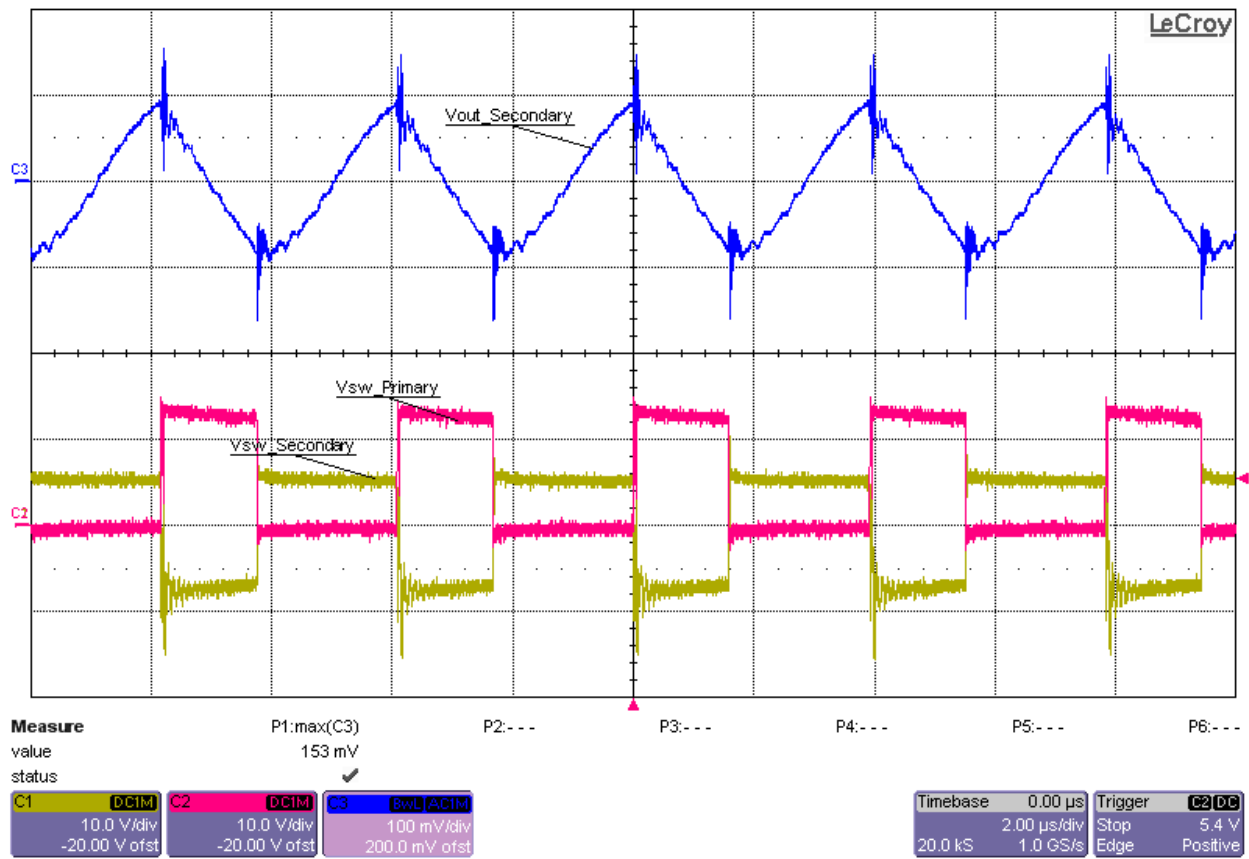
Switch Node and Secondary-Side Output Voltage Ripple at 13.2Vin and No Load ($V_{ripple} \approx 65mVp-p$)




Switch Node and Secondary-Side Output Voltage Ripple at 13.2V_{in} and Full (300mA) Load

(V_{ripple} \approx 180mV_{p-p})


7 Short Circuit Testing

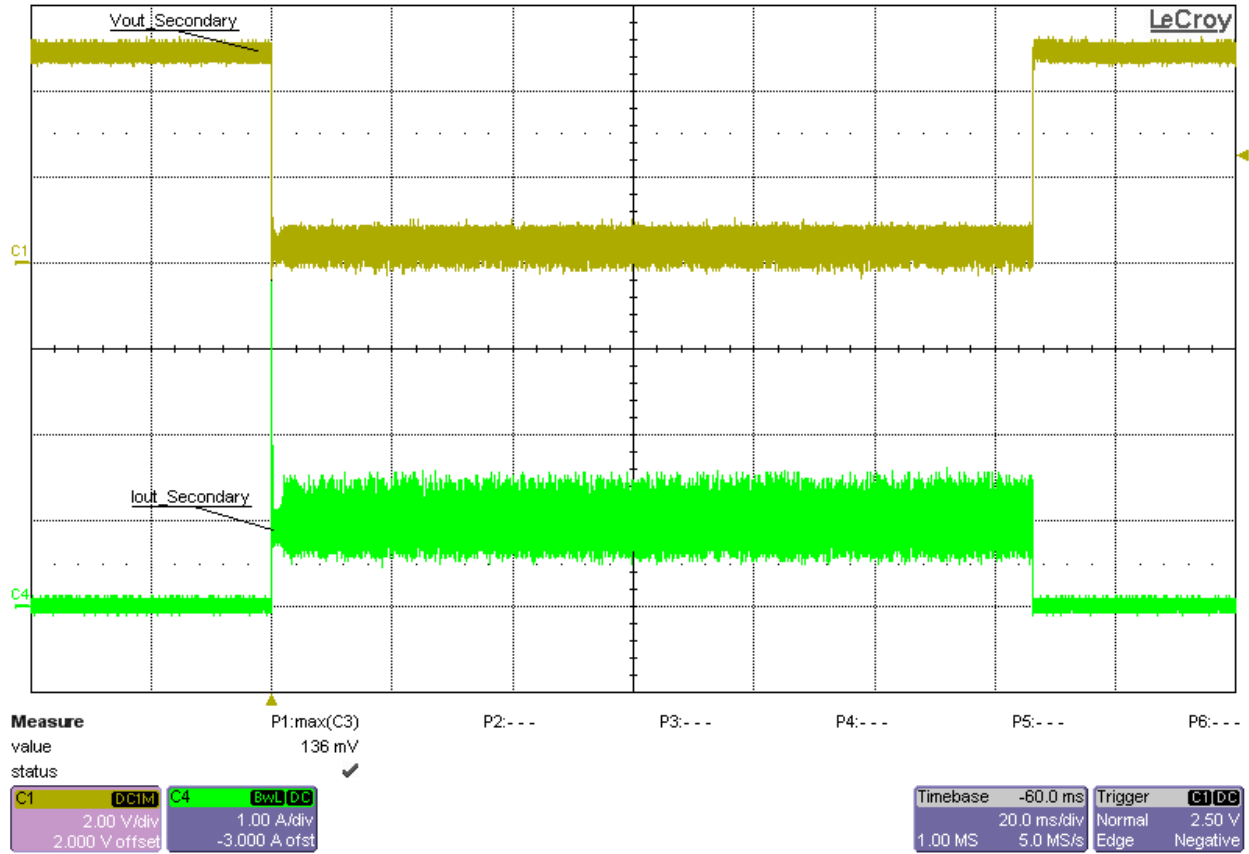

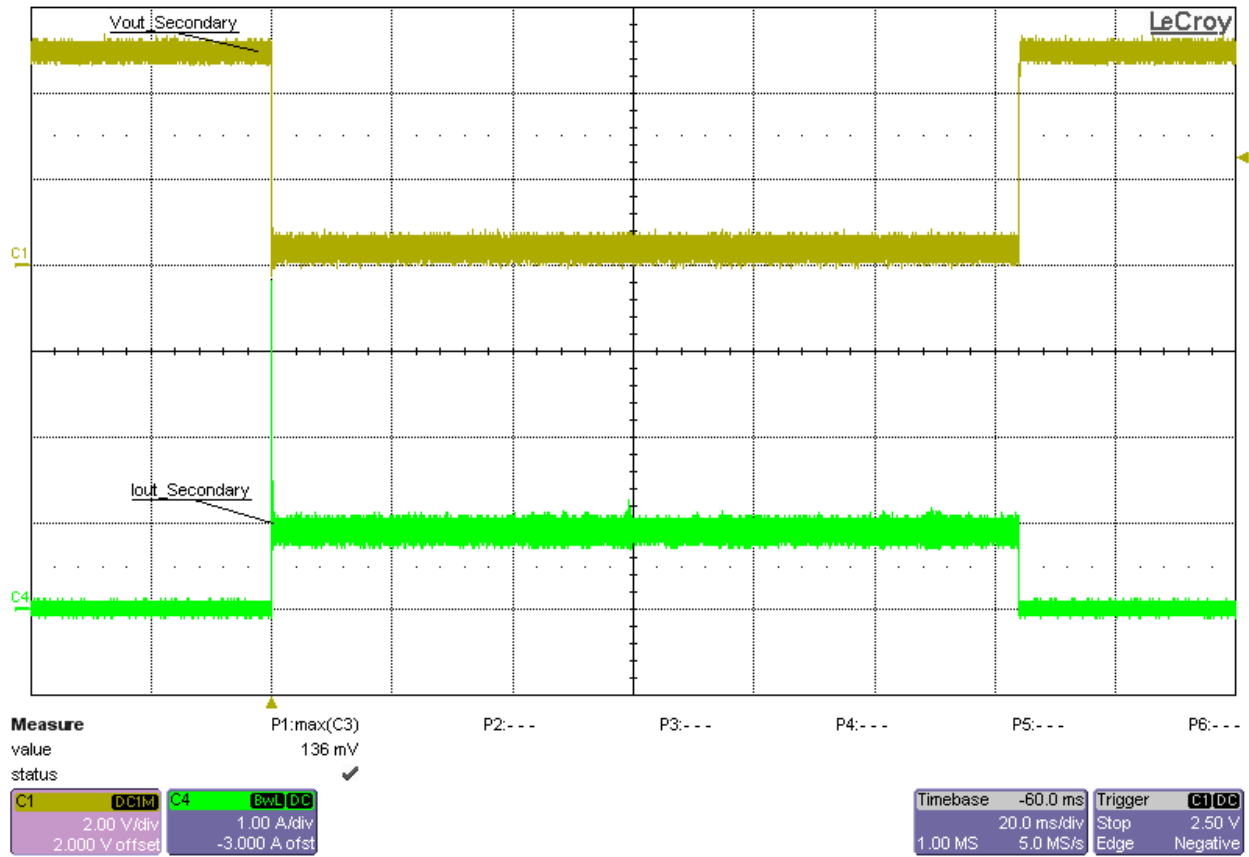Short Circuit Application and Recovery at 10.8Vin (applied from no load, recovered into no load)



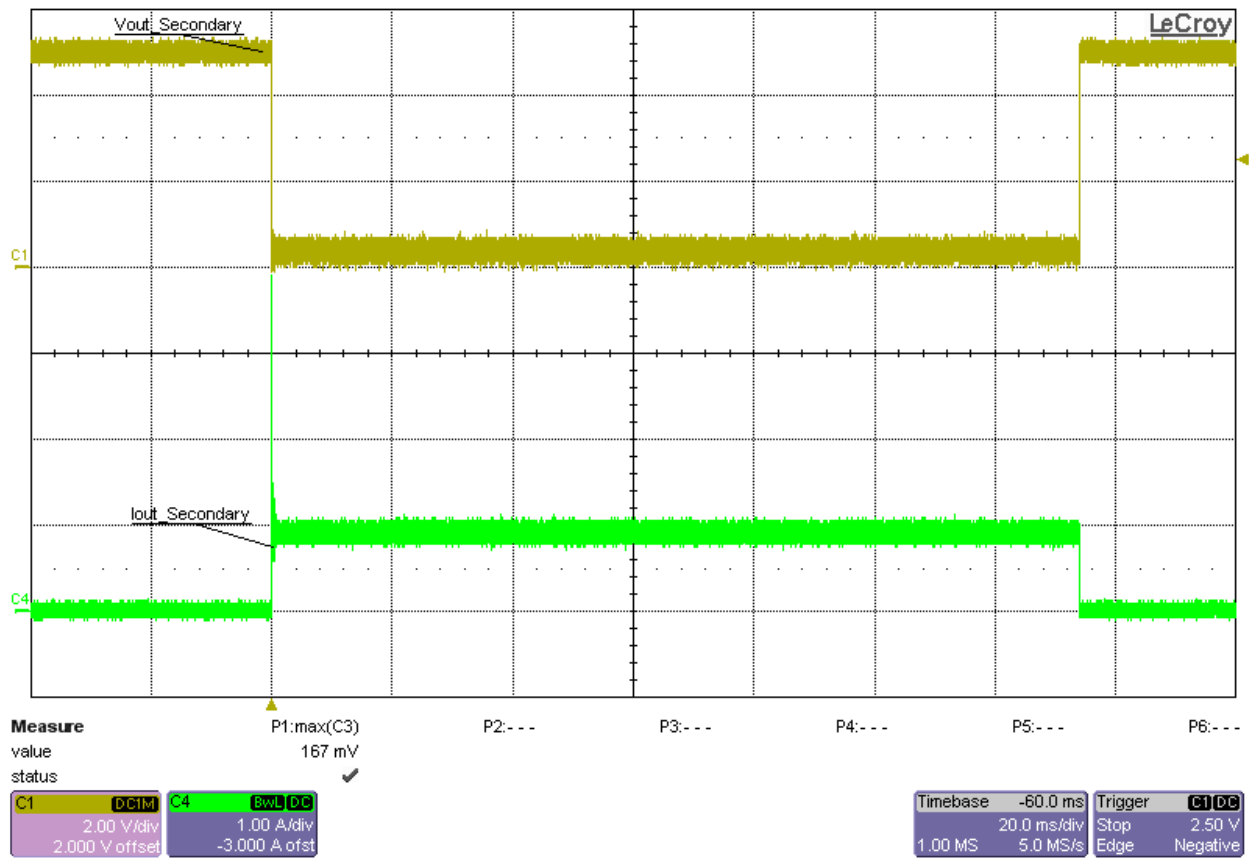Short Circuit Application and Recovery at 12Vin (applied from no load, recovered into no load)



Short Circuit Application and Recovery at 13.2Vin (applied from no load, recovered into no load)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated