

What You Need to Know about Input Bias Current – and Why



Xiyao Zhang

One of my standard interview questions for new college graduates is to describe the non-ideal aspects of an operational amplifier (op amp). While most candidates start with open-loop gain, offset voltage, bandwidth and noise, only a few mention input bias current. Even experienced circuit designers often have questions about input bias current and its effects. In this post, I'll answer some of these questions and hopefully clear up some misconceptions.

Q: What Is Input Bias Current?

A: The term “input bias current” (I_B) in datasheets – for both op amps and fully differential amplifiers (FDAs) – refers to the DC currents flowing into or out of the amplifier’s input pins to create a defined operating point during normal operation, as shown in Figure 1.

 


Figure 1. Definition of Input Bias Current for a Simple PNP Input Stage

Because a MOSFET requires very little DC gate current to operate, the input bias current of a CMOS amplifier is dominated by leakage from electrostatic discharge (ESD) protection cells and other secondary circuits connected to the inputs. The magnitude of this leakage current is small – on the order of picoamps (pA). Since the inputs of bipolar junction transistor (BJT) amplifiers require base currents for proper bias, however, the BJT input bias current is a lot larger – on the order of microamps (μA). Hence, input bias current is an important issue for BJT amplifiers.

Q: Why Do You Need BJT-input Amplifiers?

A: Since CMOS amplifiers have almost negligible input bias currents, why do you even need BJT amplifiers? The answer is that a BJT has much larger transconductance (g_m) compared to a CMOS transistor at the same quiescent current. In addition, matching between BJTs is also a lot better, and so is its flicker (or $1/f$ noise). All three advantages are crucial for high-speed precision amplifiers; hence, BJT inputs are ubiquitous in high-performance op amps and FDAs.

Q: How Do You Evaluate the Effects of Input Bias Currents?

A: While using amplifiers with significant input bias currents often requires some additional design considerations, you might be surprised to find how little they actually affect system performance. Once you understand the effects of input bias current, you can weigh the benefits of a BJT-input amplifier against these effects.

Let's investigate the effects of input bias currents using the FDA circuit shown in Figure 2. The THS4551 is the newest addition to TI's family of precision analog-to-digital converter (ADC) drivers. The THS4551 features not only 150MHz bandwidth on 1.35mA I_{q1} , but also $\pm 2\mu\text{V}/^\circ\text{C}$ max V_{OS} drift, as shown in Table 1. The BJT-input architecture enables such performance but creates a notable I_B .

 


Figure 2. THS4551 FDA Circuit with 1% Resistors

Table 1. Key Input-referred DC Parameters of the THS4551

V_{IO}	Input-referred offset voltage	$T_A = 25^\circ\text{C}$	-175	± 50	175	μV
		$T_A = 0^\circ\text{C}$ to $+70^\circ\text{C}$	-225		265	
		$T_A = -40^\circ\text{C}$ to $+85^\circ\text{C}$	-295		295	
		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$	-295		375	
	Input offset voltage drift ⁽⁴⁾	$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$ (DGK package)	-2.0	± 0.45	2.0	$\mu\text{V}/^\circ\text{C}$
I_B	Input bias current (positive current out of node)	$T_A = 25^\circ\text{C}$	0.55	1.0	1.5	μA
		$T_A = 0^\circ\text{C}$ to $+70^\circ\text{C}$	0.41		1.75	
		$T_A = -40^\circ\text{C}$ to $+85^\circ\text{C}$	0.2		1.83	
		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$	0.2		2.05	
	Input bias current drift ⁽⁴⁾	$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$ (DGK package)	2	3.3	5.5	$\text{nA}/^\circ\text{C}$
I_{OS}	Input offset current	$T_A = 25^\circ\text{C}$	-50	± 10	50	nA
		$T_A = 0^\circ\text{C}$ to $+70^\circ\text{C}$	-57		63	
		$T_A = -40^\circ\text{C}$ to $+85^\circ\text{C}$	-68		67	
		$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$	-68		78	
	Input offset current drift ⁽⁴⁾	$T_A = -40^\circ\text{C}$ to $+125^\circ\text{C}$ (DGK package)	-280	± 70	280	$\text{pA}/^\circ\text{C}$

Focusing on the mathematically simplest case, let's first assume that the FDAs are always connected with symmetrical feedback elements, since this leads to minimum signal conversion from the common-mode errors to the differential output.

You can calculate the "output referred" offset voltage V_{OOS} in two steps. First, find the amplifier's positive and negative summing-junction voltages using Equation 1:

$$V_{SJ\pm} = I_{B\pm} \times Z_{SJ\pm} = I_{B\pm} \times (R_{G\pm} || R_{F\pm}) \quad (1)$$

Then, use Equation 2 to calculate V_{OUT} based on the gain from the summing junction to the output, which is the noise gain:

$$V_{OUT\mp} = V_{SJ\pm} \times NG_{\pm} = V_{SJ\pm} \times \left(1 + \frac{R_{F\pm}}{R_{G\pm}}\right) = V_{SJ\pm} \times \left(\frac{R_{F\pm}}{R_{G\pm} || R_{F\pm}}\right) \quad (2)$$

Combining Equations 1 and 2 together, you can calculate V_{OOS} at the output as the difference between these two output voltages with Equation 3:

$$V_{OUT\mp} = I_{B\pm} \times (R_{G\pm} || R_{F\pm}) \times \left(\frac{R_{F\pm}}{R_{G\pm} || R_{F\pm}}\right) = I_{B\pm} \times R_{F\pm}$$

$$V_{OOS} = (I_{B+} \times R_{F+}) - (I_{B-} \times R_{F-}) \quad (3)$$

The output V_{OOS} is simply the difference between the input bias currents on each side, multiplied by their respective feedback-resistor values (R_F). The gain resistor (R_G) has dropped out of the V_{OOS} equation. Intuitively, this is because a small R_G , which would have reduced the impact of I_B on the summing-junction voltage, also increases the noise gain from summing junction to output, and the two effects cancel each other.

Let's use the circuit in [Figure 2](#) and the specs of the THS4551 in [Table 1](#) to calculate the worst-case output V_{OOS} from each contributing factor (input V_{OS} , I_B and I_{OS}), listed in [Table 2](#).

Table 2. THS4551 Output Referred Offset Voltage Terms for $R_F=1k\Omega$, 1%

Contributing factor	25°C max error	Worst gain to output	Worst-case contribution to output V_{OOS} (μV)	Gained up by
Input V_{OS}	$\pm 175\mu V$	3.04V/V	± 532	Noise gain
$I_{B\pm}$	1.5 μA	$\pm 20\Omega$	± 30	Feedback resistor mismatch
I_{OS}	$\pm 50nA$	1.01k Ω	± 50.5	Feedback resistor

Now, let's look at four cases for different resistor values and tolerances in the circuit. For two values of R_F (1k Ω and 5k Ω) and two tolerances (1% and 0.1%), [Table 3](#) shows the results.

Table 3. THS4551 Output Referred Offset Voltage Terms for Different R_F Choices

Case	R_F (k Ω)	R_F tolerance (%)	Worse-case output V_{OOS} terms (μV)		
			V_{OS}	$I_{B\pm}$	I_{OS}
1	1	1	± 532	± 30	± 50.5
2	1	0.1	± 526	± 3	± 50.1
3	5	1	± 532	± 150	± 252.5
4	5	0.1	± 526	± 15	± 250.3

Similarly, [Table 4](#) shows the results for the output-offset drift.

Table 4. THS4551 Output Referred Offset Drift Terms for Different R_F Choices

Case	R_F (k Ω)	R_F tolerance (%)	Worse-case output V_{OOS} drift terms ($\mu V/^\circ C$)		
			V_{OS}	$I_{B\pm}$	I_{OS}
1	1	1	± 6.1	± 0.11	± 0.283
2	1	0.1	± 6	± 0.01	± 0.28
3	5	1	± 6.1	± 0.55	± 1.41
4	5	0.1	± 6	± 0.06	± 1.4

A couple of takeaways:

- A well-designed BJT-input FDA or op amp should be able to handle several kilo-ohms of R_F without much effect on DC performance.
- When DC performance is a concern, consider improving the resistor R_F and R_G tolerances to 0.1%, which is a simple and inexpensive method to mitigate the negative effects of I_B .

Q: What about Input-current Noise?

A: Most of this post is about the impact of I_B and I_{OS} on offset voltage and offset-voltage drift. Another important effect of input current is added noise. Luckily, noise is just a time-varying offset, so you can calculate the effect of noise just as you calculated the effect of offset. For example, the output-voltage noise due to the input-current noise is simply

Another issue worth mentioning is internal input-bias cancellation. Various cancellation techniques can usually reduce I_B from the level of microamps to nanoamps. The I_{OS} will also be reduced, although not nearly as much. However, these cancellation techniques usually increase input-current noise due to uncorrelated noise from the cancellation current. So if noise limits your system's performance, input-bias cancellation is likely not the right choice.

Conclusion

Compared to CMOS-input amplifiers, BJT-input op amps and FDAs offer many benefits: higher bandwidth at lower power, lower voltage noise and 1/f noise, and better DC precision. They come with one catch, however: higher input bias currents. With careful design, you can evaluate and mitigate the negative effects of the higher input bias currents.

What is your experience dealing with issues due to input bias current? I have only scratched the surface of I_B effects, and haven't mentioned many secondary issues. What more do you want to know? Log in below and leave a comment.

Additional Resources

- Read more about the [THS4551](#) and learn about the equations involving FDA offset calculations.
- Check out this module on input bias current from [TI Precision Labs](#).
- Learn about TI's entire portfolio of [high-speed op amps](#) and explore related technical resources.

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated