


Test Report: PMP21727

Dual output SEPIC converter bias power supply reference design for solar panel applications



Description

 This non-isolated design supplies a regulated 3.3 V/0.5 A and an unregulated 10 V/0.1 A for solar applications. It operates over a dual solar panel input voltage range of 7 V - 45 V and offers low cost and a compact form factor. This SEPIC converter features minimal voltage ringing on the FET for lower stress and reduced EMI.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements

Table 1. Voltage and Current Requirements


PARAMETER	SPECIFICATIONS
Input voltage range	7 - 45V
Output voltage and current	3.3V @ 0.5A and 10V @ 0.1A
Switching frequency	150kHz
Isolation	No

1.2 Required Equipment

- Dual electronic loads (2W min each) or power resistors (resistor decade box)
- Power supply capable of handling 50V and 1A
- Oscilloscope and probes
- Digital Multimeters
- Stability measurement device (Venable or Bode)

2 Testing and Results

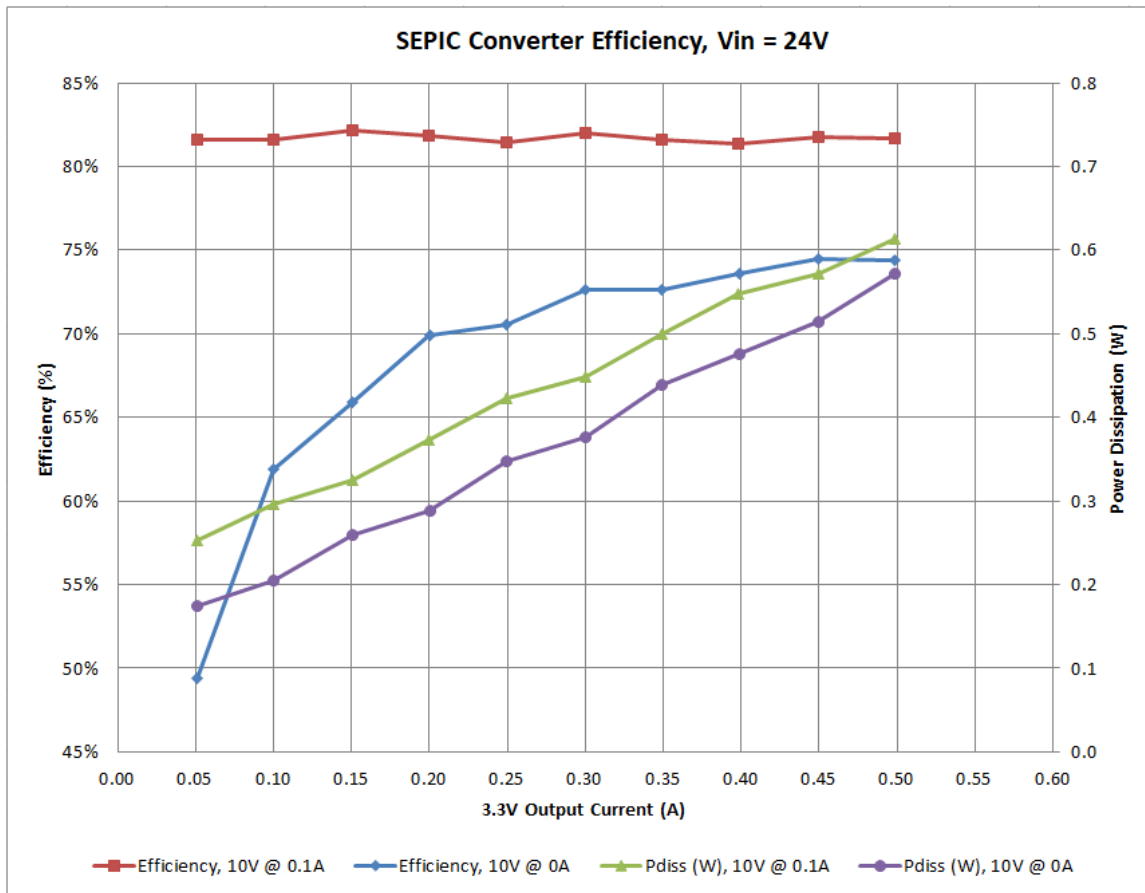2.1 Efficiency and Power Dissipation Graphs



This graph displays the efficiency and power dissipation of the converter with the 10V at full load and zero loads.

2.2 Efficiency and Power Dissipation Data

Vin	Iin	Vout1	Iout1	Vout2	Iout2	Po	Pin	Efficiency, 10V @ 0.1A	Pdiss (W), 10V @ 0.1A
24.0445	0.0572	3.3353	0.0507	9.726	0.09795	1.122	1.375	81.6%	0.254
24.0415	0.0668	3.3351	0.0999	9.850	0.09919	1.310	1.606	81.6%	0.296
24.0430	0.0759	3.3353	0.1508	9.948	0.10018	1.500	1.825	82.2%	0.325
24.0406	0.0854	3.3352	0.1999	10.029	0.10100	1.680	2.053	81.8%	0.373
24.0404	0.0949	3.3351	0.2492	10.100	0.10171	1.858	2.281	81.5%	0.423
24.0409	0.1035	3.3353	0.3000	10.162	0.10234	2.041	2.488	82.0%	0.448
24.0332	0.1130	3.3353	0.3493	10.213	0.10285	2.215	2.716	81.6%	0.500
24.0324	0.1221	3.3349	0.3983	10.255	0.10327	2.387	2.934	81.4%	0.547
24.0250	0.1306	3.3354	0.4494	10.292	0.10365	2.566	3.138	81.8%	0.572
24.0020	0.1395	3.3354	0.4984	10.323	0.10396	2.736	3.348	81.7%	0.613

This table shows the efficiency data for the converter with the 10V @ 0.1A.

Vin	Iin	Vout1	Iout1	Vout2	Iout2	Po	Pin	Efficiency, 10V @ 0A	Pdiss (W), 10V @ 0A
24.0511	0.0143	3.3355	0.0509	10.134	0	0.170	0.344	49.4%	0.174
24.0479	0.0224	3.3354	0.1000	10.354	0	0.334	0.539	61.9%	0.205
24.0475	0.0317	3.3353	0.1507	10.528	0	0.503	0.762	65.9%	0.260
24.0462	0.0397	3.3354	0.2000	10.676	0	0.667	0.955	69.9%	0.288
24.0448	0.0490	3.3352	0.2492	10.815	0	0.831	1.178	70.5%	0.347
24.0433	0.0573	3.3353	0.3000	10.952	0	1.001	1.378	72.6%	0.377
24.0416	0.0667	3.3353	0.3493	11.080	0	1.165	1.604	72.7%	0.439
24.0400	0.0751	3.3353	0.3985	11.205	0	1.329	1.805	73.6%	0.476
24.0389	0.0837	3.3353	0.4492	11.329	0	1.498	2.012	74.5%	0.514
24.0336	0.0930	3.3352	0.4986	11.447	0	1.663	2.235	74.4%	0.572


This table shows the efficiency data for the converter with the 10V @ 0A.

2.2.1 Cross Regulation

Voltage Regulation Data				
VIN (V)	VOUT 3.3V (V)	IOUT 3.3V (A)	VOUT 10V (V)	IOUT 10V (A)
No Load Conditions				
7	3.334	0	9.371	0
24	3.334	0	9.395	0
45	3.334	0	9.395	0
Full Load Conditions				
7	3.334	0.5	10.476	0.1
24	3.335	0.5	10.327	0.1
45	3.337	0.5	10.286	0.1
Cross Loading				
7	3.334	0	8.939	0.1
7	3.334	0.5	11.296	0
24	3.335	0	8.618	0.1
24	3.335	0.5	11.447	0
45	3.337	0	8.558	0.1
45	3.337	0.5	11.423	0
			10.193	High/Low Avg (V)
			-12.30	Percent Low (%)
			12.30	Percent High (%)

This table shows the voltage regulation on the unregulated 10V output under various cross load conditions. The high and low levels are highlighted in yellow.

2.3 Loop Gain

 

100

Frequency

100 k

3V@0.5A, 10V@0.1A

Vin = 7V

Bandwidth = 6.32 kHz

Phase Margin = 69 degrees

3V@0.5A, 10V@0.1A

Vin = 24V

Bandwidth = 3.39 kHz


Phase Margin = 89 degrees

3V@0.5A, 10V@0.1A

Vin = 45V

Bandwidth = 8.67 kHz

Phase Margin = 81 degrees

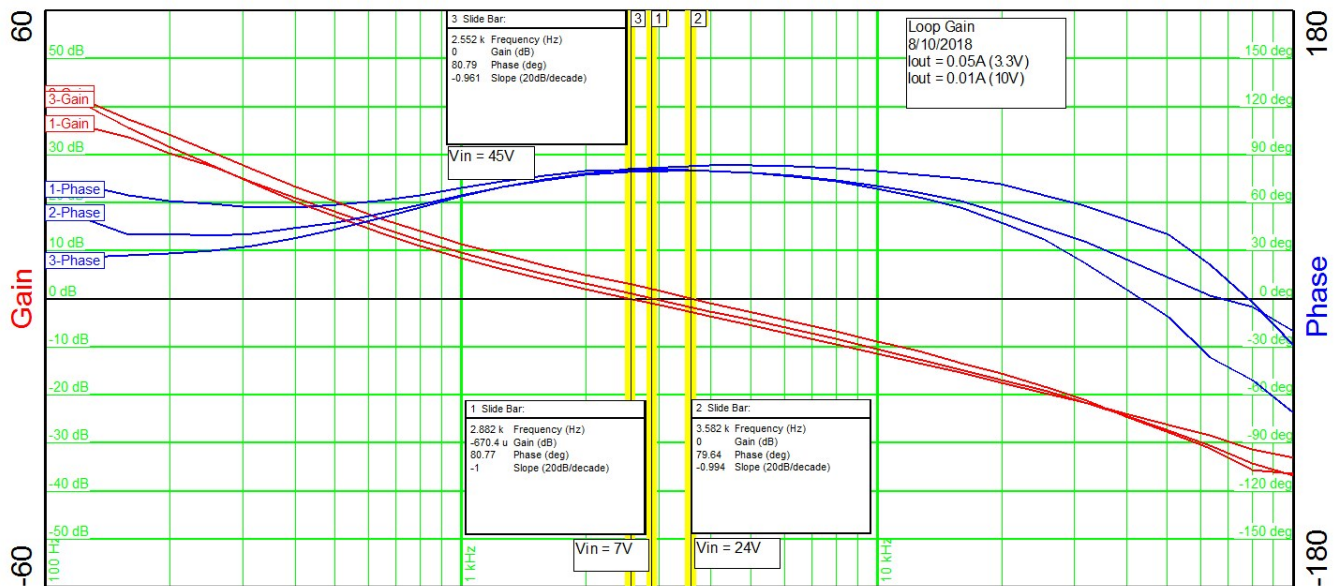

100

Frequency

100 k

3V@0.05A, 10V@0.01A

Vin = 7V

Bandwidth = 2.88 kHz

Phase Margin = 81 degrees

3V@0.05A, 10V@0.01A

Vin = 24V

Bandwidth = 3.58 kHz



Phase Margin = 80 degrees

3V@0.05A, 10V@0.01A


Vin = 45V

Bandwidth = 2.55 kHz

Phase Margin = 81 degrees

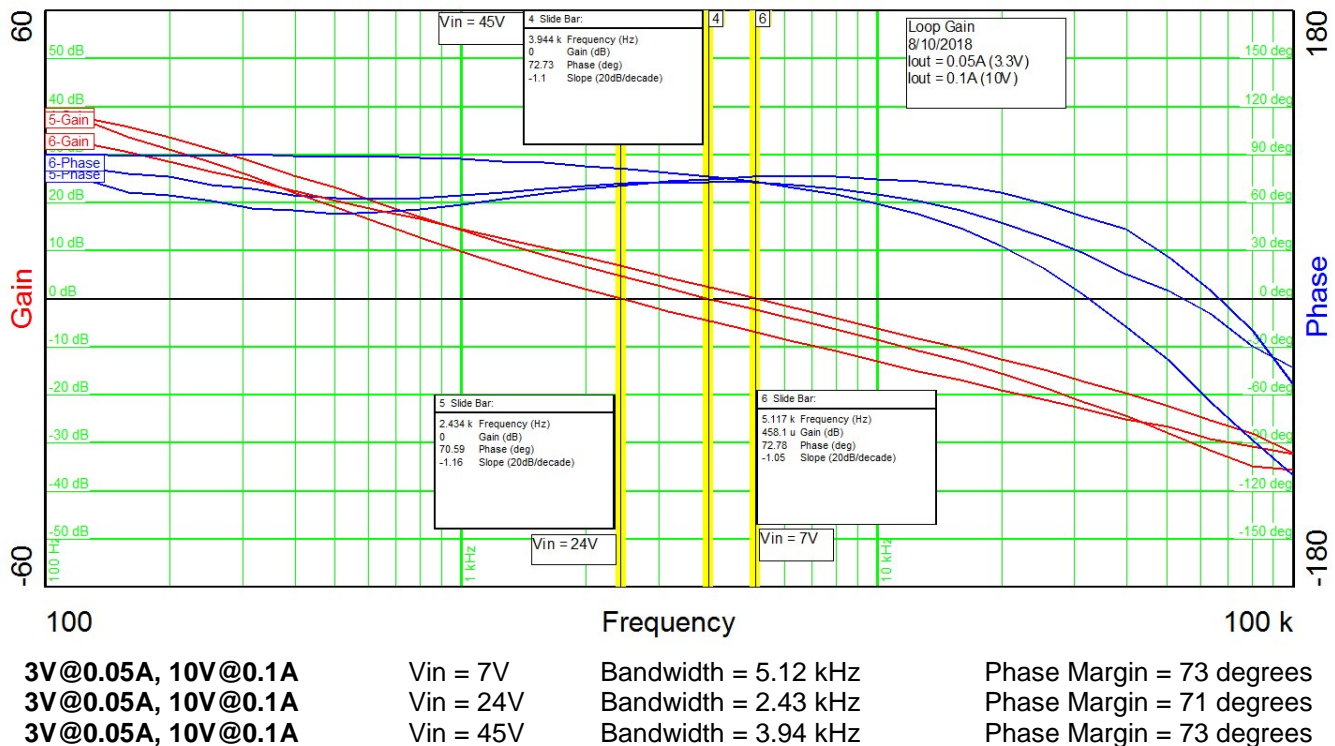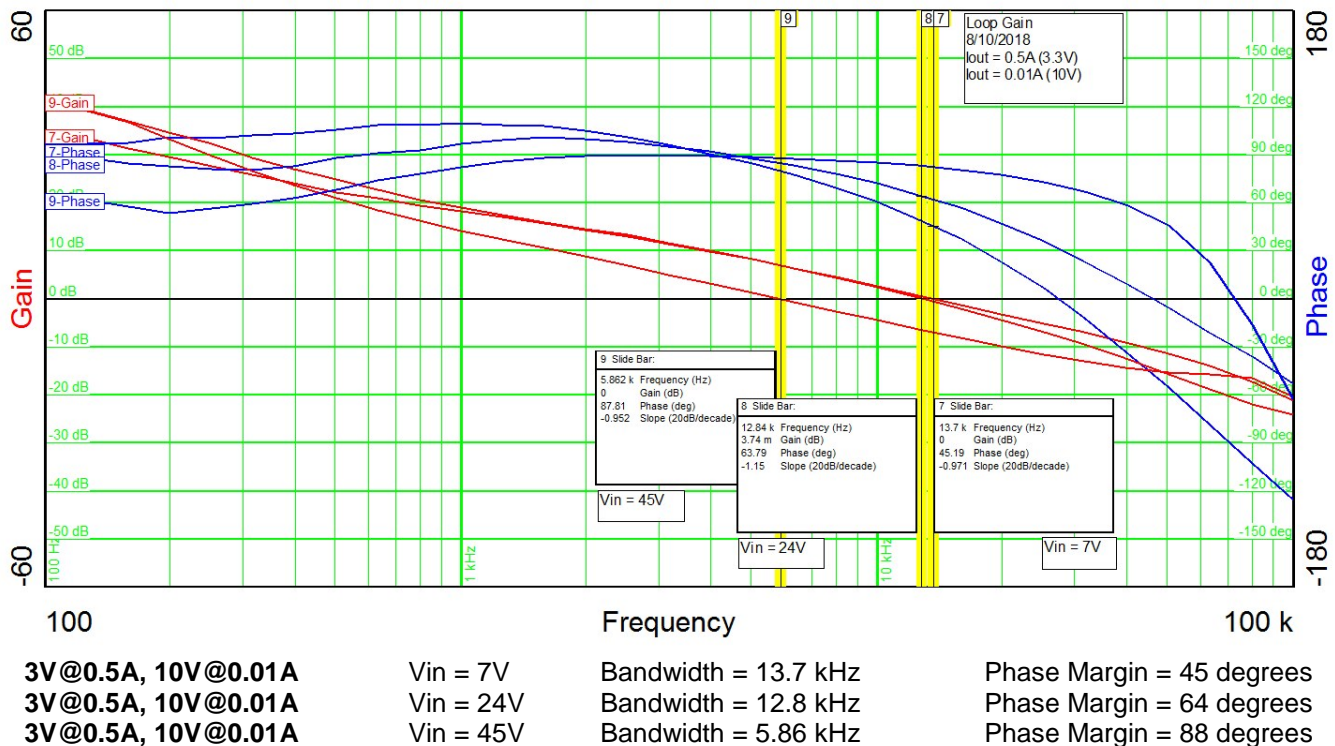


2.4 Thermal Images

 


This thermal image shows the operating temperature of the board with 24V input and max loads at room temperature.

3 Waveforms

3.1 Startup Sequence

 


 Start-up sequence for $V_{in} = 20V$ (blue) and max loads; 3.3V@0.5A (red), 10V@0.1A (yellow)




Start-up sequence for $V_{in} = 20V$ (blue) and no loads; 3.3V@0A (red), 10V@0A (yellow)


3.2 Switch Node

 

 
Switch node of FET Q2 with $V_{in} = 7V$ and $3.3V @ 0.5A$ and $10V @ 0.1A$



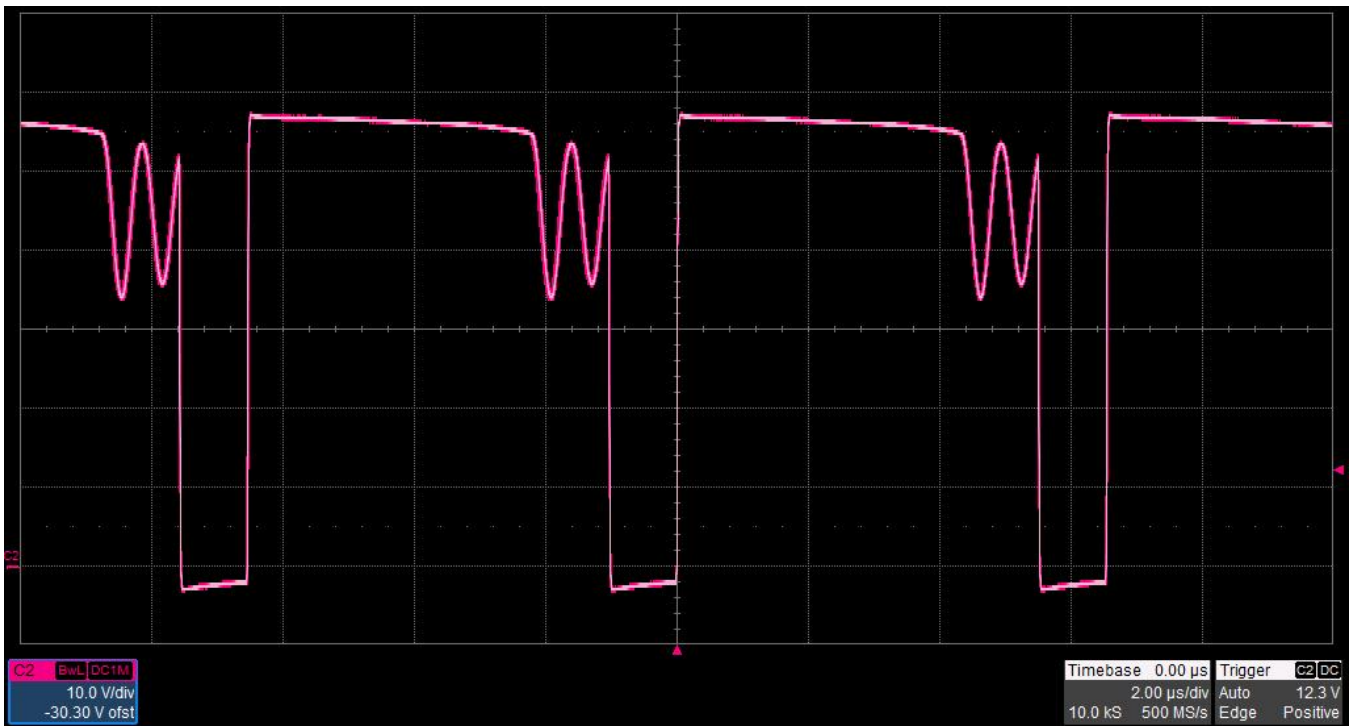Switch node of FET Q2 with $V_{in} = 7V$ and $3.3V @ 0.05A$ and $10V @ 0.01A$




 Switch node of FET Q2 with $V_{in} = 45V$ and $3.3V @ 0.5A$ and $10V @ 0.1A$




Switch node of FET Q2 with $V_{in} = 45V$ and $3.3V @ 0.05A$ and $10V @ 0.01A$


3.3 Output Voltage Ripple

 

 
3.3V ripple voltage with $V_{in} = 7V$ and $3.3V @ 0.5A$ and $10V @ 0.1A$



 3.3V ripple voltage with $V_{in} = 45V$ and $3.3V @ 0.5A$ and $10V @ 0.1A$




 10V ripple voltage with $V_{in} = 7V$ and $3.3V @ 0.5A$ and $10V @ 0.1A$




10V ripple voltage with $V_{in} = 45V$ and $3.3V @ 0.5A$ and $10V @ 0.1A$

3.4 Load Transients

 

 50% to 100% load transient on the 3.3V output with $V_{in} = 20V$. 10V output (blue) and 3.3V (red)



50% to 100% load transient on the 10V output with $V_{in} = 20V$. 10V output (blue) and 3.3V (red)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated