


# Test Report: PMP40555

## 9~60-Vdc Input, 12-V/2-A Output Flyback Reference Design


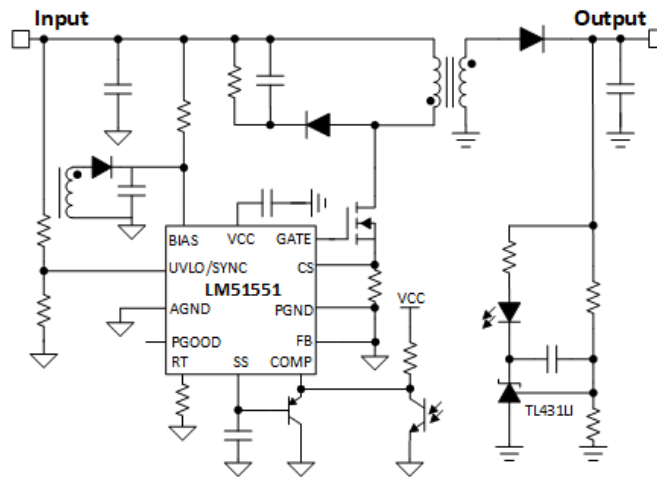
### Description


This reference design is a wide input, 12-V/2-A output isolated flyback converter using LM51551. The switching frequency is 250 kHz and the peak efficiency of the system is 89.19% at 24-V input. The load regulation in the whole input range is within  $\pm 0.5\%$ . Peak-to-peak ripple of the output is within 296 mV under load transient from 1 A to 2 A with a slew rate of 1 A/us.



Top View



Bottom View

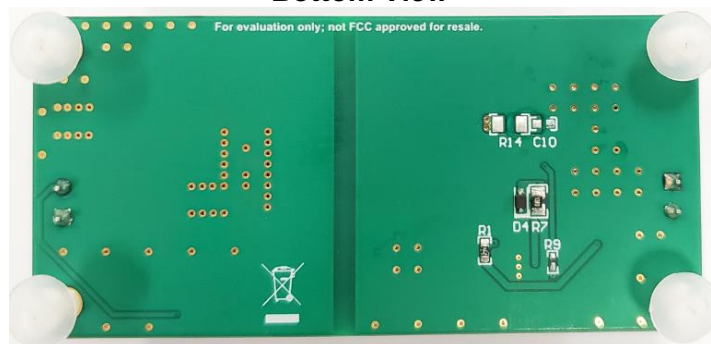

An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

## 1 Test Prerequisites

### 1.1 Voltage and Current Requirements

**Table 1. Voltage and Current Requirements**


PARAMETER	SPECIFICATIONS
Input Voltage	9~60 Vdc
Output Voltage	12 Vdc
Rated Output Current	2 A

### 1.2 Required Equipment

- Multi-meter (current): Fluke 287C
- Multi-meter (voltage): Fluke 287C
- DC Source: Chroma 62006P-100-25
- E-Load: Chroma 63103A module
- Oscilloscope: Tektronix DPO3054
- Current Probe: Tektronix TCPA300
- Electrical Thermography: Fluke TiS65

## 2 Testing and Results

### 2.1 Efficiency Graphs

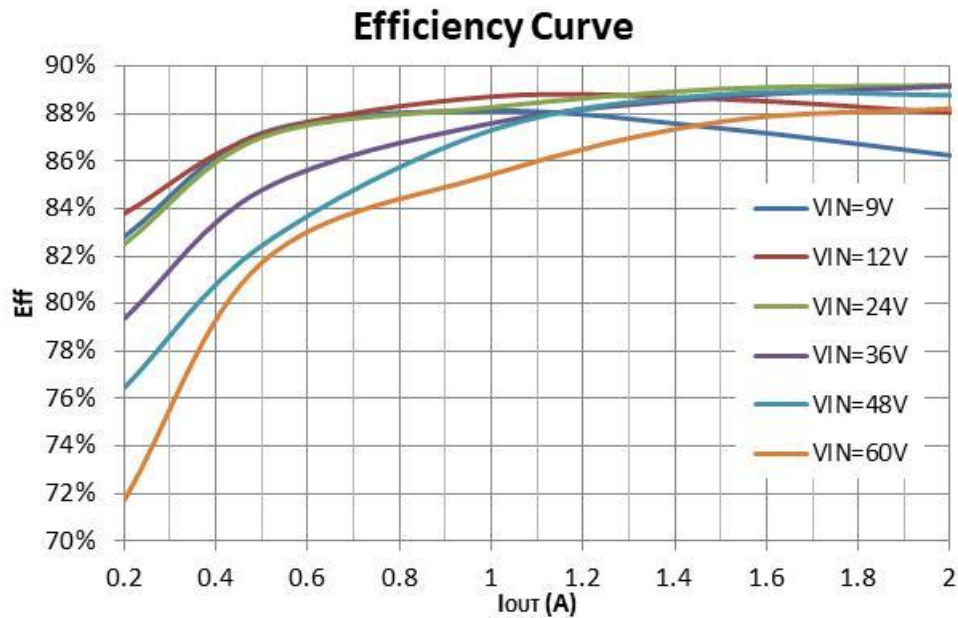


### 2.2 Efficiency Data

V <sub>IN</sub> (V)	I <sub>IN</sub> (A)	V <sub>OUT</sub> (V)	I <sub>OUT</sub> (A)	P <sub>OUT</sub> (W)	P <sub>IN</sub> (W)	Eff
8.997	3.1002	12.024	2.0006	24.0552	27.8925	<b>86.24%</b>
8.999	2.2944	12.028	1.50009	18.0431	20.6473	<b>87.39%</b>
9.000	1.5168	12.031	0.9999	12.0298	13.6512	<b>88.12%</b>
9.001	0.7678	12.034	0.5007	6.0254	6.9110	<b>87.19%</b>
8.999	0.3243	12.037	0.2008	2.4170	2.9184	<b>82.82%</b>
9.001	0.03241	12.041	0	0.0000	0.2917	
11.999	2.2777	12.027	2.0006	24.0612	27.3301	<b>88.04%</b>
12.002	1.6976	12.029	1.5009	18.0543	20.3746	<b>88.61%</b>
12.005	1.1296	12.032	0.9999	12.0308	13.5608	<b>88.72%</b>
12.006	0.5761	12.035	0.5007	6.0259	6.9167	<b>87.12%</b>
12.000	0.2404	12.038	0.2008	2.4172	2.8848	<b>83.79%</b>
12.000	0.02698	12.041	0	0.0000	0.3238	
23.998	1.1243	12.029	2.0006	24.0652	26.9810	<b>89.19%</b>
23.999	0.8450	12.031	1.5009	18.0573	20.2792	<b>89.04%</b>
24.001	0.5679	12.033	0.9999	12.0318	13.6302	<b>88.27%</b>
24.002	0.2886	12.037	0.5007	6.0269	6.9270	<b>87.01%</b>
23.998	0.1221	12.04	0.2008	2.4176	2.9302	<b>82.51%</b>
24.002	0.0132	12.043	0	0.0000	0.3156	


35.999	0.7498	12.029	2.0007	24.0664	26.9921	<b>89.16%</b>
35.997	0.5656	12.031	1.5009	18.0573	20.3599	<b>88.69%</b>
36.004	0.3815	12.033	0.9999	12.0318	13.7355	<b>87.60%</b>
36.001	0.1975	12.038	0.5008	6.0286	7.1102	<b>84.79%</b>
36.006	0.0846	12.04	0.2008	2.4176	3.0461	<b>79.37%</b>
35.998	0.00742	12.044	0	0.0000	0.2671	
47.999	0.5648	12.029	2.0007	24.0664	27.1098	<b>88.77%</b>
48.004	0.4235	12.03	1.5009	18.0558	20.3297	<b>88.82%</b>
47.999	0.2869	12.034	0.999	12.0220	13.7709	<b>87.30%</b>
48.004	0.1523	12.037	0.5008	6.0281	7.3110	<b>82.45%</b>
48.007	0.0659	12.04	0.2009	2.4188	3.1637	<b>76.46%</b>
48.009	0.00514	12.043	0	0.0000	0.2468	
60.00	0.4547	12.029	2.0007	24.06642	27.282	<b>88.21%</b>
60.00	0.3433	12.031	1.5009	18.05733	20.598	<b>87.67%</b>
60.01	0.2347	12.034	0.9999	12.0328	14.08435	<b>85.43%</b>
60.01	0.1229	12.037	0.5008	6.02813	7.375229	<b>81.73%</b>
60.01	0.0562	12.04	0.2009	2.418836	3.372562	<b>71.72%</b>
60.01	0.00404	12.042	0	0	0.24244	

### 2.3 Load Regulation

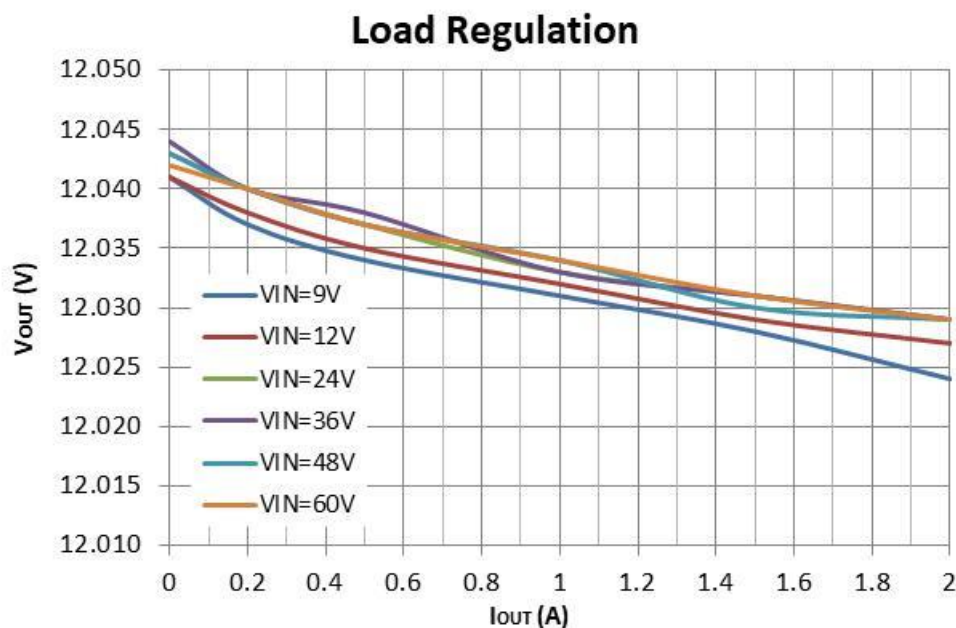


## 2.4 Thermal Images


Ta=25.0°C, 9 V input, 12V2A output

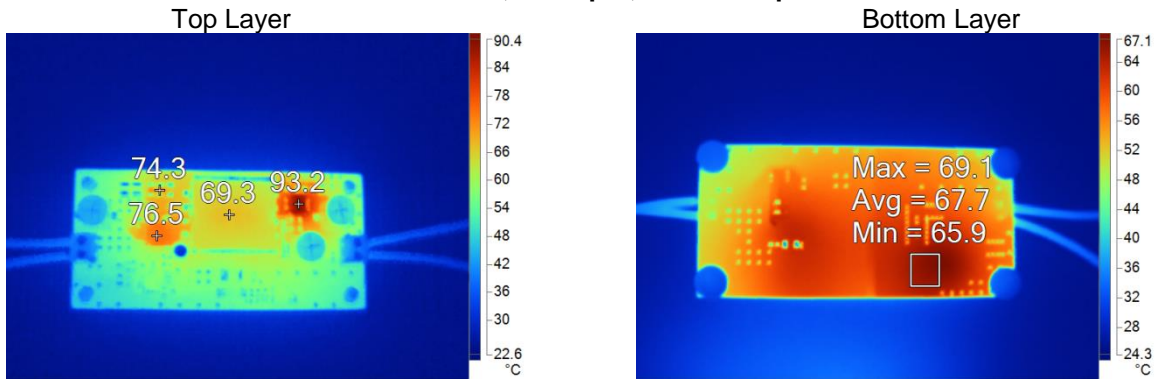


Ta=25.0°C, 12 V input, 12V2A output

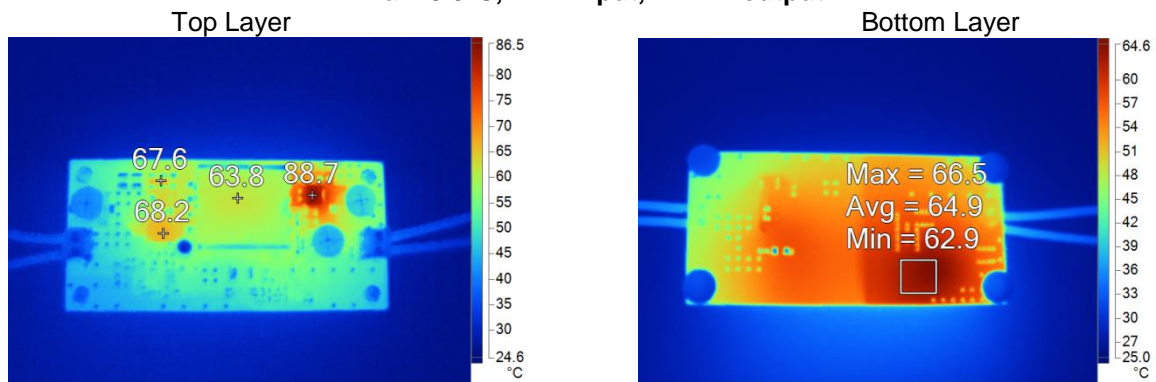

Ta=25.0°C, 36 V input, 12V2A output

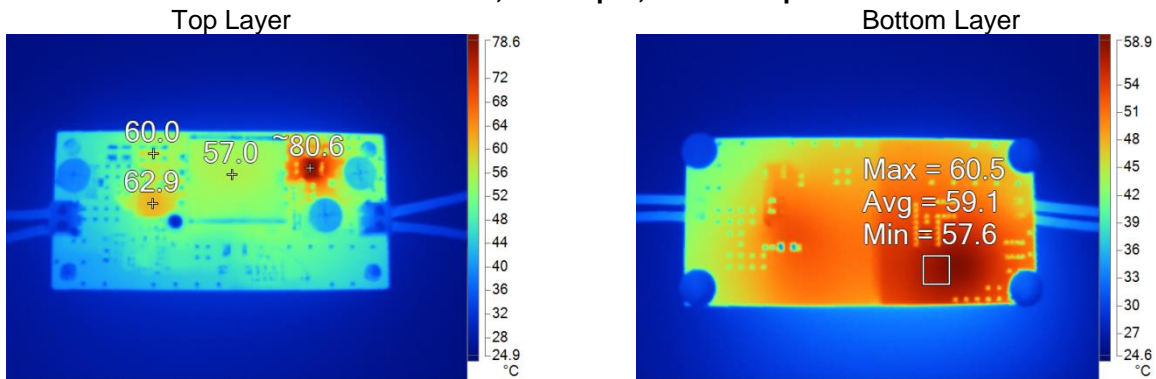


Ta=25.0°C, 60 V input, 12V2A output

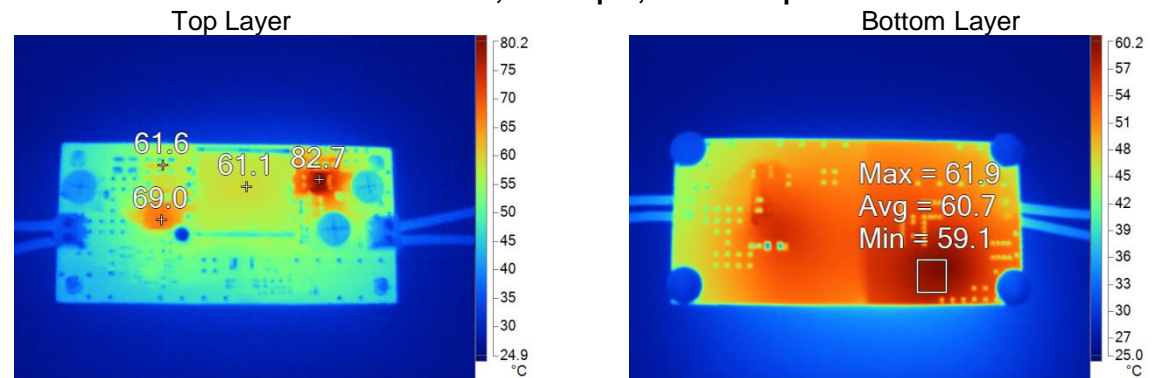


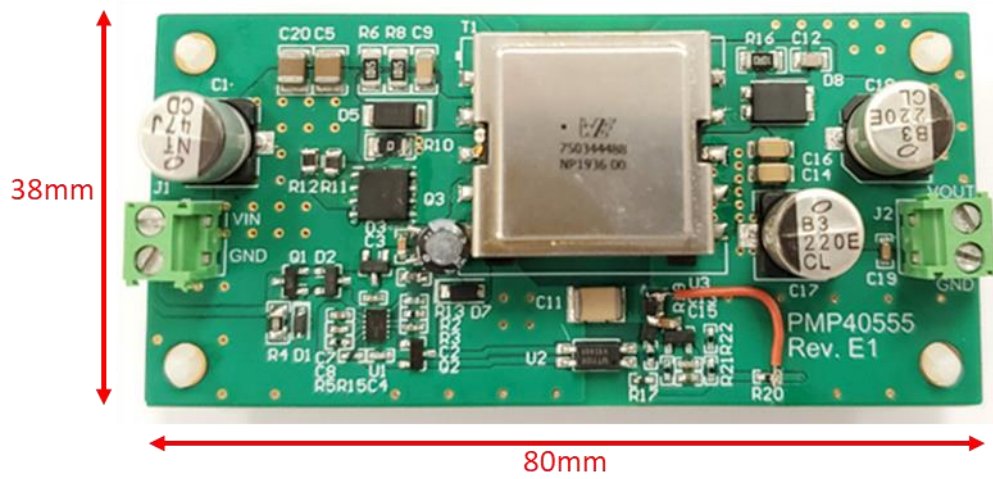
## 2.5 Dimensions







The dimension of this board is 80mm (length)\*38mm (width)\*11mm (height).




### 3 Waveforms
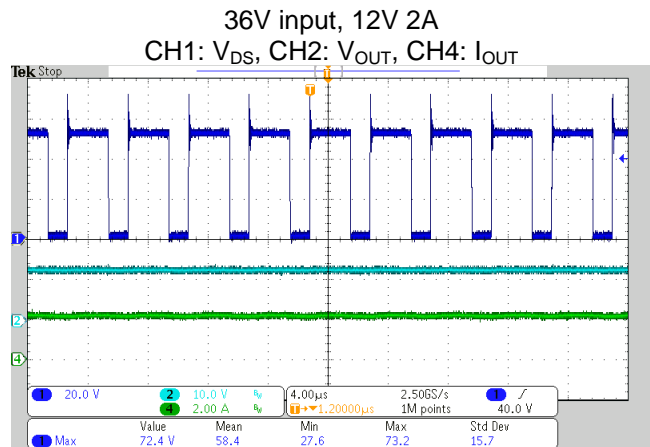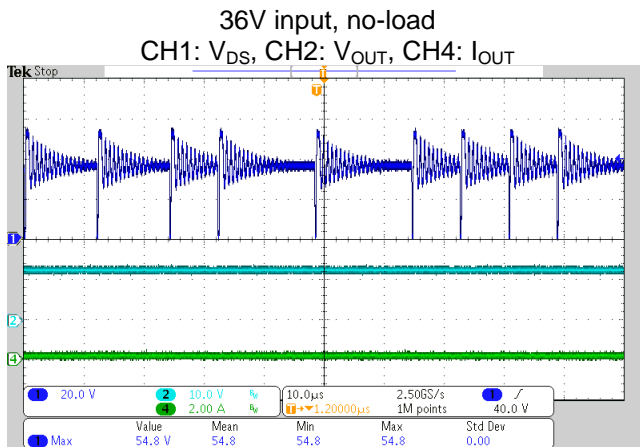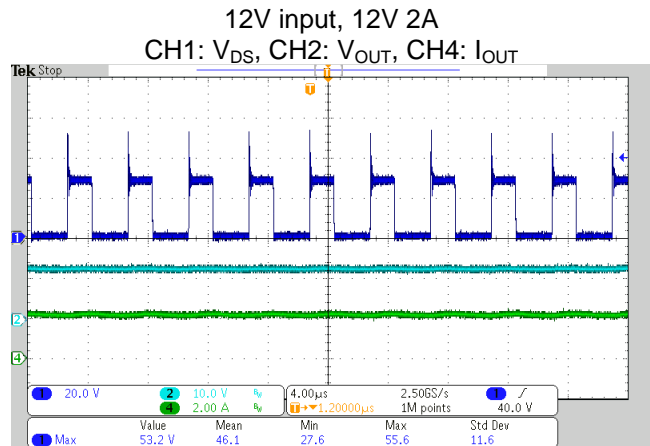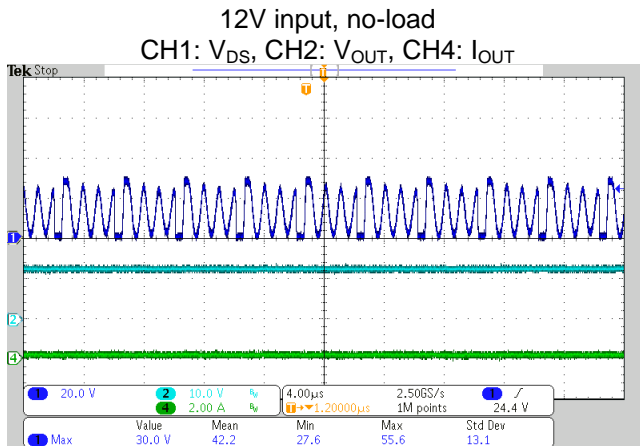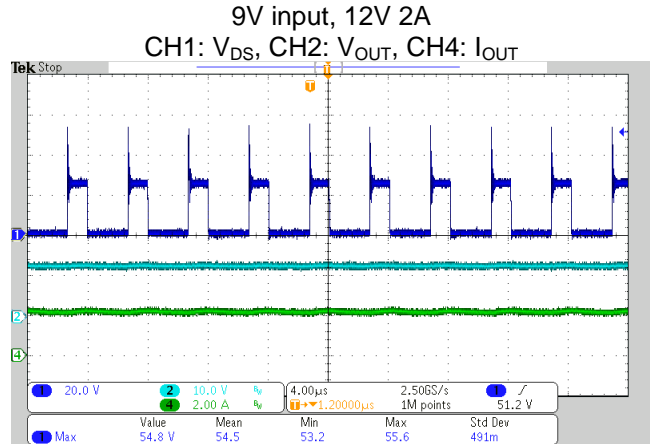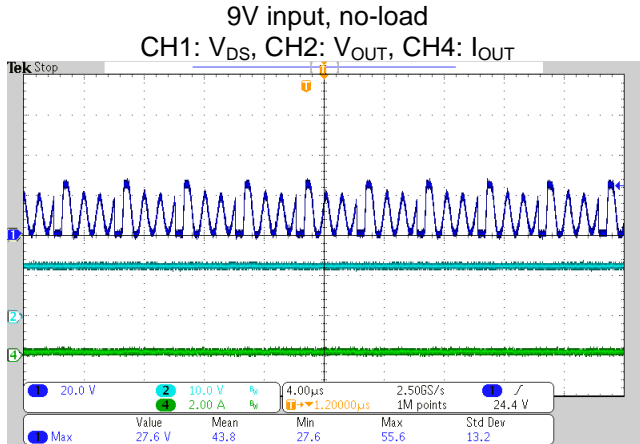
#### 3.1 Switching


The waveforms of switching nodes at no load and full load condition are shown in following pictures.



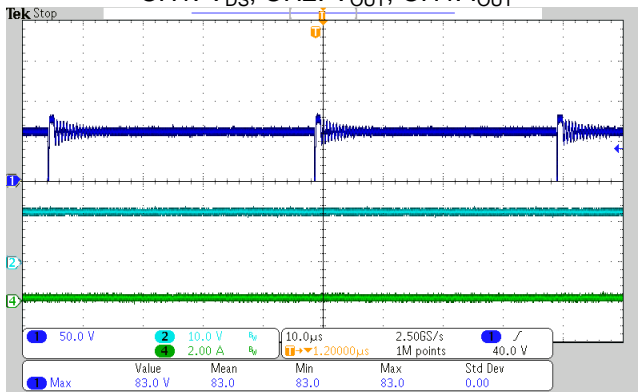60V input, no-load  
CH1: V<sub>DS</sub>, CH2: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



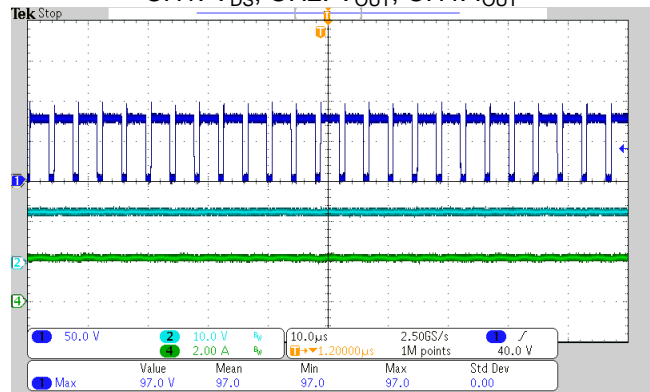
60V input, 12V 2A  
CH1: V<sub>DS</sub>, CH2: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



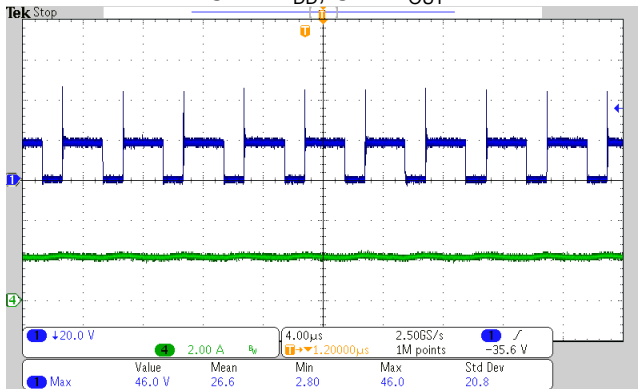
### 3.2 Rectified Diode Waveform

The waveforms of secondary rectified diode at full load condition are shown in following pictures.


9V input, 12V2A  
CH1: V<sub>DD</sub>, CH4: I<sub>OUT</sub>



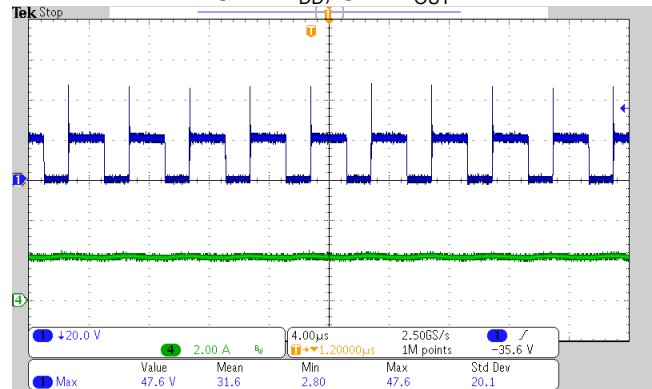
12V input, 12V2A  
CH1: V<sub>DD</sub>, CH4: I<sub>OUT</sub>



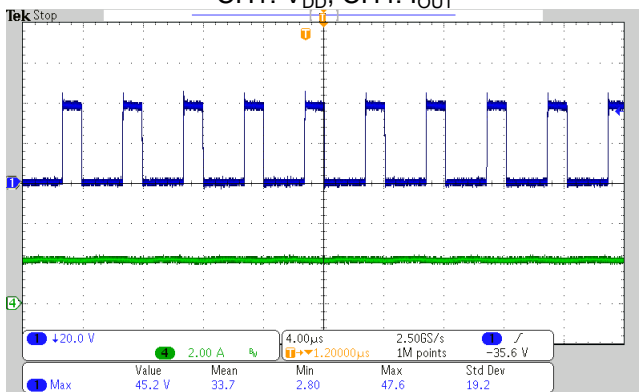36V input, 12V2A  
CH1: V<sub>DD</sub>, CH4: I<sub>OUT</sub>



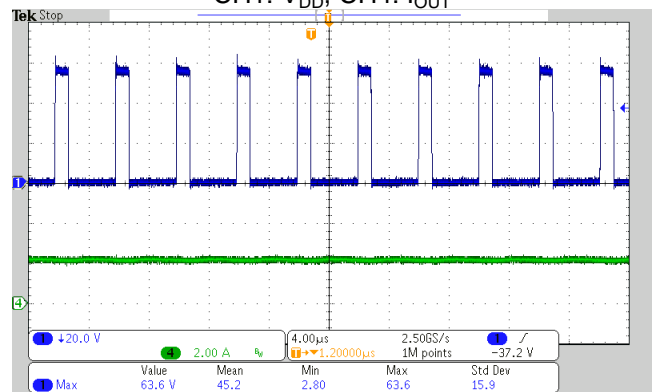60V input, 12V2A  
CH1: V<sub>DD</sub>, CH4: I<sub>OUT</sub>



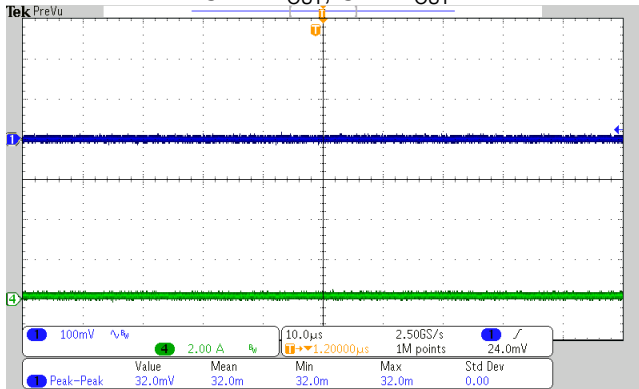
### 3.3 Output Voltage Ripple


The waveforms of output AC ripples at no load and full load condition are shown in following pictures.




9V input, no-load  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



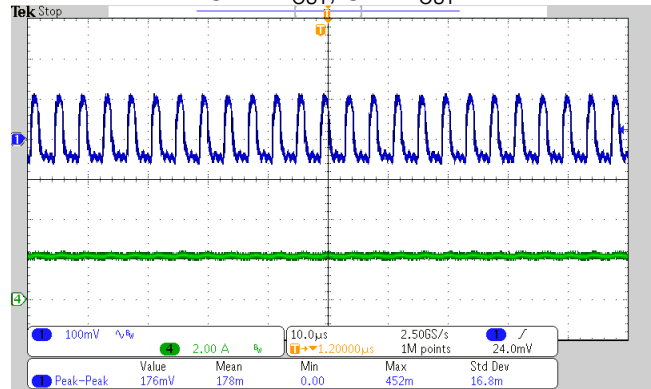
9 V input, 12V 2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



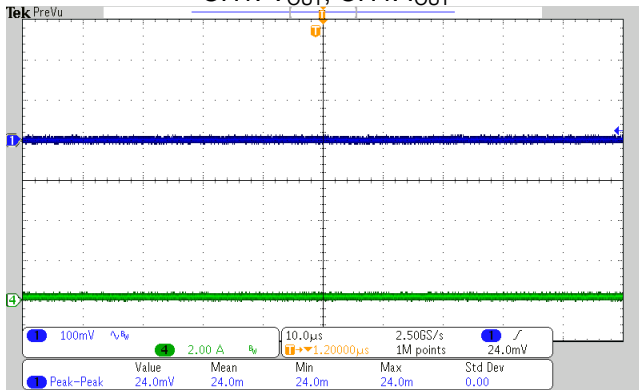
12V input, no-load  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



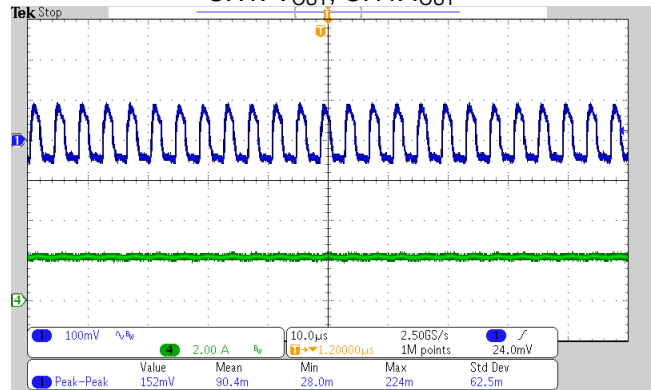
12V input, 12V 2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



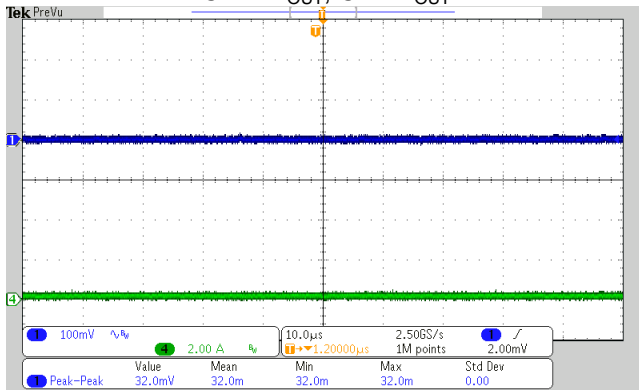
36V input, no-load  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



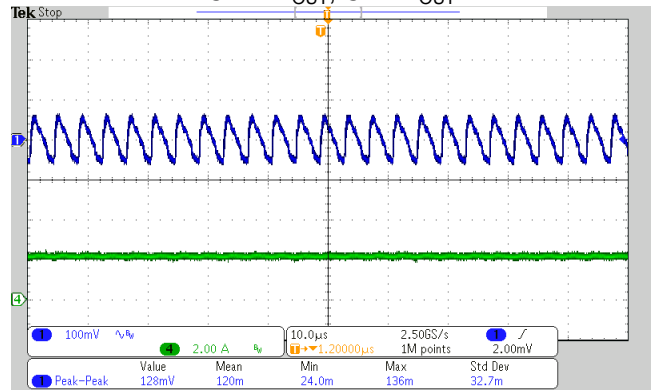
36V input, 12V 2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



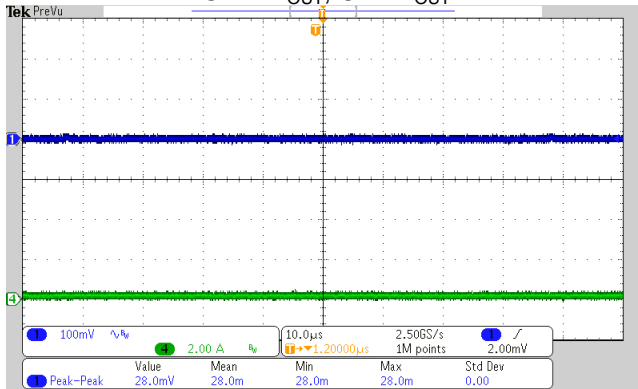60V input, no-load  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



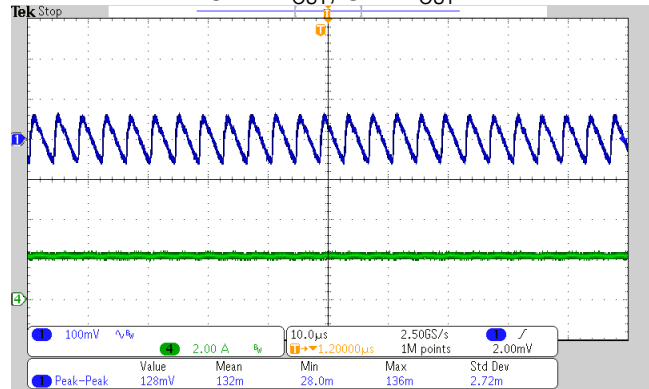
60V input, 12V 2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



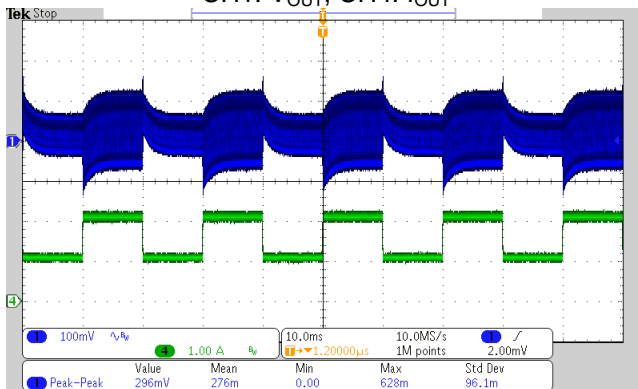
### 3.4 Load Transient

The waveforms of output AC ripples at load transient are shown in following pictures. The high current level is 2A for 10ms; the low current level is 1A for 10ms, with a slew rate of 1A/us.


9V input, 1A->2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



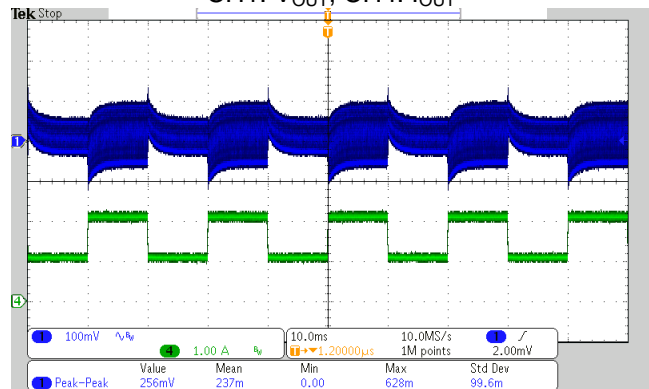
12V input, 1A->2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



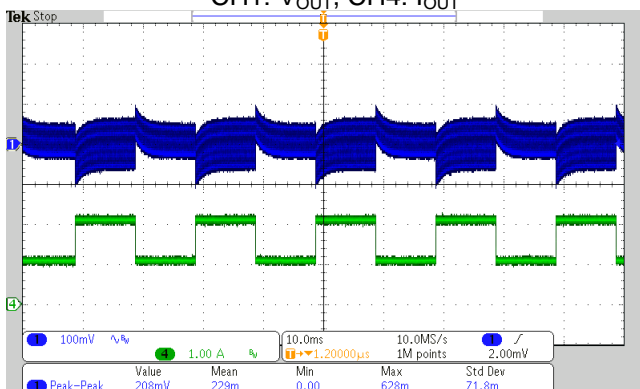36V input, 1A->2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>







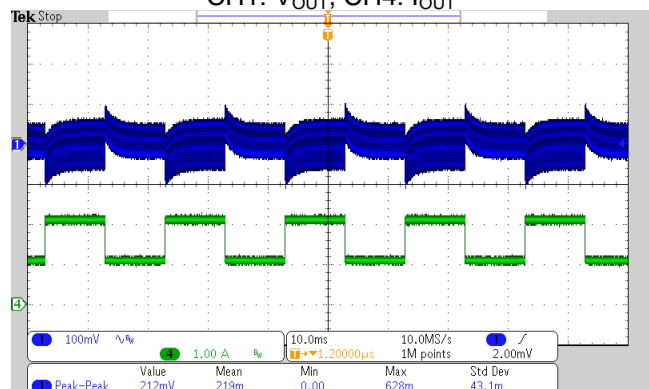60V input, 1A->2A  
CH1: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



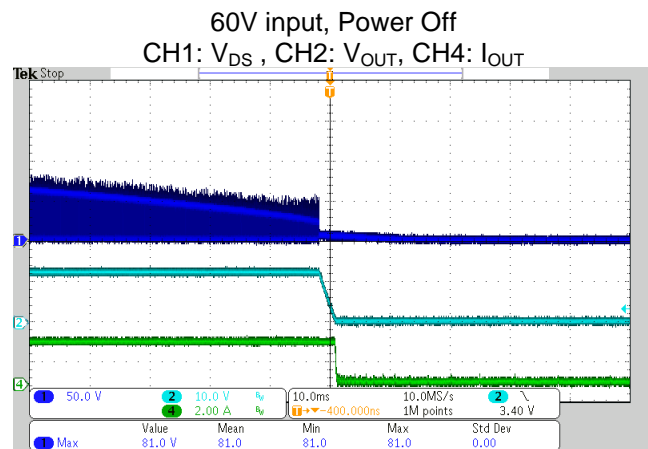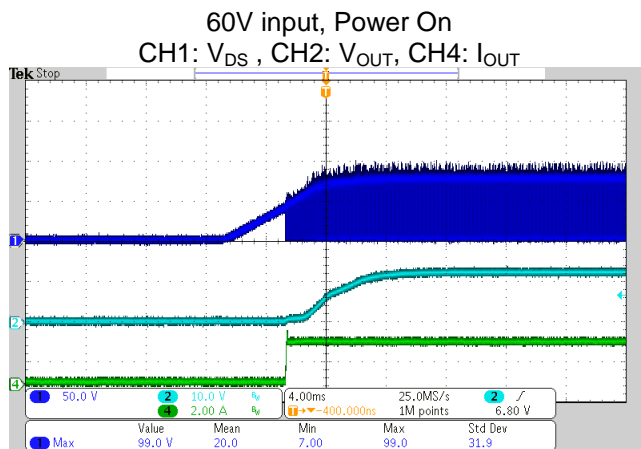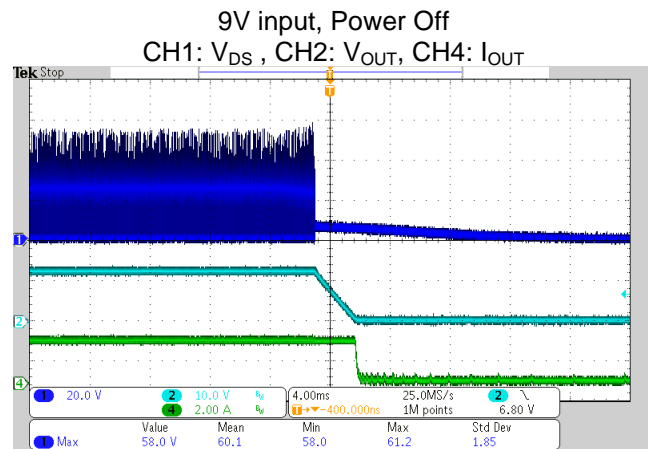
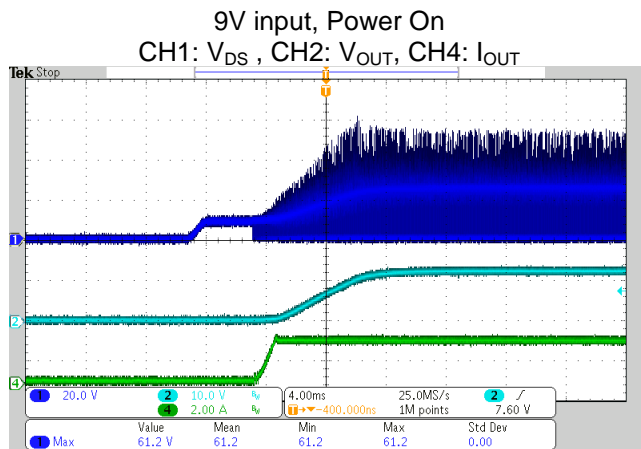
### 3.5 Power on/off

The waveforms of Power on and off with full load output are shown in following pictures.



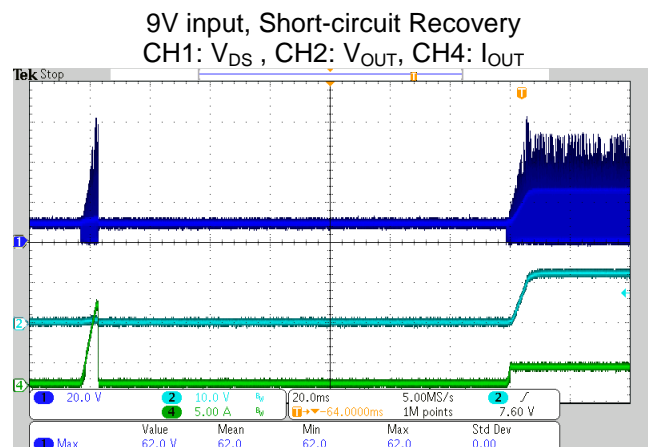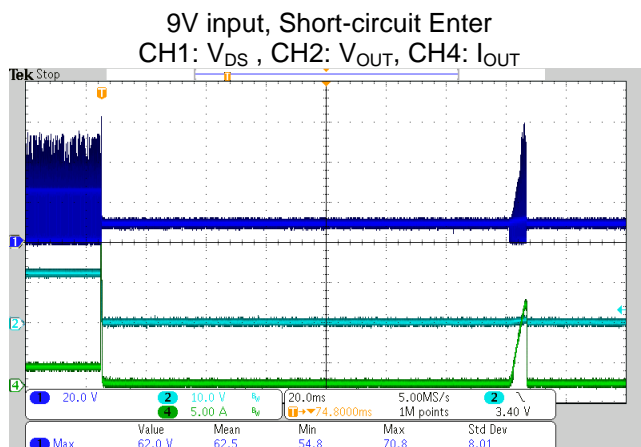
### 3.6 Output Short-circuit Protection


The waveforms of output short-circuit enter and recovery are shown in following pictures.



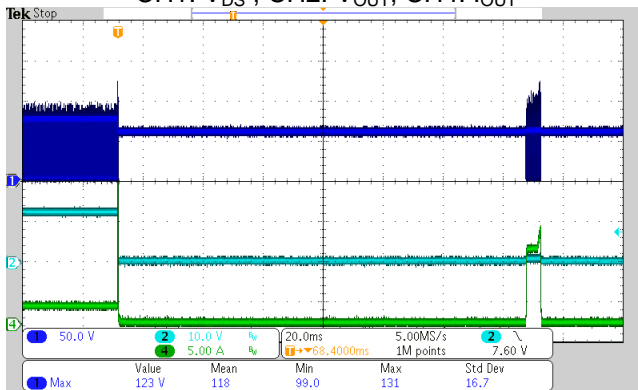60V input, Short-circuit Enter  
CH1: V<sub>DS</sub>, CH2: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



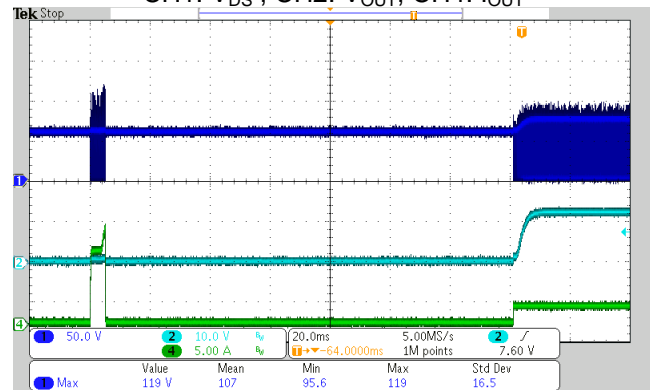
60V input, Short-circuit Recovery  
CH1: V<sub>DS</sub>, CH2: V<sub>OUT</sub>, CH4: I<sub>OUT</sub>



### 3.7 Loop Response

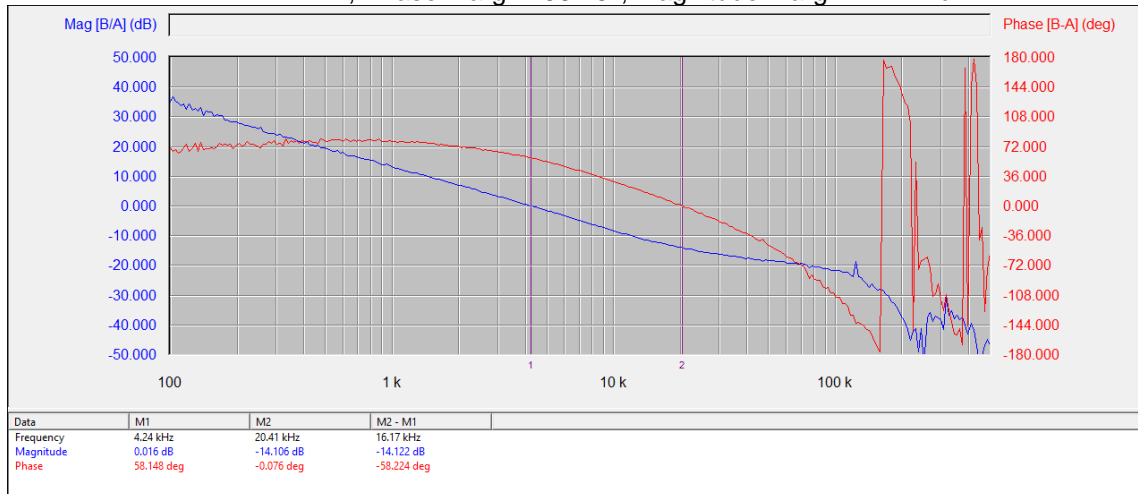
#### 9V input

BW=4.24 kHz, Phase Margin=58.15°, Magnitude Margin=14.11 dB



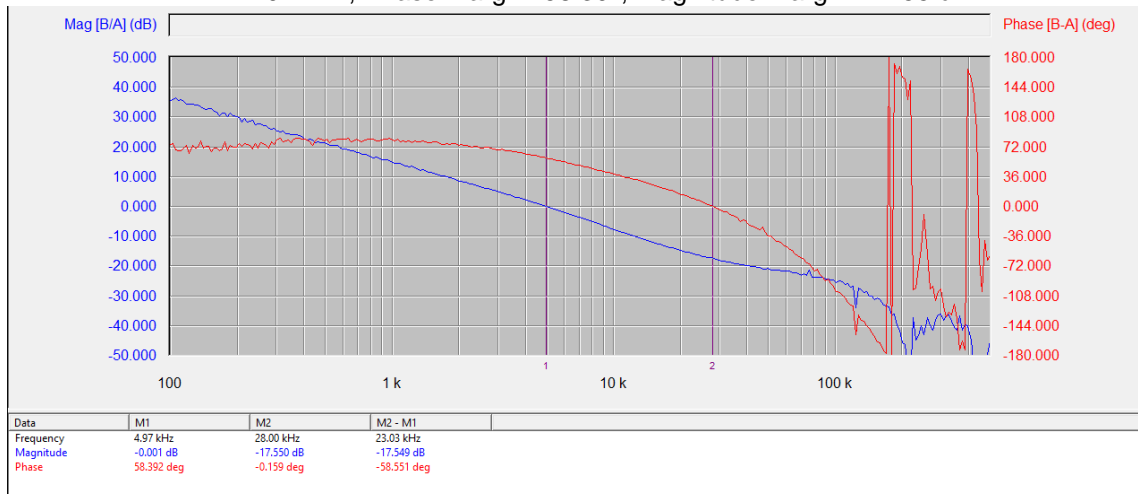
#### 12V input

BW=4.97 kHz, Phase Margin=58.39°, Magnitude Margin=17.55 dB



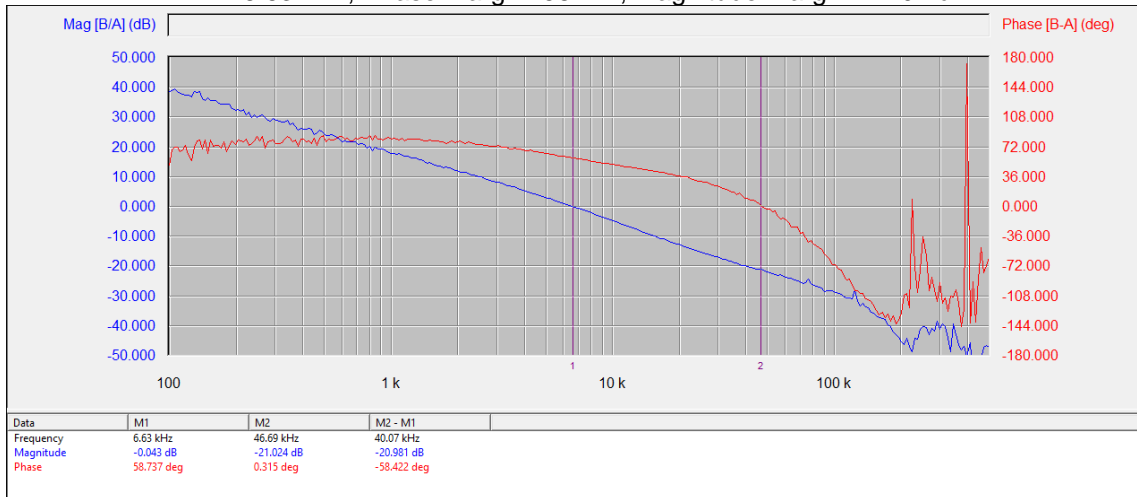
### 24V input

BW=6.63 kHz, Phase Margin=58.74°, Magnitude Margin=21.02 dB



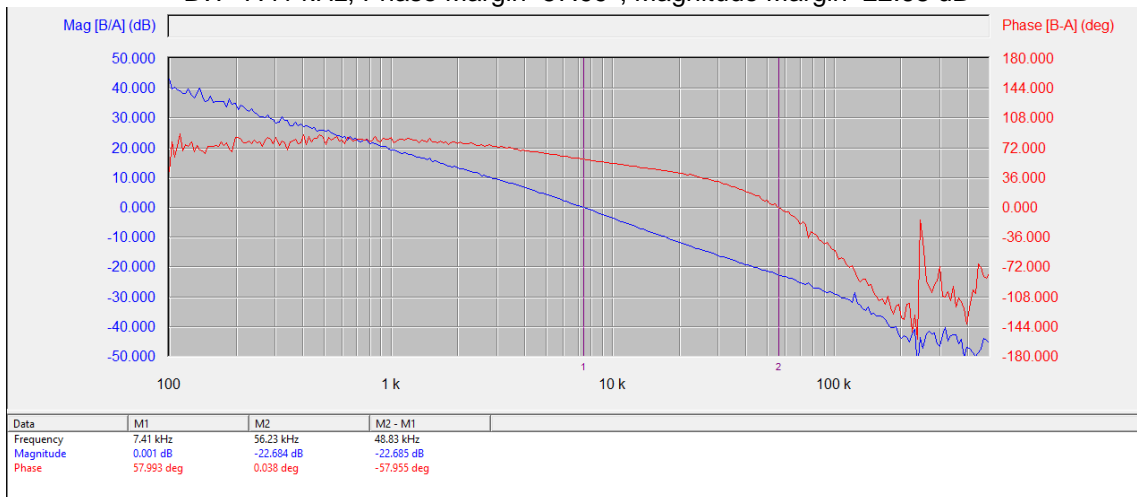
### 36V input

BW=7.41 kHz, Phase Margin=57.99°, Magnitude Margin=22.68 dB



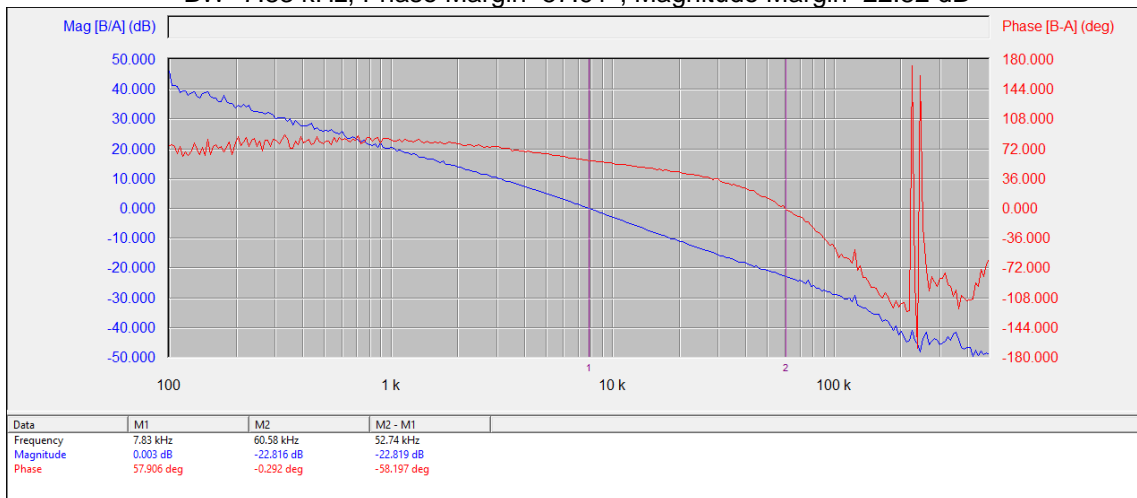
### 48V input

BW=7.83 kHz, Phase Margin=57.91°, Magnitude Margin=22.82 dB



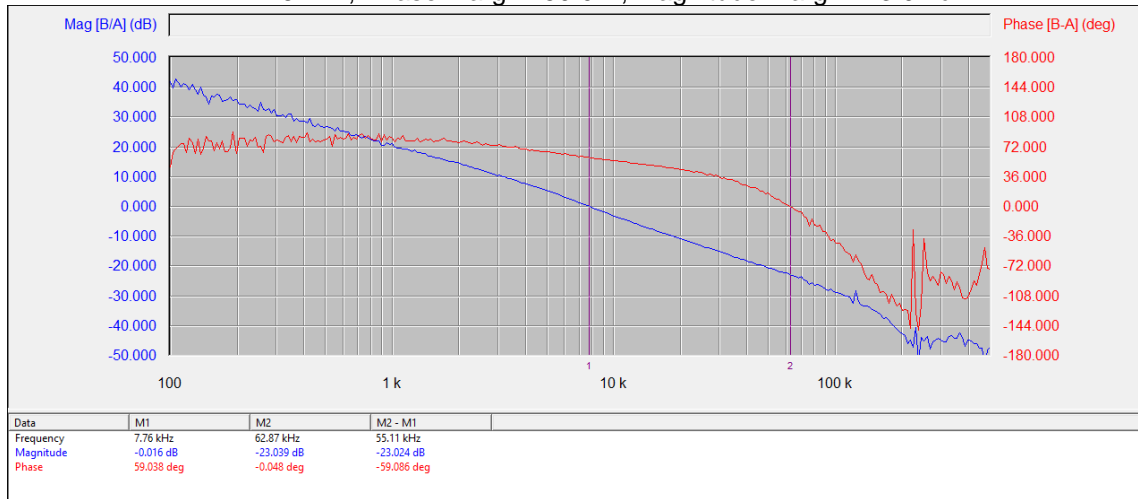**60V input**

BW=7.76 kHz, Phase Margin=59.04°, Magnitude Margin=23.04 dB





## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2021, Texas Instruments Incorporated