

# TI Precision Designs: Reference Design

## Single Supply Op Amp with True Drive to GND



### TI Precision Designs

TI Precision Designs are analog solutions created by TI's analog experts. Reference Designs offer the theory, component selection, and simulation of useful circuits. Circuit modifications that help to meet alternate design goals are also discussed.

### Circuit Description

Single supply rail-to-rail amplifiers are commonly used in analog systems. In some cases it is important to have an amplifier output that drives very close to GND (i.e. a few microvolts). However, no amplifier can inherently drive this close to GND. This TI Precision Design shows a simple design modification that allows most standard single supply rail-to-rail amplifiers to drive very close to GND.


### Design Resources

[Design Archive](#)  
[TINA-TI™](#)  
[OPA140](#)  
[OPA376](#)

All Design files  
 SPICE Simulator  
 Product Folder  
 Product Folder



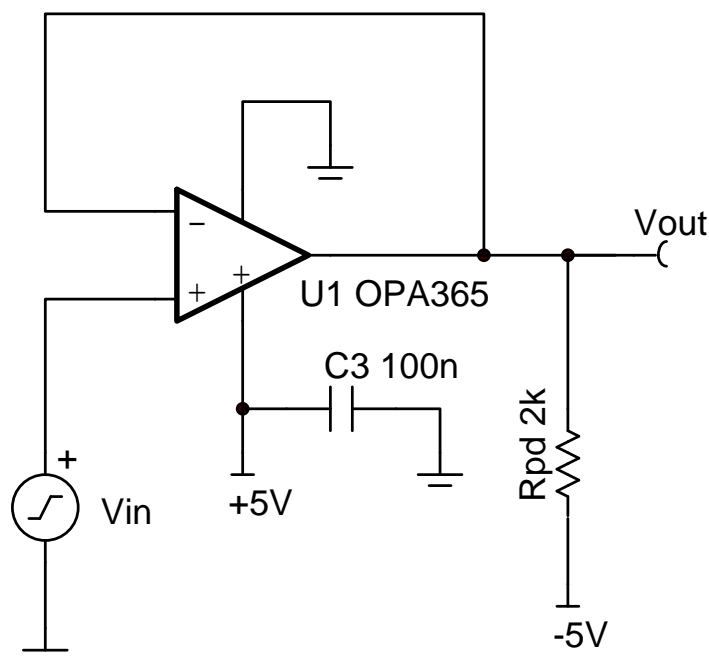[Ask The Analog Experts](#)  
[WEBENCH® Design Center](#)  
[TI Precision Designs Library](#)



**An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.**

TINA-TI is a trademark of Texas Instruments  
 WEBENCH is a registered trademark of Texas Instruments

## 1 Design Summary

The design requirements are as follows:


- Supply Voltage: +5V
- Input: 0V to 5V
- Output: 0V to 5V with accuracy at 0V

The design goals and performance are summarized in Table 1. Figure 1 depicts the difference in outputs between a traditional output connection and a pull-down to a negative supply. Note that the circuit with pull-down to negative supply can drive very close to GND ( $3.2\mu\text{V}$ ).


**Table 1. Comparison of Design Goals, Calculations, and Simulated Performance**

	Goal	Calculated	Simulated
Zero Scale Error	$\pm 500\mu\text{V}$	$\pm 100\mu\text{V}$ (Typ) $\pm 200\mu\text{V}$ (Max)	$-3.1\mu\text{V}$
Zero Scale Error (without Pull-Down)	-na-	10mV (Typ) 20mV (Max)	4.9mV

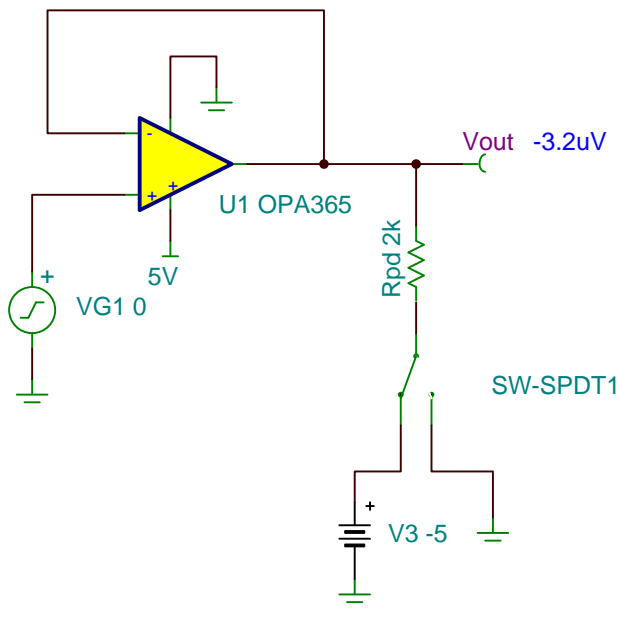**Pull-Down to -5V Allows Swing to close to GND**



**Traditional Connection Cannot Swing to GND**

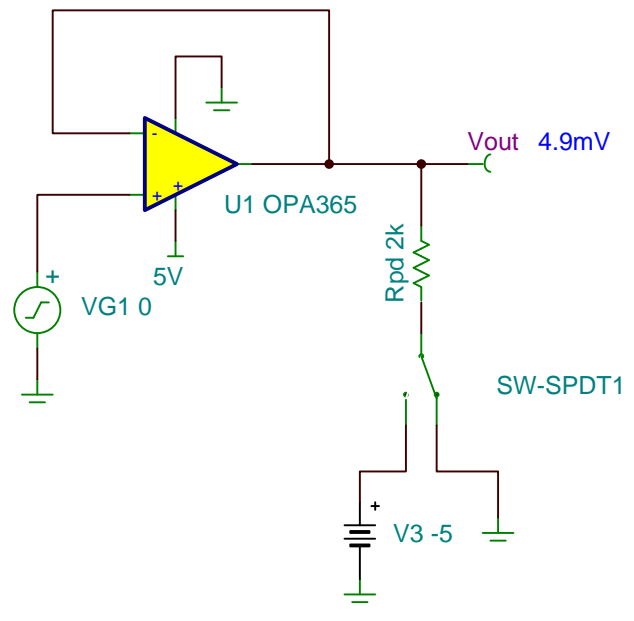

**Figure 1: Output results with pull-down to -5V and traditional output connection to GND**

## 2 Theory of Operation:

### 2.1 Normal Operation of Output Stage

Figure 2 shows the normal operation of a rail-to-rail CMOS amplifier. The quiescent current for the amplifier in this example is  $760\mu\text{A}$ . One half of the quiescent current powers the input stage (see blue arrows). The other half of the quiescent current powers the output stage (see red arrows). The output is driven to the input voltage ( $2.5\text{V}$ ) as expected for normal operation.

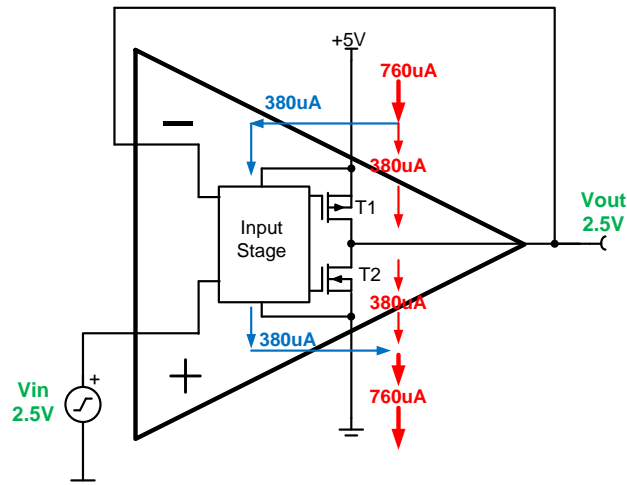


Figure 2: Normal Operation of Output Stage

Figure 3 shows the operation of a rail-to-rail CMOS amplifier with a zero volt input signal applied. In this example the ideal output is  $0\text{V}$  (true GND). However, the output cannot drive to ground because the transistor T2 has a finite resistance ( $53\Omega$  in this example). Remember that half of the quiescent current is biasing the output stage, so the voltage across T2 is about  $20\text{mV}$  ( $V_{T2} = (380\mu\text{A} \times 53\Omega) = 20\text{mV}$ ). All op amp output stages will have this limitation. The minimum output voltage will vary according to the sizing of the output stage transistors, but any practical output stage will have output swing limitations in the range of millivolts to hundreds of millivolts.


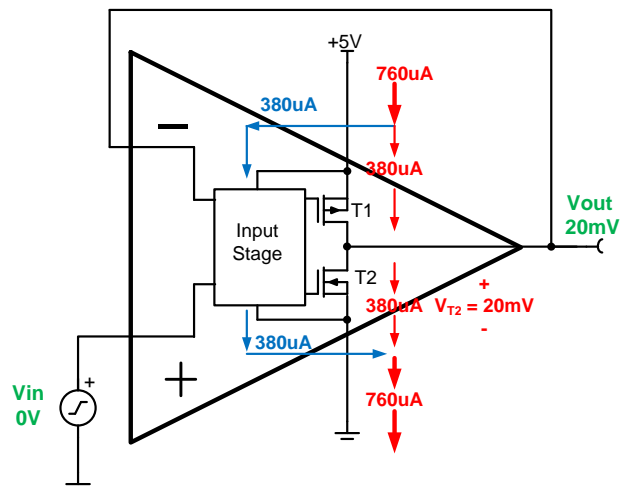


Figure 3: Output Stage Cannot Drive to Ground

Figure 4 shows the characteristics for the output stage transistor (T2) in this example. The figure is meant to emphasize the fact that the drain to source voltage across a transistor cannot be zero when current is flowing. In this example, the drain current is 380μA and the corresponding drain to source current is 20mV. The slope of the drain current curve determines its resistance (53Ω).

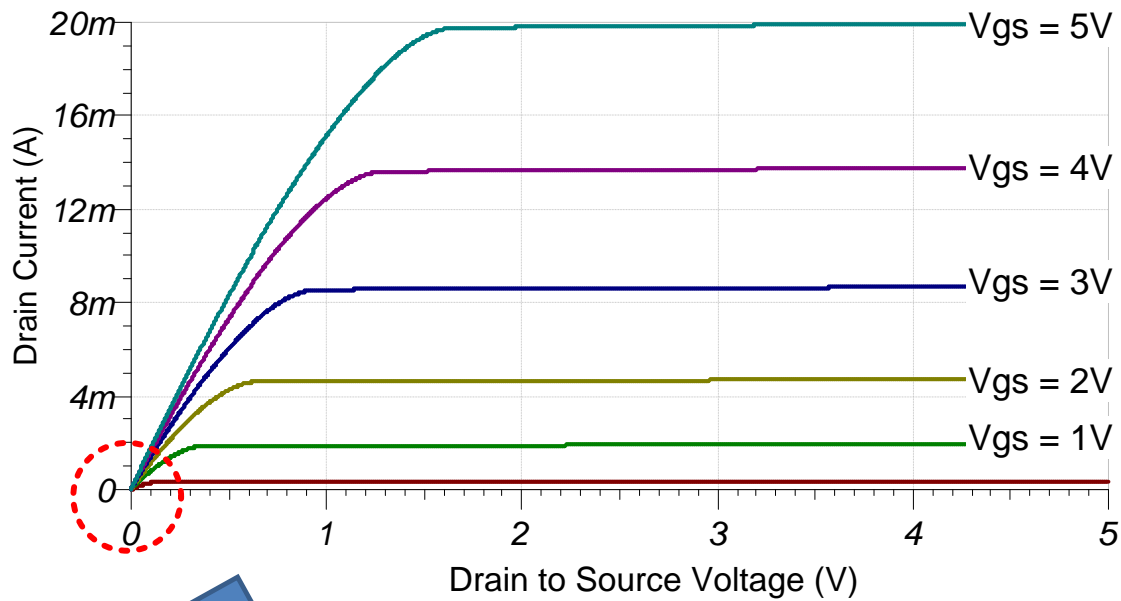

**Zoom in Below**

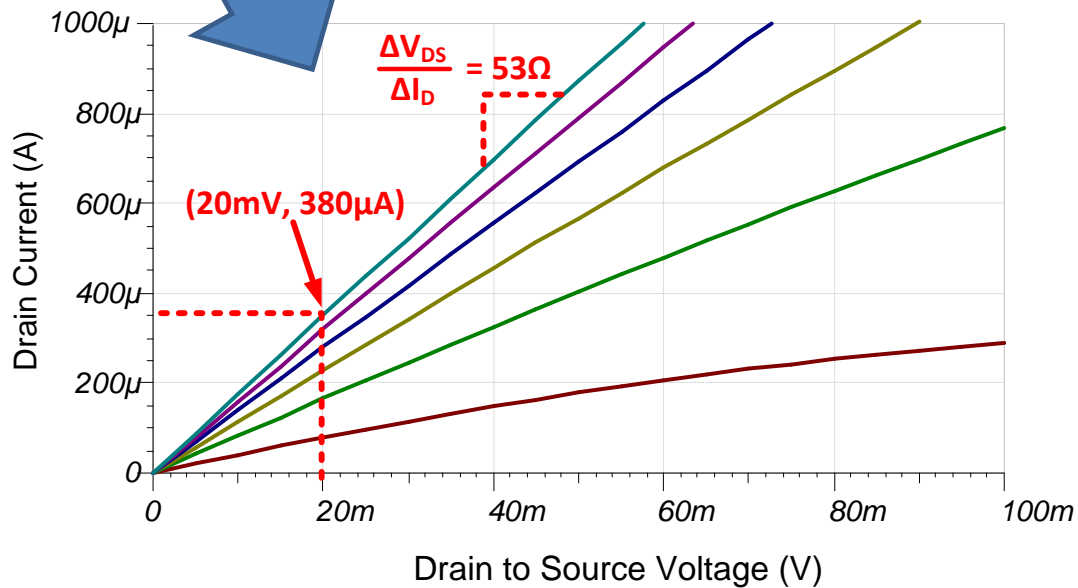


Figure 4: Output Stage Transistor Drain to Source Voltage

## 2.2 Output Stage Operation with Pull-Down Resistor

Figure 5 illustrates a simple solution that allows the output to drive down to 0V (ground). This design uses a pull-down resistor to the negative supply (RL). The pull-down resistor provides a path for the output stage current to a negative supply. When the output drives to ground, T2 will turn off allowing the output to drive to 0V. In any practical op amp configuration there will be some small error in the output voltage due to input offset voltage and other errors.

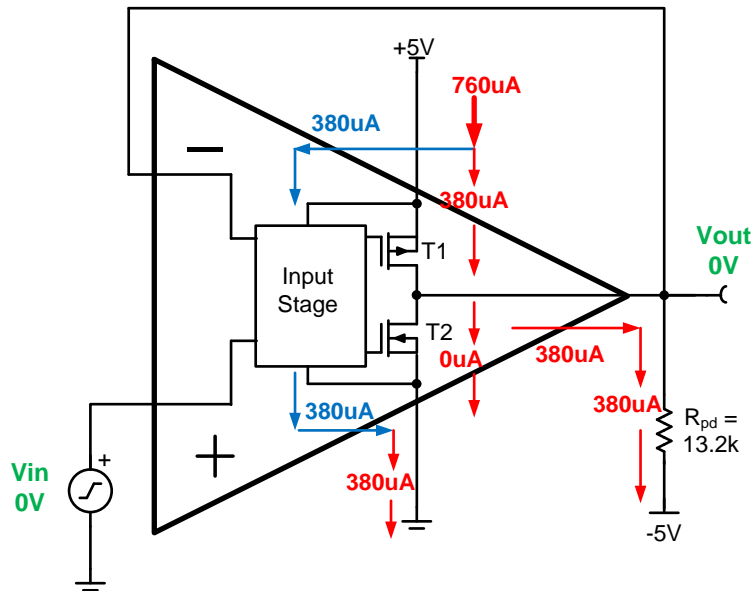


Figure 5: Pull-Down Allows Output to Reach “True GND”

### 3 Component Selection

#### 3.1 Selecting the Pull-Down Resistor

As a rule of thumb, the output stage consumes one half of the quiescent current of the op amp. To successfully swing to ground, the pull down resistor must sink all of the output stage current so that no current flows through the p-channel FET (T2). Table 1 is an excerpt from the OPA365 data sheet showing quiescent current, and Equation (1) shows the calculation for selecting the pull-down resistor. Table 3 provides a list of pull-down resistors that can be used for other single supply amplifiers. The pull-down resistors in Table 3 assume a -5V supply. Other negative supplies could be used (e.g. -15V); however, the value of the pull-down resistor would need to be recalculated.

**Table 2: Quiescent Current Specification from OPA365 Data Sheet**

PARAMETERS	CONDITIONS	OPA365			UNIT
		MIN	TYP	MAX	
Quiescent Current Per Amplifier $I_Q$	$I_O = 0A$		4.6	5.0	mA

$$R_{pd} = \frac{-V_{pd}}{0.5I_Q} = \frac{-(-5.0V)}{0.5(4.6mA)} = 2.17k\Omega \quad (1)$$

Where

$R_{pd}$  = The pull-down resistor connected from output to negative supply.

$V_{pd}$  = Pull-down supply voltage. Must be negative (current sink).

$I_Q$  = Device supply current with no load (quiescent current).

**Table 3: Pull-Down Resistor for Single Supply Amplifiers**

Part #	Resistor Value for -5V Supply
OPA364	2 k $\Omega$
OPA335	40 k $\Omega$
OPA340	7.5 k $\Omega$
OPA343	7.5 k $\Omega$
OPA348	250 k $\Omega$
OPA350	2 k $\Omega$
OPA353	2 k $\Omega$
OPA333	20 k $\Omega$

## 4 Simulation

The TINA-TI™ schematic shown in Figure 6 includes the circuit values obtained in the design process. It is important to understand that the simulation of the pull-down method will not work for all device models. Many models use behavioral blocks to match the device characters. Other models use a transistor design to model the device performance. This method can only be simulated on transistor based models. In general behavioral models are preferred because they generally converge faster with better accuracy. However, in this case a transistor based model is needed to demonstrate the interaction of the output stage and the pull-down resistor. The OPA365 is an example of a transistor based model.

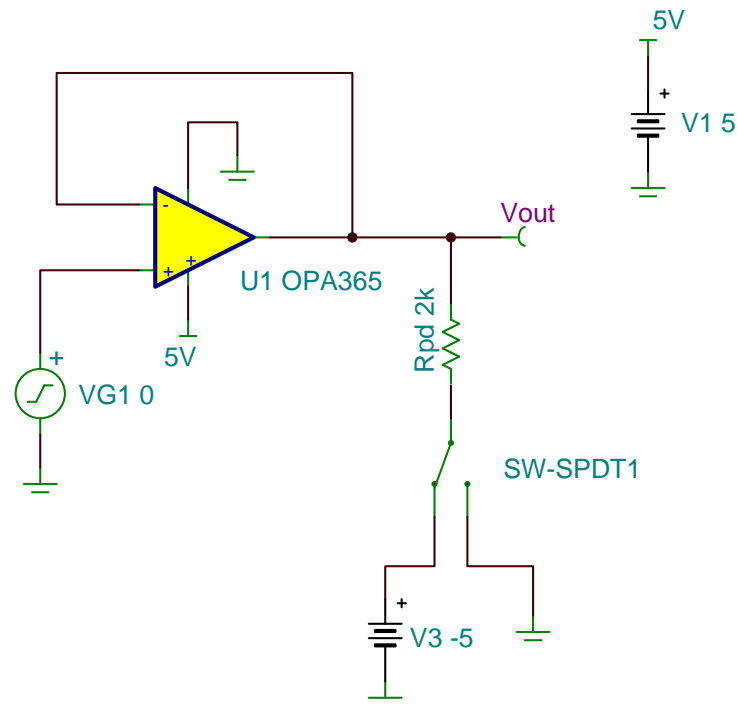


Figure 6: TINA-TI™ Schematic

### 4.1 Transfer Function

The result of the dc transfer function is shown in Figure 7. Of special interest is the region of the transfer function where the input is near zero volts.

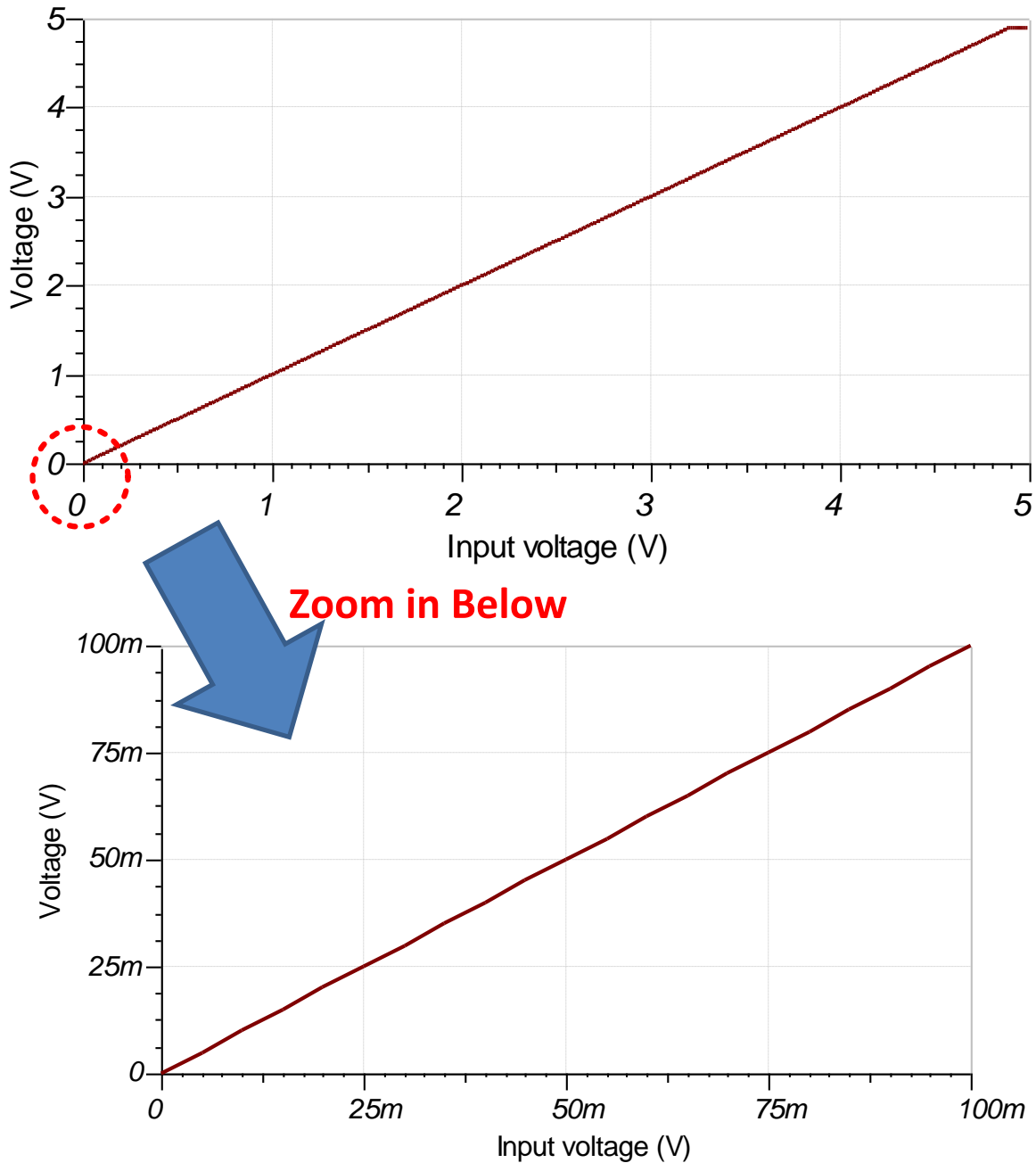


Figure 7: Simulated Transfer Function



### 4.2 Output with $V_{in} = 0V$

The goal of this circuit is to allow the output to drive to 0V (true GND). This simulation checks the drive to 0V for the circuit with the pull-down and the traditional circuit. The circuit with the pull-down drives very close to GND ( $V_{out} = -3.2\mu V$ ). The traditional circuit swing to ground is significantly limited ( $V_{out} = 4.9mV$ ). Figure 4 shows simulation of the output with a 0V input for both cases.

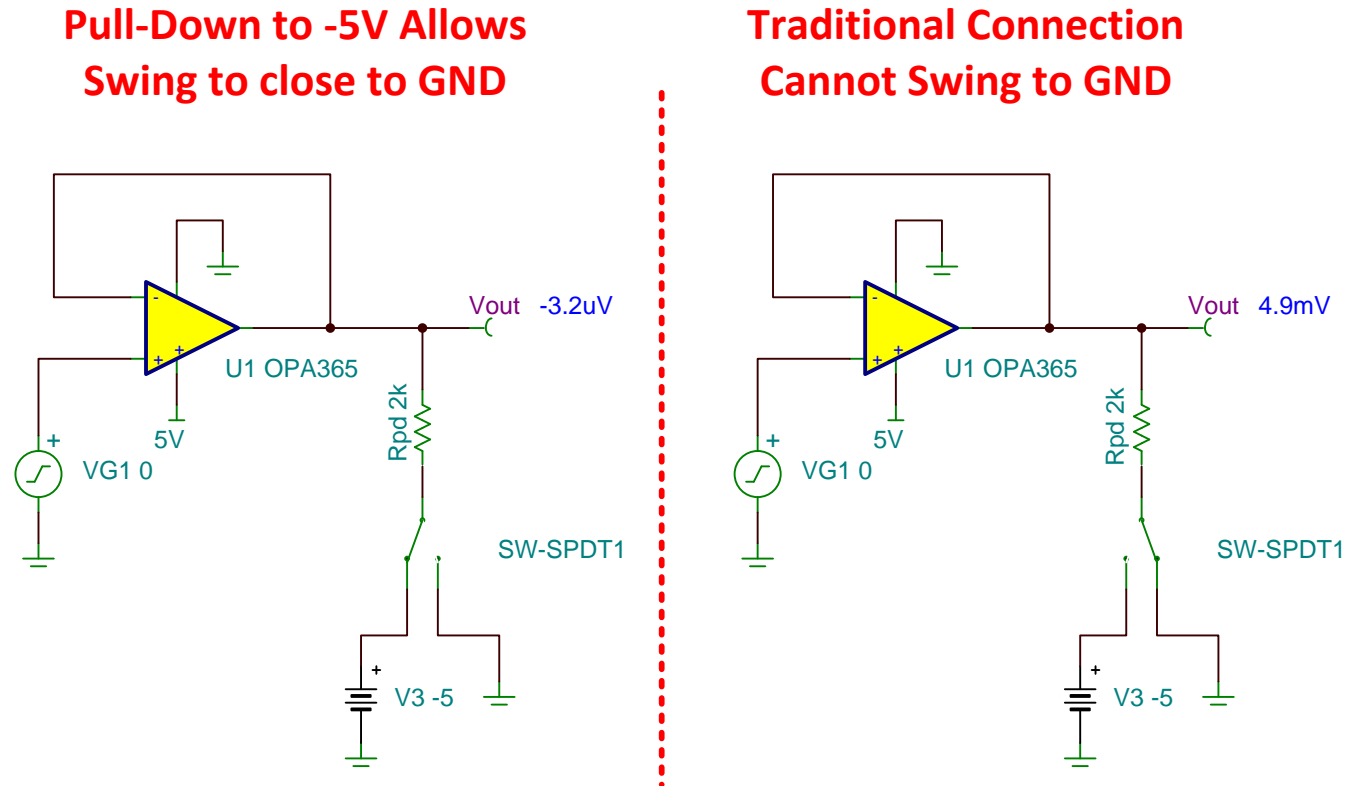


Table 4 summarizes the calculated and simulated performance of the design.

**Table 4. Comparison of Design Goals, Calculations, and Simulations**

	Goal	Calculated	Simulated
<b>Zero Scale Error</b>	$\pm 500\mu V$	$\pm 100\mu V$ (Typ) $\pm 200\mu V$ (Max)	$-3.1\mu V$
<b>Zero Scale Error (without Pull-Down)</b>	-na-	10mV (Typ) 20mV (Max)	4.9mV

## 5 Modifications

The method described Section 3.1 can be used with other single supply amplifiers. Table 5 provides examples of different amplifiers that can be used to achieve different design objectives.

**Table 5. Brief Comparison of 5V Single Supply Amplifiers**

Output Amplifier	Design Objective	V <sub>os</sub> uV	V <sub>os</sub> Drift uV/degC	I <sub>q</sub> uA	Voltage Noise nV/ $\sqrt{\text{Hz}}$	BW MHz	SR V/uS	Approx. Price US\$ / 1ku
OPA365	Wide Band, Low Noise, DC Precision, No Crossover Distortion	100	1	4600	4.5	50	25	0.65
OPA313	Low Noise, Low I <sub>q</sub>	500	2	50	25	1	0.5	0.3
OPA333	DC Precision, Low I <sub>q</sub>	2	0.02	17	50	350	0.16	0.95
OPA350	Wide Band, Low Noise, DC Precision	150	4	5200	7	38	22	1.15

## **6 About the Author**

Arthur Kay is an applications engineering manager at TI where he specializes in the support of amplifiers, references, and mixed signal devices. Arthur focuses a good deal on industrial applications such as bridge sensor signal conditioning. Arthur has published a book and an article series on amplifier noise. Arthur received his MSEE from Georgia Institute of Technology, and BSEE from Cleveland State University.

## **7 Acknowledgements & References**

### **7.1 Acknowledgements**

The author wishes to acknowledge Collin Wells, John Caldwell, Tim Green, and Marek Lis for technical contributions to this design.

## IMPORTANT NOTICE FOR TI REFERENCE DESIGNS

Texas Instruments Incorporated ("TI") reference designs are solely intended to assist designers ("Buyers") who are developing systems that incorporate TI semiconductor products (also referred to herein as "components"). Buyer understands and agrees that Buyer remains responsible for using its independent analysis, evaluation and judgment in designing Buyer's systems and products.

TI reference designs have been created using standard laboratory conditions and engineering practices. **TI has not conducted any testing other than that specifically described in the published documentation for a particular reference design.** TI may make corrections, enhancements, improvements and other changes to its reference designs.

Buyers are authorized to use TI reference designs with the TI component(s) identified in each particular reference design and to modify the reference design in the development of their end products. HOWEVER, NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY THIRD PARTY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT, IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI REFERENCE DESIGNS ARE PROVIDED "AS IS". TI MAKES NO WARRANTIES OR REPRESENTATIONS WITH REGARD TO THE REFERENCE DESIGNS OR USE OF THE REFERENCE DESIGNS, EXPRESS, IMPLIED OR STATUTORY, INCLUDING ACCURACY OR COMPLETENESS. TI DISCLAIMS ANY WARRANTY OF TITLE AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, QUIET ENJOYMENT, QUIET POSSESSION, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS WITH REGARD TO TI REFERENCE DESIGNS OR USE THEREOF. TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY BUYERS AGAINST ANY THIRD PARTY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON A COMBINATION OF COMPONENTS PROVIDED IN A TI REFERENCE DESIGN. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, SPECIAL, INCIDENTAL, CONSEQUENTIAL OR INDIRECT DAMAGES, HOWEVER CAUSED, ON ANY THEORY OF LIABILITY AND WHETHER OR NOT TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES, ARISING IN ANY WAY OUT OF TI REFERENCE DESIGNS OR BUYER'S USE OF TI REFERENCE DESIGNS.

TI reserves the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques for TI components are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

Reproduction of significant portions of TI information in TI data books, data sheets or reference designs is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards that anticipate dangerous failures, monitor failures and their consequences, lessen the likelihood of dangerous failures and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in Buyer's safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed an agreement specifically governing such use.

Only those TI components that TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components that have **not** been so designated is solely at Buyer's risk, and Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.