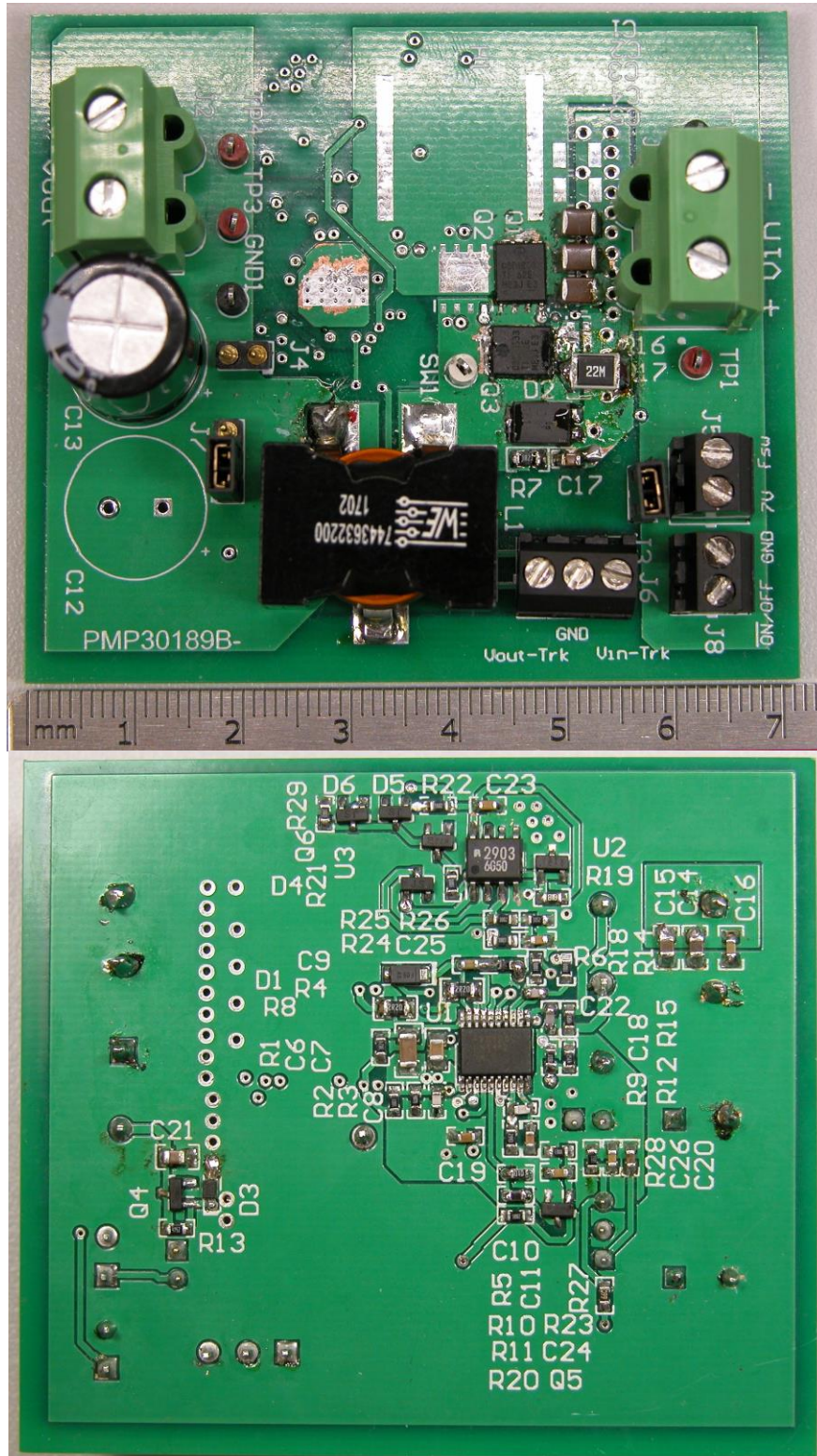


1. Photo of the prototype (71.12mm x 62.23mm).

The reference design PMP30301 Rev_A has been built on PMP30189 Rev_B PCB




2. Startup

The input and output voltage behavior at full and no-load conditions is shown in the images below.


Ch.1: Input voltage (10V/div, 20ms/div, 20MHz BWL)

Ch.3: Output voltage (5V/div, 20MHz BWL)

Load = 6.5A (full load), $V_{in} = 29V$

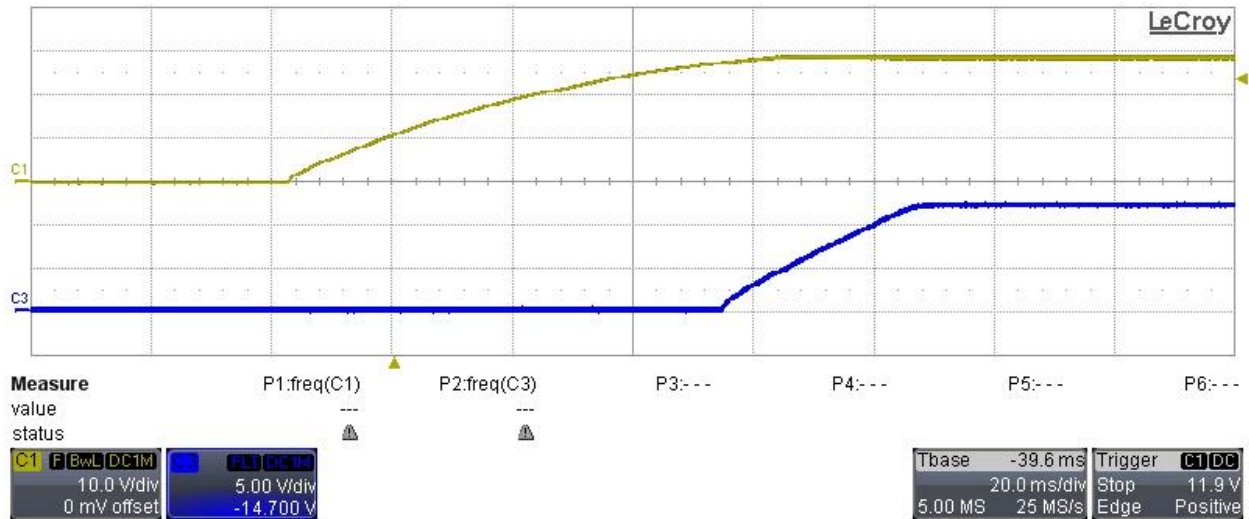

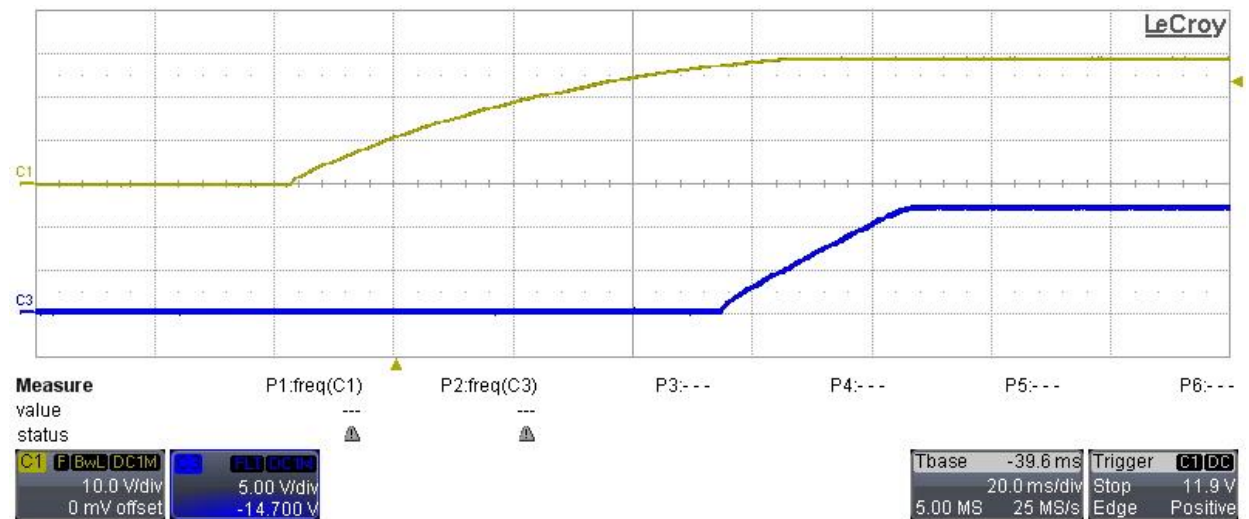Same condition as above but with zero load:




3. Shut down

The input and output voltage behavior during shut-down at full is shown below.


Ch.1: Input voltage (10V/div, 20ms/div, 20MHz BWL)

Ch.3: Output voltage (5V/div, 20MHz BWL)

Load = 6.5A, Vin = 29V

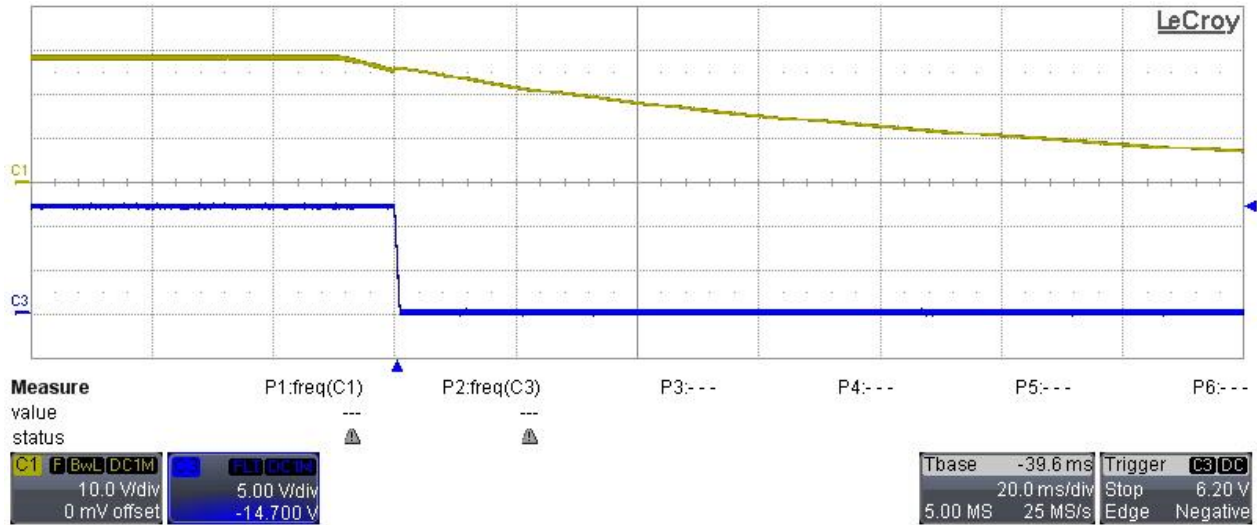


4. Output voltage regulation

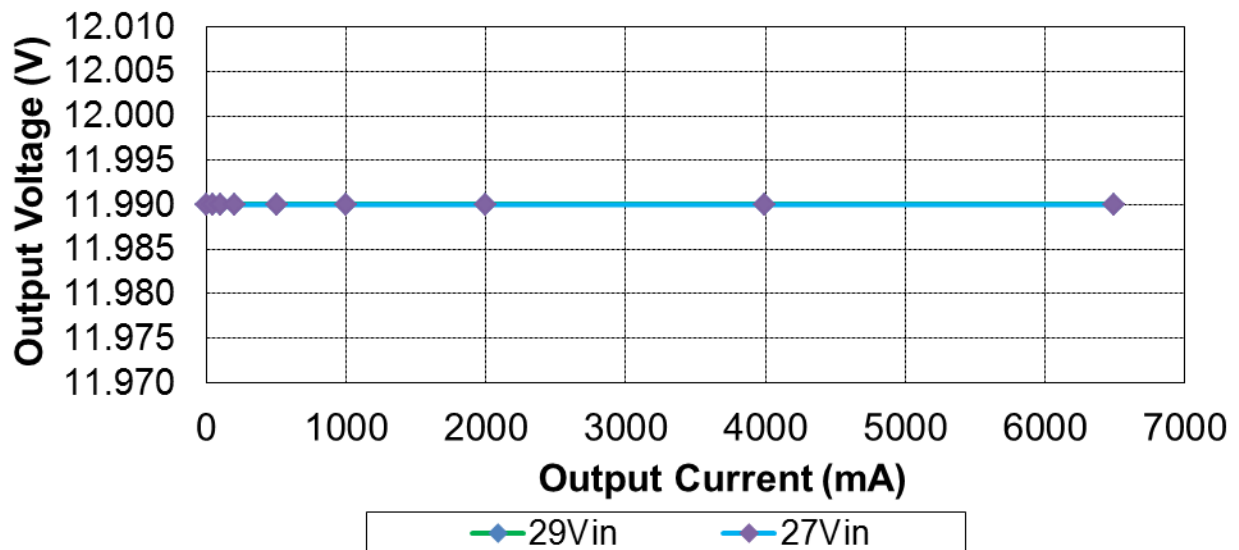

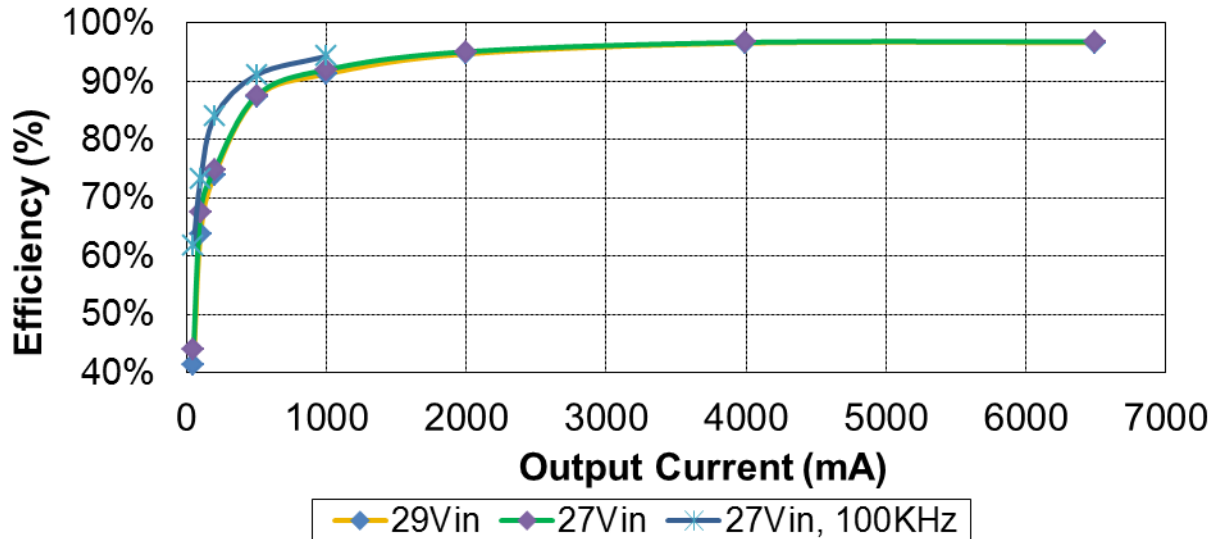5. Efficiency

The efficiency data, versus input and output voltage are shown in the tables and graphs below. The load (constant-current electronic load) has been varied from 0 to 6.5A. The input voltage has been set to 27V and 29V. Switching frequency setup:

- 100KHz: pin 1-2 of J5 left open
- 250KHz pin 1-2 of J5 shorted




29Vin, Fsw = 250 KHz						
Vin (V)	Iin(mA)	Pin (W)	Vout (V)	Iout(mA)	Pout (W)	Efficiency (%)
29.03	27.9	0.8099	11.99	0	0.00	0%
29.03	50.7	1.472	11.99	50.7	0.61	41.3%
29.03	65.7	1.907	11.99	101.5	1.22	63.8%
29.02	112.1	3.25	11.99	200.3	2.40	73.8%
29.01	238.1	6.91	11.99	502.8	6.03	87.3%
29.06	453.3	13.17	11.99	1002.8	12.02	91.3%
29.00	873	25.32	11.99	2000	23.98	94.7%
29.00	1712	49.65	11.99	3999	47.95	96.6%
29.01	2777	80.56	11.99	6495	77.88	96.7%


27Vin, Fsw = 250 KHz						
Vin (V)	Iin(mA)	Pin (W)	Vout (V)	Iout(mA)	Pout (W)	Efficiency (%)
27.00	28.6	0.7722	11.99	0	0.00	0%
27.00	51.5	1.391	11.99	50.9	0.61	43.9%
27.00	66.8	1.804	11.99	101.7	1.22	67.6%
27.04	118.9	3.22	11.99	200.4	2.40	74.7%
27.02	254.9	6.89	11.99	502.9	6.03	87.5%
27.00	484.0	13.07	11.99	1002.9	12.02	92.0%
27.05	932	25.22	11.99	2000	23.98	95.1%
27.00	1836	49.57	11.99	3998	47.94	96.7%
27.00	2979	80.43	11.99	6494	77.86	96.8%

27Vin, Fsw = 100 KHz						
Vin (V)	Iin(mA)	Pin (W)	Vout (V)	Iout(mA)	Pout (W)	Efficiency (%)
27.00	9.4	0.2538	11.99	0	0	0%
27.00	36.6	0.988	11.99	51.0	0.61	61.9%
27.00	61.7	1.666	11.99	101.8	1.22	73.3%
27.00	107.5	2.90	11.99	203.2	2.44	83.9%
27.00	245.1	6.62	11.99	503.0	6.03	91.1%
27.00	472.2	12.75	11.99	1002.9	12.02	94.3%

More details about efficiency:

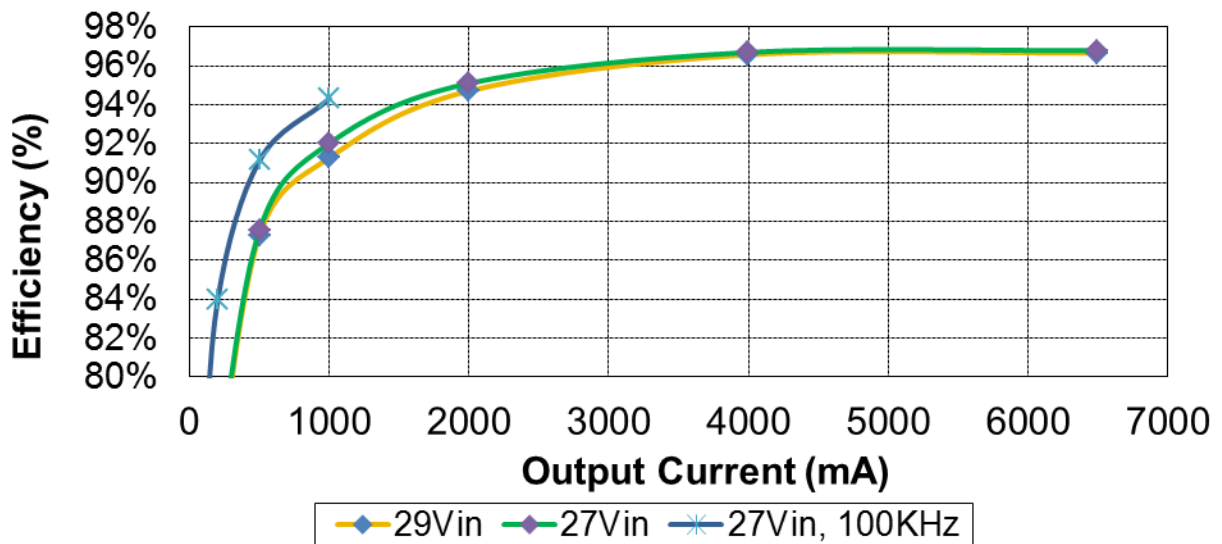


Light load details:

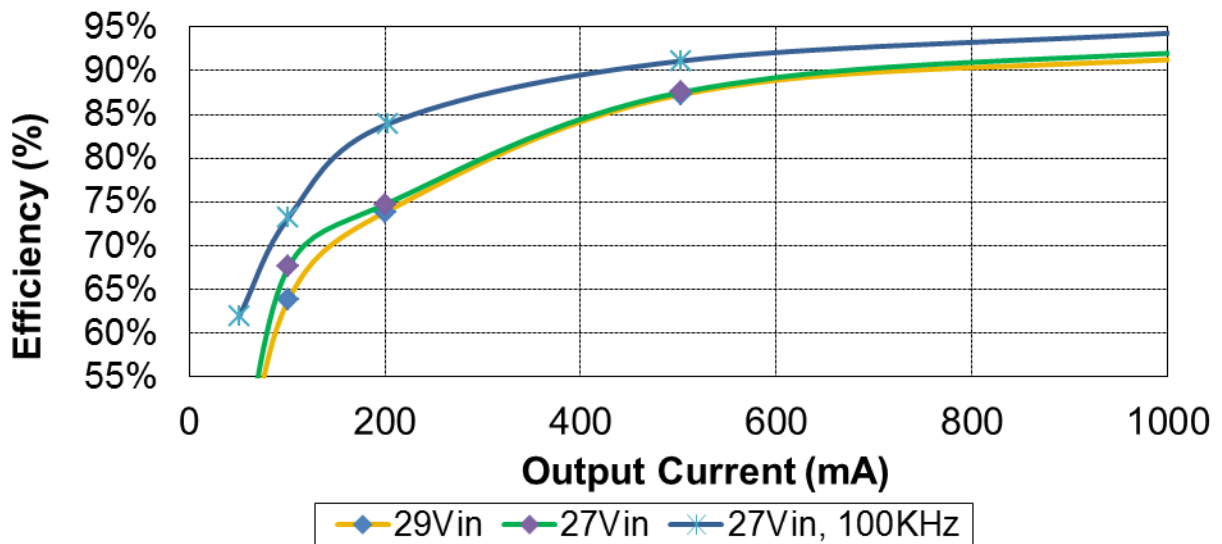

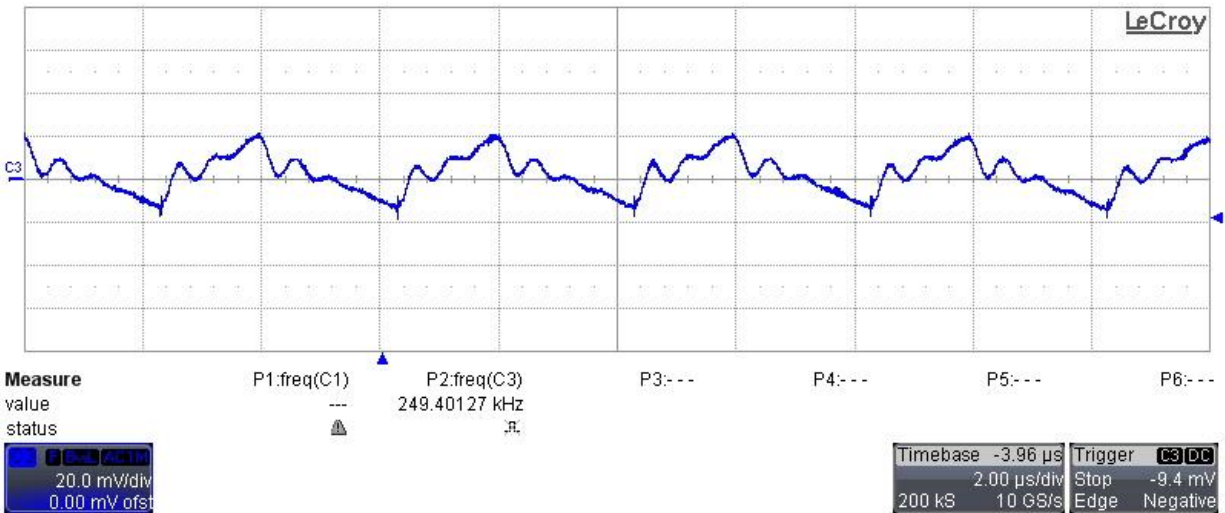6. Output Ripple Voltage


The output ripple voltage has been measured by supplying the converter at 29V while running at full load.

Ch.3: Output ripple voltage (20mV/div, AC coupling, 2usec/div, 20MHz BWL)



The following shows the measurement taken at the same conditions but without any bandwidth limit.

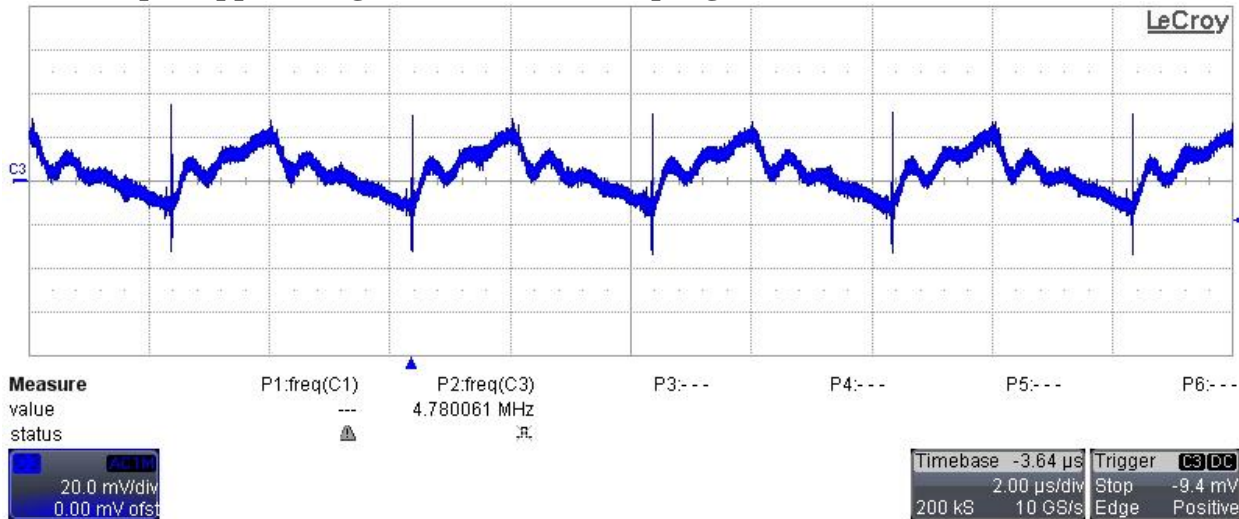
Ch.3: Output ripple voltage (20mV/div, AC coupling, 2usec/div, no BWL)



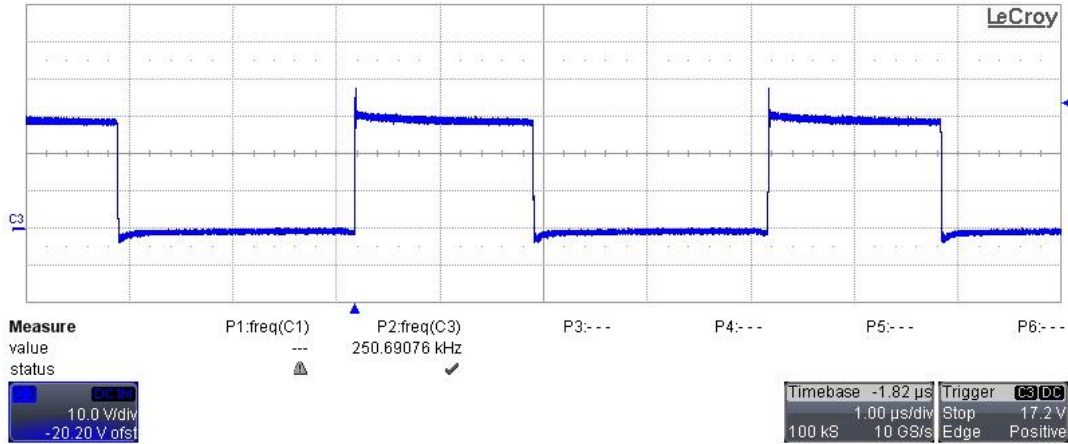7. Switch Node


The images below show the drain of Q3 taken at $V_{in} = 29V$ and full load.

Ch.3: Q3 Drain-Source voltage (10V/div, 1us/div, no BWL)




Rise time:

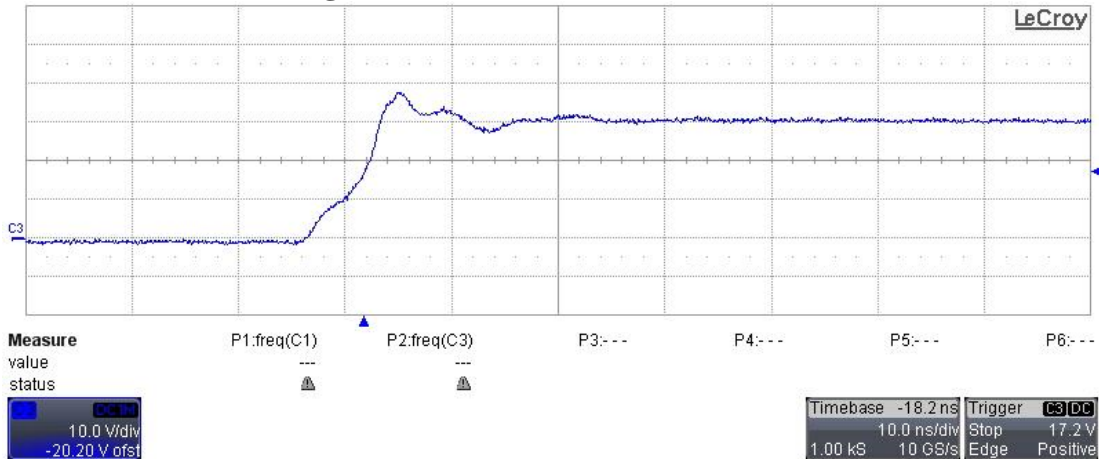Ch.3: Q3 Drain-Source voltage (10V/div, 10ns/div, no BWL)




Fall time:

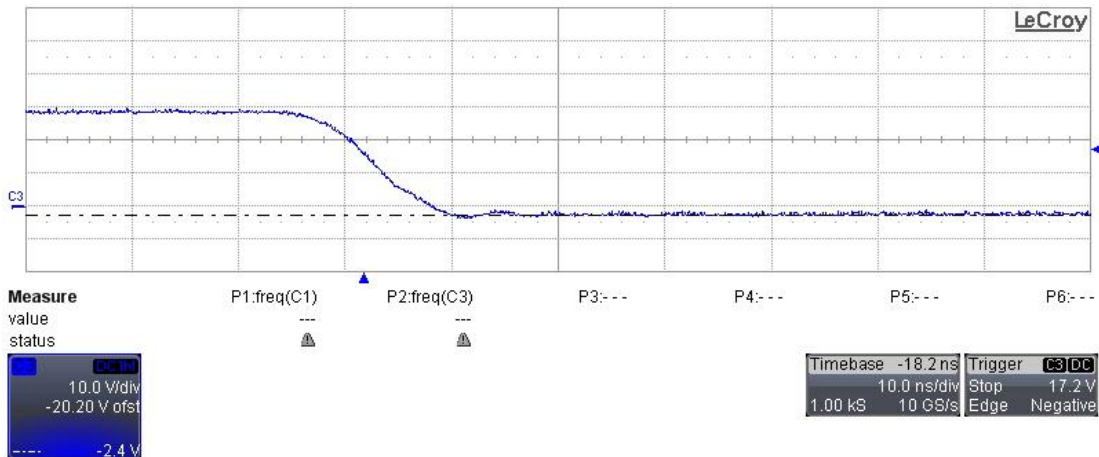

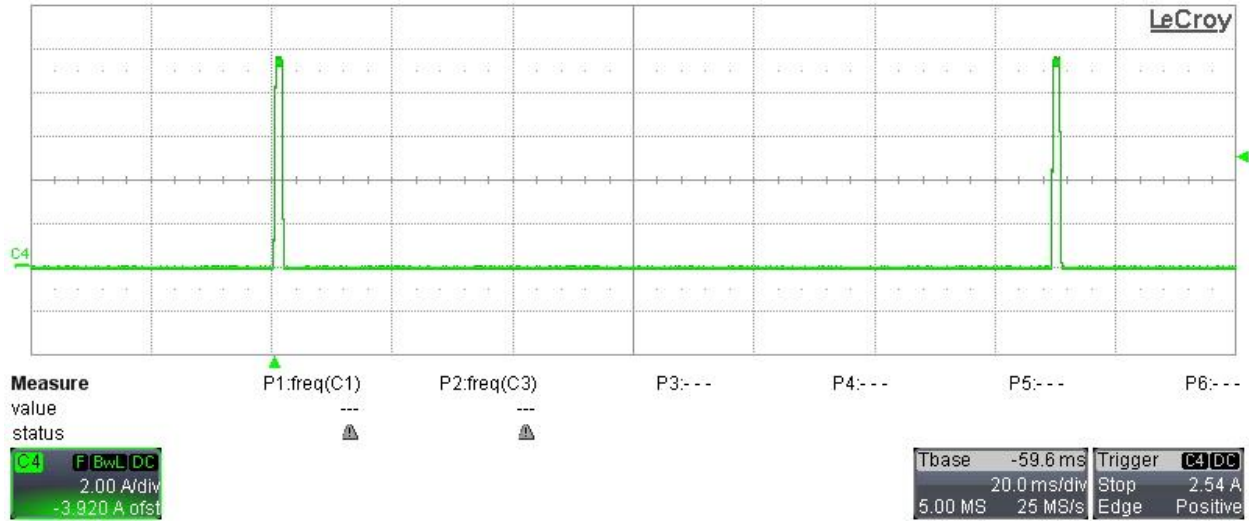8. Behavior in short circuit


The images below show the behavior of inductor current during short circuit condition at $V_{in} = 29V$.

Ch.4: L1 inductor current (2A/div, 20ms/div, 20MHz BWL)



Same measurement but with smaller time base:

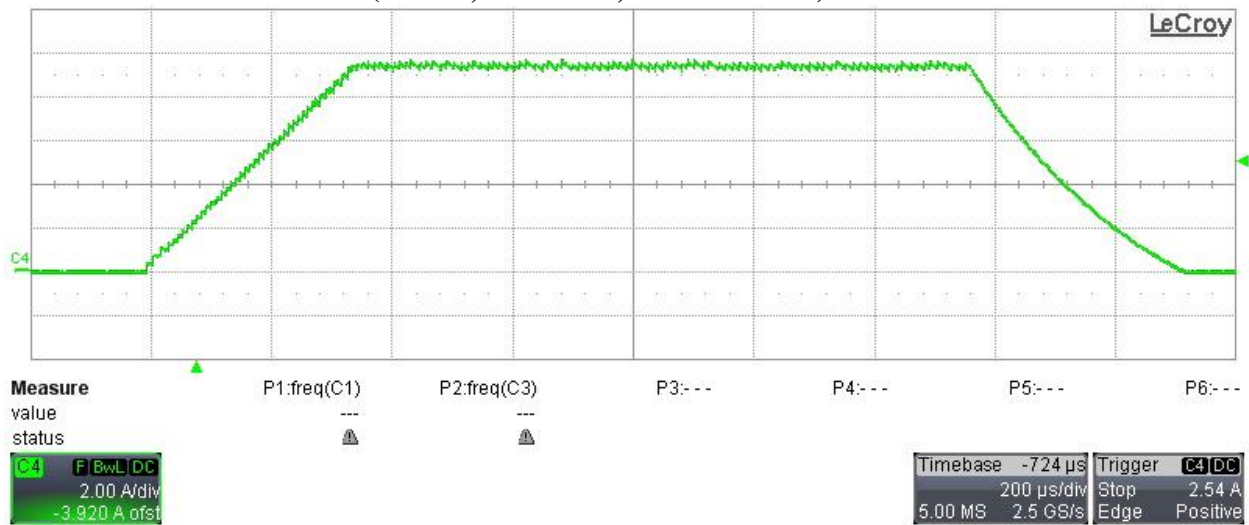Ch.4: L1 inductor current (2A/div, 200us/div, 20MHz BWL)




9. Current limit protection

The images below show the behavior of the converter during current limit protection (without latch). Vin has been set to 29V and the current increased until switch-off.

Ch.4: L1 inductor current (2A/div, 20ms/div, 20MHz BWL)

Ch.3: Output voltage (2V/div, 20MHz BWL)

Load = 7.6A

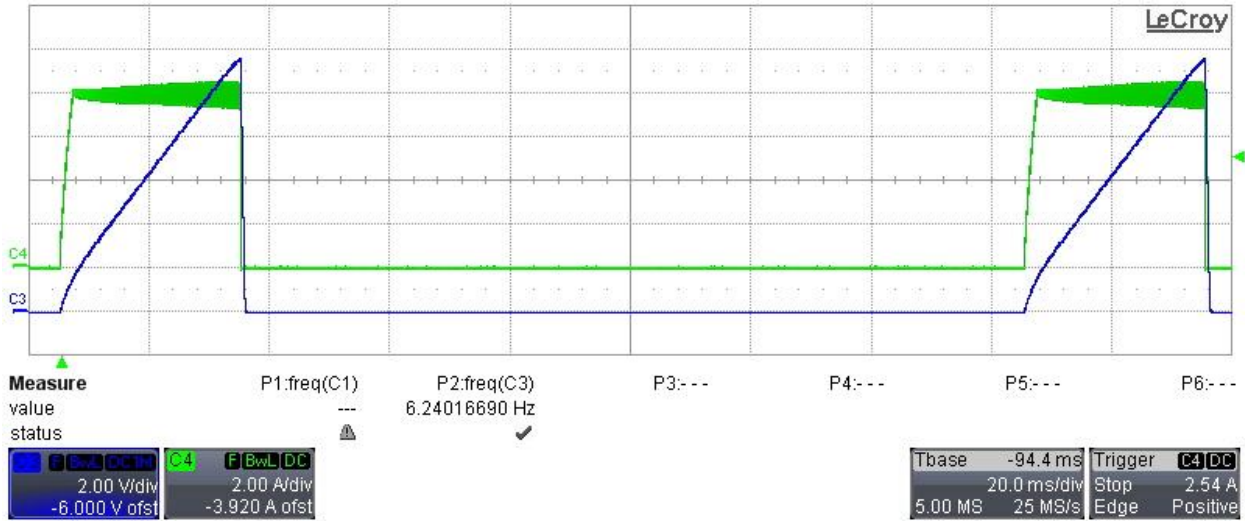


Same measurement as above, but with smaller time base:

Ch.4: L1 inductor current (2A/div, 5ms/div, 20MHz BWL)

Ch.3: Output voltage (2V/div, 20MHz BWL)

Load = 7.6A

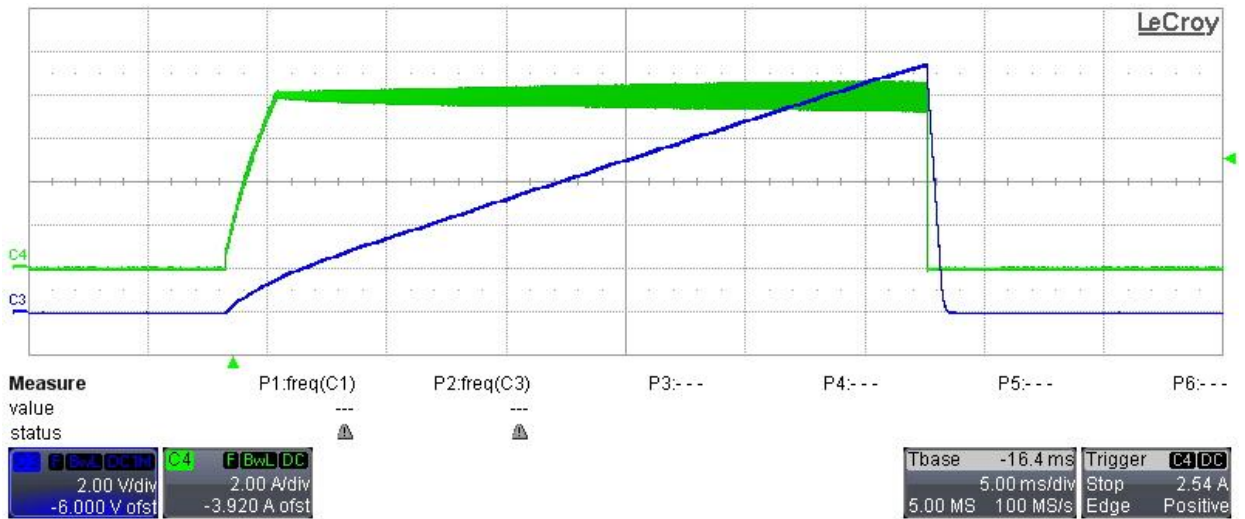


10. Behavior during over voltage protection

The images below show the behavior of the converter during over-voltage protection (with latch), performed by decreasing R9 to a value equivalent to $V_{out} = 15V$. V_{in} has been set to 29V and the load set to 1A for the first screenshot, 6.5A for the second one and unloaded for the third one.

Ch.3: Output voltage (2V/div, 5ms/div, 20MHz BWL)

Ch.4: L1 inductor current (2A/div, 20MHz BWL)


Load = 1A

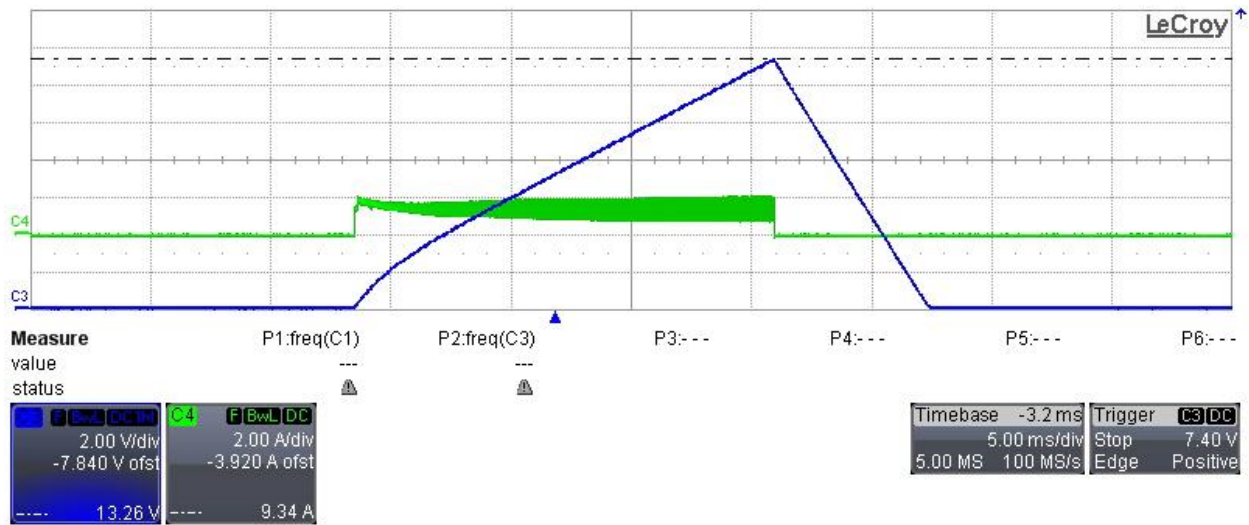

Ch.3: Output voltage (2V/div, 5ms/div, 20MHz BWL)

Ch.4: L1 inductor current (2A/div, 20MHz BWL)


Load = 6.5A

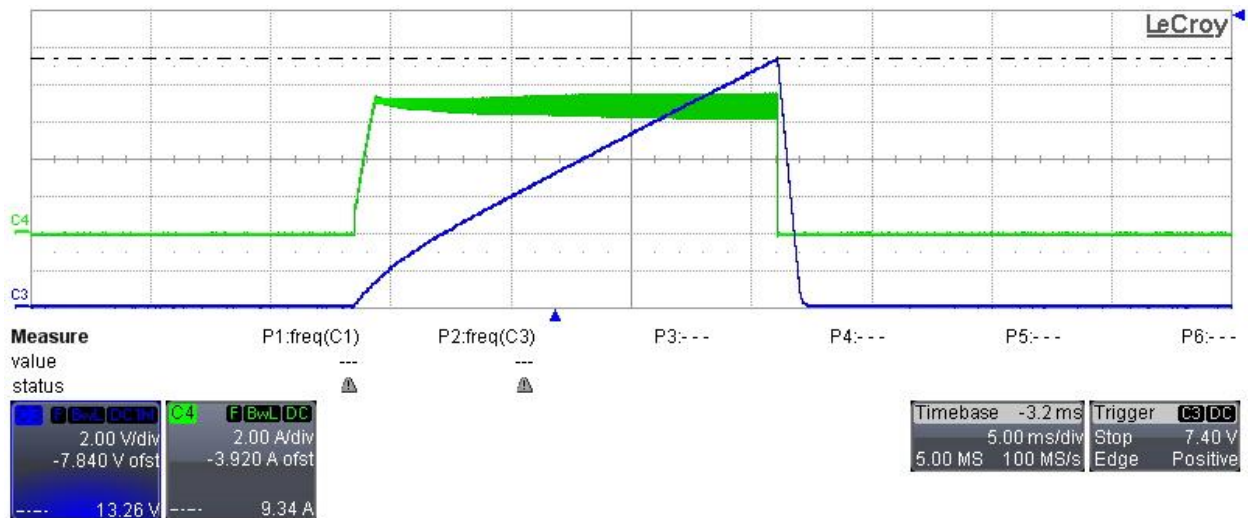

Ch.1: Output voltage (2V/div, 5ms/div, 20MHz BWL)

Ch.4: L1 inductor current (2A/div, 20MHz BWL)

Load = 0

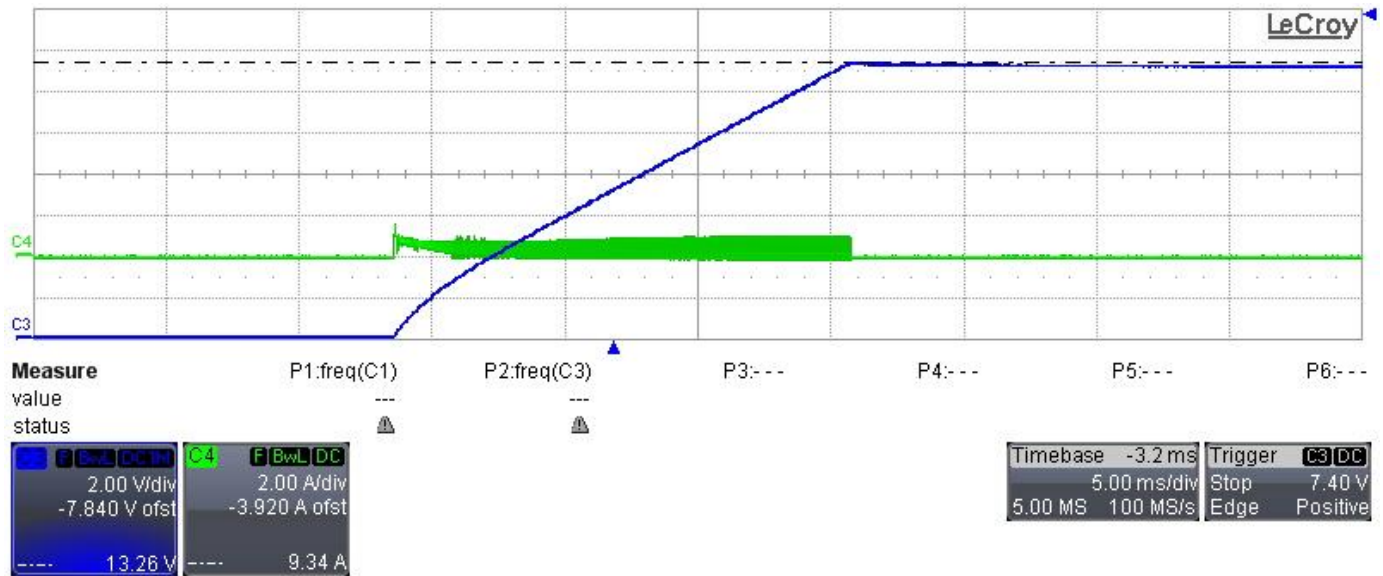


11. Load transient response

The converter has been loaded by switching the output current between 2A and 10A while supplied at 29V. The image below shows the output voltage deviation from nominal value.

Ch.3: Output voltage (100mV/div, 1ms/div, AC coupling, 20MHz BWL)

Ch.4: Output current (2A/div, 20MHz BWL)

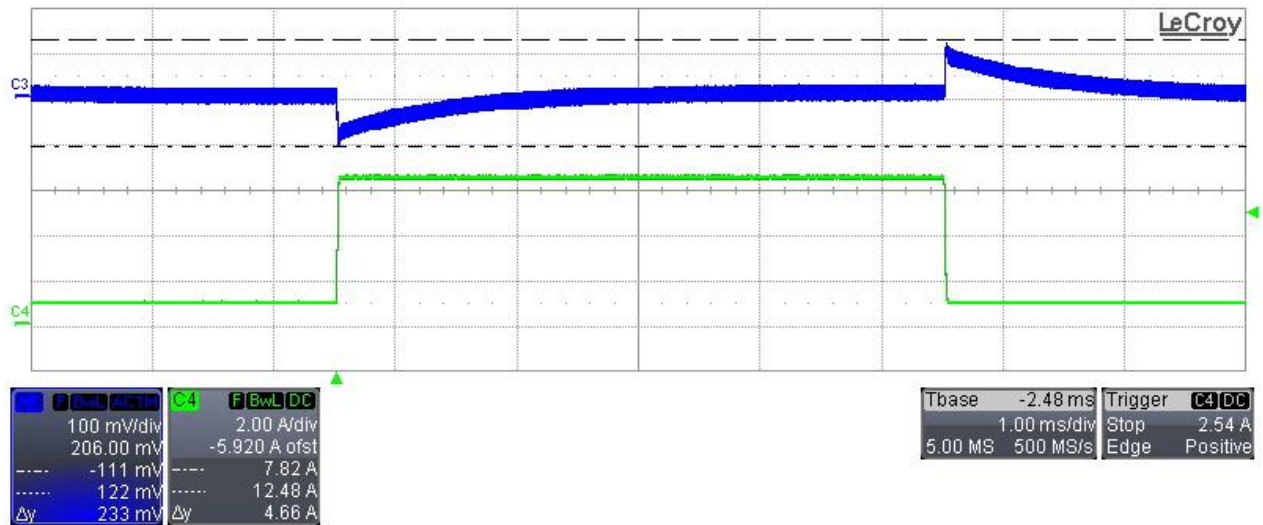


12. Feedback Loop Analysis

The image below shows the open loop gain and phase bode plot of the converter. The board has been supplied at $V_{in} = 29V$ and the load was a constant-current electronic load, set to 6.5A.

Crossover frequency: 19.6 KHz

Phase margin: 68.78 deg.


Gain margin: > 20 dB

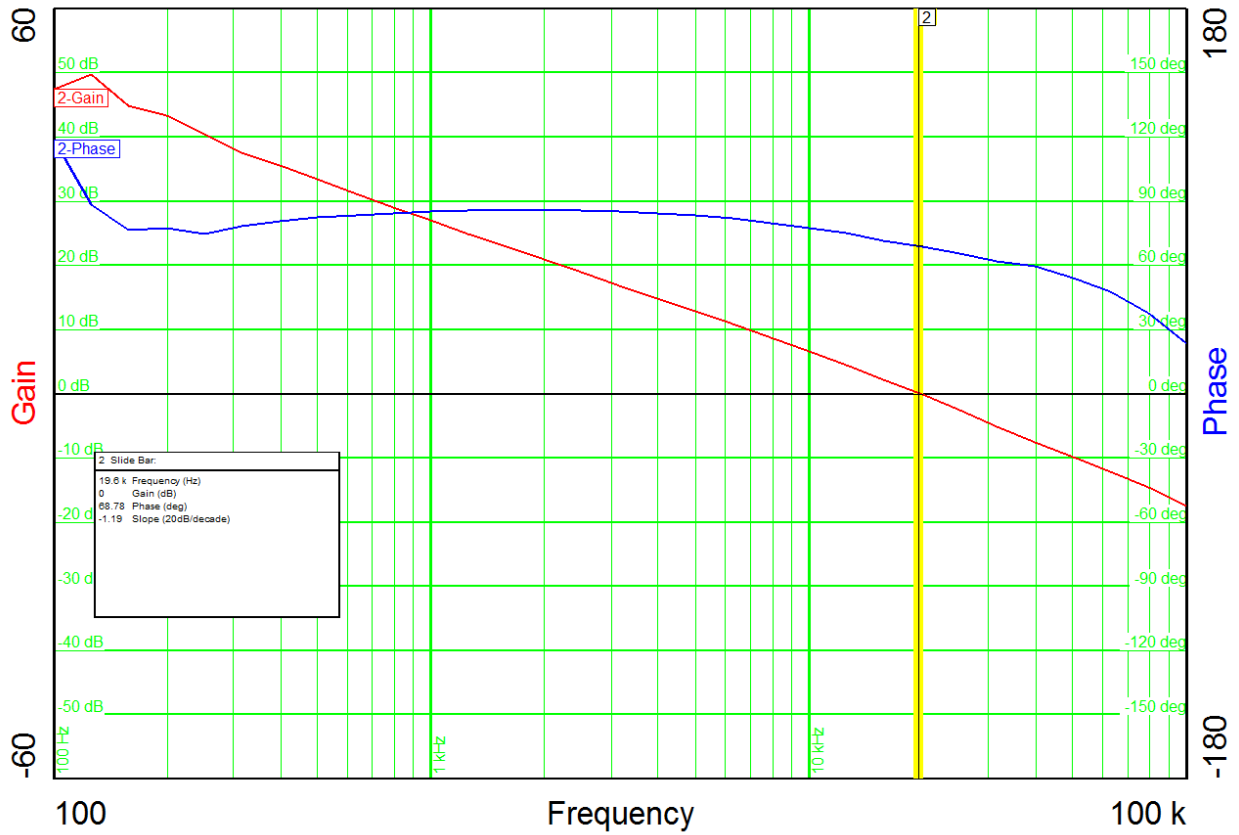

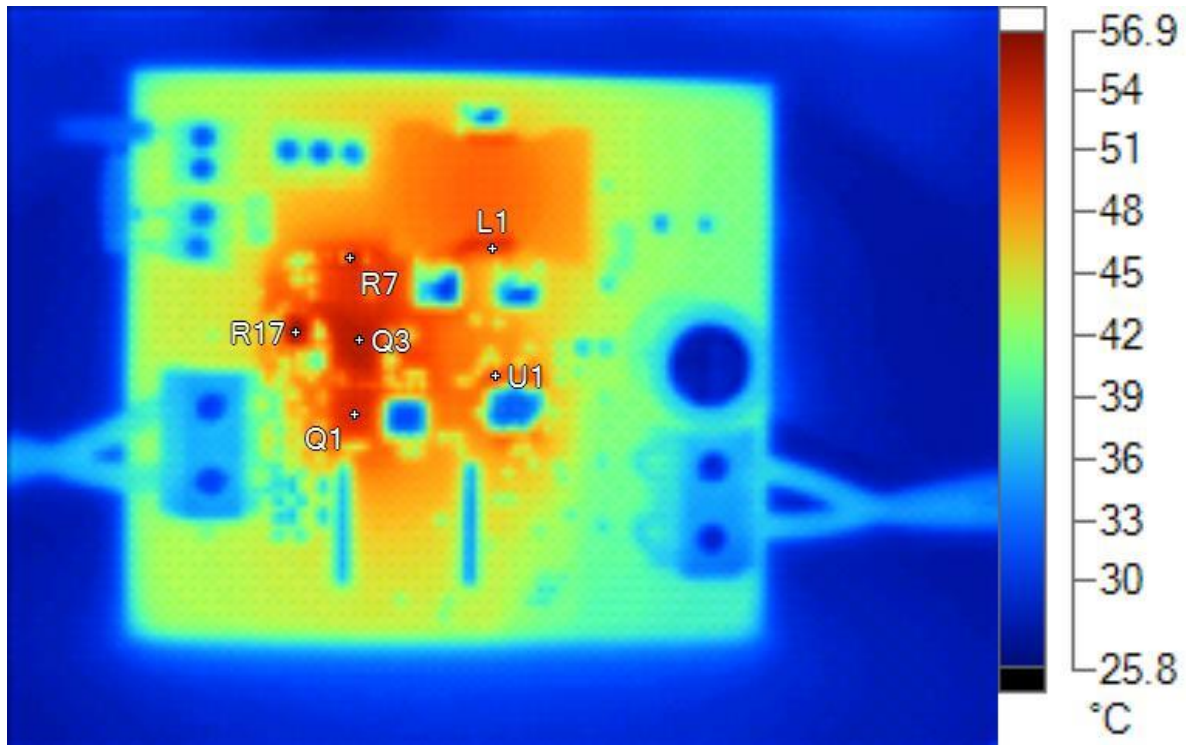13. Thermal Analysis

During the thermal analysis, the converter has been placed vertical on the bench in still air conditions, while supplied at 29V and fully loaded.

The thermal image has been taken after 30 minutes @ $T_a = 25\text{C}$.



IR20170706_1068.is2

7/6/2017 10:46:00 AM

Main Image Markers

Name	Temperature	Emissivity	Background
Q1	53.8°C	0.95	25.0°C
Q3	54.7°C	0.95	25.0°C
R17	55.7°C	0.95	25.0°C
R7	51.3°C	0.95	25.0°C
L1	52.1°C	0.95	25.0°C
U1	50.5°C	0.95	25.0°C

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated