# *Design Guide: TIDA-010947 High Resolution Low Latency Compact Absolute Angle Encoder Reference Design With AMR Sensor*



# **Description**

This reference design demonstrates a small form factor absolute single-turn magnetic rotary angle encoder circuit design using a high-precision analog AMR 360° angle sensor with sine and cosine differential ratio metric analog outputs and integrated quadrant detection using Hall sensors. The Cortex M0 MCU includes 4MSPS dual sampling 12-bit ADCs and up to 14-bit effective resolution at 250-ksps with hardware averaging for low noise and low latency absolute angle calculation and a 4Mbaud UART for high-speed data transmission. The absolute encoder requires a 5V input supply voltage with ±10% tolerance and offers a bidirectional communication interface using a half-duplex RS-485 transceiver.

# **Resources**

[TIDA-010947](https://www.ti.com/tool/TIDA-010947) Design Folder [TMAG6180](https://www.ti.com/product/TMAG6180-Q1) Product Folder [MSPM0G3507](https://www.ti.com/product/MSPM0G3507) Product Folder [THVD1454](https://www.ti.com/product/THVD1454) Product Folder [REF3533](https://www.ti.com/product/REF35), [TPS7A0533](https://www.ti.com/product/TPS7A05) Product Folder



Ask our TI E2E™ [support experts](https://e2e.ti.com/)



### **Features**

- Low noise absolute rotary angle better than 15 ENOB, angle accuracy error less than 0.05° at 25°C and low latency 16us
- Small IC packages enable a compact circular PCB with a diameter of 30mm
- AMR sensor and integrated Hall sensors for quadrant detection enable full 360° measurements and reduce BOM count
- Wide operating magnetic field range 20mT to 1T enables flexible mechanical placement
- MCU with integrated dual 12-bit ADC and up to 128-times oversampling and math accelerator help improve efficiency and reduce system cost
- RS485 transceiver with integrated 120Ω switchable termination in a VSON-10 package help reduce BOM and space

# **Applications**

- **[Servo Drive Position Sensor](https://www.ti.com/solution/servo-drive-position-sensor)**
- **[Position Sensor](https://www.ti.com/solution/position-sensor)**
- **[Traction Inverter Position Sensor](https://www.ti.com/solution/traction-inverter)**



1



# **1 System Description**

Single or multi-turn absolute rotary angle encoders are used in many applications such as servo drives and robotics, where an absolute mechanical angle position is required. Absolute encoders typically offer a serial unidirectional or bidirectional half-duplex or full-duplex RS485 interface with vendor specific or open encoder protocols.

This reference design demonstrates a small form-factor absolute single-turn magnetic rotary angle encoder circuit design using on-axis sensing, as shown in Figure 1-1. A circular disc magnet is mounted to the end of the rotating shaft of the encoder. A static PCB with the TMAG6180-Q1 high-precision analog AMR 360° angle sensor is mounted on-axis with configurable air gap from the top of the AMR sensor package to the circular disc magnet. The effective air gap includes the location of the AMR and Hall sensor inside the IC package. The integrated two independent Hall sensor outputs at X and Y axes are used to extend the angle range of the sensor to 360° mechanically.



**Figure 1-1. On-Axis Magnetic Angle Sensing Principle**

The TMAG6180-Q1 features integrated signal conditioning amplifiers and provides differential sine and cosine analog outputs related to the direction of the applied in-plane magnetic field.

A Cortex M0 MCU MSPM0G3507 with 4MSPS dual sampling 12-bit ADC with up to 128-times hardware integrated averaging enables low noise and low latency absolute angle calculation and a 4-Mbaud UART for high-speed rotary angle data transmission. The absolute encoder circuit design offers a bidirectional interface using a half-duplex RS-485 transceiver with integrated 120Ω switchable termination in a small 10-VSON package. A 5V supply with ±10% tolerance is required to power the absolute encoder circuit.



# **1.1 Key System Specifications**

The key specifications of the TIDA-010947 high resolution low latency compact absolute angle encoder reference design with AMR sensor is provided in Table 1-1.





# **2 System Overview**

# **2.1 Block Diagram**

The block diagram of this reference design is shown in Figure 2-1.



**Figure 2-1. System Block Diagram**

# **2.2 Design Considerations**

Magnetic encoders are popular in harsh industrial applications due to the magnetic encoders wide operating temperature range up to 125°C ambient and robustness against shock and vibration.

The magnetic sensor can be a Hall-effect sensor or a magneto resistive sensor, such as an Anisotropic Magneto Resistive (AMR) sensor, which typically have a lower noise than a Hall-effect sensor. However, magneto resistive sensors measure the magnitude of the magnetic field, but cannot sense the direction. Therefor additional sensors, such as digital Hall switches are required to extend the measurement range to 360°.

For motor integrated encoder applications with the magnet mounted at the end of shaft, on-axis sensing with two ARM sensors which are 45° rotated against each other are well designed.

The electrical signal chain offset and gain mismatch as well as sample rate, speed and resolution of the analog to digital converter impact the accuracy of the measured absolute angle and components with very low temperature drift help reduce the angle error. Decoding of the angle from the sine and cosine sensor signals require math functions such as division, multiply-and -accumulate and arc tangent.

Small footprint circuits with high integration and low power consumption are critical to design smallest form factor circular PCB of less than 30mm diameter. Since the encoder can be motor integrated, ambient operating temperatures at least up to 125°C are typically required.

The absolute encoder RS485 communication interface need to be designed for high EMC immunity to minimize bit errors during the data transmission.



# **2.3 Highlighted Products**

#### *2.3.1 TMAG6180-Q1*

The TMAG6180-Q1 is a high-precision angle sensor based on Anisotropic Magneto Resistive (AMR) technology. The device features integrated signal conditioning amplifiers and provides differential sine and cosine analog outputs related to the direction of the applied in-plane magnetic field. This device also features two independent Hall sensor outputs at X and Y axes that can be used to extend the angle range of the sensor to 360°. The key features with this design are:

- High-speed AMR angle sensor with ultra-low latency < 2us
- Low angle drift eliminates the need for calibration across temperatures
- Sine and cosine differential ratio metric analog outputs supports differential-ended or single-ended applications
- Wide operating magnetic field range: 20mT to 1T
- Integrated Quadrant Detection using Hall sensors
- Temperature range -40°C to 150°C



**Figure 2-2. TMAG6180 Functional Block Diagram**

#### *2.3.2 MSPM0G3507*

The MSPM0G350x microcontrollers (MCU) are part of the MSP highly integrated, ultra-low-power 32-bit MCU family based on the enhanced Arm™ Cortex®-M0+ 32-bit core platform operating at up to 80MHz frequency. These cost-optimized MCU offer high-performance analog peripheral integration, support extended temperature ranges from -40°C to 125°C, and operate with supply voltages ranging from 1.62V to 3.6V. The MSPM0G350x MCU key features with this design include:

- Two simultaneous sampling 12-bit 4-Msps analog-to-digital converters (ADC) with up to 17 external channels
- 14-bit effective resolution at 250-ksps with hardware averaging
- Optimized low-power modes
	- RUN: 96µA/MHz (CoreMark)
	- STANDBY: 1.5µA with RTC and SRAM retention
- Math accelerator supports DIV, SQRT, MAC, and TRIG computations

5



# *2.3.3 THVD1454*

The THVD1454 is a half-duplex RS-485 transceiver for industrial applications. The device has features such as an on-chip, 120Ω termination resistor and driver output slew rate control. The key features with this design are:

- Pin controlled on-chip 120Ω termination resistor between the bus pins
- Maximum Data rate configurable SLR = High: 500kbps SLR = Low or floating: 20Mbps
- Bus I/O protection
	- ±16kV HBM ESD
	- ±8kV IEC 61000-4-2 Contact discharge, ±15kV IEC 61000-4-2 Air gap discharge
	- ±4kV IEC 61000-4-4 Fast transient burst
- ±16V bus fault protection (absolute max voltage on bus pins)
- Extended industrial temperature range: -40°C to 125°C



# **3 System Design Theory**

# **3.1 Hardware Design**

#### *3.1.1 Angle Sensor Schematic Design*



**Figure 3-1. AMR Sensor TMAG6180 Schematic**

A 100nF decoupling capacitor C11 is added close to the TMAG6180's VCC and GND pin. Q0 and Q1 are open-drain outputs, and 100k pull-up resistors R7 and R9 are connected to 3.3V power rail.

The TLV9062 is optional and used to convert the TMAG6180-Q1 differential analog outputs SIN\_P, SIN\_N and COS P, COS N to a single-ended signal to connect to the MSPM0G3507 ADC. There is the possibility to bypass TLV9062 by populating R8, R11, R12 , R13, R16, R18 as 0Ω resistor. To make sure the stable supply voltage at VCC, C15(100nF) is placed between VCC and GND.

The differential gain of TLV9062 can be calculated by Equation 1.

$$
\frac{V_o}{V_{in}} = \frac{R_{12}}{R_8} = \frac{R_{19} \parallel R_{23}}{R_{17}} = \frac{1}{2}
$$
\n<sup>(1)</sup>

Chose unit gain and let R8 be 10kΩ, so R17and R20 needs to be 10kΩ, R12 needs to be 5kΩ.

C18 is added to filter out high frequency noise. The bandwidth (BW) can be calculated by Equation 2.

$$
BW = \frac{1}{2\pi C_1 8R_1 2} = \frac{1}{2\pi (C_{20} \parallel C_{22})(R_{19} \parallel R_{23})}
$$
(2)

Chose 3MHz bandwidth, C18 can C19 needs to be 10pF. C20 approximately C23 needs to be half of C18, which is 5pF.

7



#### *3.1.2 MSPM0G3507 Schematic Design*



**Figure 3-2. MSPM0G3507 Schematic**

The ceramic decoupling capacitors C3 (10µF) and C4 (1µF) are placed across the VDD and VSS pins, and C1 (100nF), C2 (0.47uF) are placed across the VCORE and VSS pins. A ferrite bead FB1 is added between VDD and 3.3V power rail to avoid the high frequency digital current impacting the analog signal chain.

The nRST reset pin is pulled up to VDD with 47kΩ resistor R2 and 10nF pulldown capacitor C7. The SYSOSC frequency correction loop (FCL) circuit uses an external 100kΩ with 0.1% tolerance resistor R5 populated between the ROSC pin and VSS.

The MSPM0G3507 accepts an external reference to further improve the accuracy of the integrated ADC. In this design, an external 3.3V reference REF3533 is used and connected to the MSPM0G3507 VREF+ and VREFpins. A 100nF decoupling capacitor (C10) is placed across VREF+ and VREF-.

#### *3.1.3 RS485 Transceiver Schematic Design*



**Figure 3-3. THVD1454 Schematic**

To avoid the switching noise of RS485 transceiver influence the 3.3V power rail, which powers the TMAG6180, a separate 5V supply is used to supply the THVD1454. For reliable operation at all data rates and supply voltages, VCC supply needs to be decoupled with a 1uF ceramic capacitor (C12) located as close to the supply pin as possible. This reference design also uses a level shifter TXU0101 to convert the 5V signal on the THVD1454 R pin to a 3.3V signal to be compatible with MSPM0 GPIO input voltage range.



DE and /RE pins are direction control pins of THVD1454, since THVD1454 works on half-duplex mode. DE and /RE pins are connected together. The pulldown resistor R25 (10kΩ) is added to make sure THVD1454 is working on receive mode by default.

THVD1454 has integrated a 120Ω terminal resistor which is controlled by the TERM pin. The TERM pin is connected to MSPM0 GPIO PA4 to to enable the internal terminal resistor through MSPM0 software.

The 100kΩ pullup resistor R15 and pulldown resistor R22 are connected to A and B separately. These resistors limit the residual clamping current into the transceiver and prevent the transceiver from latching up.

#### *3.1.4 Power Supply and Reference Voltage*



**Figure 3-4. Power Supply Schematic**

TPS7A0533 and REF3533 are used in this design to power the devices on the board. For TPS7A0533, the device accepts up to 5.5V input voltage and generates a 3.3V rail for TMAG6180, TLV9062, MSPM0G3507 and THVD1454 supply. Two parallel capacitors C5 (1μF) are used for noise decoupling, an output capacitor C6(10μF) is used for minimize the output voltage ripple.

For REF3533, the device is powered by an external 5V supply and generates precise 3.3V output as MSPM0 ADC's reference. Similarly with the TPS7A0533, C8 (100nF) is used for decoupling. C9(1uF) is used for minimize the output voltage ripple.

#### **3.2 Software Design**

To validate this reference design a TI internal test software has been developed with the MSPM0G3507 using the MSPM0 software development kit for M0 MCU.

9



# *3.2.1 Angle Calculation Timing*



**Figure 3-5. MSPM0G3507 Timing Diagram**

In this reference design, the MSPM0G3507 integrated dual ADCs convert the TMAG6180's sine and cosine output signals. The MSPM0G3507 ADC are configured for 64-times hardware averaging and are simultaneous and periodically triggered by an internal 32kHz Timer0. The ADC end-of- conversion triggers an interrupt at which the two ADC conversion results and the status of the Hall latches Q0 and Q1 are read and the absolute angle is calculated.

When the host controller sends a command request to get position data, the controller triggers a UART interrupt in the MSPM0. Then the transmit data is stored to an array, and the DMA controller starts the UART transmission to the host controller.

The Timer0 interrupt is phase locked to encoder read command frequency from the host controller to minimize angle transmission latency and jitter.



#### *3.2.2 Rotary Angle Calculation*



**Figure 3-6. Angle Calculation Flow Chart**

Since AMR sensors generate two sine and cosine periods over one mechanical revolution, additional sensing is required to distinguish between 0° to 180° and 180° to 360°. Therefore the TMAG6180 integrates two X,Y Hall switches, which help to extend the angle range from 180° to 360° using Q0 and Q1 outputs. The angle calculation flow chart is shown in Figure 3-6 and the example code in the following:

```
//----------------------------------------------------------------------
//Angle calculation
//----------------------------------------------------------------------
\left[ \frac{1}{2} \right] = \frac{1}{2}//comp0[1] = <math>\bot Q(1)</math>\frac{1}{\sqrt{c}} comp1[0] = _IQ(1)
\frac{1}{2} = _{1Q(0)}//----------------------------------------------------------------------
     SinCosInput.SinCos.Sin = SinCosInput.SinCos.Sin - Adc16bitOffset;
     SinCosInput.SinCos.Cos = SinCosInput.SinCos.Cos - Adc16bitOffset;
//ATAN2 calculation
     DL_MathACL_startArcTan2Operation(MATHACL, &gAtanOpConfig, SinCosInput.SinCos.Sin, 
SinCosInput.SinCos.Cos);
     DL_MathACL_waitForOperation(MATHACL);
     SinCosOutput.PhasePU = DL_MathACL_getResultOne(MATHACL);
    angle = _IQ(0.25) - (SinCosOutput \cdot PhasePU>>1);// Extend to 360 deg. 90 degree \sim 0.25, 45 degree \sim 0.125, 135 \sim 0.375
 if((angle <= _IQ(0.375)) && (angle>_IQ(0.125)))
         absangle=comp0[TMAG_Q0]+angle;
     else
    \mathbf{f} if (angle>_IQ(0.375))
                absangle=comp1[TMAG_Q1]+angle;
           else
                absangle=_IQ(0.5)-comp1[TMAG_Q1]+angle;
     }
```


### *3.2.3 Rotary Angle Error Sources and Compensation*

For accurate angle measurement, the center of the magnet need to be aligned to the center of the sensor with acceptable tolerances. Follow these steps to calibrate the sensor for best accuracy:

- Set the reference angle based on the magnet alignment to the sensor. This error can be saved in the microcontroller for run time absolute position calculation. This error is also known as angle offset in a system.
- Electrical offset calibration, see *[Calibration of AMR Angle Sensors](https://www.ti.com/lit/pdf/slya085)* for the offset calibration procedure. If the sensor cannot be rotated across the full range, then the electrical offsets cannot be calibrated.
- Amplitude mismatch calibration, see *[Calibration of AMR Angle Sensors](https://www.ti.com/lit/pdf/slya085)* for the amplitude mismatch calibration procedure. If the sensor cannot be rotated across the full range, then the amplitude mismatch cannot be calibrated.

Further error sources include non-linearity of the sensor signal chain such as the 3rd harmonics, and a mechanical error through coupling a reference angle encoder to the shaft of the absolute magnetic encoder. Figure 3-7 through Figure 3-10 outline the error source and the impact to the angular error to understand and compensate these types of errors.





**Figure 3-8. Angle Error Example due to Shaft Coupling Displacement**





**Figure 3-10. Angle Error Example due to AMR Sensor Displacement**

Electrical offset, gain-mismatch and non linearity ( $3<sup>rd</sup>$  harmonics) of the sensor signal chain impact the angle error, examples are shown in [Figure 3-11](#page-12-0) to [Figure 3-13](#page-12-0).

<span id="page-12-0"></span>



**Figure 3-13. Angle Error Example due to AMR Sin/Cos Signal Chain Non-Linearity (-0.1%)**

Table 3-1 summaries the impact on the angular error pattern.



#### **Table 3-1. Errors Sources and Impact on Angle Error Harmonics**

For more information on angle position calculation algorithms refer to *[Achieving Highest System Angle Sensing](https://www.ti.com/lit/pdf/sbaa539) [Accuracy](https://www.ti.com/lit/pdf/sbaa539)*, application note.

#### *3.2.4 Encoder Communication Interface*

This absolute encoder reference design communicates with the host controller through the RS485 interface to transmit the angle data. The communication runs at a 4M baud rate UART protocol. The host controller sends different T-format command request and the encoder responds with the corresponding field stipulated by the T-format protocol. [Figure 3-14](#page-13-0) shows an example communication. For more details on the T-format protocol, refer to *[TAMAGAWA Encoder Catalog](https://www.tamagawa-seiki.com/assets/img/downloads/pdf/rotaryencoder/1228N61EJ.pdf)*.



<span id="page-13-0"></span>

**Figure 3-14. Command Request**

The software is configured to respond to the ID3 command, which requires to return all of the encoder data, including command field, status field, single-turn data field, encoder ID, multi-turn field, alarm field, CRC field, total 11 bytes. The field format is listed in Table 3-2. Since the angle is calculated in IQ21 format in MCU, 3 bytes of data field are required to transmit the angle data.

#### **Table 3-2. Field Format**





# **4 Hardware, Software, Testing Requirements, and Test Results**

### **4.1 Hardware Requirements**

#### *4.1.1 PCB Overview*

The PCB top and bottom view are shown in Figure 4-1 and Figure 4-2.



**Figure 4-2. PCB Bottom View**

#### *4.1.2 Encoder and JTAG Interface*

The TIDA-010947 interfaces are listed in [Table 4-1](#page-15-0) and [Table 4-2.](#page-15-0) J1 is the RS485 data communication interface. The T-format is implemented over this interface to communicate with host MCU. J2 is the JTAG interface to MSPM0 MCU, which is used to download and debug the software.

<span id="page-15-0"></span>



#### **Table 4-2. JATG Interface**



#### *4.1.3 Software Requirements*

To validate this reference design a TI internal test software has been developed with the MSPM0G3507 using the M0 software development kit for M0 MCU.



#### **Table 4-3. Key Software Configuration**

# **4.2 Test Setup**



#### **Figure 4-3. Test Setup**



[Figure 4-3](#page-15-0) shows the static noise test setup in lab. The rotary angle accuracy test was done in external lab, there was no opportunity to take a picture there.

# **4.3 Test Results**

#### *4.3.1 AMR Sensor Sin and Cos Outputs Measurement*

Figure 4-4 and Figure 4-5 show the AMR sensor sine and cosine signals converted to single-ended at the input of the MSPM0G3507 ADCs over half a mechanical revolution from 0 to 180 degree mechanically. The signals are biased to 1.65V and the peak to peak amplitude is around 2V. The maximum voltage is around 2.65V, the minimum voltage is around 0.65V. The full-scale input range of the MSPM0 internal ADC is 3.3V using external REF3533 reference. That means the AMR sensors use 62% of the full-scale range giving enough headroom for signal chain gain and offset changes.



To measure the signal to noise ratio and effective number of bits, 2000 consecutive of the sine and cosine signals where measured at a 32kHz sample rare and a fixed angle.

The following two figures show the offset corrected sine and cosine signals in the time domain over 62.5ms. The 1.65V bias voltage was subtracted from the corresponding A/D converted sine and cosine input signal. The peak to peak noise is within 0.6mV. Figure 4-6 and Figure 4-7 show the corresponding histogram of the sine and cosine signal.











*Hardware, Software, Testing Requirements, and Test Results* [www.ti.com](https://www.ti.com)





**Figure 4-8. Histogram Sin Signal, 2000 Samples Figure 4-9. Histogram Cos Signal, 2000 Samples**

The standard deviation, signal-to-noise ratio (SNR) and effective number of bits (ENOB) versus full-scale range are shown in Table 4-4. With the ADC in 64-times averaging mode the SIN signal's ENOB is 13.3 bit, the COS is 13 bit.

**Table 4-4. Standard Deviation, SNR and ENOB versus TMAG6180 Full Scale Range**

Parameter	X-axis	<b>Y-axis</b>	∣Comment
Standard deviation [mV]	0.082	0.101	<b>RMS</b>
Sin/Cos amplitude [V]			peak
$ SNR $ $dB$	81.7	80	dB
<b>ENOB</b> [bit]	13.3	13	Bit





**Samples at 32kHz Sample Rate Figure 4-11. Histogram of Angle at 224.8 deg, 2000 Samples 1LSB at 17-bit bin Width**

Keep the motor shaft at fixed 224.8° mechanical angle. MSPM0 calculates angle at 32kHz. Get 2000 angle samples, plot the time-domain figure and histogram in Figure 4-10 and Figure 4-11.

The corresponding standard deviation and ENOB versus full-scale position measurement range are shown in [Table 4-5.](#page-18-0) The RMS of angle noise is 0.0033°, which means 94.7dB SNR versus 360° full scale range and 15.4 ENOB.

#### *4.3.2 Static Angle Noise Measurement*

<span id="page-18-0"></span>





Assuming uncorrelated noise, the theoretical total resolution of the absolute mechanical angle can increase by 2-bit versus the effective number of bits (ENOB) of the AMR sensors sine and cosine signal chain including the 12-bit ADC with 64-times oversampling. The theoretical resolution of the sin/cos interpolated angle over one electrical AMR sensor period equals the sine and cosine subsystem's ENOB + 1 bit. With this design there are two electrical periods per mechanical revolution, resulting in one additional bit.

Change the motor shaft angle with 22.5° interval. Get 2000 samples at each angle, the corresponding RMS and peak to peak value is listed in Table 4-6 and Table 4-7. The peak to peak static angle noise is around 0.02° and maximum value occurs at 225°.







#### **Table 4-7. Static Angle Noise Over Second Half Revolution (180° Approximately 360°)**

Figure 4-12 shows the peak to peak angle noise with black color with reference to the y-axis on the left over one mechanical revolution. The angle standard deviation is shown in red color with reference to x-axis in the right.



**Figure 4-12. Static Angle Noise Over One Revolution**



<span id="page-19-0"></span>

Change the effective air gap to 2.3mm, measure the static angle noise at different mechanical angle, the comparison test results are shown in Table 4-8. At a larger airgap, the maximum noise RMS is 0.0038° while it's 0.0033° under 0.8mm airgap. A larger airgap can slightly increase the noise but the impact on the SNR and ENOB can be small.



**Figure 4-13. Static Angle Noise vs Airgap**

#### *4.3.3 Rotary Angle Accuracy Measurement*

In this section, the angle accuracy when the motor is running on constant speed is tested. On test platform, the servo motor drives the tested motor at 30RPM. The host controller can send position data request command at 16kHz frequency and collect the reference encoder and TIDA-010947 position data. Compare the reference encoder and TIDA-010947 data to get the rotary angle accuracy.

For help simulating magnetic systems, the *[TI Magnetic Sense Simulator](https://webench.ti.com/timss/)* (TIMSS) tool can accelerate design and evaluation of magnetics systems.

Keep the airgap at 0.8mm and collect 30000 angle samples over one revolution. The rotary accuracy is shown in [Figure 4-14.](#page-20-0) The peak to peak error is 0.28° without any offset and gain calibration. By using post-calibration to compensate 1<sup>st</sup> and 2<sup>nd</sup> harmonic, the error can be reduced to +/-0.032°, which is shown in [Figure 4-14.](#page-20-0)

<span id="page-20-0"></span>



**Figure 4-14. Uncalibrated Rotary Angle Accuracy at 0.8mm Airgap**



**Figure 4-15. Rotary Angle Accuracy with Offset Calibration at 25°C Ambient**

To do the repeatability test, continuously sample the angle data over two revolutions. After using same calibration parameter, compare the calibration results of two cycles. Figure 4-16 shows the results. Cycle1 and cycle2 data almost complete overlap, this means the good repeatability of TIDA-010947.





#### **4.3.3.1 Impact of Airgap on Noise, Harmonics, and Total Angle Accuracy**

With the airgap increasing, the magnetic field can reduce and leads to higher noise of position sensor. This section analyzes the airgap's influence on TIDA-010947. By using gasket, the airgap changes from 0.3mm to 2.3mm. Repeat the test procedure described in [Section 4.3.3](#page-19-0), the test results are shown in [Figure 4-17](#page-21-0) to [Figure](#page-21-0)  [4-20.](#page-21-0) Under all airgap, the error with calibration are lower than  $\pm 0.037^{\circ}$ .



<span id="page-21-0"></span>

**Figure 4-17. Uncalibrated Rotary Angle Accuracy with Calibration at 0.8mm Airgap**



**Figure 4-18. Rotary Angle Accuracy with Calibration at 0.8mm Airgap**



**Calibration at 1.3mm Airgap**

**Calibration at 2.3mm Airgap**

To further analyze the airgap influence on harmonics, FFT analysis is used. The results are listed on the Table 4-9. 4<sup>th</sup> harmonic is from signal chain gain mismatch, which is not influenced by airgap. 8th harmonic is caused by AMR sensor and signal chain's non linearity, higher airgap can lead to increasing value of the 8<sup>th</sup> harmonic.







#### *4.3.4 RS485 Interface and Signal Integrity*



**Figure 4-21. Timing Diagram (Tamagawa T-format) to Request New Angle Data**

Figure 4-21 shows the communication timing diagram between host controller and TIDA-010947. The communication is based on T-format protocol. The host controller sends a command request every 62.5us (32kHz), TIDA-010947 responds with the corresponding angle data within 2us. The request command takes 6us and response data takes 35us.

In Figure 4-22 shows the rise and fall time of RS485 signal, which are around 40ns. Since UART baud rate is 4M, 1bit signal can last 250ns, so the rise and fall time do not influence communication.



**Figure 4-22. RS485 Signal Rise and Fall Time**

# **5 Design and Documentation Support**

# **5.1 Design Files**

# *5.1.1 Schematics*

To download the schematics, see the design files at [TIDA-010947](http://www.ti.com/tool/TIDA-010947)

# *5.1.2 BOM*

To download the bill of materials (BOM), see the design files at [TIDA-010947](http://www.ti.com/tool/TIDA-010947)

# *5.1.3 PCB Layout*

To download the PCB layout, find the design files at [TIDA-010947](http://www.ti.com/tool/TIDA-010947)

# *5.1.4 Altium Project Files*

To download the Altium Project Files, find the design files at [TIDA-010947](http://www.ti.com/tool/TIDA-010947)

# *5.1.5 Gerber Files*

To download the Gerber Files, find the design files at [TIDA-010947](http://www.ti.com/tool/TIDA-010947)

# *5.1.6 Assembly Drawings*

To download the Assembly Drawings, find the design files at [TIDA-010947](http://www.ti.com/tool/TIDA-010947)

# **5.2 Tools and Software**

### **Tools**

[TI-MAGNETIC-SENSE-SIMULATOR](http://www.ti.com) Magnetic simulation software that includes mechanical motion and sensor output.

#### **Software**

- [MSPM0-SDK](http://www.ti.com) The MSPM0 SDK provides the ultimate collection of software, tools and documentation to accelerate the development of applications for the MSPM0 MCU platform under a single software package.
- [MSP-IQMATHLIB](https://www.ti.com/tool/MSP-IQMATHLIB?keyMatch=IQMath&tisearch=universal_search&usecase=partmatches) The Texas Instruments® MSP IQmath and Qmath Libraries are a collection of highly optimized and high-precision mathematical functions for C programmers to seamlessly port a floating-point algorithm into fixed-point code on MSPM0, MSP430 and MSP432 devices.

# **5.3 Documentation Support**

- 1. Texas Instruments, *[Calibration of AMR Angle Sensors](https://www.ti.com/lit/pdf/slya085)*, application note.
- 2. Texas Instruments, *[Achieving Highest System Angle Sensing Accuracy](https://www.ti.com/lit/pdf/sbaa539)*, application note.
- 3. Texas Instruments, *[Introduction to TI Magnetic Sense Simulator Features](https://www.ti.com/lit/pdf/slya083)*, application brief.
- 4. TAMAGAWA SEIKI, *[Rotary Encoders Catalog](https://www.tamagawa-seiki.com/assets/img/downloads/pdf/rotaryencoder/1228N61EJ.pdf)*, product catalog

# **5.4 Support Resources**

TI E2E™ [support forums](https://e2e.ti.com) are an engineer's go-to source for fast, verified answers and design help — straight from the experts. Search existing answers or ask your own question to get the quick design help you need.

Linked content is provided "AS IS" by the respective contributors. They do not constitute TI specifications and do not necessarily reflect TI's views; see TI's [Terms of Use.](https://www.ti.com/corp/docs/legal/termsofuse.shtml)

# **5.5 Trademarks**

TI E2E™ and Arm™ are trademarks of Texas Instruments. Cortex® is a registered trademark of Texas Instruments. All trademarks are the property of their respective owners.



# **6 About the Authors**

**YUFENG ZHANG** is a system engineer in the Industrial Systems Motor Drive team at Texas Instruments, where he is responsible for specifying and developing system designs for industrial drives.

**MARTIN STAEBLER** is Senior Member Technical Staff in the Industrial Systems Motor Drive team at Texas Instruments, where he is responsible for specifying and developing system designs for industrial drives.

# **IMPORTANT NOTICE AND DISCLAIMER**

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](https://www.ti.com/legal/terms-conditions/terms-of-sale.html) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2024, Texas Instruments Incorporated