

# TLC6C5912 Flexible LED Driving Solution

## LED driving topology II

**Chen Jian, Zhang**

MSA/AVL/Marketing

[chenjian.zhang@ti.com](mailto:chenjian.zhang@ti.com)

# TLC6C5912-Q1: Flexible Simple LED Driver

## Features



- Load VCC up to 40V
- Logic supply VCC ranges from 3V to 5.5V
- PW package Current capability:
  - 12ch x 50mA
  - 8 ch x 110mA
  - 1 ch x 280mA
- DW package Current capability:
  - 12ch x 60mA
  - 8 ch x 130mA
  - 1 ch x 320mA
- Daisy chain I/F:
  - support cascade
  - 3 or 4 MCU GPIO requirement
- Output channel number:
  - 12ch for TLC6C5912
  - 8 ch for TLC6C598
- Low side MOSFET structure supports parallel connection
- Package: PW, D

## Applications

- Appliance display panel
- Industry machine LED indication panel
- Consumer product LED indication panel

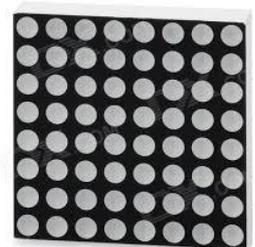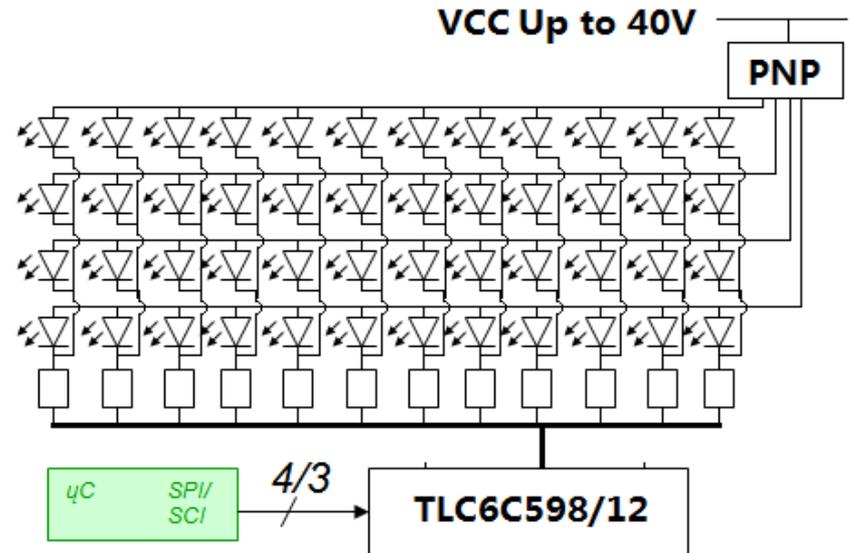
## Benefit

- Saving GPIO , PCB space,
- Simplify design
- Direct support 12V or 5V system


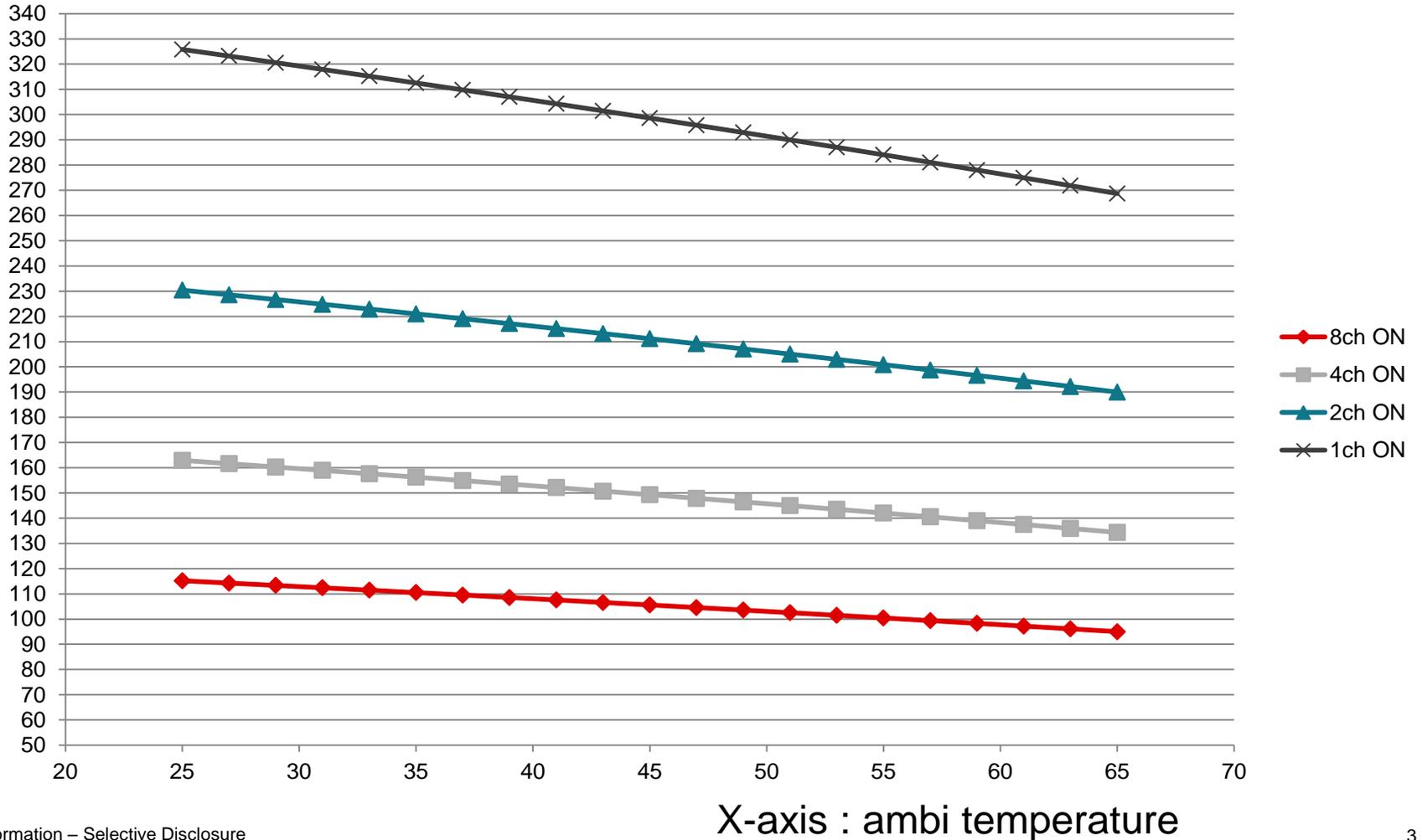
# TLC6C5912 Current Capability

Package : DW ;  $V_{CC} = 5V$  ; Output 100% duty cycle



# Detail Implementation of TLC6C5912 LED driving topology

## 1. Work with 5V I/O MCU for normal current LED load

- Resource:  $(3+N) \times$  GPIO
- LED number:  $N \times 12$

## 2. Work with 5V I/O MCU for high current LED in 5V system

- Resource:  $(3+N) \times$  GPIO ,  $N \times$  PNP
- LED number:  $N \times 12$

## 3. Drive multiple LED with only 3 GPIOs for 5V system

- Resource:  $3 \times$  GPIO,  $N \times$  74LS595
- LED number:  $N \times 96$


## 4. Drive <36 LED from 12V / 24V supply

- Resource:  $3 \times$  GPIO,  $N \times$  PNP
- LED number:  $(N \times (12-N))$  (max. is 36 when  $N=6$ )

## 5. Drive multiple LED from 12V /24V supply

- Resource:  $(3+N) \times$  GPIO,  $N \times$  NPN ,  $N \times$  PNP
- LED number:  $N \times 12$
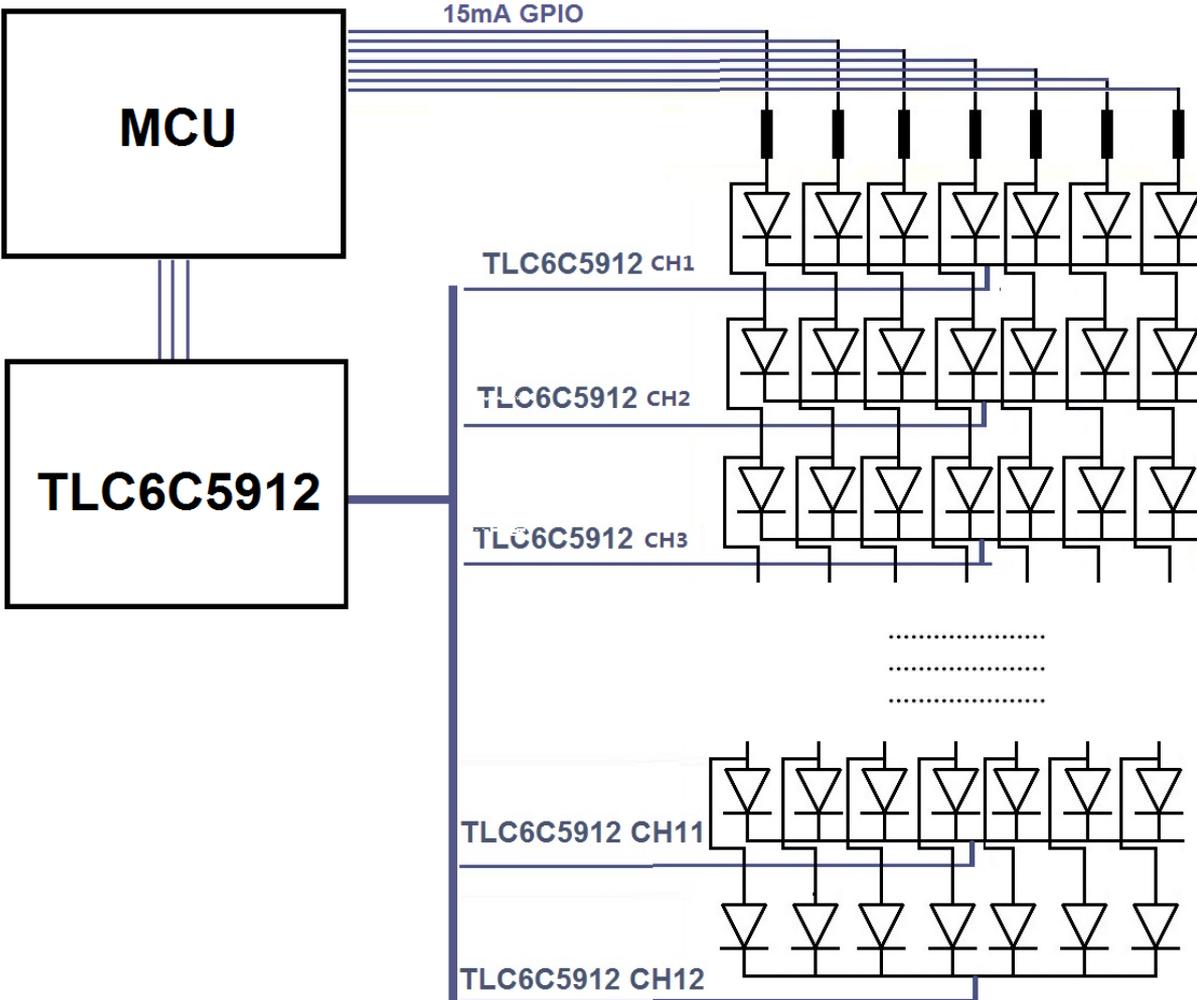
# 2.1 Work with 5V I/O MCU for normal current LED load



## 2.1 Work with 5V I/O MCU for normal current LED load

### Resource Requirement:

( N +3 ) x GPIO , 1 x TLC6C5912

**LED Load Number:** N x 12

### Detail Characters


1. MCU I/O provide LED column current, equal to single LED current. Normally 10~20mA.
2. TLC6C5912 provide common sink current for each row. The current requirement is N x (10~20)mA. Only one channel is ON and rest channels keep in Hi-Z mode, thus the ON channel can provide larger current capability.

### Benefit:

1. Save I/O and PCB
2. Easy load expansion:
  1. 1 GPIO for additional 12LED.
  2. Serial chain connect TLC6C598 for additional 8 rows

MCU GPIO	4	5	6	7	8	9	10
LED number	12	24	36	48	60	72	84
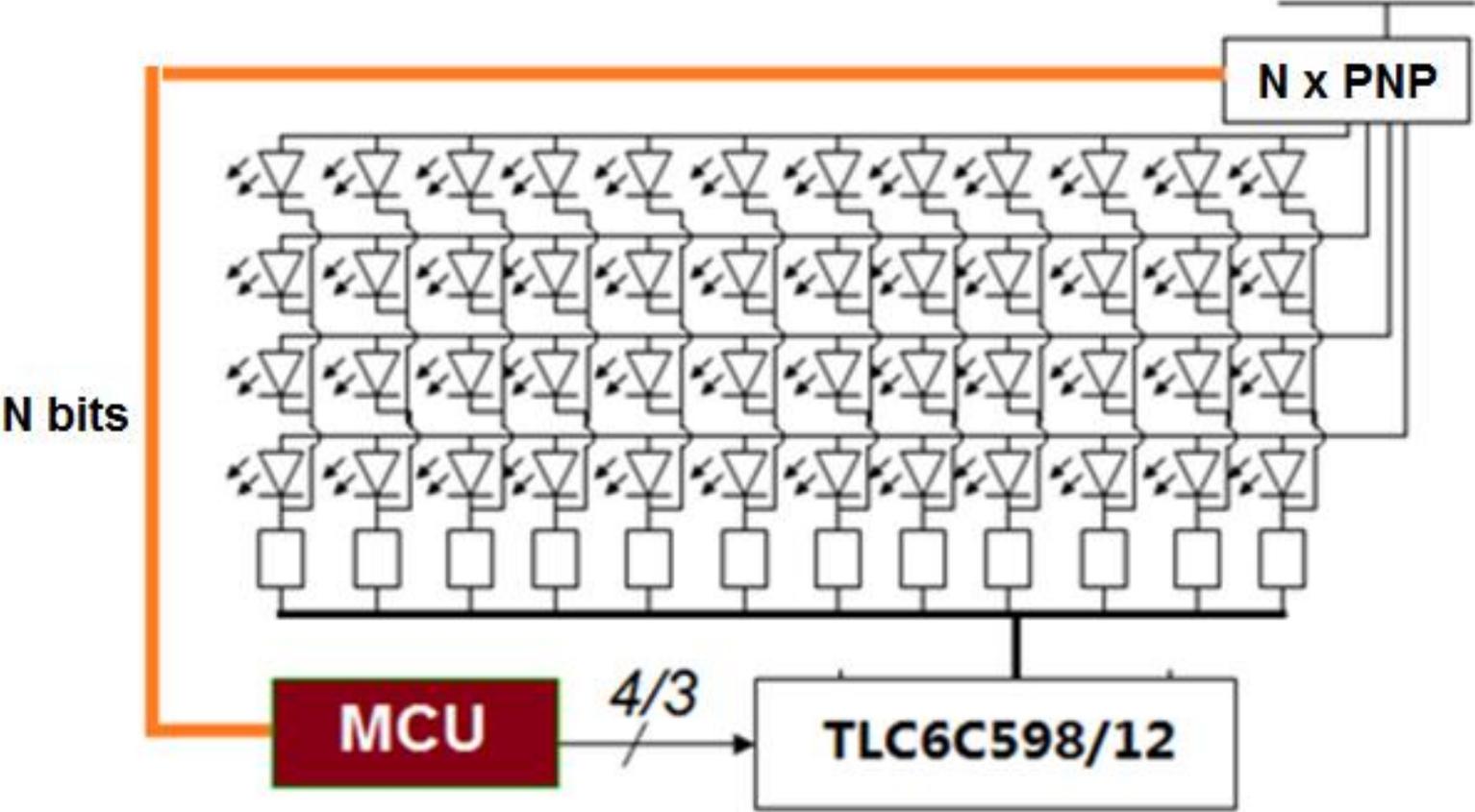
# 2.2 Work with 5V I/O MCU for HIGH current LED in 5V system



## 2.2 Work with 5V I/O MCU for HIGH current LED in 5V system

### Resource Requirement:

( N +3 ) x GPIO , 1 x TLC6C5912 , N x PNP bjt

**LED Load Number:** N x 12


### Detail Characters

1. TLC6C5912 provides LED column current, equal to single LED current. Current can be up to 12ch x 50mA. It can drive high current LED or drive two LED parallel for greater brightness. If output is controlled in time-sharing fashion, it can provide higher current capability.
2. MCU I/O drive PNP for common row current sourcing. Any moment, only one PNP is ON.

### Benefit:


1. Save I/O and PCB
2. Easy load expansion:
  1. 1 GPIO for additional 12LED.
  2. Serial chain connect TLC6C598 for additional 8 rows
3. Provide high current capability for brighter LED effect.

Better Brightness

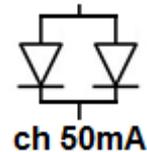

MCU GPIO	4	5	6	7	8	9	10
PNP Bjt	1	2	3	4	5	6	7
LED number	12	24	36	48	60	72	84
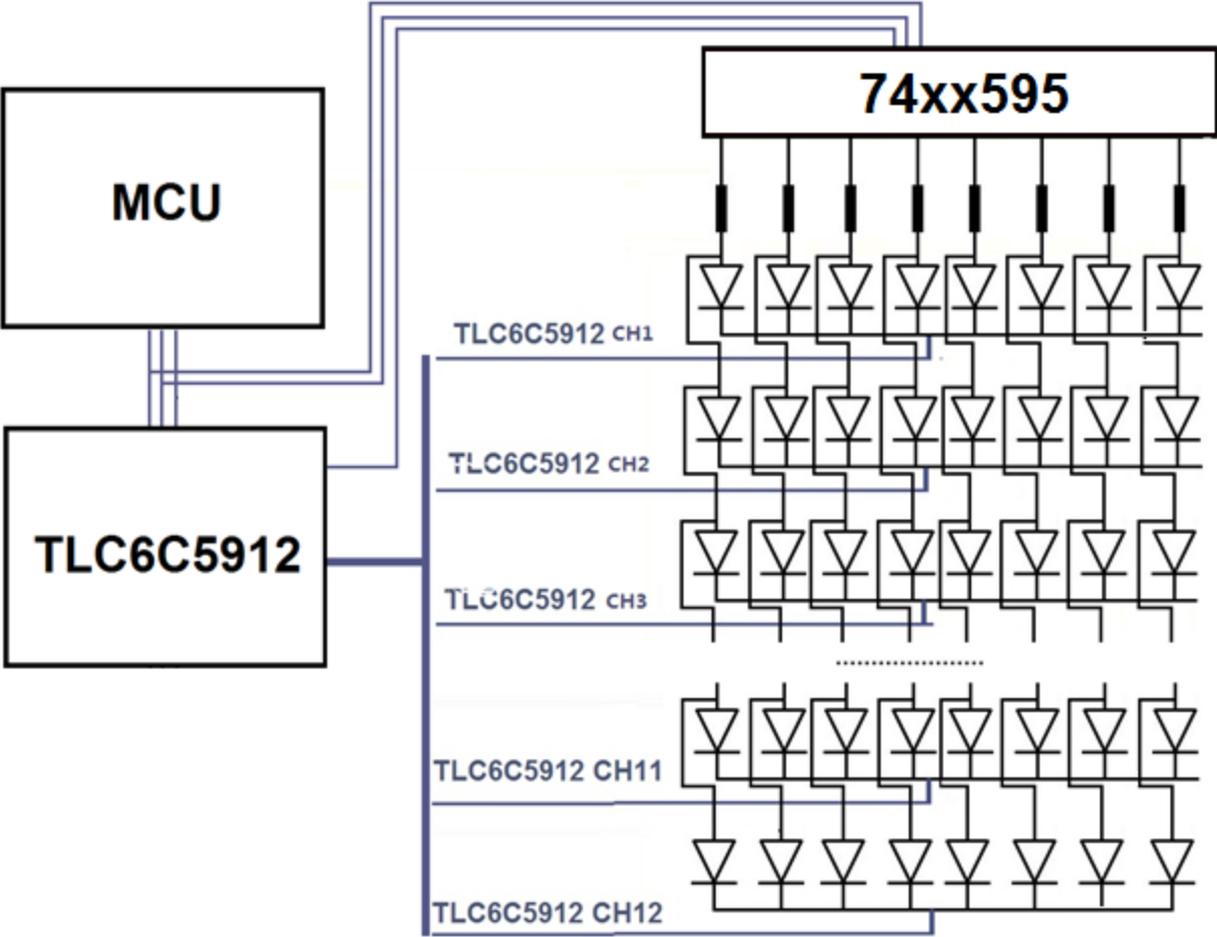
# 2.3 Drive multiple LED with ONLY 3 GPIOs for 5V system



## 2.3 Drive multiple LED with ONLY 3 GPIOs for 5V system

### Resource Requirement:

3 x GPIO , 1 x TLC6C5912, 1 x 74xx595

**LED Load Number:** N x 12

### Detail Characters

1. MCU drive TLC6C5912 and 595 through 3bit GPIO.
2. 74xx595 provides LED column current, equal to single LED current. Normally 10~20mA.
3. TLC6C5912 provides common sink current for each row. The current requirement is N x (10~20)mA. Only one channel is ON and rest channels keeps in Hi-Z mode, thus the ON channel can provide larger current capability.

### Benefit:

1. Save I/O and PCB
2. Easy load expansion:
  1. Add one 74xx595 for additional 8 columns
  2. Serial chain connect TLC6C598 for additional 8 rows

MCU GPIO	3	3	3
74xx595 number	1	2	3
LED number	96	192	288



## 2.1 Drive <36 LEDs from 12V / 24V supply

### Resource Requirement:

3 x GPIO , 1 x TLC6C5912 , N x PNP bjt

**LED Load Number:**  $N \times (12 - N)$

### Detail Characters

1. TLC6C5912 provides LED column current, equal to single LED current. Current can be up to 50mA. It can drive high current LED or drive two LED parallel for greater brightness. If output is controlled in time-sharing fashion, it can provide higher current capability.
2. N channels of TLC6C5912 outputs drive PNP BJT for common rows current sourcing

### Benefit:

1. Save I/O and PCB
2. Provide high current capability for brighter LED effect.
3. PWM chopping for LED dimming control.
4. Compare against 5V system, 12V system can save energy by PWM chopping . No energy waste on LDO.
5. Support multiple LED cascade. System can serial connects 2~4 LEDs for better brightness.


MCU GPIO	3	3	3	3	3	3
PNP number	1	2	3	4	5	6
LED number	11	20	27	32	35	36

12 V support LED cascade connection.


LED Vf (V)	2	2.5	3	
LED cascade #	5	4	3	

2 ways for Better Brightness

12V

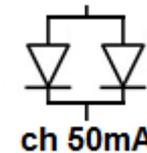


Better Energy by PWM

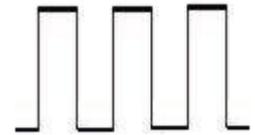

12
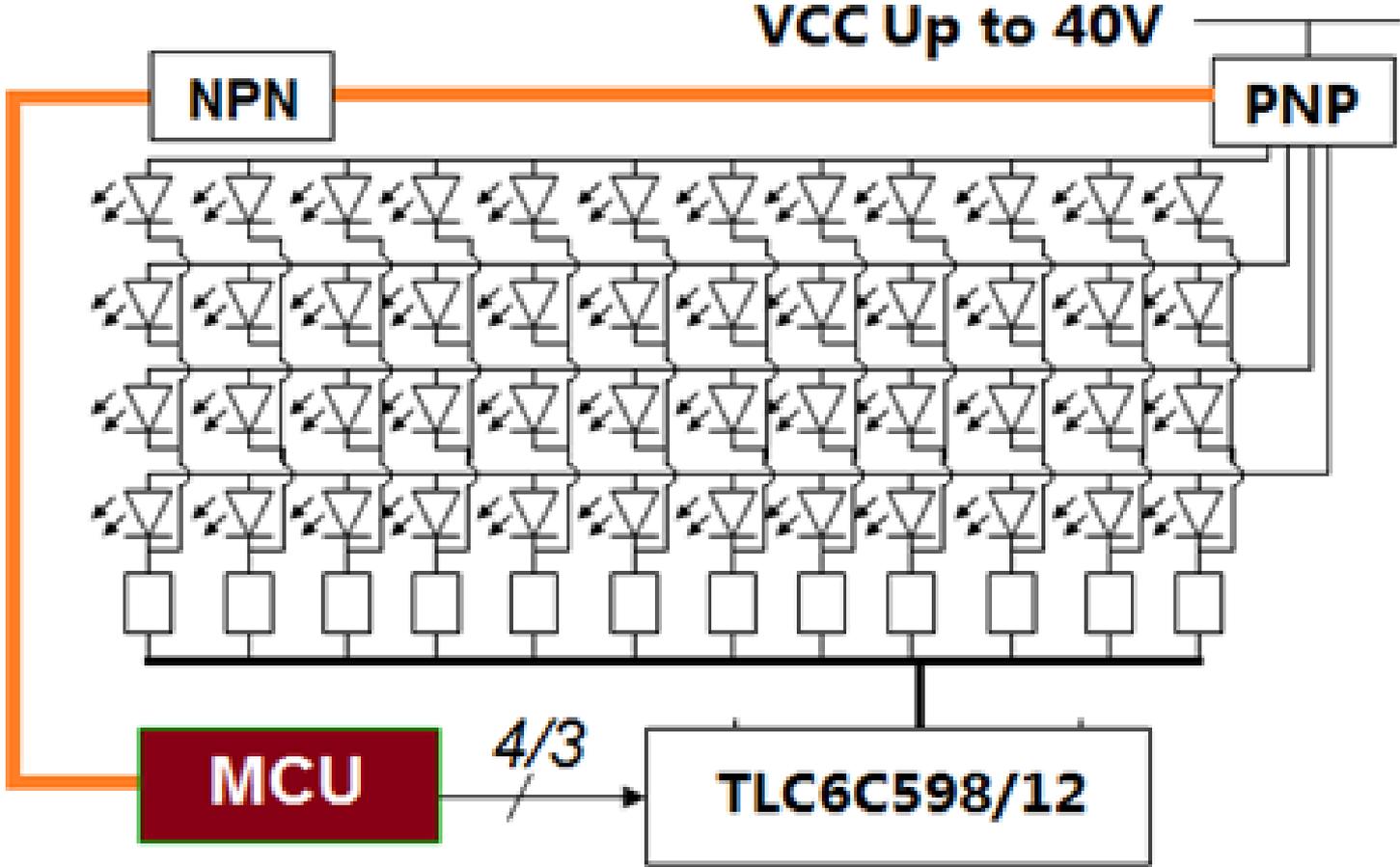
# 2.1 Drive multiple LED from 12V / 24V supply



## 2.1 Drive multiple LED from 12V / 24V supply

### Resource Requirement:

3 x GPIO , 1 x TLC6C5912 , N x PNP bjt, N x NPN bjt

**LED Load Number:** N x 12

### Detail Characters

1. TLC6C5912 provides LED column current, equal to single LED current. Current can be up to 50mA. It can drive high current LED or drive two LED parallel for greater brightness. If output is controlled in time-sharing fashion, it can provide higher current capability.
2. MCU drive NPN BTJ to control PNP BJT for common rows current sourcing.

### Benefit:

1. Save I/O and PCB
2. Provide high current capability for brighter LED effect.
3. PWM chopping for LED dimming control.
4. Compare against 5V system, 12V system can save energy by PWM chopping . No energy waste on LDO.
5. Support multiple LED cascade. System can serial connects 2~4 LEDs for better brightness.


MCU GPIO	4	5	6	7	8	9	10
NPN number	1	2	3	4	5	6	7
PNP number	1	2	3	4	5	6	7
LED number	12	24	36	48	60	72	84

12 V support LED cascade connection.

LED Vf (V)	2	2.5	3
LED cascade #	5	4	3


### 2 ways for Better Brightness

12V

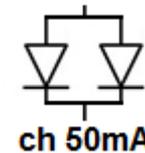

ch 50mA

### Better Energy by PWM

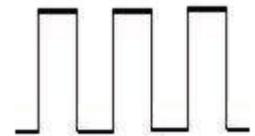

14

# Thank You

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)