

# Designing a Power Supply Solution for Pipeline ADCs – Part 1




Xavier Ramus

In my [previous posts](#), I've discussed designing a real-world power supply. Now, let's use what we know about the analog-to-digital converter (ADC) power-supply rejection (PSR) and signal-to-noise ratio (SNR), coupled with the DC/DC converter frequency content we need to suppress, to find the best possible power-supply solution. "Best" not only implies performance, but also includes printed circuit board (PCB) area and solution cost.

In my "Using a DC/DC converter to power an ADC" post, I evaluated the impact of a minimally loaded medium-current DC/DC converter. While this approach cannot be implemented cost effectively and occupies a lot of precious PCB area, it did demonstrate the minimum impact a DC/DC converter will have in the system. But how would the system react if a 3A DC/DC converter were shared between the ADC and an additional 2A load? Building on my previous posts, I'll use the quad 14-bit, 125MSPS [ADC3444](#) and the dual-output [TPS54120](#) DC/DC with a low-dropout regulator (LDO), leaving the LDO disabled for now and using the TPS54120 DC/DC converter by itself.


Let's first establish a baseline for a loaded TPS54120 DC/DC converter. [Figure 1](#) shows the fast Fourier transform (FFT) of the time-domain response represented as an amplitude in decibel milliwatt on the y-axis versus frequency on the x-axis.

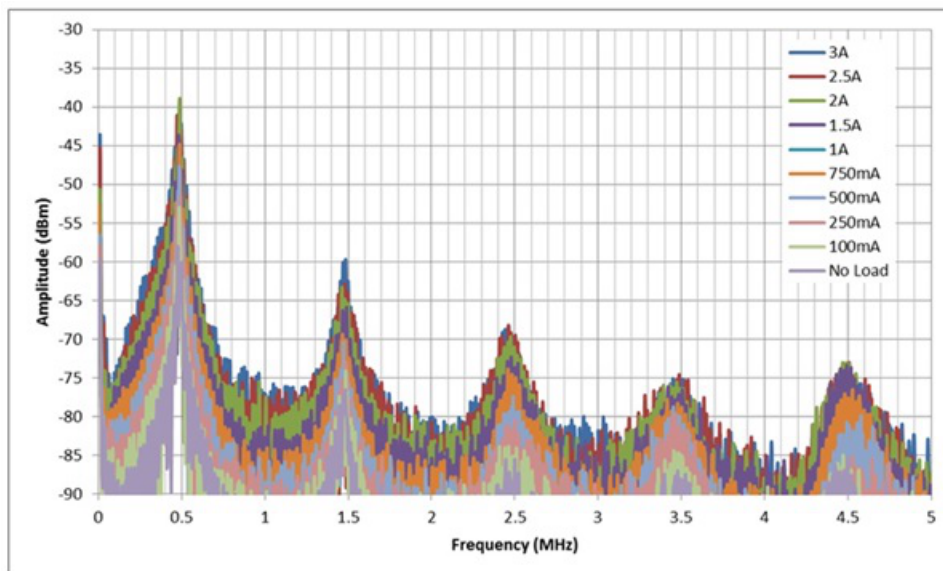

**Figure 1. TPS54120 DC/DC Converter Frequency Content versus Load**

The amplitude of the switching frequency is increasing in conjunction with the increased load. For example, going from no load to a 2A load, the 500kHz switching frequency power increases from -58dBm to -38dBm. The power present in the harmonics also rises. In the time domain, this will appear as an increase in peak-to-peak voltage.


Using the TPS54120 DC/DC converter at 1.8V followed by a  $\pi$ -filter into DVDD (while powering the AVDD with a [TPS7A47](#) LDO voltage regulator), I compared the results to the reference FFT. The reference FFT is battery-powered, with one TPS7A47 regulator for each AVDD and DVDD, for two reasons: no additional load on the DC/DC converter and a 2A external load. See [Figure 2](#).

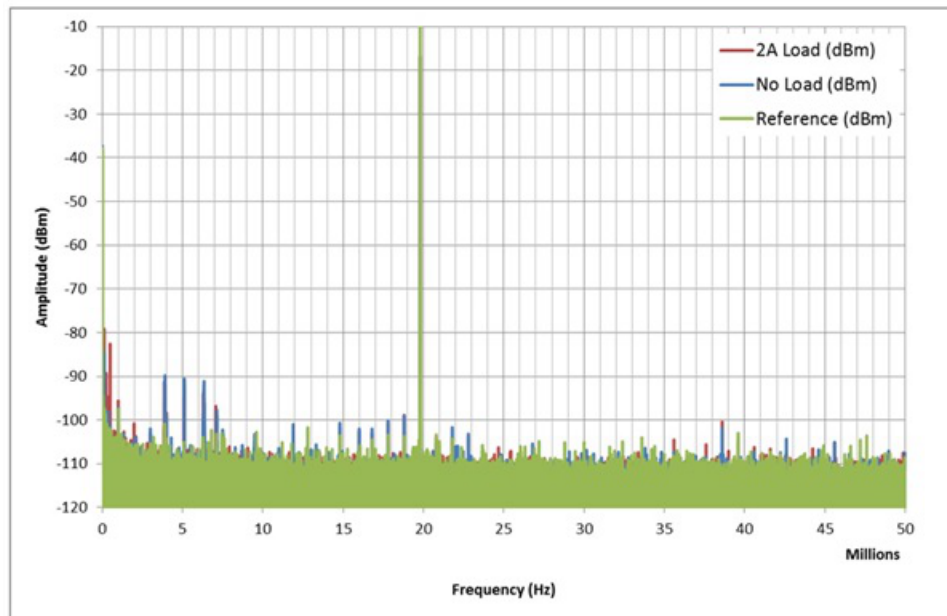

**Figure 2. TPS54120 DC/DC with Ferrite on DVDD Comparison**

As expected, the main degradation is at the switching frequency. The surprise is the 10dB degradation in the 4MHz to 8MHz band and the 5dB degradation around the 19.8MHz tone. This degradation – due to a poorer DVDD supply – has little dependency with the DC/DC converter load current.


Despite the high PSR of the ADS3444 on its DVDD supply, do not use a DC/DC converter here. Remember that the PSR measurement used a single sinewave with good phase noise, while the DC/DC converter has neither good phase noise nor good distortion. [Figure 1](#) shows that the harmonic distortion terms of the DC/DC converter switching frequency are -20dBc for HD2, -30dBc for HD3, and -35dBc for HD4 and HD5. The combination of the switcher's poor phase noise and the presence of harmonics on the switching frequency explains the new spurs appearing in the FFT, see [Figure 3](#). These additional spurs are present despite a 32kHz low-pass filter set by the ferrite bead and the ADS3444's local bypass capacitors.

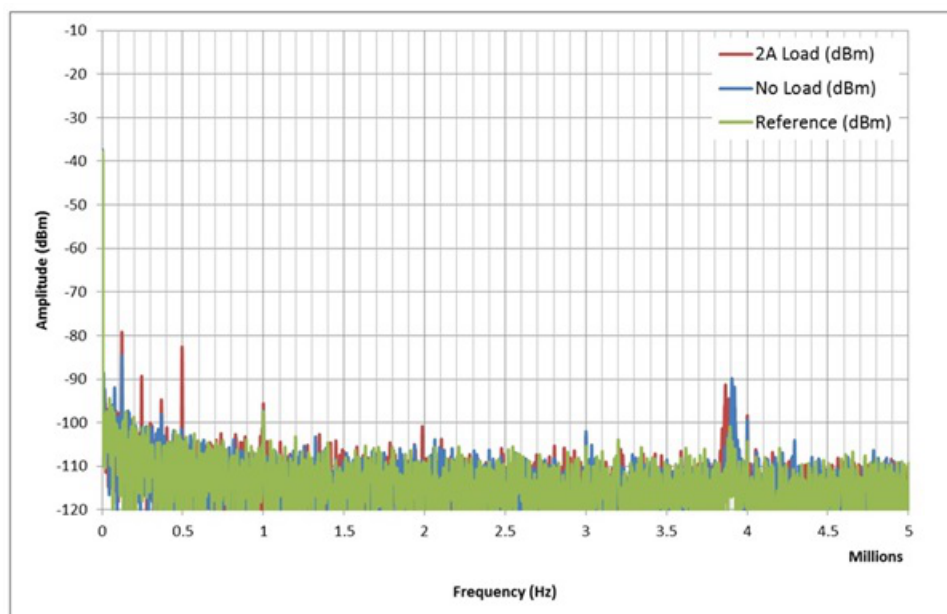

**Figure 3. DVDD with Ferrite on DVDD Comparison Details**

Looking at the DC - 5MHz band, [Figure 3](#), you can see that the PSR explanation I gave in my “[Using a DC/DC converter to power an ADC](#)” post was accurate. In that frequency band, the 2A load does bring higher spurs at the DC/DC switching frequency, in agreement with [Figure 1](#).

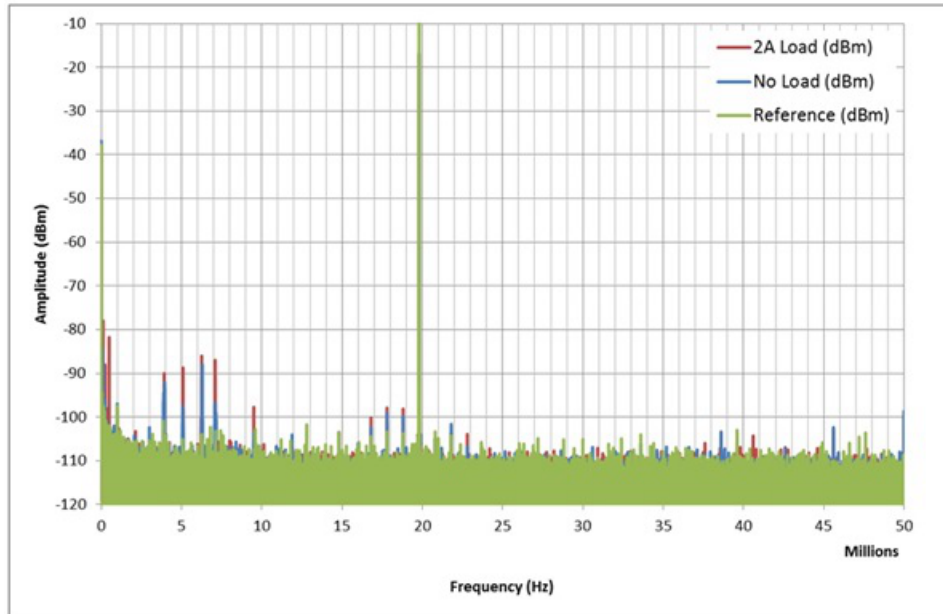
[Figure 4](#) shows the AVDD supply comparison.



The impact of the DC/DC converter with a simple  $\pi$ -filter on its output on the AVDD supply has some similarities to the DVDD supply, with spurs present at DC, the 4MHz to 8MHz band and around the signal tone.


Because the AVDD supply is more sensitive than the DVDD supply, the degradation occurring is not only more severe than with the DVDD, but also more severe as the load current on the DC/DC converter increases. The frequency band impacted is also more widespread, with noise tones appearing around 10MHz and 46MHz.

Filtering the undesirable noise tones generated by the DC/DC power supply is possible, but would require multiple  $\pi$ -filters on each supply, costing precious PCB area around the ADC.

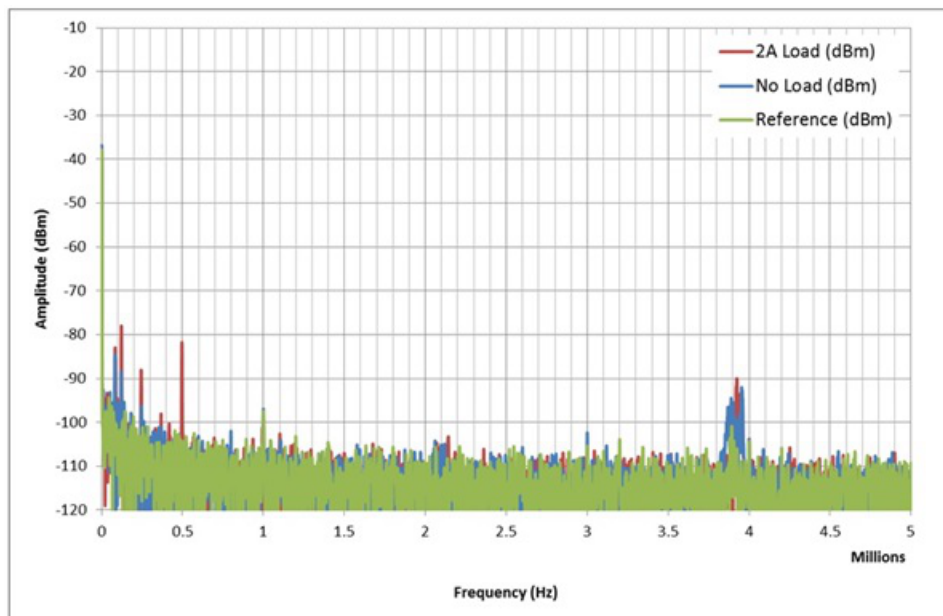

**Figure 4. TPS54120 DC/DC with Ferrite on AVDD Comparison DC to 5MHz Frequency Band Detail**

Figure 4 shows the detail of the DC to 5MHz frequency band. The  $\pi$ -filter does a good job at attenuating both the thermal and ripple noise. However, this solution falls apart with increased load current. As a reminder, the reference FFT signal uses a battery with low-noise, high-PSRR LDOs (TPS7A47) for the AVDD and DVDD supplies.

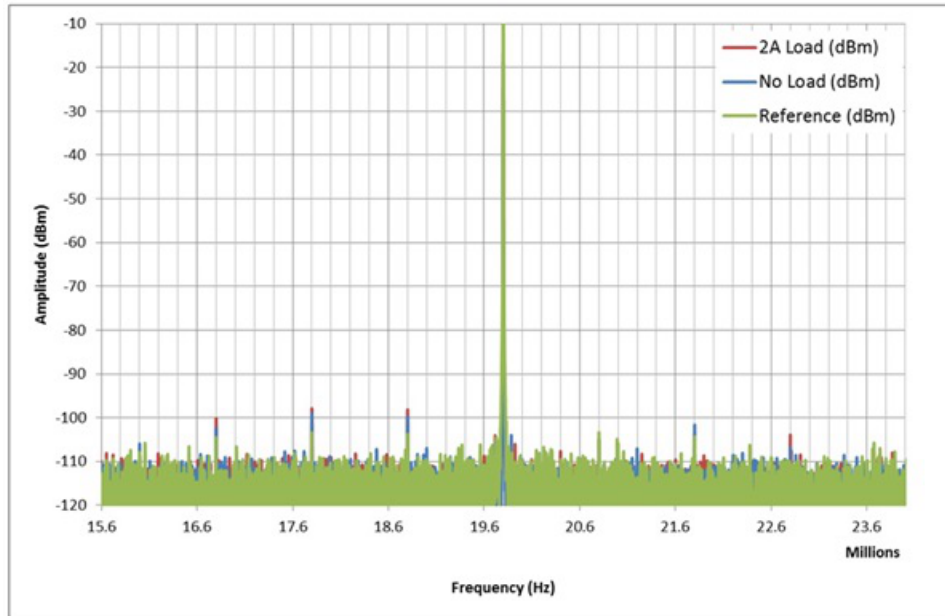

**Figure 5. TPS54120 DC/DC with Ferrite on AVDD Comparison, 15.6MHz to 23.8MHz Frequency Band Detail**

Figure 5 shows the detail taken around the signal tone. Looking closely at the plot, each spur does not originate in the power supply, as they are all present in the reference measurement and do not correspond to the switching frequency of the DC/DC converter (~500kHz). Note that the poor phase noise and harmonic distortion of the DC/DC converter interacts with the ADC spurs.

No noise tones are present at ~500kHz around the 19.8MHz signal tone, indicating that the combination of  $\pi$ -filter and lower input signal (-17dBFS) is sufficient.

As I've shown in the first part of this series, using a DC/DC converter to power a high-performance pipeline converter will significantly degrade both SNR and spurious-free dynamic range (SFDR). In [part 2](#), I will demonstrate [proper post-filtering implementation of the DC/DC converter](#) and compare the results to an ideal power supply.

In case you missed any other posts in this series, read my other blogs on [creating a power supply for ADCs](#).

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2023, Texas Instruments Incorporated