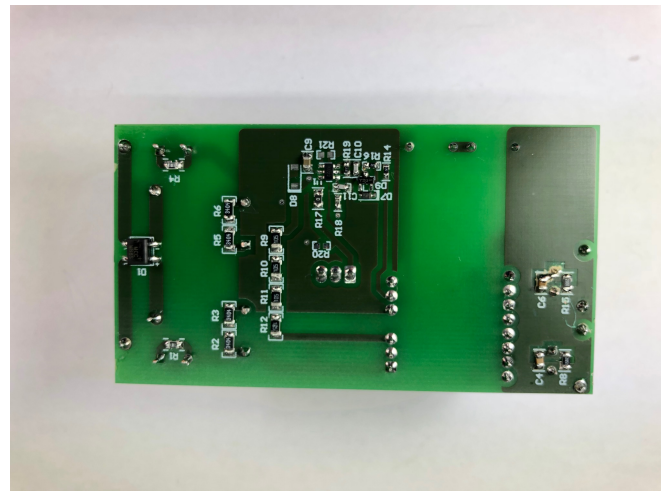


Test Report: PMP30281 85-VAC - 480-VAC Input, Multiple Output Flyback Reference Design



Description

This low cost reference design (PMP30281) generates two isolated outputs (5V@0.4A; 24V@0.3A) from a wide input voltage range (85VAC - 480VAC). The primary side regulated controller UCC28722 drives a cost-efficient bipolar transistor and provides valley-switching operation for highest overall efficiency.



An IMPORTANT NOTICE at the end of this TI reference design addresses authorized use, intellectual property matters and other important disclaimers and information.

1 Test Prerequisites

1.1 Voltage and Current Requirements


Table 1. Voltage and Current Requirements

PARAMETER	SPECIFICATIONS
V_{IN}	85VAC - 440VAC (480VAC peak)
V_{OUT}	5V@0.4A; 24V@0.3A
Nominal switching frequency	30kHz

2 Testing and Results

2.1 Efficiency Graphs

Figure 1. Efficiency for 230VAC input

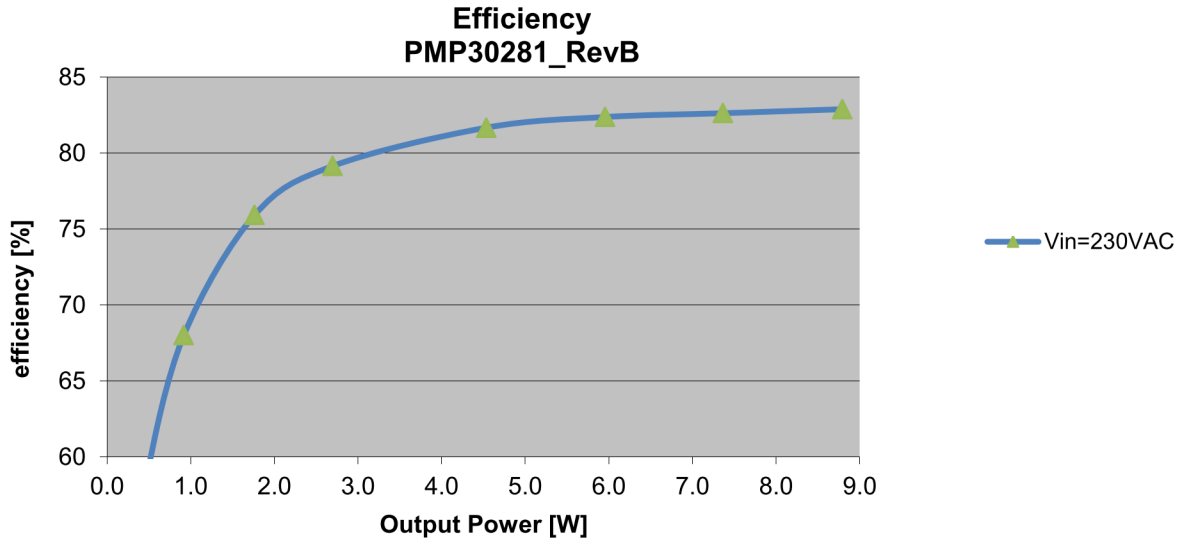


2.2 Load Regulation

Figure 2. Load Regulation Tabelle

INPUT		OUTPUT						
voltage [VAC]	power [W]	5Vout [V]	I_5Vout [A]	24Vout [V]	I_24Vout [A]	power [W]	[%]	
230.0	0.720	5.159	0.005	23.890	0.015	0.384	53.4	
230.0	0.810	5.032	0.016	23.920	0.017	0.476	58.7	
230.0	1.350	5.025	0.026	23.820	0.033	0.918	68.0	
230.0	2.324	5.020	0.050	23.820	0.064	1.764	75.9	
230.0	3.410	4.999	0.085	23.870	0.095	2.699	79.1	
230.0	5.554	4.983	0.145	23.920	0.159	4.536	81.7	
230.0	7.232	4.975	0.204	24.010	0.206	5.957	82.4	
230.0	8.916	4.977	0.253	24.050	0.254	7.366	82.6	
230.0	10.610	4.985	0.302	24.090	0.303	8.794	82.9	

2.3 Thermal Images

Figure 3. The images below show the infrared images taken from the FlexCam after 15min at full load output power and 230VAC input.

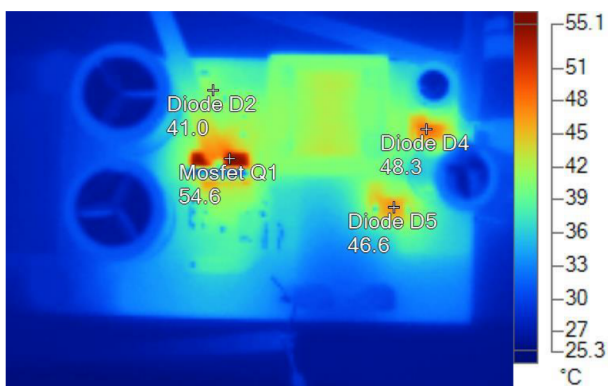

Vin=230VAC full load TOP 1226.is2

Name	Temperature
Mosfet Q1	54.6°C
Diode D2	41.0°C
Diode D5	46.6°C
Diode D4	48.3°C


2.4 Dimensions

84mm x 46mm

3 Waveforms

3.1 Switching*

Figure 4. Primary Switchnode

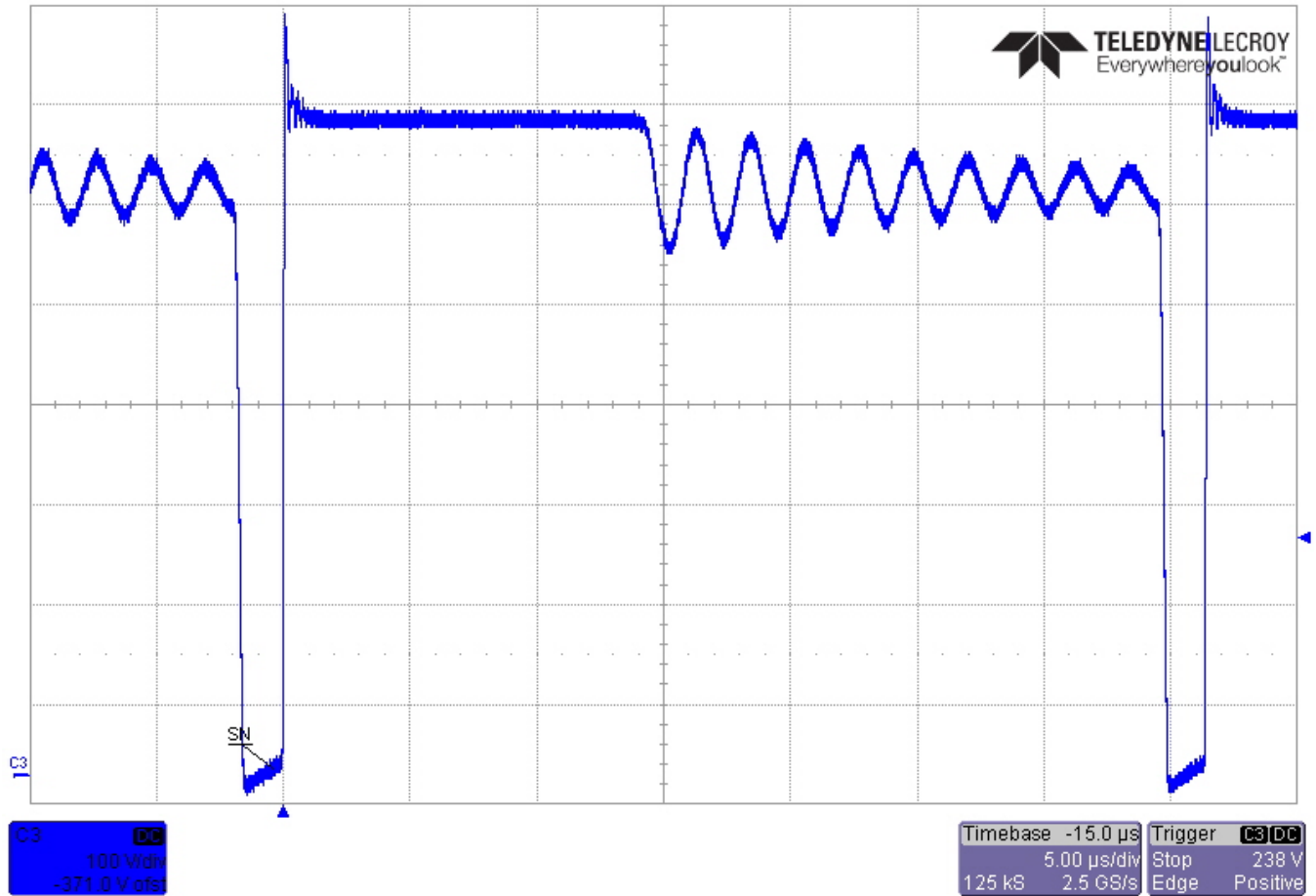


Input Voltage = 630VDC

Output Power = 9.2W (full load)

3.2 Output Voltage Ripple*


Figure 5. 5V Output Ripple

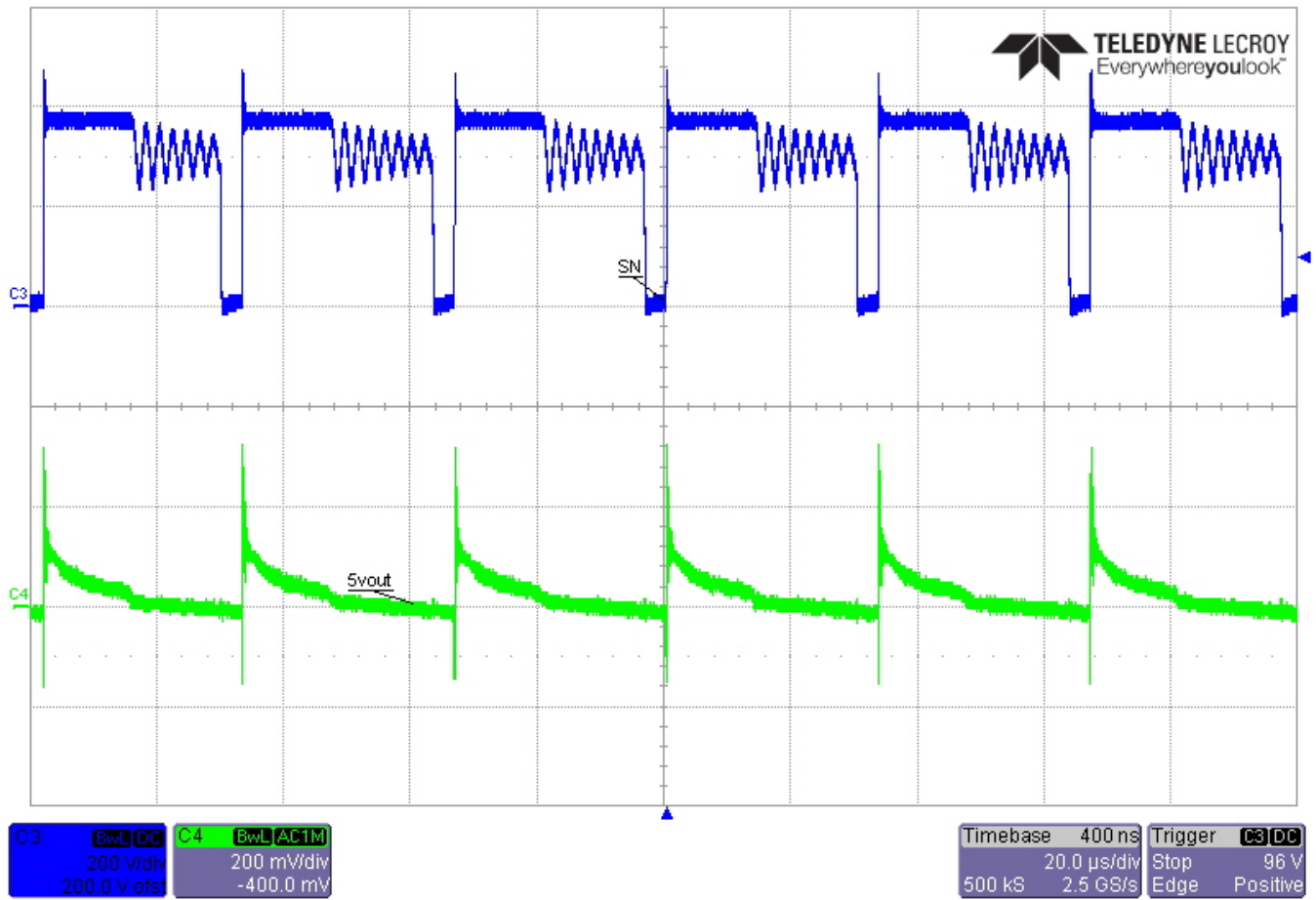

Input Voltage = 230VAC

Output Power = 9.2W (full load)


Figure 6. 24V Output Ripple

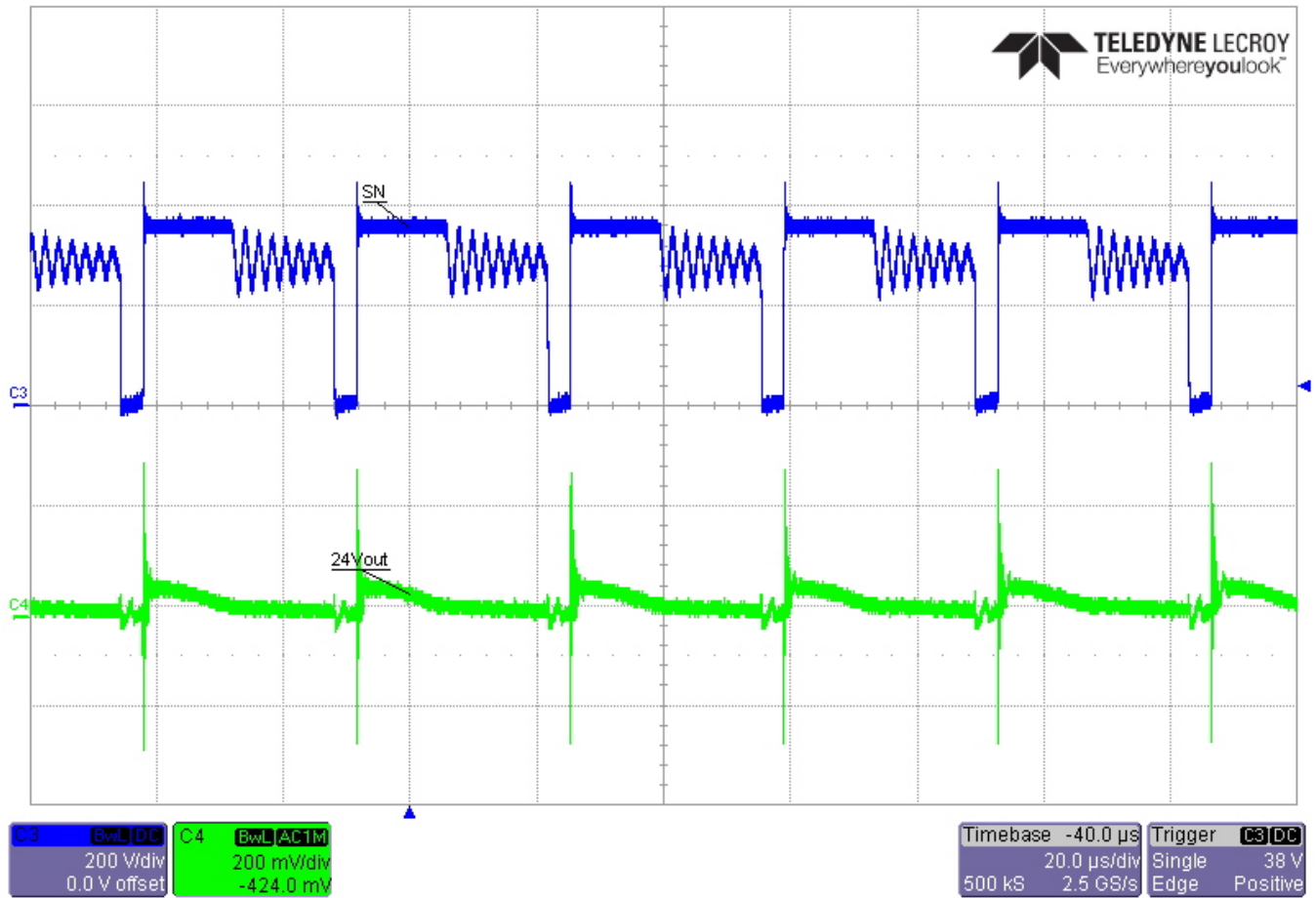

Input Voltage = 230VAC
Output Power = 9.2W (full load)

3.3 Load Transients*

Figure 7. 5Vout Load Transient

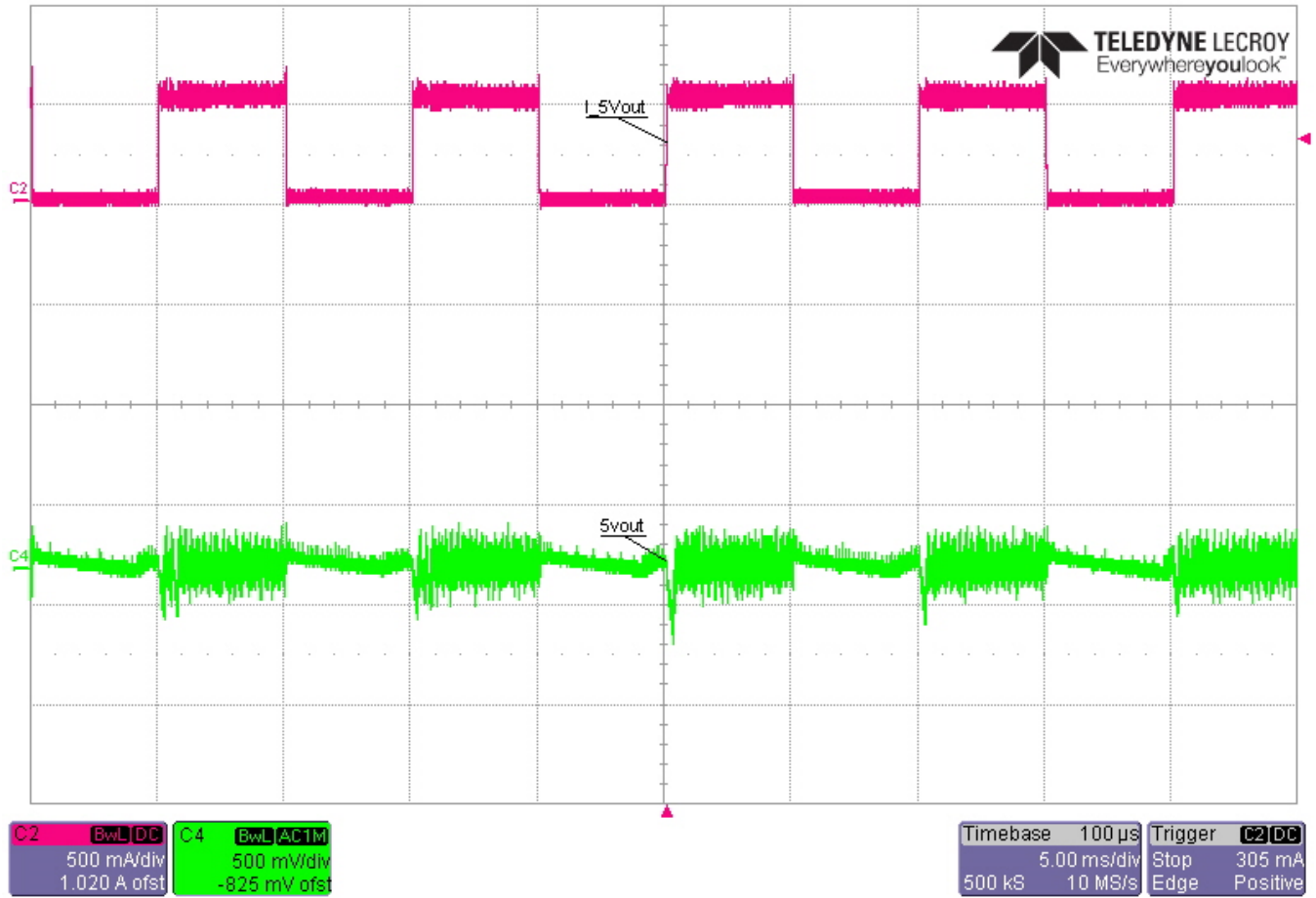


Input voltage = 230VAC

24Vout Load current = 0.05A

5Vout Load current = 0A to 0.4A


Figure 8. 24Vout Load Transient

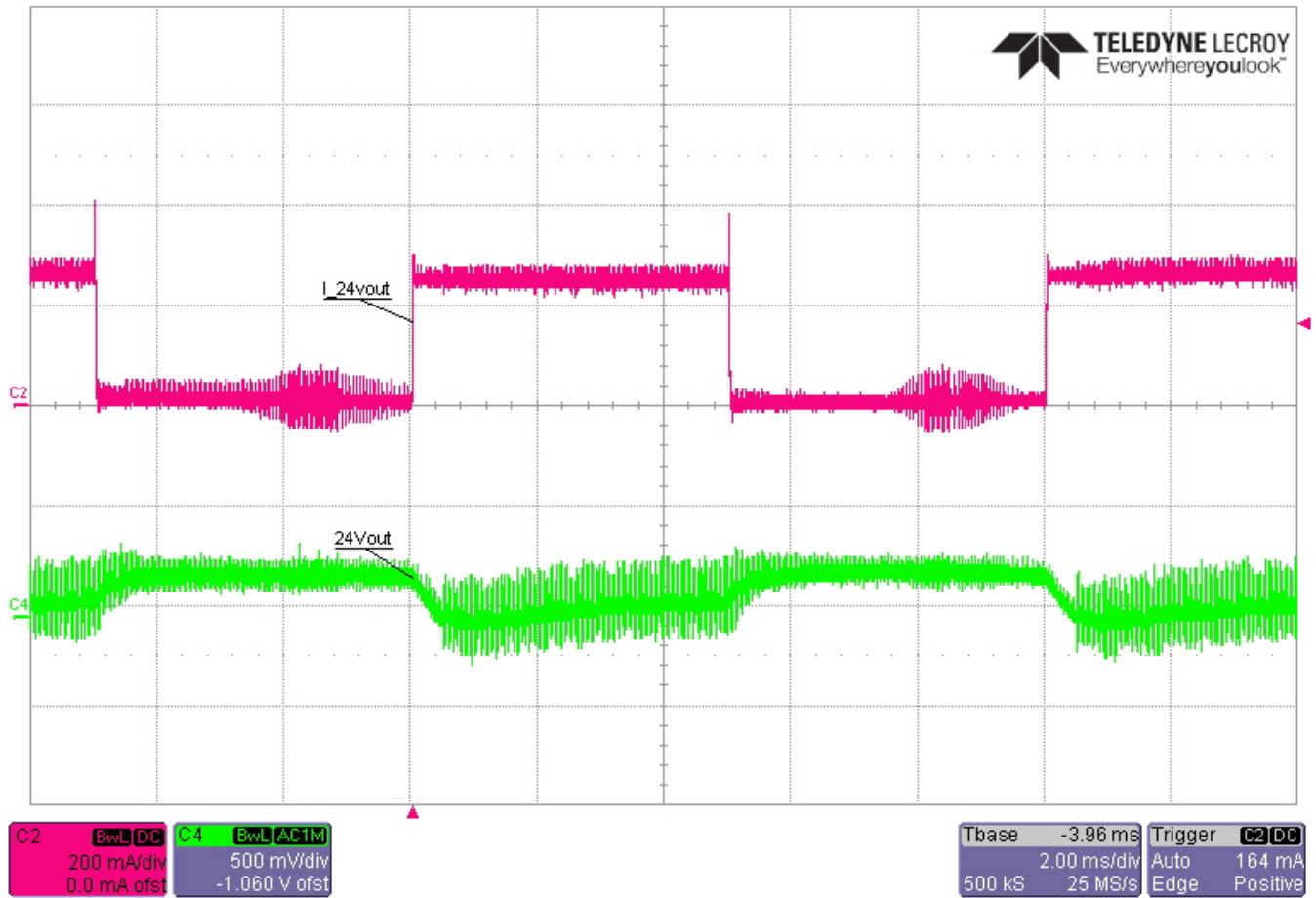

Input voltage = 230VAC
 5Vout Load current = 0A
 24Vout Load current = 0A to 0.3A

3.4 Start-up Sequence


Figure 9. Startup

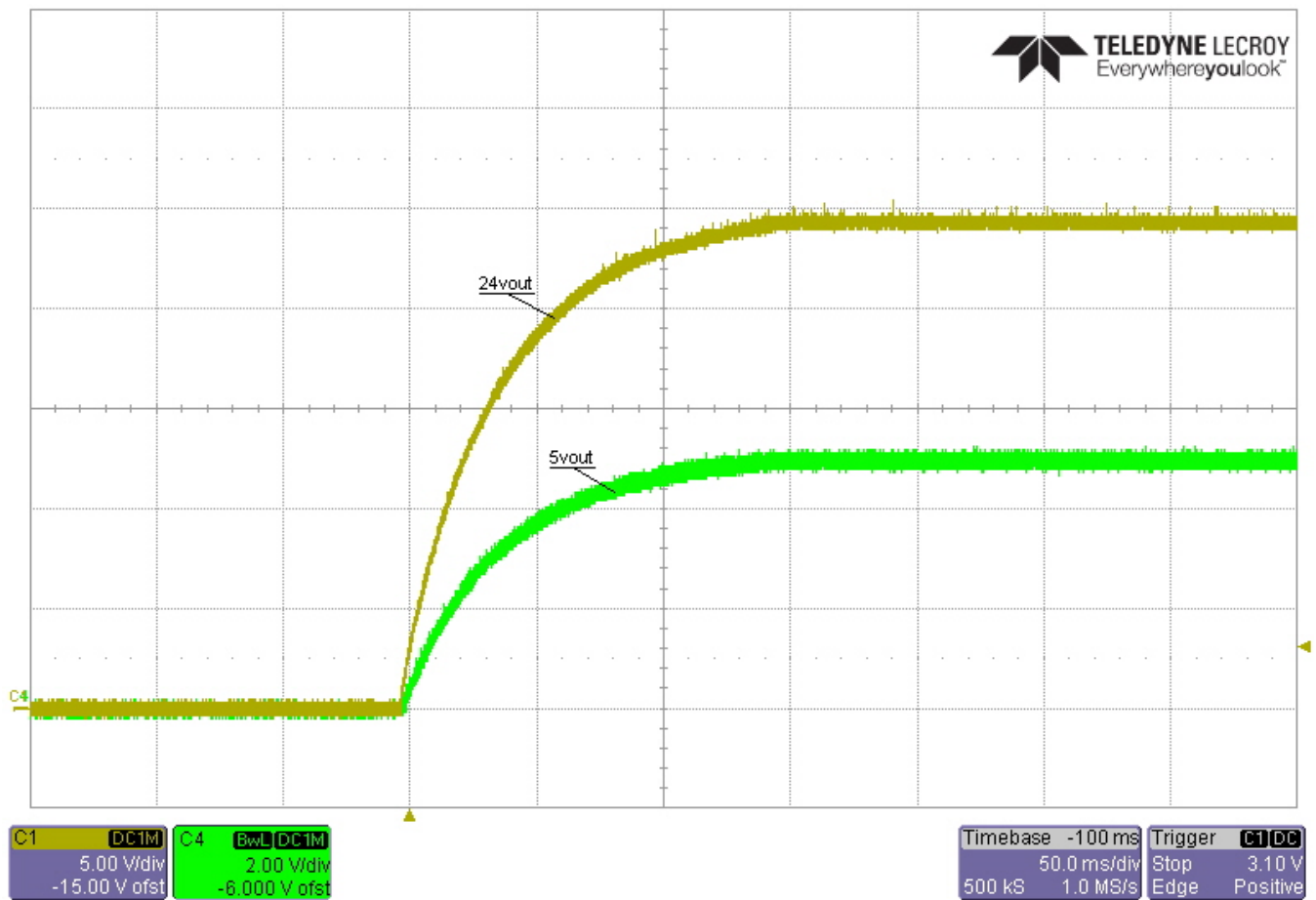

Input voltage = 85VAC


Output Power = 9.2W (full load)

Figure 10. Startup

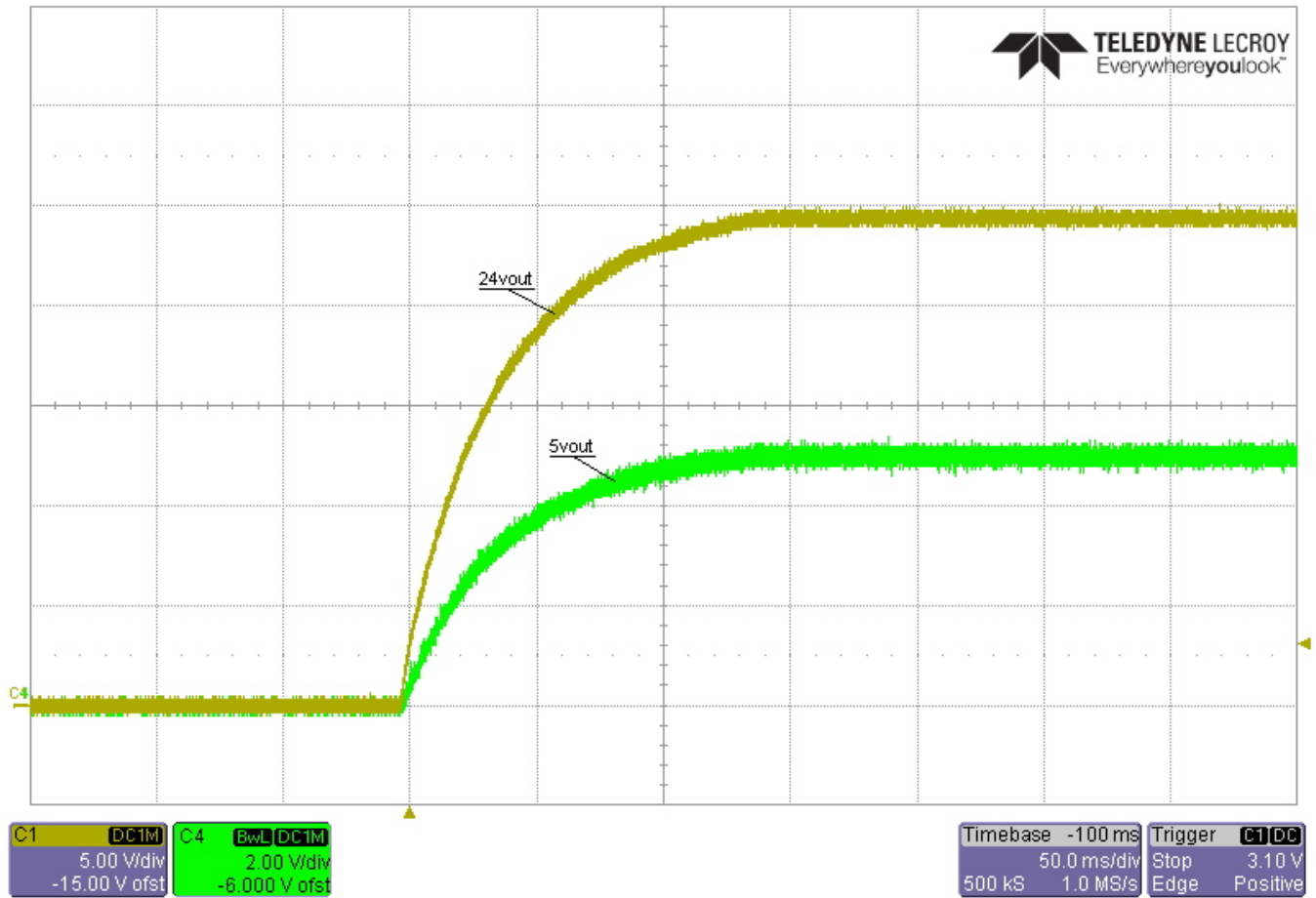


Input voltage = 272VAC
Output Power = 9.2W (full load)

Figure 11. Startup

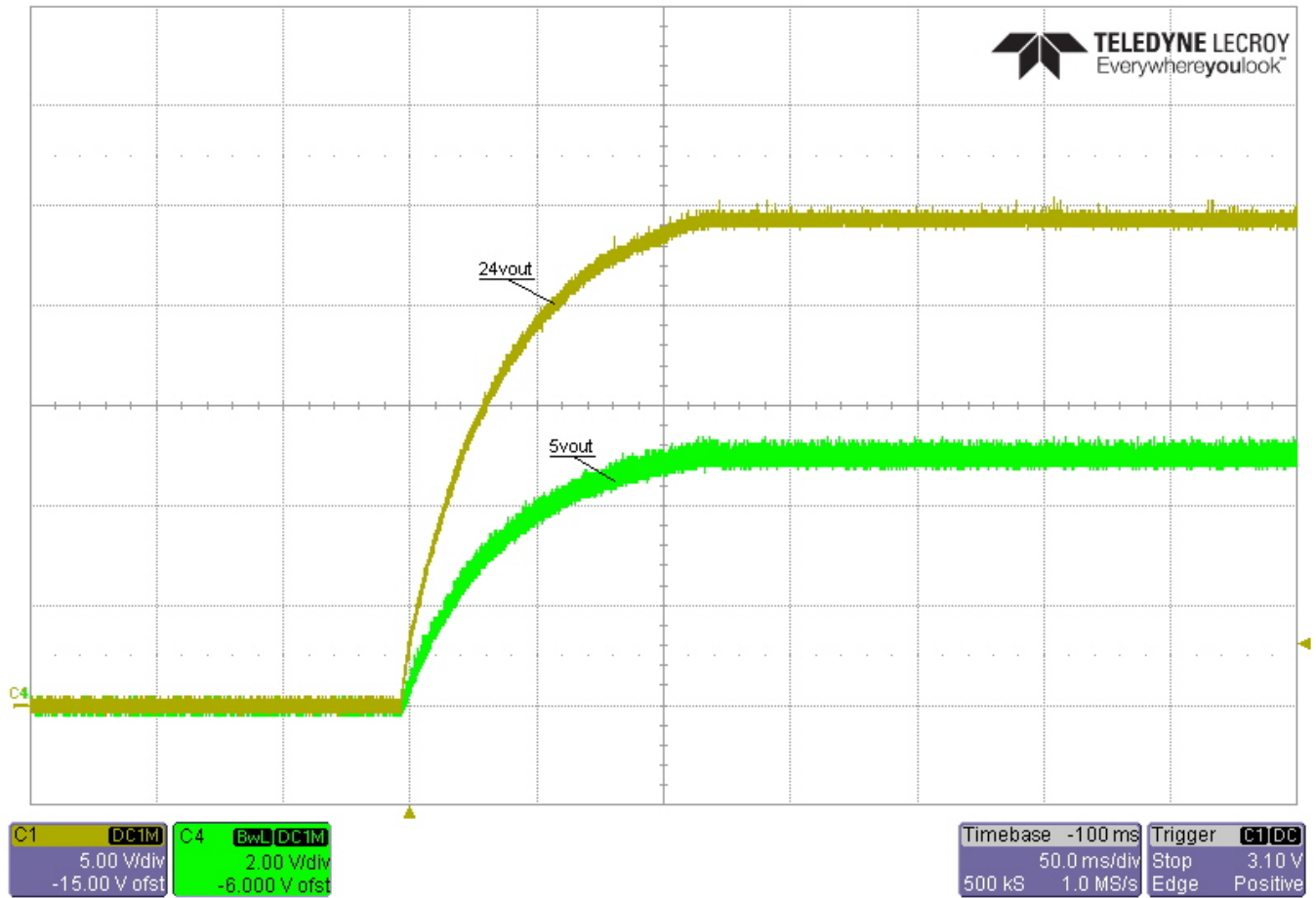


Input voltage = 630VDC
Output Power = 9.2W (full load)

Figure 12. Startup

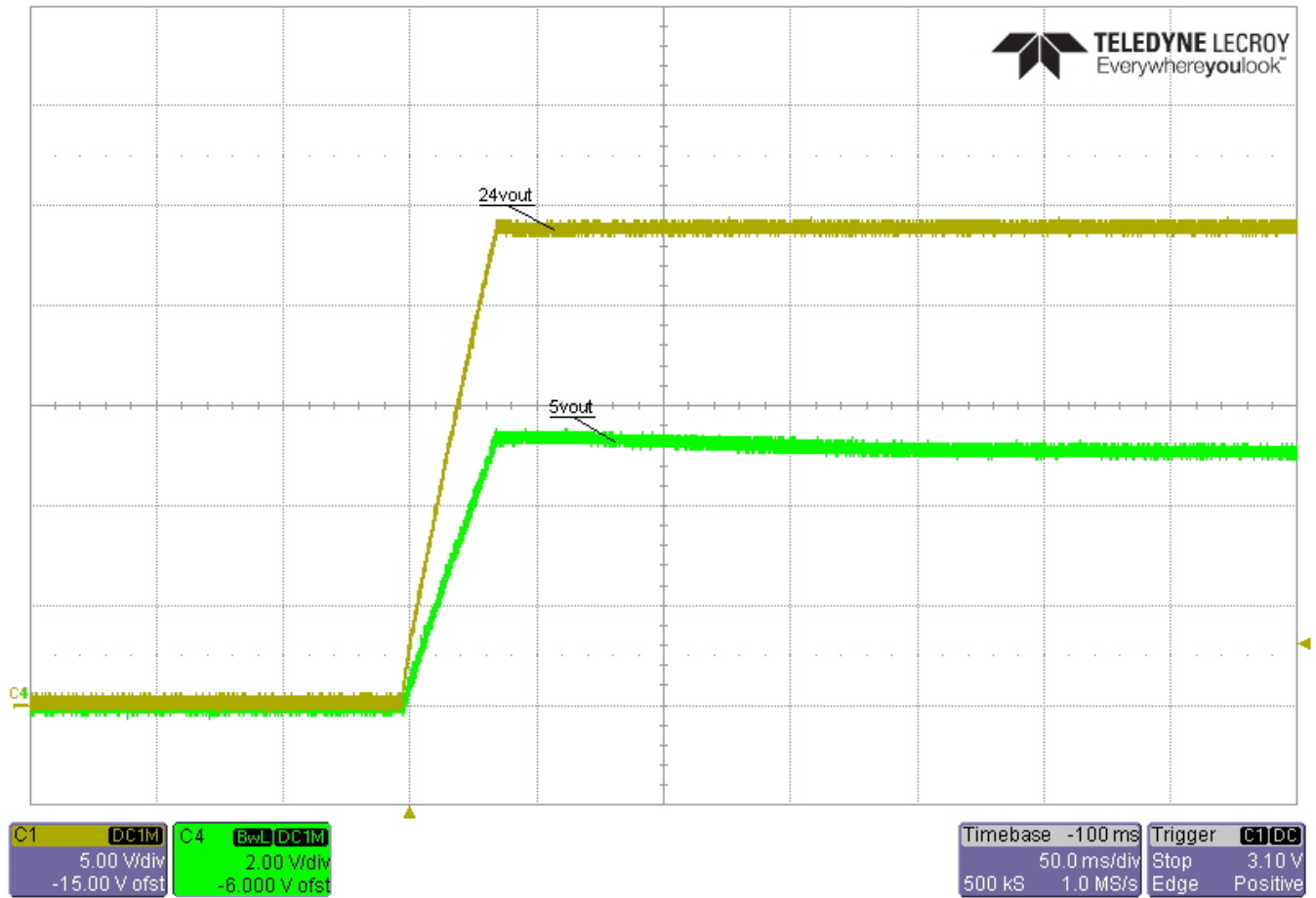


Input voltage = 85VAC
 Output Power = 0W (no load)

Figure 13.

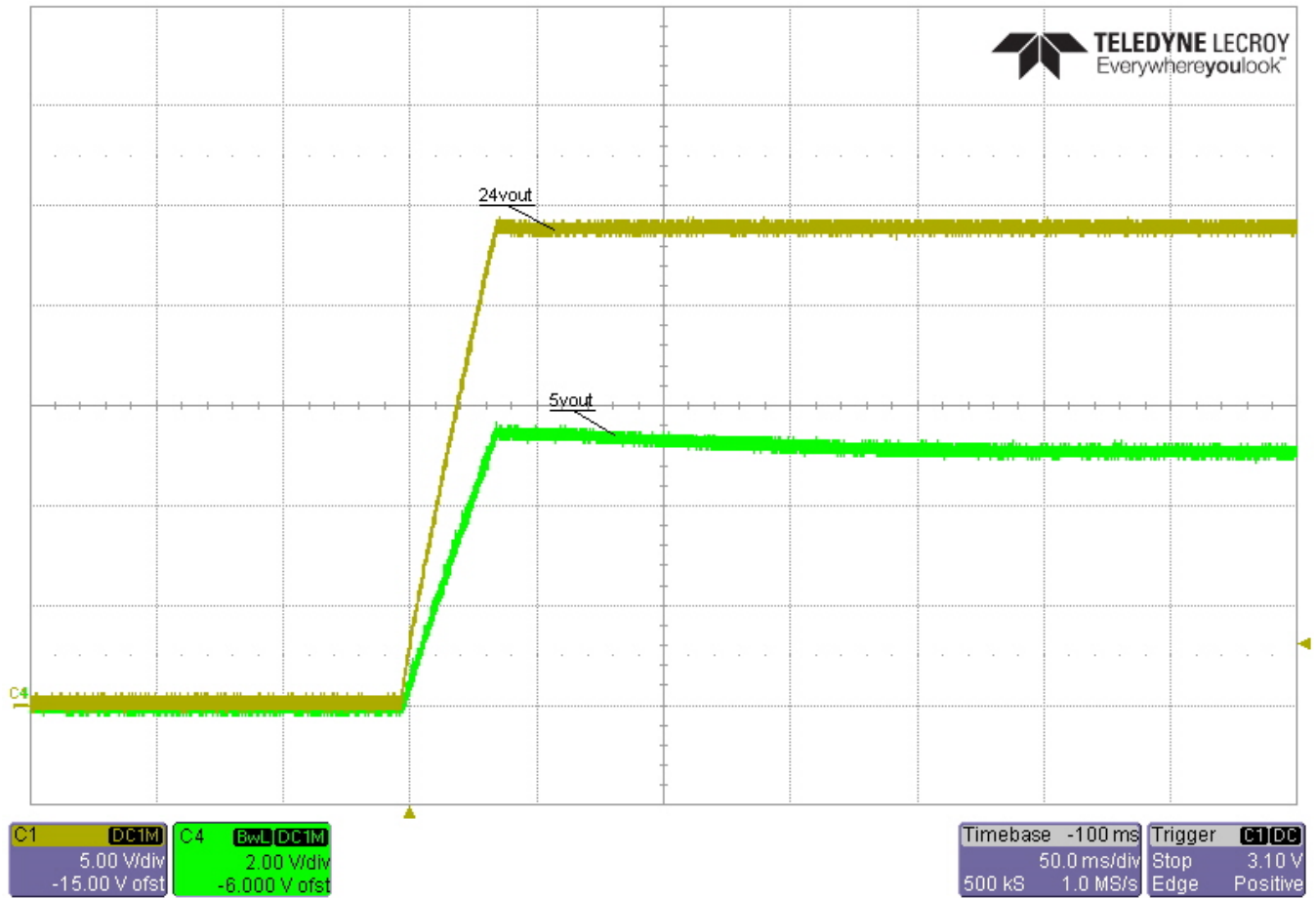

Input voltage = 273VAC
Output Power = 0W (no load)


Figure 14. Startup

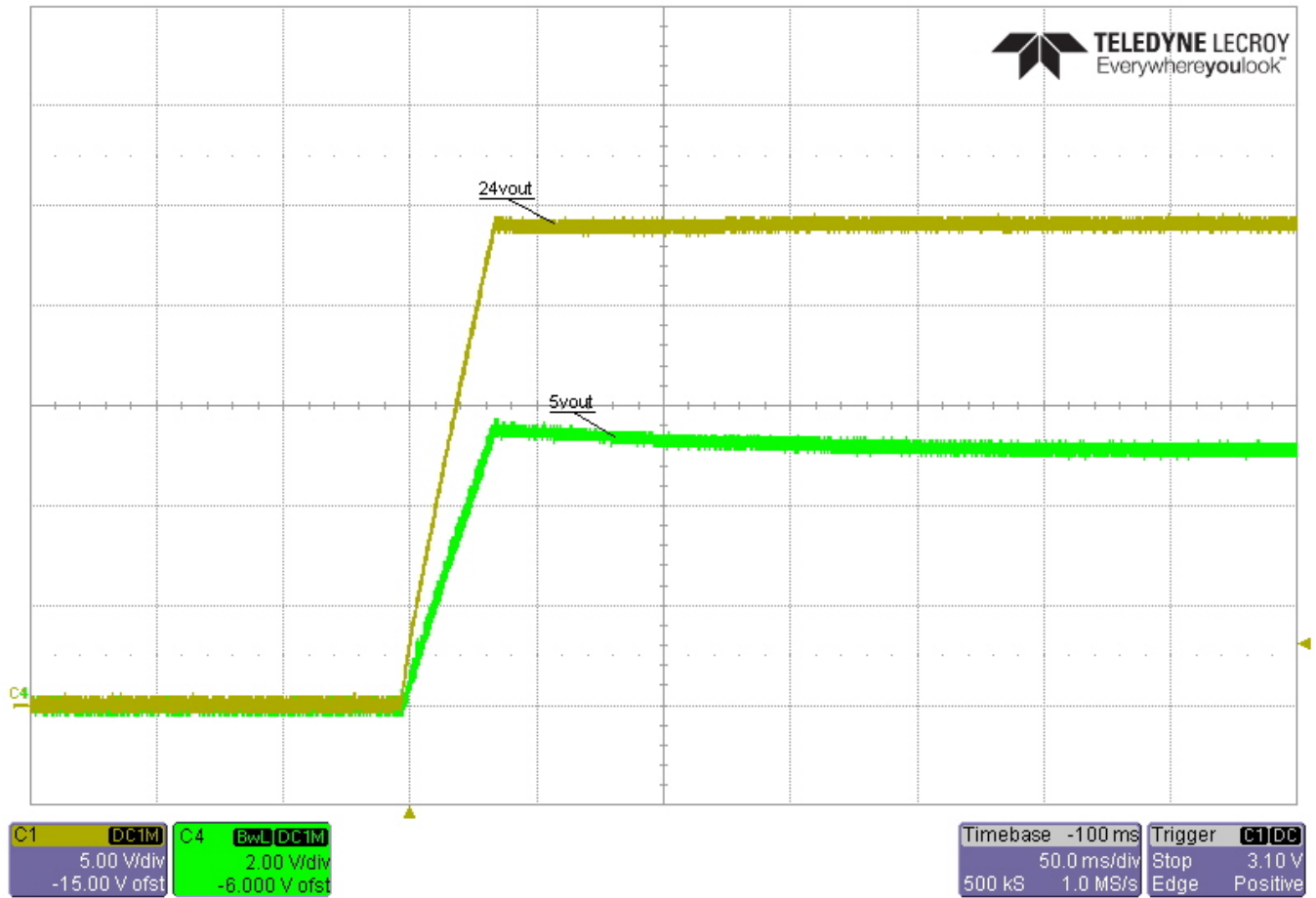

Input voltage = 630VDC
Output Power = 0W (no load)

3.5 Input Ripple

Figure 15. Bulk Input Voltage Ripple

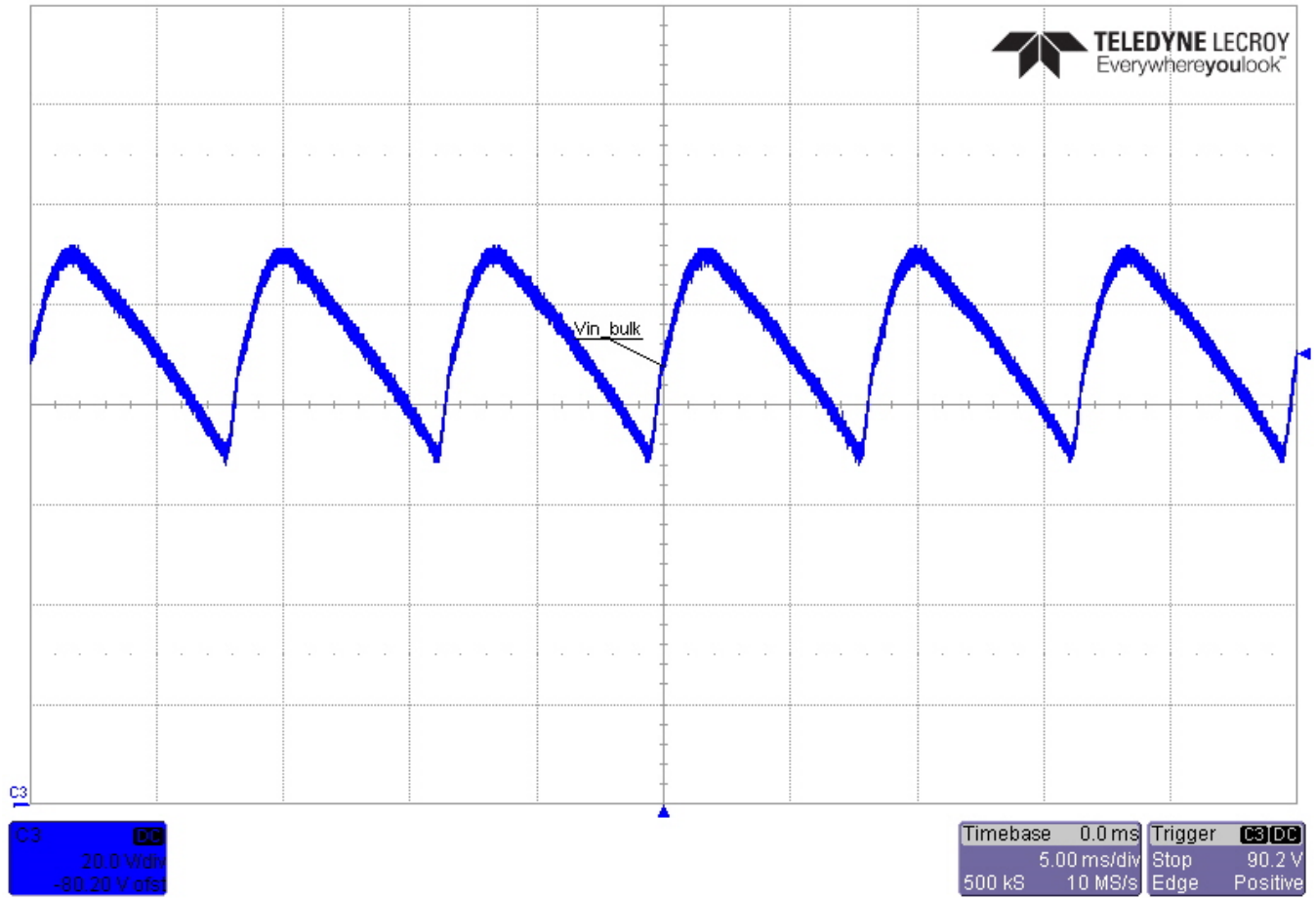

Input voltage = 85VAC
 Output Power = 9.2W (full load)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated