



UCC28700-Q1 Primary-Side Regulated Flyback Converter

TI reference design number: PMP20583 Rev A

Input: 37V to 125V
Outputs: 5V @ 80mA and Isolated 5V @ 80mA

DC – DC Test Results

Table of Contents

1	Circuit Description.....	3
2	Photos	3
3	Efficiency	5
4	Standby Input Power	7
5	Output Voltage Regulation.....	7
6	Startup Behavior	9
6.1	Turn-on from V_{in} with $C_{out} = 150\mu F$	9
6.2	Turn-on from V_{in} with $C_{out} = 82\mu F$	11
7	Switching and Ripple	12
7.1	Switching and Ripple	12
7.2	Frequency Dithering	14
7.1	Switching and Ripple into Constant-Voltage Load.....	15
8	Load Transient Response.....	16
8.1	Load Transient Response with $C_{out} = 150\mu F$	16
8.1	Load Transient Response with $C_{out} = 82\mu F$	17

1 Circuit Description


PMP20583 is a primary-side regulated flyback which provides a ground referenced 5V output and an isolated 5V output at up to 80mA each from an input voltage of 37V to 125V. This design uses the UCC28700-Q1 flyback controller for constant-voltage and constant current control of the output. Variable frequency operation minimizes standby power at no load. Features include quasi-resonant valley switching for highest efficiency and frequency dithering to improve EMI performance.

All tests were performed at room temperature on an open bench.

2 Photos

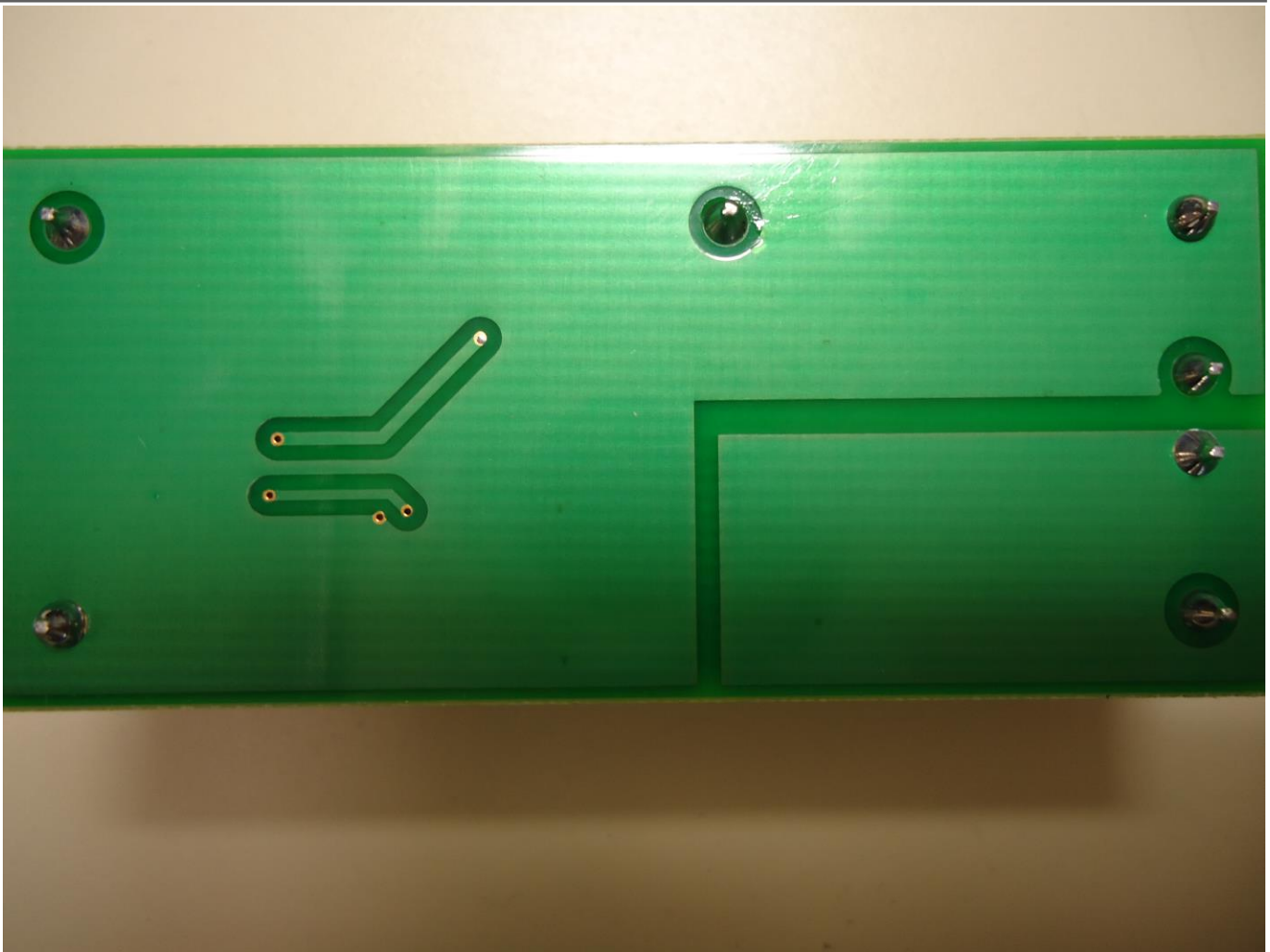
The photographs below show the PMP20583 Rev A printed circuit board assembly. This is a 2 layer board using 1 ounce copper. The overall board dimensions are 1.0" x 2.3".





3 Efficiency

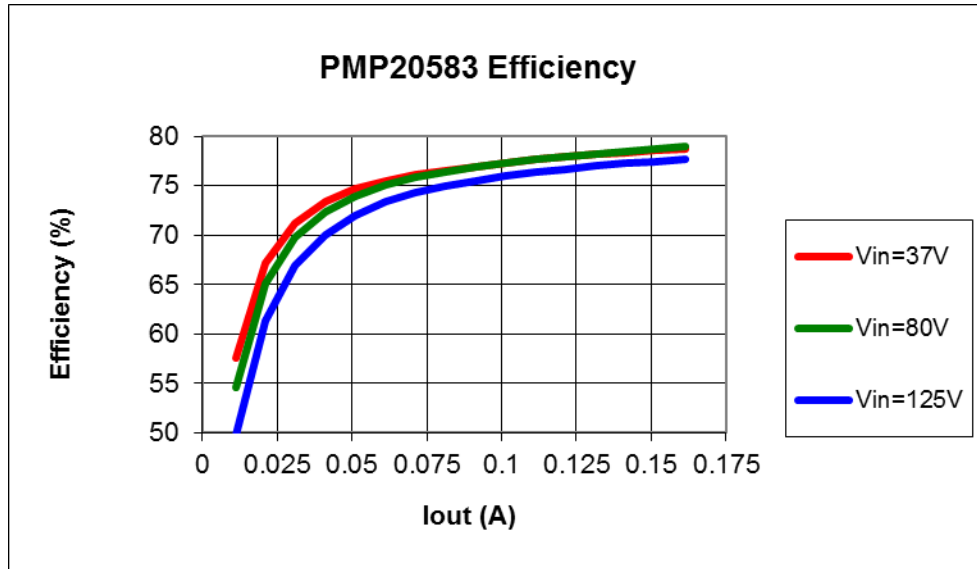The efficiency data is shown in the tables and graph below. The 5V outputs were connected in parallel for the test.



V _{in} (V)	I _{in} (A)	V _{out} (V)	I _{out} (A)	P _{in} (W)	P _{out} (W)	Losses (W)	Efficiency (%)
37.7254	0.000115	5.1402	0.00001	0.0043	0.0001	0.0043	1.19
37.6996	0.002640	5.1180	0.01120	0.0995	0.0573	0.0422	57.59
37.6825	0.004281	5.1097	0.02120	0.1613	0.1083	0.0530	67.15
37.6661	0.005930	5.1040	0.03116	0.2234	0.1590	0.0643	71.21
37.6489	0.007594	5.0970	0.04117	0.2859	0.2099	0.0760	73.40
37.6319	0.009264	5.0922	0.05115	0.3486	0.2605	0.0882	74.71
37.6141	0.010955	5.0880	0.06117	0.4121	0.3113	0.1008	75.53
37.5969	0.012641	5.0862	0.07117	0.4753	0.3620	0.1133	76.16
37.5793	0.014350	5.0840	0.08119	0.5393	0.4128	0.1265	76.55
37.5618	0.016040	5.0851	0.09118	0.6025	0.4637	0.1388	76.96
37.5442	0.017737	5.0881	0.10120	0.6659	0.5149	0.1510	77.32
37.5270	0.019433	5.0922	0.11119	0.7293	0.5662	0.1631	77.64
37.5093	0.021151	5.0995	0.12125	0.7934	0.6183	0.1750	77.94
37.4915	0.022862	5.1047	0.13126	0.8571	0.6700	0.1871	78.17
37.4744	0.024572	5.1087	0.14128	0.9208	0.7218	0.1991	78.38
37.4568	0.026275	5.1114	0.15127	0.9842	0.7732	0.2110	78.56
37.4391	0.027979	5.1139	0.16129	1.0475	0.8248	0.2227	78.74

PMP20583 Rev A Test Results



Vin (V)	Iin (A)	Vout (V)	Iout (A)	Pin (W)	Pout (W)	Losses (W)	Efficiency (%)
81.5691	0.000076	5.1369	0.00001	0.0062	0.0001	0.0062	0.82
81.5566	0.001286	5.1176	0.01118	0.1049	0.0572	0.0477	54.55
81.5494	0.002039	5.1092	0.02118	0.1663	0.1082	0.0581	65.05
81.5416	0.002794	5.1011	0.03115	0.2278	0.1589	0.0689	69.76
81.5339	0.003553	5.0929	0.04116	0.2897	0.2096	0.0801	72.36
81.5262	0.004313	5.0874	0.05113	0.3517	0.2601	0.0915	73.97
81.5180	0.005083	5.0856	0.06116	0.4143	0.3110	0.1033	75.07
81.5102	0.005853	5.0851	0.07116	0.4771	0.3618	0.1152	75.85
81.5025	0.006629	5.0851	0.08119	0.5402	0.4128	0.1274	76.42
81.4943	0.007401	5.0871	0.09117	0.6031	0.4638	0.1394	76.89
81.4866	0.008176	5.0896	0.10118	0.6663	0.5150	0.1513	77.29
81.4785	0.008948	5.0917	0.11117	0.7291	0.5661	0.1630	77.64
81.4707	0.009728	5.0960	0.12123	0.7925	0.6178	0.1747	77.95
81.4628	0.010503	5.0992	0.13123	0.8556	0.6692	0.1864	78.21
81.4547	0.011280	5.1030	0.14125	0.9188	0.7208	0.1980	78.45
81.4468	0.012046	5.1082	0.15125	0.9811	0.7726	0.2085	78.75
81.4387	0.012827	5.1134	0.16126	1.0446	0.8246	0.2200	78.94

Vin (V)	Iin (A)	Vout (V)	Iout (A)	Pin (W)	Pout (W)	Losses (W)	Efficiency (%)
125.0185	0.000087	5.1341	0.00001	0.0109	0.0001	0.0108	0.47
125.0093	0.000916	5.1145	0.01114	0.1145	0.0570	0.0575	49.79
125.0054	0.001409	5.1080	0.02115	0.1761	0.1080	0.0681	61.33
125.0002	0.001899	5.0986	0.03112	0.2373	0.1587	0.0786	66.87
124.9937	0.002393	5.0903	0.04114	0.2991	0.2094	0.0898	70.00
124.9872	0.002887	5.0846	0.05110	0.3609	0.2598	0.1011	72.00
124.9833	0.003388	5.0815	0.06112	0.4234	0.3106	0.1128	73.35
124.9781	0.003892	5.0813	0.07112	0.4864	0.3614	0.1251	74.29
124.9728	0.004400	5.0820	0.08114	0.5499	0.4123	0.1375	74.99
124.9676	0.004910	5.0852	0.09113	0.6136	0.4634	0.1502	75.52
124.9624	0.005422	5.0888	0.10115	0.6776	0.5147	0.1628	75.97
124.9572	0.005933	5.0918	0.11114	0.7413	0.5659	0.1754	76.34
124.9507	0.006447	5.0964	0.12121	0.8055	0.6177	0.1878	76.69
124.9481	0.006957	5.0990	0.13121	0.8692	0.6690	0.2002	76.97
124.9416	0.007468	5.1023	0.14123	0.9331	0.7206	0.2125	77.23
124.9351	0.007978	5.1052	0.15123	0.9967	0.7721	0.2247	77.46
124.9299	0.008490	5.1092	0.16124	1.0606	0.8238	0.2368	77.67

PMP20583 Rev A Test Results



4 Standby Input Power

The input power was measured at no load, with no voltmeters or oscilloscope connected.

Vin (V)	Iin (A)	Pin (W)
37	0.000110	0.00406
80	0.000065	0.00522
125	0.000064	0.00801

5 Output Voltage Regulation

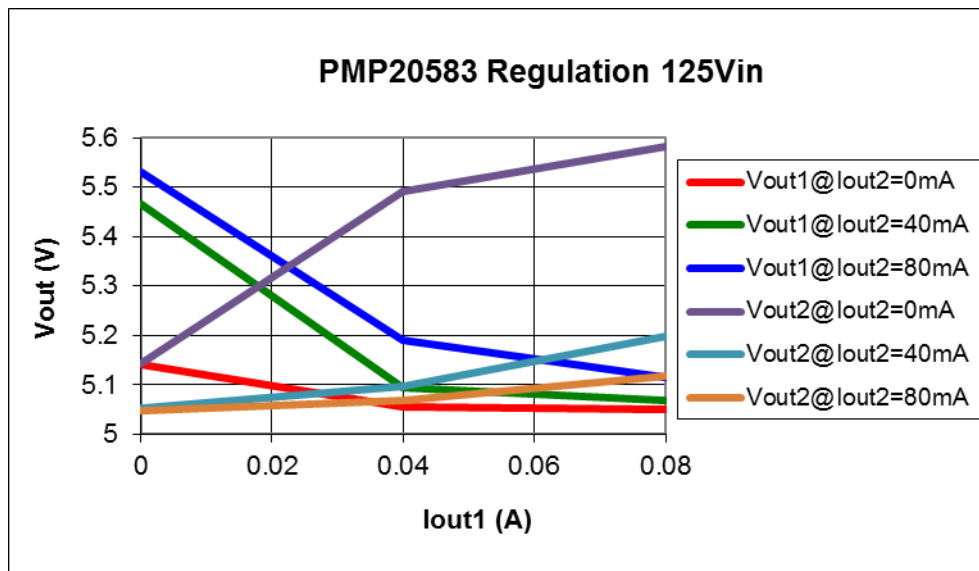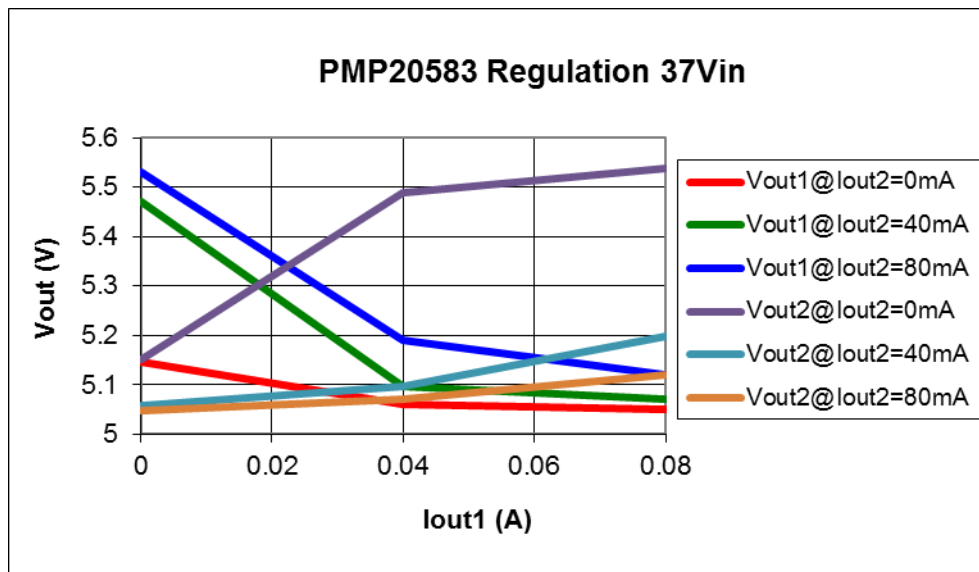Output voltage regulation data is shown in the tables and graphs below.



PMP20583 Rev A Test Results





Vin (V)	Iin (A)	Vout1 (V)	Iout (A)	Vout2 (V)	Iout2 (A)	Losses (W)	Efficiency (%)
37.01	0.00012	5.1460	0.0000	5.1510	0.0000	0.0044	0.00
37.03	0.00787	5.0610	0.0400	5.4890	0.0000	0.0890	69.47
36.95	0.01537	5.0500	0.0800	5.5370	0.0000	0.1639	71.14
37.11	0.00786	5.4710	0.0000	5.0570	0.0400	0.0894	69.35
36.95	0.01443	5.0980	0.0400	5.0980	0.0400	0.1253	76.49
36.89	0.02144	5.0700	0.0800	5.1980	0.0400	0.1774	77.57
36.95	0.01528	5.5300	0.0000	5.0480	0.0800	0.1608	71.53
36.89	0.02159	5.1910	0.0400	5.0710	0.0800	0.1831	77.01
36.82	0.02828	5.1190	0.0800	5.1210	0.0800	0.2221	78.67

Vin (V)	Iin (A)	Vout1 (V)	Iout (A)	Vout2 (V)	Iout2 (A)	Losses (W)	Efficiency (%)
125.10	0.00008	5.1410	0.0000	5.1440	0.0000	0.0100	0.00
125.07	0.00245	5.0560	0.0400	5.4910	0.0000	0.1042	66.00
125.05	0.00464	5.0490	0.0800	5.5830	0.0000	0.1763	69.61
125.07	0.00244	5.4650	0.0000	5.0530	0.0400	0.1031	66.23
125.05	0.00436	5.0950	0.0400	5.0980	0.0400	0.1375	74.78
125.03	0.00643	5.0680	0.0800	5.1980	0.0400	0.1906	76.29
125.05	0.00460	5.5300	0.0000	5.0470	0.0800	0.1715	70.19
125.03	0.00646	5.1910	0.0400	5.0680	0.0800	0.1946	75.91
125.01	0.00843	5.1140	0.0800	5.1180	0.0800	0.2353	77.67


6 Startup Behavior

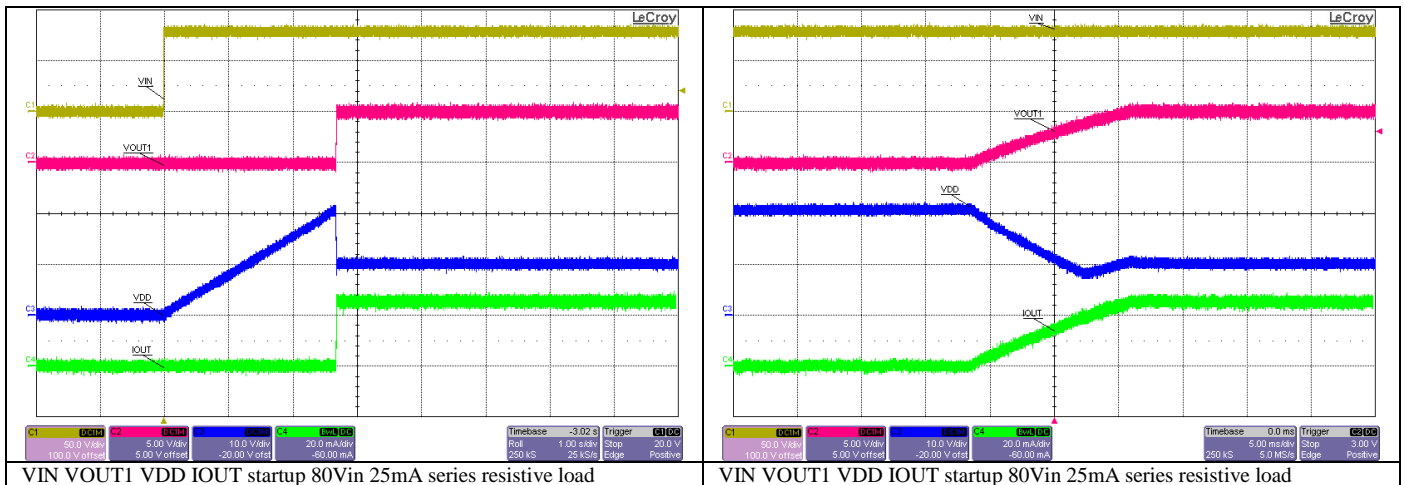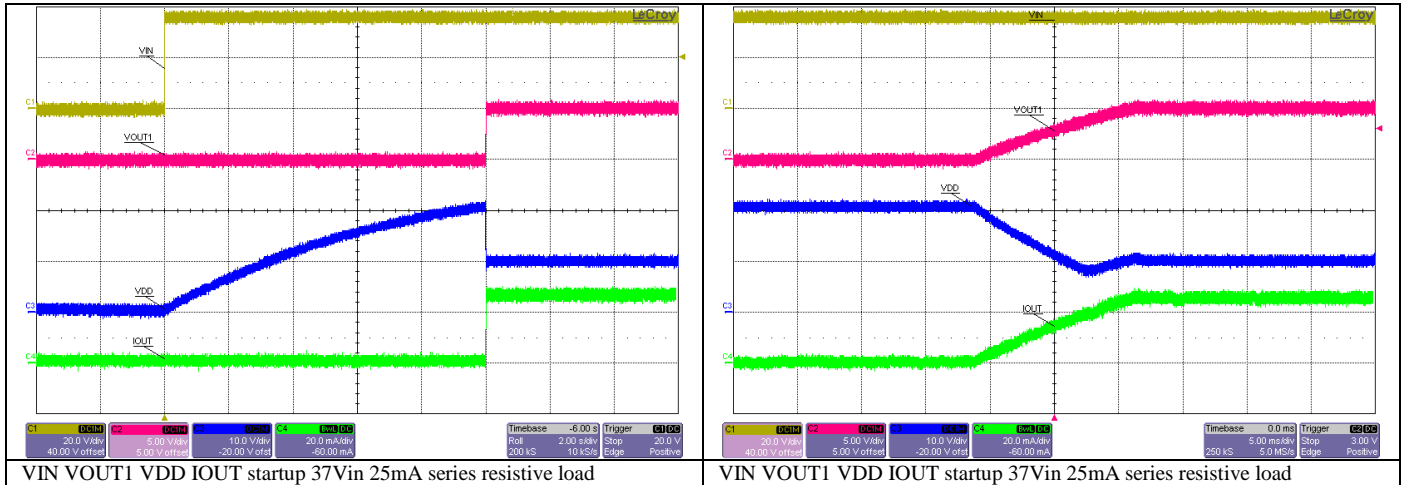6.1 Turn-on from Vin with Cout = 150uF


The output voltages were connected in series and a resistive load was used to test startup. The VDD capacitor is sized to start into 5V/25mA = 200 ohms and 150uF on each output. The startup delay time is set by the 4Meg ohm start resistor charging the 2.2uF VDD capacitor.



PMP20583 Rev A Test Results

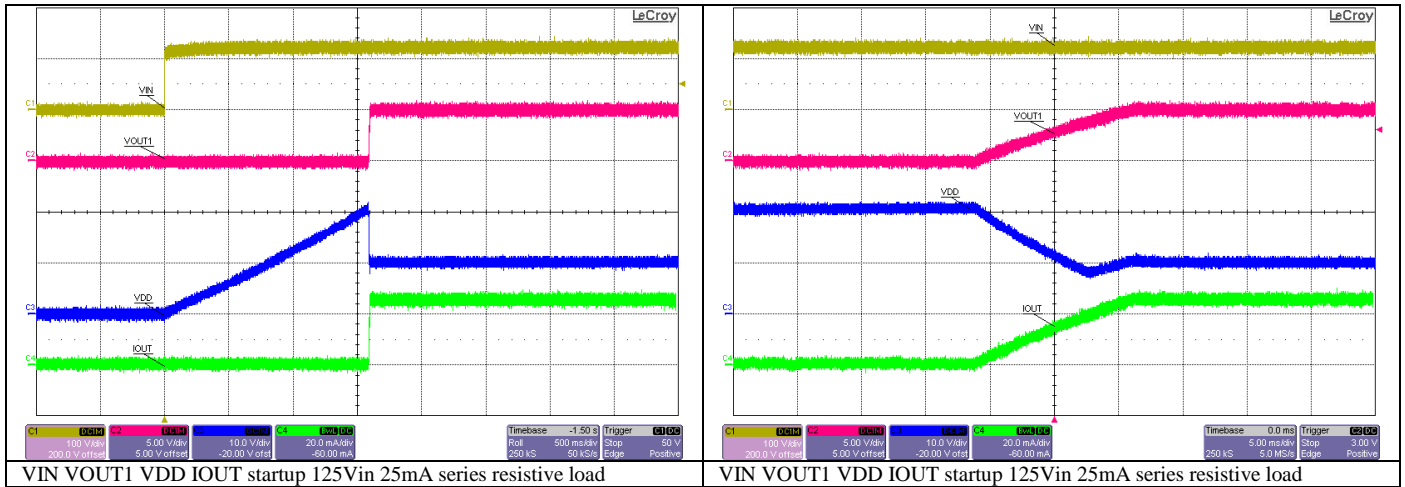

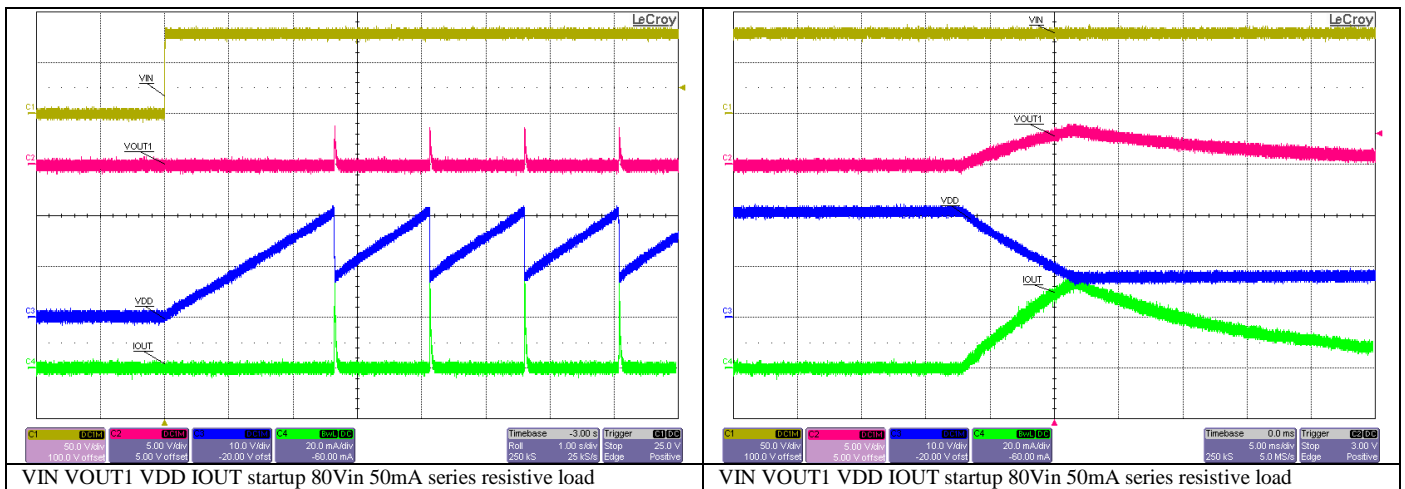
When the load is increased to 5V/50mA = 100 ohms on each output, the VDD bias voltage collapses during startup and the converter cycles on and off. This cycling provides overload protection.



PMP20583 Rev A Test Results

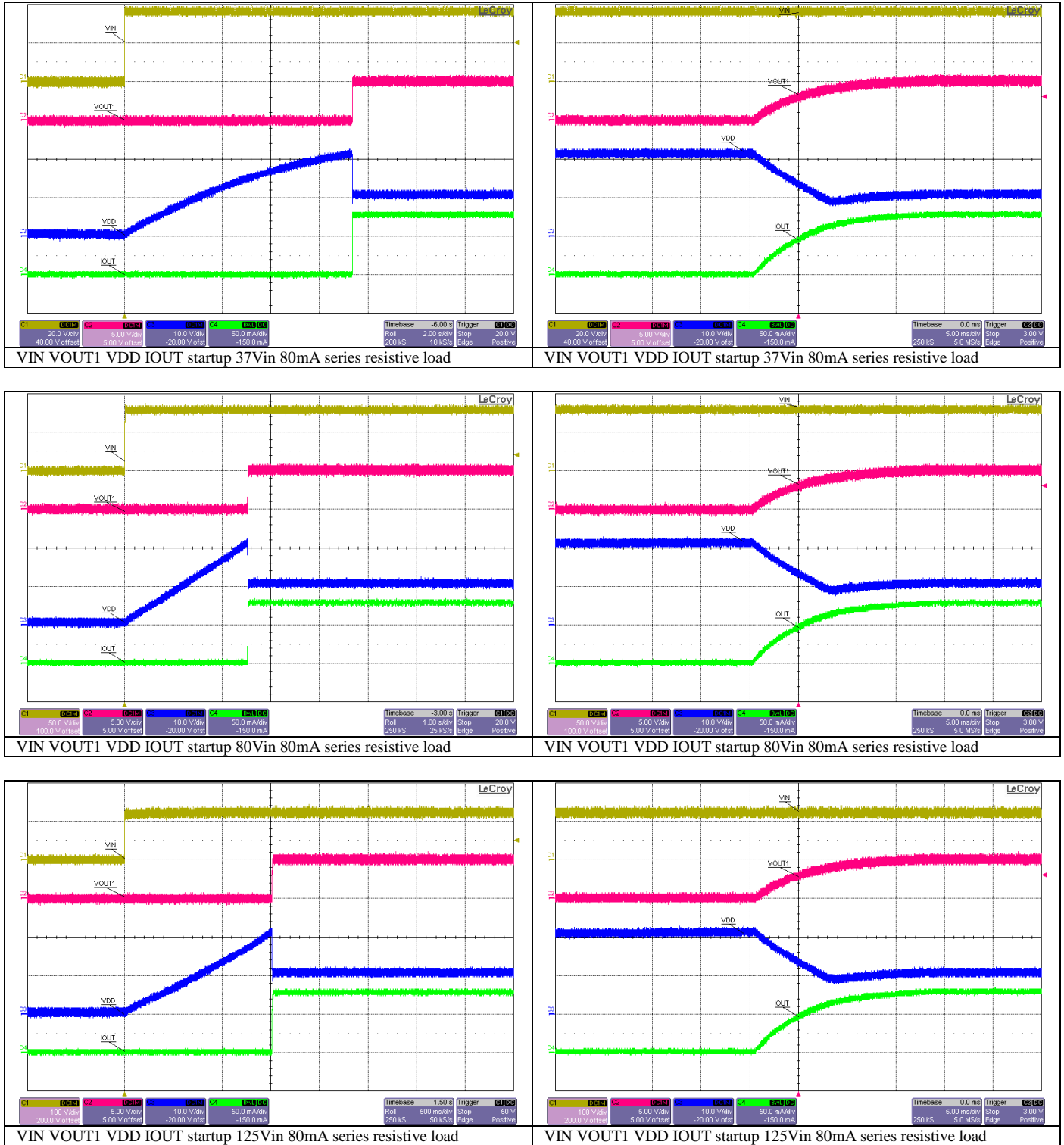6.2 Turn-on from Vin with Cout = 82uF




The output voltages were connected in series and a resistive load was used to test startup. Decreasing the output capacitors to 82uF allows the converter to start into 5V/80mA=62.5 ohms on each output.




7 Switching and Ripple

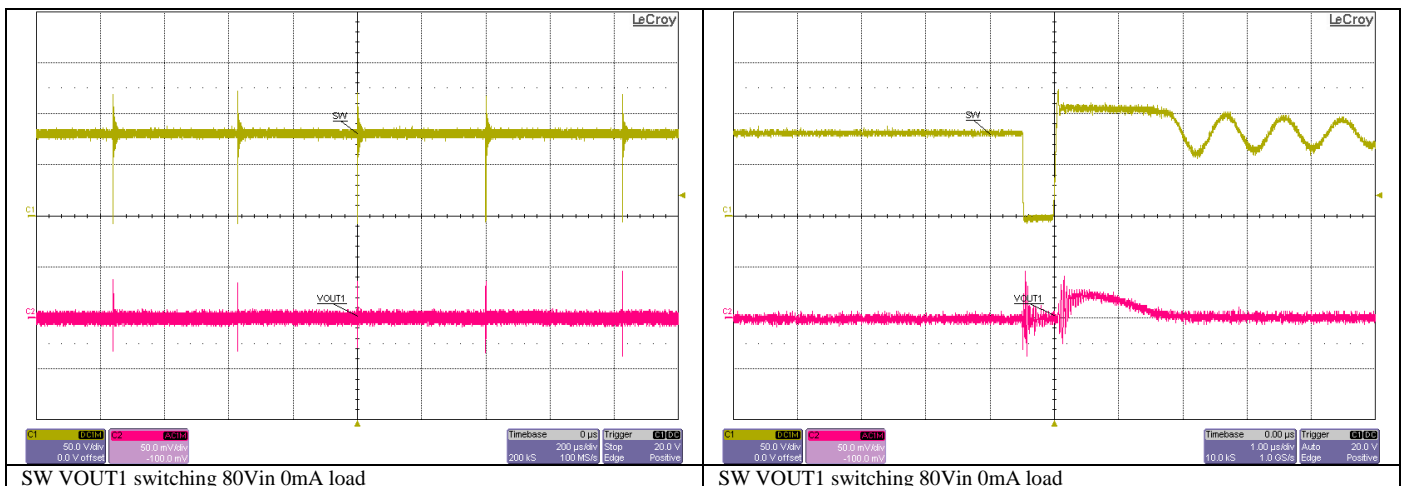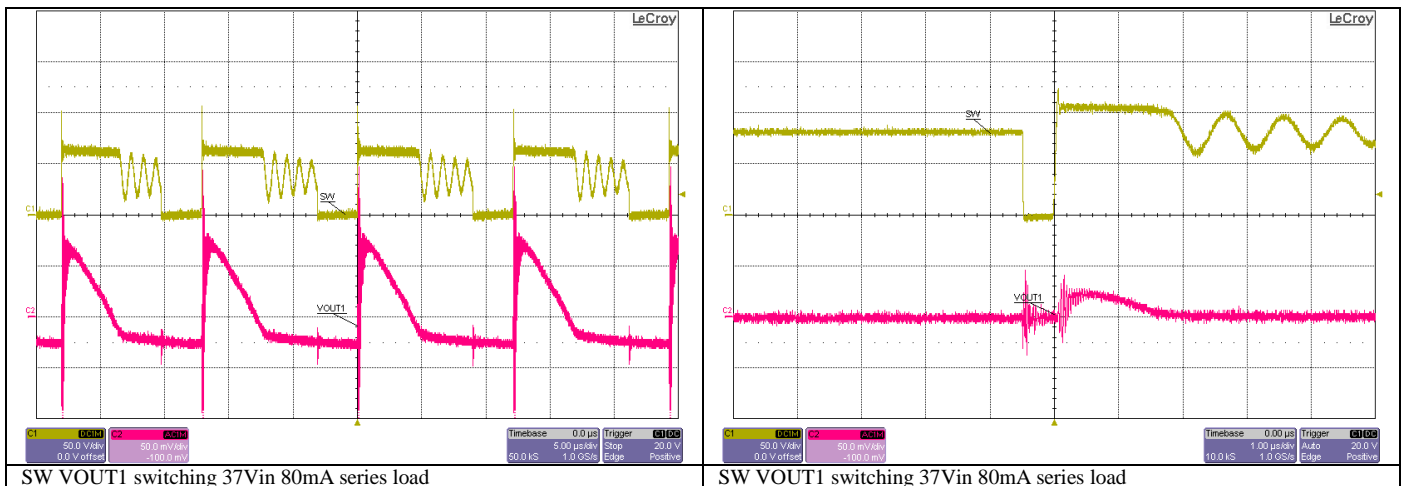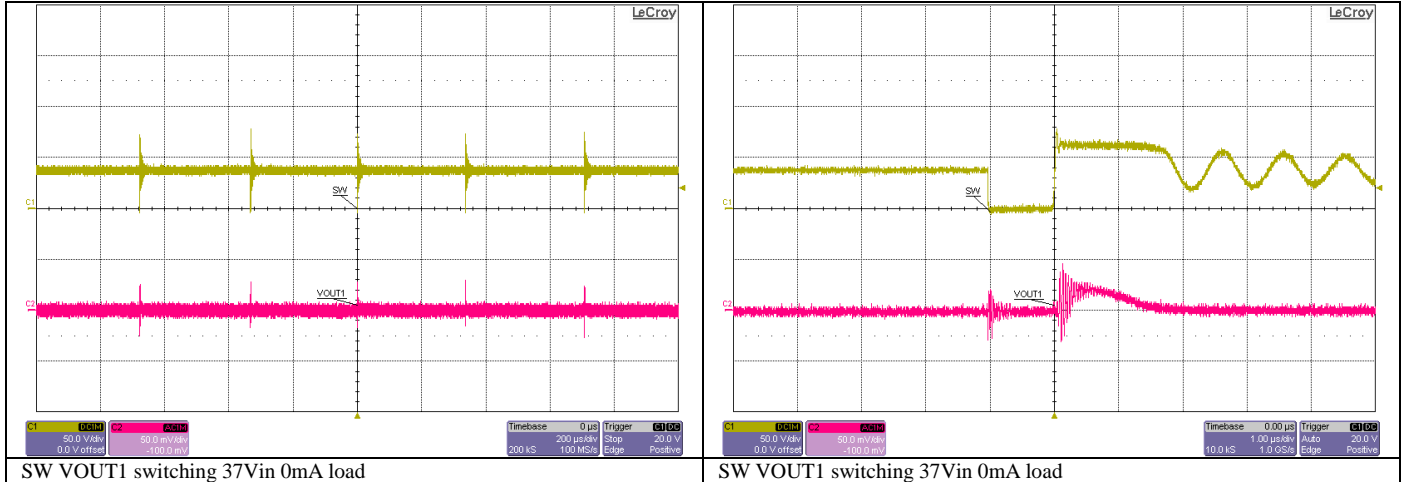7.1 Switching and Ripple


Switching and ripple were measured at full bandwidth using 500 MHz probes and 350 MHz oscilloscope.




PMP20583 Rev A Test Results

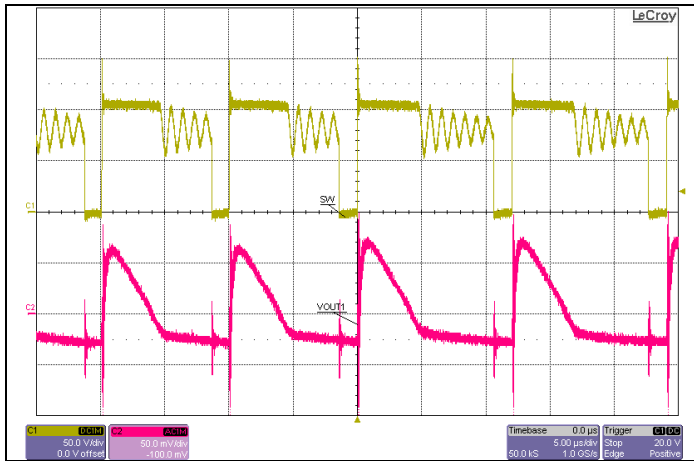

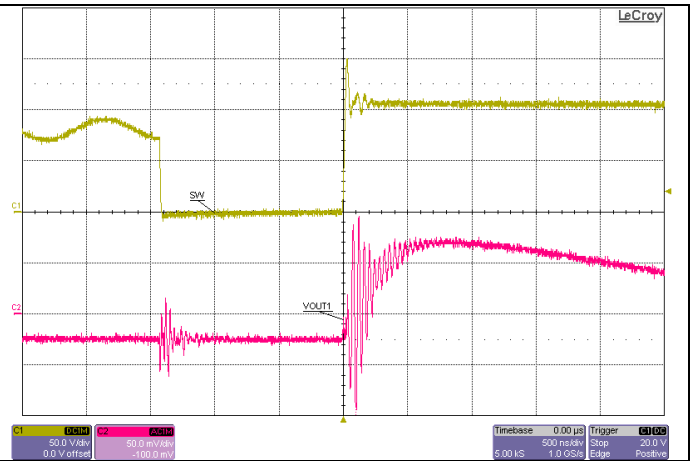
SW VOUT1 switching 80Vin 80mA series load



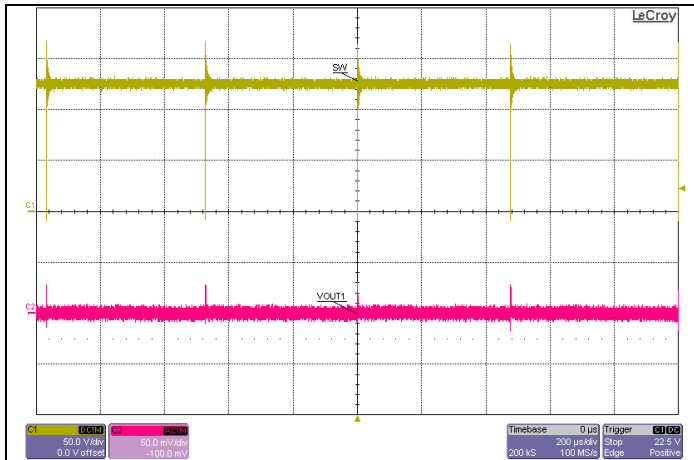
SW VOUT1 switching 80Vin 80mA series load




SW VOUT1 switching 125Vin 0A load

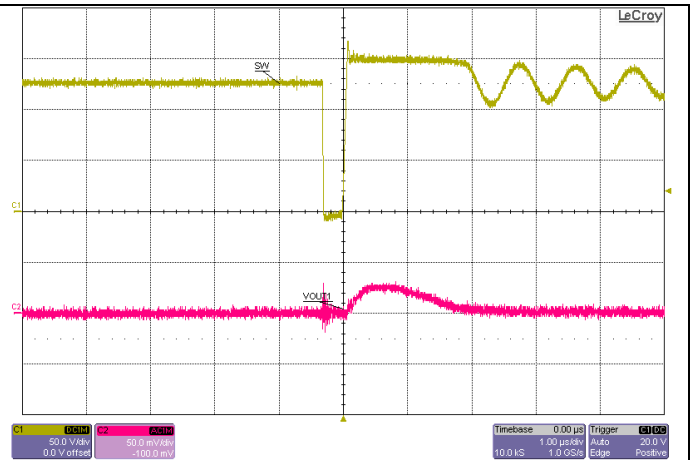

SW VOUT1 switching 125Vin 0A load






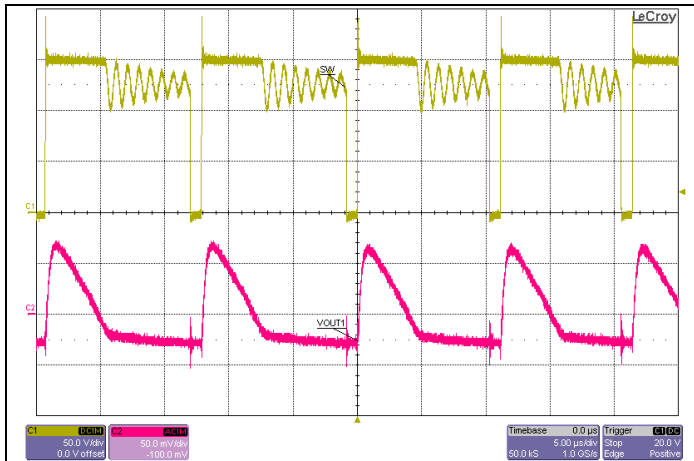


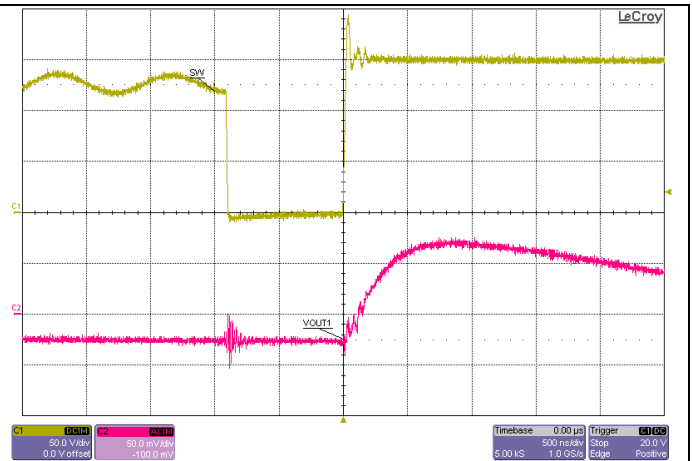SW VOUT1 switching 125Vin 80mA series load





SW VOUT1 switching 125Vin 80mA series load

7.2 Frequency Dithering

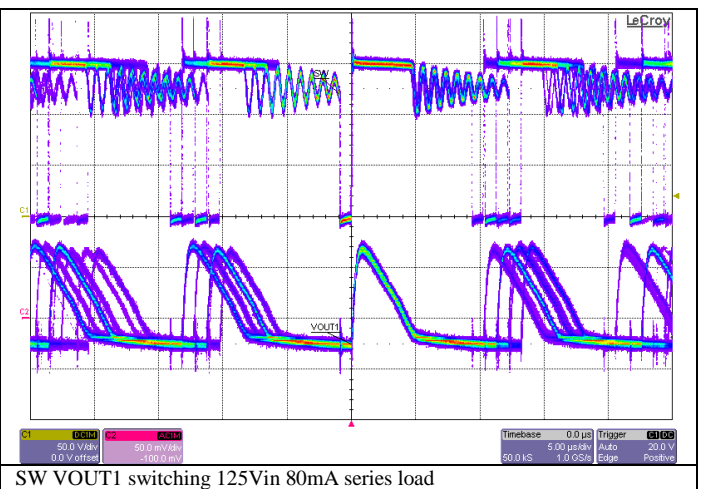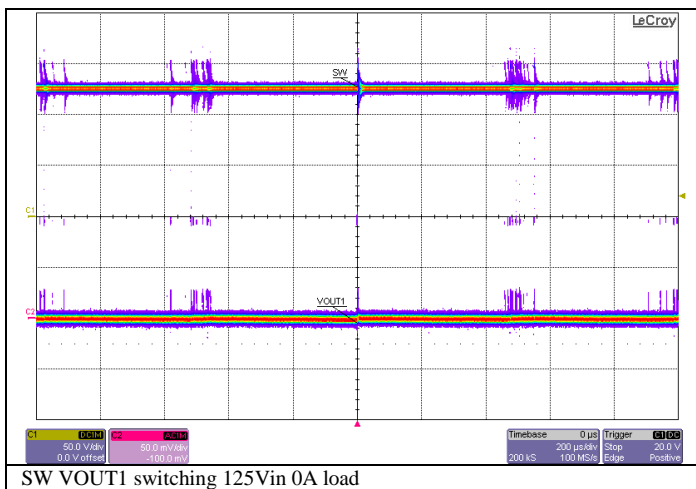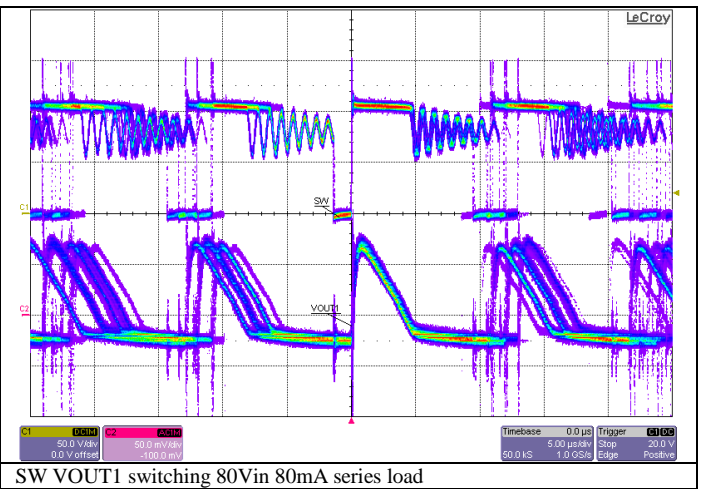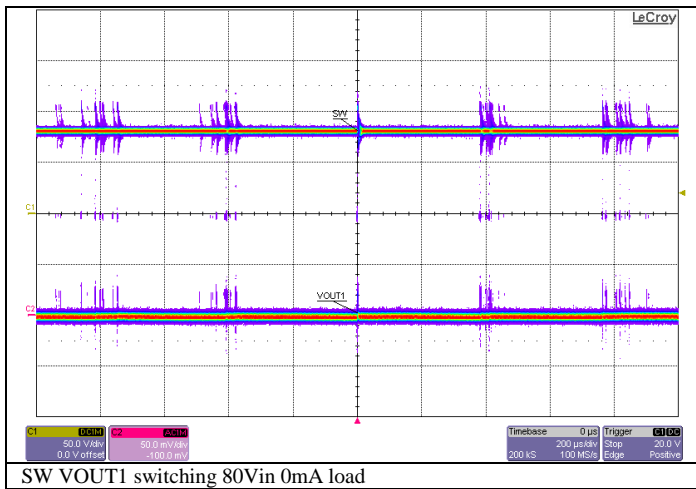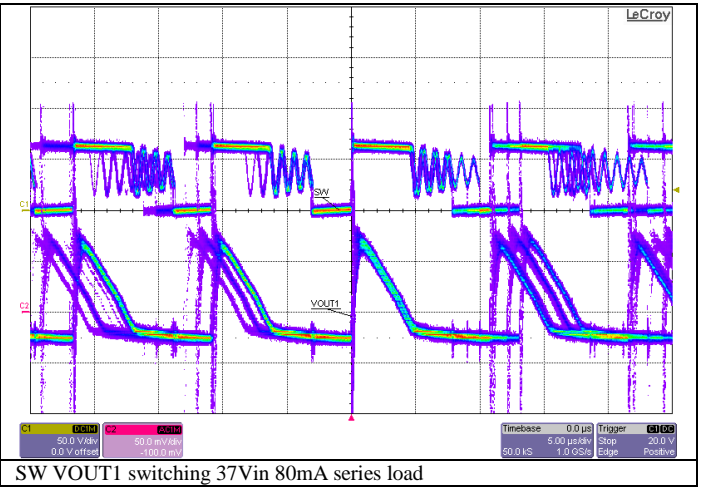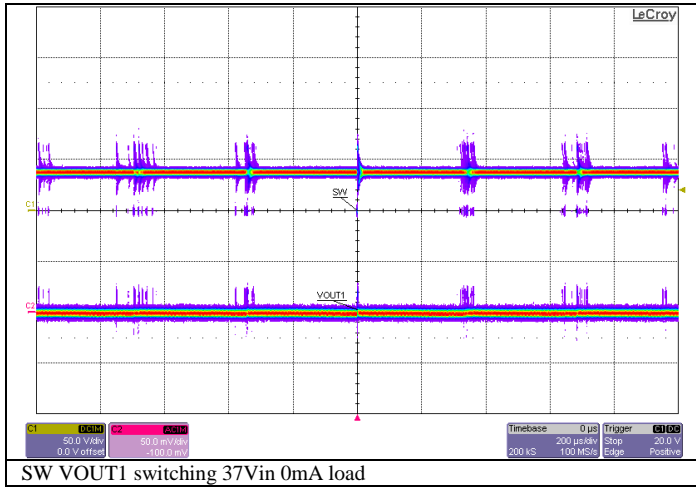

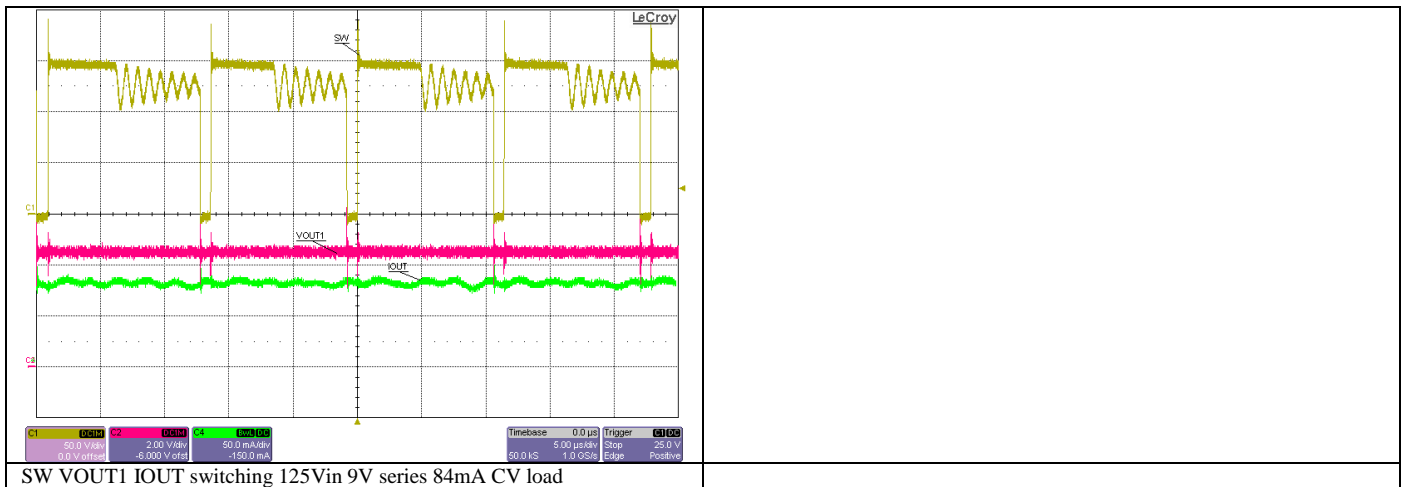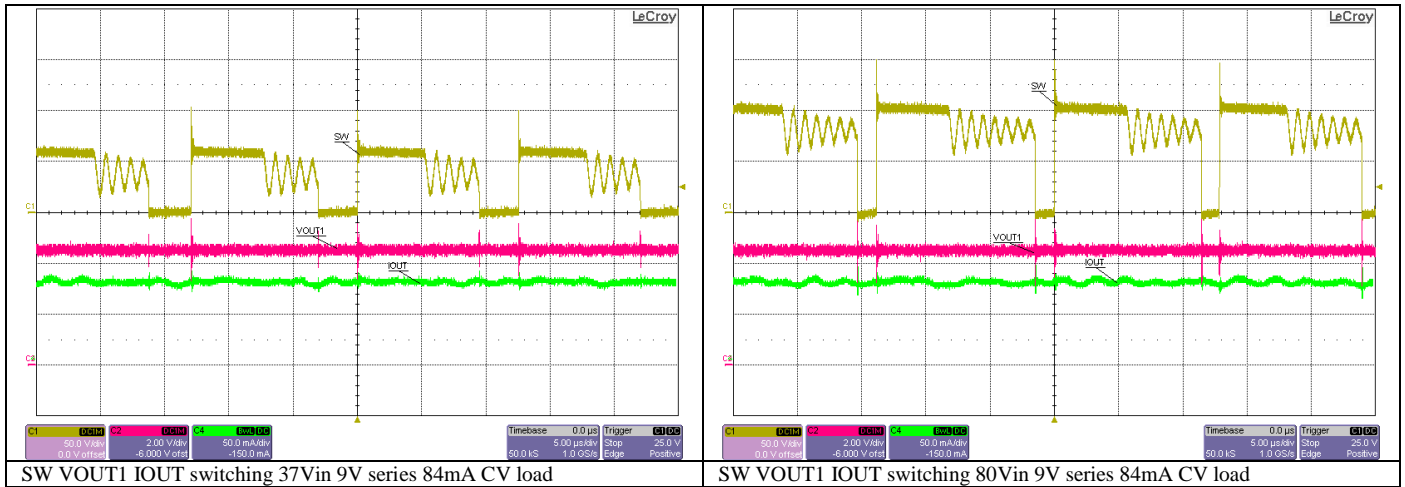7.1 Switching and Ripple into Constant-Voltage Load



The outputs were wired in series and connected to a constant 9V load. Measured current limit was 84mA.




8 Load Transient Response

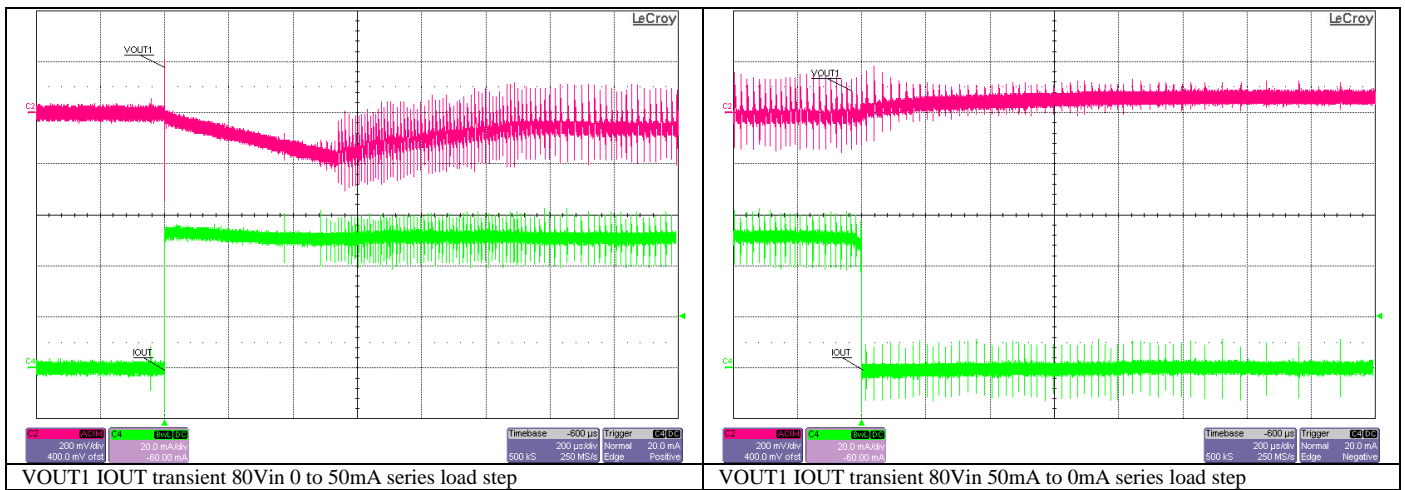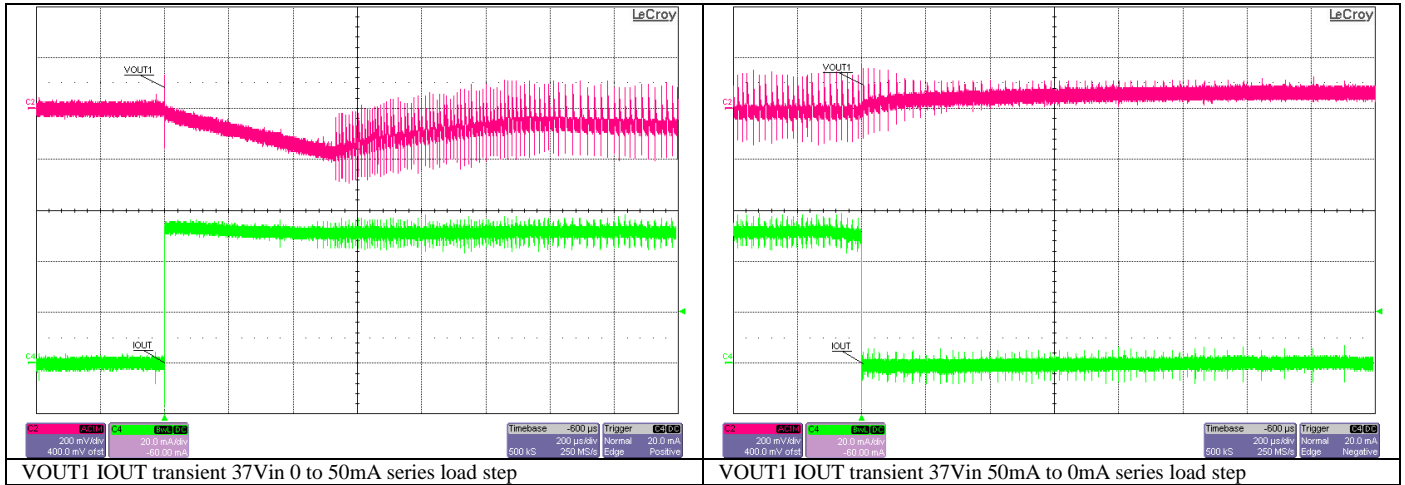8.1 Load Transient Response with $C_{out} = 150\mu F$



A fixed resistor was used to manually step the current.



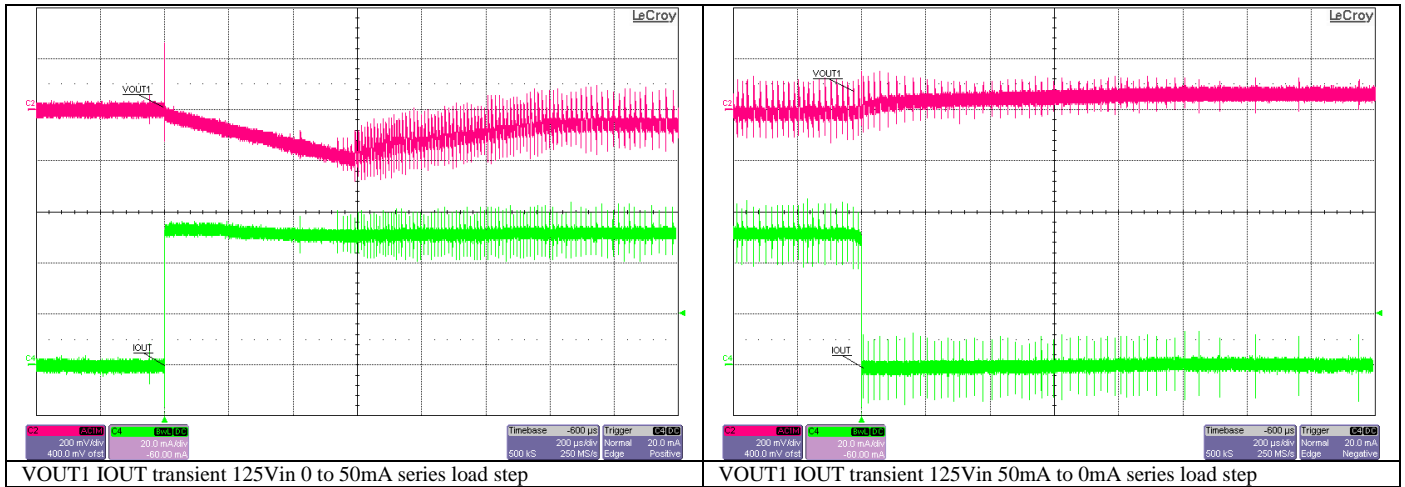


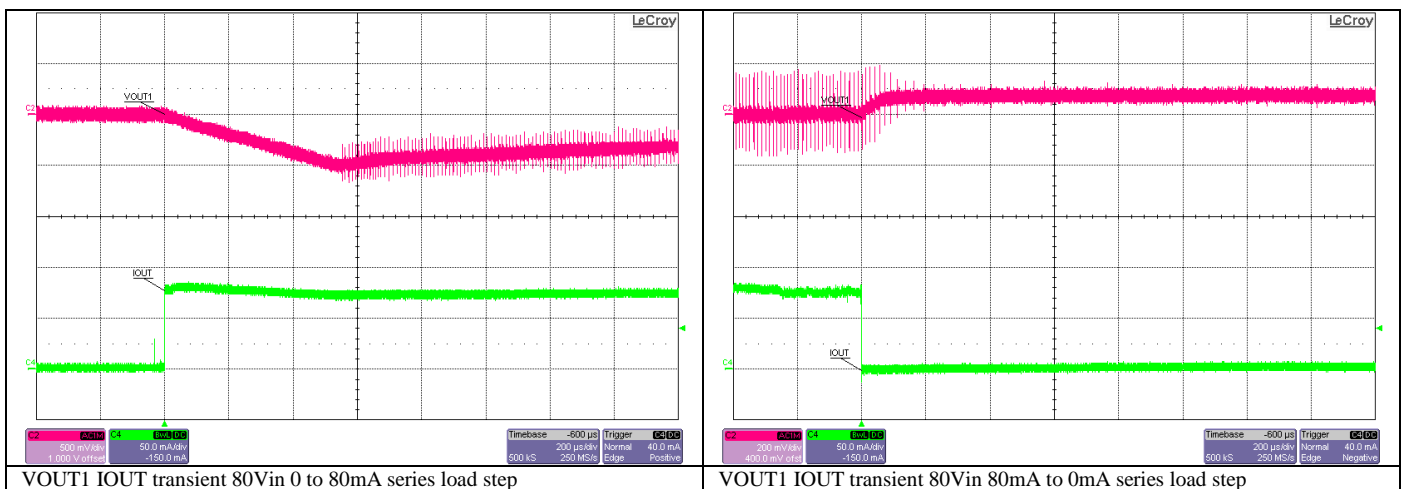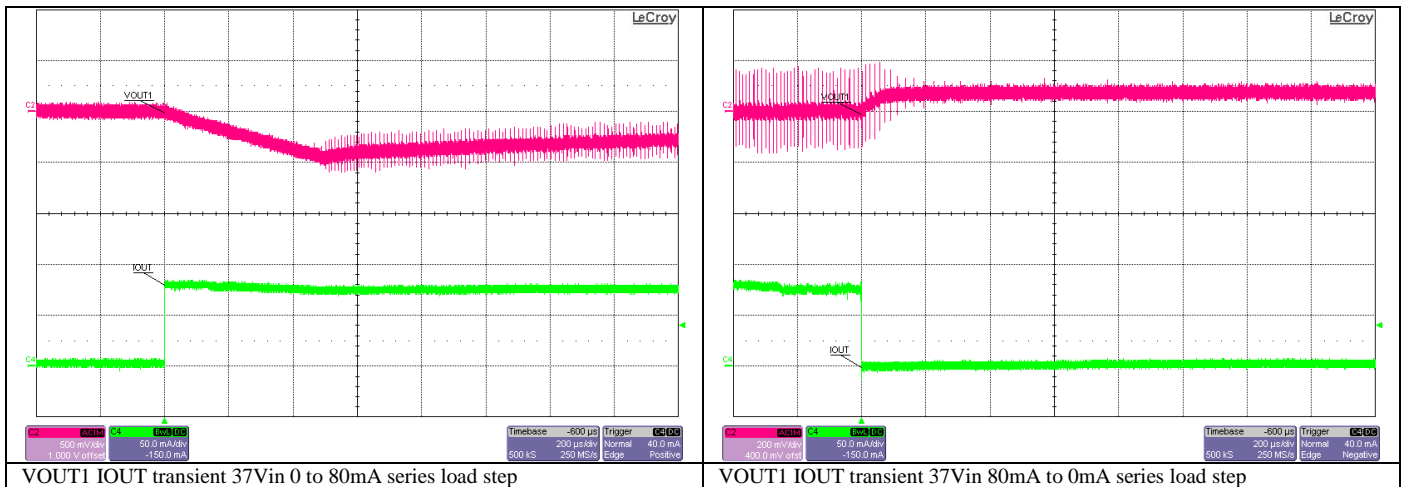8.1 Load Transient Response with $C_{out} = 82\mu F$

A fixed resistor was used to manually step the current.



PMP20583 Rev A Test Results

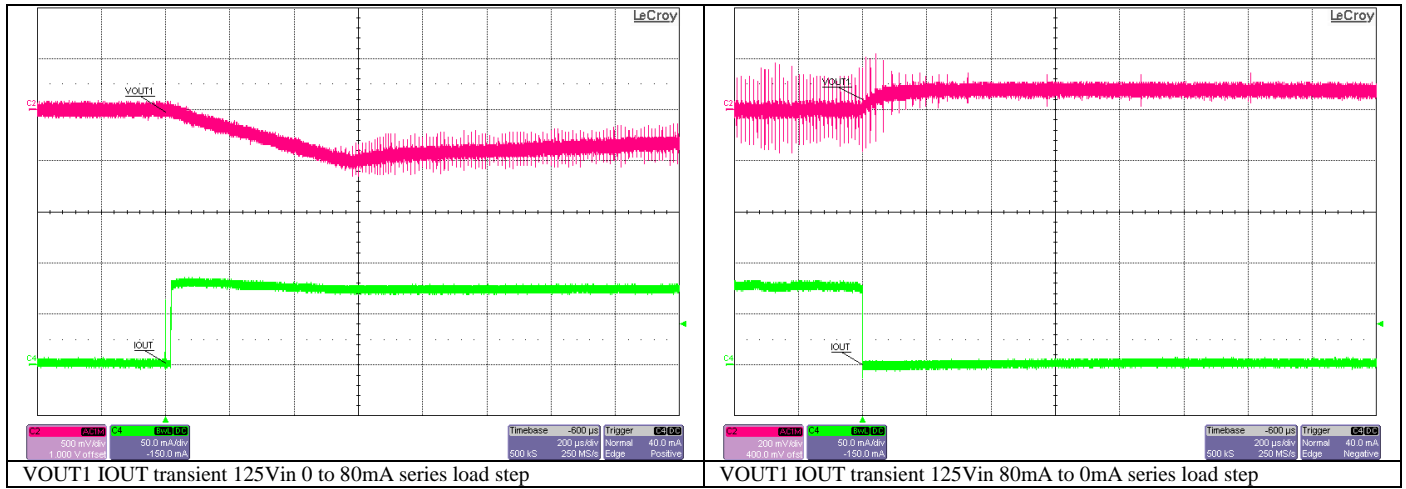

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (<https://www.ti.com/legal/termsofsale.html>) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2021, Texas Instruments Incorporated