

Analog Engineer's Circuit

Slew Rate Limiter Circuit




Design Goals

Input		Output		Supply		
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{ref}
-10 V	10 V	-10 V	10 V	15 V	-15 V	0 V

Design Description

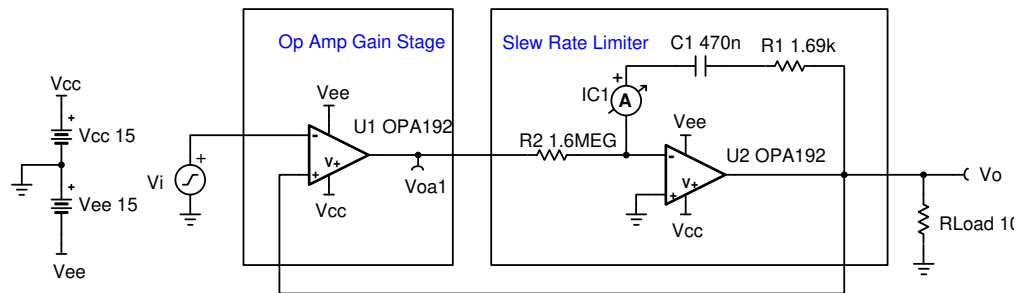This circuit controls the slew rate of an analog gain stage. This circuit is intended for symmetrical slew rate applications. The desired slew rate must be slower than that of the op amp chosen to implement the slew rate limiter.



Design Notes

1. The gain stage op-amp and slew rate limiting op amp should both be checked for stability.
2. Verify that the current demands for charging or discharging C_1 plus any load current out of U_2 will not limit the voltage swing of U_2 .

Design Steps

1. Set slew rate and choose a standard value for the feedback capacitor, C_1 .

$$C_1 = 470\text{nF}$$

$$\text{SR} = 20 \frac{\text{V}}{\text{s}}$$

2. Choose the value of R_2 to set the capacitor current necessary for the desired slew rate.

$$\text{SR} = \frac{I_{C_1}}{C_1}$$

$$20 \frac{\text{V}}{\text{s}} = \frac{I_{C_1}}{470\text{nF}} \text{ where } I_{C_1} = 9.4 \mu\text{A}$$

Gain stage op amp $V_{\text{sat}} = \pm 14.995$ (typical)

$$I_{C_1} = \frac{V_{\text{sat}}}{R_2}$$

$$9.4 \mu\text{A} = \frac{14.995\text{V}}{R_2}, \text{ so } R_2 = 1.595 \text{ M}\Omega \approx 1.6 \text{ M}\Omega \text{ (Standard Value)}$$


3. Compensate feedback network for stability. R_1 adds a pole to the $1/\beta$ network. This pole should be placed so that the $1/\beta$ curve levels off a decade before it intersects the open loop gain curve (200 Hz, for this example).

$$f_p = \frac{1}{2\pi \times R_1 \times C_1} = 200\text{Hz}$$


$$200\text{Hz} = \frac{1}{2\pi \times R_1 \times 470\text{nF}}, \text{ so } R_1 = 1.693 \text{ k}\Omega \approx 1.69\text{k}\Omega \text{ (Standard Value)}$$

Design Simulations

Transient Simulation Results

 

AC Simulation Results

 

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See the circuit SPICE simulation file [SBOC508](#).

See [TIPD140](#).

Design Featured Op Amp

OPA192	
V_{cc}	4.5 V to 36 V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	5 μ V
I_q	1 mA/Ch
I_b	5 pA
UGBW	10 MHz
SR	20 V/ μ s
#Channels	1, 2, and 4
OPA192	

Design Alternate Op Amp

TLV2372	
V_{CC}	2.7 V to 16 V
V_{inCM}	Rail-to-rail
V_{out}	Rail-to-rail
V_{os}	2 mV
I_q	750 μ A/Ch
I_b	1 pA
UGBW	3 MHz
SR	2.1 V/ μ s
#Channels	1, 2, and 4
TLV2372	

Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from February 1, 2018 to February 4, 2019

Page

- Downscale the title and changed title role to 'Amplifiers'. Added links to circuit cookbook landing page and SPICE simulation file..... **1**

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2023, Texas Instruments Incorporated