

**Analog and Mixed-Signal Products**

# **Analog Applications Journal**

**First Quarter, 2004**



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

### Mailing Address:

Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

# Contents

<b>Introduction</b> .....	4
<b>Data Acquisition</b>	
<b>Two-channel, 500-kSPS operation of the ADS8361</b> .....	5
Texas Instruments Application Report SLAA164 presented a basic method of interfacing the ADS8361 to the TMS320C6711™ DSP Starter Kit. The purpose of this article is to expand on the fundamentals presented in that application report and to explore 2- and 4-channel operation of the ADS8361 with two multichannel buffered serial ports (McBSPs). The information presented in this article can be applied to any TMS320™ series DSP with two or more McBSPs.	
<b>ADS809 analog-to-digital converter with large input pulse signal</b> .....	8
The ADS809 is a 12-bit, 80-MHz analog-to-digital converter that offers many performance features using a uniform or non-uniform clock. This article explores over-range and input step-response performance of the ADS809, including bench test data.	
<b>Power Management</b>	
<b>LED-driver considerations</b> .....	14
Many portable applications require backlight LED-driver solutions. This article covers various LED-driver techniques and typical circuit examples for current control, PWM dimming, overvoltage protection, and evaluating load disconnects.	
<b>Interface</b>	
<b>Estimating available application power for Power-over-Ethernet applications</b> .....	18
The recently approved IEEE 802.3af Power-over-Ethernet standard is gaining wide industry acceptance. The application designer is faced with a need both to simplify power delivery to the application and to limit how much power is available to the application's functional circuits. This article discusses the reality of how much power is available and tools to maximize it.	
<b>The RS-485 unit load and maximum number of bus connections</b> .....	21
The TIA/EIA-485 (RS-485) standard defines a unit load and confines bus configurations to 32. This article explains the unit-load concept and how it relates to the maximum number of bus connections. Fractional unit-load devices, such as the 1/8-unit-load SN65HVD21 and SN65HVD06, allow up to 256 devices on a single bus segment.	
<b>Amplifiers: Op Amps</b>	
<b>Op amp stability and input capacitance</b> .....	24
This article explores the effects of capacitance on stability in both internally compensated and externally compensated amplifiers.	
<b>Integrated logarithmic amplifiers for industrial applications</b> .....	28
This article describes the operation and architecture of integrated log amps and provides two application examples using the LOG112 and LOG2112.	
<b>Index of Articles</b> .....	33
<b>TI Worldwide Technical Support</b> .....	36

**To view past issues of the**  
***Analog Applications Journal*, visit the Web site**  
**[www.ti.com/sc/analogapps](http://www.ti.com/sc/analogapps)**

# Introduction

*Analog Applications Journal* is a collection of analog application articles designed to give readers a basic understanding of TI products and to provide simple but practical examples for typical applications. Written not only for design engineers but also for engineering managers, technicians, system designers and marketing and sales personnel, the book emphasizes general application concepts over lengthy mathematical analyses.

These applications are not intended as “how-to” instructions for specific circuits but as examples of how devices could be used to solve specific design requirements. Readers will find tutorial information as well as practical engineering solutions on components from the following categories:

- Data Acquisition
- Power Management
- Interface
- Amplifiers: Op Amps

Where applicable, readers will also find software routines and program structures. Finally, *Analog Applications Journal* includes helpful hints and rules of thumb to guide readers in preparing for their design.

# Two-channel, 500-kSPS operation of the ADS8361

By Tom Hendrick (Email: t-hendrick@ti.com)

*Data Acquisition Applications*

## Introduction

The ADS8361 is a member of the Texas Instruments (TI) motor control products family of serial analog-to-digital converters (ADCs). The ADS8361 is a 2+2-channel, 16-bit upgrade for the 2+2-channel, 12-bit ADS7861. Its 3.3- to 5-V digital interface is ideally suited for use with the entire TMS320 series of digital signal processors from TI.

The device features two independent 500-kSPS ADC channels, each with its own sample-and-hold circuits and serial data output pin. A user-controllable multiplexer (MUX) allows simultaneous sampling of two 2-channel pairs (4 total channels) at 250 kSPS.

## Hardware pins

The ADS8361 features three hardware pins (M0, M1, and A0) that select various operating modes (see Table 1).

Mode I allows for 2-channel operation at speeds of up to 500 kSPS by utilizing both conversion channels. Mode II reduces the maximum throughput to 250 kSPS by using a single serial output pin (OUTA) to present the simultaneously sampled data from channel pairs Ax and Bx. Toggling the address pin A0 controls the selection of channel pair 0 or 1.

Modes III and IV allow the sequential output of both simultaneously sampled channel pairs A0 and B0, followed by A1 and B1. Since Mode III uses both serial outputs A and B, the maximum throughput can be maintained at 250 kSPS. Mode IV presents all 4 converted channels at the OUTA pins, with a maximum throughput of 125 kSPS.

## Single McBSP operation

With the interface method presented in Reference 1, applications that do not require simultaneous sampling but do need two fast, independent ADCs can benefit from the ADS8361's 2- $\mu$ s conversion time. An external MUX or bus

switch between the serial outputs would allow 1- to 4-channel operation of channel A or B through a single multichannel buffered serial port (McBSP). Each channel can be independently operated at 500 kSPS. This method would require some sort of control over the state of one or more of the hardware pins M0, M1, and A0, adding additional logic to the design.

Applications with 2 channels and simultaneous-sampling rates of 250 kSPS or less also can use a single McBSP. Hardware pins M0 and M1 can be fixed at ground and  $V_{CC}$ , with A0 controlling the channel pairs to be converted (Mode II). This method uses the internal MUX to switch the conversion results from the A and B channels through OUTA. Tying both M0 and M1 to  $V_{CC}$  permits 4-channel, simultaneous-sampling applications to be realized. It also allows sequential presentation of two simultaneously sampled channel pairs, 4 channels in all (Mode IV), for applications needing sampling rates of 125 kSPS or less.

If a second McBSP is available, 2- and 4-channel, simultaneous-sampling operation can be realized with no additional "glue logic" required, at 500-kSPS throughput per channel for 2 channels and 250-kSPS for 4 channels.

## Dual McBSP operation

The simultaneous conversion properties of the ADS8361 allow conversion data from channels Ax and Bx to be presented to the OUTA and OUTB pins at the same time. Both channels use the same conversion start (CONVST) signal and the same conversion clock so that data skew between A and B outputs is minimized.

To achieve full-speed, 2- and 4-channel operation, the transmitter portion (CLKX, FSX and DX lines) of one McBSP can be used to control the conversion speed, timing, and channel selection of the ADS8361. The ADS8361's serial data outputs, along with clock and frame sync

**Table 1. Operating modes of ADS8361 hardware pins**

MODE	HARDWARE PINS			2-CHANNEL/ 4-CHANNEL OPERATION	DATA ON SERIAL OUTPUTS	CHANNELS CONVERTED	TOTAL THROUGHPUT (kSPS)
	M0	M1	A0				
I	0	0	0	2-channel	A and B	A0 and B0	500
	0	0	1	2-channel	A and B	A1 and B1	500
II	0	1	0	2-channel	A only	A0 and B0	250
	0	1	1	2-channel	A only	A1 and B1	250
III	1	0	X	4-channel	A and B	Sequential	250
IV	1	1	X	4-channel	A only	Sequential	125

return, are then fed to the receiver portions of two McBSPs as shown in Figure 1.


To enhance the control of the ADS8361 further, the unused transmitter section of the second McBSP can be configured as GPIO and connected to the control pins M0, M1, and A0 of the ADS8361. For simultaneous, 2-channel operation at a 500-kSPS-per-channel conversion rate, all that is required is a single GPIO line to toggle A0.

## Software interface

A project database for this article was developed and compiled with Code Composer Studio™ version 2.20. The most involved portion of writing the code for this simple interface was programming the McBSP. If you wish to receive the project file used in this example, please feel free to send an email to [datconvapps@list.ti.com](mailto:datconvapps@list.ti.com) with the title of this article as the subject.

Since the two converters in the ADS8361 share a common interrupt, conversion clock, and conversion start mechanism, the software requirements for the DSP are quite simple. The first McBSP is configured to transmit a frame sync pulse to act as the conversion start signal. FSR<sub>A</sub>, DX<sub>A</sub> (Serial Data A), and CLKR<sub>A</sub> are returned to the first McBSP. The ADS8361's BUSY pin acts as an interrupt to the DSP, which in turn reads the serial data. When the second serial output of the ADS8361 is used, FSR, CLKR, and Serial OUTB are returned to the receiver of the second McBSP. This enables the user to configure the transmitter portion as GPIO to control channel 0 or channel 1 selection of the ADS8361 without the use of additional decode circuits.

**Figure 1. Hardware interface example**

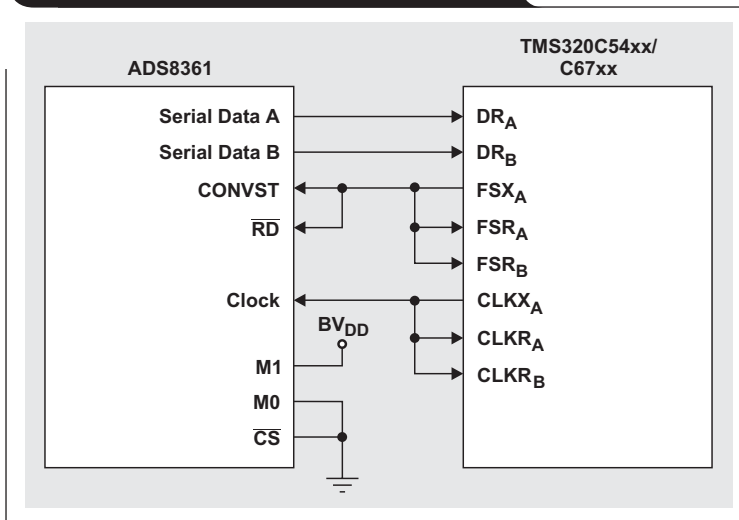

## Create a .CDB file

Code Composer Studio's graphical user interface for the DSP/BIOS™ configuration (.CDB file) and Chip Support Libraries (CSL) have made it easier than ever to write programs and set up the McBSP.

The first step in creating a project that accommodates the ADS8361 with two McBSPs is to create a .CDB file, then add it to the project. This process creates a .CMD file for the linker, which also needs to be added to the project. Additional DSP/BIOS files are created too, which are added to the project automatically when the .CDB file is loaded. All necessary files and libraries are loaded automatically, based on the DSP/BIOS configuration options set.

By expanding the CSL tab in the .CDB file, the user gains access to the McBSP Configuration Manager. A McBSP configuration is added, and the desired values for clock speed, etc., are set. Once the first configuration is done, it is simply highlighted, copied, and pasted. This creates two copies of the same configuration, each with its own name.

## McBSP settings

The McBSPs are configured as shown in the sidebar at left.

The McBSP is programmed as a serial port in nonstop clock mode (or DSP mode). Frame sync and serial clock signals are output pins. The receiver is set for 16-bit transfers with a 2-bit delay on data receive. The frame sync (FSX1) is generated by the sample-rate generator and is used for both the  $\overline{RD}$  and CONVST signals on the ADS8361 by jumper W2 on the evaluation module (EVM).

```

MCBSP_Config mcbSPCfg0 = {
    0x0000, /* Serial Port Control Register 1 */
    0x0220, /* Serial Port Control Register 2 */
    0x0060, /* Receive Control Register 1 */
    0x0000, /* Receive Control Register 2 */
    0x0060, /* Transmit Control Register 1 */
    0x0005, /* Transmit Control Register 2 */
    0x0109, /* Sample Rate Generator Register 1 */
    0x3014, /* Sample Rate Generator Register 2 */
    0x0000, /* Multichannel Control Register 1 */
    0x0000, /* Multichannel Control Register 2 */
    0x2a00, /* Pin Control Register */
};
MCBSP_Config mcbSPCfg1 = {
    0x0000, /* Serial Port Control Register 1 */
    0x0200, /* Serial Port Control Register 2 */
    0x0060, /* Receive Control Register 1 */
    0x0000, /* Receive Control Register 2 */
    0x0000, /* Transmit Control Register 1 */
    0x0000, /* Transmit Control Register 2 */
    0x010e, /* Sample Rate Generator Register 1 */
    0x3013, /* Sample Rate Generator Register 2 */
    0x0000, /* Multichannel Control Register 1 */
    0x0000, /* Multichannel Control Register 2 */
    0x0a00, /* Pin Control Register */
};

```

In the sample code (see sidebar), the ADS8361 is running at 469 kSPS with a serial clock of 9.375 MHz. The C6711 DSP Starter Kit clocks the C6711 DSP at 150 MHz. The sample-rate generator clock source is half the CPU clock, or 75 MHz. The 9.4-MHz clock on CLKX is achieved by setting the CLKGDV bit field in the sample-rate generator register to 8. The formula for calculating the serial clock is

$$\text{CLOCK} = \frac{\frac{\text{CPUCLOCK}}{2}}{\text{CLKDIV} + 1}$$

By this equation, each clock's cycle is approximately 106.6 ns, triggering a frame-sync pulse every 20 serial clock cycles, which gives a sample rate of 468 kHz. The frame period (FPER) field, in the sample-rate generator register, is where the 20-cycle period is set.


### Software flow

The software presented in this article reads 1024 samples at 469 kHz continuously. As selected in the configuration tool, all the register and peripheral programming is done during initialization. DSP/BIOS pre-initializes all the McBSP registers and other DSP registers before arriving in the main function. As a result, the main function simply enables the interrupt service routine and McBSP1; from then on, the DSP/BIOS and McBSP receive ISR do all the work. When a McBSP1 receive interrupt occurs, `McBSP1Rcv_ISR` reads the port and stores the data in `ad_buffer`. When the buffer is full, it resets the index, `i`, to the beginning and flushes the receive buffer (see Figure 2).

### Conclusion

An EVM is available that provides a platform to demonstrate the functionality of the ADS8361 ADC with various TI DSPs and microcontrollers, while allowing easy access to all analog and digital signals for customized end-user applications. For more information on the EVM, visit [www.ti.com/sc/device/ADS8361](http://www.ti.com/sc/device/ADS8361) and select Development Tools.

**Figure 2. Software flow chart**

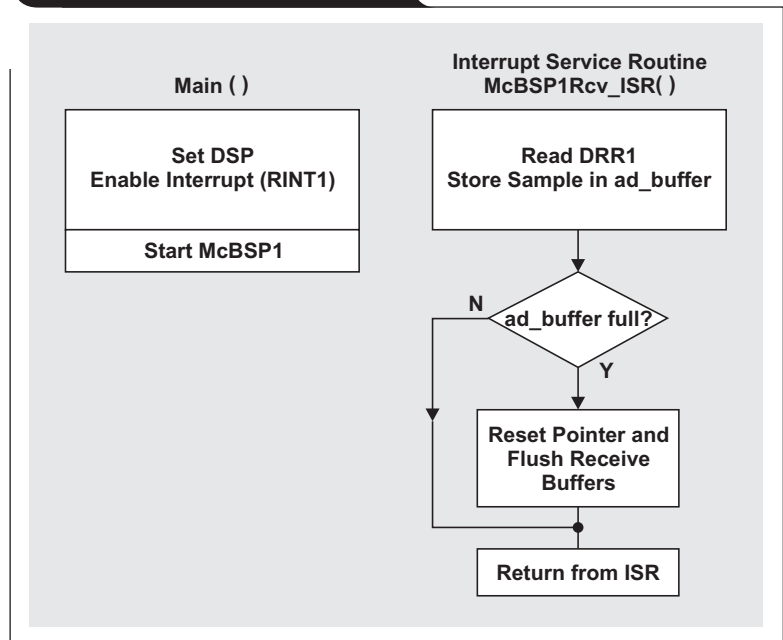

### References

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. Tom Hendrick, "Interfacing the ADS8361 to the TMS320C6711 DSP," Application Report	..slaa164
2. "Dual, 500kSPS, 16-Bit, 2 + 2 Channel, Simultaneous Sampling Analog-to-Digital Converter," ADS8361 Data Sheet	.....sbas230
3. "TMS320C6711, TMS320C6711B, TMS320C6711C Floating-Point Digital Signal Processing," Data Sheet	.....sprs088
4. "TMS320C6000 DSP/BIOS User's Guide"	.....spru303
5. "TMS320 Cross-Platform Daughtercard Specification, Revision 1.0," Application Report	.....spra711

### Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)

Replace *partnumber* with ADS7861, ADS8361 or TMS320C6711

# ADS809 analog-to-digital converter with large input pulse signal

By Hui-Qing Liu (Email: liu\_hui-qing@ti.com)

Applications Engineer, High-Speed Products

## Introduction

The Texas Instruments (TI) ADS809 is a 12-bit, 80-MHz pipeline analog-to-digital converter (ADC). It has high speed, high resolution, high-input bandwidth, and a high signal dynamic range. Its many other good features include good signal-to-noise-ratio (SNR), good linearity, low jitter, flexible clocking, an over-range indicator (OVR), “data valid” output, three-state output, an internal or external reference, and a single-ended or differential input configuration. It can be used for broadband communications, test equipment, medical instrumentation, CCD imaging, and other fast-ADC applications.


In these applications the input analog signal applied to the ADS809 varies and may be a DC, AC, narrow band, wide band, or pulse signal with a large amplitude. The sampling clock used for these applications can be up to 80 MHz with a uniform or non-uniform clock phase. Different applications require different critical features of the ADS809. In some conventional sampling applications, the ADC input analog signal is smooth with a large amplitude, and the SNR and spurious-free dynamic range (SFDR) are critical; while in some small-signal sampling applications, the SFDR and full-scale (FS) step-acquisition time are not as critical. However, the FS step-acquisition time is critical in large-signal sampling applications, especially when the sampling clock has to be high-frequency with a non-uniform phase and the analog input pulse signal is large (for example, 2 V). In this case the input signal has a sharp edge with a large voltage amplitude, and the pulse edge could be very close

to the sampling clock edge due to sampling clock phase variations. If the ADC does not have fast step response for the signal settling, the next ADC sample after the pulse edge will be unstable, which is undesirable. Therefore it is critical for the ADC to have a fast settling time when a large input pulse signal is sampled. Similarly, when the input pulse is over full-scale range (FSR), it is important for the ADC to have a fast over-range recovery time. This is tough for any ADC in applications where the input pulse signal is large and sampling speed is very high with a non-uniform clock phase. However, the ADS809 works well with this type of application. This article presents the results of recent lab tests that further prove the ADS809’s fast step response with a large, FS input pulse. The test data also covers the ADS809’s response to over-range conditions.

## Over-FSR performance of the ADS809

The ADS809’s over-voltage condition is defined as the input voltage in excess of its maximum linear conversion range. The voltage FSR of the ADS809 can be set as  $2 V_{p-p}$ ,  $1.5 V_{p-p}$ ,  $1 V_{p-p}$ , or another range based on the internal or external voltage reference configuration. For single-ended input, the maximum voltage at the ADS809 input pin is +FS ( $\frac{1}{2}$  FSR above 2.5-V common-mode voltage), and the minimum voltage at input is -FS ( $\frac{1}{2}$  FSR below 2.5-V common-mode voltage). For differential input, +FS is  $\frac{1}{4}$  FSR above 2.5-V common-mode voltage, and -FS is  $\frac{1}{4}$  FSR below 2.5-V common-mode voltage. For the input voltage over FSR, the ADS809 has control features that include 12-bit data-code control and an OVR.

Figure 1. Output of ADS809 with input pulse over FSR at 66-MHz sampling clock

 



The digital output code of the ADS809 is straight offset binary or binary two's complement. In straight offset binary format, when the input voltage is maximum, the ADS809 outputs all 12 data bits as 1s (digital value = 4095); and when the input voltage is minimum, the ADS809 outputs all 0s. When the input voltage is 0 (at the middle of the FSR) or only the common-mode voltage, the ADS809 outputs 100000000000 (digital value = 2048). The ADS809 will output data from 0 to 4095 when the input voltage is from  $-FS$  to  $+FS - LSB$ . The ADS809 will output 4095 when the input voltage is above  $+FS$ , and will output 0 when the input voltage is below  $-FS$ .

The ADS809 output-code control was tested with the ADC sampling clock at 66 MHz and the input differential pulse amplitude at 2.8 V (0.8 V over FSR). The test result shows that the ADS809 has stable output-code control and quick over-range recovery from the input pulse signal. This is shown in Figure 1. The ADS809 samples 255 digital output samples at 66 MSPS from an over-FS input pulse. The data shows that all the bits are stable at 1 when the input pulse signal is over  $+FS$ , and stable at 0 when the input pulse signal is under  $-FS$ . The data also shows that when the input pulse signal goes from over FS to under FS or vice versa, the output of the ADS809 tracks the input step change and stays at 4095 or 0 without any miss code or bit flip.

Another over-FSR control feature of the ADS809 is an OVR output pin, which indicates over-range conditions. The OVR output is a function of the reference voltage and


the output data bits, so it has the same pipeline delay as the output data bits. The OVR is logical low if the input signal is within the FSR, and logical high if the input signal is over  $+FS$  or under  $-FS$ . The OVR changes from logical low to high, or logical high to low, immediately following the change of the output data. When this happens, the input voltage changes from inside the FSR to outside the FSR or vice versa. When the input signal continues under or over FS, the OVR always remains high. When the input signal changes from under FS to over FS or vice versa, the OVR changes from high to low for  $\frac{1}{2}$  CLK period, then changes to high again. In other words, the OVR outputs a negative pulse at the transition of the input voltage from over FS to under FS or vice versa (see Figure 2). The output's most significant bit (MSB) pin is flipped based on the over-FS input pulse. It is high when the input pulse is over FS and low when the input pulse is under FS. The OVR pin outputs a negative pulse that appears half of the sampling clock period earlier than the transition at the MSB pin.

### FS step response of ADS809 and measurement method


The FS step response or step-acquisition time of the ADS809 is defined as the time for the input signal to settle or for the internal sample-and-hold (S/H) circuit to track the input signal with a certain accuracy (for example, 0.1% FS) after the FS step signal is applied to the ADS809. The ADS809 settling time of a FS step signal is 5 ns, which is typically within 0.1% FS and is the minimum required interval between the input step edge and the next sampling clock edge.

The fast step response of the ADC is important in applications with a non-uniform sampling clock, because the variation of the sampling clock phase can cause a phase change between the input pulse and the sampling clock. This is shown in Figure 3, where the rising edge of the clock samples the input pulse signal; and the time,  $t_s$ , between the input step edge and the next rising edge of the sampling clock changes with the sampling clock phase change. When  $t_s$  is less than the ADC's minimum value, the ADC will take an unstable sample from the unsettled input signal, which is undesirable.

**Figure 2. OVR of ADS809 with input pulse over FS**

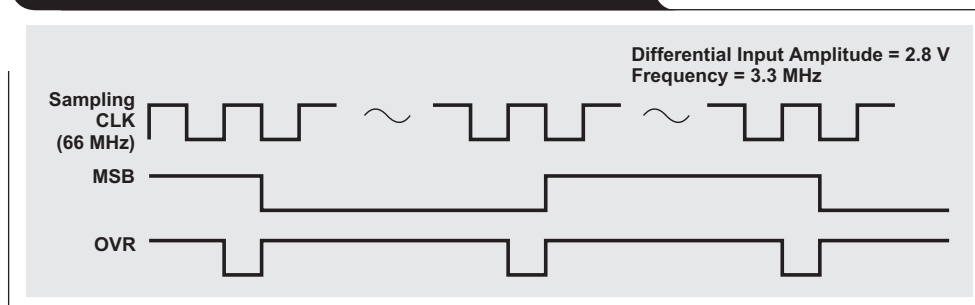

**Figure 3. The input step appears during the clock's tracking time because of clock phase variation**

 


There are two ways to evaluate the step response. One is measuring the time,  $t_s$ , shown in Figure 3. Another is measuring the relative tracking time,  $t_D$ , of the sampling clock shown in Figure 4.

In the first method, the step signal (pulse edge in this case) is applied to the input of the S/H circuit directly during the tracking phase. By delaying the input pulse or sampling clock, we can find the minimum  $t_s$ , the first stable sample location after the pulse edge, where the pulse signal level has been recovered with the accuracy specified in the data sheet. This minimum  $t_s$  is the step response of the ADC. In this method, highly accurate measurement is needed. The signal input path of the ADC should be clean. Large external input capacitance from the board can cause signal step edge distortion, and poor board layout with source impedance mismatch may cause energy reflection or ringing. The probe capacitance of the oscilloscope is also a concern. The shape of the step edge and the detailed timing between the step signal and the ADS809 sampling clock should be carefully measured, including the ADS809 aperture time.

The second and simpler method of step-response evaluation is to measure the clock's tracking time,  $t_D$ , shown in Figure 4. In this method the clock's tracking edge appears after the input signal step edge. The clock's tracking edge triggers the ADS809 S/H circuit, changing the previous voltage at the sampling capacitor to the current voltage of the input pulse. The step-response time of the ADS809 S/H circuit should be the same as in the first method (measuring  $t_s$ ) due to the same RC constant. If the tracking time during  $t_D$  measurement is too short, the first sample after the step signal will be unstable. The minimum tracking

**Figure 4. The input step does not appear during the clock's tracking time**

 


time of the ADC should be less than or close to half of the sampling clock cycle at the maximum speed specified.


### Bench test of ADS809 step response

A real bench test was performed to determine the ADS809 step response with the method shown in Figure 3 (measuring  $t_s$ ). The basic test block diagram of the ADS809 is shown in Figure 5. The ADS809 was configured with an internal reference, a differential analog input with 2-V FSR, a differential clock input, and an external 2.5-V common-mode voltage for the analog input, with no added load on the common-mode (CM) pin except normal bypass capacitance.

The differential analog input of the ADS809 was a pulse from the pulse generator with a frequency of 3.3 MHz and an amplitude of 2.92 to 2.08 V (high to low) at each analog input, near FSR. This input produced the digital output values of 3770 and 300 (high and low), including a small amount of DC offset. The input pulse's transition from high to low was used as the step signal in the bench test. The single-ended, 66-MHz sampling clock from the pulse generator was converted differentially through a differential translator. A Tektronix logic analyzer (TLA) was used to collect the digital output of the ADS809 to determine whether the sample was stable. After the input step signal, the digital value of the first sample should be 300, within an accuracy

**Figure 5. Basic test block diagram for ADS809 step response**

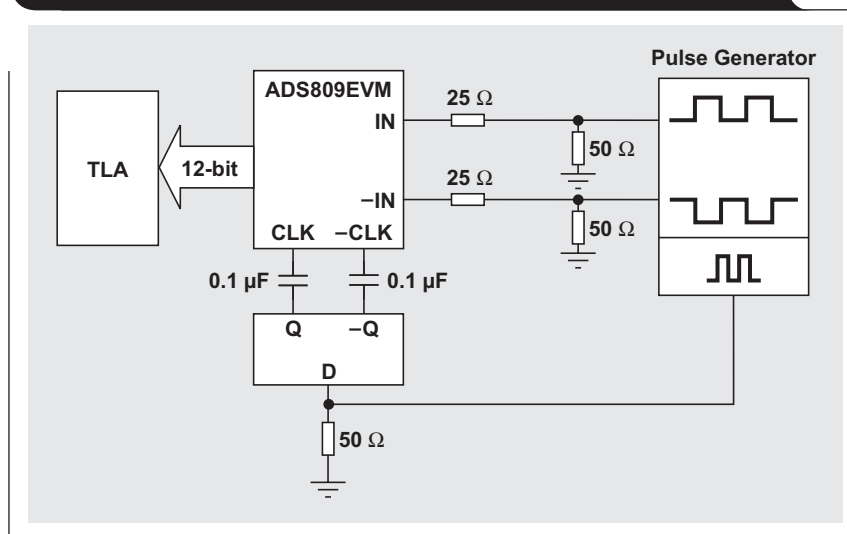

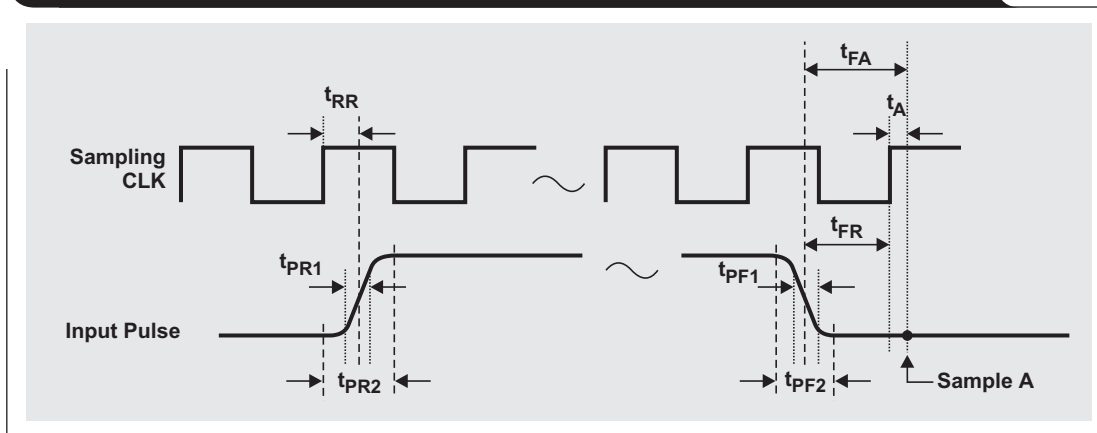**Figure 6. Timing measurement of sampling clock and input pulse at zero delay**

of 0.1% FS, if the time interval between the step signal and the clock sampling edge is 5 ns or more as specified.

Three measurements were necessary in this bench test: aperture delay; input signal timing between the sampling clock and the input pulse; and the digital output of the ADS809 with input pulse delay.

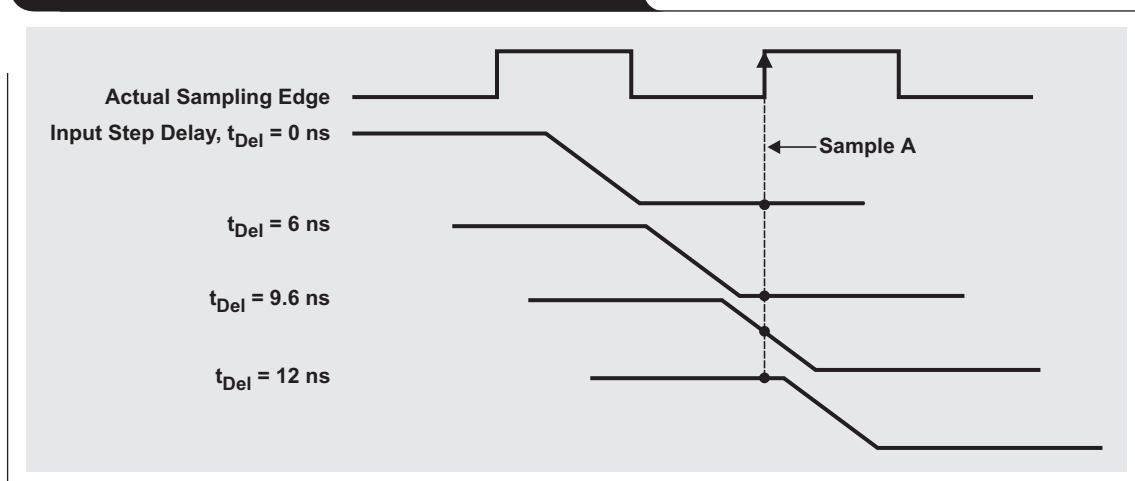
The aperture delay,  $t_A$ , is the time from the rising edge of the sampling clock to the time when the sampling actually happens (see Figure 6). The data sheet provides only a typical value for  $t_A$  (3 ns). In the bench test the aperture delay was found by measuring the MSB and the time from the rising edge of the sampling clock to the falling edge of the pulse.

Figure 6 shows the measurement of the input signal timing between the sampling clock and the input pulse at zero delay. This measurement provides pulse edge information and a time reference for the input signal delay. The measurement was taken by Tektronix scope at the ADS809 input and clock input pins. The measurement data is shown in Table 1.

**Table 1. Bench test measurement data**

PARAMETER	MEASURED VALUE
Input pulse rising time (10% to 10%), $t_{PR1}$	1.1 ns at analog input pin IN
Input pulse falling time (10% to 10%), $t_{PF1}$	0.8 ns at analog input pin IN
Input pulse rising time (0.01% to 0.01%), $t_{PR2}$	2.7 ns at analog input pin IN
Input pulse falling time (0.01% to 0.01%), $t_{PF2}$	2.8 ns at analog input pin IN
Clock rising edge to pulse rising edge (50% to 50%), $t_{RR}$	8.5 ns at pins CLK and IN
Pulse falling edge to clock rising edge (50% to 50%), $t_{FR}$	6.59 ns at pins CLK and IN

After the input timing was measured, the input pulse delay,  $t_{Del}$ , was up to 12 ns in steps of 1 ns or less. When  $t_{Del}$  was 0, the time from the input pulse falling edge to the next rising edge of the sampling clock,  $t_{FR}$ , was 6.59 ns; and Sample A, the first sample after the high-to-low transition of the input pulse, was located at 9.59 ns ( $t_{FR} + t_A = t_{FA}$ ) from the pulse falling edge (see Figure 6). With the increase of the input pulse delay,  $t_{FR}$  decreased and Sample A moved close to the falling edge of the input pulse. When the pulse delay was more than 9.5 ns, Sample A moved to the left side of the falling edge of the input pulse (see Figure 7).

**Figure 7. Sample A moves with step signal delay**

Sample A was collected by TLA, and its digital data is shown in Table 2. The Sample A output value of the ADS809 should be 300 (within an accuracy of  $\pm 0.1\%$  FS) if  $t_{FR}$  is 2 ns or longer. In other words, Sample A is settled if the time  $t_{FA}$  ( $t_{FR} + t_A$ ), from the falling edge of the input pulse to the actual sampling time of Sample A, is 5 ns or longer. For example, the digital value of Sample A is 299 when  $t_{FA}$  is 5.59 ns, and 300 when  $t_{FA}$  is about 9.59 ns, due to the input signal tracked by the ADS809 at these times. Sample A is unstable (the digital value is out of the range of  $300 \pm 0.1\%$  FS) if  $t_{FA}$  is shorter than 5 ns. This is shown in Table 2 and Figure 8. For example, when  $t_{FA}$  is 3.59 ns, the digital value of Sample A is 358, which is significantly higher than 300, because the input signal has not recovered its low level after the high-to-low step of the input pulse. When  $t_{FA}$  is between 0.09 and  $-0.01$  ns (see Table 2), Sample A hits the center of the falling edge or the middle scale of the ADS809. At this point  $t_{FR}$  reflects the aperture time of the ADS809. Continually delaying the input pulse eventually moves Sample A into the high level of the input pulse. When  $t_{FA}$  is less than  $-1.41$  ns, the digital value of Sample A is about 3770 (see Figure 8). By this measurement, the step-acquisition time of the ADS809 is evaluated as 5 ns, within an accuracy of 0.1% FS, which matches the data sheet.


The test data introduced here includes a small error from the input timing measurement by the scope. There are actually many factors that can affect this type of measurement. The main one to point out here is that different input signal path conditions will have different digital values of Sample A at the same time space,  $t_{FA}$ . This could lead to a misinterpretation of the step-response time measurement. During the measurement, three different input signal path conditions were tested. In Condition 1, a 100-pF capacitor

**Table 2. Digital value of Sample A versus input signal delay**

$t_{Del}$ (ns)	$t_{FR}$ (ns)	$t_{FA}$ (ns)	A (digital value)
0	6.59	9.59	300
1	5.59	8.59	299
2	4.59	7.59	301
3	3.59	6.59	296
4	2.59	5.59	299
5	1.59	4.59	315
6	0.59	3.59	358
7	-0.41	2.59	480
8	-1.41	1.59	739
9	-2.41	0.59	1277
9.5	-2.91	0.09	1902
9.6	-3.01	-0.01	2195
10	-3.41	-0.41	3334
11	-4.41	-1.41	3768
12	-5.41	-2.41	3767

was added at the input of the ADS809 on the EVM board. In Condition 2, this 100-pF capacitor was taken off the board. In Condition 3, the 100-pF capacitance was taken off the board and a 25- $\Omega$  damping resistor was added on the input path of the board. All three conditions ran with the sampling clock at 66 MHz, the input pulse at 3.3 MHz, the differential pulse amplitude at 1.68 V, and a zero delay to all input signals. The test data shows significant variation of the digital value of Sample A. Condition 1 produced the largest variation, mainly caused by edge distortion of the input pulse due to the external capacitor. Condition 3 produced the smallest variation, mainly caused by board layout and mismatch of the signal source impedance.

**Figure 8. Step-response measurement data**

 

## Conclusion

The ADS809, with 12-bit resolution and an 80-MSPS sampling speed, is used not only for conventional but also for nonconventional ADC sampling applications. An example of the latter is an ADC with a high-speed sampling clock with a non-uniform sampling phase that converts a large-amplitude input pulse signal. Such an application requires fast ADC settling time. This article has provided some test data based on the conditions of this type of application, including an over-FS control function and FS step-response measurement. The test data shows that the ADS809 has stable output-code control and stable OVR output when the input pulse signal is over 2-V FS. The ADS809 can convert a 2-V FS input pulse signal at an 80-MHz sampling rate and produce a stable output code. An actual bench test of the ADS809's FS step response was conducted; and the test method, procedure, and test results have been presented. The test data shows that the ADS809 has a FS step-acquisition time of 5 ns. It also indicates that the ADS809 has a large input dynamic range, a high-input bandwidth, and a fast, FS step response, making it suitable for large-signal sampling applications.

## References

For more information related to this article, you can download an Acrobat Reader file at [www-s.ti.com/sc/techlit/litnumber](http://www-s.ti.com/sc/techlit/litnumber) and replace "litnumber" with the **TI Lit. #** for the materials listed below.

Document Title	TI Lit. #
1. "12-Bit, 80MHz Sampling Analog-to-Digital Converter," ADS809 Data Sheet . . . . .	sbas170
2. Mikael Gustavsson, J.J. Wikner, and N.N. Tan, <i>CMOS Data Converters for Communications</i> (Kluwer Academic Publishers, 2000).	—

## Acknowledgments

Special thanks go to Bryan McKay for his work on the test board and to Wallace Burney for his article review.

## Related Web sites

[analog.ti.com](http://analog.ti.com)  
[www.ti.com/sc/device/ADS809](http://www.ti.com/sc/device/ADS809)

# LED-driver considerations

By Michael Day (Email: m-day@ti.com)

Applications Manager, Portable Power Products

Many of today's portable electronics require backlight LED-driver solutions with the following features: direct control of current, high efficiency, PWM dimming, over-voltage protection, load disconnect, small size, and ease of use. This article discusses each of these features and how they are achieved, and concludes with a typical circuit that implements each of these features.

## Direct control of current

LEDs are current-driven devices whose brightness is proportional to their forward current. Forward current can be controlled in two ways. The first method is to use the LED V-I curve to determine what voltage needs to be applied to the LED to generate the desired forward current. This is typically accomplished by applying a voltage source and using a ballast resistor as shown in Figure 1. However, this method has several drawbacks. Any change in LED forward voltage creates a change in LED current. With a nominal forward voltage of 3.6 V, the LED in Figure 1 has 20 mA of current. If this voltage changes to 4.0 V, which is within the specified voltage tolerance due to temperature or manufacturing changes, the forward current drops to 14 mA. This 11% change in forward voltage causes a much larger 30% change in forward current. Also, depending upon the available input voltage, the voltage drop and power dissipation across the ballast resistor waste power and reduce battery life.

The second, preferred method of regulating LED current is to drive the LED with a constant-current source. The constant-current source eliminates changes in current due to variations in forward voltage, which translates into a constant LED brightness. Generating a constant-current source is fairly simple. Rather than regulating the output voltage, the input power supply regulates the voltage across a current-sense resistor. Figure 2 shows this implementation. The power-supply reference voltage and the value of the current-sense resistor determine the LED current. Multiple LEDs should be connected in a series configuration to keep an identical current flowing in each LED. Driving LEDs in parallel requires a ballast resistor in each LED string, which leads to lower efficiency and uneven current matching.

## High efficiency

Battery life is critical in portable applications. For an LED driver to be useful, it must be efficient. An efficiency measurement of an LED driver differs from that of a typical power supply. An efficiency measurement of a typical power supply is defined as the output power divided by

Figure 1. Voltage source with ballast resistor


 


Figure 2. Constant-current source for driving LEDs

 

the input power. With an LED driver, the output power is not the parameter of interest. What is important is the amount of input power required to generate the desired LED brightness. This is easily determined by dividing the power in the LEDs by the input power. Defining the efficiency in this way means that the power dissipated in the current-sense resistor contributes to the power lost in the

supply. The following equation shows that smaller current-sense voltages contribute to higher-efficiency LED drivers.

$$\text{Efficiency} = \frac{P_{\text{LED}}}{P_{\text{LED}} + P_{\text{Supply\_Losses}} + P_{\text{Current\_Sense}}}$$

Figure 3 shows that choosing a power supply with a 0.25-V reference voltage versus a supply with a 1-V reference voltage improves efficiency. A supply with a lower current-sense voltage is more efficient regardless of input voltage or LED current. With all else being equal, a lower reference voltage significantly improves efficiency and extends battery life.


## PWM dimming

Many portable LED applications require dimming. In applications such as LCD backlighting, dimming provides brightness and contrast adjustment. Two types of dimming are available: analog and PWM. With analog dimming, 50% brightness is achieved by applying 50% of the maximum current to the LED. Drawbacks to this method include LED color shift and the need for an analog control signal, which is not usually readily available. PWM dimming is achieved by applying full current to the LED at a reduced duty cycle. For 50% brightness, full current is applied at a 50% duty cycle. The frequency of the PWM signal must be above 100 Hz to ensure that the PWM pulsing is not visible to the human eye. The maximum PWM frequency depends upon the power-supply startup and response times. To provide the most flexibility and ease of integration, the LED driver should be able to accept PWM frequencies as high as 50 kHz.

## Overvoltage protection

Operating a power supply in a constant-current mode requires overvoltage protection. A constant-current supply generates a constant output current regardless of load. If the load resistance increases, the supply's output voltage also must increase to supply a constant current. If the supply encounters an excessive load resistance, or if the load is disconnected, the output voltage can increase above the voltage rating of the IC or of the other discrete circuit components. Several overvoltage protection schemes are available for constant-current LED drivers. One scheme is to place a zener diode in parallel with the LEDs. This limits the output voltage to the zener's breakdown voltage plus the supply's reference voltage. During an overvoltage condition, the output voltage increases to the point where the zener breaks down and begins to conduct. The output current flows through the zener, then through the current-sense resistor to ground. The supply continues to generate the constant output current while the zener limits the maximum output voltage. A more preferred method of overvoltage protection is to monitor the output voltage and shut down the supply when the overvoltage trip point is reached. Shutting down the supply under an overvoltage condition reduces power dissipation and extends battery life in the event of a fault.

**Figure 3. LED driver efficiency versus current sense voltage**

 

## Load disconnect

An often overlooked feature in an LED-driver supply is load disconnect. Load disconnect electrically removes the LEDs from the power supply when the supply is disabled. This is important in two situations: shutdown and PWM dimming. As shown in Figure 2, during shutdown of a boost converter, the load is still connected to the input through the inductor and catch diode. Since the input voltage is still connected to the LEDs, a small current continues to flow, even when the supply is disabled. Even small leakage currents significantly reduce battery life during extended periods of off time. Load disconnect is also important during PWM dimming. During the off time of the dimming period, the supply is disabled; but the output capacitor is still connected across the LEDs. Without load disconnect, the output capacitor discharges through the LEDs until the dimming pulse turns the supply on again. Since the capacitor is partially discharged at the beginning of each dimming cycle, the supply must charge up the output capacitor at the beginning of each dimming cycle. This creates a spike of inrush current during each dimming cycle. The inrush current lowers system efficiency and creates voltage transients on the input bus. With load disconnect, the LEDs are removed from the circuit so there is no leakage current when the supply is disabled, and the output capacitor remains fully charged during PWM dimming. A load-disconnect circuit is best implemented by placing a MOSFET between the LEDs and the current-sense resistor. Placing the MOSFET between the current-sense resistor and ground creates an additional voltage drop that manifests itself as an error in the output-current setpoint.

## Ease of use

Ease of use is a relative concept. A circuit's ease of use not only encompasses the complexity of the initial design but also involves any future effort required to modify the circuit quickly and reuse it for other programs that may have slightly different requirements. In general, hysteretic controllers are very easy to use. A hysteretic controller

eliminates the need for the complicated frequency compensation required in a classical power-supply design. While frequency compensation is not difficult for an experienced power-supply designer, most novice power-supply designers find it tedious. Since the optimal compensation changes for different input and output conditions, a classical power-supply design does not lend itself to quick modifications for different operating conditions. A hysteretic controller is inherently stable and requires no changes as input and output conditions change.

### Small size

Small size is an important feature for portable circuitry. Several factors contribute to the size of the circuit components. One factor is switching frequency. Higher switching frequencies allow the use of smaller passive components. A modern LED driver intended for portable applications should be able to switch at frequencies of up to 1 MHz. Switching at frequencies greater than 1 MHz is not typically recommended because it does not significantly reduce circuit size; but it does reduce efficiency and lower battery life due to the higher switching losses. Integration of features into the control IC is the single most important factor that contributes to a small-driver solution. If all the features

described in the preceding paragraphs were implemented with discrete components, the board area required would take up more space than the power supply itself. Integrating these features into the control IC significantly reduces the overall driver size. A second but equally important benefit of feature integration is a reduction in the total solution cost. Implemented discretely, all desirable features in an LED driver can add an additional sixty to seventy cents in component cost. When integrated into the control IC, these features typically add only pennies to the cost of the IC.

### Practical solution

The TPS61042 is an excellent example of a modern LED-driver control IC. Figure 4 is a block diagram of the TPS61042 with a highly integrated control IC. Q1 is a low-resistance, integrated power FET. The low resistance of this component contributes to an extremely high efficiency. The 0.25-V reference voltage reduces losses in the current-sense resistor. PWM dimming is easily implemented with this IC by applying a PWM signal to the CTRL pin at frequencies as high as 50 kHz. Q2 implements the integrated load-disconnect circuitry. Since it is integrated, this circuitry is perfectly synchronized to the PWM dimming frequency.

**Figure 4. Block diagram of TPS61042 with high level of integration**


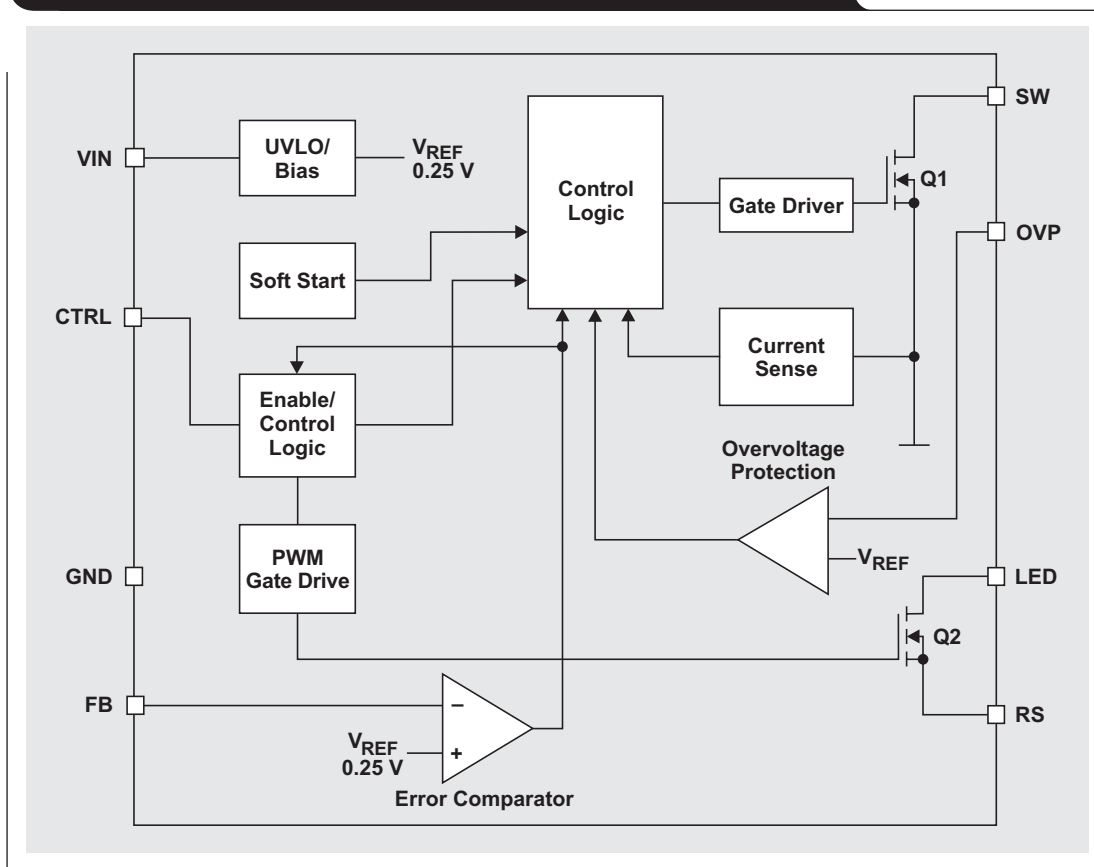


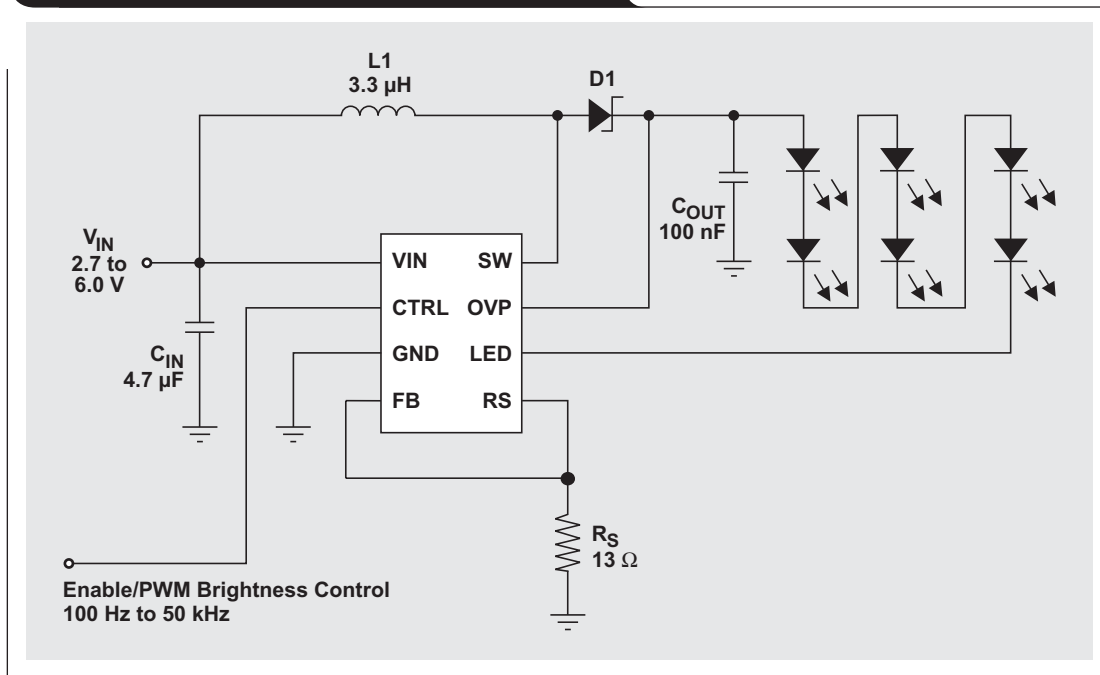

Figure 5. Typical TPS61042 LED-driver solution



Overvoltage protection is also integrated into the IC. Most seasoned power-supply designers will note the absence of an error amplifier and any associated compensation circuitry. This function has been replaced by the error comparator. This IC operates with hysteretic-control feedback topology, which requires no compensation and is inherently stable. Not shown in the block diagram is the physical size of the IC. All control circuitry and features are integrated into a  $3\text{ mm} \times 3\text{ mm}$  QFN package. Figure 5 shows a typical LED-driver application that drives four LEDs with 20 mA of forward current and operates from an input voltage range of 1.8 to 6.0 V. The entire circuit consists of the control IC,

two small ceramic caps, an inductor, a diode, and a current-sense resistor. This small circuit shows the high level of integration that is achieved with today's LED drivers. The primary power-supply functions and the secondary features such as load disconnect, overvoltage protection, and PWM dimming have been implemented with a control IC and five small surface-mount passive components.

### Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/TPS61042](http://www.ti.com/sc/device/TPS61042)

# Estimating available application power for Power-over-Ethernet applications\*

By **Martin Patoka** (Email: mpatoka@ti.com)

Systems Engineer

## Introduction

Many existing Ethernet devices are being converted from wall-adaptor power sources to utilize the newly released IEEE 802.3af Power-over-Ethernet (PoE) standard. Power-system efficiency formerly was not much of an issue with a wall adapter—but PoE changes that. Applications whose functional circuits begin to draw power in the 10-W range need close control of their power usage. This article helps the designer determine how much power is available when an application operates from a PoE source.

First we will determine the net power available once the functions required by the 802.3af standard are performed. Then a method of modeling the usual DC/DC converters to compute the power available for the applications circuits will be presented, with two example topologies for comparison. The modeling process allows the designer to identify topology and technology issues before the first circuit is designed. In this discussion, application circuits are considered to be everything in the powered device (PD) except the PoE front end and DC/DC converters.

## PoE front-end losses

Figure 1 is a basic block diagram that shows the interconnection of the power-source equipment (PSE) through the

DC/DC converter and application circuits. Calculations yielding the results in Table 1 assume that the PSE output (44 V minimum) is connected through 20  $\Omega$  of cable into a PD. The PD front end has a transformer (1  $\Omega$  total, with

**Table 1. Analysis of PoE distribution and front-end losses**


PARAMETERS	MIN	TYP	MAX
PSE output (V)	44	—	57
Distribution resistance ( $\Omega$ )	—	—	20
Source power (W)	—	—	15.4
PD average current (A)	—	—	0.35
<b>Constants</b>			
Diode forward drop (V)	—	0.8	—
Transformer resistance ( $\Omega$ )	—	—	1
PD-controller switch resistance ( $\Omega$ )	—	1	—
PD-controller bias power (A)	—	0.0012	—

LOSS SOURCE	LOSS (W)	AVAILABLE POWER (W)
		15.40**
Distribution	2.45	12.95
Input diode	0.56	12.39
Input transformer	0.06	12.33
PD-controller switch	0.12	12.21
PD-controller bias	0.04	12.16

\*\*Total PoE power available

\*An edited version of this article was published December 3, 2003, on PlanetAnalog.com, an *EE Times* online community.

**Figure 1. Basic PoE block diagram**

 

0.5  $\Omega$  each side to the center tap), a full-wave bridge, and a hot-swap controller (or PD controller) with a 1- $\Omega$  switch (FET) in series.

There is a maximum of 12.16 W available for PD functional circuits. The 802.3af standard defines the 2.45-W worst-case cable loss, and the input diode bridge dominates the additional front-end losses of 0.78 W.

## Modeling of power-conversion stage

Simple modeling techniques allow the designer to understand the effects of different topology and technology choices before an actual design is done. Simple efficiency assumptions give quick, qualitative results to allow topology comparison and optimization. The end results will be only as good as the assumptions, so the designer should always allow some margin by specifying the available power below these results.

First, let's look at the baseline of a single-stage conversion to one output voltage. A single 3.3-V output converter at 90% efficiency will yield an available output power of  $0.9 \times 12.16 = 10.9$  W. Although the 90% efficiency may be viewed as optimistic, it does provide a baseline for comparison to other topologies.

Next we will estimate the output power available from a more complex power supply. A simple modeling technique is used to study how the topology and technology for each regulator affect output power. Output voltages of +5 V at 0.2 A, 3.3 V at 2 A, 2.5 V at 0.25 A, and 1.8 V at 0.25 A are assumed. These add up to a reasonable 9.6 W.

Figure 2 shows two possible supply architectures and technology choices. Topology 1 represents adaptation of an

existing appliance design that had a 12-V wall adapter, which was replaced with a 48-V to 12-V front end.

Topology 2 attempts to maximize the available power.

To evaluate the model, start at the right-most regulators, calculating their loss and total input power, and then use these results to evaluate the next regulator to the left. For simplification, assume 90% efficiency for a switcher and no bias current for linear regulators. These calculations are summarized for the regulator types as follows.

### Definitions

$I_{OUT}$  = application load current

$P_{IN\_Next\_Stage}$  = power drawn by a downstream converter or linear regulator

### Linear regulator stage

$$P_{OUT} = (V_{OUT} \times I_{OUT}) + P_{IN\_Next\_Stage}$$

$$P_{IN} = V_{IN} \times \frac{P_{OUT}}{V_{OUT}}$$

$$P_{Loss} = P_{IN} - P_{OUT}$$

### Switching regulator stage

$$P_{OUT} = (V_{OUT} \times I_{OUT}) + P_{IN\_Next\_Stage}$$

$$P_{IN} = \frac{P_{OUT}}{\text{Efficiency}}$$

$$P_{Loss} = P_{IN} - P_{OUT}$$

Figure 2. Alternative supply topologies

 


Table 2. Topology 1 model

MODEL COMPONENTS	OUTPUT VOLTAGE (V)	REGULATOR TYPE	INPUT VOLTAGE (V)	REGULATOR EFFICIENCY (%)	APPLICATION CURRENT (A)	ADDITIONAL OUTPUT LOAD (W)	COMPUTED INPUT POWER (W)	STAGE LOSS (W)
Chain 1	1.8	Linear	2.5	—	0.25	0.00	0.63	0.18
	2.5	Linear	3.3	90	0.25	0.63	1.65	0.40
	3.3	Switcher	12	90	<b>1.83</b>	1.65	<b>8.54</b>	<b>0.85</b>
Chain 2	5	Linear	12	—	0.2	0.00	2.40	1.40
First-stage input power	—	Switcher	48	90	0	<b>10.94</b>	<b>12.16</b>	<b>1.22</b>
Total loss								<b>4.05</b>
Apparent efficiency = 67%								
Available output power = 8.11 W								

Table 3. Topology 2 model

MODEL COMPONENTS	OUTPUT VOLTAGE (V)	REGULATOR TYPE	INPUT VOLTAGE (V)	REGULATOR EFFICIENCY (%)	APPLICATION CURRENT (A)	ADDITIONAL OUTPUT LOAD (W)	COMPUTED INPUT POWER (W)	STAGE LOSS (W)
Chain 1	1.8	Linear	2.5	—	0.25	0.00	0.63	0.18
	2.5	Switcher	3.3	90	0.25	0.63	1.39	0.14
	3.3	—	—	100	2.532	1.39	9.74	0.00
Chain 2	5	Linear	6	—	0.2	0.00	1.20	0.20
First-stage input power	—	Switcher	48	90	0	10.94	12.16	1.22
Total loss								1.73
Apparent efficiency = 86%								
Available output power = 10.43 W								

Using data in Table 2, let's go through the calculations for the Topology 1 model shown in Figure 2. Looking at the lower branch, Chain 1, data in Table 2, start with the 1.8-V regulator's input power and loss; notice that there is no next-stage power. The 2.5-V regulator is computed similarly, with the output power now comprised of the 0.25 A to the load multiplied by 2.5 V, plus the 1.8-V regulator's input power previously computed. The 3.3-V switching regulator's input power is the total output power divided by the efficiency of this stage (0.9%). The power loss of the 3.3-V regulator is still the input power minus the output power. The upper branch is computed in a like manner with the Chain 2 data. The 48-V to 12-V regulator's parameters are calculated like those of the 3.3-V regulator, where the total output power is the sum of the upper- and lower-branch input powers. To get a handle on the topology's performance, the individual losses are summed and the apparent efficiency is computed as

$$\text{Efficiency} = 1 - \frac{\text{Total\_Losses}}{\text{Input\_Power}}$$

The available output power in Table 2 is the input power minus all the computed individual losses.

Topology 1's input power exceeds the amount available. To provide a more interesting result, the 3.3-V load shown was adjusted until the input power was 12.16 W. Bold values in Table 2 reflect the reduction of the 3.3-V supply load from 2 A to 1.83 A.

Topology 2 is modeled with data in Table 3 much as Topology 1, with a small wrinkle. A dummy 3.3-V regulator is modeled with an efficiency of 1 for proper totaling of the power and loss.

The efficiency of 90% used for the 48-V to 3.3-V converter in Topology 2 is a fairly optimistic number for a practical, synchronous output-rectifier circuit.

## Conclusion

After the 802.3af standard functions are considered, 12.16 W is the maximum power available for other electronics, including regulator losses.

The effects of topology and technology choices for PoE applications are quite startling. Topology 1 makes only 8.11 W available to the application's circuits, while Topology 2 makes 10.43 W available. This is an increase of 28%. The baseline single-output converter provided 10.9 W, so all the processing represented by the additional three outputs in Topology 2 cost only 0.47 W! Using a diode output converter (85% efficiency) instead of a synchronous rectifier for the 3.3-V converter drops the available power by 0.61 W.

This modeling technique allows the designer to calculate available output power rapidly based on topology and technology choices. The designer can use this information to trade off available power, complexity, and cost.

## Related Web site

[analog.ti.com](http://analog.ti.com)

# The RS-485 unit load and maximum number of bus connections

By Kevin Gingerich (Email: k-gingerich@ti.com)

High-Performance Analog/Interface Products

## Introduction

TIA/EIA-485 (RS-485) is a popular electrical standard for data interchange over a multipoint differential bus. Multipoint buses are three or more stations connected to a common transmission medium that allow bidirectional data communication between any two nodes. Figure 1 schematically shows an example of a multipoint bus.

Maintaining a practical limit to the output-drive capability of an RS-485 driver requires that a limit be imposed on the steady-state load presented by the bus. This in turn constrains the input resistance of stations and, ultimately, the maximum number of connections.

RS-485 does not specify the maximum number of bus connections. Instead, the standard defines the steady-state electrical load presented by a bus connection in unit loads. The following paragraphs explain the unit load and how it is used to determine the maximum number of nodes connected to an RS-485 bus segment.

## The unit load

TIA/EIA-485-A defines a unit load as a 15-k $\Omega$  resistor connected to a -3- or 5-V source (see Figure 2). The -3-V case applies for positive input current, and the 5-V case applies for negative bus current. The definition and model are valid for input voltages from -7 to 12 V to account for driver outputs between 0 and 5 V, with up to  $\pm 7$  V of common-mode noise voltage between a driver and receiver.

Figure 2. Electrical model of 1 unit load


 



Figure 1. Schematic of an example multipoint bus

 

The number of unit loads (nUL) presented by any proposed connection to the RS-485 bus is then determined as the ratio of its measured input current and the current of 1 unit load. Since the current of 1 unit load is a function of voltage, the input current must be measured and the ratio determined throughout the entire -7- to 12-V input-voltage range, with the highest ratio determining the unit-load rating.

Figure 3 shows a hypothetical example where the measured input current of a circuit is nonlinear. It can be shown (see sidebar on next page) that, at its maximum value, the ratio of the measured and unit-load current is equal to the ratio of the slopes of the two functions and lies on a line with an intercept at -3 V for positive current and 5 V for negative current. Conceptually, this amounts to rotating a line pivoted at  $I = 0$  mA and  $V = -3$  V until it is tangent to the curve of measured positive current versus

Figure 3. Example unit-load analysis

 

**Proof that nUL is the slope ratios**

Let the input current of a unit load be defined by  $f_1(V)$  and the measured circuit by  $f_2(V)$ . The number of unit loads (nUL) is then

$$nUL = \frac{f_2(V)}{f_1(V)}$$

for  $-7V < V < 12V$ .

The maximum nUL occurs when the first derivative equals zero, or

$$\frac{d}{dV} \frac{f_2(V)}{f_1(V)} = \frac{1}{f_1(V)} \frac{d}{dV} f_2(V) - \frac{f_2(V)}{f_1^2(V)} \frac{d}{dV} f_1(V) = 0.$$

$$\frac{d}{dV} f_2(V) = \frac{f_2(V)}{f_1(V)} \frac{d}{dV} f_1(V).$$

$$\frac{f_2(V)}{f_1(V)} = \frac{\frac{d}{dV} f_2(V)}{\frac{d}{dV} f_1(V)} \tag{1}$$

Therefore, the maximum nUL is equal to the ratio of the first derivative (slopes) of the input-current function.

The following equations are used to solve for the unit-load circuit:

$$f_1(V) = \frac{V+3}{15} \text{ mA or}$$

$$f_1(V) = \frac{V-5}{15} \text{ mA and } \frac{d}{dV} f_1(V) = \frac{1}{15} \text{ mho.}$$

Substituting these into Equation 1 yields

$$\frac{f_2(V)}{\frac{V+3}{15}} = \frac{\frac{d}{dV} f_2(V)}{\frac{1}{15}}$$

$$f_2(V) = \frac{d}{dV} f_2(V) \times (V+3)$$

or

$$\frac{f_2(V)}{\frac{V-5}{15}} = \frac{\frac{d}{dV} f_2(V)}{\frac{1}{15}}$$

$$f_2(V) = \frac{d}{dV} f_2(V) \times (V-5).$$

These line equations mean that the input current where the nUL is maximum lies on a line that intersects the points  $I = 0 \text{ mA}$  and  $V = -3 \text{ V}$  for positive current and  $I = 0 \text{ mA}$  and  $V = 5 \text{ V}$  for negative current.


voltage. For negative currents, the line is pivoted at  $I = 0 \text{ mA}$  and  $V = 5 \text{ V}$ . In our example, the maximum ratio occurs at measured input currents of  $0.65 \text{ mA}$  and  $-0.72 \text{ mA}$ .

The ratio and nUL may be calculated by dividing the measured value at the intercept by the value derived from solving the unit-load circuit; or, for convenience, the lines are often extended to the 12- or -7-V intercept. Since the slopes for 1 unit load and the tangential lines are constants, their ratios are constant and may be determined at any voltage. By definition, the current into 1 unit load at 12 V will be 1 mA, and at -7 V will be -0.8 mA. These values are respectively divided into the current-intercept values of the tangential lines at 12 V and -7 V, and the maximum number determines the nUL for the circuit. In the example, the input-current-versus-voltage characteristics of the hypothetical circuit result in 1.22 unit loads.

**Maximum unit loads**



The minimum output-drive capability of a standard RS-485 driver is established in clause 4.2.3 of TIA/EIA-485-A, which specifies a differential output voltage of at least 1.5 V with a common-mode load. Figure 4 shows a schematic of this test circuit.

**Figure 4. Differential output voltages with a common-mode load**

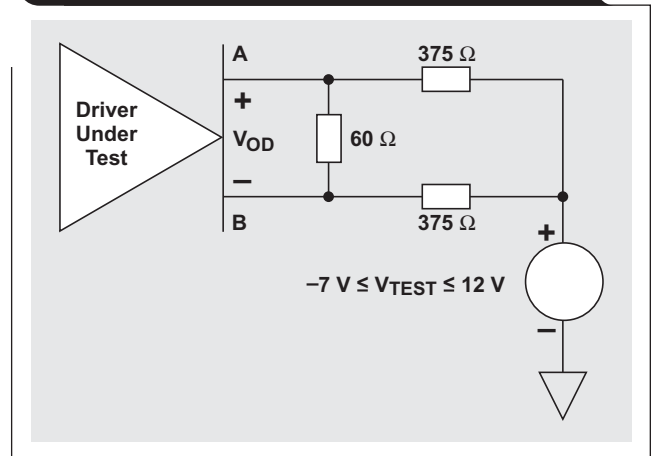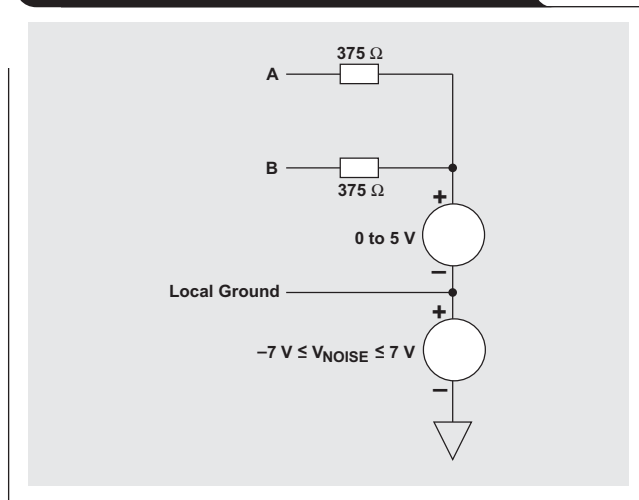 

The 375-Ω resistors are certainly part of the common-mode load. What is not obvious is that the test voltage of -7 to 12 V actually represents a ±7-V common-mode noise source and a 0- to 5-V local supply voltage at the load(s). This is important in that the local supply is included in the unit-load determination for this test circuit. Figure 5 shows the common-mode test circuit with the insertion of a “local” ground used as the reference for the unit-load calculation.

To determine the unit load of this test circuit, we plot the input-current-versus-voltage function between point A or B and the “local” ground of Figure 5, then apply the unit-load definition described earlier. This is done in Figure 6, and we find that the current at the intercepts of the tangential lines is 32 mA at  $V = 12 \text{ V}$ , and -32 mA at  $V = -7 \text{ V}$ . By definition, this represents 32 unit loads and 40 unit loads, respectively.

**Figure 5. Physical representation of the test circuit****Figure 6. Unit load of common-mode test circuit**

The reader may have noted the discrepancy between the unit-load model and the driver test circuit. One can only assume that this was an oversight or compromise by the authors of TIA/EIA-485. As tested, the unit-load model should consist of a 12-k $\Omega$  resistor to a 0- to 5-V source rather than 15 k $\Omega$  to a -3- to 5-V source. If we use this modified definition, the differential output voltage with common-mode load test of TIA/EIA-485-A ensures that a standard driver will work with 32 unit loads.

### Using the unit load

Other than a refresher on analytic geometry, of what use is the unit-load concept to the designer of a data-interchange circuit? Primarily, it provides a single standard parameter for calculating the maximum number of connections and for specifying the input characteristics of possible line circuits. Since we know a driver will support 32 unit loads in a standard bus configuration, we need only divide 32 by the total number of nodes (N) to derive the maximum

unit-load rating for each of the line circuits. For example, if 48 nodes were to be connected, each line receiver or transceiver would have to have no more than 0.67 unit loads (32/48).

The unit load also can be useful when nonstandard bus configurations are implemented. In addition to the differential termination of the differential signal pair, pull-up and pull-down resistors often are connected to the lines to provide a known bus state when all of the connected drivers are idle. The resistor values used for this fail-safe termination are usually around 1 k $\Omega$ . If so, this termination would consume 12 unit loads (12 mA at 12 V) out of the budget of 32 unit loads. This leaves 20 unit loads for the line circuits; and, if 48 nodes are still to be connected, each of the line circuits must now be no more than 0.42 unit loads (20/48).

Texas Instruments (TI) offers numerous options, some of which are shown in Table 1, for supporting a large number of RS-485 bus connections.

**Table 1. Fractional unit-load devices from TI**

UNIT LOADS	MAXIMUM NUMBER OF DEVICES ON A SINGLE BUS SEGMENT	PART NUMBER
0.5	64	SN65HVD05
		SN65HVD10
		SN65HVD20
		SN65HVD23
0.25	128	SN65LBC182
		SN65LBC184
0.125	256	SN65HVD06
		SN65HVD07
		SN65HVD08
		SN65HVD11
		SN65HVD12
		SN65HVD21
		SN65HVD22
		SN65HVD24

### Conclusion

The unit load is a relative parameter that provides a basis for determining the maximum number of connections to an RS-485 bus segment or for specifying the input characteristics of line circuits. A standard RS-485 driver will handle 32 unit loads that could consist of 256 devices with a rating of  $\frac{1}{8}$  unit load.

### Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/partnumber](http://www.ti.com/sc/device/partnumber)

Replace *partnumber* with SN65HVD05, SN65HVD06, SN65HVD07, SN65HVD08, SN65HVD10, SN65HVD11, SN65HVD12, SN65HVD20, SN65HVD21, SN65HVD22, SN65HVD23, SN65HVD24, SN65LBC182 or SN65LBC184

# Op amp stability and input capacitance

By Ron Mancini (Email: [rmancini@ti.com](mailto:rmancini@ti.com))

Staff Scientist, Advanced Analog Products

## Introduction

Op amp instability is compensated out with the addition of an external RC network to the circuit. There are thousands of different op amps, but all of them fall into two categories: uncompensated and internally compensated. Uncompensated op amps always require external compensation components to achieve stability; while internally compensated op amps are stable, under limited conditions, with no additional external components.

Internally compensated op amps can be made unstable in several ways: by driving capacitive loads, by adding capacitance to the inverting input lead, and by adding in phase feedback with external components. Adding in phase feedback is a popular method of making an oscillator that is beyond the scope of this article. Input capacitance is hard to avoid because the op amp leads have stray capacitance and the printed circuit board contributes some stray capacitance, so many internally compensated op amp circuits require external compensation to restore stability. Output capacitance comes in the form of some kind of load—a cable, converter-input capacitance, or filter capacitance—and reduces stability in buffer configurations.

## Stability theory review

The theory for the op amp circuit shown in Figure 1 is taken from Reference 1, Chapter 6. The loop gain,  $A\beta$ , is critical because it solely determines stability; input circuits and sources have no effect on stability because inputs are grounded for the stability analysis. Equation 1 is the loop-gain equation for the resistive case where  $Z = R$ .

$$A\beta = \frac{aR_G}{R_F + R_G} \quad (1)$$

Beware of Equation 1; its simplicity fools people because they make the assumption that  $A = a$ , which is not true for all cases. Stability can be determined easily from a plot of the loop gain versus frequency. The critical point is when the loop gain equals 0 dB (gain equals 1) because a circuit must have a gain  $\geq 1$  to become unstable. The phase margin, which is the difference between the measured phase angle and  $180^\circ$ , is calculated at the 0-dB point. A typical open-loop-gain curve for the TLV278x family of op amps is used as a teaching example and is shown in Figure 2.

The op amp's open-loop gain and phase ( $a$  in Equation 1) are represented in Figure 2 by the left and right vertical axes, respectively. Never assume that the op amp open-loop gain curve is identical to the loop gain because external components have to be accounted for to get the loop-gain

Figure 1. Equation 1 can be written from the op amp schematic by opening the feedback loop and calculating gain


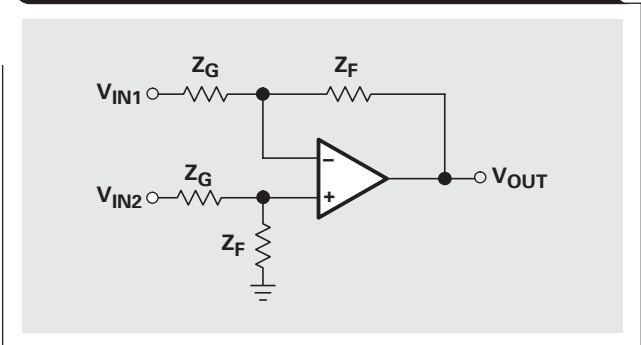


Figure 2. Open-loop-gain/phase curves are critical stability-analysis tools

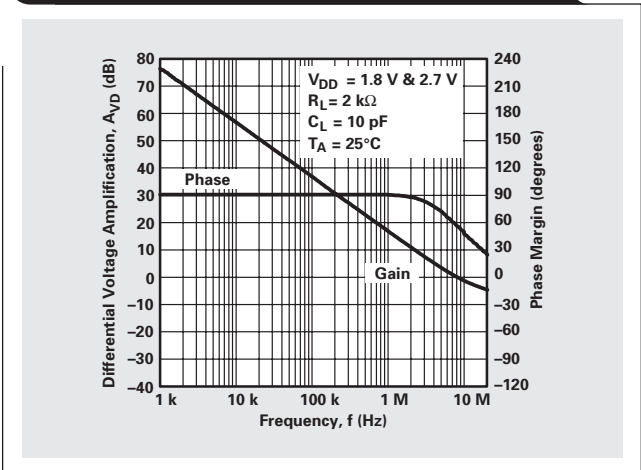


curve. When  $R_F = 0$  and  $R_G = \infty$ , the op amp reduces to a noninverting buffer amp (unity gain) and the loop gain becomes equal to the op amp open-loop gain. We can obtain the buffer phase margin directly from Figure 2 by tracing the gain line down from its vertical intercept (at approximately 78 dB) to where it crosses the 0-dB line at approximately 8 MHz. Then we can trace the 8-MHz line up until it intersects the phase curve, and read the phase margin as approximately  $56^\circ$ . This plot was made with phase margin, but many plots are made instead with phase shift. For plots made with phase shift, the phase shift must be subtracted from  $180^\circ$  to obtain the phase margin.

Now that we have the phase margin, what can we do with it other than to say that the circuit does not oscillate?



Figure 3 is a plot of phase margin and percent maximum overshoot versus a dummy variable, the damping ratio. Enter this plot at a phase margin of  $56^\circ$  and go up to the phase curve intersection. At this point, go horizontally (constant damping ratio) to the intersection of the overshoot curve, and then drop down to read an overshoot of approximately 11%. This plot enables the designer to predict the transient step response from the phase margin, and transient response is a measure of relative stability.

**Figure 3. Phase margin/percent overshoot versus damping ratio**

 

The external resistors come into play when the op amp is configured as an inverting, noninverting, or differential amplifier. When  $R_F = R_G$ , Equation 1 reduces to  $A\beta = a/2$ ; and the vertical intercept for the amplifier reduces from that of the buffer by 6 dB. Although the vertical intercept has changed, the pole location remains constant because gain is not tied to phase. The 0-dB crossover frequency changes to approximately 3 MHz because of the gain drop; the phase margin increases to approximately  $87^\circ$ ; and the percent overshoot is negligible. Notice that the buffer is less stable than any of the amplifier circuits and that, at the same phase margin, the inverting gain is  $-1$  while the noninverting gain is 2.


### Added input capacitance and its effect

When input capacitors are added to the circuit (see Figure 4), they cause a pole to occur in the loop gain, as shown in Equation 2.

$$A\beta = \frac{aZ_G}{Z_G + R_F} = \frac{aR_G}{R_G + R_F} \times \frac{1}{R_G \parallel R_F C_{IN} + 1} \quad (2)$$


The input capacitor,  $C_{IN}$ , is the summation of all the inverting input capacitances, and it adds a pole to the loop

**Figure 4. Input capacitance includes IC internal, lead, and PCB capacitance**

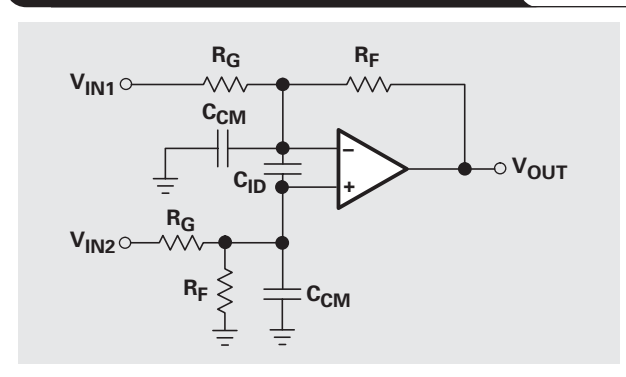

gain. Adding a pole to the loop gain does not always change the stability because the pole location and its added phase shift may not affect the phase margin. Consider the case where the pole is located at a very high frequency—say, 100 MHz—for the TLV278x. Notice from Figure 2 that the op amp open-loop gain is so low above 10 MHz that the overall gain can never equal 1, so the added pole is of no value. The case where the pole is located at a very low frequency—say, 0.001 Hz—is harder to calculate because the low-frequency response is not shown in Figure 2. However, we can be sure that the phase shift is close to zero at this frequency. A pole with a frequency intercept that low would cause the gain to be down 120 dB at 1 kHz, and again the loop gain would be less than 1 before the phase margin went to zero. An op amp open-loop gain/phase plot that shows low-frequency response is shown in Figure 5. Notice that the phase shift (not phase margin in this plot) approaches zero at low frequencies. In addition, notice that the phase shift approaches  $180^\circ$  at very high frequencies and that the gain is given in ratios rather than in decibels.

**Figure 5. Gain/phase plots of medium-frequency op amps show frequency extremes**

 


The DC gain in Equation 2 remains the same as it was without an input capacitor, but the pole is added at  $f = 1/(2\pi R_F \parallel R_G C_{IN})$ . If this pole occurs at approximately 3 MHz, it reduces the gain by 3 dB and adds a 45° phase shift at that frequency. Using  $C_{IN} = 20$  pF and  $R_G \parallel R_F = 2.7$  kΩ yields a 3-dB frequency of 2.94 MHz, so it is reasonable to assume a pole frequency of 3 MHz. The gain in Figure 4 must be moved down 9 dB to account for the resistors and the pole. The new 0-dB crossover frequency is 2 MHz, and the phase margin at 2 MHz (as shown in Figure 4) is 89°. The pole phase shift of 45° must be subtracted from the curve phase margin to obtain the final circuit phase margin; thus  $\phi = 89^\circ - 45^\circ = 44^\circ$ . The percent overshoot corresponding to the 44° phase margin is 24.45%. Adding  $C_{IN}$  reduces the phase margin from 87° in the purely resistive case to 44° with input capacitance. If the op amp initially had less than a 44° phase margin, the circuit would be unstable rather than just bouncy.

If the resistor values were larger than 5.4 kΩ, the pole would move down in frequency. The exact pole location that does the most damage to stability is hard to calculate because the phase is a nonlinear tangent function. In this case, it is best to move the resistors down in value to about 1 kΩ, thus moving the pole to 8 MHz and reducing the added phase shift to about 14°. A second problem crops up in the noninverting configuration because  $C_{ID}$  couples a portion of the input signal to the inverting input. This action reduces the common-mode rejection capability and introduces high-frequency distortion.

The buffer circuit with an input capacitance is shown in Figure 6. Notice that the input capacitance includes the output capacitance and load capacitance in the absence of a feedback resistor, and that the output impedance,  $Z_{OUT}$ , comes into play.

**Figure 6. Input, output, and load capacitors are in parallel in the buffer circuit**

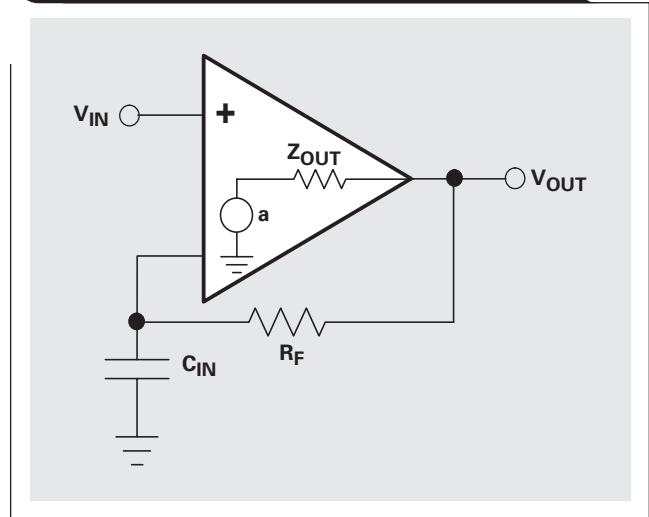


The buffer loop gain is given as

$$A\beta = \frac{a}{(R_F + Z_{OUT})C_{IN} + 1} \tag{3}$$

First, consider the case when  $R_F = 0$ ;  $Z_{OUT}$  is obtained from Figure 7 as 70 Ω at 8 MHz. Assuming that the input, output, and load capacitance is 100 pF, the pole frequency is located at 22.7 MHz; and this pole adds a 19.4° phase shift at the 0-dB crossover frequency. This added phase shift subtracts directly from the previously calculated phase margin of 56° because the pole attenuation doesn't

**Figure 7. Op amp output impedance increases with increasing frequency**

 

occur until after the 0-dB crossover frequency. This circuit has a phase margin of  $56^\circ - 19.4^\circ = 36.6^\circ$ , leading to an overshoot of 33%.

When  $R_F = 1 \text{ k}\Omega$ , the  $R_F C_{IN}$  pole is located at 8 MHz; so it becomes dominant. Under these conditions, the gain curve moves down 3 dB and the phase shift is increased  $45^\circ$ . Moving the gain curve down 3 dB yields an  $80^\circ$  phase margin at  $f = 4 \text{ MHz}$ . Subtracting  $45^\circ$  plus  $19.4^\circ$  from  $80^\circ$  yields a phase margin of  $15.6^\circ$ , and the overshoot increases to approximately 50%. It is obvious that increasing the value of  $R_F$  makes it dominant over  $Z_{OUT}$  and will quickly make the circuit oscillate.

### $C_F$ increases stability

Input and output capacitors always decrease stability. Input capacitors are a pole in the open-loop transfer function, but they are a zero in the closed-loop transfer function. The closed-loop zero increases the circuit (not the op amp) bandwidth, so sometimes input capacitors are added to the circuit to improve high-frequency response.

A capacitor placed in parallel with the feedback resistor,  $C_F$ , introduces a zero into the loop gain:

$$A\beta = \frac{aR_G}{R_F + R_G} \times \frac{R_F C_F + 1}{R_F \parallel R_G (C_F + C_G) + 1} \quad (4)$$

When the closed-loop gain is greater than 1 and  $C_F$  is greater than  $C_G$ , the zero precedes the pole. In this case, which is not unusual, the zero contributes a positive phase shift to the loop-gain plot, causing an increase in stability. The more the zero leads the pole, the more stable the

circuit becomes; but the pole always ends up canceling the zero. The idea is to place the zero so that we achieve the required overshoot and then to accept the pole location. The open-loop zero translates to a closed-loop pole; thus  $C_F$  always decreases high-frequency performance. Optimal performance is gained when the acceptable overshoot is obtained at an acceptable frequency response.

### Conclusion

The addition of input, output, or load capacitance to an op amp circuit decreases stability, which leads to overshoot in the time domain. The stability decrease is worse for a buffer than for other amplifier configurations. Reducing the resistance value that makes up the RC circuit reduces the effect of the capacitance; this effect leads to the rule of thumb that high frequencies and low resistance go together. Input capacitance is easily compensated by adding a feedback capacitor into the circuit. The value of the feedback capacitor should be just large enough to achieve the desired overshoot response, because larger values cause a loss of high-frequency performance.

### Reference

1. Ron Mancini, *Op Amps For Everyone* (Newnes Publishers, 2003). An earlier 2002 edition is available at [www-s.ti.com/sc/techlit/slod006](http://www-s.ti.com/sc/techlit/slod006)

### Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/TLV278x](http://www.ti.com/sc/device/TLV278x)

# Integrated logarithmic amplifiers for industrial applications


By Thomas Kugelstadt (Email: tk@ti.com)  
Senior Systems Engineer, Industrial Systems

Many industrial applications measure physical quantities over a wide dynamic range. These applications use logarithmic amplifiers (log amps) to match a transmitter's dynamic output to the linear input range of a signal gauge. Figure 1 shows a typical signal chain to measure photo currents over a dynamic range of seven decades.

Log amps of the past were built with hybrid techniques. Today's CMOS technology enables the integration of the logging circuit and additional support functions, such as voltage references and uncommitted op amps, into a single chip.

This article describes the operation and architecture of integrated log amps and provides two application examples using the Texas Instruments (TI) LOG112 and LOG2112.

**Figure 1. Matching a sensor's dynamic output to the linear input of a voltmeter**

 

## Operation


A log amp makes use of the logarithmic relationship between the voltage and current of a forward-biased diode. Figure 2 shows the characteristic of the forward current, given by the exponential function

$$I_F = I_{S(T)} \times \left( e^{\frac{V_F}{m \times V_T}} - 1 \right) \tag{1}$$

where  $V_F$  and  $I_F$  are the forward voltage and forward current of the diode, respectively;  $I_S$  is the theoretical reverse-saturation current;  $m$  is a correction factor; and  $V_T$  is the temperature-equivalent voltage. Exchanging the  $x$  for the  $y$  axes and vice versa yields the forward voltage as a logarithmic function of the forward current. Mathematically, this corresponds to solving Equation 1 for  $V_F$ :

$$V_F = m \times V_T \times \ln \left( \frac{I_F}{I_S} + 1 \right) \tag{2}$$

**Figure 2. Diode characteristic in exponential and logarithmic form**

 


For a forward-biased diode, the forward current is larger by far than the reverse current ( $I_F \gg I_S$ ). Thus, Equation 2 simplifies to

$$V_F = m \times V_T \times \ln \frac{I_F}{I_S} \tag{3}$$

A simple log amp whose transfer function satisfies Equation 3 is shown in Figure 3. The op amp operates as an inverting amplifier with a feedback diode. With the diode being virtually anode-grounded, the op amp needs to generate a negative output voltage to forward bias the diode. For a given input current,  $I_{IN}$ , the corresponding output voltage,  $V_{OUT}$ , is

$$V_{OUT} = -m \times V_T \times \ln \frac{I_{IN}}{I_S} \tag{4}$$

**Figure 3. Log amp with diode**

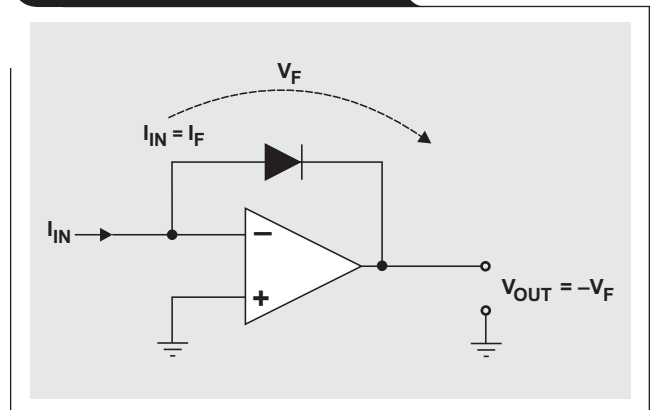

The drawback of this circuit is that  $V_{OUT}$  depends not only on  $I_{IN}$  but also on  $m$ ,  $I_{S(T)}$ , and  $V_T$ , all of which are either current- or temperature-dependent.

- The correction factor,  $m$ , takes into account the deviation between the diode characteristic and Shockley's simplified theory of diodes. However,  $m$  strongly depends on the forward current, thus varying its value between 1 and 2.
- The reverse-saturation current,  $I_S$ , is temperature-dependent. For a constant forward current,  $I_S$  doubles with every 10-K increase in temperature. Thus, for a 100-K rise in temperature,  $I_S$  increases by a factor of 1000.
- The temperature-equivalent voltage,  $V_T = k \times T/e_0$ , increases linearly with temperature. With Boltzman's constant  $k = 1.38 \times 10^{-23}$  J/K, the electron charge  $e_0 = 1.6 \times 10^{-19}$  C, and an ambient temperature of  $T = 296$  K (23°C),  $V_T$  yields

$$V_T = \frac{1.38 \times 10^{-23} \text{ J/K} \times 296 \text{ K}}{1.6 \times 10^{-19} \text{ C}} = 25.5 \text{ mV.}$$

When the circuit operates at a constant temperature, the impact of  $m$  still limits the measurable input range to 1 or 2 decades of acceptable accuracy. To eliminate  $m$ , the diode is replaced by a transistor (Figure 4). Its exponential transfer characteristic in Figure 5 is similar to that of a diode. In contrast to a diode, however, the correction factor equals 1 and simplifies Equation 4 to

$$V_{OUT} = -V_T \times \ln \frac{I_C}{I_{ES}}, \text{ or } V_{BE} = V_T \times \ln \frac{I_C}{I_{ES}}. \quad (5)$$

The input current,  $I_{IN}$ , becomes the collector current,  $I_C$ ; and  $I_S$  becomes the emitter reverse-saturation current,  $I_{ES}$ . The elimination of  $m$  increases the measurable input range to several decades.  $V_{OUT}$ , however, is still temperature-dependent via  $I_{ES(T)}$  and  $V_T$ . Therefore, it is impossible to determine whether a change in  $V_{OUT}$  is caused by the input current or by a change in temperature.

Figure 4. Log amp with transistor


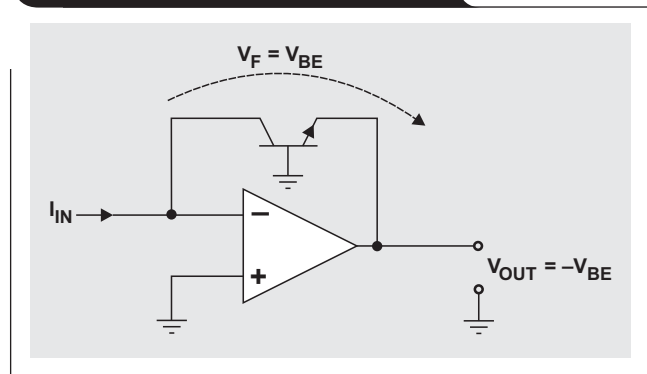



Figure 5. Transistor input characteristic

 

To avoid output changes due to temperature, the temperature-compensated log amp in Figure 6 is required. Here, generating the difference of two logarithms eliminates  $I_{ES}$ . From the previous example, we take the logarithmic relationship between the basis-emitter voltage,  $V_{BE}$ , and the collector current,  $I_C$ , for both transistors,  $Q_1$  and  $Q_2$ :

$$V_{BE1} = V_T \times \ln \frac{I_{C1}}{I_{ES1}}, \text{ and } V_{BE2} = V_T \times \ln \frac{I_{C2}}{I_{ES2}}.$$

Figure 6. Temperature-compensated log amp

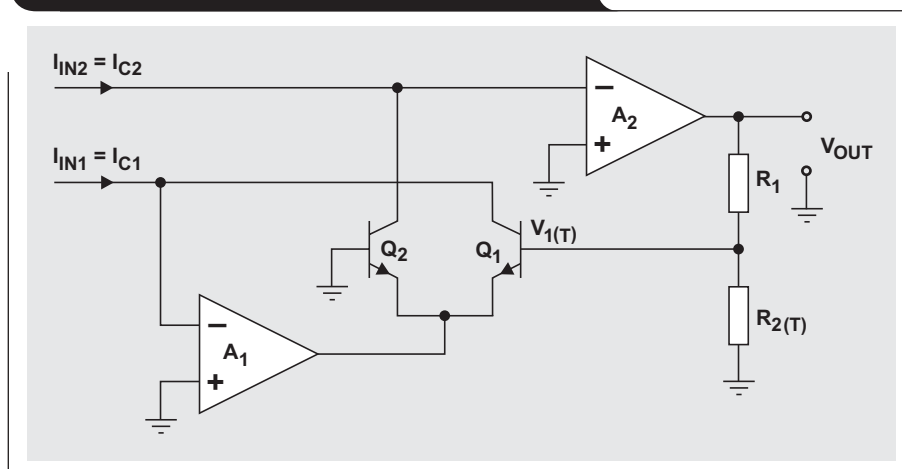

The two logging transistors build a difference amplifier whose output voltage,  $V_1$ , yields the difference of both base-emitter voltages:

$$V_1 = V_{BE1} - V_{BE2} = V_T \times \ln \frac{I_{C1}}{I_{ES1}} - V_T \times \ln \frac{I_{C2}}{I_{ES2}} \quad (6)$$

With matched and isothermal transistors,  $I_{ES1} = I_{ES2} = I_S$ , and Equation 6 simplifies to

$$V_{1(T)} = V_T \times \ln \frac{I_{C1}}{I_{C2}} \quad (7)$$

A remaining temperature dependency exists via only  $V_T$ . Via the voltage divider,  $R_1$  and  $R_2$ ,  $V_1$  represents only a part of the entire circuit's output voltage,  $V_{OUT}$ :

$$V_{OUT(T)} = \left(1 + \frac{R_1}{R_2}\right) \times V_1 = \left(1 + \frac{R_1}{R_2}\right) \times V_T \times \ln \frac{I_{C1}}{I_{C2}} \quad (8)$$

To compensate for the effect of  $V_T$ ,  $R_2$  is replaced by a temperature-dependent resistor with a positive temperature coefficient. This keeps

$$\left(1 + \frac{R_1}{R_{2(T)}}\right) \times V_T$$

constant over a certain temperature range. Practical values for the temperature coefficient vary between 3500 and 3700 ppm/K.

During the manufacturing process of log amps, the internal components and the temperature coefficient are trimmed to a fixed value. In addition, the natural logarithm is converted to  $\log_{10}$  by applying a correction factor,  $n = 2.3$ , according to  $\ln x = 2.3 \times \log x$ . The expression  $(1 + R_1/R_{2(T)}) \times V_T \times 2.3$  becomes a constant,  $q$ , with the unit V/decade, simplifying the computation of  $V_{OUT}$  to

$$V_{OUT} = q \times \log \frac{I_{C1}}{I_{C2}} \quad (9)$$

### Log-amp structure

Figure 7 shows a block diagram of the integrated log amp, LOG112. The actual logging circuit consists of the amplifiers,  $A_1$  and  $A_2$ , and the transistors,  $Q_1$  and  $Q_2$ . The designation of the collector currents,  $I_{C1}$  and  $I_{C2}$ , changes to  $I_1$  and  $I_2$ . In most cases,  $I_1$  represents the input current to be measured, while  $I_2$  is the reference current for the logarithmic computation.

The device minimizes external component count by providing a voltage reference and an uncommitted op amp,  $A_3$ , on-chip. The reference allows  $I_2$  to be generated via an external resistor,  $R_{REF}$ . Via  $A_3$ , the logarithmic output signal,  $V_{LOGOUT}$ , can be filtered or further amplified.  $A_3$  also can be configured as a comparator to provide a loss-of-signal indication.

The LOG112 is trimmed to provide an output voltage of 0.5 V per decade of input current. The device uses patented temperature compensation in which  $R_2$  is laid out as an aluminum frame with a temperature coefficient of 3700 ppm/K, resulting in extremely temperature-stable operation. For an input current of 10  $\mu$ A, for example, the output voltage changes by only 50  $\mu$ V/K.


The output voltage of the log amp is made available at the  $V_{LOGOUT}$  pin:

$$V_{LOGOUT} = 0.5 \times \log \frac{I_1}{I_2},$$

with input currents ranging from 100 pA to 3.5 mA. The voltage at the  $V_{OUT3}$  pin is defined via the external gain,  $G = 1 + R_F/R_G$ , and yields

$$V_{OUT3} = G \times V_{LOGOUT} = G \times 0.5 \times \log \frac{I_1}{I_2}.$$

Figure 7. Internal block diagram of LOG112

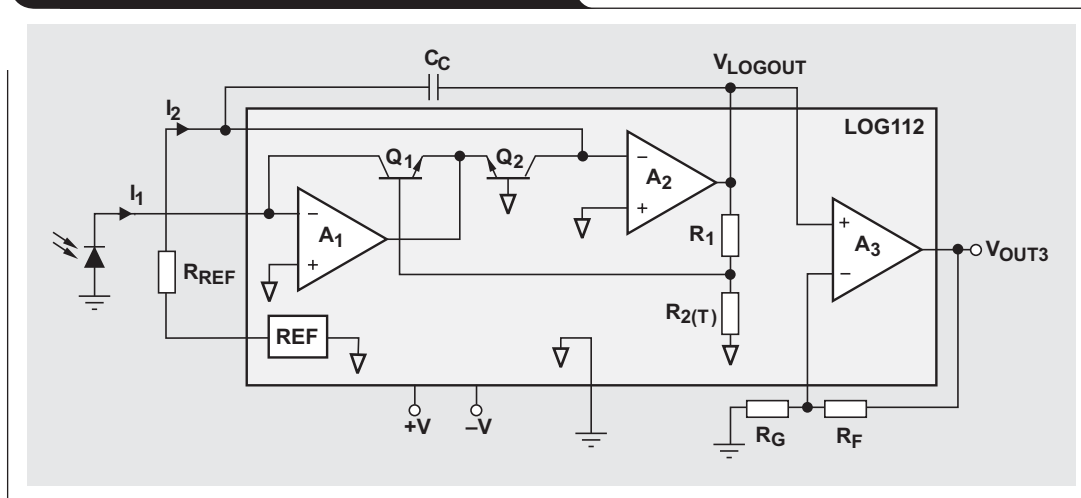


### Application examples

The circuit in Figure 8 controls the optical output power of a laser diode ( $LD_1$ ). With the output power decreasing over the lifetime of the diode, a control loop that keeps the output power constant is required. In the feedback path, a fraction of the output signal is fed back via a photodiode ( $PD_1$ ) and converted into electrical current.

The laser is calibrated by making the reference current,  $I_{REF}$ , equal to the  $PD_1$  current,  $I_1$ . Deviations between  $I_{REF}$  and  $I_1$  are converted into an error signal and applied to the bias input of the laser-diode driver. The driver then changes the bias current of  $LD_1$  until the error signal diminishes to zero.


Another application example is the constant-gain control and gain adjustment of an op amp shown in Figure 9. Two log amps measure the optical input and output power of the amplifier. A difference amplifier subtracts the output signals of both log amps and applies an error voltage to the proportional-integral-derivative (PID) controller. The

Figure 8. Controlling the optical output power of a laser diode

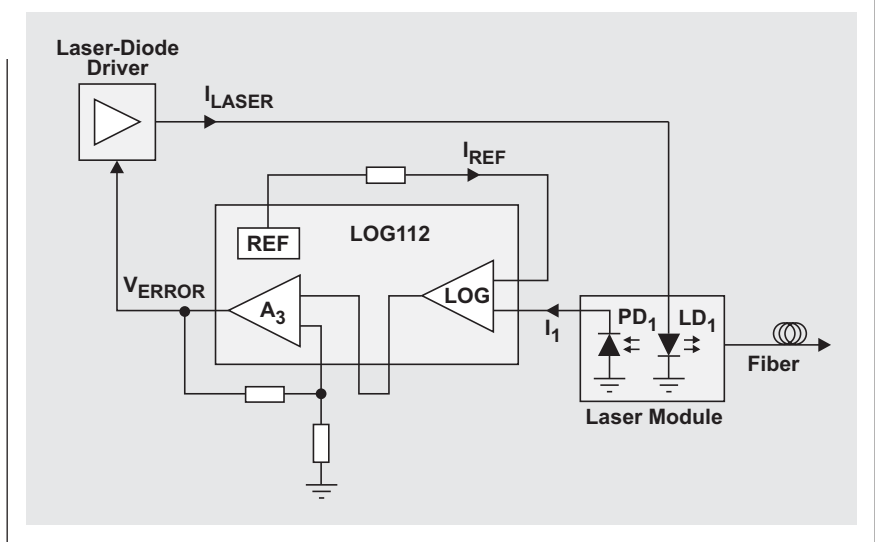

controller output adjusts a voltage-controlled current source ( $V_{CCS}$ ), which then drives the actual pump laser. The amplifier operates at the desired optical gain when the error voltage at the PID output is zero.

Figure 9. Constant-gain control and gain adjustment of an op amp

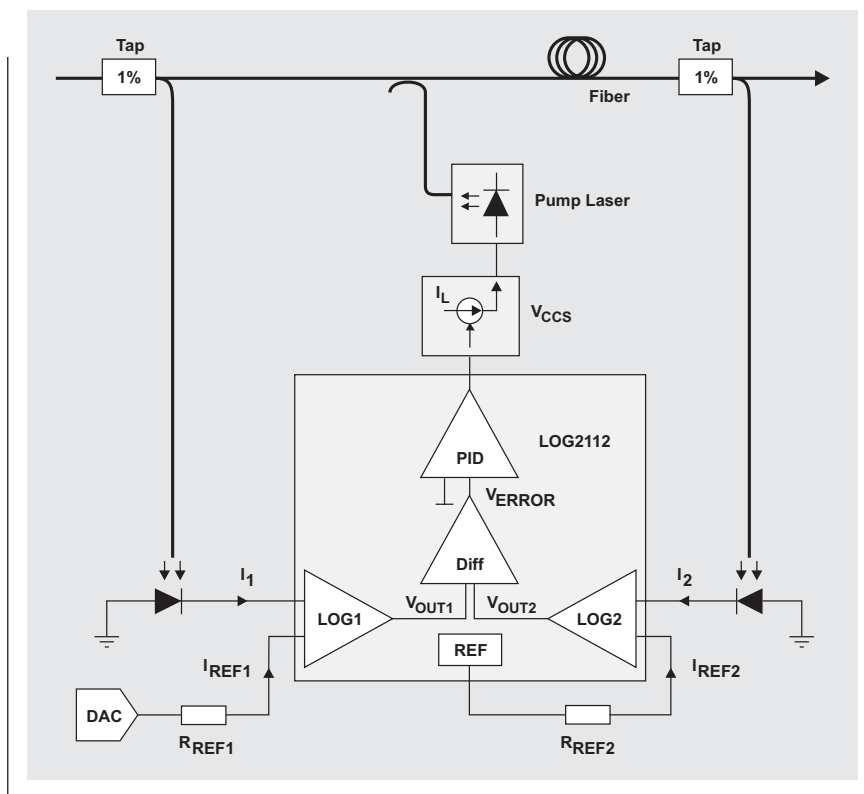

The log amp at the amplifier input builds the reference source. Its output voltage is

$$V_{\text{OUT1}} = \log \frac{I_1}{I_{\text{REF1}}},$$

where  $I_1$  is the input photo current and  $I_{\text{REF1}}$  is an adjustable reference current. The log amp at the amplifier output provides an output voltage of

$$V_{\text{OUT2}} = \log \frac{I_2}{I_{\text{REF2}}},$$

where  $I_2$  is the output photo current and  $I_{\text{REF2}}$  is a fixed reference current.

It is important to observe that  $I_2 = I_1 \times G_{\text{OPT}}$ , where  $G_{\text{OPT}}$  is the optical gain factor. In steady state, the output voltages of both log amps are equal ( $V_1 = V_2$ ), and

$$\log \frac{I_1}{I_{\text{REF1}}} = \log \frac{I_1 \times G_{\text{OPT}}}{I_{\text{REF2}}}, \text{ or } \frac{I_1}{I_{\text{REF1}}} = \frac{I_1 \times G_{\text{OPT}}}{I_{\text{REF2}}}.$$

Solving for  $G_{\text{OPT}}$  yields

$$G_{\text{OPT}} = \frac{I_{\text{REF2}}}{I_{\text{REF1}}}.$$

The preceding equation shows that the optical gain of the amplifier is adjusted simply by reducing  $I_{\text{REF1}}$  by a factor of  $G_{\text{OPT}}$  smaller than  $I_{\text{REF2}}$ . In addition to the constant-gain control, this circuit also allows the electronic gain setting of  $G_{\text{OPT}}$  in the range of 0 to 30 dB.

LOG2112 is well suited for this application. The device contains two log amps to measure the input and output power; an on-chip voltage reference to generate  $I_{\text{REF2}}$ ; and two uncommitted op amps configurable as difference amplifier and PID controller.

## Conclusion

TI offers a series of integrated, high-precision log amps with varying input-current ranges and output-scale factors.

## Related Web sites

[analog.ti.com](http://analog.ti.com)

[www.ti.com/sc/device/LOG112](http://www.ti.com/sc/device/LOG112)



# Index of Articles

Title	Issue	Page
<b>Data Acquisition</b>		
Aspects of data acquisition system design	August 1999	1
Low-power data acquisition sub-system using the TI TLV1572	August 1999	4
Evaluating operational amplifiers as input amplifiers for A-to-D converters	August 1999	7
Precision voltage references	November 1999	1
Techniques for sampling high-speed graphics with lower-speed A/D converters	November 1999	5
A methodology of interfacing serial A-to-D converters to DSPs	February 2000	1
The operation of the SAR-ADC based on charge redistribution	February 2000	10
The design and performance of a precision voltage reference circuit for 14-bit and 16-bit A-to-D and D-to-A converters	May 2000	1
Introduction to phase-locked loop system modeling	May 2000	5
New DSP development environment includes data converter plug-ins (PDF - 86 Kb)	August 2000	1
Higher data throughput for DSP analog-to-digital converters (PDF - 94 Kb)	August 2000	5
Efficiently interfacing serial data converters to high-speed DSPs (PDF - 80 Kb)	August 2000	10
Smallest DSP-compatible ADC provides simplest DSP interface (PDF - 120 Kb)	November 2000	1
Hardware auto-identification and software auto-configuration for the TLV320AIC10 DSP Codec — a “plug-and-play” algorithm (PDF - 105 Kb)	November 2000	8
Using quad and octal ADCs in SPI mode (PDF - 94 Kb)	November 2000	15
Building a simple data acquisition system using the TMS320C31 DSP (PDF - 235 Kb)	February 2001	1
Using SPI synchronous communication with data converters — interfacing the MSP430F149 and TLV5616 (PDF - 182 Kb)	February 2001	7
A/D and D/A conversion of PC graphics and component video signals, Part 1: Hardware (PDF - 191 Kb)	February 2001	11
A/D and D/A conversion of PC graphics and component video signals, Part 2: Software and control	July 2001	5
Intelligent sensor system maximizes battery life: Interfacing the MSP430F123 Flash MCU, ADS7822, and TPS60311	First Quarter, 2002	5
SHDSL AFE1230 application	Second Quarter, 2002	5
Synchronizing non-FIFO variations of the THS1206	Second Quarter, 2002	12
Adjusting the A/D voltage reference to provide gain	Third Quarter, 2002	5
MSC1210 debugging strategies for high-precision smart sensors	Third Quarter, 2002	7
Using direct data transfer to maximize data acquisition throughput	Third Quarter, 2002	14
Interfacing op amps and analog-to-digital converters	Fourth Quarter, 2002	5
ADS82x ADC with non-uniform sampling clock	Fourth Quarter, 2003	5
Calculating noise figure and third-order intercept in ADCs	Fourth Quarter, 2003	11
Evaluation criteria for ADSL analog front end	Fourth Quarter, 2003	16
Two-channel, 500-kSPS operation of the ADS8361	First Quarter, 2004	5
ADS809 analog-to-digital converter with large input pulse signal	First Quarter, 2004	8
<b>Power Management</b>		
Stability analysis of low-dropout linear regulators with a PMOS pass element	August 1999	10
Extended output voltage adjustment (0 V to 3.5 V) using the TI TPS5210	August 1999	13
Migrating from the TI TL770x to the TI TLC770x	August 1999	14
TI TPS5602 for powering TI's DSP	November 1999	8
Synchronous buck regulator design using the TI TPS5211 high-frequency hysteretic controller	November 1999	10
Understanding the stable range of equivalent series resistance of an LDO regulator	November 1999	14
Power supply solutions for TI DSPs using synchronous buck converters	February 2000	12
Powering Celeron-type microprocessors using TI's TPS5210 and TPS5211 controllers	February 2000	20

Title	Issue	Page
<b>Power Management (Continued)</b>		
Simple design of an ultra-low-ripple DC/DC boost converter with TPS60100 charge pump	May 2000	11
Low-cost, minimum-size solution for powering future-generation Celeron™-type processors with peak currents up to 26 A	May 2000	14
Advantages of using PMOS-type low-dropout linear regulators in battery applications (PDF - 216 Kb)	August 2000	16
Optimal output filter design for microprocessor or DSP power supply (PDF - 748 Kb)	August 2000	22
Understanding the load-transient response of LDOs (PDF - 241 Kb)	November 2000	19
Comparison of different power supplies for portable DSP solutions working from a single-cell battery (PDF - 136 Kb)	November 2000	24
Optimal design for an interleaved synchronous buck converter under high-slew-rate, load-current transient conditions (PDF - 206 Kb)	February 2001	15
-48-V/+48-V hot-swap applications (PDF - 189 Kb)	February 2001	20
Power supply solution for DDR bus termination	July 2001	9
Runtime power control for DSPs using the TPS62000 buck converter	July 2001	15
Power control design key to realizing InfiniBand™ benefits	First Quarter, 2002	10
Comparing magnetic and piezoelectric transformer approaches in CCFL applications	First Quarter, 2002	12
Why use a wall adapter for ac input power?	First Quarter, 2002	18
SWIFT™ Designer power supply design program	Second Quarter, 2002	15
Optimizing the switching frequency of ADSL power supplies	Second Quarter, 2002	23
Powering electronics from the USB port	Second Quarter, 2002	28
Using the UCC3580-1 controller for highly efficient 3.3-V/100-W isolated supply design	Fourth Quarter, 2002	8
Power conservation options with dynamic voltage scaling in portable DSP designs	Fourth Quarter, 2002	12
Understanding piezoelectric transformers in CCFL backlight applications	Fourth Quarter, 2002	18
Load-sharing techniques: Paralleling power modules with overcurrent protection	First Quarter, 2003	5
Using the TPS61042 white-light LED driver as a boost converter	First Quarter, 2003	7
Auto-Track™ voltage sequencing simplifies simultaneous power-up and power-down	Third Quarter, 2003	5
Soft-start circuits for LDO linear regulators	Third Quarter, 2003	10
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 1	Third Quarter, 2003	13
UCC28517 100-W PFC power converter with 12-V, 8-W bias supply, Part 2	Fourth Quarter, 2003	21
LED-driver considerations	First Quarter, 2004	14
<b>Interface (Data Transmission)</b>		
TIA/EIA-568A Category 5 cables in low-voltage differential signaling (LVDS)	August 1999	16
Keep an eye on the LVDS input levels	November 1999	17
Skew definition and jitter analysis	February 2000	29
LVDS receivers solve problems in non-LVDS applications	February 2000	33
LVDS: The ribbon cable connection	May 2000	19
Performance of LVDS with different cables (PDF - 57 Kb)	August 2000	30
A statistical survey of common-mode noise (PDF - 131 Kb)	November 2000	30
The Active Fail-Safe feature of the SN65LVDS32A (PDF - 104 Kb)	November 2000	35
The SN65LVDS33/34 as an ECL-to-LVTTL converter	July 2001	19
Power consumption of LVPECL and LVDS	First Quarter, 2002	23
Estimating available application power for Power-over-Ethernet applications	First Quarter, 2004	18
The RS-485 unit load and maximum number of bus connections	First Quarter, 2004	21

Title	Issue	Page
<b>Amplifiers: Audio</b>		
Reducing the output filter of a Class-D amplifier	August 1999	19
Power supply decoupling and audio signal filtering for the Class-D audio power amplifier	August 1999	24
PCB layout for the TPA005D1x and TPA032D0x Class-D APAs	February 2000	39
An audio circuit collection, Part 1 (PDF - 93 Kb)	November 2000	39
1.6- to 3.6-volt BTL speaker driver reference design (PDF - 194 Kb)	February 2001	23
Notebook computer upgrade path for audio power amplifiers (PDF - 202 Kb)	February 2001	27
An audio circuit collection, Part 2 (PDF - 215 Kb)	February 2001	41
An audio circuit collection, Part 3	July 2001	34
Audio power amplifier measurements	July 2001	40
Audio power amplifier measurements, Part 2	First Quarter, 2002	26
<b>Amplifiers: Op Amps</b>		
Single-supply op amp design	November 1999	20
Reducing crosstalk of an op amp on a PCB	November 1999	23
Matching operational amplifier bandwidth with applications	February 2000	36
Sensor to ADC — analog interface design	May 2000	22
Using a decompensated op amp for improved performance	May 2000	26
Design of op amp sine wave oscillators (PDF - 56 Kb)	August 2000	33
Fully differential amplifiers (PDF - 51 Kb)	August 2000	38
The PCB is a component of op amp design (PDF - 64 Kb)	August 2000	42
Reducing PCB design costs: From schematic capture to PCB layout (PDF - 28 Kb)	August 2000	48
Thermistor temperature transducer-to-ADC application (PDF - 97 Kb)	November 2000	44
Analysis of fully differential amplifiers (PDF - 96 Kb)	November 2000	48
Fully differential amplifiers applications: Line termination, driving high-speed ADCs, and differential transmission lines (PDF - 185 Kb)	February 2001	32
Pressure transducer-to-ADC application (PDF - 185 Kb)	February 2001	38
Frequency response errors in voltage feedback op amps (PDF - 184 Kb)	February 2001	48
Designing for low distortion with high-speed op amps	July 2001	25
Fully differential amplifier design in high-speed data acquisition systems	Second Quarter, 2002	35
Worst-case design of op amp circuits	Second Quarter, 2002	42
Using high-speed op amps for high-performance RF design, Part 1	Second Quarter, 2002	46
Using high-speed op amps for high-performance RF design, Part 2	Third Quarter, 2002	21
FilterPro™ low-pass design tool	Third Quarter, 2002	24
Active output impedance for ADSL line drivers	Fourth Quarter, 2002	24
RF and IF amplifiers with op amps	First Quarter, 2003	9
Analyzing feedback loops containing secondary amplifiers	First Quarter, 2003	14
Video switcher using high-speed op amps	Third Quarter, 2003	20
Expanding the usability of current-feedback amplifiers	Third Quarter, 2003	23
Op amp attenuators	Fourth Quarter, 2003	28
Calculating noise figure in op amps	Fourth Quarter, 2003	31
Op amp stability and input capacitance	First Quarter, 2004	24
Integrated logarithmic amplifiers for industrial applications	First Quarter, 2004	28
<b>General Interest</b>		
Synthesis and characterization of nickel manganite from different carboxylate precursors for thermistor sensors (PDF - 194 Kb)	February 2001	52
Analog design tools	Second Quarter, 2002	50

## TI Worldwide Technical Support

### Internet

#### TI Semiconductor Product Information Center Home Page

support.ti.com

#### TI Semiconductor KnowledgeBase Home Page

support.ti.com/sc/knowledgebase

### Product Information Centers

#### Americas

Phone +1(972) 644-5580  
 Fax +1(972) 927-6377  
 Internet/Email support.ti.com/sc/pic/americas.htm

#### Europe, Middle East, and Africa

Phone  
 Belgium (English) +32 (0) 27 45 55 32  
 Finland (English) +358 (0) 9 25173948  
 France +33 (0) 1 30 70 11 64  
 Germany +49 (0) 8161 80 33 11  
 Israel (English) 1800 949 0107  
 Italy 800 79 11 37  
 Netherlands (English) +31 (0) 546 87 95 45  
 Spain +34 902 35 40 28  
 Sweden (English) +46 (0) 8587 555 22  
 United Kingdom +44 (0) 1604 66 33 99  
 Fax +(49) (0) 8161 80 2045  
 Internet support.ti.com/sc/pic/euro.htm

#### Japan

Fax International +81-3-3344-5317  
 Domestic 0120-81-0036  
 Internet/Email International support.ti.com/sc/pic/japan.htm  
 Domestic www.tij.co.jp/pic

#### Asia

Phone  
 International +886-2-23786800  
 Domestic Toll-Free Number  
 Australia 1-800-999-084  
 China 800-820-8682  
 Hong Kong 800-96-5941  
 Indonesia 001-803-8861-1006  
 Korea 080-551-2804  
 Malaysia 1-800-80-3973  
 New Zealand 0800-446-934  
 Philippines 1-800-765-7404  
 Singapore 800-886-1028  
 Taiwan 0800-006800  
 Thailand 001-800-886-0010  
 Fax 886-2-2378-6808  
 Email tiasia@ti.com  
 ti-china@ti.com  
 Internet support.ti.com/sc/pic/asia.htm

**Important Notice:** The products and services of Texas Instruments Incorporated and its subsidiaries described herein are sold subject to TI's standard terms and conditions of sale. Customers are advised to obtain the most current and complete information about TI products and services before placing orders. TI assumes no liability for applications assistance, customer's applications or product designs, software performance, or infringement of patents. The publication of information regarding any other company's products or services does not constitute TI's approval, warranty or endorsement thereof.

A111103