

# Evaluating operational amplifiers as input amplifiers for A-to-D converters

By James Karki

Application Specialist, Operational Amplifiers

This application note describes a method for comparing the ac performance of the TI TLV2462 and TLV2772 operational amplifiers to the TI TLV2544/TLV2548 analog-to-digital converter. Amplifiers like the TLV2462 and TLV2772 are used to condition the signal input to ADCs (TLV2544/TLV2548). Normally the functions performed include level shifting, impedance matching and amplification. The drive amplifier is the link between the input source and the ADC.

When selecting an amplifier, ac performance factors such as bandwidth, slew rate, noise and distortion drive the decision-making process with dc errors considered secondarily. One of the difficulties that arises during amplifier selection is that op amps are not normally specified in the same manner as ADCs. ENOB (effective

number of bits) is a key ac parameter used for ADCs. It is calculated based on SINAD (signal to noise + distortion) in dB, where

$$ENOB = \frac{SINAD - 1.76}{6.02}$$


By measuring the THD+N (total distortion + noise) in dB of the TLV2462 and TLV2772 in different circuit topologies and substituting THD+N for SINAD when calculating ENOB, the amplifier's performance is directly comparable to the TLV2544/TLV2548 ADC.

## Test circuits

The input to the TLV2544/TLV2548 ADC is modeled as shown in Figure 1. During sampling the input is active and appears as a series resistor and shunt capacitor. Typical values are 1 kΩ and 60 pF. When not sampling, the input impedance of the ADC is high.


Figure 2 shows the non-inverting, inverting and differential amplifier circuits that are tested. A 1-kΩ resistor in series with a 68-pF capacitor is placed on the output of each amplifier to simulate the input of the ADC. The value of resistive components, R, is varied between 1 kΩ,

Figure 1. Equivalent ADC input

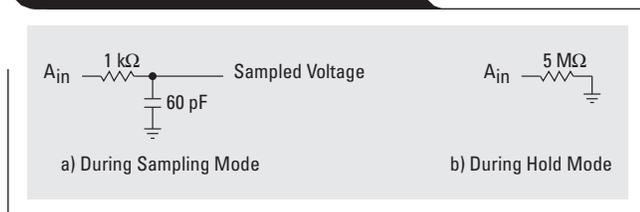

Continued on next page

Figure 2. Test circuits

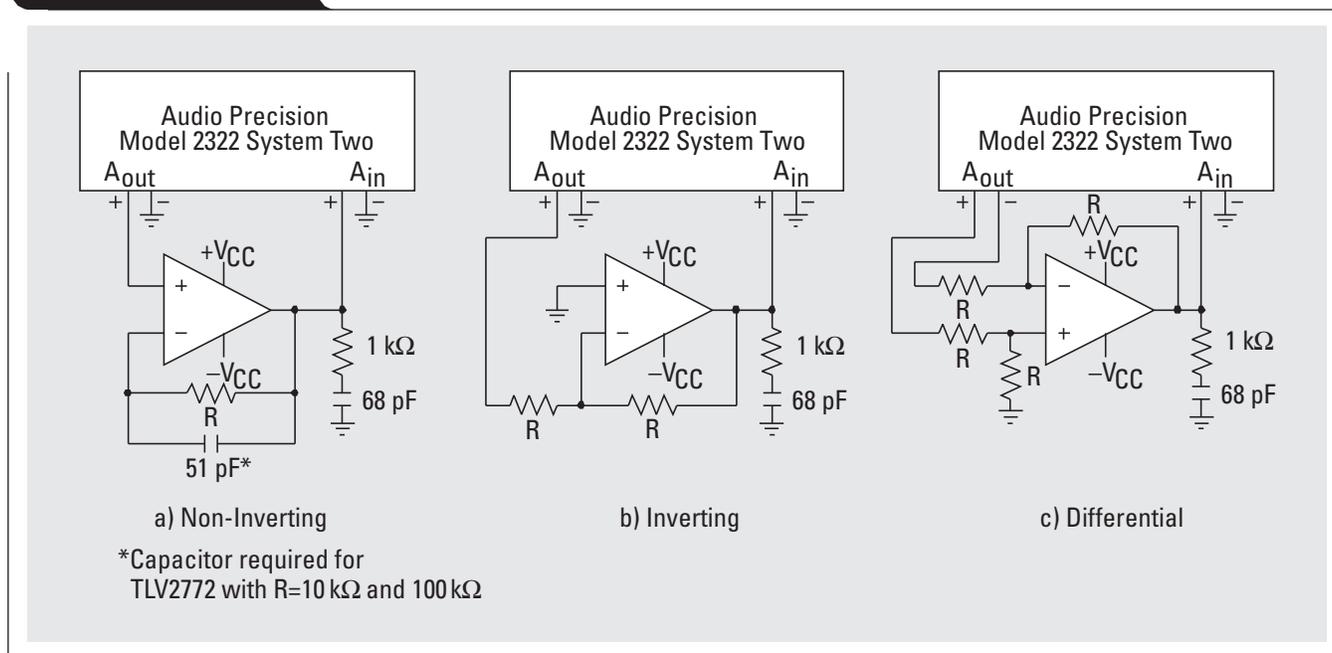

\*Capacitor required for TLV2772 with R=10 kΩ and 100 kΩ

See next two pages for related websites

## Continued from previous page

10 k $\Omega$  and 100 k $\Omega$  to measure their effect on the ENOB performance. Note that in the TLV2772 non-inverting circuit with 10-k $\Omega$  and 100-k $\Omega$  resistor values, a small capacitor is required in the feedback circuit for stability due to the capacitance of the cabling and measuring instrument. Note also that R = 0  $\Omega$  is tested for the non-inverting amplifiers. Compare the test results from the TLV2462 in Figures 3 and 4 with the TLV2772 in Figures 5 and 6.

An Audio Precision model 2322 – System Two is used to measure the THD+N of the amplifier circuits. The analog test signal is a sine wave that is swept from 10 Hz to 200 kHz. The measurement bandwidth is 10 Hz to 500 kHz.

It is assumed that the amplifier is operated at the same voltage as the ADC—3.3 V or 5 V. Typically, the amplifier is biased so that with zero input the output is at half the full-scale voltage of the ADC. To simplify testing, the amplifiers use supply voltages of  $\pm 1.65$  V to simulate a 3.3-V system and  $\pm 2.5$  V to simulate a 5-V system. The input signal is referenced to ground with peak levels of 0.89 V and 1.78 V. These are equivalent to -1-dB levels in 2-V and 4-V full-scale systems.

## Test results

Calculating


$$\text{ENOB} = \frac{(\text{THD} + N) - 1.76}{6.02},$$

Figures 3 to 6 show the results of testing the ENOB with the TLV2544/TLV2548 ADC shown for comparison.


## Conclusion

The data shows the TLV2462 and TLV2772 inverting and differential amplifier topologies with resistive elements of R=10 k $\Omega$  result in the best amplifier performance. This result may appear surprising at first since the noise gain of the inverting amplifier is twice that of the non-inverting amplifier. The larger values of measured THD+N in the non-inverting mode stem from the fact that the input bias point is made to move through most of its common mode voltage range resulting in larger distortion products, with noise being less dominant. The input bias point of the differential amplifier is also made to change, but only one quarter as much. In the inverting topology, the input remains biased midway between the power supply rails. This optimizes distortion performance.


Figure 3. The TLV2462 at 3.3 V

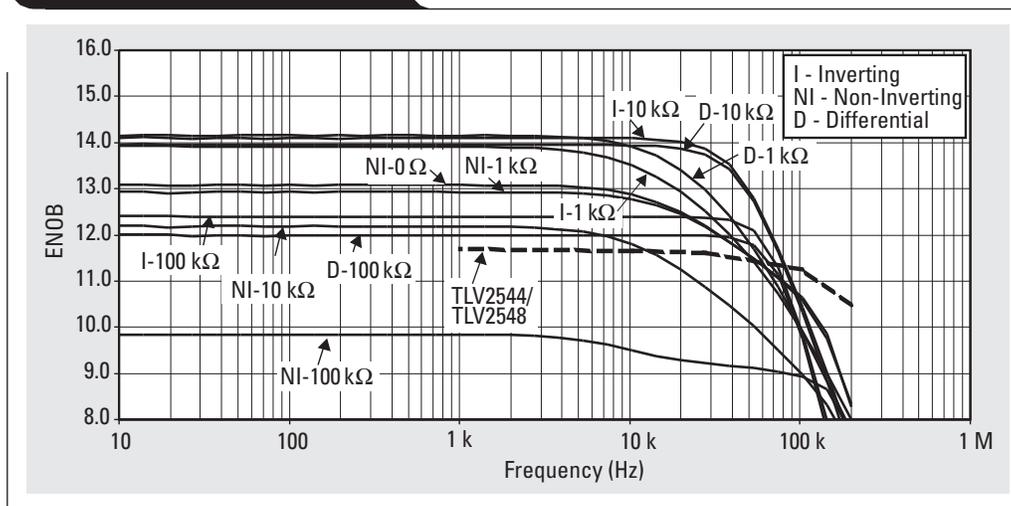


**Figure 4. The TLV2462 at 5 V**

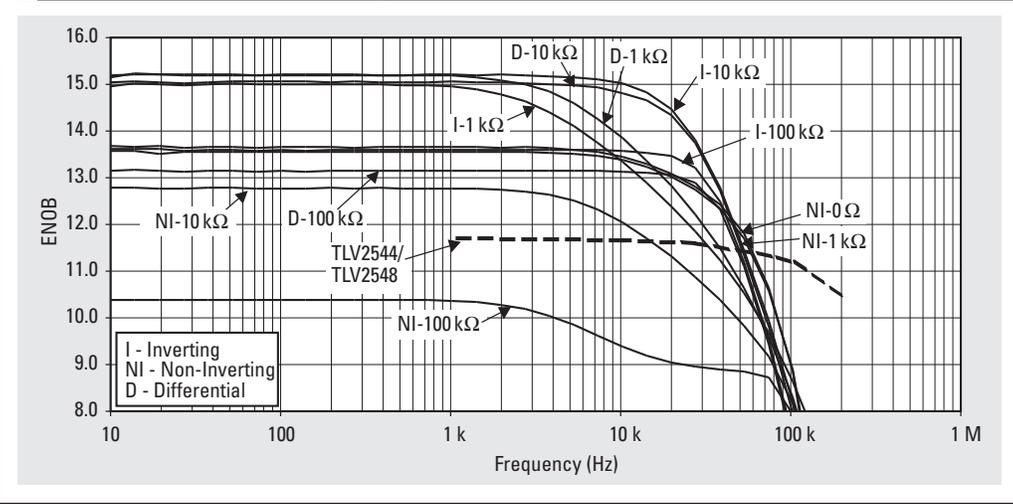

**Figure 5. The TLV2772 at 3.3 V**

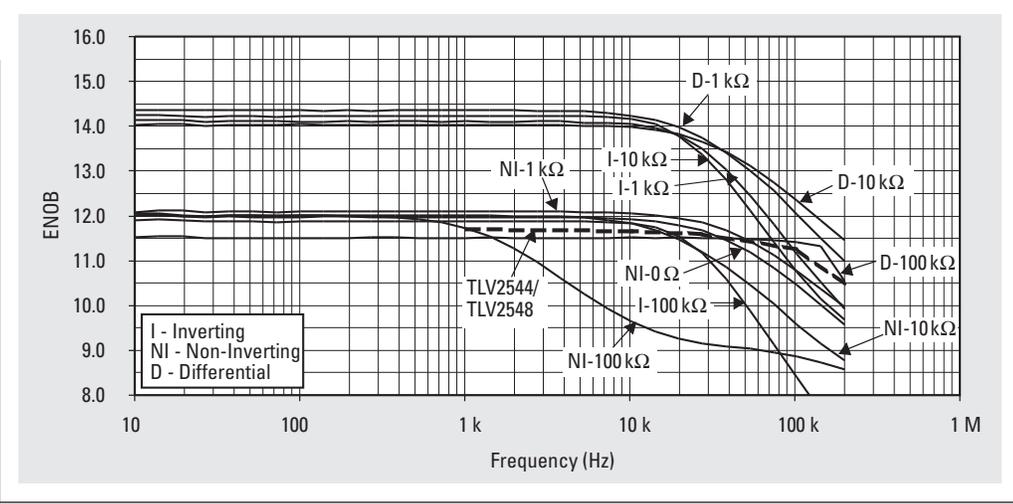

**Figure 6. The TLV2772 at 5 V**

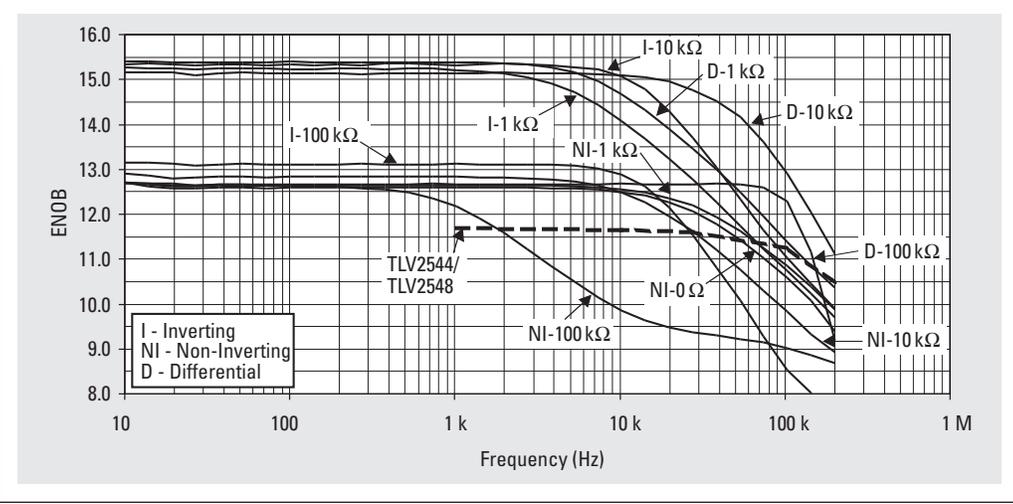

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>

### Applications

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Broadband	<a href="http://www.ti.com/broadband">www.ti.com/broadband</a>
Digital control	<a href="http://www.ti.com/digitalcontrol">www.ti.com/digitalcontrol</a>
Military	<a href="http://www.ti.com/military">www.ti.com/military</a>
Optical Networking	<a href="http://www.ti.com/opticalnetwork">www.ti.com/opticalnetwork</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Telephony	<a href="http://www.ti.com/telephony">www.ti.com/telephony</a>
Video & Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>
Wireless	<a href="http://www.ti.com/wireless">www.ti.com/wireless</a>

## TI Worldwide Technical Support

### Internet

**TI Semiconductor Product Information Center Home Page**  
[support.ti.com](http://support.ti.com)

**TI Semiconductor KnowledgeBase Home Page**  
[support.ti.com/sc/knowledgebase](http://support.ti.com/sc/knowledgebase)

### Product Information Centers

#### Americas

Phone	+1(972) 644-5580	Fax	+1(972) 927-6377
Internet/Email	<a href="http://support.ti.com/sc/pic/americas.htm">support.ti.com/sc/pic/americas.htm</a>		

#### Europe, Middle East, and Africa

Phone			
Belgium (English)	+32 (0) 27 45 54 32	Netherlands (English)	+31 (0) 546 87 95 45
Finland (English)	+358 (0) 9 25173948	Russia	+7 (0) 95 7850415
France	+33 (0) 1 30 70 11 64	Spain	+34 902 35 40 28
Germany	+49 (0) 8161 80 33 11	Sweden (English)	+46 (0) 8587 555 22
Israel (English)	1800 949 0107	United Kingdom	+44 (0) 1604 66 33 99
Italy	800 79 11 37		
Fax	+(49) (0) 8161 80 2045		
Internet	<a href="http://support.ti.com/sc/pic/euro.htm">support.ti.com/sc/pic/euro.htm</a>		

#### Japan

Fax			
International	+81-3-3344-5317	Domestic	0120-81-0036
Internet/Email			
International	<a href="http://support.ti.com/sc/pic/japan.htm">support.ti.com/sc/pic/japan.htm</a>		
Domestic	<a href="http://www.tij.co.jp/pic">www.tij.co.jp/pic</a>		

#### Asia

Phone			
International	+886-2-23786800		
Domestic	Toll-Free Number		
Australia	1-800-999-084	New Zealand	0800-446-934
China	800-820-8682	Philippines	1-800-765-7404
Hong Kong	800-96-5941	Singapore	800-886-1028
Indonesia	001-803-8861-1006	Taiwan	0800-006800
Korea	080-551-2804	Thailand	001-800-886-0010
Malaysia	1-800-80-3973		
Fax	886-2-2378-6808	Email	<a href="mailto:tiasia@ti.com">tiasia@ti.com</a>
Internet	<a href="http://support.ti.com/sc/pic/asia.htm">support.ti.com/sc/pic/asia.htm</a>		<a href="mailto:ti-china@ti.com">ti-china@ti.com</a>

**C011905**

**Safe Harbor Statement:** This publication may contain forward-looking statements that involve a number of risks and uncertainties. These "forward-looking statements" are intended to qualify for the safe harbor from liability established by the Private Securities Litigation Reform Act of 1995. These forward-looking statements generally can be identified by phrases such as "TI or its management believes," "expects," "anticipates," "foresees," "forecasts," "estimates" or other words or phrases of similar import. Similarly, such statements herein that describe the company's products, business strategy, outlook, objectives, plans, intentions or goals also are forward-looking statements. All such forward-looking statements are subject to certain risks and uncertainties that could cause actual results to differ materially from those in forward-looking statements. Please refer to TI's most recent Form 10-K for more information on the risks and uncertainties that could materially affect future results of operations. We disclaim any intention or obligation to update any forward-looking statements as a result of developments occurring after the date of this publication.

**Trademarks:** All trademarks are the property of their respective owners.

Mailing Address: Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

© 2005 Texas Instruments Incorporated

SLYT193