

***Lower Operating Voltages Force Higher Efficiency Conversion in Battery
Operated Appliances***



Literature Number: SNVA554

Lower Operating Voltages Force Higher Efficiency Conversion in Battery Operated Appliances

Contact Information:

Jim Schuessler
Strategic Marketing Manager
National Semiconductor Corp.
james.schuessler@nsc.com
530-274-4972

Unlike Chicken Little, who seemed to fear the sky falling, Engineers today have good reason to welcome lower operating voltages. As the fundamental power equation shows, dropping the operating voltage on CMOS gates is the only exponential factor in an otherwise linear relationship between power, capacitance and switching frequency. ($P = f_{sw} \cdot C \cdot V^2$) In short, lower operating voltages give the biggest bang for the buck when longer operating life in battery powered devices is your goal.

However, since battery voltages are not changing, lower operating voltages bring new challenges to the power supply designer to wring every last watt-hour from the battery. Two major factors contribute to the power conversion circuit's ability to accomplish this task. The obvious metric to check is the basic conversion efficiency when the power supply is operating. Not so obvious may be the voltage at which the power supply stops operating.

Operating Efficiency

Although a good understanding of the effect efficient energy transfer has on operating life and heat buildup seems intrinsic to every engineer, the ease with which this information is extracted from some semiconductor data sheets sometimes requires far too much guesswork. Most often efficiency data is presented at fixed input voltages. Designers of battery operated equipment *never* have the luxury of assuming a relatively fixed input voltage. As the battery discharges, input voltage clearly declines dramatically, thus altering the efficiency of the conversion circuit. An average operating efficiency is needed over the discharge profile of the battery.

When using a Low-dropout Regulator (LDO), the linear conversion efficiency is proportional to $V_{IN} - V_{OUT}$, making an estimate of average efficiency over the life of the battery relatively simple. Inductor-based switching regulators have highly variable efficiency as input voltage changes, thus making the task of producing an average operating efficiency number difficult.

Dropout Voltage

All too often devices today force users to discard (or at least change) batteries "before their time". Regardless of the amount of energy remaining in the battery, when the power supply stops working, so do you. The critical factor here is dropout voltage. (By the way, keep those batteries for your flashlights!) For instance a Lithium-ion (LiIon) battery can be safely operated between about 4.2V and 2.5V. If an LDO needed to produce a 3.3V output, it may stop working

at 3.45V -- assuming a 150mV dropout voltage. In the case of a coke anode type Lilon battery, over 40% of the energy is unused! A 3-cell Alkaline pack still contains 33% of its power under the same conditions.

Another factor driving the engineer's focus on dropout voltage is the effect highly variable or pulsed loads have on the output voltage of the battery. Depending on the equivalent series resistance (ESR) of the battery, output voltage can drop substantially as the applied load changes.

Lithium-ion Powers the World of Cellular Telephones

Nowhere is a pulsed load more prevalent than in Cellular Telephone devices. The increasingly popular time-division multiple access (TDMA) protocols used in GSM (Europe), PCS (USA) and PDC (Japan) all require rapid pulsing of the Cell Phone power amplifier (PA). As the PA draws 1000 to 1500mA, input voltage to the power supplies for the digital signal processor (DSP), frequency synthesizers, mixers, low-noise amplifiers, audio and display circuitry may dip 0.5V or more for Lilon batteries. Although the Lilon chemistry provides the highest available energy density measured by both weight and size; unfortunately the ESR can be much higher when compared with NiCad or NiMH type batteries. In addition, it increases as the cell discharges.

A power supply's ability to operate with a very low minimum input voltage becomes critical to extending the talk-time of the phone.

Today's Requirements Drive Focus on Dropout Voltage

When the input voltage (3.6V nominal from Lilon) is close to the desired output voltage (see Table 1.), using LDO to generate these voltages is a fairly high efficiency proposition. For a 3.3V rail, an LDO achieves about 88% average efficiency over the portion of the battery discharge cycle it uses. As output voltage requirements drop, efficiency will linearly decline. But do we care? In fact, empirical evidence would suggest we don't. Users today enjoy over 200 hours of standby time on cellular telephones -- the vast majority of which the PA is inactive. Market data suggests that users will not pay more for more standby time; what they want, and will pay for, is more talk time. Talk time is dominated at an 8:1 to 10:1 ratio by the PA power consumption. If all the other circuitry in the phone is consuming only 10% of the power, increasing conversion efficiency on that portion does not noticeably effect talk time.

So what is the limiting factor to talk time? Many transmit power amplifiers shut down around 3.0V today (they are typically connected directly to the battery). However, since LDO cannot boost, any supply rail above about 2.9V shuts down earlier. That may be acceptable, except that these steady-state assumptions do not account for the load profile of TDMA phones. As the PA pulses on, drawing an amp or more, the ESR of the battery causes a transient voltage drop that may knock an LDO out of regulation long before it normally would with a lower steady load.

This effect is shown in Figure 1. The top line is the typical 1C (1C refers to the load applied to the battery where C is equal to the Amp-hour

Rail V	Today		Tomorrow	
	mA	mW	mA	mW
1.8	0	0	50	90
2.5	0	0	125	313
2.9	40	116	10	29
3.0	150	450	0	0
5.0	5	25	3	15
			591	447

Table 1. Hypothetical power used for everything except the PA.

rating. The battery shown is rated at 275mAh, thus a 1C discharge rate would be 275mA) discharge curve of voltage verses time for a graphite anode type Lilon battery. The bottom curve shows the effect of the battery's ESR as the load is doubled. Note that ESR increases

slightly as the battery becomes depleted, amplifying the effect of lower than normal input voltage to the power supply.

This increasing ESR burdens the power supply with very low input voltages, even though the battery has a large amount of energy remaining. For example, one commercially available 600mAh graphite anode battery has an 830 milli-Ohm ESR at 3.5V, dropping the output voltage to 3.0V with a 1200mA load. Now at 3.5V, 12% of the battery capacity remains unused. (Other Lilon chemistries, such as coke anode materials can result in much higher remaining capacities.)

Tomorrow's Voltages Present a Dual Challenge

We have found that from a power supply perspective, a low minimum input voltage (dropout voltage) has the biggest effect on increasing talk time, since it utilizes the battery more completely. However as *output* voltages decline (See Table 1) the conversion efficiency of an LDO-based power supply architecture becomes a much bigger factor. A 1.8V rail results in an awful 49% average efficiency using an LDO alone. Not only is the low dropout important, but increasing efficiency now has a 5 to 10% effect on increased talk time.

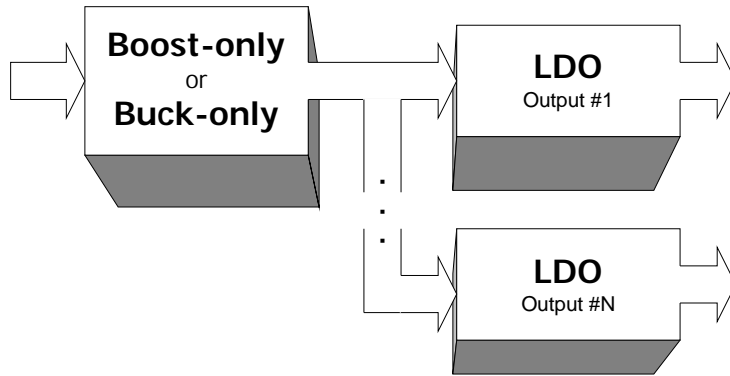


Figure 2. Boost-only can result in poor efficiency while Buck-only has a very high minimum input voltage.

Buck-Boost Switched Capacitor Solution

One method cellular telephone power supply designers have used to combat this problem is by fronting the LDOs with either inductive boost or inductive buck regulators. See Figure 2. Boosting a Lilon battery above its fully charged voltage (about 4.2V) and then using LDOs has the advantage of utilizing the full battery capacity, but with the penalty of poor conversion efficiency especially at lower output voltages. Buck-only solutions suffer from a higher dropout voltage, especially when used to generate voltages between 3.3 and 3.0V. So although good efficiency can be obtained during operation, some significant portion of battery energy will remain untapped, shortening potential operating life.

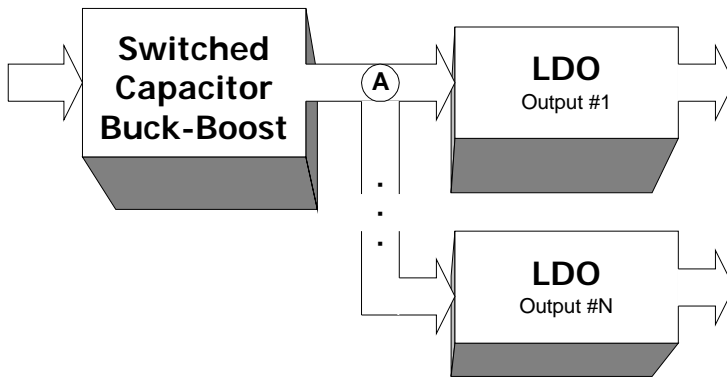


Figure 3. Lacking the need for any inductors, Switched Capacitor architectures are becoming available with Buck-Boost functionality.

Using step-up/step-down or buck-boost converters solves both problems since an output voltage can be picked that allows efficient conversion with trailing LDOs, and yet utilizes the full battery capacity due to very low minimum input voltages. For instance choosing a 3.0V output at "A" in Figure 3 will satisfy the "Tomorrow" voltage requirements in Table 1. at relatively high efficiency, and enable users to get maximum talk time by fully utilizing the battery.

Only now are Switched Capacitor architectures becoming available that dynamically move between buck and boost modes depending on the input voltage and output load. Average operating efficiency compares quite favorably with single-ended primary inductance (SEPIC) converters. Utilizing multiple gain modes to optimize efficiency, one buck-boost switched capacitor converter achieves between 82 and 84% average efficiency over the discharge profile of both coke and graphite anode Lilon batteries when producing a 3.0V output voltage. Since the input voltage range encompasses the entire operating range of the battery, the full battery capacity can be converted for the loads.

No Inductors Means Lower System Costs

Most inductive SEPIC converters require two inductors while buck-only or boost-only require one. Removing the need for inductors in portable systems not only saves space and allows thinner designs, it also can lower manufacturing costs and ease difficult procurement issues in high volume production. In addition to being more expensive than capacitors, inductors can increase manufacturing costs due to more stringent soldering requirements. And although newer thin inductors are available, they are frequently single-sourced items, which introduces another potential for line-down conditions in manufacturing.

Switched capacitor buck-boost regulators are not a panacea however. In particular care must be taken to mitigate switching noise caused by the relatively fast current flow into and out of the switching capacitors. Fortunately the trailing LDOs in this distributed power architecture can act as effective filters providing up to 60dB of noise isolation depending on the frequency of the noise.

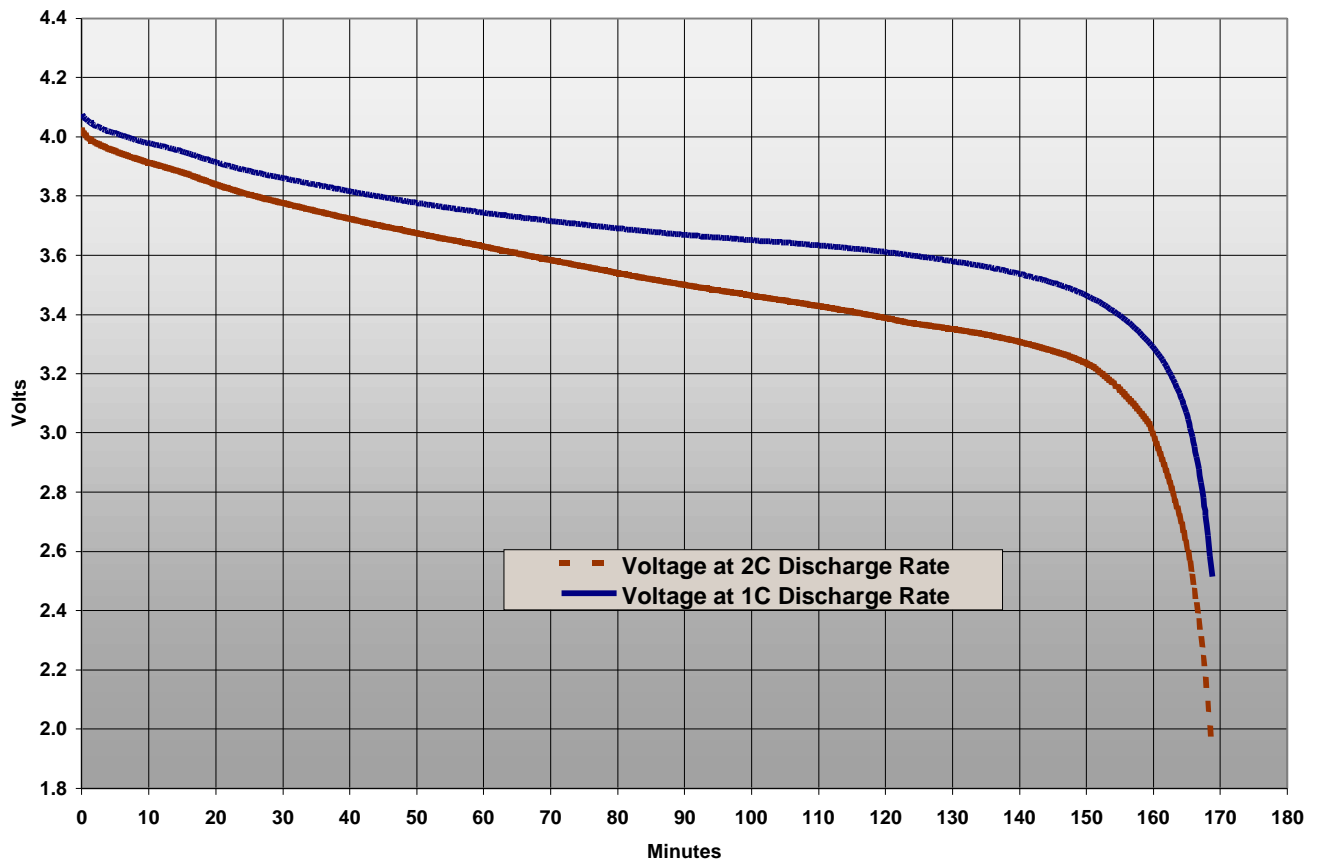


Figure 1. Although the graphite anode Lilon battery has a very flat discharge characteristic, the ESR can cause a substantial voltage drop as heavy loads are applied. 1C=275mA for this battery.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated