 


TI TECH DAYS



Solving Common Buck Converter Design Challenges

Rich Nowakowski
Texas Instruments

Agenda

1. Reducing voltage ripple for signal chain power.
2. Achieving high output voltage accuracy for FPGA power.
3. Understanding impact of thermal SOA.
4. Smaller size with faster switching frequencies.
5. Control mode types.
6. Using WEBENCH® to address the latest buck converter design challenges.

Challenge #1: low noise for signal chain power

Achieving low-ripple output voltage noise without a linear regulator, using higher current DC/DC converters.

LDO drawbacks compound at higher currents:

- Cost penalty, but some designers may not care.
- Thermal penalty.
- Efficiency penalty.
- Size penalty.
- Paralleling LDOs is possible, but complicated.

Attribute	400-kHz Design with LDO	4-MHz Design	Advantage
Size	640 mm ²	195 mm ²	4-MHz design
Full-load efficiency	77.2%	86.8%	4-MHz design
Power loss	2.06 W	1.1 W	4-MHz design
IC temperature	57.8°C + 51.6°C	37.1°C	4-MHz design
Transient overshoot	146 mV	35.5 mV	4-MHz design
Ripple voltage	11.5 mV	6.7 mV	4-MHz design
Output voltage noise	14.9 μ V	135 μ V	400-kHz design
Solution cost	\$9.55 at 1 Ku	\$7.50 at 1 Ku	4-MHz design

- 12V to 1.8V @ 4A
- No additional noise reduction techniques employed

Low noise means different things to different designers

Low noise problem	Specific need	Market	IC solution	Package solution	PC board solution	System solution
Low output voltage ripple (μV_{PP})	High speed ADC and AFE systems need to reduce the output ripple to $\sim 200\mu\text{V}$ to maintain high ENOB (effective number of bits).	Wireless Infrastructure, Test and Measurement	2 nd loop compensation, Higher Fsw (reduced inductor ripple), Spread Spectrum	Hotrod packaging, RLF with integrated input cap	Ferrite output filter, post regulate with LDO, multiple caps to reduce ESL	
Phase noise (μV_{RMS})	Clocking systems need low phase noise from from 100Hz to 100kHz $20\mu\text{V}_{\text{RMS}}$ or less output noise voltage	Wireless Infrastructure, Test and Measurement	optimize bandgap and optimize error amplifier design for low intrinsic device noise			
1/f noise	Thermal and flicker noise can cause errors in low frequency bands	Test and Measurement	Reduce bandgap noise			
Power supply rejection	ADC requires $\sim 40\text{dB}$ of input power supply rejection to minimize cross coupling noise from the input rails	Test and Measurement	IC may meet the spec		Additional input filtering	
Electromagnetic interference (EMI)	Meet FCC Unintentional Radiator Limits	Radio and TV receivers, PE		Hotrod packaging		
	Meet FCC Intentional Radiator Limits	Wireless (WLAN and BT, etc) devices	Adjustable slew rate and/or optimized gate drive, Spread Spectrum	Hotrod packaging, RLF with integrated input cap	Good board layout to minimize coupling power supply noise	Metal shielding
	Meet CISPR 25 Class 5	Automotive applications	Adjustable slew rate and/or optimized gate drive, Spread Spectrum, allow SYNC to external clock with Spread Spectrum	Hotrod packaging, RLF with integrated input cap	Chokes to the power supply input	Metal shielding


Low noise: tips to reduce noise conduction to the load

- High self-resonant frequency for inductor.
- Place vias for bypass capacitors between terminals.
- Keep non-ground vias spaced wide enough to allow ground planes to flow between vias
- Ramp capacitors up and down from inductor to load: 1.0uF, 2.2uF, 4.7uF, 10uF, 22uF, 47uF, 100uF, 47uF, 22uF, 10uF, 4.7uF, 2.2uF, 1.0uF.
- Mix capacitor values with 2:1 or 3:1 values and different packages.
- Use Multi-phase converter.
 - Synchronized and phase-shifted multi-phase architecture increase ripple frequency and reduce ripple currents.
 - Use different boot resistors and snubbers on each phase to spread noise spike frequencies.
- Use Second-stage Output Filter.
 - Ferrite Bead or soft-resonating inductor between first and second stage.
 - DC regulation feedback after second filter, with feed-forward capacitor from first stage to minimize loop impact of 2-stage filter.

Low noise: two-stage output filter example

TPS54618-Q1 example:

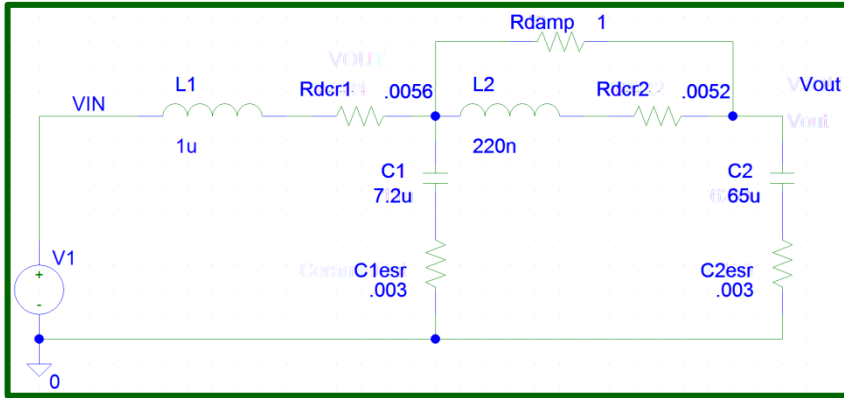- $5 V_{IN}$ to $3.3 V_{OUT}$ @ 5 A
- $F_{sw} = 750 \text{ kHz}$
- $C_{out} = 22 \text{ uF } 6.3 \text{ V X5R ceramic}$
- $L = 1 \text{ uF}$
- Ripple is 39 mV (~1%)
- Target ripple: 1 mV ripple



Step #1:

- Make the second-stage capacitor 4x to 10x bigger than the first-stage capacitor. Choose 100 uF X5R.

Step#2

- Choose new resonant frequency – 150 kHz. Rule of thumb (3-5x higher than loop cross-over frequency).
- Calculate second stage inductor value (L2) using equation. Choose 220 nH.

Step #3


- Damp the second filter resonance properly. That means carefully choosing the ESR of the second inductor.

Step #4



- Re-compensate the loop.

$$F_{,res2} = \frac{1}{(2\pi\sqrt{L2 \times Cs})}, \text{ where } Cs = \frac{1}{\frac{1}{C1} + \frac{1}{C2}}$$

Two-stage filter waveform results

 

 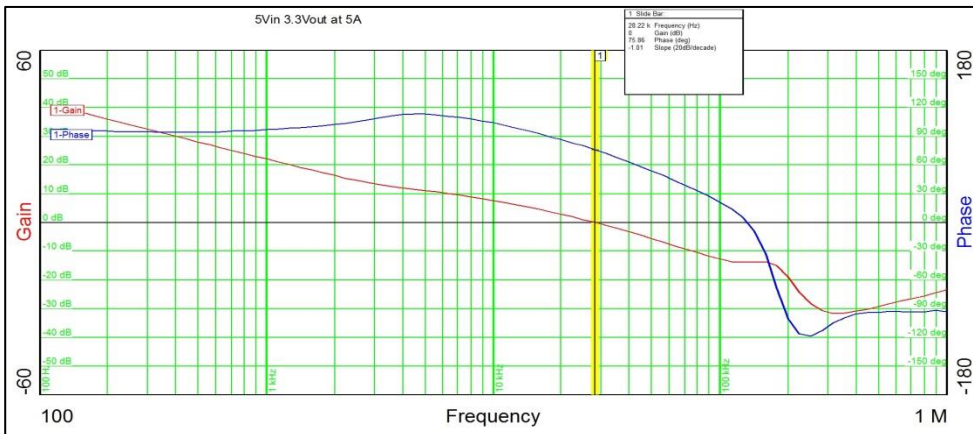- Transfer function before and after the second LC shown. There are two resonances: 25 kHz and 150 kHz.
- Simulating the power-stage gain and phase shows the output pole at 6.5 kHz.
- Measured loop response is also shown.
- <1mV ripple achieved.



Low noise: WEBENCH example

- Create design.
- Click on “Add Input EMI Filter” from design suggestions.
- Choose “Noise Standard” and “Noise Class”.

The screenshot displays the WEBENCH POWER DESIGNER interface for a power converter design. The top navigation bar includes 'NEW DESIGN' and 'MY DESIGNS'. The main header shows the design title 'Customize LM5117QPMH/NOPB - 8V-15V to 3.30V @ 10A' and input/output specifications: 'Input: DC 8V - 15V', 'Output: 3.3 V at 10 A', and 'Temp: 30 °C'. The interface is divided into several sections:

- Summary:** Displays key metrics: Efficiency: 93.8%, BOM Cost: \$6.10, and Footprint: 685 mm². A 'CHANGE OPTIMIZATION' button is present.
- Configuration Options:** Lists various parameters such as Soft Start Time (1 ms), Hold Mode Rise Time (50 ms), and switching/sync frequencies. There are radio buttons for 'User Preferred Frequency' and 'User Sync Frequency'. An 'Enable Ideal Fets' option is also visible.
- REDESIGN:** A red circle highlights the 'Design Suggestions' section, which includes the 'Add Input EMI Filter' option.
- Operating Values:** Shows 'Vin (V)' set to 15 and 'Iout (A)' set to 10. A 'RECALCULATE' button is located to the right.

The central area features a detailed circuit schematic of the power converter, including the LM5117QPMH controller, MOSFETs, diodes, and various passive components like capacitors and inductors. A disclaimer at the bottom of the schematic area states: 'This regulator device is qualified for Automotive applications. All passives and other components selected in this design may not be qualified for Automotive applications. The user is required to verify that all components in the design meet the qualification and safety requirements for their specific application. View WEBENCH(R) Disclaimer.'

Low noise: resources

Application reports:

- [Reducing output ripple and noise with the TPS84259 module.](#)
- [Not all jitter is created equal](#)
- [Reduce buck-converter EMI and voltage stress by minimizing inductive parasitics.](#)
- [Reducing noise on the output of a switching regulator.](#)
- [Understanding and managing buck regulator output ripple](#)

Technical articles:

- [Power tips: Designing a two-stage LC filter TPS54678 \(TPS54618-Q1\).](#)
- [Design a second-stage filter for sensitive applications LMZ23601.](#)

White papers:

- [Simplify low-EMI design with power modules.](#)

Reference designs:

- [Paralleling multiple LDOs \(14A\) reference design.](#)

Challenge #2: voltage regulation accuracy

As process technology advances, processor voltage requirements are lower and require high accuracy.

More Expensive Virtex Ultrascale+

Recommended Operating Conditions (16 nm)

Symbol	Description ^{1,2}	Min	Typ	Max	Units
FPGA Logic					
V _{CCINT}	Internal supply voltage	0.825	0.850	0.876	V
	For -2LE (V _{CCINT} = 0.72V) devices: internal supply voltage	0.698	0.720	0.742	V
	For -3E devices: internal supply voltage	0.873	0.900	0.927	V
V _{CCINT_IO} ³	Internal supply voltage for the I/O banks	0.825	0.850	0.876	V
	For -2LE (V _{CCINT} = 0.72V) devices: internal supply voltage for the I/O banks	0.825	0.850	0.876	V
	For -3E devices: internal supply voltage for the I/O banks	0.873	0.900	0.927	V
V _{CCBRAM}	Block RAM supply voltage	0.825	0.850	0.876	V
	For -3E devices: block RAM supply voltage	0.873	0.900	0.927	V
V _{CCAUX}	Auxiliary supply voltage	1.746	1.800	1.854	V

[DS923 - Virtex UltraScale+ FPGA Data Sheet: DC and AC Switching Characteristics \(v1.15\)](#)

V _{CCINT}	±3%
V _{CCBRAM}	±3%
V _{CCAUX}	±3%

Cheaper Spartan 7

Recommended Operating Conditions (28 nm)

Symbol	Description	Min	Typ	Max	Units
FPGA Logic					
V _{CCINT} ⁽³⁾	For -2 and -1 (1.0V) devices: internal supply voltage.	0.95	1.00	1.05	V
	For -1L (0.95V) devices: internal supply voltage.	0.92	0.95	0.98	V
V _{CCAUX}	Auxiliary supply voltage.	1.71	1.80	1.89	V
V _{CCBRAM} ⁽³⁾	For -2 and -1 (1.0V) devices: block RAM supply voltage.	0.95	1.00	1.05	V
	For -1L (0.95V) devices: block RAM supply voltage.	0.92	0.95	0.98	V
V _{CCO} ⁽⁴⁾⁽⁵⁾	Supply voltage for HR I/O banks.	1.14	-	3.465	V

[DS189 - Spartan-7 FPGAs Data Sheet: DC and AC Switching Characteristics \(v1.9\)](#)

V _{CCINT}	±3%, ±5%
V _{CCBRAM}	±3%, ±5%
V _{CCAUX}	±5%

Voltage regulation accuracy: sources of error

Sources of output voltage error:

- Routing distance and trace losses of the circuit board.
- DC/DC converter:
 - Temperature swings.
 - Input voltage variations.
 - Feedback voltage accuracy.
- Ratio of the resistor divider & tolerance of resistors.
- Voltage ripple.
- Load transients.

Voltage regulation accuracy: DC/DC converter datasheet

Choose DC/DC with $V_{FB} \leq 1\%$ accuracy

Cheaper TPS568230 17 V / 8 A

$T_J = -40^\circ\text{C}$ to 125°C , $V_{VIN} = 12\text{ V}$, unless otherwise noted

PARAMETER		TEST CONDITION	MIN	TYP	MAX	UNIT
FEEDBACK VOLTAGE						
V_{FB}	FB voltage	$T_J = 25^\circ\text{C}$	594	600	606	mV
		$T_J = -40^\circ\text{C}$ to 125°C	592	600	611	mV


More expensive TPS54824 17 V / 8 A

$T_J = -40^\circ\text{C}$ to 150°C , $V_{IN} = 4.5\text{ V}$ to 17 V (unless otherwise noted)


PARAMETER		TEST CONDITIONS	MIN	TYP	MAX	UNIT
FB						
V_{FB}	Regulated FB voltage	$T_J = 25^\circ\text{C}$	596	600	604	mV
		$T_J = -40^\circ\text{C}$ to 150°C	595	600	605	mV

- Consider line and temperature changes.
- Avoid the 'front page' accuracy number.

 Voltage regulation accuracy: remote sense




 - Ohm's Law: $V = I \times R$
- Line resistance cannot be eliminated, only reduced or managed.



- Waveforms with and without remote sensing.
- Notice voltage drop during load transient w/o remote sense.

 Maintaining voltage accuracy during load transient



- Transient from light load to heavy load creates an under shoot.
- PWM delivers maximum duty until the control loop catches up.
- Output capacitor supplies load until inductor catches up.
- Similarly when load changes from heavy load to light load, output will overshoot.
- Duty cycle goes to zero, $V_L = V_O$.

Voltage regulation accuracy: $\pm 3\%$ & $\pm 5\%$ example

$$V_{\text{UNDER}} = \frac{I \times dt}{C} \quad \text{where} \quad I = \frac{I_{\text{STEP}}}{2} \quad (\text{Avg. current})$$

$$dt = \frac{L \times dl}{D_{\text{MAX}} \times V_L} \quad \text{where} \quad dl = I_{\text{STEP}}, V_L = V_{\text{IN}} - V_O$$

$$V_{\text{OVER}} = \frac{L \times I_{\text{STEP}}^2}{2 \times C_O \times V_O} \quad (V_L \text{ is } V_{\text{out}}) \quad V_{\text{UNDER}} = \frac{L \times I_{\text{STEP}}^2}{2 \times C_O \times D_{\text{max}} \times (V_{\text{IN}} - V_O)}$$

$$C_O > \frac{L \times I_{\text{STEP}}^2}{2 \times V_{\text{OVER}} \times V_{\text{OUT}}} \quad C_O > \frac{L \times I_{\text{STEP}}^2}{2 \times V_{\text{UNDER}} \times D_{\text{max}} \times (V_{\text{IN}} - V_{\text{OUT}})}$$

Example: 4-A TPS62136

- Transient: 0.8-A to 3.2-A load step
- Input voltage: 12 V
- Output voltage: 1.8 V
- Inductor: 1.5 μH
- V_{under} : 1.746 V, 1.71 V
- V_{over} : 1.854 V, 1.89 V

C_O for $\pm 5\%$ is 26 μF

C_O for $\pm 3\%$ is 44 μF

Voltage regulation accuracy: WEBENCH example

- Transient: 1-A to 6-A load step @ 1A/us
- Input voltage: 12 V
- Output voltage: 0.85 V
- Inductor: 470 nH

3% 5%

- V_{under} : 0.825 V, 0.808 V
- V_{over} : 0.876 V, 0.893 V

Use WEBENCH to get 1% ripple and 3% transient with TPS54824.

Create a new DC/DC power design

WEBENCH® Power Designer creates customized power supply circuits based on your requirements. The environment gives you end-to-end power supply design capabilities that save you time during all phases of the design process. [Learn more](#)

Q TPS54824

Great! We found **TPS54824** and auto-filled the inputs for you

Input

Supply type is

DC AC

$V_{\text{in Min}}^*$
12 V (4.5 - 17)

$V_{\text{in Max}}^*$
12 V (4.5 - 17)

Advanced

Output

V_{out}^*
0.85 V (0.6 - 12)

$I_{\text{out Max}}^*$
6 A (0 - 8)

Isolated Output

Advanced

Design Consideration

I want my design to be

Balanced Low Cost High Efficiency Small Footprint

Design Parameters

[VIEW DESIGN TPS54824](#)

Voltage regulation accuracy: resources

Application Reports:

- [Achieving Better than 1% Output Voltage Accuracy with 40A TPS546D24A, 20A TPS546B24A, & 10A TPS546A24A](#)
- [Remote Sensing for Power Supplies](#)
- [Power Supply Design Considerations for Modern FPGAs](#)
- [Calculating Output Capacitance to Meet Transient and Ripple Requirements of Integrated POL](#)

Technical Articles:


- [“Kollman Power Tip #18” voltage dividers and Vout accuracy](#)

On-line training:

- [How to meet FPGA's DC voltage accuracy and AC load transient specification](#)

Challenge #3: higher switching frequency to reduce area

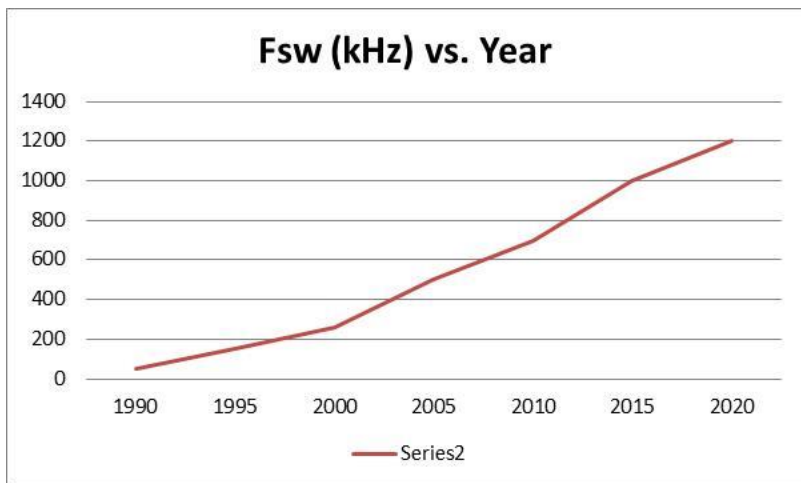Achieve higher power density by increasing the DC/DC converter's switching frequency.



- Board space is valuable.
- Suppliers are releasing faster DC/DC converters that claim to save space.
 - How much space is really saved?
 - What are the trade-offs?

Higher switching frequency: considerations

Switching frequency considerations:

- Minimum on-time.
- Pulse-skipping.
- Efficiency and power losses.
- LC filter area.
- Voltage ripple.
- Transient response.
- Component cost.

Higher switching frequency: minimum on-time

Check the minimum controllable on-time in the datasheet, not the maximum oscillator frequency!

100-V synchronous buck DC/DC controller with wide duty cycle

LM5146-Q1 PWM Control		Min	Typ	Max	unit
$t_{ON(MIN)}$	Minimum controllable on-time		40	60	ns
$t_{OFF(MIN)}$	Minimum off-time		140	200	ns
DC _{100kHz}	Maximum duty cycle	98%	99%		
DC _{400kHz}		90%	94%		

Min. Duty Cycle = Min. On time x Switching Frequency

$$0.06 = 60 \text{ ns} \times 1 \text{ MHz}$$

Examples at 1 MHz:

$$0.8 \text{ V}_{OUT} = V_{INMAX} \times 0.06; V_{INMAX} = 13 \text{ V}$$

$$3.3 \text{ V}_{OUT} = V_{INMAX} \times 0.06; V_{INMAX} = 55 \text{ V}$$

Pulse-skipping happens when the DC/DC converter cannot extinguish the gate drive pulses fast enough to maintain the desired duty cycle.

- Converter will still regulate, but:
- Ripple voltage increases due to the pulses being further apart.
- Frequency is no longer predictable.
- Current limit may no longer work since the IC cannot respond in time.
- Control loop may be unstable. Transient response is also affected.
- Reduce F_{sw} , lower the input voltage, or pick a different part.



Higher switching frequency: power loss & efficiency

Design example (TPS54388C-Q1):

- 5 V_{IN}, 1.8 V_{OUT}, 3 A, 20-mV ripple, 1A_{p-p}
- Total power loss 350 kHz: 0.95 W
- Total power loss 1.6 MHz: 1.15 W

Power losses:

 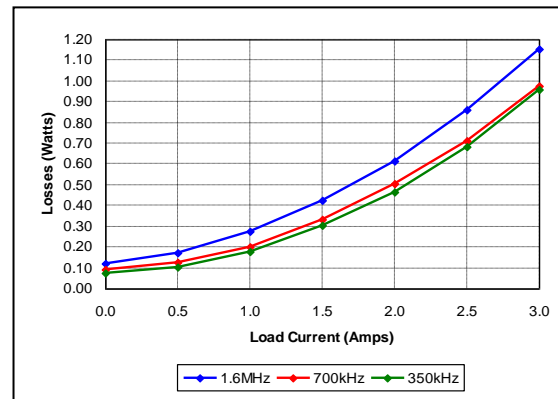- FET driving loss ($Q_g * V * F_{sw}$)
- FET switching loss $f(V_{in}, I_{out}, T_{on/off}, F_{sw})$
- FET resistance ($I^2 * R_{ds(on)}$)
- Inductor loss ($I^2 * DCR + \text{Core losses}$):
- Capacitor loss ($I_{RMS}^2 * ESR$)
- IC loss (I_q)



Higher switching frequency: transient & ripple

$$L = V * \Delta I / \Delta t$$

$$L \geq V_{out} * (1-D) / (\Delta I * F_s)$$

$\Delta I = 1-A$ peak to peak

- 350 kHz: $L \geq 3.3 \mu\text{H}$ → Choose 3.5 μH (84mm²)
- 1.6 MHz: $L \geq 0.7 \mu\text{H}$ → Choose 1.0 μH (41mm²)

$R = V/I$ → $\text{ESR} \leq \Delta V / \Delta I$; use 0 m Ω for ceramic





$I = C * dv/dt$ → $C \geq \Delta I / (8 * F_s * \Delta V)$

Total $\Delta V = \Delta I / (8 * C * F_s) * 2$ (to account for DC bias)

- 350 kHz: $C \geq 36 \mu\text{F}$ → Choose 47 μF 1206 (5mm²)
- 1.6 MHz: $C \geq 7.9 \mu\text{F}$ → Choose 10 μF 0603 (1.4mm²)

Space savings: 45 mm²

Not counting keep-out

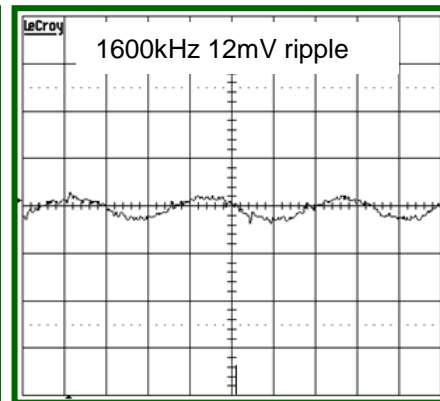 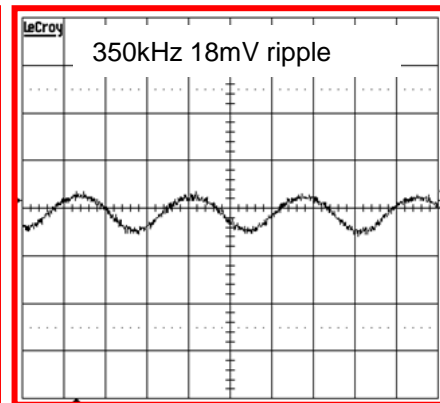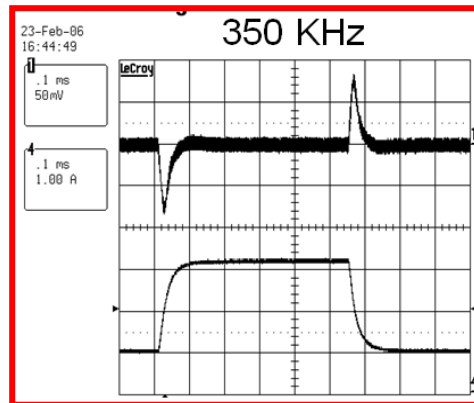

Higher switching frequency: WEBENCH example

- Customer using LM61460
- $V_{IN}=24$, $V_{OUT}=3.3$ $I_{OUT} = 5$ A
- What are some of the ways we can use WEBENCH to reduce the overall size of our design?

The screenshot displays the WEBENCH POWER DESIGNER interface. At the top, there is a red navigation bar with the text "WEBENCH® POWER DESIGNER" and "MY DESIGNS" with a user icon. Below the navigation bar, the main heading reads "Create a new DC/DC power design". A sub-heading states: "WEBENCH® Power Designer creates customized power supply circuits based on your requirements. The environment gives you end-to-end power supply design capabilities that save you time during all phases of the design process. [Learn more](#)".

A search bar contains the text "LM61460" and a close button (X). Below the search bar, a message says: "Great! We found **LM61460** and auto-filled the inputs for you".

The interface is divided into two main columns: "Input" and "Output".

Input Section:

- Supply type is: DC AC
- Vin Min * V (range: 3 - 36)
- Vin Max * V (range: 3 - 36)
- Advanced options (dropdown arrow)

Output Section:

- Vout * V (range: 1 - 34.2)
- Iout Max * A (range: 0 - 6)
- Isolated Output
- Advanced options (dropdown arrow)

Design Consideration Section:

- I want my design to be:
- Balanced Low Cost High Efficiency Small Footprint
- Design Parameters (dropdown arrow)

At the bottom, there is a red button labeled "VIEW DESIGN LM61460".

Higher switching frequency: WEBENCH example

- Beginning size with "balanced" design=146 mm²
- Efficiency 85.7%
- Now let's click "Change Optimization"

Optimization options

	Small Footprint Design	Low Cost Design	Balanced Design	High Efficiency Design
Efficiency	81.2 %	84.1 %	85.7 %	88.4 %
Bom Cost	\$3.74	\$4.74	\$3.82	\$4.72
Footprint	130 mm ²	138 mm ²	146 mm ²	181 mm ²
	SELECT	SELECT	SELECT	SELECT

Higher switching frequency: resources

Application Notes:

- [Benefits of a Multiphase Buck Converter](#)


Technical Articles:

- [Trade-Offs In Switching High-Input-Voltage Step-Down Converters at High Frequencies](#)
- [Choosing the optimum switching frequency of your DC/DC converter](#)

Challenge #4: safe operating area

Will the small QFN package of the DC/DC converter or the power module handle the rated high current?

 
- Safe Operating Area (SOA) represents operating conditions where the maximum electrical and thermal rating of the component will not be exceeded.
- Recommended operating points are always less than the SOA limits.
- Cooler is always better for reliability.



SOA: using SOA curves


- SOA curves tell the designer:
 - Desired current at the desired T_a .
 - Airflow is needed.
 - How much margin or reserve is available.
- The farther the operating point is from the SOA boundary, the cooler the supply will operate.
- SOA curves do *not* represent thermal shutdown points. Some products will not reach shutdown until pushed past SOA limits.
- Catalog current rating may be rated under different conventions.

SOA: comparison

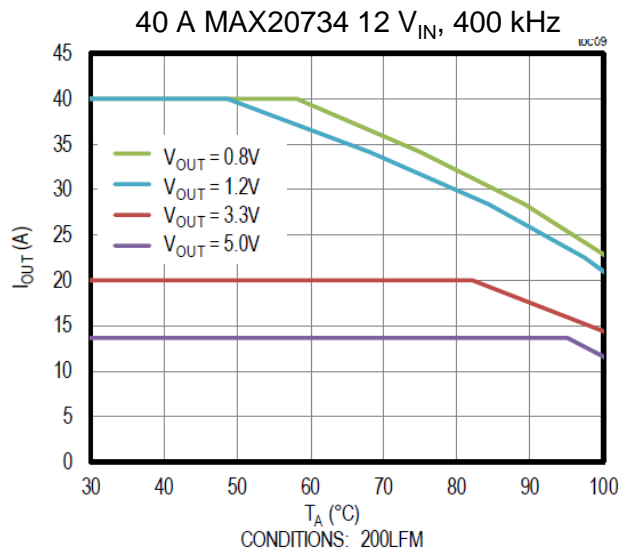

- 22A @ 84C Ta, no airflow, 30A @ 84C, 200LFM
- EVM board results shown with 4 layers of 2 oz copper

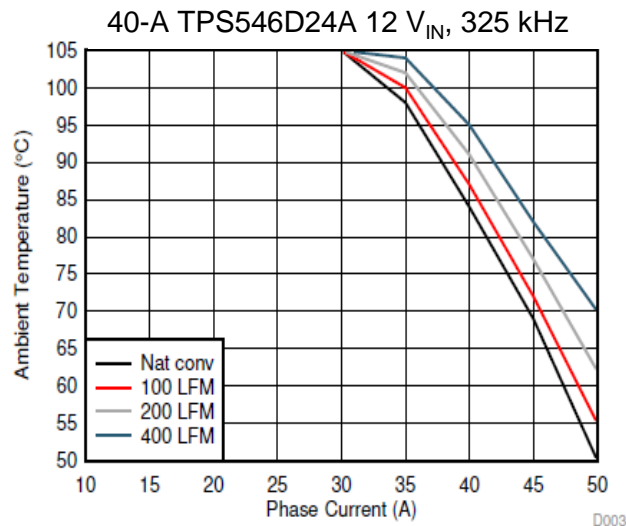
4.15x9 mm QFN
JEDEC $\theta_{JA} = \text{N/A } ^\circ\text{C/W}$
EVM $\theta_{JA} = 12^\circ\text{C/W}$



- 40A @ 84C Ta, no airflow
- EVM board results shown with 4 layer, 2 oz copper

5x7 mm Clip QFN
JEDEC $\theta_{JA} = 28.9^\circ\text{C/W}$
EVM $\theta_{JA} = 8.1^\circ\text{C/W}$

 SOA: rough estimation using SOA and θ_{JA}



TPSM84824 example:


- 12 V_{IN} , 3.3 V_{OUT} , 8 A , 1 MHz
- $T_A = 70^\circ\text{C}$, no airflow
- $\theta_{JA} = 12^\circ\text{C/W}$ (4 layer, 2 oz copper-100 mmx100 mm)

Will it work?

- SOA curve inspection passes $70^\circ\text{C } T_A$ with 5°C margin

What temperature will the module heat up to?

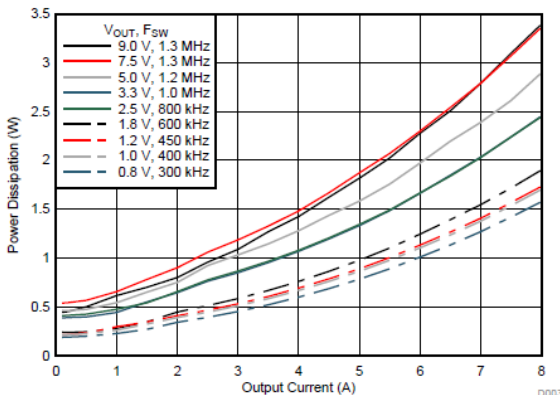- $8\text{ A @ } 3.3\text{ V}$ dissipates 2.7 W
- $2.7\text{ W} \times 12^\circ\text{C/W} = 32^\circ\text{C}$ temp rise above ambient
- Module junction temperature will be $\sim 102^\circ\text{C}$



SOA: what does WEBENCH say?

TPSM84824 example:

- $12V_{IN}$, $3.3V_{OUT}$, 8A, 1 MHz
- $T_A = 70^\circ\text{C}$, no airflow
- $\theta_{JA} = 12^\circ\text{C/W}$ (4 layer, 2 oz copper-100 mmx100 mm)

Will it work?

Oh NO!

Let's try 65°C

SUCCESS!

Takeaway, We are very close to the edge with this design.

The screenshot displays the WEBENCH POWER DESIGNER interface. At the top, the title bar reads "WEBENCH® POWER DESIGNER" with navigation links for "NEW DESIGN" and "MY DESIGNS". The main header shows the project name "Customize TPSM84824MOLR - 12V-12V to 3.30V @ 8A" and input/output specifications: "Input: DC 12 V - 12 V", "Output: 3.3 V at 8 A", and "Temp: 65 °C".

The interface is divided into several sections:

- Summary:** Shows Efficiency: 91.6%, BOM Cost: \$6.64, and Footprint: 160 mm². A red "CHANGE OPTIMIZATION" button is present.
- Configuration Options:** Includes three toggle switches: "User Preferred Frequency" (checked), "User Sync Frequency" (unchecked), and "Programmable UVLO" (unchecked). Below each toggle are numerical values and ranges for switching frequency, sync frequency, and UVLO voltage.
- Schematic:** Displays a circuit diagram of the TPSM84824MOLR converter. The input is labeled V_{in} and the output is labeled V_{out} . The schematic includes input capacitors C_{in} and C_{in1} , a feedback network with resistors R_{fb} and R_{fb1} , and a load resistor R_{load} .
- Operating Values:** Shows V_{in} (V) set to 12 and I_{out} (A) set to 8. A "RECALCULATE" button is available.

SOA: resources

Application Reports:

- [Method of Graphing Safe Operating Area \(SOA\) Curves for DC-DC Converters](#)
- [Understanding the thermal-resistance specification of DC/DC converters with integrated power MOSFETs](#)
- [How to Evaluate Junction Temperature Properly with Thermal Metrics](#)
- [Improving the Thermal Performance of a MicroSiP™ Power Module](#)

Challenge #5: control mode confusion

There are a lot of control mode architectures to chose!
Which one is best for my application?

A screenshot of a parametric search filter. The 'Control Mode' section is expanded, showing a list of options: Constant on-time (COT), Current Mode, D-CAP, D-CAP+, D-CAP2, and D-CAP3. A grey box below the list indicates '844 total parts'. At the bottom of the filter, there is a 'Duty Cycle (Max) (%)' dropdown menu.

2300	0.6	Dynamic Voltage Scaling, Enable, Frequency Synchronization, Light Load Efficiency, Phase Interleaving, Power Good, Synchronous Rectification, UVLO Adjustable	Current Mode
580	0.4	Enable, Synchronous Rectification	D-CAP2
580	0.4	Enable, Light Load Efficiency, Synchronous Rectification	D-CAP2
2000	4.3	Adjustable Current Limit, Enable, Frequency Synchronization, N/A, Over Current Protection, Phase Interleaving, Power Good, Pre-Bias Start-Up, Remote Sense, Synchronous Rectification	Current Mode

Control mode information located in the parametric search.

Control mode: history – buck converters and controllers

Linear control

Voltage mode

- Good noise margin with fixed ramp amplitude
- Higher component count for compensation

Current mode

- Fast response to output current changes
- Fewer components than VM
- Sensitive to current noise

Voltage mode w/ feed forward

- Ramp slope varies with input voltage
- Fast change to input voltage variation
- Higher component count for compensation

Emulated current mode

- Ramp current estimated with sample and hold circuit
- Very small duty cycles w/o current noise susceptibility
- High duty cycles difficult due to S&H blanking time

Internally compensated advanced current mode

- Internally generated ramp to represent inductor current
- No loop compensation required
- Allows wide output capacitance range
- Higher frequency, faster min on-time

Non-linear control

Constant on-time

- Fast transient response
- On-time proportional to input voltage
- No loop compensation
- Jitter. Frequency not fixed

D-CAP

- Fast transient response
- On-time proportional to input and output voltage
- No loop compensation
- Needs ESR capacitance
- Frequency not fixed

D-CAP+

- Fast transient with single V_{out} multiphase (load line)
- On pulse issued when summed inductor current is lower than desired target
- No loop compensation

D-CAP2

- Fast transient response
- Same as D-CAP but with ripple injection circuit for ceramic output caps
- No loop compensation
- Frequency not fixed
- Offset voltage affects V_{ref}

D-CAP3

- Fast transient response
- Same as D-CAP2 but with sample and hold circuit to reduce injection circuit offset voltage for higher V_{ref} accuracy
- No loop compensation


Synchronizable constant on-time

- Fast transient response
- Same as COT, but sync's to external clock during steady state
- Uses Ceramic capacitance
- Low duty cycle, fast minimum on-time
- No loop compensation


Timeline

Control mode: basic circuit block elements


Error amplifier

 


Oscillator

 


PWM comparator

 

One shot timer

 


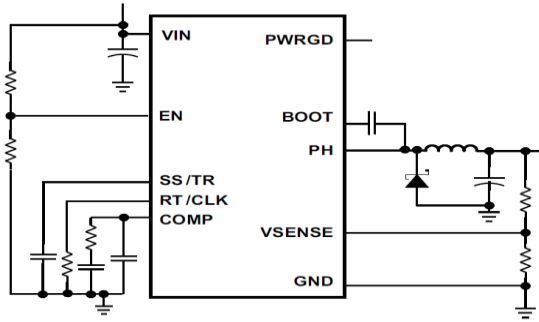Control mode: internal, external, or no compensation




External compensation

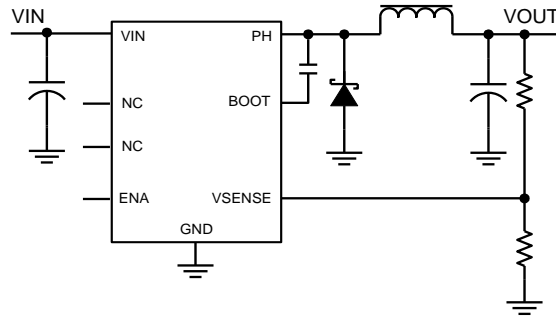- Control over gain and phase margin.
- Wide selection of filter components.
- Flexible switching frequency.
- Complex small-signal feedback network.



Internal compensation

 
- Fewer external components.
- Easy design & less verification.
- Limited L & C components.
- Be careful with large number bypass capacitance.




No compensation

- D-CAP versions, DCS or Constant On Time (COT).
- Fast transient response.
- Easy design & less verification.
- Limited L & C components.

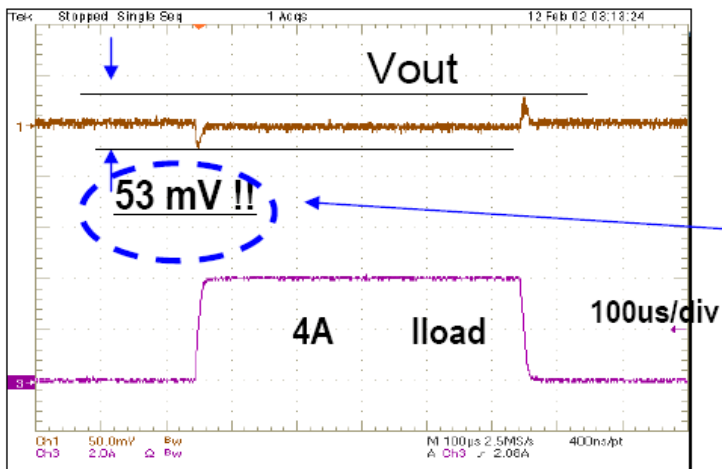Control mode: linear and non-linear transient response



Non-linear D-CAP mode
transient response

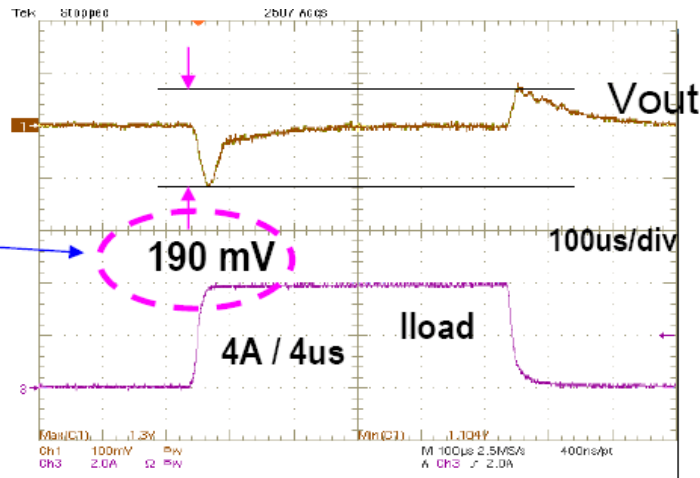

Linear voltage mode
transient response

$C_{out}=22\mu F \times 3$



$C_{out}=100\mu F \times 4$

Control mode: rules of thumb

Concern	Linear control	Non-linear control
Frequency behavior	Predictable	Not so predictable
Synchronization	With Frequency Sync pin	Not possible over dynamic load condition
Transient response	Typically slower. Needs to wait for clock pulse	Typically faster. No internal clock circuit
Load profile	Signal chain power, noise sensitive PCB area, static load behavior	Higher current, dynamic load conditions. "Moving data around"
Typical market segment	Industrial, Communications, Automotive	Enterprise, Personal Electronics
Customer effort	External compensation needs customer validation effort. Internal compensation limits components	Less customer validation effort. Limits external capacitance selection
External components	Most flexibility with output capacitance with external compensation	Limited flexibility with output capacitance, fewer Cout to meet overshoot/undershoot
Models	Average, Transient	Transient. Average models are difficult
WEBENCH support	Yes. WEBENCH can help compensate	Yes

In some cases, customers don't understand control mode nuances, but want "easy, or "fewer caps"

Control mode: WEBENCH example


TPS54824 example:

- 12-14 V_{IN} , 1.2 V_{OUT} , 8 A
- Required Inductor from Customer AVL:
 - Coilcraft
 - XAL1010-822MEB
 - 8.2 μH

Original WEBENCH design:

- 1.2 μH Coilcraft
- Switching Freq: 374.6 kHz
- Crossover Freq: 37.5 kHz
- Phase Margin: 67.8 Deg
- Gain Margin: -18.2 dB

All point to good stability.

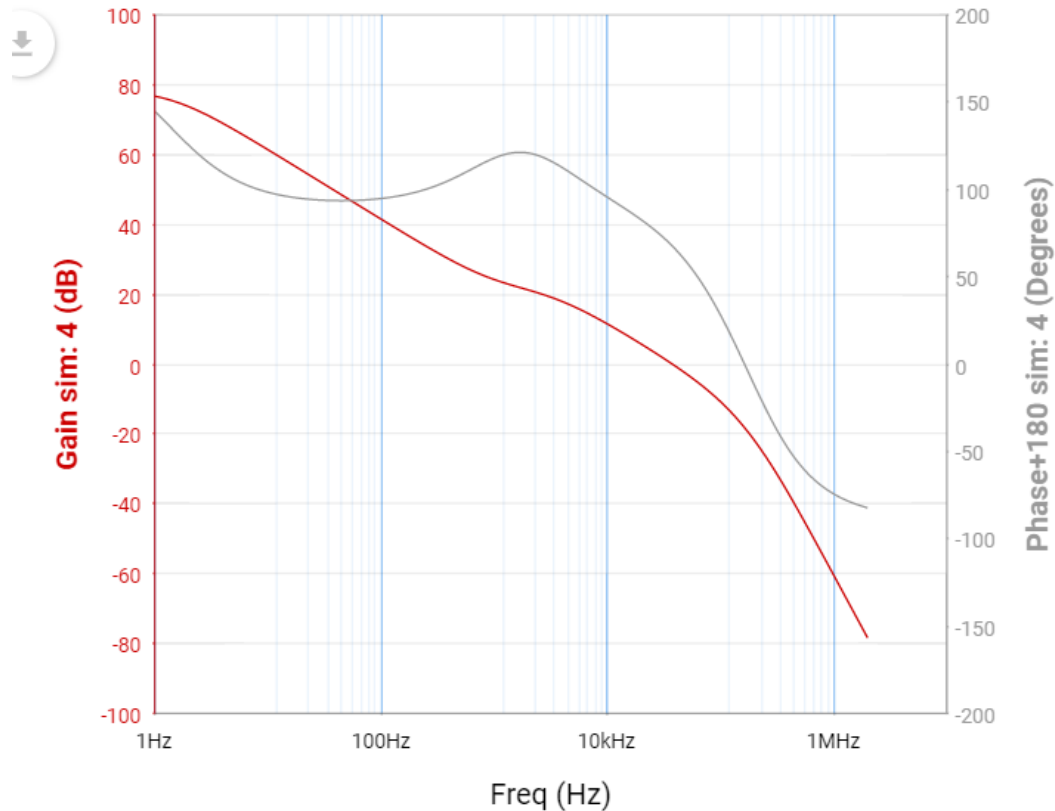

Control mode: resources

Reference Guides:

- [Control-Mode Quick Reference Guide](#)

Application Reports:

- [Choosing the Right Fixed-Frequency Buck-Regulator Control Strategy](#)
- [Choosing the Right Variable-Frequency Buck-Regulator Control Strategy](#)
- [How to Measure the Loop Transfer Function of Power Supplies](#)
- [Understanding Frequency Variation in the DCS-Control™ Topology](#)

White Papers:

- [Internally Compensated Advanced Current Mode \(ACM\)](#)

Technical Articles:

- [Comparing Internally-compensated Advanced Current Mode \(ACM\) with D-CAP3™ Control](#)

Remember!

- TI DC/DC solutions and content help customers solve their problems.
- When using Embedded Processing and Signal-Chain products, remember TI DC/DC conversion products address both processor and signal-chain power concerns.
- Use WEBENCH to help understand the trade-offs as well as find working solutions.
- Our factory applications engineers are here to help.
- [Check out](#): The Essential Collection of DC/DC Buck Switching Regulator Technical Documentation.



©2020 Texas Instruments Incorporated. All rights reserved.

The material is provided strictly "as-is" for informational purposes only and without any warranty.
Use of this material is subject to TI's **Terms of Use**, viewable at [TI.com](https://www.ti.com)

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale (www.ti.com/legal/termsofsale.html) or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2020, Texas Instruments Incorporated