

# Reducing effects of external RC filter circuit on gain and drift error for integrated analog front ends (AFEs): $\pm 10V$




Cynthia Sosa

Input	ADC Input	Digital Output
VinMin = -10V	AIN-xP = -10V, AIN-xGND = 0V	-32768 <sub>10</sub> , 8000 <sub>H</sub>
VinMax = 10V	AIN-xP = 10V AIN-xGND = 0V	32767 <sub>10</sub> , 7FFF <sub>H</sub>

Power Supplies	
AVDD	DVDD
5V	5V
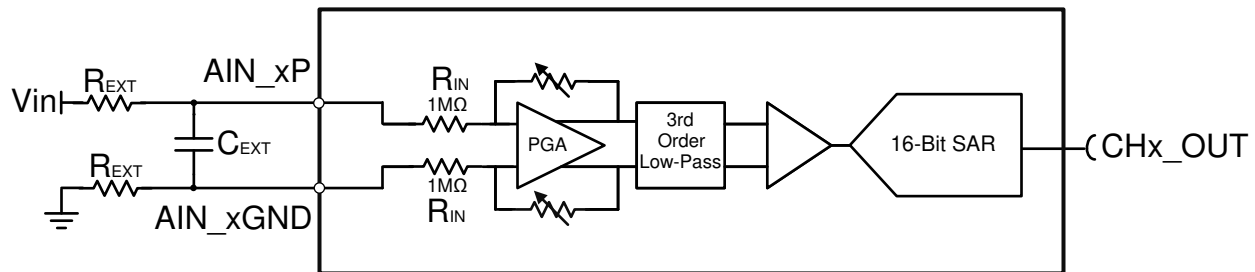
## Design Description

This cookbook design describes how to select filter component values and how to minimize the gain error and drift introduced by this filter on a fully-integrated analog front end (AFE) SAR ADC. The design uses the input impedance drift at the full scale range of  $\pm 10V$  of the ADS8588S. This external RC filter minimizes external noise and provides protection from electrical overstress. Minimizing gain error and drift are important to end equipment such as: [Multi-Function Relays](#), [AC Analog Input Modules](#), and [Terminal Units](#). This design describes two correction methods, a no-calibration correction factor and a 2-point calibration. Implementing calibration can minimize both the gain error introduced by the external resistor and the internal device gain error to negligible levels.



## Specifications

Specification	Calculated	Measured
Introduced Gain Error (25°C)	0.9901%	0.9894%
Introduced Gain Error (125°C)	0.995%	-1.1388%
Introduced Gain Error Drift	0.49ppm/°C	-0.8031ppm/°C

## Design Notes

1. Use low drift  $R_{EXT}$  resistors to maintain low drift and minimize gain error. This design uses resistors with a temperature coefficient of 25ppm/°C and  $\pm 0.1\%$  tolerance.
2. The internal programmable gain amplifier (PGA) presents a constant resistive impedance of 1MΩ.
3. The  $R_{EXT}$  value introduced is directly proportional to the introduced error.
4. Calibration can also be used to eliminate system offset gain error.

5. The *TI Precision Labs – ADCs* training video series covers methods for calculating gain and offset error and eliminating these errors through calibration, see *Understanding and Calibrating the Offset and Gain for ADC Systems. Using SPICE Monte Carlo Tool for Statistical Error Analysis* explains how to use *Monte Carlo Analysis* for statistical error analysis.

### Component Selection

External anti-aliasing RC filters reduce noise and protect from electrical overstress; if a large resistor value is used, then this further limits the input current. A large external resistive value also provides a low cutoff frequency, which is desired for relay protection applications as the input frequencies are usually 50 or 60Hz. Furthermore, a balanced RC filter configuration is required for better common-mode noise rejection; matching external resistors are present on both the negative and positive input paths. To minimize the introduced drift error, the external resistors need to be low drift; 25ppm/°C resistors.

1. Choose a high-value  $R_{EXT}$  based on the desired cutoff frequency. A cutoff frequency of 320Hz was used to eliminate harmonics from a 50 or 60Hz input signal.

$$R_{EXT} = 10k\Omega$$

2. Choose  $C_{EXT}$

$$C_{EXT} = \frac{1}{2 \cdot \pi \cdot f_C \cdot 2 \cdot R_{EXT}} = \frac{1}{2 \cdot \pi \cdot 320\text{Hz} \cdot 2 \cdot 10k\Omega} = 24.8\text{nF}$$

Nearest standard capacitor value available,  $C_{EXT} = 24\text{nF}$

### Calculate Gain Error Drift

This section demonstrates how to calculate the introduced gain error drift. The additional drift from the external filter resistor is small compared to the internal device drift.

$$R_{IN} = 1M\Omega, R_{EXT} = 10k\Omega, C_{EXT} = 24\text{nF}$$

1. Calculate effective internal impedance due to maximum negative drift (–25ppm/°C)

$$R_{IN(-25\text{ppm}/^\circ\text{C})} = R_{IN} \cdot [\text{Drift}(\text{ppm} / ^\circ\text{C}) \cdot \delta T(^{\circ}\text{C}) + 1]$$

$$R_{IN(-25\text{ppm}/^\circ\text{C})} = 1M\Omega \cdot [-25\text{ppm} / ^\circ\text{C} \cdot (125^{\circ}\text{C} - 25^{\circ}\text{C}) + 1]$$

$$R_{IN(-25\text{ppm}/^\circ\text{C})} = 0.9975M\Omega$$

2. Calculate effective external resistance due to maximum positive drift (25ppm/°C)

$$R_{EXT(+25\text{ppm}/^\circ\text{C})} = R_{EXT} \cdot [\text{Drift}(\text{ppm} / ^\circ\text{C}) \cdot \delta T(^{\circ}\text{C}) + 1]$$

$$R_{EXT(+25\text{ppm}/^\circ\text{C})} = 10k\Omega \cdot [25\text{ppm} / ^\circ\text{C} \cdot (125^{\circ}\text{C} - 25^{\circ}\text{C}) + 1]$$

$$R_{EXT(+25\text{ppm}/^\circ\text{C})} = 10.025k\Omega$$

3. Calculate nominal gain error introduced by the external resistor at room temperature

$$\text{GainError}(R_{EXT})_{\text{RoomTemp}} = \frac{1}{1 + \frac{R_{IN}}{R_{EXT}}}$$

$$\text{GainError}(R_{EXT})_{\text{RoomTemp}} = \frac{1}{1 + \frac{1M\Omega}{10k\Omega}}$$

$$\text{GainError}(R_{EXT})_{\text{RoomTemp}} = 0.009901 \text{ or } 0.9901\%$$

4. Calculate nominal gain error introduced by the external resistor at highest rated temperature

$$\text{GainError}(R_{\text{EXT}})_{125^{\circ}\text{C}} = \frac{1}{1 + \frac{0.9975\text{M}\Omega}{10.025\text{k}\Omega}}$$

$$\text{GainError}(R_{\text{EXT}})_{125^{\circ}\text{C}} = 0.009950 \text{ or } 0.995\%$$

5. Calculate gain error drift introduced by the external resistor

$$\text{GainError\_Drift}(R_{\text{EXT}}) = \frac{\text{GainError}(R_{\text{EXT}})_{\text{RoomTemp}} - \text{GainError}(R_{\text{EXT}})_{125^{\circ}\text{C}}}{\delta T} \cdot 10^6$$

$$\text{GainError\_Drift}(R_{\text{EXT}}) = \frac{0.009901 - 0.00950}{(125^{\circ}\text{C} - 25^{\circ}\text{C})} \cdot 10^6$$

$$\text{GainError\_Drift}(R_{\text{EXT}}) = -0.49\text{ppm} / ^{\circ}\text{C}$$

The maximum gain error temperature drift of the ADS8588S is  $\pm 14\text{ppm}/^{\circ}\text{C}$ , which is orders of magnitude larger than the calculated drift error introduced, making the introduced error negligible. The minimal drift error introduced by the external resistors has greatly to do with the low drift coefficient of the input impedance ( $\pm 25\text{ppm}/^{\circ}\text{C}$ ).

To measure the introduced gain error drift, two test signals are sampled and applied at 0.5V from the full scale input range within the linear range of the ADC. The signals are applied and sampled with and without the external RC filter present. These measurements are performed at both temperatures, 25°C and 125°C. The percent gain errors are solved for by finding the percent error of the ideal slope and the measured slope for each of the four distinctive test conditions, resulting in four distinct percent gain error measurements. The drift (ppm/°C) with and without the RC present is then calculated by converting the percent gain errors to decimal format then following step 5 shown above. The introduced gain error drift is then solved for by subtracting the drift of the RC and no RC present.

### Uncalibrated Correction

An uncalibrated correction targets to solve the input voltage before any losses occur due to the RC filter by working backwards from the ADC measured samples using a voltage divider.

1. Apply known test signal and measure equivalent code

$V_{\text{in}}$	Measured Code	Equivalent Measured Input
9.5V	30841	9.412

2. Calculate the input voltage before RC losses

$$V_{\text{IN\_NoLoss}} = V_{\text{IN\_Equivalent}} \cdot \frac{R_{\text{EXT}} + R_{\text{IN}}}{R_{\text{IN}}}$$

$$V_{\text{IN\_NoLoss}} = 9.412 \cdot \frac{1\text{M}\Omega + 10\text{k}\Omega}{1\text{M}\Omega}$$

$$V_{\text{IN\_NoLoss}} = 9.50612\text{V}$$

### Uncalibrated Correction Measurements

Using a voltage correction can be beneficial, but not the most comprehensive. The correction factor can have a worst-case error of 0.2456% at room temperature due to change in internal impedance.

Room Temperature (25°C) Measurements				
$V_{\text{in}}$	Code	Reading	Correction	Error %
9.5	30841	9.412	9.506120	0.0644
8.5	27594	8.421	8.505210	0.0613

Room Temperature (25°C) Measurements				
V <sub>in</sub>	Code	Reading	Correction	Error %
5	16232	4.954	5.003540	0.0708
0	1	0	0.000000	–
–5	–16230	–4.953	–5.002530	0.0506
–8.5	–27593	–8.421	–8.505210	0.0613
–9.5	–30839	–9.411	–9.505110	0.0538

## 2-Point Calibration Method

A two point calibration applies and samples two test signals at 0.5V from the full scale input range within the linear range of the ADC. These sample measurements are then used to calculate the slope and offset of the linear transfer function. Calibration eliminates both the gain error introduced by the external resistor and the internal device gain error.

1. Apply test signal at 2.5% of input linear range

V <sub>min</sub>	Measured Code
–9.5V	–30839

2. Apply test signal at 97.5% of input linear range

V <sub>max</sub>	Measured Code
9.5V	30841

3. Calculate slope and offset calibration coefficients

$$m = \frac{\text{Code}_{\text{max}} - \text{Code}_{\text{min}}}{V_{\text{max}} - V_{\text{min}}}$$

$$m = \frac{30841 - (-30839)}{9.5 - (-9.5)} = 3246.3158$$

$$b = \text{Code}_{\text{min}} - m \cdot V_{\text{min}}$$

$$b = (-30839) - 3246.3 \cdot (-9.5 \text{ V}) = 1.0001$$

4. Apply calibration coefficient to all subsequent measurements

$$V_{\text{in Calibrate}} = \frac{\text{Code} - b}{m}$$

$$V_{\text{in Calibrate}} = \frac{30841 - 1.0001}{3246.3158} = 9.5000$$

## 2-Point Calibration Method Measurements

Calibration Coefficients

$$m = 3246.3158; b = 1.0001$$

At room temperature without calibration, a gain error is present. Once calibration is applied to the measured results from the ADC, the gain error is minimized to nearly zero.

Room Temperature (25°C) Measurements					
V <sub>IN</sub>	Code	Uncalibrated V <sub>IN</sub>	Calibrated V <sub>IN</sub>	Voltage Error Without Calibration %	Voltage Error With Calibration %
9.5	30841	9.412	9.500000	–0.926316	–0.000001
8.5	27594	8.421	8.499789	–0.929412	–0.002480

Room Temperature (25°C) Measurements					
V <sub>IN</sub>	Code	Uncalibrated V <sub>IN</sub>	Calibrated V <sub>IN</sub>	Voltage Error Without Calibration %	Voltage Error With Calibration %
5	16232	16232	4.999822	-0.920000	-0.003568
0	1	0	0.000000	-	-
-5	-16230	-4.953	-4.999822	-0.0940000	-0.003567
-8.5	-27593	-8.421	-8.500097	-0.929412	0.001144
-9.5	-30839	-9.411	-9.500000	-0.936842	0.000000

When exposed to high temperatures, the gain error increases, as expected. Once calibration is applied, the voltage error is decreased but not eliminated; the error still present is the drift error.

High Temperature (125°C) Measurements					
V <sub>IN</sub>	Code	Uncalibrated V <sub>IN</sub>	Calibrated V <sub>IN</sub>	Relative Voltage Error Without Calibration %	Relative Voltage Error With Calibration %
9.5	30826	9.407	9.495379	-0.978947	-0.048639
8.5	27582	8.417	8.496093	-0.976471	-0.045968
5	16224	4.951	4.997357	-0.980000	-0.052854
0	0	0	-0.000308	0	-
-5	-16224	-4.951	-4.997973	-0.980000	-0.040531
-8.5	-27581	-8.417	-8.496401	-0.976471	-0.042344
-9.5	-30826	-9.407	-9.495995	-0.978947	-0.042153

## Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

## Design Featured Devices

Device	Key Features	Link	Similar Devices
<a href="#">ADS8588S</a>	16-bit, high-speed 8-channel simultaneous-sampling ADC with bipolar inputs on a single supply	<a href="http://www.ti.com/product/ADS8588S">www.ti.com/product/ADS8588S</a>	<a href="http://www.ti.com/adcs">www.ti.com/adcs</a>

## Trademarks

All trademarks are the property of their respective owners.

## Revision History

NOTE: Page numbers for previous revisions may differ from page numbers in the current version.

Changes from Revision A (January 2019) to Revision B (September 2024)	Page
• Updated the format for tables, figures, and cross-references throughout the document.....	1
<hr/>	
Changes from Revision * (April 2018) to Revision A (January 2019)	Page
• Downscale title, updated header on first page.....	1

## IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to [TI's Terms of Sale](#) or other applicable terms available either on [ti.com](https://www.ti.com) or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2024, Texas Instruments Incorporated