

Optimize Output Filter on D-CAP2™ for Stability Improvement

Antony Ahn

ABSTRACT

Buck converters using D-CAP2™ mode control scheme are used in applications such as personal electronics and industrial and automotive systems. D-CAP2 mode supports superior load transient response with high system bandwidth (F_{co}). Its internal ripple injector block allows for low equivalent series resistance (ESR)-type output capacitor usage and reinforces loop stability. Although D-CAP2 mode ensures stability without external compensation components, optimizing the output filter in the design stage maximizes stability results to meet local specifications. This application report shows how to visually interpret D-CAP2 mode control to improve stability.

Contents

1	D-CAP2™ Characteristics in the Frequency Domain	2
2	Improve Phase Margin by Visual Interpretation	3
3	Conclusion	7
4	References	7

List of Figures

1	Ripple Injection of D-CAP2™	2
2	Gain and Phase Movement of D-CAP2™	3
3	Phase Margin of the TPS54327 and Phase Drop Caused by On-Time Delay	4
4	On-Time Versus Phase Delay of the TPS54327	4
5	Reducing Corner Frequency (F_n) and Bandwidth	5
6	Output Voltage Level Versus Bandwidth	6
7	Increasing Corner Frequency (F_n) and Bandwidth	7

List of Tables

1	TPS54327 PM and BW Results According to V_{IN} With Fixed $1.05 V_{OUT}$	3
2	TPS54327 PM and BW Results According to L, C in $5 V_{IN}$ to $1.05 V_{OUT}$ Condition	5
3	TPS54327 PM and BW Results According to V_{OUT} With Fixed $12V_{IN}$	6
4	TPS54327 PM and BW Results According to L, C in $12 V_{IN}$ to $5 V_{OUT}$ Condition.....	7


Trademarks

D-CAP2 is a trademark of Texas Instruments.
 Mathcad is a trademark of PTC Inc.
 All other trademarks are the property of their respective owners.

1 D-CAP2™ Characteristics in the Frequency Domain

1.1 Internal Ripple Injector of D-CAP2™

Figure 1 shows how D-CAP2 mode control has an internal ripple injection block and how the block catches inductor current information. The R_F and C_F network across the inductor generate voltage ripple that is sent to the IC's feedback node (V_{FB}). This feedback results in high field effect transistor (FET) turnon of the internal comparator and allows for low ESR-type capacitor usage such as with the multi-layer ceramic capacitor (MLCC).

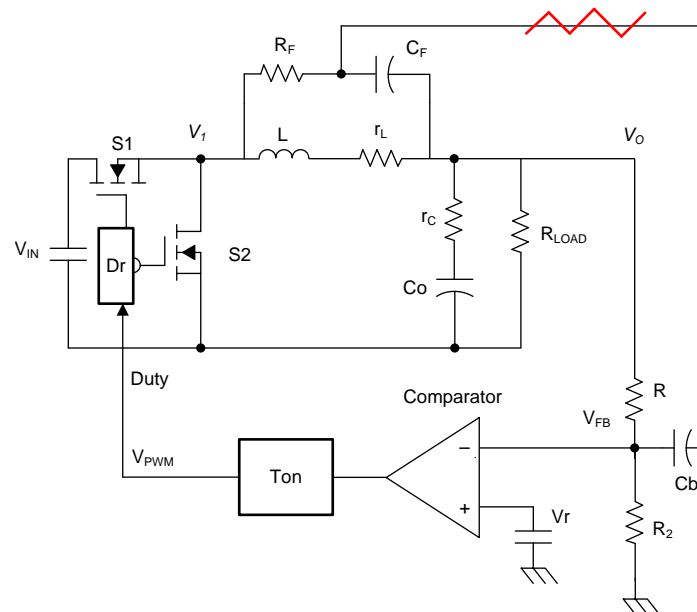

Copyright © 2017, Texas Instruments Incorporated

Figure 1. Ripple Injection of D-CAP2™

1.2 Frequency Domain Analysis With Ripple Injector of D-CAP2™ Converter

The TPS54327, a D-CAP2 converter, has an internal, radio-controlled (RC) network for receiving ripple information from the switching node. When the sensed ripple voltage hits the internal reference, high-side FET is turned on and sustained on-time by an internal timing generator. In the frequency domain, the ripple injector generates additional zero which increases gain and boosts phase movement at its zero frequency around. Usually in voltage and current mode control, the phase movement rolls off around bandwidth (BW). The system may operate unstably if there isn't enough phase margin. Loop stability issues should be cleared in the design stage. Alternatively, Figure 2 shows how D-CAP2 mode control has different phase movement around bandwidth (crossover frequency). The output inductor and capacitor set corner frequency and produce 2 poles in the frequency domain. Around corner frequency, the phase margin drops rapidly if the ceramic capacitor is used as the output filter. The phase will then be boosted around bandwidth by internal zero which is made from the IC's ripple injector block.

 


Figure 2. Gain and Phase Movement of D-CAP2™

Because of additional zero caused by the ripple injector, D-CAP2 easily compares the phase margin in the voltage and current mode control scheme. In some designs, the phase margin should be over a certain degree regardless of phase behavior in the frequency domain.

2 Improve Phase Margin by Visual Interpretation

2.1 Low V_{OUTPUT} and High Duty Cycle Condition

Table 1 shows the phase margin and system bandwidth (f_{bw}) results on the TPS54327 according to input voltage with the fixed $1.05 \cdot V_{OUT}$. The phase margin decreases when V_{IN} is reduced from $12 V_{IN}$ to $5 V_{IN}$. The output capacitor value is $44 \mu F$ and the inductor value is $1.5 \mu H$. The feedforward capacitor is not populated, and the load current is $3 A$.

Table 1. TPS54327 PM and BW Results According to V_{IN} With Fixed $1.05 V_{OUT}$

V_{INPUT} (V_{dc})	Bandwidth (KHz)	Phase Margin (degree)
12	219	31
10	216	28.3
8	216	28.2
6	216.7	26.9
5	216.7	18.9

Figure 3 shows how low V_{OUTPUT} has high system bandwidth over approximately 200 KHz and how the high duty cycle system causes phase drop around bandwidth. Phase drop at high frequency is caused by the IC's on-time delay.

 


Figure 3. Phase Margin of the TPS54327 and Phase Drop Caused by On-Time Delay

When Input voltage is decreased from 12 V_{dc} to 5 V_{dc} with the fixed 1.05- V_{OUT} , the buck converter's duty cycle will increase, resulting in the IC's on-time causing phase delay around bandwidth following transfer function.

$$H_d(s) = e^{-sT_{\text{ON}}/2}$$

 


Figure 4. On-Time Versus Phase Delay of the TPS54327

Figure 4 shows how the Mathcad™ tool can help estimate how much phase delay exists in the system. Figure 4 also shows that the phase drop starts at approximately 50–60 KHz, at 5 V_{in} and 1.05 V_{out} , and gets 15°–20° phase delay at 200 KHz band. Improve delay in the design stage to get substantial phase margin.

2.1.1 Optimize Output Filter in Low V_{OUTPUT} and High Duty Cycle Condition

Previous tests show that a high duty cycle and low output condition, such as 5 V_{in} to 1.05 V_{out} , results in high bandwidth and low phase margin. Reduce bandwidth to avoid a phase drop that is caused by fixed on-time delay in a high frequency range. In D-CAP2 mode control, corner frequency (Fn) is mainly set by the output inductor and capacitor. Bandwidth can be decreased by increasing the L and C output value. However, this decrease may cause poor load transient response by increasing inductor value.

 


Figure 5. Reducing Corner Frequency (Fn) and Bandwidth

Figure 5 shows how the system bandwidth can be reduced by increasing the value of the output inductor and the capacitor value which sets corner frequency.

Table 2. TPS54327 PM and BW Results According to L, C in 5 V_{IN} to 1.05 V_{OUT} Condition

Output L,C	Bandwidth (KHz)	Phase Margin (degree)
1.5 uH, 44 uF (Default)	220 (F _{BW1})	19
2.2 uH, 44 uF	167	29
3.3 uH, 44 uF	153	30
2.2 uH, 66 uF	130	33
4.7 uH, 44 uF	118 (F _{BW2})	35

Table 2 shows that when bandwidth reduces from 220 KHz to 118 KHz by adjusting output L and C, phase margin is increased from 19° to 35°. Load transient response time will increase as the system bandwidth is reduced, and the inductor current will follow load current slowly if inductance is increased. Consider the effects of the time domain even though the system has a substantial phase margin.

2.2 High V_{OUTPUT} Condition

High V_{OUTPUT} conditions is another factor considered that affects the stability characteristic. Unlike in the case of low V_{OUTPUT} , the system will have low bandwidth if the absolute output voltage is increased. Figure 6 compares the system bandwidth between high and low output voltage case and shows the approximate DC gain of D-CAP2.

 


Figure 6. Output Voltage Level Versus Bandwidth

The converter, which has a high output voltage, will have low DC gain and low bandwidth.

Table 3 shows the results of the TPS54327 EVM using a 4.7- μ H output inductor and 44- μ F output capacitor. Input voltage is fixed at 12 V_{dc} .

Table 3. TPS54327 PM and BW Results According to V_{OUT} With Fixed 12 V_{IN}

Output Voltage (Vdc)	Bandwidth (KHz)	Phase Margin (degree)
1.05	133 (F_{BW1})	32
1.8	108	32
2.7	89	31
3.3	81	29.5
5	70 (F_{BW2})	27

Table 3 shows that phase margin also drops when system bandwidth is lower than 80 KHz. This drop means that the TPS54327's internal zero frequency from the ripple injector is higher than the bandwidth, and the phase-boosting effect cannot affect the result. The output filter needs to be redesigned to achieve the phase-boosting effect by internal zero of D-CAP2.

2.2.1 Optimize Output Filter in High V_{OUT} Condition

 


Figure 7. Increasing Corner Frequency (F_n) and Bandwidth

Figure 7 shows how the system bandwidth can be increased by reducing the value of the output inductor and capacitor. Achieve more of a phase-boosting effect by placing system bandwidth greater than internal zero frequency.

Table 4. TPS54327 PM and BW Results According to L, C in 12 V_{IN} to 5 V_{OUT} Condition

Output L,C	Bandwidth (KHz)	Phase Margin (degree)
4.7uH, 66uF	49	23
4.7uH, 44uF	70 (F_{BW2})	27
3.3uH, 44uF	92	33
2.2uH, 44uF	110	33
1.5uH, 44uF	135 (F_{BW1})	33

Table 4 shows the phase margin recovering when bandwidth is increased from a lower range. It can be assumed that the IC's internal zero is located around 90 KHz because that is the point that the phase margin jumps. Optimize system stability by redesigning output filter in high V_{OUT} condition as well.

3 Conclusion

D-CAP2 shows stable behavior in the loop stability but is sometimes faced with meeting specifications required by local systems. The design system must be more robust so that D-CAP2 control schemes can be optimized by the output filter design. By analyzing the IC's on-time and V_{OUT} level and bandwidth, a maximum phase margin can be achieved.

4 References

- Texas Instruments, [D-CAP2™ Frequency Response Model based on frequency domain analysis of Fixed On-Time with Bottom Detection having Ripple Injection Application Report](#)

IMPORTANT NOTICE FOR TI DESIGN INFORMATION AND RESOURCES

Texas Instruments Incorporated ("TI") technical, application or other design advice, services or information, including, but not limited to, reference designs and materials relating to evaluation modules, (collectively, "TI Resources") are intended to assist designers who are developing applications that incorporate TI products; by downloading, accessing or using any particular TI Resource in any way, you (individually or, if you are acting on behalf of a company, your company) agree to use it solely for this purpose and subject to the terms of this Notice.

TI's provision of TI Resources does not expand or otherwise alter TI's applicable published warranties or warranty disclaimers for TI products, and no additional obligations or liabilities arise from TI providing such TI Resources. TI reserves the right to make corrections, enhancements, improvements and other changes to its TI Resources.

You understand and agree that you remain responsible for using your independent analysis, evaluation and judgment in designing your applications and that you have full and exclusive responsibility to assure the safety of your applications and compliance of your applications (and of all TI products used in or for your applications) with all applicable regulations, laws and other applicable requirements. You represent that, with respect to your applications, you have all the necessary expertise to create and implement safeguards that (1) anticipate dangerous consequences of failures, (2) monitor failures and their consequences, and (3) lessen the likelihood of failures that might cause harm and take appropriate actions. You agree that prior to using or distributing any applications that include TI products, you will thoroughly test such applications and the functionality of such TI products as used in such applications. TI has not conducted any testing other than that specifically described in the published documentation for a particular TI Resource.

You are authorized to use, copy and modify any individual TI Resource only in connection with the development of applications that include the TI product(s) identified in such TI Resource. NO OTHER LICENSE, EXPRESS OR IMPLIED, BY ESTOPPEL OR OTHERWISE TO ANY OTHER TI INTELLECTUAL PROPERTY RIGHT, AND NO LICENSE TO ANY TECHNOLOGY OR INTELLECTUAL PROPERTY RIGHT OF TI OR ANY THIRD PARTY IS GRANTED HEREIN, including but not limited to any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information regarding or referencing third-party products or services does not constitute a license to use such products or services, or a warranty or endorsement thereof. Use of TI Resources may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

TI RESOURCES ARE PROVIDED "AS IS" AND WITH ALL FAULTS. TI DISCLAIMS ALL OTHER WARRANTIES OR REPRESENTATIONS, EXPRESS OR IMPLIED, REGARDING TI RESOURCES OR USE THEREOF, INCLUDING BUT NOT LIMITED TO ACCURACY OR COMPLETENESS, TITLE, ANY EPIDEMIC FAILURE WARRANTY AND ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF ANY THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

TI SHALL NOT BE LIABLE FOR AND SHALL NOT DEFEND OR INDEMNIFY YOU AGAINST ANY CLAIM, INCLUDING BUT NOT LIMITED TO ANY INFRINGEMENT CLAIM THAT RELATES TO OR IS BASED ON ANY COMBINATION OF PRODUCTS EVEN IF DESCRIBED IN TI RESOURCES OR OTHERWISE. IN NO EVENT SHALL TI BE LIABLE FOR ANY ACTUAL, DIRECT, SPECIAL, COLLATERAL, INDIRECT, PUNITIVE, INCIDENTAL, CONSEQUENTIAL OR EXEMPLARY DAMAGES IN CONNECTION WITH OR ARISING OUT OF TI RESOURCES OR USE THEREOF, AND REGARDLESS OF WHETHER TI HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.

You agree to fully indemnify TI and its representatives against any damages, costs, losses, and/or liabilities arising out of your non-compliance with the terms and provisions of this Notice.

This Notice applies to TI Resources. Additional terms apply to the use and purchase of certain types of materials, TI products and services. These include; without limitation, TI's standard terms for semiconductor products (<http://www.ti.com/sc/docs/stdterms.htm>), [evaluation modules](#), and [samples](http://www.ti.com/sc/docs/sampterm.htm) (<http://www.ti.com/sc/docs/sampterm.htm>).

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2017, Texas Instruments Incorporated